

# INF4420

## Non-linearity

Spring 2012

Jørgen Andreas Michaelsen (jorgenam@ifi.uio.no)

1 / 18

## Outline

Non-linearity and harmonic distortion

Differential circuits

Feedback

Improving linearity

2 / 18

# Introduction

Linear distortion from filtering (not considered)

Soft non-linearity (expanding, compression)


Hard non-linearity (clipping)

3 / 18
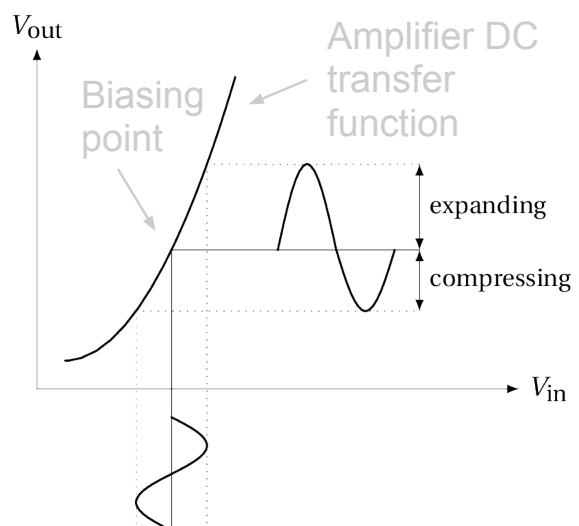
# Introduction

Amplification and  
non-linearity  
depends on the  
biasing point.


Soft non-linearity  
Hard non-linearity  
(clipping)



4 / 18


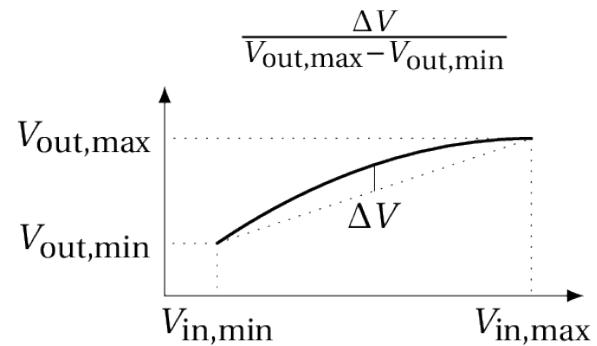
# Introduction

Measure deviation from ideal straight line approximation



5 / 18

# Common source amp

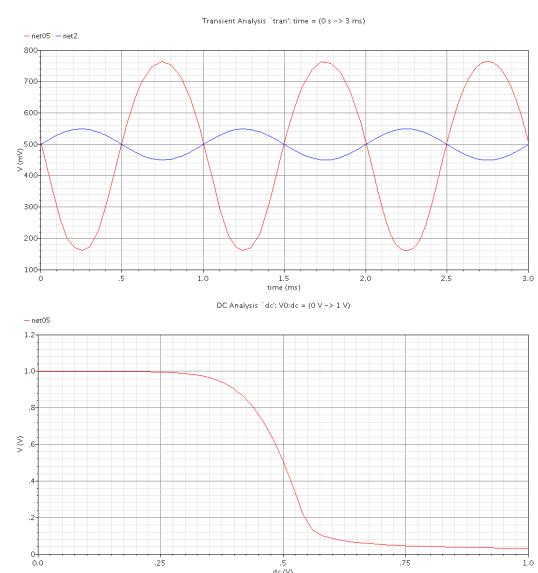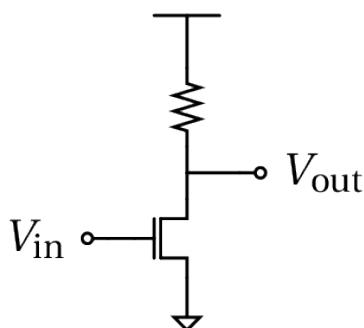

6 / 18

# Taylor series

Using Taylor series allows studying distortion independent of the specific shape of the non-linearity.

Generic expression for total harmonic distortion (THD).

7 / 18

# Taylor series

$$y = \alpha_0 + \alpha_1 x + \alpha_2 x^2 + \alpha_3 x^3 + \dots$$


$$\alpha_0 = f(0)$$

$$\alpha_1 = \frac{df(0)}{dx}$$

$$\alpha_2 = \frac{1}{2} \frac{d^2f(0)}{dx^2}$$

$$\alpha_3 = \frac{1}{6} \frac{d^3f(0)}{dx^3}$$

...

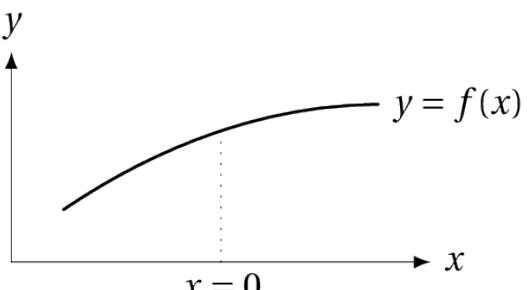

8 / 18

# Harmonic distortion

$$x(t) = A \cos \omega t$$


$$\cos^2 \theta = \frac{1 + \cos 2\theta}{2}$$

$$\cos^3 \theta = \frac{3 \cos \theta + \cos 3\theta}{4}$$

$$\begin{aligned} \Rightarrow y(t) &= \alpha_0 + \alpha_1 A \cos \omega t + \alpha_2 A \cos^2 \omega t + \alpha_3 A^3 \cos^3 \omega t + \dots \\ &= \alpha_0 + \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} [1 + \cos(2\omega t)] + \\ &\quad \frac{\alpha_3 A^3}{4} [3 \cos \omega t + \cos(3\omega t)] + \dots \end{aligned}$$

9 / 18

# Harmonic distortion

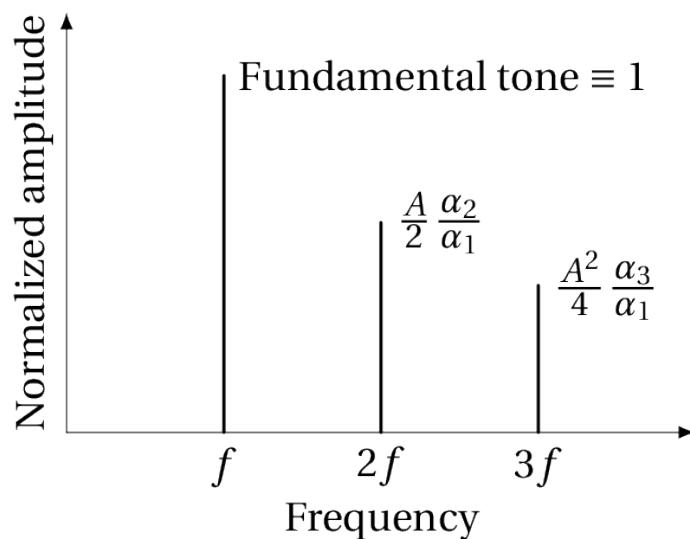

10 / 18

# Harmonic distortion

$$\text{THD} = \frac{\left(\frac{\alpha_2 A^2}{2}\right)^2 + \left(\frac{\alpha_3 A^3}{4}\right)^2}{\left(\alpha_1 A + \frac{3\alpha_1 A}{4}\right)^2}$$
$$\approx \frac{(2A\alpha_2 + A^2\alpha_3)^2}{16\alpha_1^2}$$

11 / 18


# Common source linearity

Large signal current:

$$\frac{\beta}{2}(V_{GS} - V_{TH} + V_m \cos \omega t)^2 =$$
$$\frac{\beta}{2}(V_{GS} - V_{TH})^2 +$$

Input signal
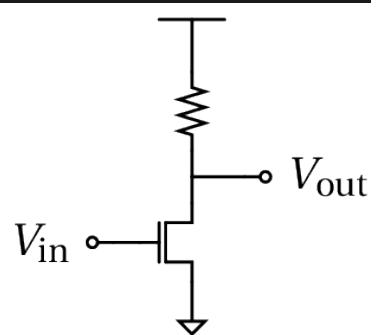
$$\beta(V_{GS} - V_{TH})V_m \cos \omega t +$$
$$\frac{\beta}{4}V_m^2(1 + \cos 2\omega t)$$





Harmonic distortion:

$$\frac{V_m}{4(V_{GS} - V_{TH})}$$

12 / 18

# Differential pair

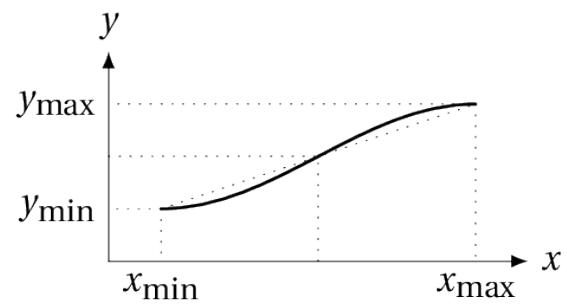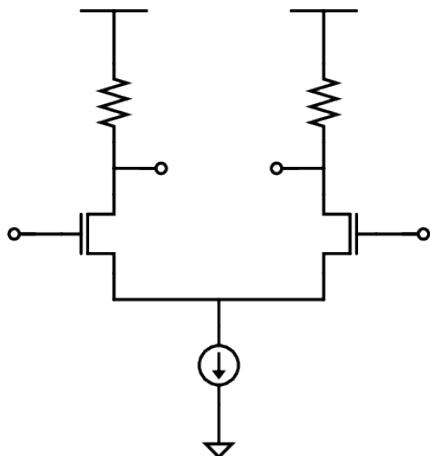

Harmonic distortion:

$$\approx \frac{V_m^2}{32(V_{GS} - V_{TH})^2}$$

13 / 18


# Differential pair

Differential circuits exhibit much less distortion  
(5 % vs 0.125 % for  $V_m = 0.2(V_{GS} - V_{TH})$ )

Linearity is also better when accounting for 2x current.

14 / 18

# Feedback

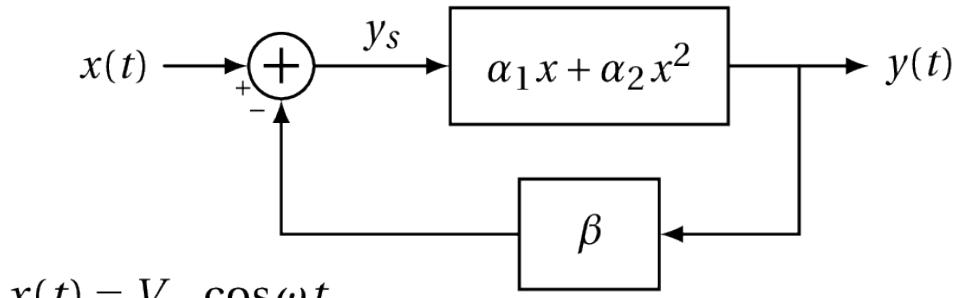



$$x(t) = V_m \cos \omega t$$

$$y(t) \approx a \cos \omega t + b \cos 2\omega t \quad a = \frac{\alpha_1}{1 + \beta \alpha_1} V_m$$

$$\frac{b}{a} = \frac{\alpha_2 V_m}{2} \frac{1}{\alpha_1} \frac{1}{(1 + \beta \alpha_1)^2} \quad b = \frac{\alpha_2 V_m^2}{2} \frac{1}{(1 + \beta \alpha_1)^2}$$

15 / 18


# Resistive degeneration

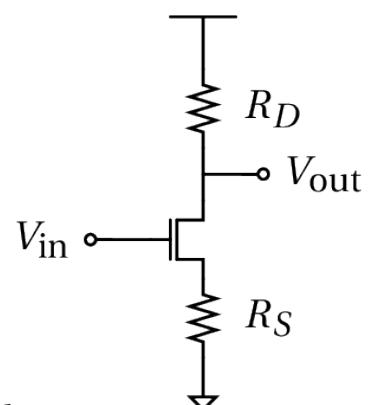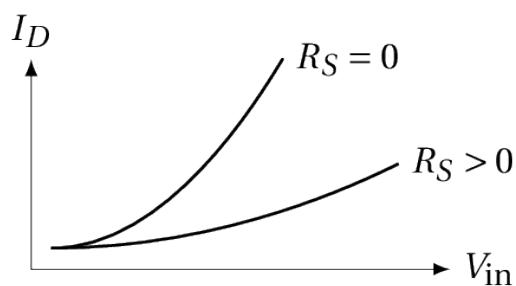

$$G_m = \frac{g_m}{1 + g_m R_S} \approx \frac{1}{R_S}, \quad g_m R_s \gg 1$$

16 / 18

# Resistive degeneration

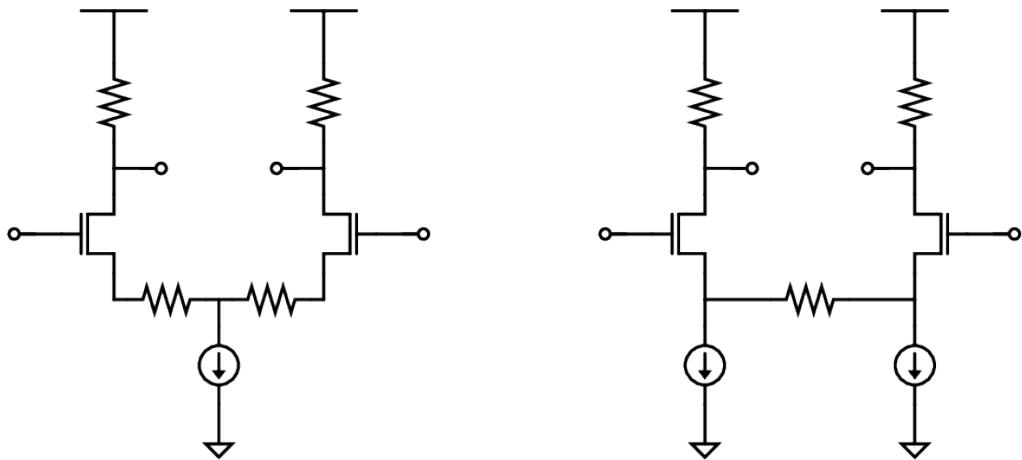



Resistive degeneration also works for diff pairs

17 / 18
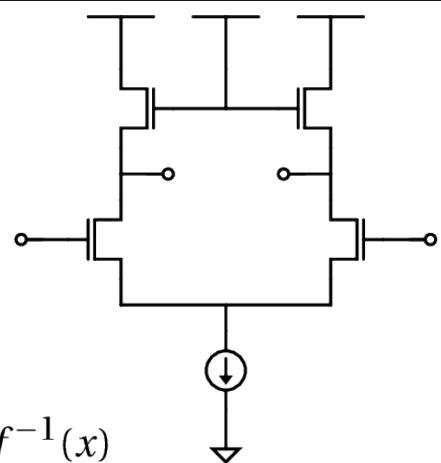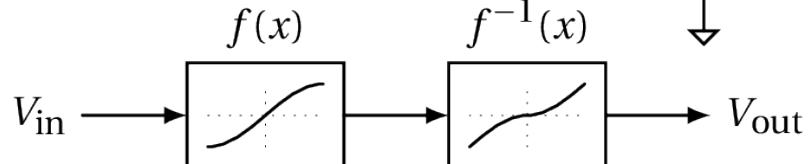
# Post correction

Cascade non-linear stage  
with inverse non-linearity.

Ideally gives overall linear  
transfer function



18 / 18