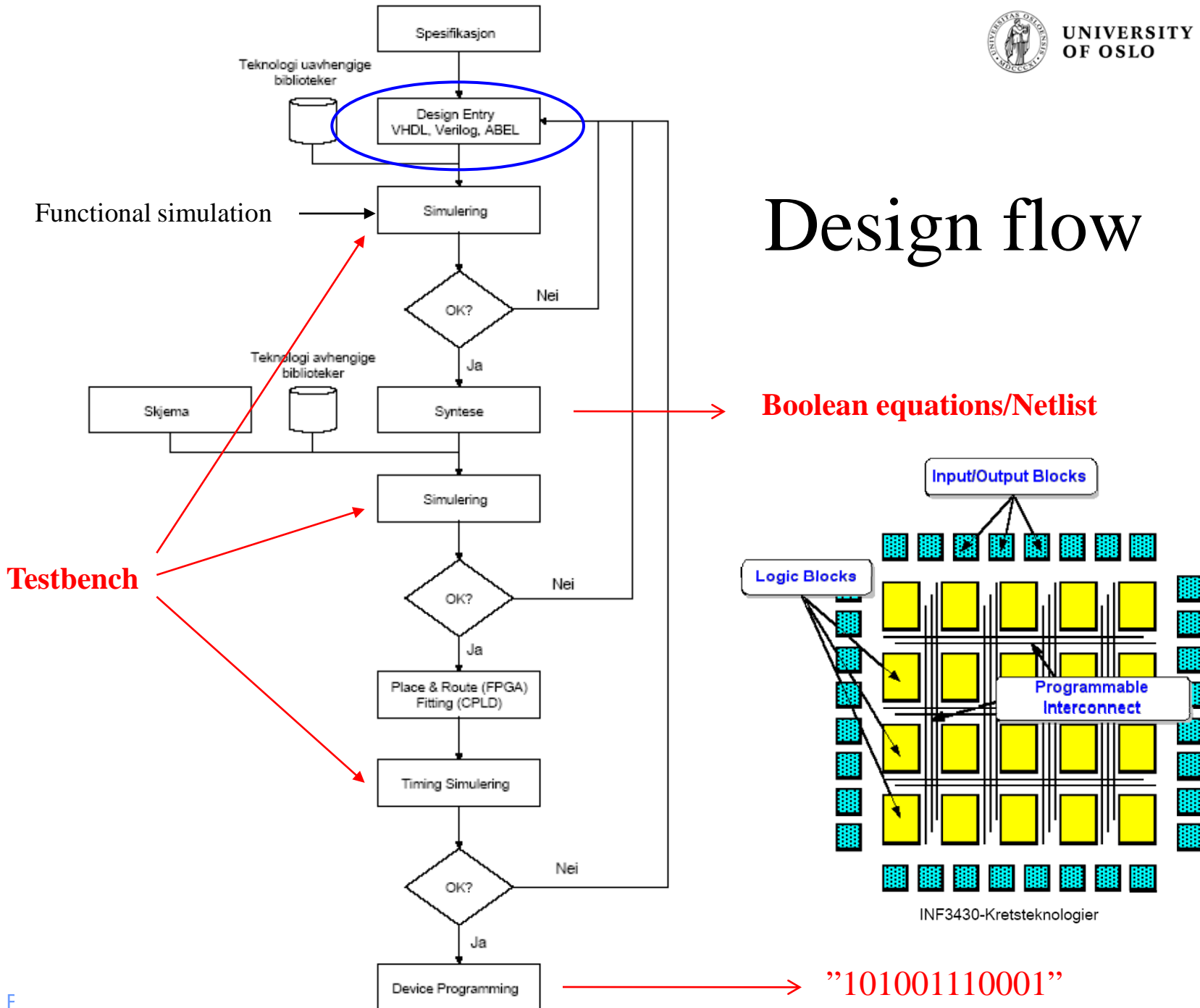



# **Introduction to VHDL**

## **Lecture #2**

# Design flow



# Syntese til design

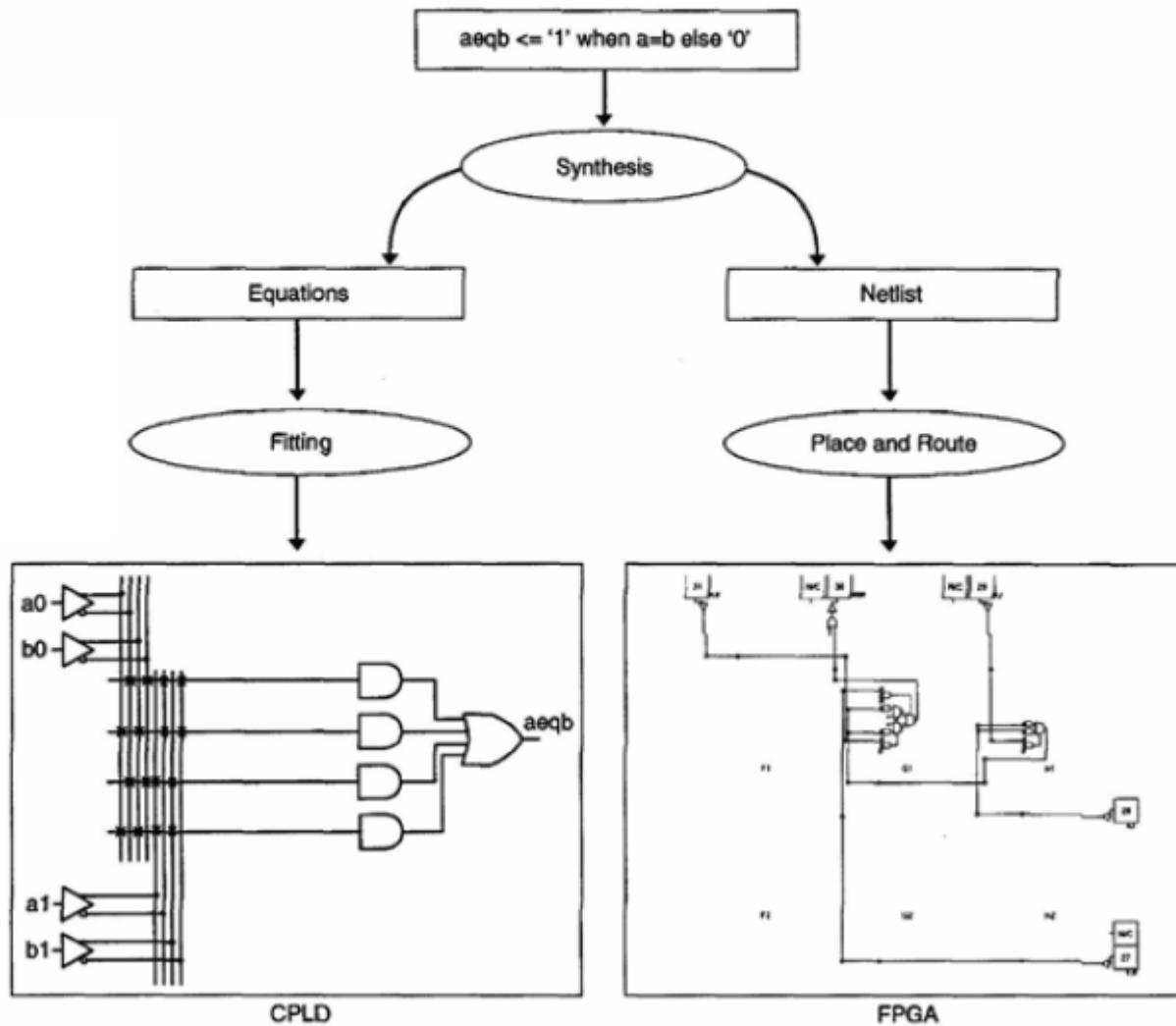

# VHDL



- VHDL = Very high-speed integrated circuit Hardware Description Language
- VHDL is an industry standard for description, modeling and synthesis of digital circuits and systems
- Introduced in 1981 for the Department of Defence (DoD)
- Became an IEEE standard in 1987
- **We will look at VHDL for synthesis of logic**
- **VHDL standards: VHDL 93, 2000, 2002, 2007, 200x**



# Recommended free VHDL editors

## ■ Notepad ++


- <http://notepad-plus.sourceforge.net/uk/site.htm>

## ■ EmacsW32

- <http://ourcomments.org/Emacs/EmacsW32.html>

# First VHDL example

## D-flip-flop

 

```
library ieee;  
use ieee.std_logic_1164.all;
```

File name: **dff\_logic.vhd**

```
entity dff_logic is port (  
    d, clk : in std_logic;  
    q      : out std_logic);  
end dff_logic;
```

entity

**Note: the file  
name must be the  
same as the name  
of the entity!**


```
architecture example of dff_logic is  
begin
```

```
    process (clk) begin  
        if (clk'event and clk = '1') then  
            q <= d;  
        end if;  
    end process;  
end example;
```


architecture
 
# Entities and architectures

- Entity declaration and architecture body



 - Compared with an IC:
  - The **entity** describes the **interface** (the connection pins of the package)
  - The **architecture** describes the **functionality of the entity** (the functionality of the circuit)



# Template - Entity/Architecture

```
entity model_name is
```

```
port
```

```
(
```

```
    list of inputs and outputs
```

```
);
```

```
end model_name;
```

← Same name as the file, e.g. **test.vhd**

```
architecture architecture_name of model_name is
```

```
begin
```

```
    ...
```

```
    VHDL concurrent statements
```

```
    ....
```

```
end architecture_name ;
```

**concurrent = samtidig**



# Comparator

 


Figure 3-1 Schematic symbol equivalent of eqcomp4 entity

-- eqcomp4 is a four bit equality comparator

**entity** eqcomp4 **is**

```
port (a, b : in std_logic_vector(3 downto 0);
```

```
      equals: out std_logic);
```

```
end eqcomp4;
```

**architecture** dataflow **of** eqcomp4 **is**

**begin**

```
    equals <= '1' when (a = b) else '0';
```

```
end dataflow;
```

MSB

[a(3) a(2) a(1) a(0)]  
[b(3) b(2) b(1) b(0)]

<= "settes lik"

# Ports




- Each port must have a **name, direction (mode) and data type**

```
entity add4 is port(  
    a, b:  in std_logic_vector(3 downto 0);  
    ci:    in std_logic;  
    sum:   out std_logic_vector(3 downto 0);  
    co:    out std_logic);  
end add4;
```

name →

mode →

data type →

 

**Figure 3-3** Symbol equivalent of entity add4

# Name




- Names can be constructed using:
  - a b c...z (letters)
  - 0 1..9 (numbers)
  - \_ (underscore)
- With the following reservations:
  - Always start with a letter
  - Can not use VHDL reserved words
  - Last character must be a letter or a number
  - Two following underscores are not allowed
  - Not case sensitive
    - TcK = tck
 
# Direction (mode)



- **In** – flow into the entity
- **Out** – flow out of the entity, no feedback

- **Buffer** - flow out of the entity, feedback allowed
- **Inout** - for bi-directional signals





# Important Data types

- bit, bit\_vector ('1' or '0')
- ieee.std\_logic\_1164:
  - std\_logic ('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-')
  - std\_logic\_vector (e.g. "010101")
- The IEEE library must be made visible by *library* and *use*

for synthesis of logic

```
library ieee;
use ieee.std_logic_1164.all;
entity add4 is port(
    a, b:   in std_logic_vector(3 downto 0);
    ci:     in std_logic;
    sum:    out std_logic_vector(3 downto 0);
    co:     out std_logic);
end add4;
```

# The data type `std_logic 1164`

```
type std_ulogic is ( 'U', -- Uninitialized
                    'X', -- Forcing Unknown
                    '0', -- Forcing 0
                    '1', -- Forcing 1
                    'Z', -- High Impedance ← Three-state
                    'W', -- Weak Unknown
                    'L', -- Weak 0
                    'H', -- Weak 1
                    '-' -- Don't care
                    );
```

**9 different values!**

# Std\_logic 1164 resolution function


The sub type **std\_logic** is "resolved" **std\_ulogic**. When two or more drivers are connected together the value is determined by a "resolution table"

	U	X	0	1	Z	W	L	H	-	
( 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U' ),	--									U
( 'U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' ),	--									X
( 'U', 'X', '0', 'X', '0', '0', '0', '0', '0', 'X' ),	--									0
( 'U', 'X', 'X', '1', '1', '1', '1', '1', '1', 'X' ),	--									1
( 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', 'X' ),	--									Z
( 'U', 'X', '0', '1', 'W', 'W', 'W', 'W', 'X' ),	--									W
( 'U', 'X', '0', '1', 'L', 'W', 'L', 'W', 'X' ),	--									L
( 'U', 'X', '0', '1', 'H', 'W', 'W', 'H', 'X' ),	--									H
( 'U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' )	--									-


 
# Bus



- The resolution function is used to simulate a data bus
- Useful that the simulator can indicate an unknown value if two or more entities write to the same bus line at the same time with opposite logic values.
- **Two entities can not write to a bus line at the same time!**
- **If an entity write to the bus the other entities must be in three-state (high impedance) on their outputs**
- **The unknown value ('X') has no meaning for synthesis!**


  
```
architecture multiply_driven_signal of my_design is  
begin  
  y <= a and b;  
  y <= a or b;  
end multiply_driven_signal;
```



~~$y <= 'X'$~~




# Arithmetic and logical operators


 
## Arithmetic operators:

- + Addition
- - Subtraction
- \* Multiplication
- / Division



**Use with care, creates much logic**

## Logical operators:

- and, nand, or, nor, not, xor, xnor

Example of Hex-number:

X"FA" = "11111010"



# Logical operators

- **and, or, not, nand, nor, xor og xnor** are predefined for **bit** and **boolean**
- IEEE 1164 uses these operators in **std\_logic**
- Logical operators do not have precedence in VHDL, therefore parenthesis is demanded in multi level logic:
  - $A + B \cdot C$  is ok in Boolean algebra due to precedence
  - $X \leq A \text{ or } B \text{ and } C$  gives an error in VHDL
  - $A \text{ or } (B \text{ and } C)$
  - $(A \text{ or } B) \text{ and } C$  } Correct for VHDL

Precedence in Boolean algebra:

()  
not  
and ·  
or +



# Relational operators

- equality =
  - inequality /=
  - Size operators < , <= , > , >=
- The operands must both be of the same type, and the result is a Boolean value (true/false)

---

## Example:

```
signal a : std_logic_vector(7 downto 0);
```

```
.....
```

```
if a = 3 then
```

← Gives an error, because *a* is *std\_logic*, while 3 is an *integer*

# Coding style (Architecture )



## Structural description

```
u1: xor2 port map(a(0), b(0), x(0));  
u2: xor2 port map(a(1), b(1), x(1));  
u3: nor2 port map(x(0), x(1), aeqb);
```

Netlists

```
aeqb <= '1' when a = b else '0';
```

Concurrent statements  
**Dataflow**

## Dataflow

```
aeqb <= (a(0) XOR b(0)) NOR  
        (a(1) XOR b(1));
```

Boolean equations

```
if a = b then aeqb <= '1';  
  else aeqb <= '0';  
end if;
```

Sequential statements  
**Behavioral**

# ”Process”



- The process is executed when one of the signals in the sensitivity list has a change (an event)
- Then, the sequential signal assignments are executed
- The process continues to the last signal assignment, and terminates
- **The signals are updated just before the process terminates!**
- The process is not executed again before one of the signals in the sensitivity list has a new event (change)

```
proc1: process (a, b, c)
  begin
    x <= a and b and c;
  end process;
```

```
process (<sens list>)
  < declaration>
  begin
    <signal assignment1>
    .
    .
    <signal assignment n>
  end process;
```

```
clk: process is -- without sensitivity list
  begin
    clock <= '0';
    wait for 50 ns;
    clock <= '1';
    wait for 50 ns; -- wait needed!
  end process;
```



# Three-state buffers

- The output buffer can be put into a high impedance ('Z') state, such that only one entity writes to the bus
  - Three possible signal levels: '0', '1', 'Z'
- FPGAs and CPLDs have three-state buffers on the outputs (the signals defined as **port** in the entity)
- However, many programmable logic devices can not have three-state buffers internally on the circuit (on internal signals)

# Three-state buffer



```
oes: process (oe, cnt)
begin
  if oe = '0' then
    cnt_out <= (others => 'Z');
  else
    cnt_out <= cnt;
  end if;
end process oes;

end archcnt8;
```


 


Figure 4-17 A three-state buffer

Or:

```
y <= output_signal when output_enable = '1' else 'Z';
```

# 8-bits register

 


```
library ieee;
use ieee.std_logic_1164.all;
entity reg_logic is port (
    d : in std_logic_vector(7 downto 0);
    clk : in std_logic;
    q : out std_logic_vector(7 downto 0)
);
end reg_logic;
architecture r_example of reg_logic is
begin
    process (clk) begin
        if (clk'event and clk = '1') then
            q <= d;
        end if;
    end process;
end r_example;
```

A new value is transferred to the q output on the rising clock edge



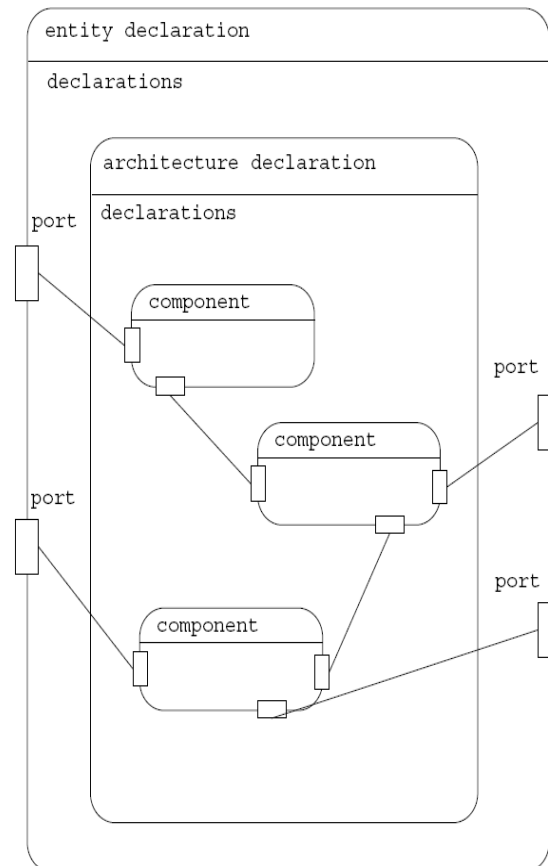
# Component

- A component is an entity that is used in another entity



# Use of components

 

**Fil: dflop.vhd**

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity dflop is port (  
    d, clk : in std_logic;  
    q      : out std_logic);  
end dflop;
```

```
architecture arch_dflop of dflop is  
begin
```

```
    process (clk) begin
```

```
        if (clk'event and clk = '1') then
```

```
            q <= d;
```

```
        end if;
```

```
    end process;
```

```
end arch_dflop;
```

```
entity test_dff is port (  
    async, clock: in std_logic;  
    filt        : out std_logic);  
end test_dff;
```

```
architecture arch_test_dff of test_dff is
```

```
-- Component declaration
```

```
component dflop
```

```
port(  
    d, clk : in  std_logic  
    q      :out std_logic);
```

```
end component;
```

```
-- Declaration of internal signals
```

```
signal temp : std_logic;
```

```
begin
```


```
-- Component instantiation
```

```
u1: dflop port map (async, clock, temp);
```

```
u2: dflop port map (temp, clock, filt);
```

```
end arch_test_dff ;
```

# "Port map"

 

-- Position based  
u2: dflop **port map** (temp, clock, filt);



-- Name based (component name to the left of the arrow)  
u2: dflop **port map** (d => temp, clk => clock, q => filt);

**Can not directly connect together the input/output of a component to another component's output/input! Must use an internal signal (such as temp in this example), unless a connection to a port is made**

U3: navn input output  
port map (a, b, c, **open**, d);

**All inputs to a component must be connected! If an output is not needed, the reserved word **open** can be used**

# Direct Instantiation

- An alternative coding style
- Used in Zwolinski, see e.g. page 42-43, and page 49
- WORK = Current working directory
- No explicit component declaration before they are used (port map).


```
architecture netlist of comb_function is
  signal p, q, r : BIT;
begin
  g1: entity WORK.Not1(ex1) port map (a, p);
  g2: entity WORK.And2(ex1) port map (p, b, q);
  g3: entity WORK.And2(ex1) port map (a, c, r);
  g4: entity WORK.Or2(ex1) port map (q, r, z);
end architecture netlist;
```

Where the model  
is located

The name of  
the model's  
entity


The name of the  
architecture; not need if only  
one architecture is related to  
this entity

# Design flow

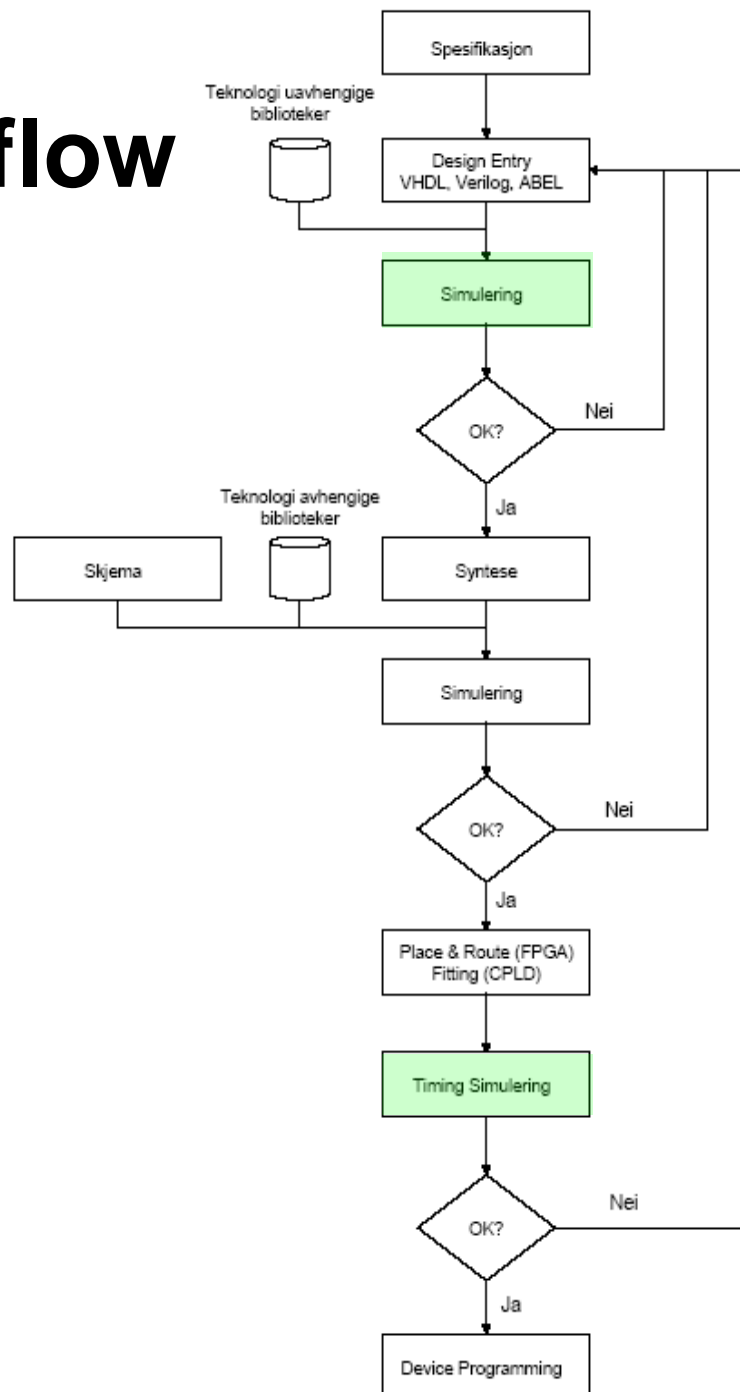




# Test vectors

 

# Test bench

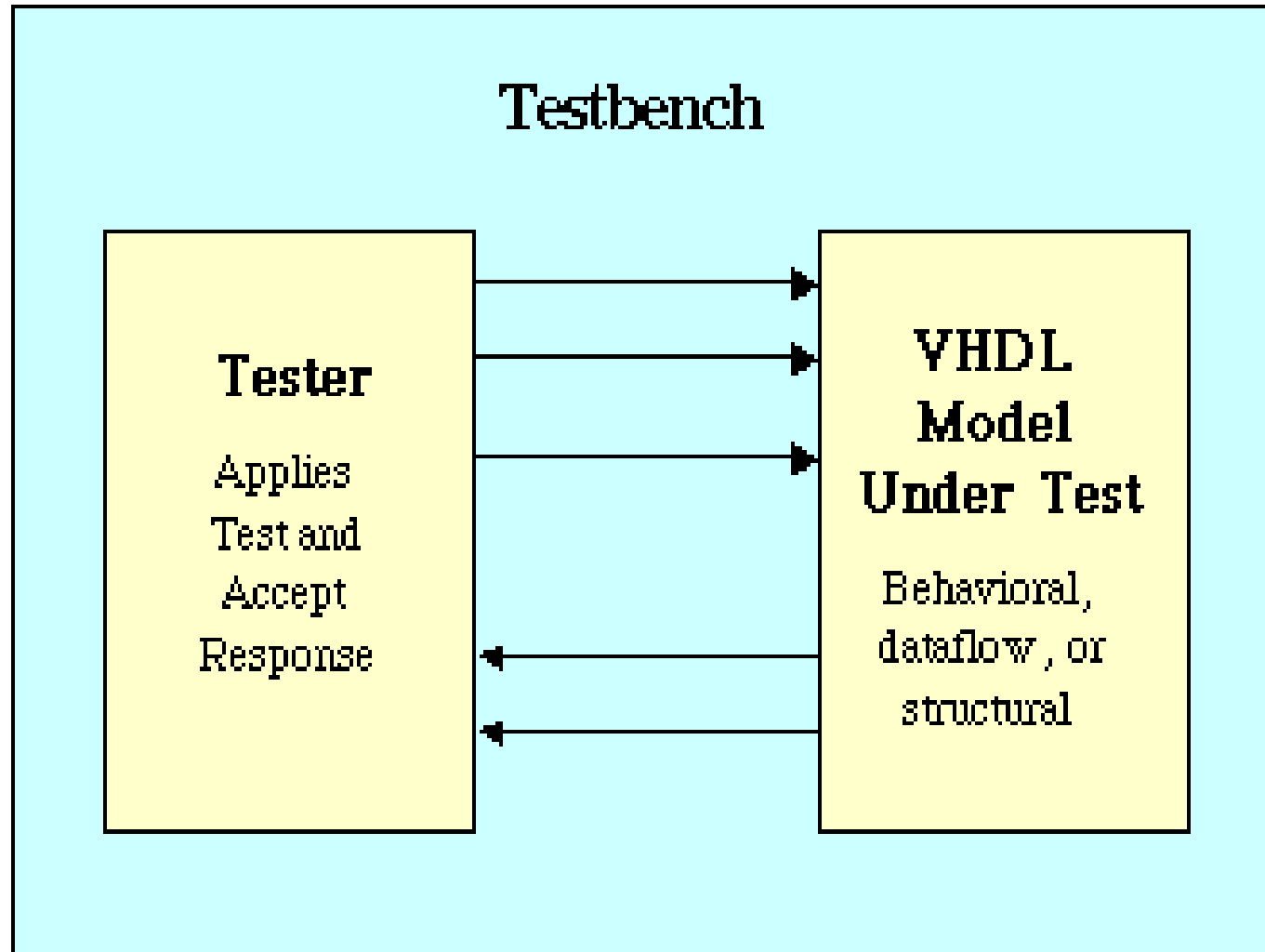



# Test benches

- Add a stimuli (input) to the circuit under test, and observe the outputs to verify correct behavior/functionality
- When a test bench has been made, a functional test can be repeated quickly after a design change
- The same test bench can be used to verify the VHDL-code functionality (RTL level), and to verify the functionality and timing after synthesis and fitting (simulation on post-fit VHDL-model generated by the design tool)
- Test benches are not to be synthesized, and can therefore use the entire VHDL language (e.g. **after**)

```
x <= '1' after 4 ns;
```



# Testbench "template"



```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity test_UUT is    -- empty entity  
end test_UUT
```

(UUT = Unit Under Test)

```
architecture testbenk_arch of test_UUT is
```

```
component UUT:
```

```
port
```

```
(
```

```
.....
```

```
);
```

```
end component;
```

```
signal .....
```

```
signal ..... := '0'; -- start value for inputs
```

```
begin
```

```
U1: UUT
```

```
port map (.....);
```

```
STIMULI:
```

```
process
```

```
begin
```

```
.....
```

```
wait;
```

```
end process;
```

Component declaration

Defines a signal for each port in the UUT

Component instantiation

Add stimuli

# Generating a Test Bench Template from Quartus II



1. If you have not already done so, open an existing project
2. If you have not already done so, perform a full compilation
3. Specify Modelsim-Altera as the simulation tool under **Assignments – EDA tool settings - Simulation**
4. In the Processing menu, point to **Start**, then click **Start Test Bench Template Writer**. The test bench file is written to the location specified as the output directory for the tool you selected. The default is ***/<project directory>/simulation/<EDA simulation tool>***.

# Testbench clock generation

## Clock generation

The most important signal in any design is the clock. In the simplest case, a clock can be generated by inverting its value at a regular interval:

```
clock <= not clock after 10 NS;
```

If clock is of type BIT, the initial value is automatically '0'. If clock is of type std\_logic, an initial value must be assigned at the time of declaration:

```
signal clock : std_logic := '0';
```

If this initialization is not performed, the initial value is 'U', and '**not** 'U'' is also 'U'.

The same effect can be achieved by explicitly assigning values to the clock within a process:

```
clk: process is  
  begin  
    clock <= '0';  
    wait for 10 NS;  
    clock <= '1';  
    wait for 10 NS;  
  end process clk;
```

# Testbench example



```
signal clk : std_logic := '0';
```

```
begin
```

```
clk <= not(clk) after 50 ns;    -- gives a clock period of 100 ns
```

STIMULI:

```
process
```

```
begin
```

```
.....
```

```
reset <= '0', '1' after 100 ns;
```

```
cnt  <= "0000", "1010" after 600 ns;
```

```
.....
```

```
wait; ← A process without a sensitivity list
```

```
end process; must have a wait at the end
```



# A better way to write the testbench stimuli

```
process is  
begin  
  Cin <= '0';  
  A <= "0000";  
  B <= "0000";  
  wait for 5 NS;  
  A <= "1111";  
  wait for 5 NS;  
  Cin <= '1';  
  wait for 5 NS;  
  A <= "0111";  
  wait for 5 NS;  
  B <= "1111";  
  wait for 5 NS;  
  Cin <= '0';  
  wait;  
end process;
```



# Test benches

- Add a stimuli (input) to the circuit under test, using VHDL, and observe the outputs to verify correct behavior/functionality
- Can have a table with test vectors integrated into the test bench or in a separate file
- Test benches are not to be synthesized, and can therefore use the entire VHDL language (e.g. **after**)
- File I/O [Package defined in IEEE 1076: \*\*textio\*\*](#)
  - Read test patterns from file
  - Write results to file and compare manually with an answer file
  - The test bench can also read the answer file such that the test bench can compare the results and the correct answers
- Can build in models for external circuits on the PCB
  - demands correct modeling of the external circuits



# Self-testing test benches

- In a self-testing test bench all outputs are checked against an answer, and the result of the simulation is reported as "Ok" or "Not Ok".
- The advantage is that search in timing diagrams are not needed (saves time)
- Other people can more easily maintain the code
- However, it is a demanding task to make a self-testing test bench!