

# **VHDL – combinational and synchronous logic**

**Lecture #3**



# Combinational vs Sequential logic

- In **combinational logic** the output is only dependent on the present input.
- In **sequential logic** the output is dependent on both the present input and the state (memory, based on earlier inputs).
- Therefore, sequential logic has memory, while combinational logic does not.



# Comparator - Behavioral (I) Style

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 entity eqcomp4 is port(
4     a, b:          in std_logic_vector(3 downto 0);
5     equals:       out std_logic);
6 end eqcomp4;
7
8 architecture behavioral of eqcomp4 is
9 begin
10 comp: process (a, b) ← Sensitivity list
11     begin
12         if a = b then
13             equals <= '1';
14         else
15             equals <= '0';
16         end if;
17     end process comp;
18 end behavioral;
```

Sequential statements

# Comparator - Behavioral (II)



```
1 architecture behavioral of eqcomp4 is
2 begin
3   comp: process (a, b)
4     begin
5       equals <= '0';    -- Default value
6       if a = b then
7         equals <= '1';
8       end if;
9     end process comp;
10  end behavioral;
```

**Note: Signals are set when the process terminates**

- **The order of the statements is important!**
- **Only the last assignment of a signal has any effect!**

# ”Process”



- The process is executed when one of the signals in the sensitivity list has a change (an event)
- Then, the sequential signal assignments are executed
- The process continues to the last signal assignment, and terminates
- **The signals are updated just before the process terminates!**
- The process is not executed again before one of the signals in the sensitivity list has a new event (change)

```
proc1: process (a, b, c)
  begin
    x <= a and b and c;
  end process;
```

```
process (<sens list>)
  < declaration>
begin
  <signal assignment1>
  .
  .
  <signal assignment n>
end process;
```

```
clk: process is -- without sensitivity list
begin
  clock <= '0';
  wait for 50 ns;
  clock <= '1';
  wait for 50 ns; -- wait needed!
end process;
```

# Combinational logic and "process"



- Remember to include all inputs in the sensitivity list!

```
proc4: process (a, b, c)
  begin
    x <= a and b and c;
  end process;
```

# Comparator - Dataflow (I)



- Does not use process!

```
1 -- eqcomp4 is a four bit equality comparator
2 library ieee;
3 use ieee.std_logic_1164.all;
4 entity eqcomp4 is port(
5     a, b:          in std_logic_vector(3 downto 0);
6     equals:       out std_logic);
7 end eqcomp4;
8
9 architecture dataflow of eqcomp4 is
8 begin
9     equals <= '1' when (a = b) else '0';
10 end dataflow
```

} when - else

# Combinational logic

- Does not have memory (only dependent on present input)
- To avoid unwanted memory:
  - Include **else** in if then else
  - Include **when others** in case
  - and/or use **"default"** values

## Gives a circuit with memory:

```
process (ctrl, A)
begin
  if ctrl = '1' then
    Z <= 'A';
  end if;
end process;
```

## Gives a combinational circuit:

```
process (ctrl, A)
begin
  if ctrl = '1' then
    Z <= 'A';
  else
    Z <= '0';
  end if;
end process;
```



# More about unwanted memory

```
process (sel, A, B)
begin
  case sel is
    when "00" => Y <= A;
    when "10" => Y <= B;
  end process;
```

Gives memory, because  
 ”**when others**” or  
 ”**default**” values are  
 missing

```
process (sel, A, B)
begin
  case sel is
    when "00"    => Y <= A;
    when "10"    => Y <= B;
    when others => Y <= '0';
  end process;
```

Equivalent  
descriptions, which  
gives combinational  
logic

```
process (sel, A, B)
begin
  Y <= '0'; ← Default value
  case sel is
    when "00"    => Y <= A;
    when "10"    => Y <= B;
  end process;
```

# Data objects



- **Constants**: increase readability
  - **constant** width: integer := 8;
- **Signals** – a signal line or a memory element
  - **signal** count: std\_logic\_vector (3 **downto** 0);
- **Variables** – synthesis of variables is not well defined
  - **variable** result: std\_logic := '0';
- **Aliases** – not a new object

```
signal address: std_logic_vector(31 downto 0);  
alias top_ad: std_logic_vector(3 downto 0) is address(31 downto 28);  
alias bank: std_logic_vector(3 downto 0) is address(27 downto 24);  
alias row_ad: std_logic_vector(11 downto 0) is address(23 downto 12);
```



# Signals and variables

## Signals:


- Signal assignment  $\leq$
- Defined in architecture (before *begin*)
- Signals are updated just before the process terminates!
- Use signals instead of variables when possible!

## Variable:

- Variable assignment  $:=$
- Variable assignment is instantaneous
- In synthesis they are used as index variables and temporal storage of data
- Can be used to simplify algorithms
- Can be used inside a process
- Must be defined inside a process
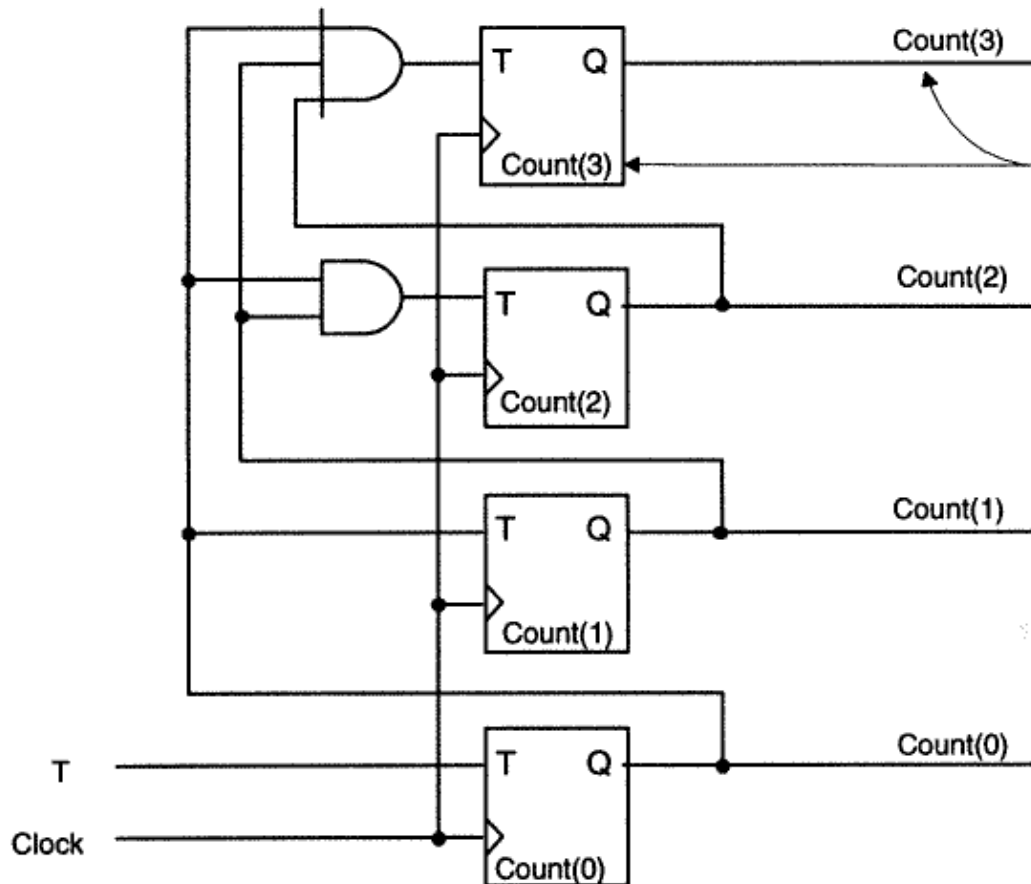
# Signals

signal count: std\_logic\_vector(3 downto 0);




Count(3) refers to the contents of the memory element or the value of the attached wire.

**Figure 3-17** A signal can refer to the memory elements or the wires attached to the outputs of the memory elements
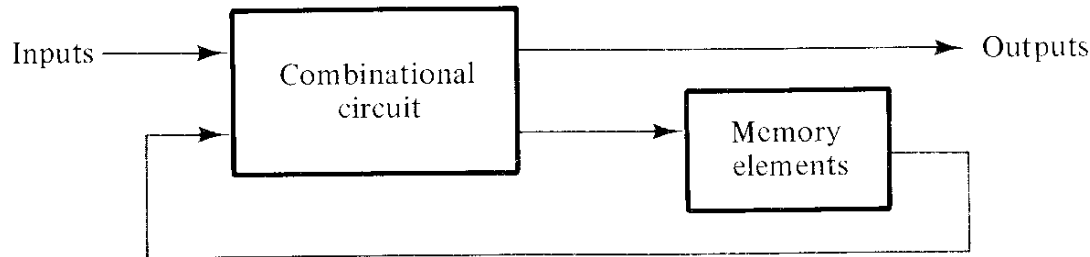
# Sequential and synchronous logic

- Most digital systems have memory elements (e.g. flip-flops) in addition to combinational logic, and is then called **sequential logic**
- The output in a sequential circuit is dependent on both present input and present state (of a memory element)



- Synchronous logic use a clock such that the memory elements are updated only at specific times (at the rising/falling clock edge)



# rising\_edge og falling\_edge


- Defined by the package **std\_logic\_1164**
- The signal must be of the type **std\_logic** in order to use these two functions
- Detects rising/falling edge on the signal

# Only one single test on rising/falling clock edge for each process!

```
FSM : process(clk) IS  
begin
```

```
if (rising_edge(clk1MHz)) then  
    Datin    <= Dout;  
    ncs     <= nCS_control;  
end if;
```
 
```
if(falling_edge(clk1MHz)) then  
    Case present_state is
```



```
library ieee;  
use ieee.std_logic_1164.all;  
entity dff_logic is port (  
    d, clk : in std_logic;  
    q      : out std_logic);  
end dff_logic;
```

```
architecture example of dff_logic is  
begin
```

```
    process (clk) begin  
        if (clk'event and clk = '1') then  
            q <= d;
```

no else; gives implicit  
memory

```
        end if;  
    end process;  
end example;
```


```
if (clk'event and clk = '1') then  
if rising_edge(clk) then
```

-- rising edge

```
if (clk'event and clk = '0') then  
if falling_edge(clk) then
```

-- falling edge

D-flip-flop

 





# Example: 3-bit counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all; -- for + operator
use ieee.std_logic_unsigned.all
.

signal bit_cnt : std_logic_vector(2 downto 0);

.

BITCOUNTER:
process (sclk, reset_sync)
begin
  if (reset_sync = '1') then
    bit_cnt <= (others => '0');
  elsif falling_edge(sclk) then
    bit_cnt <= bit_cnt + 1;
  end if;
end process;
```



# Operator overloading & important functions I

- To add a constant to a signal of type **std\_logic**, an overloaded operator is required (in addition to the native VHDL operators)
  - Solution: Add the package **std\_logic\_arith**
- The expression **if a = "1--1"** is always evaluated to false in native VHDL, except for **"1--1"**
  - Solution: include the package **std\_logic\_arith**, and use the function **std\_match**: **if std\_match(a, "1--1")**
- Overloading of the = operator
  - The expression **a = "00001"** only true if array sizes are equal in native VHDL
  - Solution: Include a package that overloads the = operator, e.g. the **numeric\_std** package



# Operator overloading & important functions II

- The following packages solve most of these problems:

**library IEEE;**

**use IEEE.std\_logic\_1164.all;**

**use IEEE.numeric\_std.all;**

**use IEEE.std\_logic\_arith.all;**

**use IEEE.std\_logic\_unsigned.all;**

- Some other packages:

**math\_real**

**math\_complex**

**std\_logic\_textio**

# Clock divider (using variable)



- Clock division different from  $2^n$
- Wants ~ 50 % clock duty-cycle

library ieee;

use ieee.std\_logic\_1164.all;

use ieee.std\_logic\_arith.all;

use ieee.std\_logic\_unsigned.all;

entity clock12div is

port

(

clk\_in : in std\_logic;

reset : in std\_logic;

clk\_out : out std\_logic

);

end clock12div;

architecture clock\_div\_arch of clock12div is

**constant** DivFactor : integer := 12;

**constant** DivFactor\_half : integer := 6;

begin

CLK\_DIV: process (clk\_in, reset)

**variable** div\_cnt : integer range 0 to DivFactor - 1;

begin

if reset = '1' then -- asynchronous reset

div\_cnt := 0;

clk\_out <= '0';

elsif rising\_edge(clk\_in) then

if (div\_cnt = DivFactor - 1) then

div\_cnt := 0; -- reset the counter

else

div\_cnt := div\_cnt + 1; -- increment the counter

end if;

if (div\_cnt >= DivFactor\_half) then

clk\_out <= '0';

else

clk\_out <= '1';

end if;

end if;

end process CLK\_DIV;

end clock\_div\_arch;

# Some Data types



- Enumeration – important for state machines
  - type state is (idle, preamble, data, error);
- integer
  - variable a: integer range 0 to 255
- Physical - time is only predefined type, not used in synthesis
  - ns, us, ms
- Floating - usually not supported directly in programmable logic

- Integers :  $011_2$  represents  $3_{10}$
- Fixed-point numbers :  $110.01_2$  represents  $6.25_{10}$   
( $2^2 + 2^1 \cdot 2^{-2}$ )  
store  $11001_2 = 25_{10}$  and divide by  $2^2$
- Floating-point numbers :  $(-1)^{\text{sign}} * \text{mantissa} * 2^{\text{exponent}}$

# Sequential statements (if-then-else)



- Used in **process**, functions and procedures

```
if (condition) then
  do something;
else
  do something different;
end if;
```

**Note:** The order of the signal assignments affects the logic which is produced!

```
signal step: std_logic;
signal addr: std_logic_vector(7 downto 0);
.
.
.
```

```
similar1: process (addr)
begin
  step <= '0';
  if addr > x"0F" then
    step <= '1';
  end if;
end process;
```

Functional  
identical  
processes

```
similar2: process (addr)
begin
  if addr > x"0F" then
    step <= '1';
  else
    step <= '0';
  end if;
end process similar2;
```

## Sequential statements

**process**(.....)

```
if (condition) then
  do something;
else
  do something different;
end if;
```

**process**(.....)

```
if (condition) then
  do something;
else
  do something different;
end if;
```

- The order of the sequential statements (in the process) is important!
- If there are multiple processes they are all executed in parallel and concurrent with other "concurrent statements" in the architecture!

## Concurrent statements

`aeqb <= '1' when (a = b) else '0';`

`ceqd <= '1' when (c = d) else '0';`


- "concurrent statements" are used outside "process"
- Executed concurrently (samtidig)
- The order of "concurrent statements" is arbitrary
 
# Important about seq. statem.



architecture careful of dangerous is

```
signal x: bit;  
begin  
p1: process begin  
  wait until clk = '1';  
  x <= '0';  
  y <= '0';  
  if a = b then  
    x <= '1';  
  end if;  
  if x = '1' then  
    y <= '1';  
  end if;  
end process p1;  
end careful;
```



***x is not assigned the new value here!  
The comparison is with the value x  
got the last time the process was  
executed!***

Listing 4-37 A signal in an assignment and as an operand within the same process



# with-select-when : Multiplexer (I)



```
with selection_signal select
  signal_name <= value_a when value_1_of_selection_signal,
                 value_b when value_2_of_selection_signal,
                 value_c when value_3_of_selection_signal, ...
                 value_x when last_value_of_selection_signal;
```


All values of selection signal must be listed using *when*, and they must be "mutually exclusive". This demands use of *when others*

## Example – 4 to 1 multiplexer

```
library ieee;
use ieee.std_logic_1164.all;
entity mux is port(
  a, b, c, d:      in std_logic_vector(3 downto 0);
  s:              in std_logic_vector(1 downto 0);
  x:              out std_logic_vector(3 downto 0));
end mux;
```

```
architecture archmux of mux is
begin
with s select
  x <= a when "00",
      b when "01",
      c when "10",
      d when others; ←
end archmux;
```

 *s* is of the type `std_logic` which has 9 possible values. This gives 81 possibilities for simulation (for synthesis "11" is the only additional value)



# when-else : Multiplexer (II)



```
signal_name <= value_a when condition1 else  
               value_b when condition2 else  
               value_c when condition3 else ...  
               value_x;
```

*signal\_name* is assigned to the first condition which is true (inherent priority)

## Example – 4 to 1 multiplexer

```
library ieee;  
use ieee.std_logic_1164.all;  
entity mux is port(  
    a, b, c, d:      in std_logic_vector(3 downto 0);  
    s:              in std_logic_vector(1 downto 0);  
    x:              out std_logic_vector(3 downto 0));  
end mux;  
  
architecture archmux of mux is  
begin  
    x <= a when (s = "00") else  
        b when (s = "01") else  
        c when (s = "10") else  
        d;  
end archmux;
```

# case-when : Multiplexer (III)



**architecture mux\_arch of mux is**  
**begin**

**process(a, b ,c, d, s)**  
**begin**

**case s is**

**when "00" => x<=a;**

**when "01" => x<=b;**

**when "10" => x<=c;**


**when others=> x<=d;**

**end case;**

**end process;**

**end mux\_arch;**

 **Combinational logic demands that all input signals must be included in the sensitivity list of the process!**



# if-else : Multiplexer (IV)




```
if (condition1) then
  do something;
elsif (condition2) then
  do something different;
else
  do something completely different;
end if;
```
 
## Example : 4-1 multiplexer

```
architecture archmux of mux is
begin
mux4_1: process (a, b, c, d, s)
begin
  if s = "00" then
    x <= a;
  elsif s = "01" then
    x <= b;
  elsif s = "10" then
    x <= c;
  else
    x <= d;
  end if;
end process mux4_1;
end archmux;
```

Combinational logic demands that all input signals must be included in the sensitivity list of the process!



# Loops

## for loop

```
for i in 7 downto 0 loop
    fifo(i) <= (others => '0');
end loop;
```

Loop variable  $i$  automatically  
declared in a *for loop*

## while loop

```
reg_array: process (rst, clk)
    variable i: integer :=0;
begin
    if rst = '1' then
        while i < 7 loop
            fifo(i) <= (others => '0');
            i := i + 1;
        end loop;
    end if;
end process;
```

Declaration and initializing of  
the loop variable  $i$

Increments the loop variable  $i$

# Synchronous reset

architecture `sync_rexample` of `dff_logic` is  
**begin**

```
process (clk) begin
```

```
  if rising_edge(clk) then
```

```
    if (reset = '1') then
```

```
      q <= '0';
```

```
    else
```

```
      q <= d;
```

```
    end if;
```


```
  end if;
```

```
  end process;
```

```
end sync_rexample;
```

Synchronous  
logic

 
← **reset** located  
inside the part of  
the process which  
is synchronous to  
the clock


 
# Reset in synchronous logic; asynchronous reset



```
library ieee;  
use ieee.std_logic_1164.all;  
entity dff_logic is port (  
    d, clk, reset: in std_logic;  
    q           : out std_logic);  
end dff_logic;
```



architecture rexample of dff\_logic is  
begin

```
    process (clk, reset) begin  
        if reset = '1' then  
            q <= '0';  
        elsif rising_edge(clk) then  
            q <= d;  
        end if;  
    end process;
```

end rexample;

reset and preset are used to set the logic in a known state

For preset function:

```
if preset = '1' then  
    q <= '1'
```

# Asynchronous Reset and Preset, synchronous Load




## Example : 8 bit counter


```
library ieee;
use ieee.std_logic_1164.all;
use work.numeric_std.all;
entity cnt8 is port(
    txclk, grst, gpst:    in std_logic;
    enable, load:        in std_logic;
    data:                in unsigned(7 downto 0);
    cnt:                 buffer unsigned(7 downto 0));
end cnt8;
```

```
architecture archcnt8 of cnt8 is
begin
count: process (grst, gpst, txclk)
begin
    if grst = '1' then
        cnt <= (others => '0');
    elsif gpst = '1' then
        cnt <= (others => '1');
    elsif (txclk'event and txclk='1') then
        if load = '1' then
            cnt <= data;
        elsif enable = '1' then
            cnt <= cnt + 1;
        end if;
    end if;
end process count;
end archcnt8;
```

cnt <= (others => '0')

 

cnt <= "00000000";

 

for i in 0 to 7 loop  
 cnt(i) <= '0';  
end loop;

Listing 4-28 A counter with asynchronous reset and preset





# Avoid latches

- Latches are created by "if" statements which are not completely specified.
- A Latch is created when an "else" statement is omitted, when values are not assigned a value, or when the "event" statement is missing.
- To avoid a Latch being developed assign an output for all possible input conditions.
  - Use an "else" statement instead of an "elsif" statement in the final branch of an "if" statement to avoid a latch.
  - Be sure to assign default values for all outputs at the beginning of a process.

```
-- VHDL Latch example  
process (enable, data_in)  
begin  
    if enable = '1' then  
        q <= data_in;  
    end if;  
end process;
```

```
-- VHDL D flip-flop example  
process (clk) begin  
    if (clk'event and clk = '1') then  
        q <= d;  
    end if;  
end process;  
end example;
```

# Coding for Synthesis

- Omit the **wait for XX ns** statement
- Omit the **... after XX ns** statement
- Omit initial values
  - Do not assign signals and variables initial values because initial values are ignored by most synthesis tools. **The functionality of the simulated design may not match the functionality of the synthesized design.** For example, do not use initialization statements like the following: **variable SUM:INTEGER:=0;**
- Make sure that all outputs are defined in all branches of an if statement. If not it can create latches
  - A good way to prevent this is to have default values for all outputs before the *if statements*.

```
similar1: process (addr)
begin
  step <= '0';
  if addr > x"0F" then
    step <= '1';
  end if;
end process;
```