

Summary of FPGA & VHDL

Lecture #6

Jan Kenneth Bekkeng, University of Oslo - Department of Physics



Curriculum (VHDL & FPGA part)

Curriculum (Syllabus) defined by:

■ Lectures

Forelesninger vhdl

Lecture1- Introduction to programmable logic.pdf

Sist endret 3. jul. 2011 21:44

Lecture2 - VHDL introduction v2.pdf

Sist endret 3. sep. 2011 19:58

Lecture3 - VHDL Combinational Sequential Synchron Logic v2.pdf

Sist endret 3. sep. 2011 19:59

Lecture4 - FSMs and Large Designs.pdf

Sist endret 17. jul. 2011 17:53

Lecture5 - Digital Techniques and Embedded Systems.pdf

Sist endret 17. jul. 2011 17:53

~~Radiation effects on space electronics.pdf~~

~~Sist endret 17. jul. 2011 17:53~~

SOPC_EmbeddedSystems_article.pdf

Sist endret 3. jul. 2011 22:26

Lecture6: Summary

■ Laboratory exercises + documentation

Laboppgaver VHDL

FYS9220_Lab4_FPGA.zip

Sist endret 3. jul. 2011 21:50

Lab1_FPGA.zip

Sist endret 3. jul. 2011 21:45


Lab2_FPGA.zip

Sist endret 3. jul. 2011 21:46

Lab3_FPGA.zip

Sist endret 3. jul. 2011 21:46

Design flow

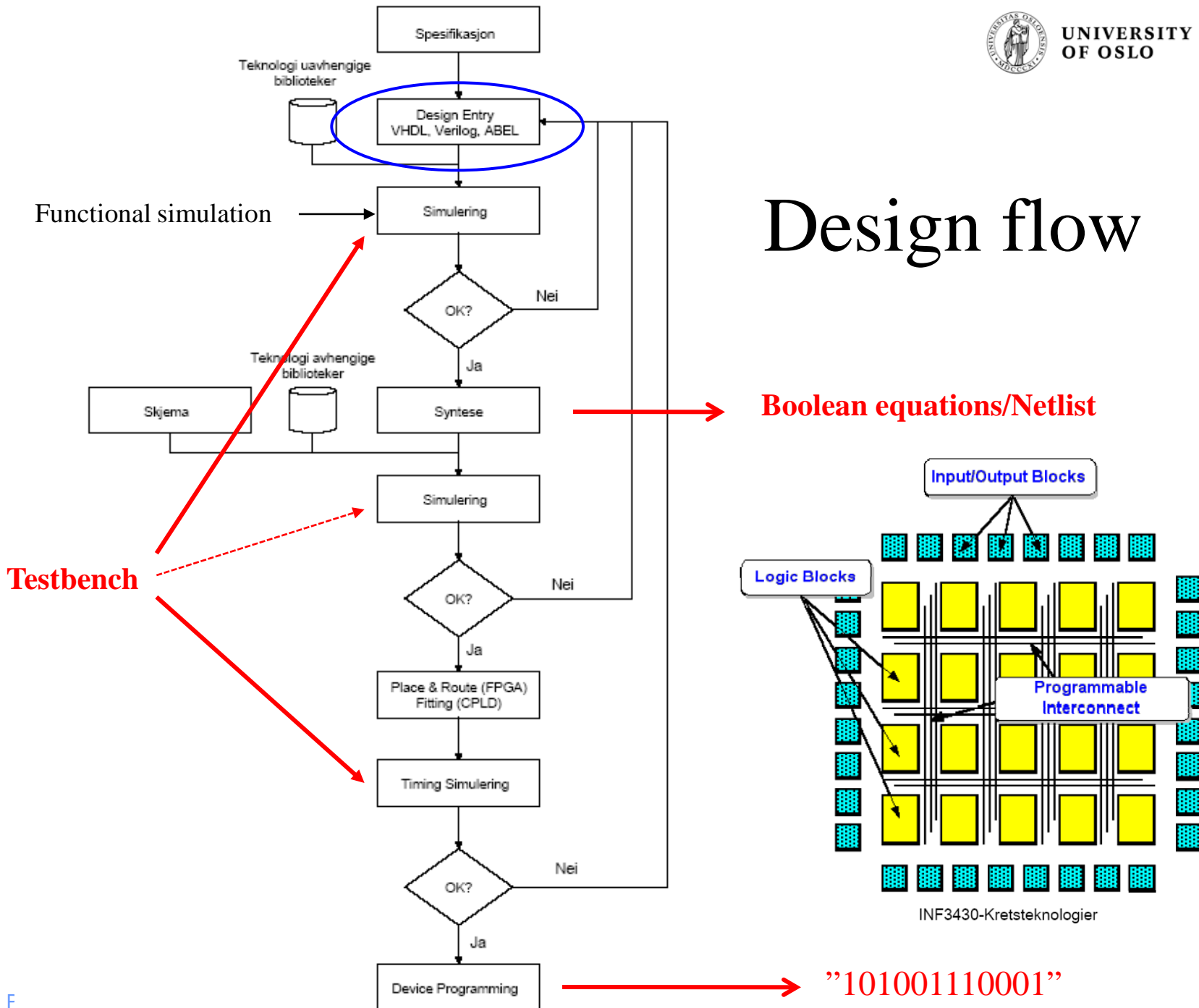



Improved code

```
entity counter_lab2 is
generic(size: integer := 3);
port
(
    clk      : in std_logic;
    enable   : in std_logic;
    reset    : in std_logic;
    c_out    : out std_logic_vector(size-1 downto 0)
);
end counter_lab2;

architecture counter_ARCH of counter_lab2 is
signal count      : std_logic_vector(size-1 downto 0) := (others => '0');
begin

process(clk)
|
begin

    if rising_edge(clk) then

        if(reset = '1') then
            count <= (others => '0');

        elsif(enable='1') then
            count <=count + 1;

        else
            count      <=count;

        end if;

        c_out <= count;

    end if;

end process;

end counter_ARCH;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

-- counter lab2

ENTITY counter_lab2 IS
PORT (
Clock : in std_logic;
Enable : in std_logic;
Reset : in std_logic;
C_out : buffer std_logic_vector(2 downto 0)
);
END counter_lab2;

ARCHITECTURE lab2_part1 OF counter_lab2 IS
BEGIN

process(Clock)
begin
    if rising_edge(Clock) then
        if (Reset = '1') then
            C_out <= (others => '0');
        else
            if (Enable = '1') then
                C_out <= C_out + 1;
            end if;

            -- else not needed ; implicit memory

        end if;
    end if;
end process;
END lab2_part1;
```

Coding for Synthesis


- Omit the **wait for XX ns** statement
- Omit the **... after XX ns** statement
- Omit initial values
 - Do not assign signals and variables initial values because initial values are ignored by most synthesis tools. **The functionality of the simulated design may not match the functionality of the synthesized design.** For example, do not use initialization statements like the following: **variable SUM:INTEGER:=0;**
- Make sure that all outputs are defined in all branches of an if statement. If not it can create latches
 - A good way to prevent this is to have default values for all outputs before the *if statements*.

```
similar1: process (addr)
begin
  step <= '0';
  if addr > x"0F" then
    step <= '1';
  end if;
end process;
```

Common VHDL coding "errors"

- Missing indent (low readability of the code)
- Wrong sensitivity list
 - Too many/too few signals listed
 - Can create wrong behavior, e.g. in state machines, resulting in needless calls of the process or wrong VHDL description of the implemented circuit
- A mix of 1 process and 2 process FSM
- Declaration of unnecessary internal signals
- ASM chart different (e.g. simplified) compared to the VHDL code
 - The ASM chart is the documentation of your VHDL code, and must show all the states, the correct state transitions and the decisions (based on inputs).
 - Outputs can be given in the ASM chart and/or in a state-output table (e.g. give the most important outputs in the ASM chart to ensure correct coding)
 
```
process(Clock)
begin
  if rising_edge(Clock) then
    if (Reset = '1') then
      C_out <= (others => '0');
    else
      if (Enable = '1') then
        C_out <= C_out + 1;
      end if;
    end if;
  end if;
end if;
```





Avoid latches


- Latches are created by "if" statements which are not completely specified.
- A Latch is created when an "else" statement is omitted, when values are not assigned a value, or when the "event" statement is missing.
- To avoid a Latch being developed assign an output for all possible input conditions.
 - Use an "else" statement instead of an "elsif" statement in the final branch of an "if" statement to avoid a latch.
 - Be sure to assign default values for all outputs at the beginning of a process.

```
-- VHDL Latch example  
process (enable, data_in)  
begin  
    if enable = '1' then  
        q <= data_in;  
    end if;  
end process;
```

```
-- VHDL D flip-flop example  
process (clk) begin  
    if (clk'event and clk = '1') then  
        q <= d;  
    end if;  
end process;  
end example;
```

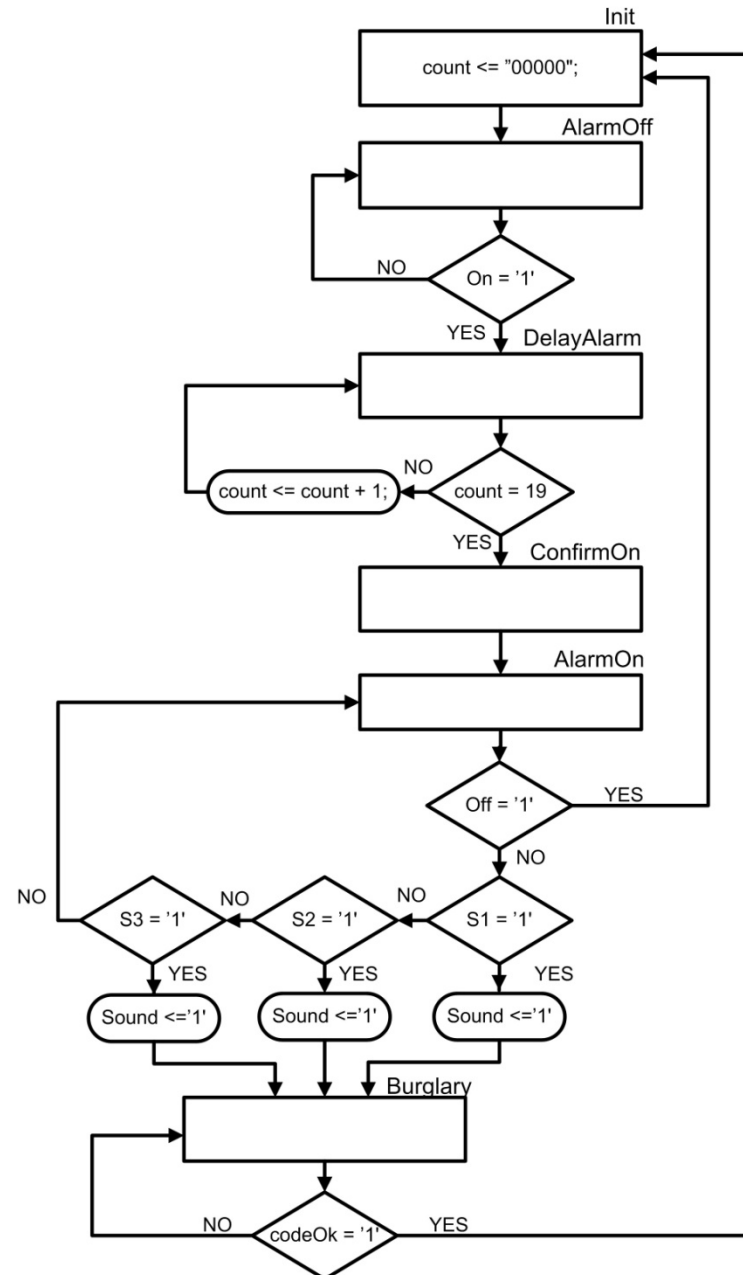
Example of a good ASM chart:

- Yes/No (1/0) labels together with decision boxes
- Arrows to show the program flow
- State names in top right corner of the state boxes
- Selected outputs listed in conditional output boxes and inside the state boxes



State flow diagram and output tabell

Tilstandsdiagram

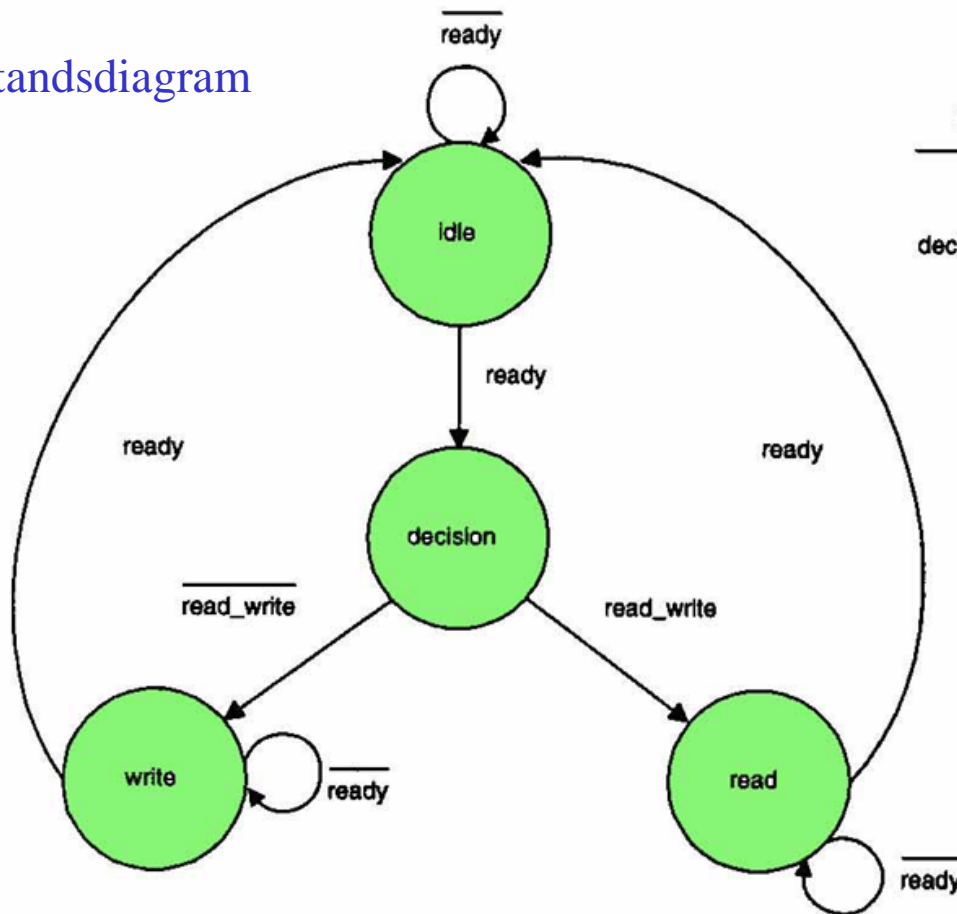

Output tabell

State	Outputs	
	oe	we
idle	0	0
decision	0	0
write	0	1
read	1	0


$ready = '1'$

$\overline{ready} = '0'$

Figure 5-1 Simple state machine

State machines in VHDL

 - An ASM chart (or a state diagram) can easily be translated to a VHDL description!
- In VHDL the state machine can be described in two different ways:
 - 1-process FSM ← **Recommended!**
 - 2-process FSM
 - One process describes the combinational logic, and another describes synchronization of state transitions to the clock



Example: 2 process FSM



```
library ieee;
use ieee.std_logic_1164.all;
entity memory_controller is port (
    reset, read_write, ready, burst, clk    : in std_logic;
    bus_id                                  : in std_logic_vector(7 downto 0);
    oe, we                                   : out std_logic;
    addr                                     : out std_logic_vector(1 downto 0));
end memory_controller;

architecture state_machine of memory_controller is
    type StateType is (idle, decision, read1, read2, read3, read4, write);
    signal present_state, next_state : StateType;
begin
    state_comb:process(reset, bus_id, present_state, burst, read_write, ready) begin
        if (reset = '1') then
            oe <= '-'; we <= '-'; addr <= "--";
            next_state <= idle;
        else
            case present_state is
                ...
            end case;
        end if;
    end process state_comb;

    state_clocked:process(clk) begin
        if rising_edge(clk) then
            present_state <= next_state;
        end if;
    end process state_clocked;
end;
```

Combinational
logic

Synchronous
logic



Asynchronous reset in 2-process FSM

```
state_clocked:process(clk,reset) begin
  if reset= '1' then
    present_state <= idle;
  elsif rising_edge(clk) then
    present_state <= next_state;
  end if;
end process state_clocked;
```



1-process FSM

Functionally identical to the 2-process FSM, and the same logic is produced

```
architecture state_machine of memory_controller is
    type StateType is (idle, decision, read1, read2, read3, read4, write);
    signal state : StateType;
begin
    state_tr:process(reset, clk) begin
        -- one process fsm
        -- asynchronous reset
        if reset = '1' then
            state <= idle;
        elsif rising_edge(clk) then
            -- synchronization to clk
            -- state transitions defined
            case state is
                when idle =>
                    if (bus_id = "11110011") then
                        state <= decision;
                    else
                        -- not req'd; for clarity
                        state <= idle;
                    end if;
                when decision=>
                    if (read_write = '1') then
                        state <= read1;
                    else
                        --read_write='0'
                        state <= write;
                    end if;
            end case;
        end if;
    end process;
end architecture;
```

FSM with 3 undefined states

```
type states is (s0, s1, s2, s3, s4, u1, u2, u3);  
signal next_state, present_state: states;  
...  
case present_state is  
    ...  
    when others => next_state <= s0;  
end case;
```

Output from a state machine



1)

```
FSM: process (reset, clk)
begin
  if (reset = '1') then
    state <= idle;

  elsif rising_edge (clk) then
    case state is
      when idle =>
        oe <= '1';
        if (input1 = '1') then
          state <= s1;
        else
          state <= idle;
        end if;
      when s1 =>
        oe <= '0';

        .....
```

2)

Recommended!

↓

```
FSM: process (reset, clk)
begin
  if (reset = '1') then
    state <= idle;

  elsif rising_edge (clk) then
    oe <= '1'; -- Default value
    case state is
      when idle =>
        if (input1 = '1') then
          state <= s1;
        else
          state <= idle;
        end if;
      when s1 =>
        oe <= '0';

        .....
```

3)

```
FSM: process (reset, clk)
begin
  if (reset = '1') then
    state <= idle;

  elsif rising_edge (clk) then
    case state is
      when idle =>
        if (input1 = '1') then
          state <= s1;
        else
          state <= idle;
        end if;
      when s1 =>
        .....
```

end process;

with state select

```
  oe <= '1' when idle,
    '0' when S1;
end state_machine;
```



Example: Use of default values in FSMs

```
FSM_CONF_READ:
process(clk)
begin
    if falling_edge(clk) then
        .....
        -- set default values
        cs          <= '0' ;
        sr_enable <= '0' ;
        DataReady <= '0' ;
        Din        <= '0' ;

        case state is
        .....
        when PowerUp =>
```


- The width of a signal can be specified using a parameter
- Useful for **registers** and **counters** with different number of bits; only necessary to make one component

Entity using a generic

```
entity SR_SerIn_redge is
  generic (
    width : integer := 16);

  port
  (
    clk      : in  std_logic;
    DataIn   : in  std_logic;
    shift_en : in  std_logic;
    DataOut  : out std_logic_vector(width-1 downto 0)
  );
end SR_SerIn_redge;
```

How to use this component with a generic

```
component SR_SerIn_redge
  generic (width : integer);

  port
  (
    clk      : in  std_logic;
    DataIn   : in  std_logic;
    shift_en : in  std_logic;
    DataOut  : out std_logic_vector(width-1 downto 0)
  );
end component;

SR_DATA: SR_SerIn_redge
  generic map (
    width => 12)

  port map (sclk, Dout, sr_enable, Pdata );
```



The data type `std_logic` 1164

```
type std_ulogic is ( 'U', -- Uninitialized
                    'X', -- Forcing Unknown
                    '0', -- Forcing 0
                    '1', -- Forcing 1
                    'Z', -- High Impedance
                    'W', -- Weak Unknown
                    'L', -- Weak 0
                    'H', -- Weak 1
                    '-' -- Don't care
                    );
```

9 different values!

”Process”



- The process is executed when one of the signals in the sensitivity list has a change (an event)
- Then, the sequential signal assignments are executed
- The process continues to the last signal assignment, and terminates
- **The signals are updated just before the process terminates!**
- The process is not executed again before one of the signals in the sensitivity list has a new event (change)

```
proc1: process (a, b, c)
  begin
    x <= a and b and c;
  end process;
```

```
process (<sens list>)
  < declaration>
  begin
    <signal assignment1>
    .
    .
    <signal assignment n>
  end process;
```

Sequential statements

process(.....)

```
if (condition) then
  do something;
else
  do something different;
end if;
```

process(.....)

```
if (condition) then
  do something;
else
  do something different;
end if;
```

- The order of the sequential statements (in the process) is important!
- If there are multiple processes they are all executed in parallel and concurrent with other "concurrent statements" in the architecture!

Concurrent statements

`aeqb <= '1' when (a = b) else '0';`

`ceqd <= '1' when (c = d) else '0';`

- "concurrent statements" are used outside "process"
- Executed concurrently (samtidig)
- The order of "concurrent statements" is arbitrary



Signals and variables

Signals:

- Signal assignment \leq
- Defined in architecture (before *begin*)
- Signals are updated just before the process terminates!
- **Use signals instead of variables when possible!**

Variable:


- Variable assignment $:=$
- Variable assignment is instantaneous
- In synthesis they are used as index variables and temporal storage of data
- Can be used to simplify algorithms
- Can be used inside a process
- Must be defined inside a process

Important - signal assignment



architecture careful of dangerous is
 
```
signal x: bit;  
begin  
p1: process begin  
  wait until clk = '1';  
  x <= '0';  
  y <= '0';  
  if a = b then  
    x <= '1';  
  end if;  
  if x = '1' then  
    y <= '1';  
  end if;  
end process p1;  
end careful;
```



***x is not assigned the new value here!
The comparison is with the value x
got the last time the process was
executed!***

Listing 4-37 A signal in an assignment and as an operand within the same process



Building blocks

■ Library

- library IEEE
- use IEEE.std_logic_1164.all;

} To make the library visible

■ Packages

- use work.my_package.all; -- your own package
- **work** is the directory where the design files are located

■ Components

- An entity used in another entity
- Needs a component declaration to make the component visible
- Needs a component instantiation to connect the component to the top entity – using *port map()*



Operator overloading & important functions

- Understand the need and use of the following packages:


```
use IEEE.std_logic_1164.all;
```

```
use IEEE.numeric_std.all;
```

```
use IEEE.std_logic_arith.all;
```


FPGA advantages

 - High reliability
 - High determinism
 - High performance
 - True parallelism
 - Reconfigurability
-
- Scalability
 - System integration (System On a Programmable Chip)




Levels of Design Abstractions

<i>Design Levels</i>	<i>Design Descriptions</i>	<i>Primitive Components</i>	<i>Theoretical Techniques</i>
Algorithmic	Specifications High-level lang. Math. equations	Functional blocks 'black boxes'	Signal processing theory Control theory Sorting algorithm
Functional	VHDL, Verilog FSM language C/Pascal	Registers Counters ALU	Automata theory Timing analysis
Logic	Boolean equations Truth tables Timing diagrams	Logic gates Flip-flops	Boolean algebra K-map Boolean minimization
Circuit	Circuit equations Transistor netlist	Transistors Passive comp.	Linear/non-linear eq. Fourier analysis

The difference between a processor and programmable logic

 - A processor is programmed with *instructions*
- A programmable logic circuit is programmed with *a circuit description*
- A programmable logic circuit contains configurable blocks with logics and configurable connection lines between these blocks





CPLD - Complex Programmable Logic Device


- Programming technology: non-volatile memory, such as EEPROM or FLASH.
 - Configuration stored in the circuit (even without power)
 - High voltage (EEPROM) or logic voltage (FLASH)
- Used in "small and medium size" designs

FPGA - Field Programmable Gate Array



- Typically contains more logic than a CPLD
- Have many flip-flops (memory elements)
- Usually have on-chip memory (RAM)
- Supports processor cores, IPs etc


FPGA

 

Flash



 - Programming technology: usually static memory (SRAM)
 - Needs an external configuration circuit with a non-volatile memory (based on EEPROM/FLASH) which loads the configuration into the FPGA at power on.
 - SRAM memory inside the FPGA stores the circuit configuration (when the power is on).







Combinational vs. Sequential logic, and synchronous logic



- In **combinational logic** the output is only dependent on the present input.
- In **sequential logic** the output is dependent on both the present input and the state (memory, based on earlier inputs).
- Synchronous logic use a clock such that the memory elements are updated only at specific times (at the rising/falling clock edge)

Block diagrams

 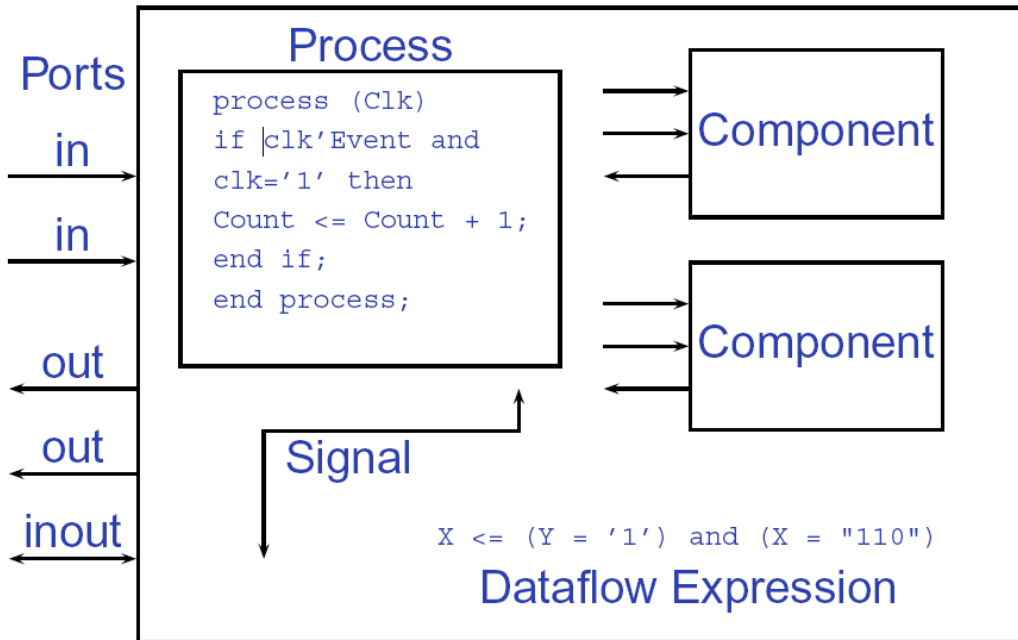

Why focus on Verification

  Consider a) FPGA development and
b) Further work related to FPGA quality



Average Design & Functional
Verification tasks
- as seen in some reasonably
structured projects.



Test benches

- Add a stimuli (input) to the circuit under test, using VHDL, and observe the outputs to verify correct behavior/functionality
- Can have a table with test vectors integrated into the test bench or in a separate file
- Test benches are not to be synthesized, and can therefore use the entire VHDL language (e.g. **after**)
- File I/O [Package defined in IEEE 1076: **textio**](#)
 - Read test patterns from file
 - Write results to file and compare manually with an answer file
 - The test bench can also read the answer file such that the test bench can compare the results and the correct answers
- Can build in models for external circuits on the PCB
 - demands correct modeling of the external circuits



Testbench example

```
signal clk : std_logic := '0';
```

```
begin
```

```
clk <= not(clk) after 50 ns; -- gives a clock period of 100 ns
```

```
process is
```

```
begin
```

```
  Cin <= '0';
```

```
  A <= "0000";
```

```
  B <= "0000";
```

```
  wait for 5 NS;
```

```
  A <= "1111";
```

```
  wait for 5 NS;
```

```
  Cin <= '1';
```

```
  wait for 5 NS;
```

```
  A <= "0111";
```

```
  wait for 5 NS;
```

```
  B <= "1111";
```

```
  wait for 5 NS;
```

```
  Cin <= '0';
```

```
  wait;
```

```
end process;
```