 



# Programmable logic

- Logic gates, multiplexers, flip-flops
- Programmable logic devices
  - PROM, PLA, PAL, GAL, CPLD, FPGA
- Look-up Table (LUT)



 
# The Basic Logic Gates


These three gates are logical sufficient to express any boolean operation!



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


A	Y
0	1
1	0


**NAND**

 


**NOR**

 

**XOR**

 

**XNOR**

 

# Apollo Guidance Computer

 


Image credit: NASA

Sources:

<http://history.nasa.gov/computers/Ch2-5.html>


[https://en.wikipedia.org/wiki/Apollo\\_Guidance\\_Computer](https://en.wikipedia.org/wiki/Apollo_Guidance_Computer)

<https://history.nasa.gov/computers/Ch2-5.html>

<http://www.ibiblio.org/apollo/>


<https://newatlas.com/apollo-11-guidance-computer/59766/>

# Multiplexer


 


$$Y = AS + B\bar{S}$$

A	B	S	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



 


# D flip-flop

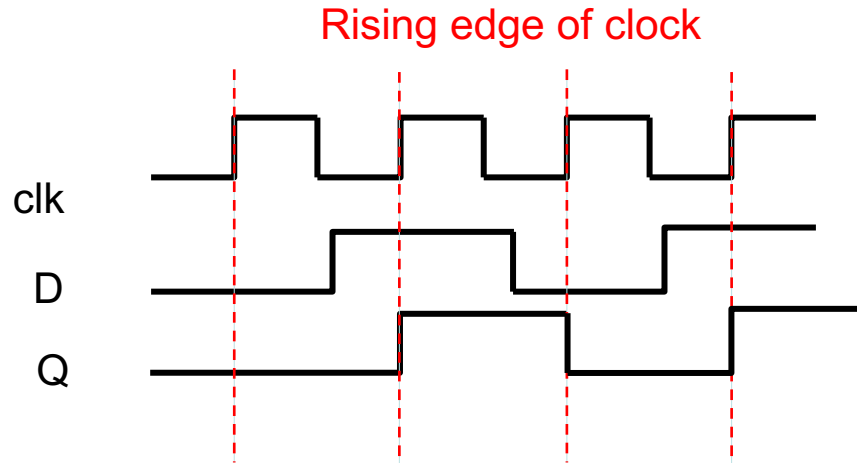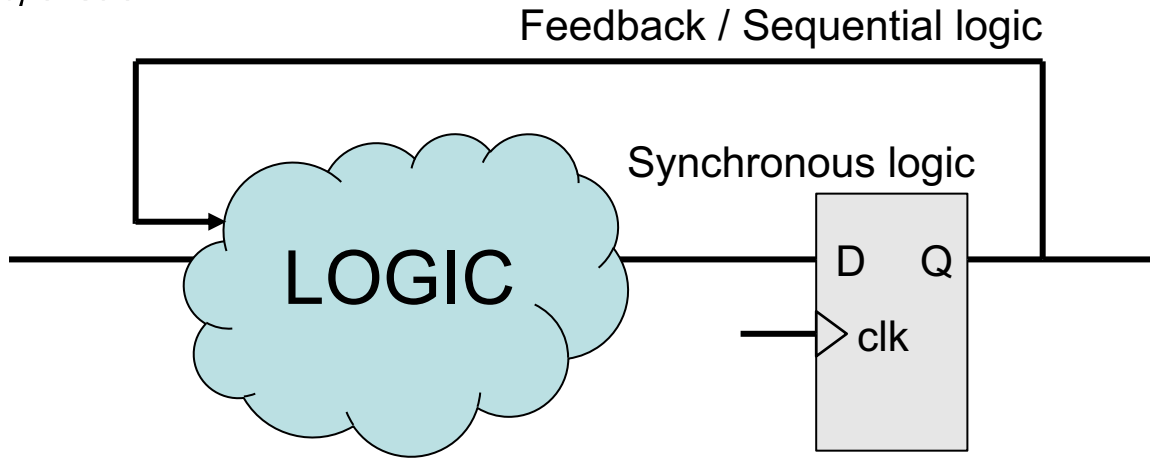


- Standard transistor-transistor logic (TTL) integrated circuits (mid 1960s)
- 100's of devices, ready for use, that provide e.g.
  - basic logic gates
  - Flip-flops & memory
  - Counters
  - Arithmetic Logic Units (ALU)
- "Programmability": wires!
- Glue logic in computers and industrial electronics

# Integrated Circuits

   
 
# Programmable Logic Devices (PLD)



- PROM: Programmable Read Only Memory
- PLA: Programmable Logic Array
- PAL: Programmable Array Logic
  
- GAL: Generic Array Logic







- First simple PLD

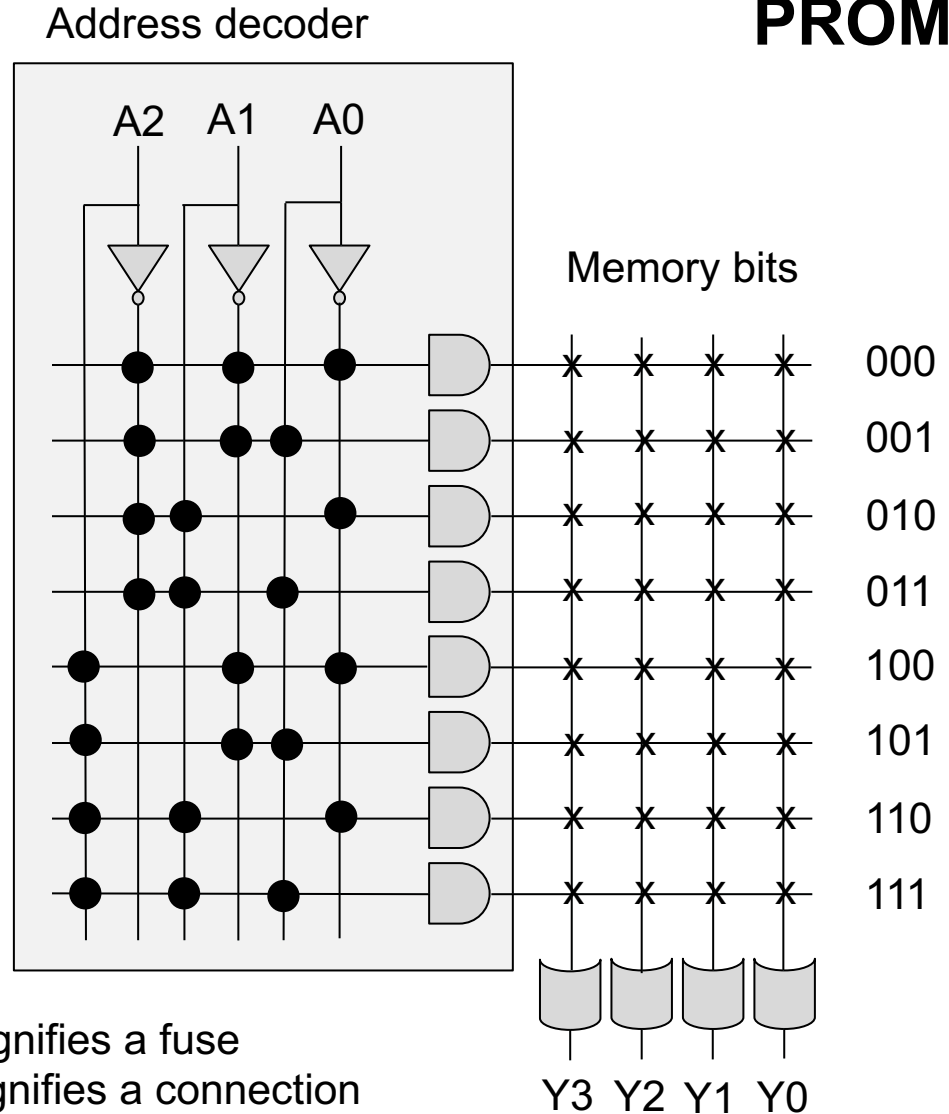 Can be viewed as a **fixed** array of **AND** functions driving a **programmable** array of **OR** functions



# Programmable Logic Array (PLA)


- Programmable AND & OR gate array

  


X signifies a fuse  
● signifies a connection

# Programmable Logic Array (PLA)

- Example of multiplexer

 

$$Y = AS + B\bar{S}$$

 

X signifies a fuse  
● signifies a connection

# Programmable Array Logic (PAL)

- Programmable AND & fixed OR



 



Photo: Michael Holley, 2006.  
Accessed from: <http://commons.wikimedia.org>

 

# Generic Array Logic

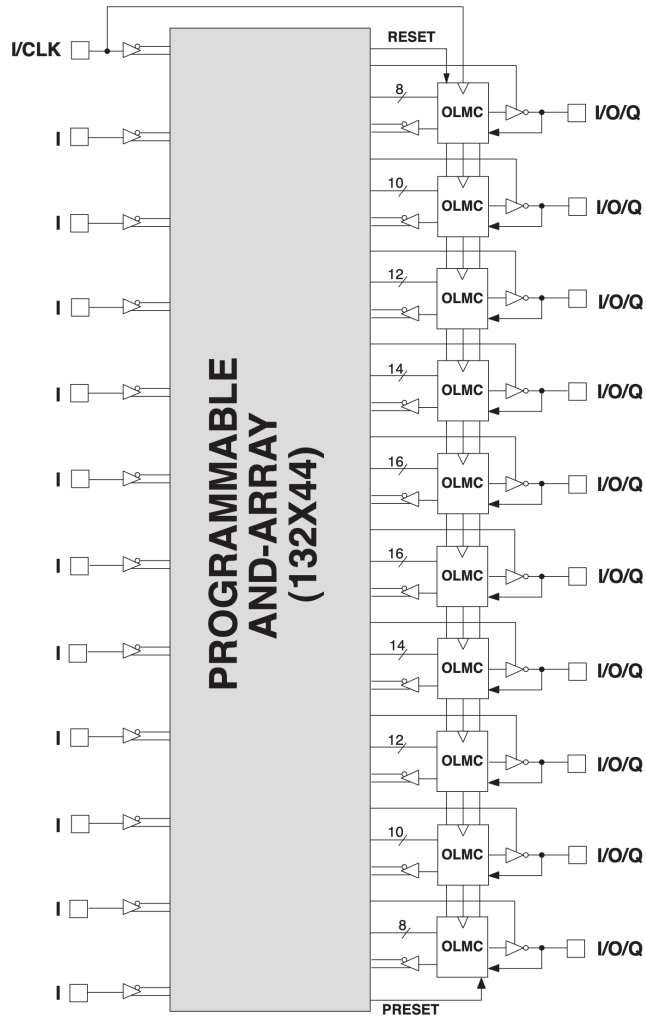

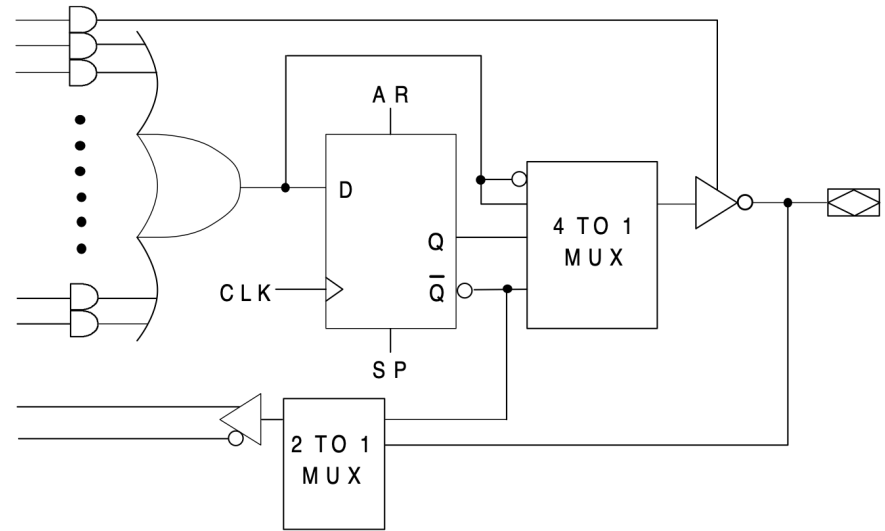- PAL + output macrocell
  - w/ e.g flip-flop & mux



GAL22V10 OUTPUT LOGIC MACROCELL (OLMC)

# Complex PLDs

- More advanced PLDs (end 70s, beg. 80s)
  - CPLD: Complex Programmable Logic Devices (Array of PAL/GAL linked by programmable interconnections)
  - FPGA: Field Programmable Gate Array (Based on concept of Look-Up Table, LUT)

The FPGA was invented by Ross Freeman in 1984.  
Inventor's hall of fame: <https://www.invent.org/inductees/ross-freeman>




Photo: Altera Corporation




Photo: Xilinx

# Look-Up Table (LUT)


A1	A0	M
0	0	0
0	1	0
1	0	0
1	1	1

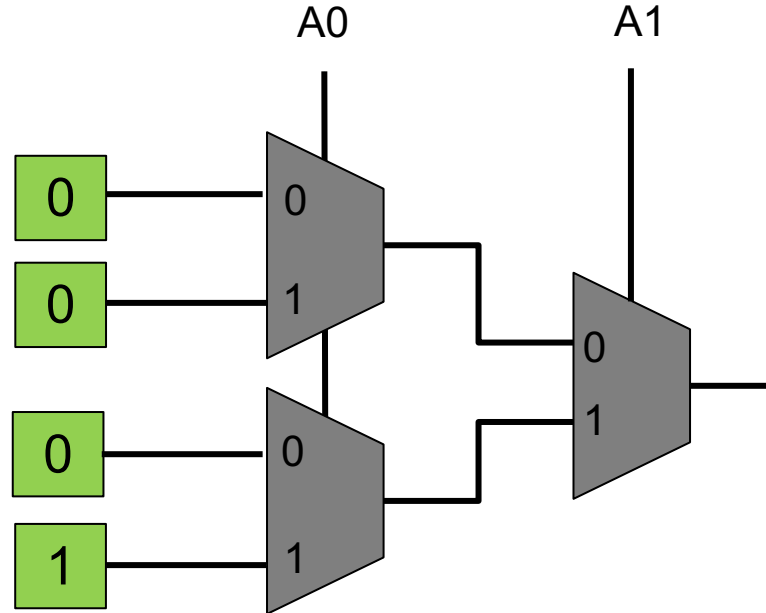

Two input AND-gate

 


# Programmable Logic Devices

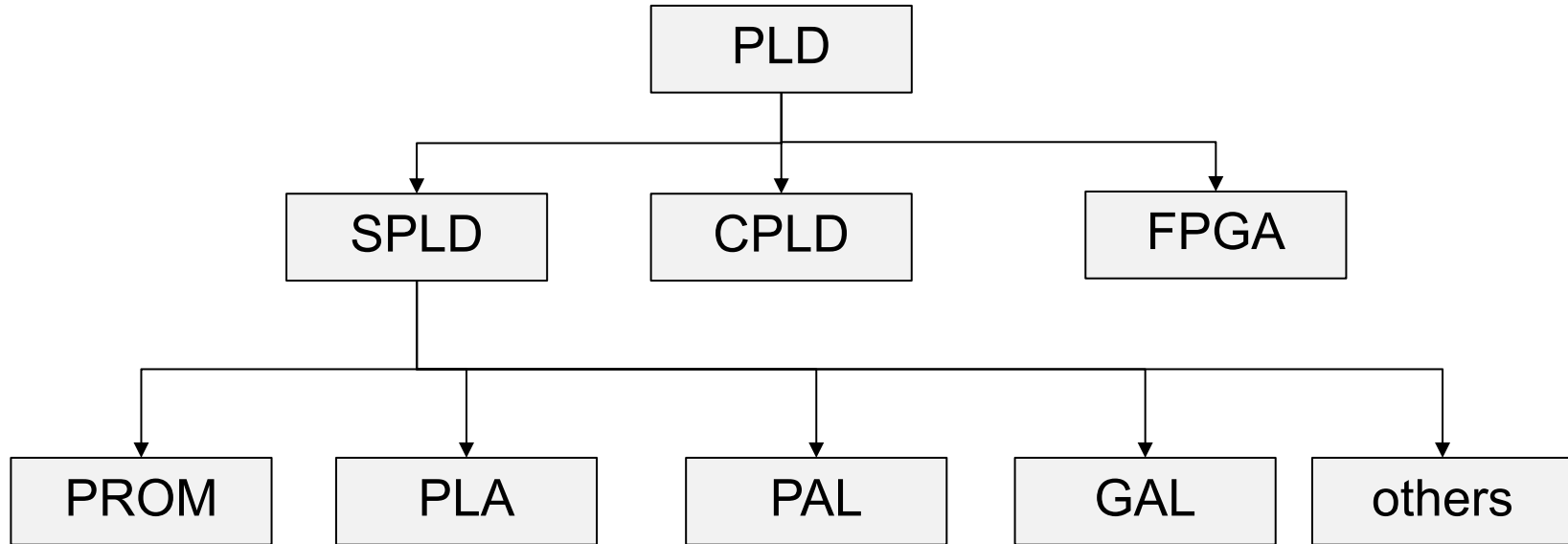

Based on figure 16.19 in Clive Maxfield, “Bebop to the Boolean Boogie”, 3<sup>rd</sup> Edition, Elsiver.



 - Logic gates, multiplexers, flip-flops
- Programmable logic devices
  - PROM, PLA, PAL, GAL, CPLD, FPGA
- Look-up Table (LUT)



- Clive Maxfield, “Who made the first PLD?”, EETimes, 2011.  
<https://www.eetimes.com/who-made-the-first-pld/>
- Clive Maxfield, “Bebop to the Boolean Boogie, 3<sup>rd</sup> Edition. Elsevier. [Available online at UB.](#)
- Wikipedia
- And links used elsewhere in this presentation.