

Fasit INF3430/4431 eksamen 2017

Oppgave 11a)

```
-- Fasit oppgave 11 a)
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity fibonacci is
  generic
  (
    FIBWIDTH : natural := 32 --antall bit i generert Fibonaccitall
  );
  port
  (
    rst      : in std_logic; --asynkron reset
    clk      : in std_logic; --clock
    run      : in std_logic; --en klokkepuls starter funksjonsgeneratoren
    funcsel  : in std_logic_vector(2 downto 0); --funksjonsvalg, "001"
                                           --velger Fibonacci
    nmax     : in std_logic_vector(7 downto 0); --angir max antall Fibonacci
                                           --tall som skal genereres
    inum     : out std_logic_vector(7 downto 0); --angir Fibonaccitall index n
    rdy      : out std_logic; --en positiv puls med en clk-periodes
                               --varighet for å angi et gyldig
    fn       : out std_logic_vector (FIBWIDTH-1 downto 0) --Fibonaccitall n
  );
end fibonacci;

architecture RTL_fibonacci of fibonacci is
  signal f0, next_f0 : unsigned(FIBWIDTH-1 downto 0);
  signal f1, next_f1 : unsigned(FIBWIDTH-1 downto 0);
  signal f2, next_f2 : unsigned(FIBWIDTH-1 downto 0);
  signal n, next_n   : unsigned(7 downto 0);

  type fib_st is (idle_st, calc_st, fn_st, f1_st, f0_st, update_st, rdy_st);
  signal curr_st, next_st : fib_st;
begin

  state_reg :
  process (clk, rst)
  begin
    if rst = '1' then
      curr_st <= idle_st;
      f0      <= (others => '0');
      f1      <= ((0)    => '1', others => '0');
      f2      <= (others => '0');
      n       <= (others => '0');
    elsif rising_edge(clk) then
      curr_st <= next_st;
      f0      <= next_f0;
      f1      <= next_f1;
      f2      <= next_f2;
      n       <= next_n;
    end if;
  end process;

  next_state_comb :
  process (run, funcsel, nmax, curr_st, f0, f1, f2, next_n, n)
  ---process (all) --vhdl 2008
  begin
    next_st <= curr_st;
```

```

next_n    <= n;
rdy      <= '0';
next_f0  <= f0;
next_f1  <= f1;
next_f2  <= f2;

case curr_st is
  when idle_st =>
    next_f0 <= (others => '0');
    next_f1 <= (others => '0');
    next_f2 <= (others => '0');
    next_n   <= (others => '0');
    if run = '1' then
      if funcsel = "001" then
        next_st <= calc_st;
      end if;
    end if;

  when calc_st =>
    if n >= 2 then
      next_st <= fn_st;
    elsif N = 1 then
      next_st <= f1_st;
    else
      next_st <= f0_st;
    end if;

  when f0_st =>
    next_f2 <= (others => '0');
    next_st  <= update_st;

  when f1_st =>
    next_f2 <= ((0) => '1', others => '0');
    next_st  <= update_st;

  when fn_st =>
    next_f2 <= f0 + f1;
    next_st  <= update_st;

  when update_st =>
    next_f0 <= f1;
    next_f1 <= f2;
    if n = unsigned(nmax) then
      next_st <= idle_st;
    else
      next_st <= rdy_st;
    end if;

  when rdy_st =>
    rdy      <= '1';
    next_n   <= n + 1;
    next_st  <= calc_st;

end case;
end process;

inum <= std_logic_vector(n);
fn   <= std_logic_vector(f2);

end RTL_fibonacci;

```

Oppgave 11b)

```

--Fasit oppgave 11b)
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tb_fibonacci is
end tb_fibonacci;

architecture testbench of tb_fibonacci is

constant MYNMAX : natural:= 20;
type fibfasit is array (0 to MYNMAX-1) of natural;
signal myfasit : fibfasit := (0,1,1,2,3,5,8,13,21,34,55,89,144,233,377,610,
                             987,1597,2584,4181);
constant MYWIDTH : natural:= 16;

component fibonacci is
  generic
  (
    FIBWIDTH : natural := 32 --antall bit i generert Fibonaccitall
  );
  port
  (
    rst      : in  std_logic; --asynkron reset
    clk      : in  std_logic; --clock
    run      : in  std_logic; --en klokkepuls starter funksjonsgeneratoren
    funcsel  : in  std_logic_vector(2 downto 0); --funksjonsvalg, "001"
                                                    --velger Fibonacci
    nmax     : in  std_logic_vector(7 downto 0); --angir max antall Fibonacci
                                                    --tall som skal genereres
    inum     : out std_logic_vector(7 downto 0); --angir Fibonaccitall index n
    rdy      : out std_logic; --en positiv puls med en clk-periodes
                                                    --varighet for å angi et gyldig
    fn       : out std_logic_vector (FIBWIDTH-1 downto 0) --Fibonaccitall n
  );
end component fibonacci;

signal rst      : std_logic := '0';
signal clk      : std_logic := '0';
signal run      : std_logic := '0';
signal funcsel  : std_logic_vector(2 downto 0) := "001";
signal nmax     : std_logic_vector(7 downto 0) :=
std_logic_vector(to_unsigned(MYNMAX,8));
signal inum     : std_logic_vector(7 downto 0);
signal rdy      : std_logic;
signal fn       : std_logic_vector (MYWIDTH-1 downto 0);

begin

  UUT : fibonacci
    generic map
    (
      MYWIDTH
    )
    port map
    (
      rst      => rst,
      clk      => clk,
      run      => run,
      funcsel  => funcsel,
      nmax     => nmax,
      inum     => inum,
      rdy      => rdy,
      fn       => fn
    );

```

```

clk <= not clk after 5 ns;


stimuli :
process
  variable errorcnt : integer := 0;
begin
  rst <= '1', '0' after 100 ns;
  wait for 120 ns;
  run <= '1', '0' after 20 ns;
  funcsel <= "001";
  for i in 0 to MYNMAX-1 loop
    wait until rising_edge(rdy);
    wait for 5 ns;
    if (unsigned(fn) /= to_unsigned(myfasit(i),mywidth)) then
      errorcnt := errorcnt +1;
      --assert (unsigned(fn) = to_unsigned(myfasit(i),mywidth))
      report "Fibonacci number " & integer'image(i) & " incorrect @ time: "
& time'image(now) &
      " Expected " & natural'image(myfasit(i)) & " Actual " &
natural'image(to_integer(unsigned(fn)))
      severity error;
    end if;
  end loop;

  assert not(errorcnt = 0)
  report "Passed"
  severity note;



  assert (errorcnt = 0)
  report "Failed with " & integer'image(errorcnt) & " errors"
  severity error;
  wait;
end process;

end testbench;


```

 

Oppgave 11c)

 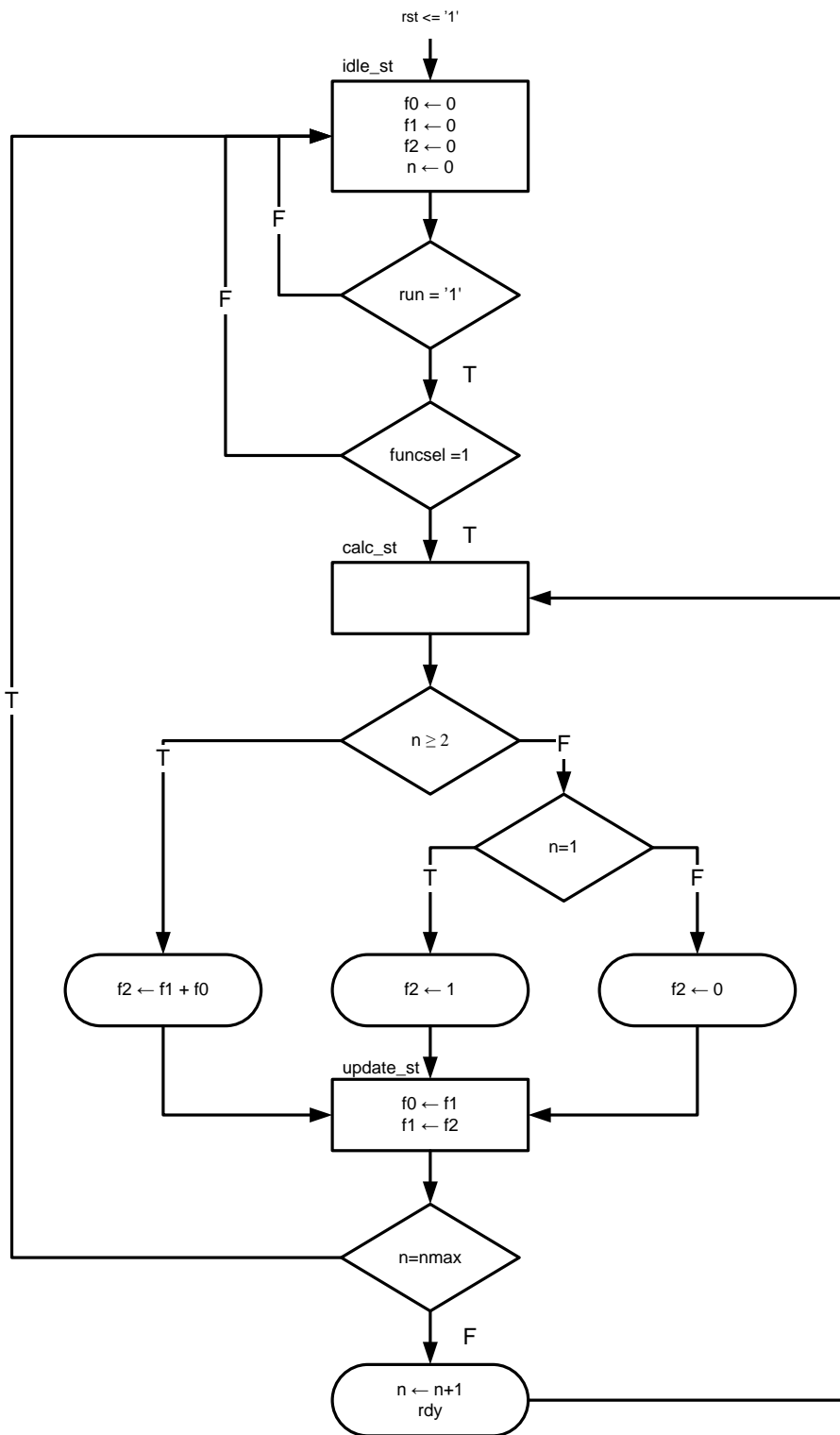

Oppgave 11d)

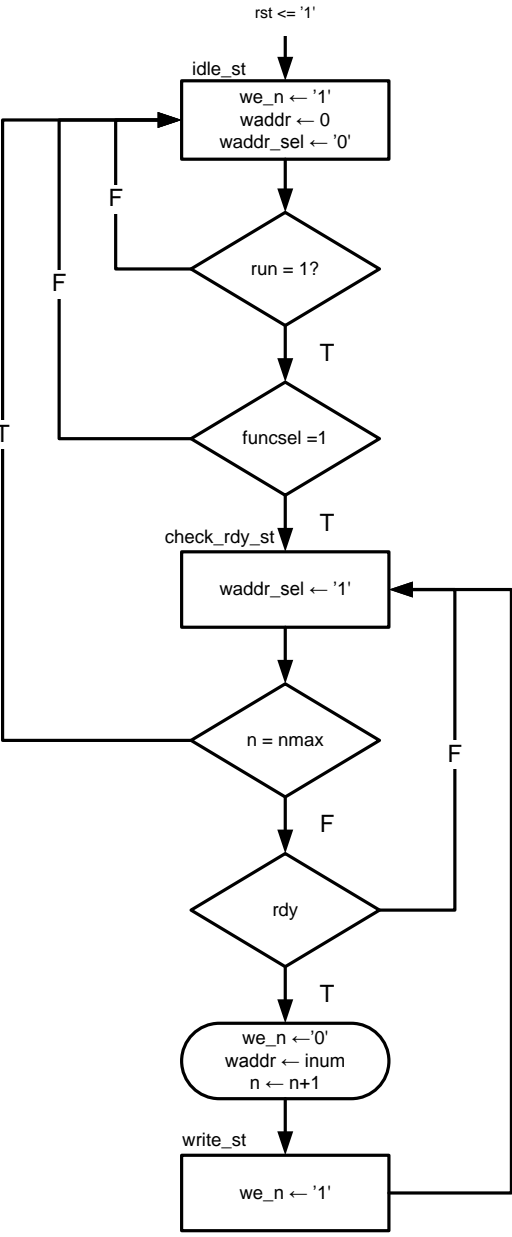

Oppgave 11e)

```
tristate_buffer:
process (nwe,wdata)
begin
  if nwe = '0' then
    data <= wdata;
  else
    data <= (others => 'Z');
  end if;
end process;

addressmultiplexer:
process (waddr,raddr,waddr_sel)
begin
  addr <= raddr;
  if waddr_sel = '1' then
    addr <=waddr;
  end if;
end process;
```