

INF3430/INF4431 H2017.

Fasit oppgavene 1-5 og 9-10:

Oppgave	A	B	C	D	E
1			X		
2		X	X	X	X
3		X		X	
4				X	
5			X	X	X
9			X		
10	X*				X*

Kommentar til oppgave 10:

Vi har valgt å la de som har oppgitt enten alternativ A (dvs. 51) eller alternativ E (dvs. 69) få poeng i oppgave 10. De som har oppgitt feil eller unnlatt å besvare oppgaven 10 vil IKKE få minus poeng. Se fasit for oppgave 8 for begrunnelse.

Oppgave 6)

```
library ieee;
use ieee.std_logic_1164.all;

entity arbitrary_sequence_gen is
  port
  (
    rst    : in  std_logic;
    clk    : in  std_logic;
    run    : in  std_logic;
    q      : out std_logic_vector(2 downto 0)
  );
```

```

end entity arbitrary_sequence_gen;

architecture rtl of arbitrary_sequence_gen is

    type state_type is (VALUE1, VALUE2, VALUE3, VALUE4, VALUE5, VALUE6,
VALUE7);
    signal present_state, next_state : state_type;

begin

    --stateregister
    STATE_REG :
    process (rst, clk) is
    begin
        if rst = '1' then
            present_state <= VALUE1;
        elsif rising_edge(clk) then
            present_state <= next_state;
        end if;
    end process state_reg;

    --Nextstate logic and output logic
    COMB :
    process (present_state, run) is
    begin

        -- Set default next state to current state
        next_state <= present_state;

        case present_state is
            when VALUE1 =>
                q <= "100"; -- i.e. 4
                if run='1' then
                    next_state <= VALUE2;
                end if;
            when VALUE2 =>
                q <= "010"; -- i.e. 2
                if run='1' then
                    next_state <= VALUE3;
                end if;
            when VALUE3 =>
                q <= "101"; -- i.e. 5
                if run='1' then
                    next_state <= VALUE4;
                end if;
            when VALUE4 =>
                q <= "110"; -- i.e. 6
                if run='1' then
                    next_state <= VALUE5;
                end if;
            when VALUE5 =>
                q <= "111"; -- i.e. 7

```

```

        if run='1' then
            next_state <= VALUE6;
        end if;
    when VALUE6 =>
        q <= "011";    -- i.e. 3
        if run='1' then
            next_state <= VALUE7;
        end if;
    when VALUE7 =>
        q <= "001";    -- i.e. 1
        if run='1' then
            next_state <= VALUE1;
        end if;
    end case;
end process COMB;

```

```
end architecture rtl;
```

-- Det er ikke krav om testbenk i besvarelsen

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tb_arbitrary_sequence_gen is
    -- empty;
end tb_arbitrary_sequence_gen;

architecture beh of tb_arbitrary_sequence_gen is

    component arbitrary_sequence_gen
        port (
            rst : in  std_logic;
            clk : in  std_logic;
            run : in  std_logic;
            q   : out std_logic_vector(2 downto 0));
    end component;

    signal rst : std_logic;
    signal clk : std_logic:= '0';
    signal run : std_logic;
    signal q   : std_logic_vector(2 downto 0);

begin

    arbitrary_sequence_gen_0: arbitrary_sequence_gen
        port map (
            rst => rst,
            clk => clk,
            run => run,
            q   => q);

```

```

-- Clock and reset generation
clk <= not clk after 10 ns;
rst <= '1', '0' after 20 ns;

P_TEST: process
begin

    run <= '0';

    wait until falling_edge(rst);

    wait for 40 ns;

    run <= '1';

    wait for 200 ns;

    run <= '0';

    wait for 40 ns;

    run <= '1';

    wait for 200 ns;

    run <= '0';

    wait for 20 ns;

    wait;

end process;

end beh;

```

Oppgave 7)

I oppgave 7 var det ved en feil ikke blitt oppgitt funksjonen til signalet run. Det vil derfor ikke bli trukket noen poeng hvis run ikke har blitt brukt i løsningen.

Load av ny seed kan enten gjøres som vist i fasiten eller alternativt brukes med en gang uten «else» statementet ettersom det heller ikke var oppgitt i oppgaven.

```

library ieee;
use ieee.std_logic_1164.all;

```

```

entity lfsr is
  port
    (rst    : in  std_logic;
     clk    : in  std_logic;
     load   : in  std_logic;
     seed   : in  std_logic_vector(2 downto 0);
     run    : in  std_logic;
     q      : out std_logic_vector(2 downto 0);
     err    : out std_logic);
end entity lfsr;

```

```

architecture rtl of lfsr is

```

```

  -- Shift register
  signal q_i : std_logic_vector(2 downto 0);

```

```

begin

```

```

  process (rst, clk) is
    variable feedback : std_logic;
  begin
    if rst = '1' then
      q_i <= "100";
      err <= '0';
    elsif rising_edge(clk) then
      if load='1' then
        if seed="000" then
          err <= '1';
        else
          err <= '0';
        end if;
        q_i <= seed;
      else
        if run='1' then
          feedback := q_i(0) xor q_i(1);
          q_i <= feedback & q_i(2 downto 1);
        end if;
      end if;
    end if;
  end process;

```

```

  -- Concurrent output statements
  q <= q_i;

```

```

end architecture rtl;

```

-- Det er ikke krav om testbenk i besvarelsen

```

library ieee;

```

```

use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tb_lfsr is
  -- empty;
end tb_lfsr;

architecture beh of tb_lfsr is

  component lfsr
    port (
      rst : in  std_logic;
      clk : in  std_logic;
      load : in  std_logic;
      seed : in  std_logic_vector(2 downto 0);
      run : in  std_logic;
      q : out std_logic_vector(2 downto 0);
      err : out std_logic);
  end component;

  signal rst : std_logic;
  signal clk : std_logic:= '0';
  signal load : std_logic;
  signal seed : std_logic_vector(2 downto 0);
  signal run : std_logic;
  signal q : std_logic_vector(2 downto 0);
  signal err : std_logic;

begin

  lfsr_0: lfsr
    port map (
      rst => rst,
      clk => clk,
      load => load,
      seed => seed,
      run => run,
      q => q,
      err => err);

  -- Clock and reset generation
  clk <= not clk after 10 ns;
  rst <= '1', '0' after 20 ns;

  P_TEST: process
  begin

    load <= '0';
    seed <= (others => '0');
    run <= '0';

    wait until falling_edge(rst);

```

```
wait for 40 ns;
load <= '1';
seed <= "100";

wait for 20 ns;
load <= '0';
seed <= "000";

wait for 20 ns;
run <= '1';

wait for 200 ns;
run <= '0';

wait for 40 ns;
run <= '1';

wait for 200 ns;
run <= '0';

wait for 20 ns;
load <= '1';
seed <= "000";

wait until rising_edge(err);

wait for 20 ns;
load <= '0';
seed <= "000";

wait for 40 ns;
load <= '1';
seed <= "100";

wait for 20 ns;
load <= '0';
seed <= "000";

wait for 20 ns;
run <= '1';

wait for 100 ns;
run <= '0';

wait for 40 ns;

wait;

end process;

end beh;
```

Oppgave 8)

I oppgaven kom antall pipelinetrinn for dårlig frem. Derfor blir det flere løsningen hvor det enten kan utføres 2 addisjoner i første pipelinetrinn og deretter en addisjon og en større enn operasjon i neste pipelinetrinn, eller det er også mulig å tolke oppgaven slik at i første pipelinetrinn utføres 2 addisjoner i parallell, deretter en addisjon i neste pipelinetrinn og i tredje pipelinetrinn utføres større enn operasjonen.

Oppgaven kan enten løses med 1 prosess eller med 3 prosesser.

Det er mulig å la alle pipeline registrene i VHDL koden være på 18 bit (dvs. 17 downto 0). Da vil syntese verktøyet til Vivado fjerne/optimalisere bort unødvendige registre (dvs. 2) slik at antall registre/flip-flop i oppgave 10 blir 51 (pga. $17+17+16+1=51$) for 2 pipeline løsningen og 69 (pga. $17+17+18+16+1=69$) for 3 pipeline løsningen.

Vi har valgt å la de som har oppgitt enten 51 eller 69 få poeng i oppgave 10. De som har oppgitt feil eller unnlatt å besvare oppgaven 10 vil IKKE få minus poeng.

Løsning med 3 pipelinetrinn:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity compute is
  port
    (rst      : in  std_logic;
     clk      : in  std_logic;
     a        : in  std_logic_vector(15 downto 0);
     b        : in  std_logic_vector(15 downto 0);
     c        : in  std_logic_vector(15 downto 0);
     d        : in  std_logic_vector(15 downto 0);
     result   : out std_logic_vector(15 downto 0);
     max      : out std_logic);
end entity compute;
```

```
library ieee;
use ieee.std_logic_1164.all;
```



```

use ieee.numeric_std.all;

architecture pipelined_rtl of compute is

    signal ab_tmp    : unsigned(16 downto 0);
    signal cd_tmp    : unsigned(16 downto 0);
    signal result_i  : unsigned(17 downto 0);

begin

    process (rst, clk) is
    begin
        if rst = '1' then
            ab_tmp    <= (others => '0');
            cd_tmp    <= (others => '0');
            result_i  <= (others => '0');
            result    <= (others => '0');
            max       <= '0';
        elsif rising_edge(clk) then
            ab_tmp    <= unsigned('0' & a) + unsigned('0' & b);
            cd_tmp    <= unsigned('0' & c) + unsigned('0' & d);
            result_i  <= ('0' & ab_tmp) + ('0' & cd_tmp);
            if result_i > "00111111111111111" then
                result <= (others => '1');
                max    <= '1';
            else
                result <= std_logic_vector(result_i(15 downto 0));
                max    <= '0';
            end if;
        end if;
    end process;

end architecture pipelined_rtl;

```

Alternativ løsning med 3 prosesser og 3 pipelinetrinn:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture pipelined2_rtl of compute is

    signal ab_tmp    : unsigned(16 downto 0);
    signal cd_tmp    : unsigned(16 downto 0);
    signal result_i  : unsigned(17 downto 0);

begin

    process (rst, clk) is

```

```

begin
  if rst = '1' then
    ab_tmp <= (others => '0');
    cd_tmp <= (others => '0');
  elsif rising_edge(clk) then
    ab_tmp <= unsigned('0' & a) + unsigned('0' & b);
    cd_tmp <= unsigned('0' & c) + unsigned('0' & d);
  end if;
end process;

process (rst, clk) is
begin
  if rst = '1' then
    result_i <= (others => '0');
  elsif rising_edge(clk) then
    result_i <= ('0' & ab_tmp) + ('0' & cd_tmp);
  end if;
end process;

process (rst, clk) is
begin
  if rst = '1' then
    result <= (others => '0');
    max <= '0';
  elsif rising_edge(clk) then
    if result_i > "001111111111111111" then
      result <= (others => '1');
      max <= '1';
    else
      result <= std_logic_vector(result_i(15 downto 0));
      max <= '0';
    end if;
  end if;
end process;

end architecture pipelined2_rtl;

```

Alternativ løsning med 3 pipelinetrinn:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture pipelined3_rtl of compute is

  signal ab_tmp    : unsigned(17 downto 0);
  signal cd_tmp    : unsigned(17 downto 0);
  signal result_i  : unsigned(17 downto 0);

```

```

begin

  process (rst, clk) is
  begin
    if rst = '1' then
      ab_tmp    <= (others => '0');
      cd_tmp    <= (others => '0');
      result_i  <= (others => '0');
      result    <= (others => '0');
      max       <= '0';
    elsif rising_edge(clk) then
      ab_tmp    <= unsigned("00" & a) + unsigned("00" & b);
      cd_tmp    <= unsigned("00" & c) + unsigned("00" & d);
      result_i  <= ab_tmp + cd_tmp;
      if result_i > "0011111111111111" then
        result  <= (others => '1');
        max     <= '1';
      else
        result  <= std_logic_vector(result_i(15 downto 0));
        max     <= '0';
      end if;
    end if;
  end process;

end architecture pipelined3_rtl;

```

Alternativ løsning med 2 pipelinetrinn:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture pipelined4_rtl of compute is

  signal ab_tmp    : unsigned(16 downto 0);
  signal cd_tmp    : unsigned(16 downto 0);

begin

  process (rst, clk) is
  begin
    if rst = '1' then
      ab_tmp    <= (others => '0');
      cd_tmp    <= (others => '0');
      result    <= (others => '0');
      max       <= '0';
    elsif rising_edge(clk) then

```

```

    ab_tmp    <= unsigned('0' & a) + unsigned('0' & b);
    cd_tmp    <= unsigned('0' & c) + unsigned('0' & d);
    result_i := ('0' & ab_tmp) + ('0' & cd_tmp);
    if result_i > "001111111111111111" then
        result <= (others => '1');
        max    <= '1';
    else
        result <= std_logic_vector(result_i(15 downto 0));
        max    <= '0';
    end if;
end if;
end process;

end architecture pipelined4_rtl;

```

Alternativ løsning med 2 pipelinetrinn:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

architecture pipelined5_rtl of compute is

    signal ab_tmp    : unsigned(17 downto 0);
    signal cd_tmp    : unsigned(17 downto 0);

begin

    process (rst, clk) is
        variable result_i : unsigned(17 downto 0);
    begin
        if rst = '1' then
            ab_tmp    <= (others => '0');
            cd_tmp    <= (others => '0');
            result    <= (others => '0');
            max       <= '0';
        elsif rising_edge(clk) then
            ab_tmp    <= unsigned("00" & a) + unsigned("00" & b);
            cd_tmp    <= unsigned("00" & c) + unsigned("00" & d);
            result_i := ab_tmp + cd_tmp;
            if result_i > "001111111111111111" then
                result <= (others => '1');
                max    <= '1';
            else
                result <= std_logic_vector(result_i(15 downto 0));
                max    <= '0';
            end if;
        end if;
    end if;
end process;

```

```
end architecture pipelined5_rtl;
```

-- Det er ikke krav om testbenk i besvarelsen

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tb_compute is
  -- empty;
end tb_compute;

architecture beh of tb_compute is

  component compute
    port (
      rst      : in  std_logic;
      clk      : in  std_logic;
      a        : in  std_logic_vector(15 downto 0);
      b        : in  std_logic_vector(15 downto 0);
      c        : in  std_logic_vector(15 downto 0);
      d        : in  std_logic_vector(15 downto 0);
      result   : out std_logic_vector(15 downto 0);
      max      : out std_logic);
  end component;

  signal rst      : std_logic;
  signal clk      : std_logic:= '0';
  signal a        : std_logic_vector(15 downto 0);
  signal b        : std_logic_vector(15 downto 0);
  signal c        : std_logic_vector(15 downto 0);
  signal d        : std_logic_vector(15 downto 0);
  signal result   : std_logic_vector(15 downto 0);
  signal max      : std_logic;

begin

  compute_0: compute
    port map (
      rst      => rst,
      clk      => clk,
      a        => a,
      b        => b,
      c        => c,
      d        => d,
      result   => result,
      max      => max);

  -- Clock and reset generation
  clk <= not clk after 10 ns;
```

```
rst <= '1', '0' after 20 ns;

P_TEST: process
begin

    a <= (others => '0');
    b <= (others => '0');
    c <= (others => '0');
    d <= (others => '0');

    wait until falling_edge(rst);

    wait for 40 ns;

    a <= x"0001";
    b <= x"0002";
    c <= x"0003";
    d <= x"0004";

    wait for 100 ns;

    a <= x"0105";
    b <= x"0206";
    c <= x"0307";
    d <= x"0408";

    wait for 100 ns;

    a <= x"FFFF";
    b <= x"0000";
    c <= x"0001";
    d <= x"0000";

    wait until rising_edge(max);
    wait for 90 ns;

    a <= x"FFFF";
    b <= x"FFFF";
    c <= x"FFFF";
    d <= x"FFFF";

    wait for 100 ns;

    a <= x"0111";
    b <= x"0222";
    c <= x"0333";
    d <= x"0444";

    wait for 100 ns;

    wait;
```

```
end process;
```

```
end beh;
```