

IN 3160, IN4160

Combinational building blocks

Yngve Hafting



Messages

- **Avoid rebooting LISP machines**
 - Issues with new Redhat kernel & nVidia => black screen when booted
 - Fixing this is work in progress.
- Covid update
 - Lab supervision on Friday may be canceled/ or zoom only...
 - Lisp is still open.
 - 1m requirement is lifted for education

In this course you will learn about the design of advanced digital systems. This includes programmable logic circuits, a hardware design language and system-on-chip design (processor, memory and logic on a chip). Lab assignments provide practical experience in how real design can be made.

After completion of the course you will:

- understand important principles for design and testing of digital systems
- **understand the relationship between behaviour and different construction criteria**
- **be able to describe advanced digital systems at different levels of detail**
- **be able to perform simulation and synthesis of digital systems.**

Goals for this lesson:

- Know the basic structure and function of widely used combinational structures.
 - Multiplexers
 - Encoders
 - Decoders
 - Arbiter
 - Comparator
 - Shifters
 - ROM

Recap from previous lessons

- Process runs within 1 delta delay.
- Processes are interpreted in a sequence that creates priority for how things happen
 - Last change takes precedence.
- Variables have values based on position, and are updated «within» one process run.
 - Changes to variables are not added to the queue, they take effect immediately.
 - A variable can thus be used with many values within a process...
- Changes to signals are put in the queue of delta delays, so they are not updated within the process.

Today: Building blocks

- About dataflow representations
- Encoders vs Decoders
- Decoder
- Multiplexer
- Encoders
- Arbiters
- Shifters
- Comparators
 - VHDL: dataflow vs RTL examples
- ROM
- RAM

Next lecture:



- Subroutines
- Packages & Libraries
- Clocked statements.

Data flow representations

- Dataflow
 - Matches port/gate schematics
 - Use *when this is the only way* to achieve desired function
 - (speed / area / power).
- high level code is...
 - *easier to read,*
 - *easier to maintain*
- **Use high level code whenever possible!**
 - *To show how building blocks are made,*
this presentation uses low level representations
 - *Normally we want our code to be at a higher level*


Encoders and decoders

  - Encoders and decoders convert signals from one type to another
- decoder = inverse encoder
- Several types:
 - One hot decoder " $n \rightarrow 2^n$ "
 - Binary encoder " $n \rightarrow \log_2(n)$ "
 - Priority encoder
 - Arbiter
- A ‘**case**’ or ‘**select**’ statement generally creates encoder logic...



n to 2^n Decoder

 - Ex: generic N to 2^N decoder
 - (binary to *one hot* converter)
- Is at the same time an example of the strict type check in VHDL
 - numeric_std is required for
 - ‘`unsigned`’ and ‘`integer`’ conversions



```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity decoder is
  generic(n : positive := 4);
  port(
    a: in std_logic_vector(n-1 downto 0);
    z: out std_logic_vector(2**n-1 downto 0)
  );
end entity decoder;


architecture rotate of decoder is
  constant one_vector : unsigned(z'range):= to_unsigned(1, z'high+1);
begin
  z <= std_logic_vector(one_vector sll to_integer(unsigned(a)));
end architecture rotate;

-- signal shift: integer;
-- shift <= to_integer(unsigned(a));
-- z <= std_logic_vector(one sll shift);
  
```



Multiplexer

- Multiplexer:
 - n k -bit inputs
 - n -bit one-hot select signal s
 - Multiplexers are commonly used as *data selectors*

 
Selects one of n k -bit inputs
 s must be one-hot
 $b=a[i]$ if $s [i] = 1$



Multiplexer Implementation

 
 


k-bit Binary-Select Multiplexer

 

Selects one of n k-bit inputs
 s must be one-hot
 $b=a[i]$ if $s[i] = 1$

k-bit Binary-Select Multiplexer (Cont)

  

```
-- three input mux with one-hot select (arbitrary width)
library ieee;
use ieee.std_logic_1164.all;

entity Mux3a is
    generic( k : integer := 1 );
    port( a2, a1, a0 : in std_logic_vector( k-1 downto 0 ); -- inputs
          s : in std_logic_vector( 2 downto 0 ); -- one-hot select
          b : out std_logic_vector( k-1 downto 0 ) );
end Mux3a;

architecture case_impl of Mux3a is
begin
    process(all) begin
        case s is
            when "001" => b <= a0;
            when "010" => b <= a1;
            when "100" => b <= a2;
            when others => b <= (others => '-');
        end case;
    end process;
end case_impl;
```

```
architecture select_impl of Mux3a is
begin
    with s select b <=
        a0 when "001",
        a1 when "010",
        a2 when "100",
        (others => '-') when others;
end select_impl;
```


- Can this be implemented using ‘**select**’ statement?
 - Single input vector
 - Single output vector...
 - QED...

Structural Implementation of k-bit Binary-Select Multiplexer

```
-- 3:1 multiplexer with binary select (arbitrary width)
library ieee;
use ieee.std_logic_1164.all;
use work.ch8.all;

entity Muxb3 is
    generic( k : integer := 1 );
    port( a2, a1, a0 : in std_logic_vector( k-1 downto 0 ); -- inputs
          sb : in std_logic_vector( 1 downto 0 ); -- binary select
          b : out std_logic_vector( k-1 downto 0 ) );
end Muxb3;

 architecture struct_impl of Muxb3 is
    signal s: std_logic_vector(2 downto 0);
begin
    -- decoder converts binary to one-hot
    d: Dec generic map(2,3) port map(sb,s);
    -- multiplexer selects input
    mx: Mux3 generic map(k) port map(a2,a1,a0,s,b);
end struct_impl;
```



Encoder: Don't cares vs ordered priority:

```

architecture dont_care of priority is
begin
    with a select y <=
        "00" when "0001",
        "01" when "001-",
        "10" when "01--",
        "11" when "1---",
        "00" when others;

    with a select valid <=
        '1' when "1---" | "01--" | "001-" | "0001",
        '0' when others;

end architecture dont_care;
    
```

| A3 | A2 | A1 | A0 | Y1 | Y0 | Valid |
|----|----|----|----|----|----|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | - | 0 | 1 | 1 |
| 0 | 1 | - | - | 1 | 0 | 1 |
| 1 | - | - | - | 1 | 1 | 1 |

```

architecture ordered of priority is
begin
    y <=
        "11" when a(3) else
        "10" when a(2) else
        "01" when a(1) else
        "00" when a(0) else
        "00";

    valid <= '1' when or a else '0';
end architecture ordered;
    
```

Don't cares vs sequential ordered priority

```
architecture mcase of priority is
begin
  process(a) is
  begin
    --default values
    y <= "00";
    valid <= '1';
    case? a is
      when "0001" => y <= "00";
      when "001-" => y <= "01";
      when "01--" => y <= "10";
      when "1---" => y <= "11";
      when others => valid <= '0';
    end case?;
  end process;
end architecture mcase;
```

```
architecture default_if of priority is
begin
  process(a) is
  begin
    --default values
    y <= "00";
    valid <= '1';
    if a(3) then y <= "11";
    elsif a(2) then y <= "10";
    elsif a(1) then y <= "01";
    elsif a(0) then y <= "00";
    else valid <= '0';
    end if;
  end process;
end architecture default_if;
```

```
architecture non_default of priority is
begin
  process(a) is
  begin
    --no default values
    if a(3) then
      y <= "11";
      valid <= '1';
    elsif a(2) then
      y <= "10";
      valid <= '1';
    elsif a(1) then
      y <= "01";
      valid <= '1';
    elsif a(0) then
      y <= "00";
      valid <= '1';
    else
      y <= "00";
      valid <= '0';
    end if;
  end process;
end architecture non_default;
```

| A3 | A2 | A1 | A0 | Y1 | Y0 | Valid |
|----|----|----|----|----|----|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | - | 0 | 1 | 1 |
| 0 | 1 | - | - | 1 | 0 | 1 |
| 1 | - | - | - | 1 | 1 | 1 |

Benefits:

- Test on input (a) is done only once

Pitfalls:

- Easy to forget specifying all outputs for all inputs
- Using if, readability will suffer when complexity grows
- Synthesis on ordered priority..?

Generic priority encoder


```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
entity priority is
generic( n : positive);
port
( a      : in  std_logic_vector(2**n-1 downto 0);
  y      : out std_logic_vector(n-1 downto 0);
  valid : out std_logic
);
end entity priority;

architecture iterative of priority is
begin
  process (a) is
begin
  valid <= '0';           -- default value
  y     <= (others => '0'); -- default value
  for i in a'range loop    -- a'range = (2**n-1 downto 0)
    if a(i) = '1' then
      y     <= std_logic_vector(to_unsigned(i, n));
      valid <= '1';
      exit;          -- exit ends the loop..
    end if;         -- exit ensures the priority (!) along with
  end loop;            -- a'range starting on highest bit. Without
end process;          -- exit y might be overwritten multiple times
end architecture iterative;
```

- Note how the priority changes due to the **exit** statement in the for-loop.
- Changing the direction of a'range would also change priority...
 - (ie **(0 to 2**n-1)**)

Arbiter

- Arbiters is used to sort requests for resources
 - interrupt handling in a cpu or microprocessor
 - Finds the least (or most significant) one-bit
 - cascaded vs look-ahead principle
 - VHDL = priority encoder (previous page).
 - Normally we let synthesis tool decide
 - FPGA => mostly LUT based
 - Structural code may bind a solution
 - Is it a critical feature?
 - Does not synthesis provide desired result?

 


Priority encoder test bench

- The example makes stimuli to a combinational function independent of number of bits
- The attribute x'high gives the highest bit number to the vector x and x'low the lowest bit number

```
STIMULI :  
process  
    variable ain : integer := 0;  
begin  
    loop  
        for ain in 0 to 2**(a'high-a'low+1)-1 loop  
            a <= std_logic_vector  
                (TO_UNSIGNED(ain, a'high-a'low+1));  
            wait for 50 ns;  
        end loop;  
    end loop;  
end process;
```






Shifters

 - Ex, 4 bit :
 - a) SLL
 - b) SRL
 - c) SRA



Shift operators in VHDL

     - The shift operators are defined for **bit_vector** (originally)
 - and **unsigned** and **signed** in numeric_std
- If you are defining shift operators for other types, you have to make so called “overload”-operators
- By overload we mean that there are an already existing operator with the same name, but is written for another data type



```
-- simple shift left operation in VHDL
variable n : positive := 5;
...
a(31 downto n) <= a(31-n downto 0); -- a'high is 31,
a(n-1 downto 0) <= (others => '0'); -- a'low is 0.
```

```
-- using sll
a <= std_logic_vector( to_unsigned(a) sll (n) );
```

Shift operators



- The standard libraries does not define shift operators for **std_logic_vector**
- The standard synthesis library **numeric_std** defines two data types which are sub types of **std_logic**:
 - **unsigned**
 - **signed**
 - For these two it exists shift operators (overload)
- Use type casting to go between **std_logic_vector** and **signed / unsigned**

```
-- a is std_logic_vector.  
a <= std_logic_vector( to_unsigned(a) sll(n) );
```

Comparators

- Equality ‘=’
- Magnitude ‘<’, ‘>’

Equality Comparator

  

```
-- high level comparator use, IF
if (a = b) then
    p <= q;
else
    p <= (others => '0');
end if;

-- high level comparator use, WHEN ... ELSE
p <= q when (a = b) else (others => '0');
```



Magnitude Comparator

- **if** ($a > b$) **then** ...'
- will infer what you need most of the time
- Dataflow example.


```
library ieee;
use ieee.std_logic_1164.all;

entity MagComp is
  generic( k: integer := 8 );
  port( a, b: in std_logic_vector(k-1 downto 0);
        gt: out std_logic );
end MagComp;

  
architecture impl of MagComp is
  signal eqi, gti : std_logic_vector(k-1 downto 0);
  signal gtb: std_logic_vector(k downto 0);
begin
  begin
    eqi <= a xnor b;
    gti <= a and not b;
    gtb <= (gti or (eqi and gtb(k-1 downto 0))) & '0';
    gt <= gtb(k);
  end impl;
```



Read-only memory (ROM)

 

2-D array implementation

 

ROM using VHDL

- ROM can be implemented using
 - selected statement
 - case
 - D&H demonstrates this.
 - constants
 - Example next slide
- File IO *can* be used to store ROM values.
 - Tools may be picky about implementations.
 - *We will look into that later.*

Example: ROM

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;

entity ROM is
  generic(
    data_width: natural := 8;
    addr_width: natural := 2);
  port(
    address: in std_logic_vector(addr_width-1 downto 0);
    data: out std_logic_vector(data_width-1 downto 0));
end entity;


architecture synth of ROM is
  type memory_array is array(2**addr_width-1 downto 0) of
    std_logic_vector(data_width-1 downto 0);

  constant ROM_DATA: memory_array := (
    8x"00", -- address 3 (from 'left to 'right)
    8x"A5", -- address 2
    8x"5A", -- address 1
    8x"FF" -- address 0
  );

begin
  data <= ROM_DATA(to_integer(unsigned(address)));
end architecture synth;

```

 - 4 byte ROM example
 - 8 bit data
 - 2 bit address
- We can define array types in VHDL
- Constants are set using :=
- Array data is listed in the sequence given by the type (array) definition
 - Here: $(2^{addr_width-1} \text{ downto } 0) \Rightarrow 3, 2, 1, 0$
- Indexing requires conversion to integer



RAM using VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;


entity RAM is
generic(
    data_width: natural := 8;
    addr_width: natural := 2
);
port(
    address: in std_logic_vector(addr_width-1 downto 0);
    data_in: in std_logic_vector(data_width-1 downto 0);
    data_write: in std_logic;
    data_out: out std_logic_vector(data_width-1 downto 0)
);
end entity RAM;

architecture synth of RAM is
type memory_array is array(2**addr_width-1 downto 0) of
    std_logic_vector(data_width-1 downto 0);

signal ram_data: memory_array :=
    (8x"00", 8x"00", 8x"00", 8x"FF");
begin
    data_out <=
        ram_data(to_integer(unsigned(address)));
    ram_data(to_integer(unsigned(address))) <=
        data_in when data_write; -- else latched
end architecture synth;

```

 - 4 Byte RAM example
- Mostly like the ROM example
 - Added write and data_in
 - Data is a **signal**, not **constant**
- Signals *may* have default values in synthesis (RAM based FPGAs)
- Writing is latched
 - *not strictly combinational*



Suggested reading

- D&H 8.1- 8.9 p157-192
- *(8.10 PLA -> Architecture)*