



UiO : **Department of Informatics**  
University of Oslo

**IN3160 IN4160**  
**Datapath state machines**  
Yngve Hafting



In this course you will learn about the **design of advanced digital systems**. This includes programmable logic circuits, a **hardware design language** and system-on-chip design (processor, memory and logic on a chip). **Lab assignments provide practical experience in how real design can be made.**

*After completion of the course you will:*

- understand important **principles for design** and testing of digital systems
- understand the relationship between behaviour and different construction criteria
- **be able to describe advanced digital systems at different levels of detail**
- be able to perform simulation and synthesis of digital systems.

# Course Goals and Learning Outcome

<https://www.uio.no/studier/emner/matnat/ifi/IN3160/index-eng.html>

**Goals for this lesson:**

- Know what is
  - Datapath state machines (FSMD)
- Know how to divide larger designs and state machines
  - Principles
  - Design strategies
    - Divide and conquer-

**Next lesson:**



- Diagrams and schematics?
- ~~Microcoded state machines~~
- ~~Microcoded processors~~

# Overview

- What is data path finite state machines (FSMD)?
  - Example with code and diagrams
- Factoring state machines
  - When and how do we split
- Next lesson:
  - Examples with diagrams and code

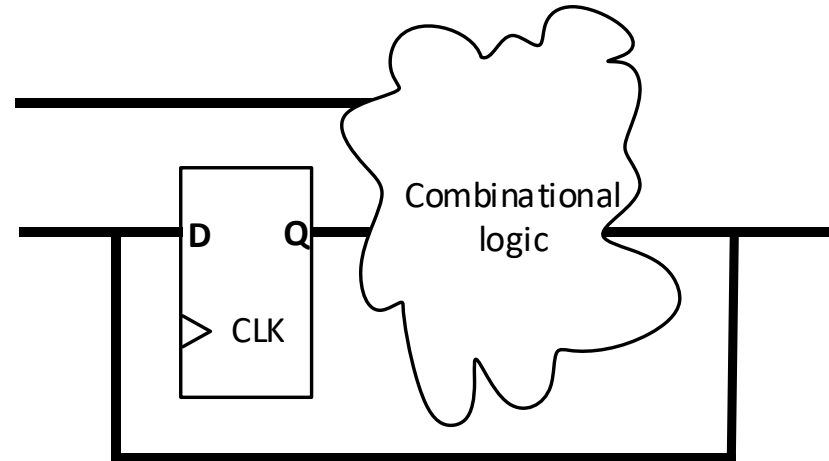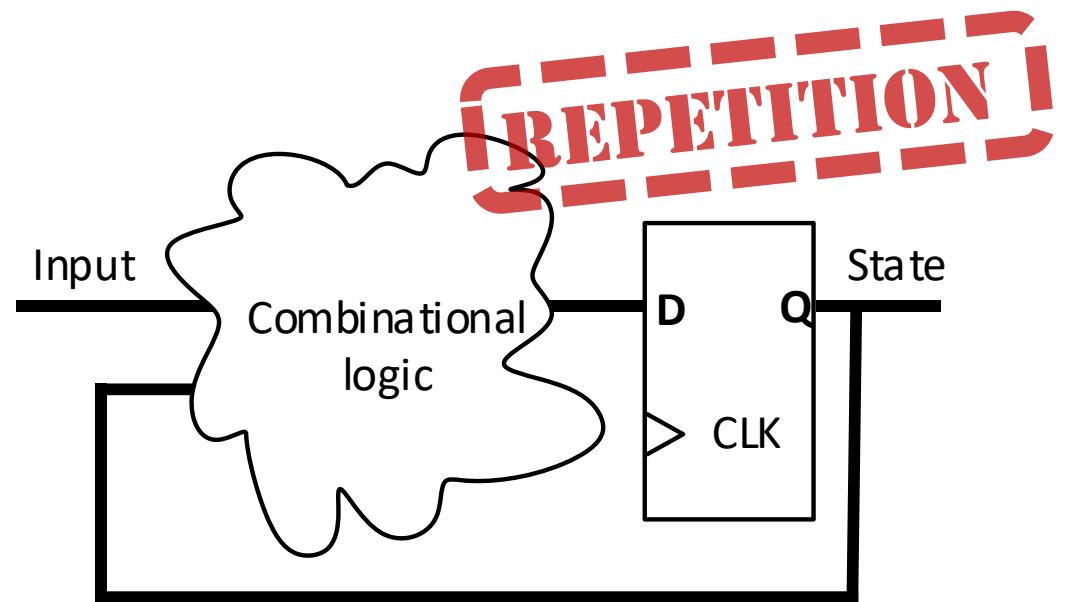
## General FSM

- General FSM
  - Combinational logic connected to registers with feedback


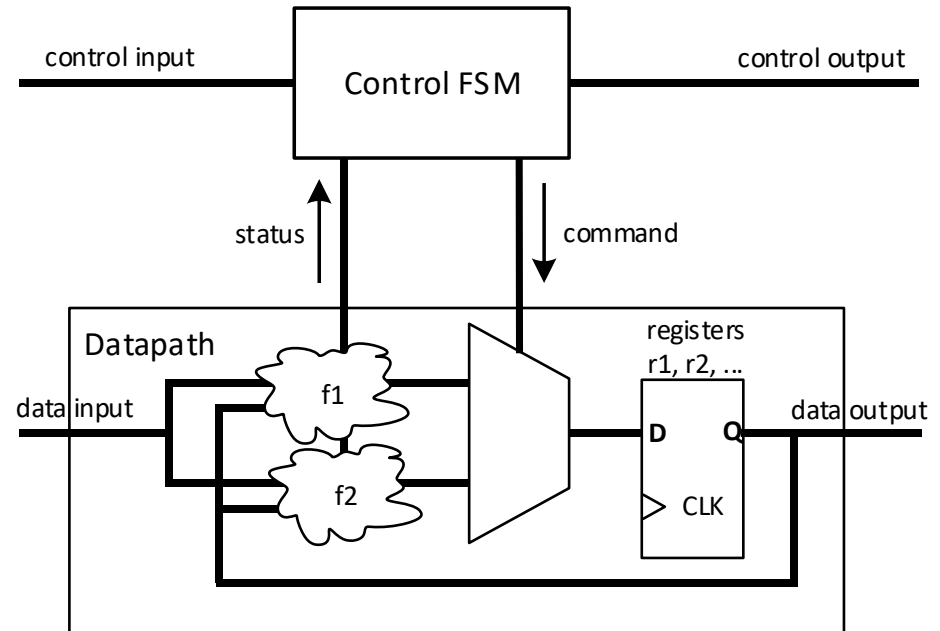
## «Datapath» FSM

- Datapath is described by a function rather than a table
  - Counters
  - Mathematical operations
  - Shift registers
  - Etc.
- We usually divide into control FSM and Datapath



# «Register operations» in data-path FSM (FSMD) -and how to deal with it


- Common notations for register operations:

- on clock edge we increment r1  $\longrightarrow$   $r1 \leftarrow r1 + 1$
- on clock edge we update r1 based on a function of register outputs  $\longrightarrow$   $r1 \leftarrow f(r1,r2)$
- on clock edge, set r1 to r2+r3  $\longrightarrow$   $r1 \leftarrow r2 + r3$

This notation can be confusing, as it implies one clock delay if it is put into an ASM chart.

Solution:

 **Use '←' for datapath only** (not for FSM)  
Know that '←' implies the use of registers that are not a part of the FSM states



# Use of register in decision box


- a)  $n$  will be updated after  $n=0$  check
- b)  $n$  will be updated after  $n=1$  check...

- Even if we want this behavior, it is poor design...
  - it seems we do not know what we are doing, as with a).

c) Do we need to introduce single cycle wait states?..

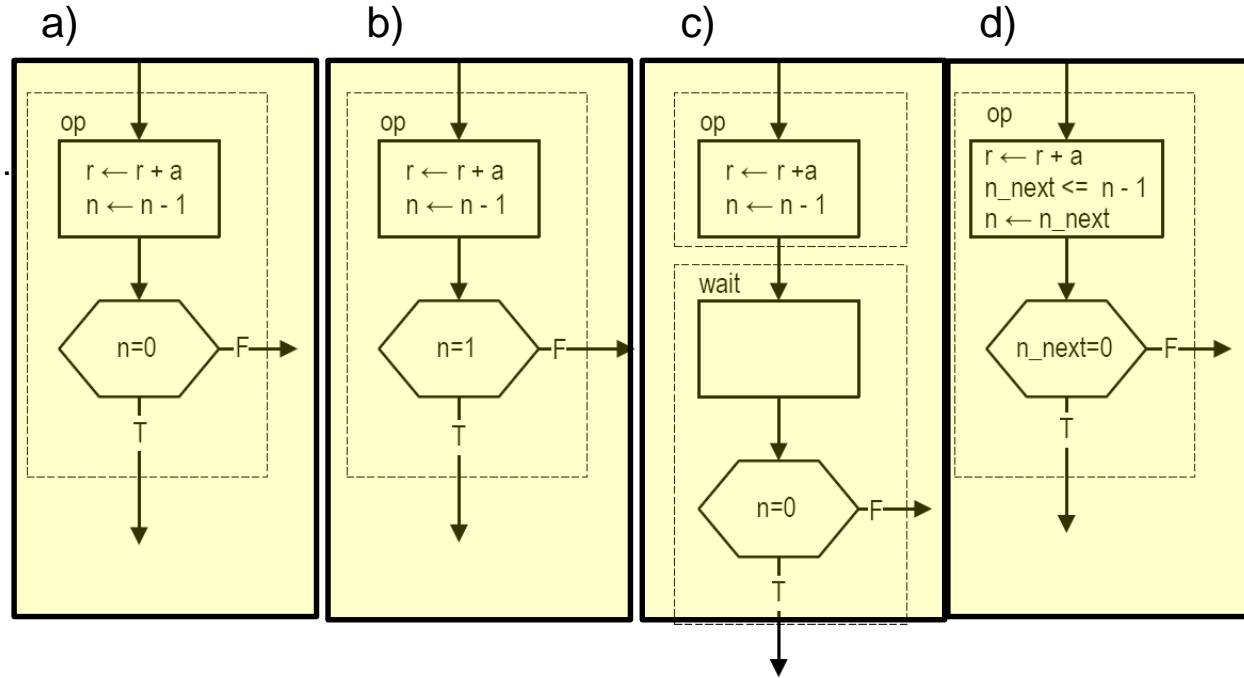d) is clear about


- **what we want** and
- **how we will do it**
- => no doubt on our intention



- Register is updated when the FSM exits current state
  - NOTE: We “exit” current state each cycle- even if we re-enter...
- => Use solution d)!
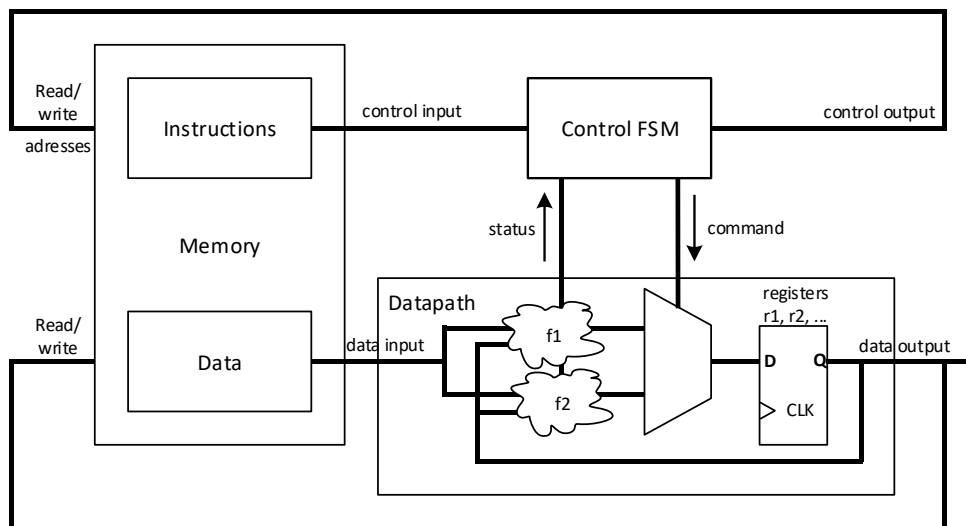
# Processor system is a datapath FSM


- Control output is memory instructions
- FSM decodes instructions and decides which part of the datapath is used
  - Pipeline flushes, stalls etc.
- Datapath contains ALU, pipeline registers etc.




 
## Example Factoring state machine with Datapath

- Exchange machine
  - Green LED ‘ready’/ can accept coins
  - Can take a number of up to 100 coins
    - Count each coin type
    - 1, 5, 10, 20 NOK
    - Close intake at maximum (! Green)
    - Close intake when counting
    - Close intake when no more coins (assume new coin each clock edge)
  - Give out the highest possible bills (assuming infinite supply)
    - 50, 100, 200 NOK
  - Return the least amount of coins
    - Use only coin from machine



## When state count is nuts...


- Millions of states possible => Cannot make «one» FSM

=> several smaller state\_machines or  
state machine + data path with registers


# Divide into models that can be conquered

- Partition by..?
  - State (FSMs vs datapath),
  - Task (counters, FSMs,...)
  - Interface (entities)


- Entity:

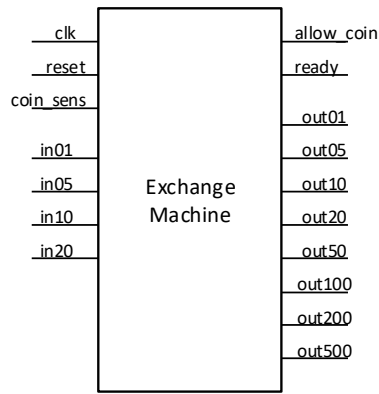

- FSM(s)

 


- Datapath

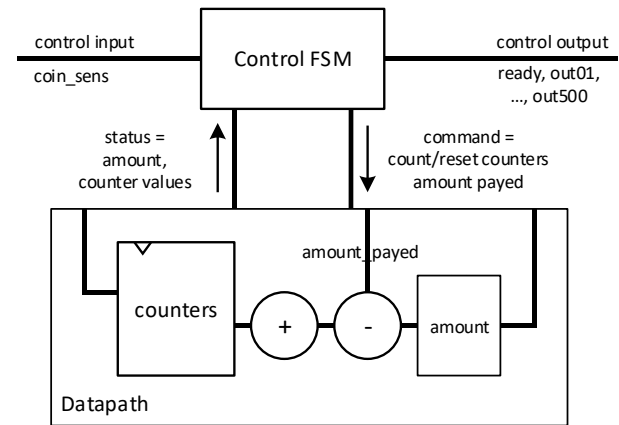


 
## Detailed datapath

- 4 counters
  - Can they be of the same type?
  - Up/ down / reset
- «Coins» and «amount»
  - Why/ why not registers?


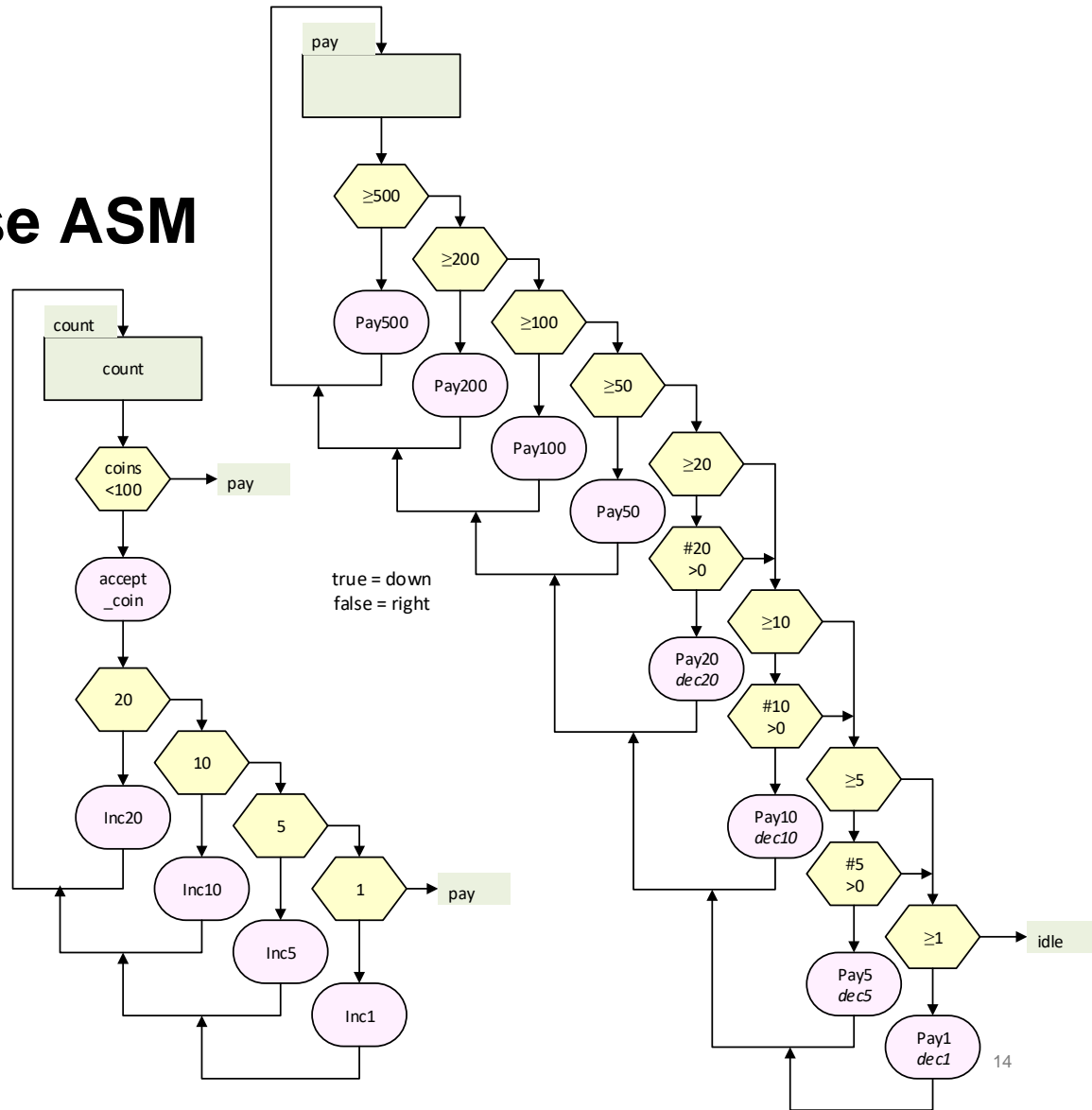 
# Detailed FSM = use ASM

- Make sure
  - all transition decisions are covered
  - all control output is set




## Reiterate and refine

- You will likely need a couple of rounds refining before deciding on VHDL modules
  - Entity
  - FSM(s)
  - Detailed datapath
  - ASM diagrams
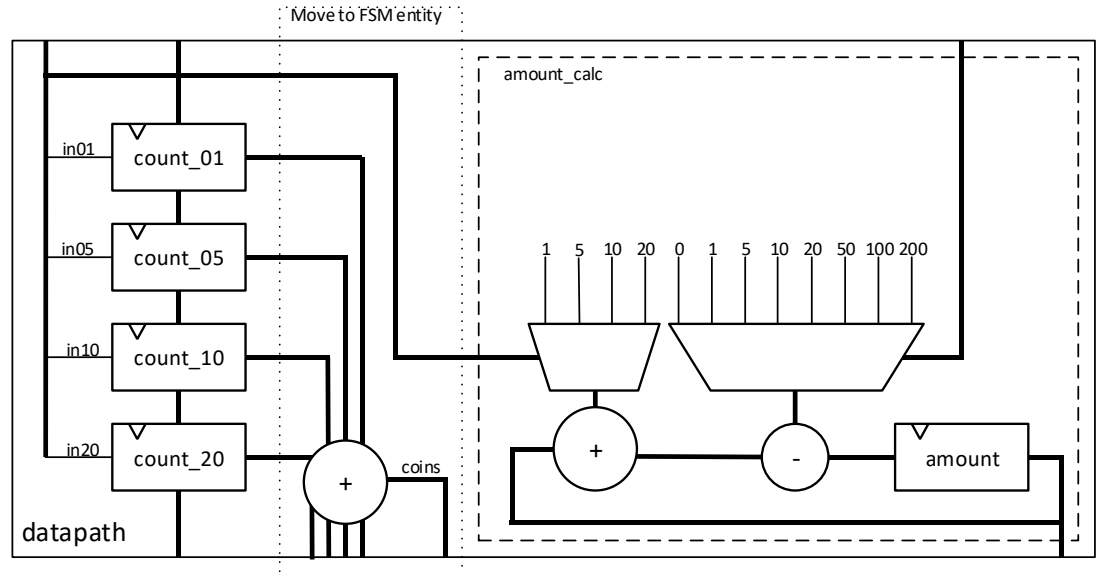
# Example reiteration

- Simpler by using
  - Only increments or decrements for amount calculation




# VHDL modules and hierarchy

- What makes a good hierarchy?
  1. Structural top
  2. RTL
  3. data flow modules
    - Complex designs may have several structural layers
      - Do not overdo this
- What makes good modules..?
  - One type of code within module
    - (Structural vs RTL vs Data Flow)
  - One purpose for each module
  - Loosely coupled / few dependencies
    - Minimum communication between modules
    - Changes can be made within one module without changing an other
  - Little or no duplicate code...
    - Use functions, loops, constants etc.
  - Scalable
- Example modules:
  - Toplevel (structural)
  - Control FSM
  - Counter(s)
    - One VHDL module, four instances
  - ~~Datapath..?~~
    - (code within toplevel...)
    - Datapath..?
  - *Amount calculation*



# Top

 

Only internal signals are connected in drawing

# Toplevel shell

- Filling in the rest should be easy once the modules are ready
- We need names for signals that go between modules.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exchange_machine is
port(
    clk, reset
        : in std_logic;
    coin_sens, in01, in05, in10, in20
        : in std_logic;
    ready, accept_coin
        : out std_logic;
    out01, out05, out10, out20
        : out std_logic;
    out50, out100, out200, out500
        : out std_logic
    );
end entity exchange_machine;

architecture toplevel of exchange_machine is
    component control_FSM is
    port(
        clk, reset : in std_logic);

    component counter is
    port(
        clk, reset : in std_logic);

    component amount_calc is
    port(
        clk, reset : in std_logic);

    -- signal decl. for communication between modules

begin
    FSM: control_FSM
    port map(
        clk => clk,
        reset => reset);

    count01: counter
    port map(
        clk => clk,
        reset => reset);

    count05: counter
    port map(
        clk => clk,
        reset => reset);

    count10: counter
    port map(
        clk => clk,
        reset => reset);

    count20: counter
    port map(
        clk => clk,
        reset => reset);

    amount: amount_calc
    port map(
        clk => clk,
        reset => reset);

end architecture toplevel;

```

# Counter

- Processes *can be* used to sort priority by order
  - OK when conditions are mutually exclusive?
- When-else can do the same sorting explicitly
  - Less need for process..

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;

entity counter is
generic(
    COUNT_WIDTH : natural := 7);
port(
    clk, reset : in std_logic;
    inc, accept : in std_logic;
    dec, zero   : in std_logic;
    count      : out unsigned(COUNT_WIDTH-1 downto 0));
end entity counter;

architecture RTL of counter is
    signal next_count : unsigned(count'range);
begin
    -- registry update
    count <= (others => '0') when reset else next_count when rising_edge(clk);

    --next count CL
    next_count <=
        count + 1 when inc and accept else
        count - 1 when dec else
        (others => '0') when zero else
        count;

end architecture RTL;
```

# amount\_calc

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;

entity amount_calc is
  generic(
    -- 100*20 = 2000 < 2048 = 2^11.
    AMOUNT_WIDTH : natural := 11);
  port(
    clk, reset          : in std_logic;
    in01, in05, in10, in20 : in std_logic;
    zero, accept_coin   : in std_logic;
    dec50, dec100, dec200, dec500 : in std_logic;
    dec20, dec10, dec05, dec01   : in std_logic;
    amount: out unsigned(AMOUNT_WIDTH-1 downto 0));
end entity amount_calc;

```

- Process + if because..

- Use of priority
- Several levels
  - Single output *can be resolved using when-else* only
    - Readability/Maintainability would suffer (...and accept\_coin x 4 )

```

architecture RTL of amount_calc is
  signal next_amount : unsigned (amount'range);
begin
  -- registry update
  amount <=
    (others => '0') when reset else
    next_amount when rising_edge(clk);

  -- CL next_amount
  process(all) is
  begin
    -- default statement:
    next_amount <= amount;
    -- conditional statements (priority doesnt matter)
    if zero then
      next_amount <= (others => '0');
    elsif accept_coin then
      next_amount <= amount + 1 when in01;
      next_amount <= amount + 5 when in05;
      next_amount <= amount + 10 when in10;
      next_amount <= amount + 20 when in20;
    else
      next_amount <= amount - 500 when dec500;
      next_amount <= amount - 200 when dec200;
      next_amount <= amount - 100 when dec100;
      next_amount <= amount - 50 when dec50;
      next_amount <= amount - 20 when dec20;
      next_amount <= amount - 10 when dec10;
      next_amount <= amount - 5 when dec05;
      next_amount <= amount - 1 when dec01;
    end if;
  end process;
end architecture RTL;

```

# FSM

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;

entity control_FSM is
generic(
    COUNT_WIDTH : natural := 7;
    AMOUNT_WIDTH : natural := COUNT_WIDTH+4;
    COIN_LIMIT : natural := 100);
port(
    clk, rese : in std_logic;
    coin_sens, in01, in05, in10, in20 : in std_logic;
    count01 : in unsigned(COUNT_WIDTH-1 downto 0);
    count05 : in unsigned(COUNT_WIDTH-1 downto 0);
    count10 : in unsigned(COUNT_WIDTH-1 downto 0);
    count20 : in unsigned(COUNT_WIDTH-1 downto 0);
    amount : in unsigned(AMOUNT_WIDTH-1 downto 0);
    ready, accept_coin : out std_logic;
    out01, out05, out10, out20 : out std_logic;
    out50, out100, out200, out500 : out std_logic;
    reset_counters, reset_amount : out std_logic);
end entity control_FSM;
```

```
architecture RTL of control_FSM is
    type state_type is (idle, count, pay);
    signal current_state, next_state : state_type;
    signal coins : unsigned(COUNT_WIDTH-1 downto 0);
begin
    -- clocked logic
    current_state <=
        idle when reset else
        next_state when rising_edge(clk);

    -- CL (moved from datapath)
    coins <= count01 + count05 + count10 + count20;

    next_state_cl: process(all) is
    begin
        -- default value prevents latches
        next_state <= current_state;
        case current_state is
            when idle =>
                next_state <= count when coin_sens;
            when count =>
                next_state <= pay when coins > COIN_LIMIT-1;
                next_state <= pay when not (in01 or in05 or in10 or in20);
            when pay =>
                -- this should be equivalent to all tests listed
                next_state <= idle when or(amount) = '0';
        end case;
    end process;

    -- more next slide...
```

## FSM 2/2

```
output_cl: process(all) is
begin
  -- default values to prevent latching
  reset_counters <= '0';
  reset_amount   <= '0';
  ready          <= '0';
  accept_coin    <= '0';
  out01         <= '0';
  out05         <= '0';
  out10         <= '0';
  out20         <= '0';
  out50         <= '0';
  out100        <= '0';
  out200        <= '0';
  out500        <= '0';
```

NOTE: with this prioritisation order, the sequence becomes more complex than necessary.

- Readability?
  - What would happen if we mixed next\_state CL into the output CL?
- Default values for all signals
  - => no latches
    - No need for **else** after **when** or **if** since default clause will apply.
- Use «if» to sort priorities, when having multiple conditions and multiple outputs
  - That are depending on each other..


```
case current_state is
when idle =>
  reset_counters <= '1';
  reset_amount   <= '1';
  ready <= '1';
when count =>
  accept_coin <= '1' when coins < COIN_LIMIT;
when pay =>
  if amount >= 500 then out500 <= '1';
  elsif amount >= 200 then out200 <= '1';
  elsif amount >= 100 then out100 <= '1';
  elsif amount >= 50 then out50 <= '1';
  elsif amount < 50 and amount >= 20 then
    if count20 > 0 then out20 <= '1';
    elsif count10 > 0 then out10 <= '1';
    elsif count05 > 0 then out05 <= '1';
    else out01 <= '1';
    end if;
  elsif amount < 20 and amount >= 10 then
    if count10 > 0 then out10 <= '1';
    elsif count05 > 0 then out05 <= '1';
    else out01 <= '1';
    end if;
  elsif amount < 10 and amount >= 5 then
    if count05 > 0 then out05 <= '1';
    else out01 <= '1';
    end if;
  elsif amount < 5 and amount >= 1 then
    out01 <= '1';
  end if;
end case;
end process;

end architecture RTL;
```

true = down  
false = right  
A = amount
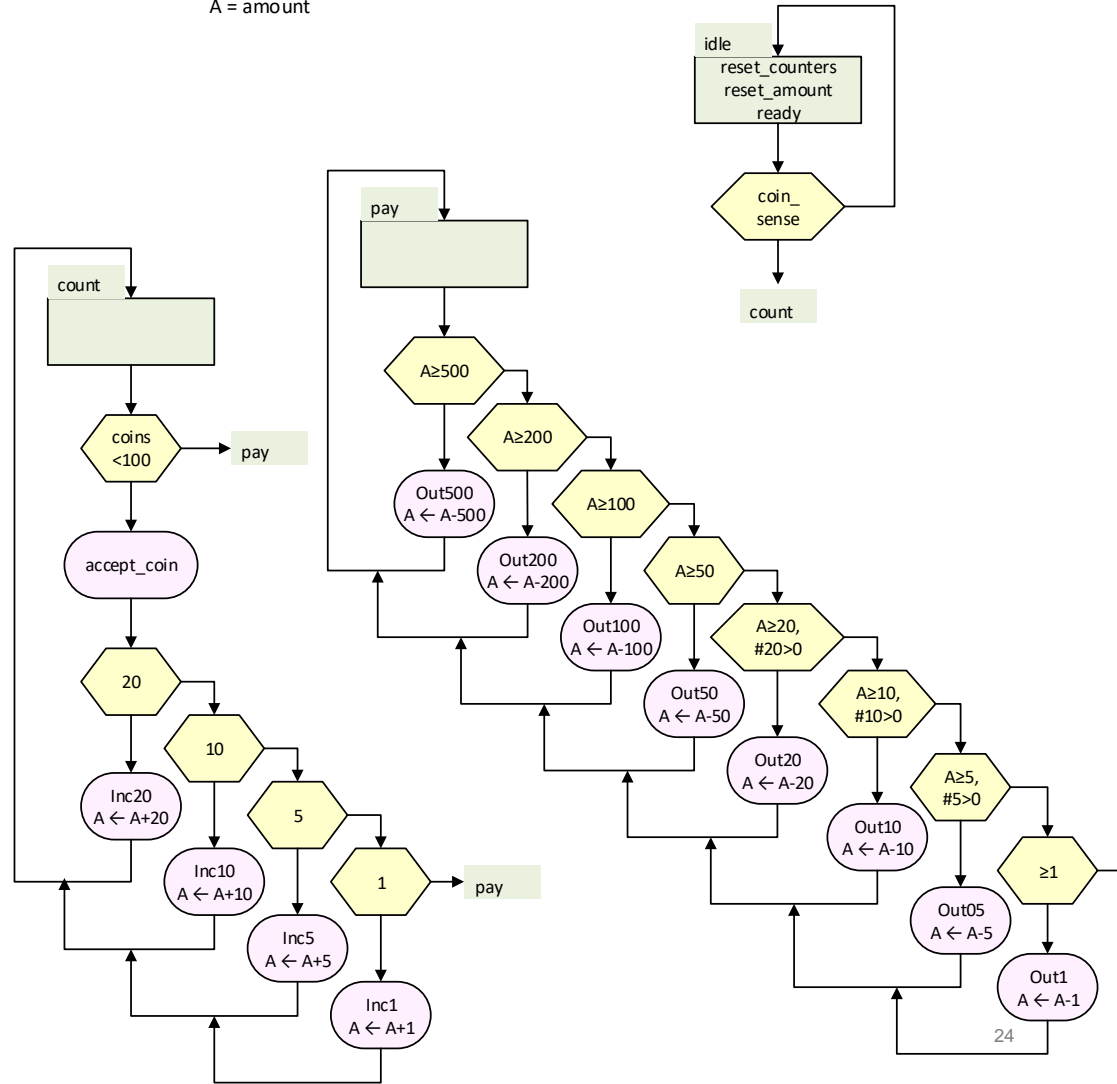
# Recap ASMD

- D for datapath ASM
- '←' in a Mealy box?
  - OK because the register is a part of the data path (*and not the FSM itself*)
- Can we go without '←' ?
- Should we?




**REPETITION**

# «Register operations» in data-path FSM (FSMD) -and how to deal with it

- Common notations for register operations:
  - on clock edge we update r1 based on a function of register outputs
  - on clock edge we increment r1,
  - on clock edge, set r1 to r1+r2

$$r1 \leftarrow r1 + 1$$
$$r1 \leftarrow f(r1,r2)$$
$$r1 \leftarrow r2 + r3$$

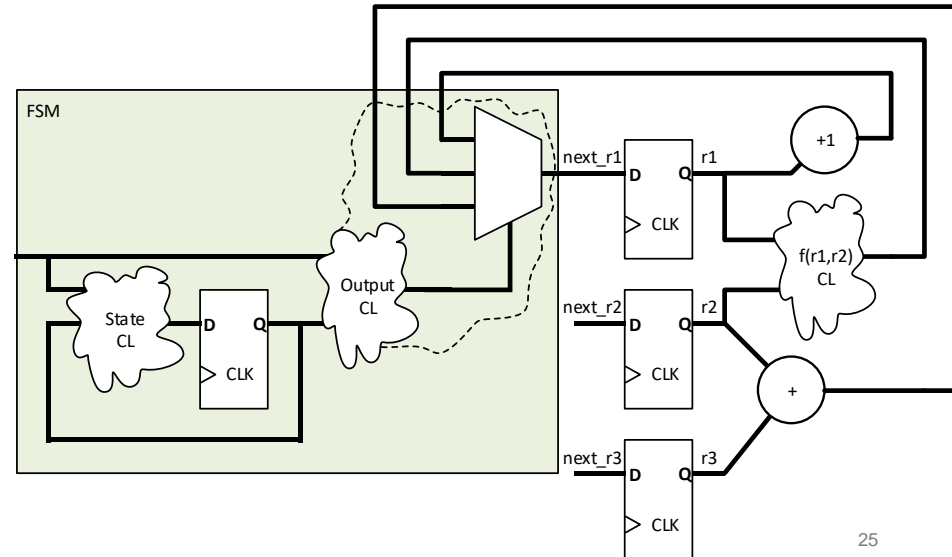- This notation can be confusing, as it implies one clock delay if it is put into an ASM chart.
- Solution:
  - Use ' $\leftarrow$ ' for datapath only (not for FSM)
  - Know that ' $\leftarrow$ ' implies the use of additional registers





## Suggested reading

- D&H:
  - 17 p 375 - 393
  - 21 p 467 – 477
- Hva nå? <=  
next\_page **when** time\_left > 15 min **else** questions ..?

# Pushbutton register storage (not in Oblig 6 2021)

- All storage elements should be clocked!
- *should reset have top priority?*
  - Use asynchronous reset for the time being (topic for later)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```


```
entity my_reader is  
port(  
    clk, reset : in std_logic;  
    enable : in std_logic;  
    input : in std_logic_vector(7 downto 0);  
    output : out std_logic_vector(7 downto 0);  
);  
end entity my_reader;
```

```
process(all) is  
begin  
    if enable then  
        output <= input;  
    else if reset then  
        output <= "00000000";  
    end if;  
end process;
```

```
architecture single_process of my_reader is  
begin  
    process(clk, reset) is  
begin  
        if reset then  
            output <= (others => '0');  
        elsif rising_edge(clk) then  
            output <= input when enable;  
        end if;  
    end process;  
end architecture;
```


 
```
architecture two_statement of my_reader is  
    signal next_out: std_logic_vector(7 downto 0);  
begin  
    process(clk, reset) is  
begin  
        if reset then  
            output <= (others => '0');  
        elsif rising_edge(clk) then  
            output <= next_out;  
        end if;  
    end process;
```



```
-- latched input: Don't do this  
next_out <= input when enable / else next_out* / ;
```


```
-- CL alternative  
with enable select next_out <=  
    input when '1',  
    output when others;
```

```
end architecture FSM_style;
```


# Pushbutton register storage

- Can be seen as a single state storage operation

- With default value

 

- Without default

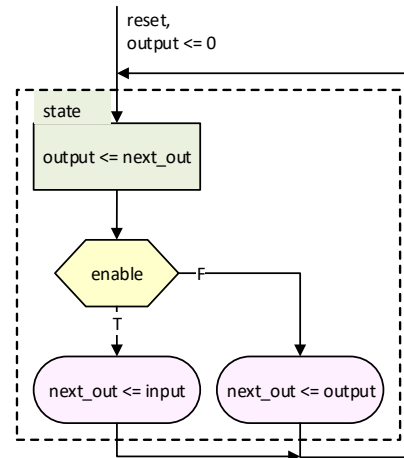

- As a register operation

