

UiO : **Department of Informatics**  
University of Oslo

**IN3160 IN4160**  
**Diagrams,**  
**Yngve Hafting**

**Reset circuits, ASMD/ desing example**



In this course you will learn about the **design of advanced digital systems**. This includes programmable logic circuits, a hardware design language and system-on-chip design (processor, memory and logic on a chip). Lab assignments provide practical experience in how real design can be made.

*After completion of the course you will:*

- understand important **principles for design** and testing of digital systems
- understand the relationship between behaviour and different construction criteria
- **be able to describe advanced digital systems at different levels of detail**
- be able to perform simulation and synthesis of digital systems.

# Course Goals and Learning Outcome

<https://www.uio.no/studier/emner/matnat/ifi/IN3160/index-eng.html>

**Goals for this lesson:**

- Be able to read, use and create -diagrams
  - Timing-/ waveform-
  - Datapath-
  - Block-
  - State-
  - ASM-,
  - ASMD
- Know the purpose of reset circuits
  - Why do we reset at all?
  - What are potential pitfalls for reset handling?
- Practice in reading code
  - Design considerations



**Next lesson: Microcoded FSMs**

## Wave diagrams

- When do we read clocked signals?
- When does assignment occur?
- Does phase matter?

  
# Basic wave diagram layout

- Undefined values are usually hatch-patterned
- Single bit signals
  - Are usually displayed as high ('1') or low ('0')
  - Defined signals of arbitrary values are usually shown as an area without hatching
    - Can be named (here a, b)
- Multi-bit is usually shown as an area
  - Values or names are often used
  - Multi-bit vector vs single-bit signal
    - Sometimes you must use context to understand which is which.
- Edges
  - Both vertical and slanted edges mean the same.
    - *Hand drawing mostly vertical...*
  - Normally sequential logic relate to the rising\_edge
  - RTL-simulation of sequential logic:
    - Signals are read when edge occurs
    - Signals are assigned immediately after the edge


 
# Basic wave diagram layout


- Combinational logic (CL) responds immediately when input changes




- Sequential logic (clocked circuits)
  - responds to the **input status** present *when the clock edge occurs*.
  - output** is changed *immediately after* the clock edge occurs.
    - Unless specific timing information is given
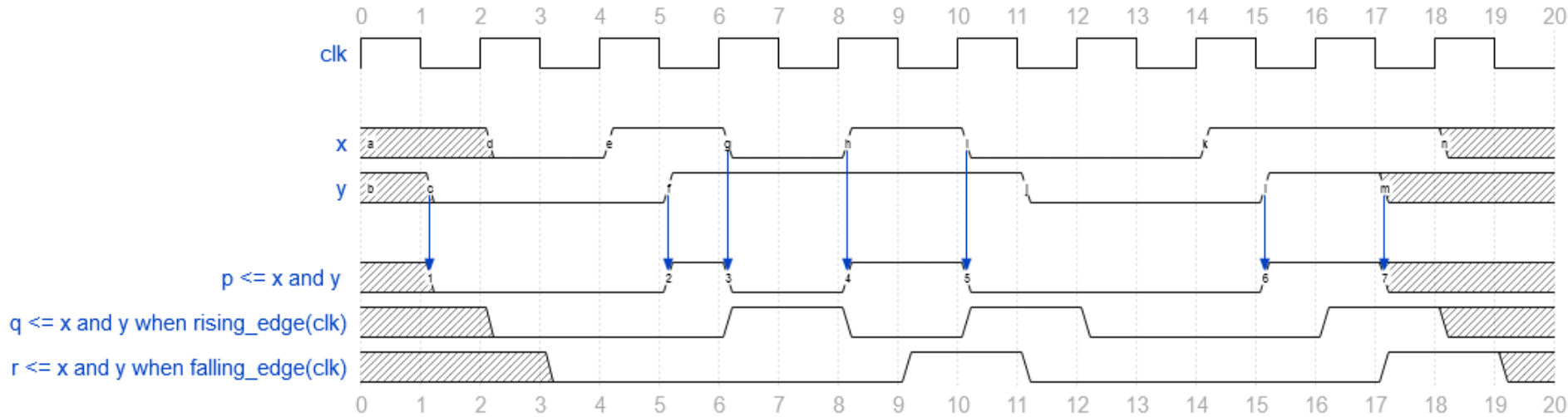
## Waveform combinational

- Combinational response is immediate in a waveform.
  - *Timing diagrams will show gate delays*
  - *Clock does not matter*




## Sequential logic, rising\_edge

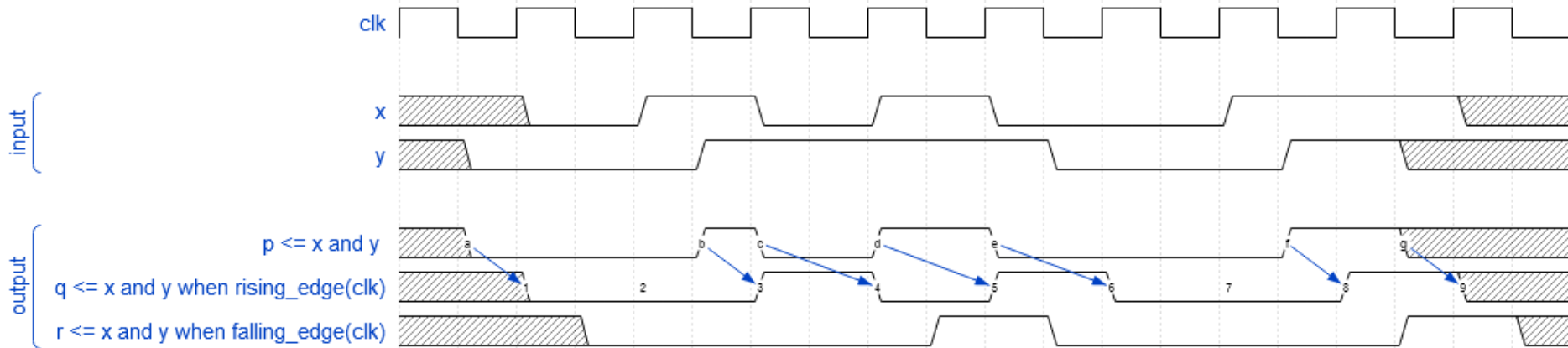

– Look at what the input status **was** when the clock edge occurs.

- Here: The b-c pulse activates q for one whole clock cycle
  - even though (a and b) is high for a shorter duration
    - Only what is present when the clock edge occurs matters

## Sequential logic, falling\_edge

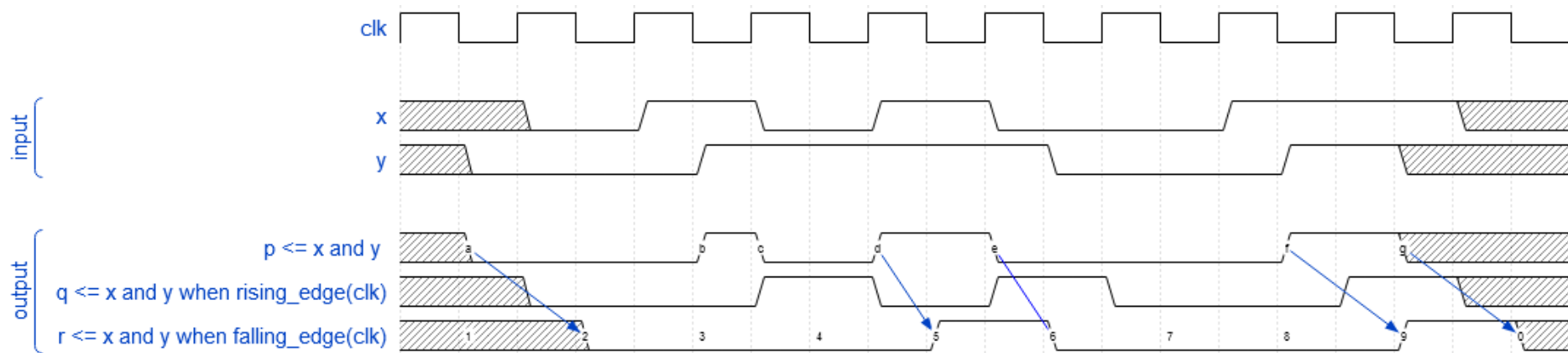

- Here: The b-c pulse is too short to activate r
  - (a and b) is low on the next falling edge




## Timing diagrams


- = Waveforms with timing information for a specified circuit.
  - Typically found in a data sheets
    - Printed circuit boards (PCBs),
    - components (chips)
    - communication protocol standards
  - Can be generated when doing post-synthesis simulation.
  - Useful...
    - .. when considering *setup and hold timing requirements* in a system
      - selecting circuits for a PCB (Printed Circuit Board)
    - .. when optimizing data-flow circuitry..
      - High performance ASIC design
- *So far today: no timing information given (only RTL sim)*
 
# Block diagrams

- Shows how modules are connected *or* communicate
  - Level of detail may vary
  - May include
    - digital and analog components
- Suited for system level overview
  - Or partial overview
  - May* be used for connection




Oblig 6 diagram

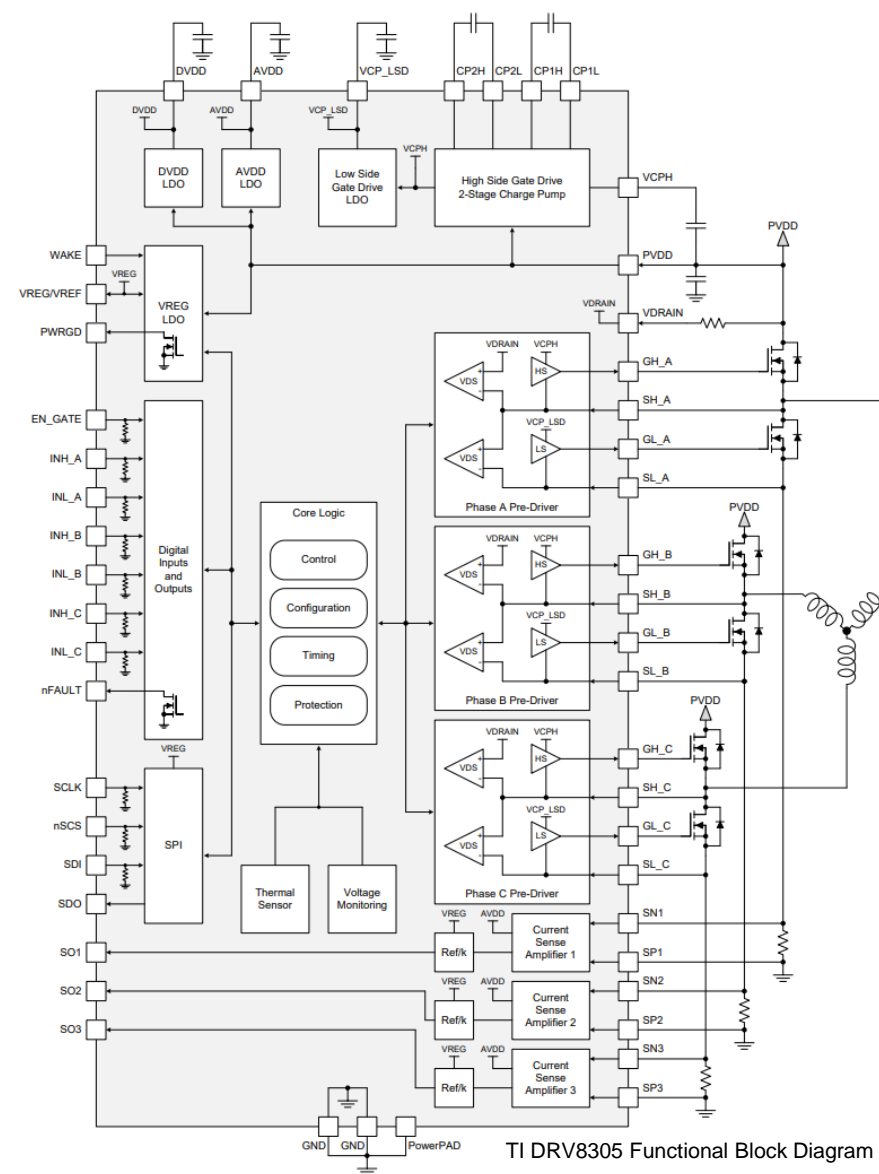


TI DRV8305 Functional Block Diagram
 
# Block diagrams

- Many variants...
  - Entire- or parts of systems
  - *HW block diagrams tend to be more detailed than those used for other purposes (SW, business, ...)*
- *Usually the first diagrams drawn in a design process*
  - Several may be added and edited later
- Almost always present in design documentation.



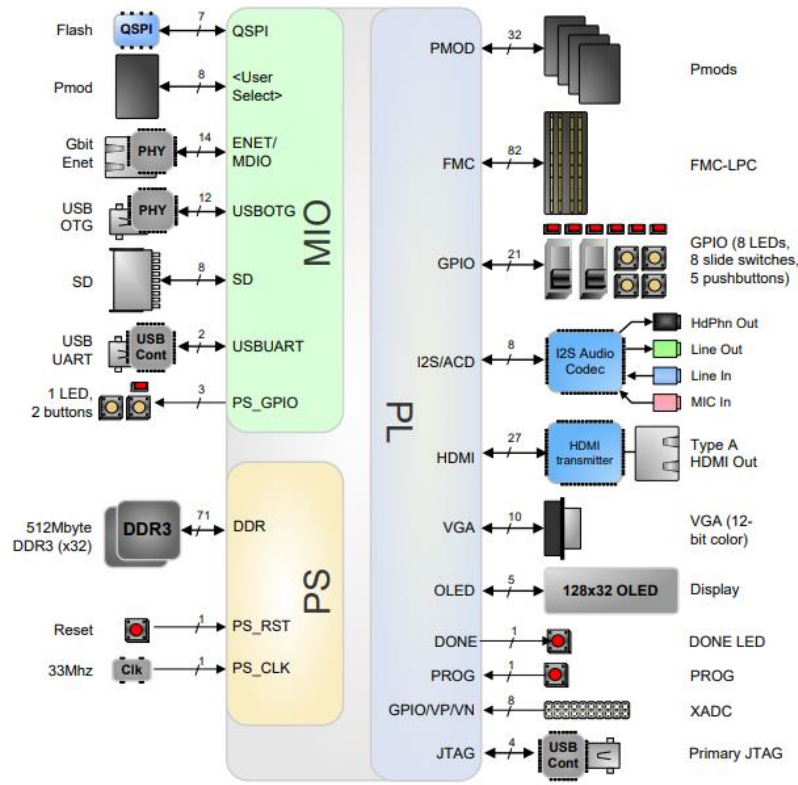
[https://commons.wikimedia.org/wiki/File:Windows\\_2000\\_architecture.png](https://commons.wikimedia.org/wiki/File:Windows_2000_architecture.png)



ZYNQ XC7Z020-CSG484


ZedBoard Block Diagram

← ↑ Zedboard Users guide

 



USB-UART Bridge Interface

# Datapath Diagrams

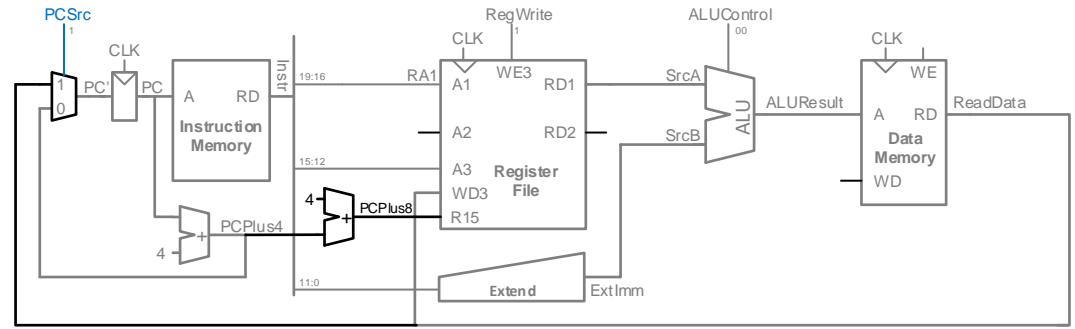

- A specialised block diagram that **show how data moves within a system or module.**
- Should normally contain
  - How data travels between modules or functional units
  - Registers (flipflops) used for storing data (not FSM - registers)
  - Bit widths for each path
- Usually direction of travel is from left to right
- Modules, such as **FSMs** will contain **registers**, however these registers **are considered control**, and *not a part of the datapath*.
  - I.e. A processor may have many states but data still moves through the pipeline one stage at a time.
  - (Thus we have non datapath modules using clk.)

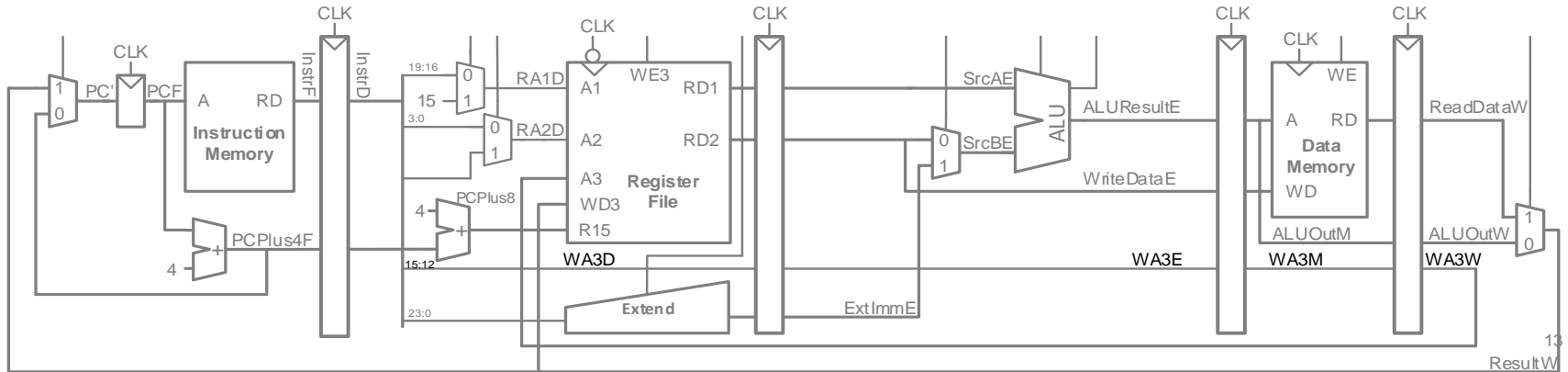

 

- Often used to describe parts of an architecture
- RTL logic *can* be represented using datapath diagrams
  - It is not necessarily the best representation...
    - FSMs are better described using ASM diagrams...
    - Counters..
    - LFSR..
- Drawing a datapath diagram will in some cases be a very efficient way to gain understanding..
  - => Pipelining
    - **Example:** Exam 2021, Assignment 6 (next page)-

# Example: Exam 2021 Assignment 6, «Pipelining»

- The pipelined module entity is described above.
- In this assignment a module which **calculates result = a+b+c** shall be implemented.
- In order to meet timing closure at the required frequency, **pipelining shall be used.**
- All input are synchronized to the clock signal clk.
- Reset can be either synchronous or asynchronous.
- The implementation shall be synchronous to the clock signal clk.
- **All output should be driven by registers** to avoid propagating hazards.
- The computation shall use unsigned arithmetic operation on the operands a, b and c.
- *When the start signal is high the computation shall start, and the result\_valid signal shall be high when valid data is present on the result signal.*
- Implement the architecture for the pipelined module.


```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
entity pipelined is  
port (  
  clk : in std_logic;  
  rst : in std_logic;  
  a : in std_logic_vector(7 downto 0);  
  b : in std_logic_vector(7 downto 0);  
  c : in std_logic_vector(7 downto 0);  
  result : out std_logic_vector(9 downto 0);  
  start : in std_logic;  
  result_valid : out std_logic  
);  
end entity pipelined;
```

- We read this as the control signal shall be pipelined along with the data
  - It is not necessary to block computation when there is no start signal.
- NOTE: It does not make sense to pipeline unless a, b, c and the control signal follows each other.
  - I.e: expect new data each clock cycle
- *Make your own datapath diagram for this task (2 min)!*

# Ex2021-pipelining

- VHDL code may come in many flavours:

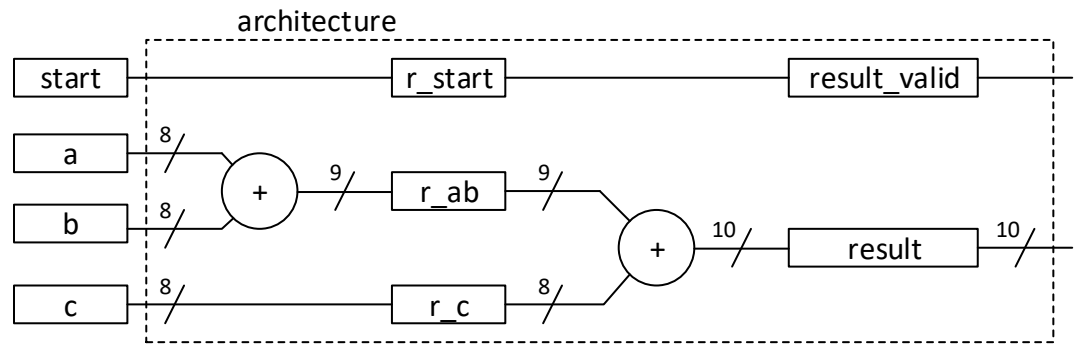





```
architecture RTL of pipelined is
begin
  pipeline: process(rst, clk) is
    variable r_start : std_logic;
    variable r_c : unsigned(7 downto 0);
    variable r_ab : unsigned(8 downto 0);
  begin
    if rst then
      r_start := '0';
      r_c := (others => '0');
      r_ab := (others => '0');
      result <= (others => '0');
      result_valid <= '0';
    elsif rising_edge(clk) then
      -- Note: Variables must be used before being
      -- assigned to form registers...
      result <= std_logic_vector("00" & r_c + "0" & r_ab);
      result_valid <= r_start;
      r_start := start;
      r_ab := ("0" & unsigned(a) + "0" & unsigned(b));
      r_c := unsigned(c);
    end if;
  end process;
end architecture RTL;
```

```
architecture RAW of pipelined is
  signal r_c : unsigned(7 downto 0);
  signal r_ab : unsigned(8 downto 0);
  signal r_start : std_logic;
begin
  r_start <= '0' when rst else start when rising_edge(clk);
  result_valid <= '0' when rst else r_start when rising_edge(clk);
  r_ab <= (others => '0') when rst else ("0" & unsigned(a) + "0" & unsigned(b)) when rising_edge(clk);
  r_c <= (others => '0') when rst else (unsigned(c)) when rising_edge(clk);
  result <= (others => '0') when rst else std_logic_vector("00" & r_c + "0" & r_ab) when rising_edge(clk);
end architecture RAW;
```

- Getting to this code should be doable when having the diagram...
- Common mistakes:
  - Forgetting to put c in pipeline before calculating step 2.
  - Believing start shall be valid for 3 clock cycles...
  - Attempting SW-style loops(!)..
    - Think of VHDL as a circuit description language...
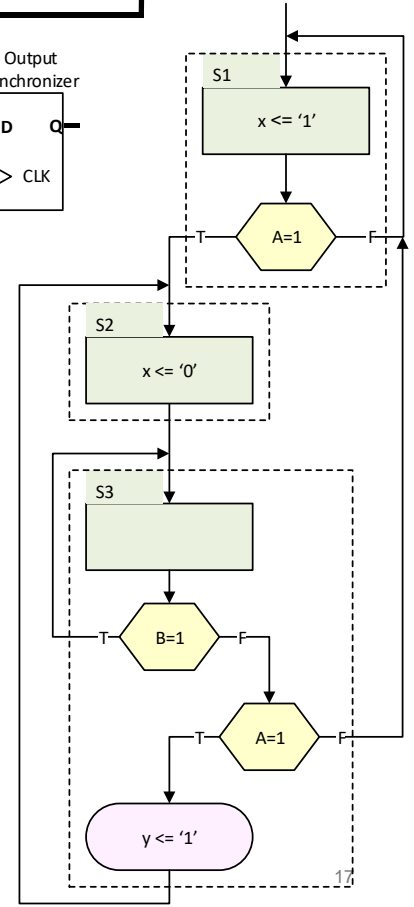 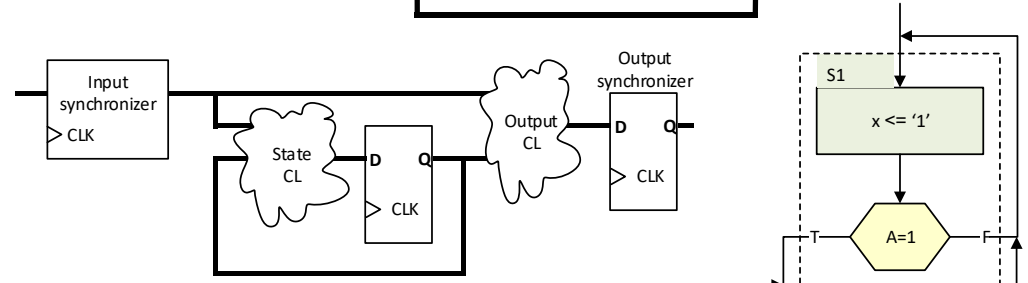 
# FSMs and their diagrams


- Datapath shows
  - Moore vs Mealy machine
  - Synchronizers
  - ...
- State- and ASM diagrams
  - Shows state transitions
    - conditions (and priority)
  - Output
  - Register operations (ASMD)





 
# State diagram

- States
- Transitions between states
- Beside transition arc:
  - Decision parameter
  - / Mealy output
- Inside bubble:
  - Moore output
- Frequently used, but not always with all parameters.
- Note: *Default values often omitted*
  - Here: default:  $x, y = 0$  (boolean false)



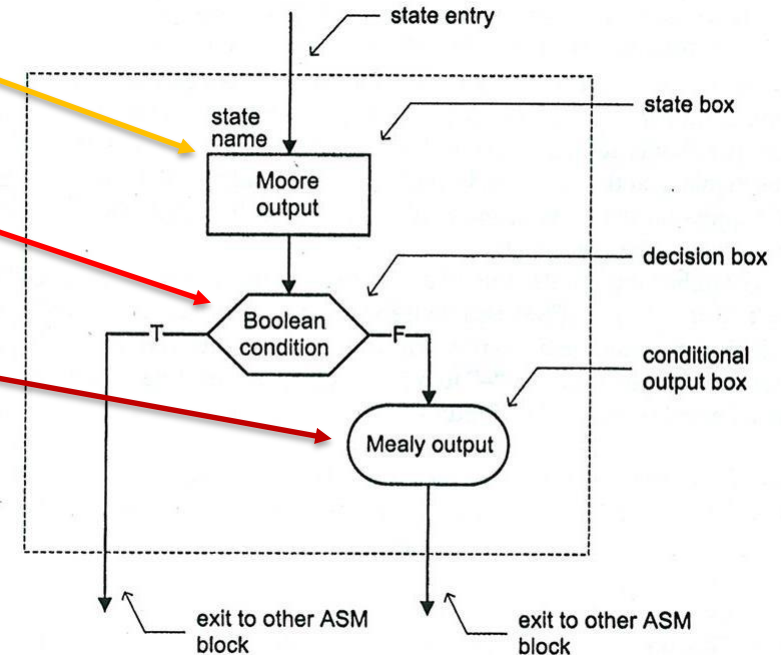
# ASM (Algorithmic State Machine) block

- The **state box** represents a state in the FSM,
  - State based output is shown inside (i.e. the **Moore outputs**).
- The **decision box** tests an input condition to determine the exit path of the current ASM block.
- A **conditional output box** (“**Mealy box**”)
  - lists conditionally asserted signals.
  - Can only be placed after an exit path of a decision box
  - (i.e. the **Mealy outputs** that depends on the state and input values).


 
## «Datapath» FSM

- Datapath is described by a function rather than a table
  - Counters
  - Mathematical operations
  - Shift registers
  - Etc.
- We usually divide into control FSM and Datapath



# «Register operations» in data-path FSM (FSMD) -and how to deal with it


- Common notations for register operations:

- on clock edge we increment r1  $\rightarrow r1 \leftarrow r1 + 1$
- on clock edge we update r1 based on a function of register outputs  $\rightarrow r1 \leftarrow f(r1,r2)$
- on clock edge, set r1 to r2+r3  $\rightarrow r1 \leftarrow r2 + r3$

This notation can be confusing, as it implies one clock delay if it is put into an ASM chart.


Solution:

 **Use '←' for datapath only** (not for FSM)  
Know that '←' implies the use of registers that are not a part of the state machine



## Other drawings or schematics

- System sketches, drawings
  - Usually used to display a concept or an idea
  - Can be anything (*vague block diagram..?*)
- Circuit diagrams
  - Show how the current flows in a circuit
  - Netlists can be made from VHDL
    - (and then turned into circuit diagrams)

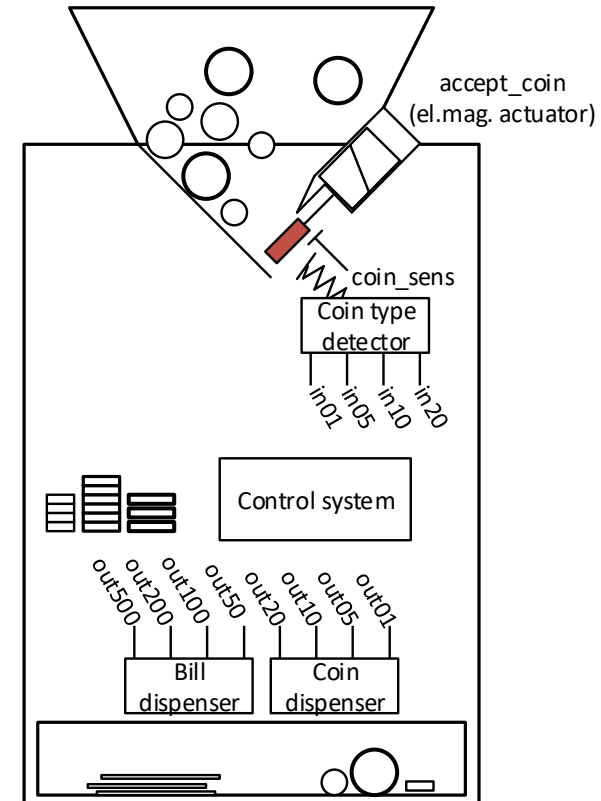

**IN3160**

**Reset circuits**

Synchronous or Asynchronous reset?




# Outline

- Combinational logic and floating pins
- Why reset?
- Asynchronous reset
- Synchronous reset
- Reset circuits
 
## Combinational logic and I/O pins

- No need for reset circuitry for CL
  - No values are stored in CL
  - Setting the input will give the desired output
- However... avoid floating gates
  - Floating gates may cause power surges and noise
  - All input pins should be driven
    - Potentially unconnected inputs should be pulled high or low
      - Pull-up or pull-down on PCB or
      - FPGAs may have internal pull up/down circuitry for IO-pins.
        - » *Can be a life saver... (Product/ project / etc).*







# Why reset?

- Avoid unpredictable behavior during startup
  - Metastability creating unpredictable results
    - Both in our system and surrounding systems
  - Random register values may lead to undesired or illegal states
    - Lockup – states with no exit
    - undesired output can have unpleasant consequences
- To get out of illegal states
  - Unpredicted behaviour may lead to illegal states
  - Noise
    - Crosstalk / EMP
    - Radiation - both thermal and radioactive
    - Floating gates
- ... To ensure verifiable predictability ...
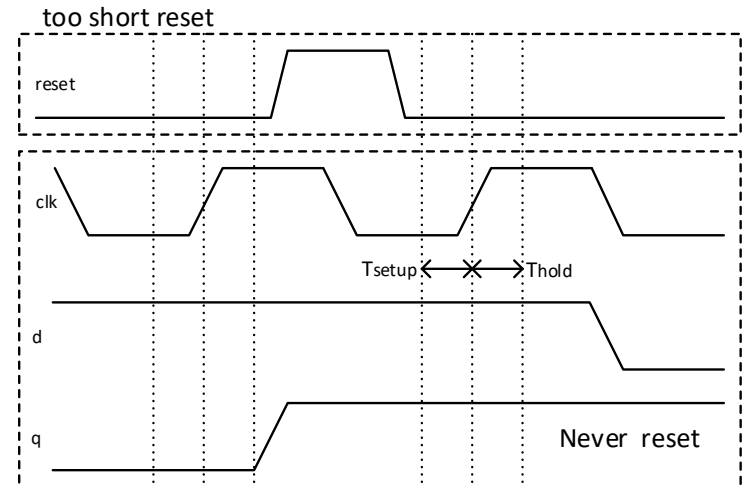 
# Synchronous reset

- Externally activated resets are per definition asynchronous
  - Synchronization is needed.
- Synchronous reset 'and flip-flop input
  - Added logic can add to critical path
  - FPGA primitives may have this option built in.
- Reset pulses coming from faster clock domains may be missed entirely.



```
next_q <= '0' when reset else d;  
q <= next_q when rising_edge(clk);
```


  
# Asynchronous reset


- Asynchronous assertion will always trigger
  - Reset duration must be longer than setup+hold...
- Asynchronous deassertion may cause metastability
  - Deassertion during setup/hold period

```
q <= '0' when reset else d when rising_edge(clk);
```



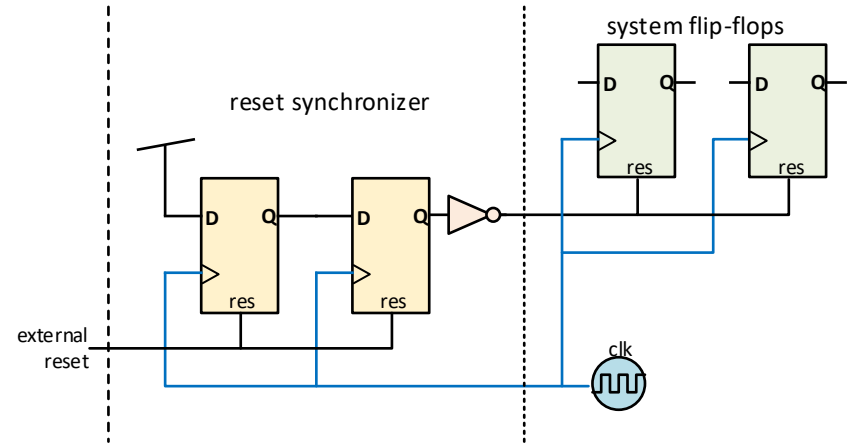
# Reset circuit(s)

- Asynchronous assertion,  
Synchronous deassertion
  - Short reset pulses will trigger
  - 2FF mitigates metastability
    - More in clock domain crossing lecture...
- Pitfalls?
  - Hazards => random reset
  - This circuit should not be used unless external reset is hazard-free.
- Multiple sources for reset?
  - Ensure resetpulses are long enough
  - Use Synchronous reset
    - 2FF when crossing domains


 
```
ff1 <= '0' when ext_reset else '1' when rising_edge(clk);  
ff2 <= '0' when ext_reset else ff1 when rising_edge(clk);  
reset <= not ff2;
```



## Resets in IN3160

- All designs should start in a known state
  - Predefined values for all registers, no metastability.
  - Well implemented reset functionality ensures this.
    - Can be invoked both at start and later
- The FPGAs *we use* are RAM based and
  - will always start in a predictable configuration
  - => We *can* start without using reset
    - Default state is '0' (*the FPGA's we use*)
- Not using reset at start is an exception
  - Reset functionality should always be implemented
  - There is no guarantee for (other) designs to be safe without implicit initialization
  - *If we do not have a predefined source for reset signals, use one button...*

## Reset summary

- External reset is asynchronous
  - Should be synchronized to avoid causing metastability.
- It is OK to use asynchronous reset once synchronized...
  - Once synchronized, synchronous reset is perfect...
    - Some FPGA primitives prefer synch reset only.
- Reset pulse must be long enough for reset circuitry  
*(depends on technology / logic family, not clk frequency..)*

**Non-FSM example with ASMD diagram**  
(Theory covered earlier)



# Example: Decade counter

```
entity dec_count is
  port (
    Clock,
    Reset,
    Enable,
    Load,
    Mode : in Std_logic;
    Data : in Std_logic_vector(7 downto 0);
    Count : out Std_logic_vector(7 downto 0));
end;
```

```
architecture doullos_model_solution of dec_count is
  constant nibble_max : Unsigned(3 downto 0) := "1111";
  constant decade_max : Unsigned(3 downto 0) := "1001";
  constant zero_nibble : Unsigned(3 downto 0) := "0000";
  constant zero_byte : Unsigned(7 downto 0) := "00000000";
  signal Q : Unsigned(7 downto 0);
begin
  process (Clock, Reset)
  begin
    if Reset = '0' then
      Q <= zero_byte;
    elsif RISING_EDGE(Clock) then
      if Enable = '0' then
        if Load = '0' then
          Q <= Unsigned(Data);
        elsif (Mode = '0' and Q(3 downto 0) /= nibble_max) or
              (Mode = '1' and Q(3 downto 0) /= decade_max) then
          Q(3 downto 0) <= Q(3 downto 0) + 1;
        else
          Q(3 downto 0) <= zero_nibble;
          if (Mode = '0' and Q(7 downto 4) /= nibble_max) or
              (Mode = '1' and Q(7 downto 4) /= decade_max) then
            Q(7 downto 4) <= Q(7 downto 4) + 1;
          else
            Q(7 downto 4) <= zero_nibble;
          end if;
        end if;
      end if;
    end process;
    count <= Std_logic_vector(Q);
  end;
```

Enable	Load	Mode	Next Count
0	0	X	Data
0	1	0	Count+1 (bin)
0	1	1	Count+1 (dec)
1	X	X	Count

- Critique design**

  - Readability
    - Uses negative logic
    - «Mode» requires explanation
  - Portability
    - Asynchronous reset

**Critique implementation**


  - Readability
    - Mix of CL and register storage
    - If-based...
    - CL style assignment in clocked process
  - Maintainability
    - Not scaleable
    - Duplicate code
      - For each nibble



## Decade counter

- A new slightly different design:
  - Synchronous reset
  - High and low indicators
  - Hazard free output
    - **all output in registers**
  - Positive logic
    - enable
    - load
    - decade (nbinary)
    - up (ndown)
  - **Generic ?**
    - *Will be bound by 4bit nibble size*
- New implementation
  - Separate CL and register assignment
- But first:
  - Diagrams & tables
    - Entity
    - ASMD
      - *Algorithmic state machine with data path*

# 8 bit decade counter

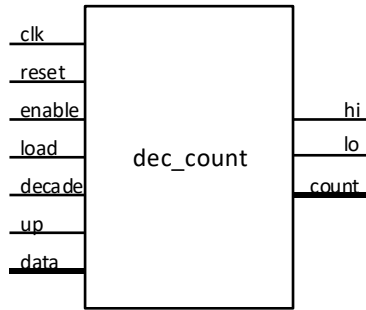


- load, up/down, dec/bin
  - Indicates function
- High/low signal

- Counter
  - not considered FSM
    - State is only by counter value
    - Input and counter value decides output
      - No real state storage
  - More than just counting
    - Complex decision tree
      - Suitable for *data path diagram*
      - *ASMD for the sake of instruction*


enable	load	decade	up	next_count
0	X	X	X	count
1	1	X	X	data
1	0	0	1	count+1 (bin)
1	0	0	0	count-1 (bin)
1	0	1	1	count+1 (dec)
1	0	1	0	count-1 (dec)

decade	count	high	low
X	0x00	0	1
0	0x01-0xFE	0	0
0	0xFF	1	0
1	0x01-0x98	0	0
1	0x99	1	0
1	0xA0-0xFF	1	1

# Datapath and ASMD



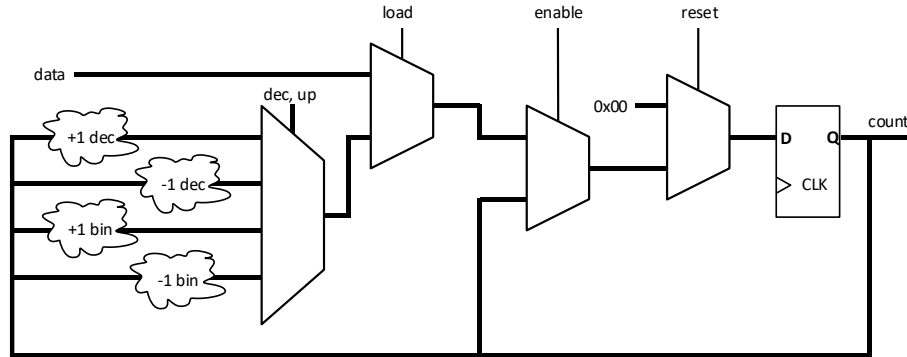


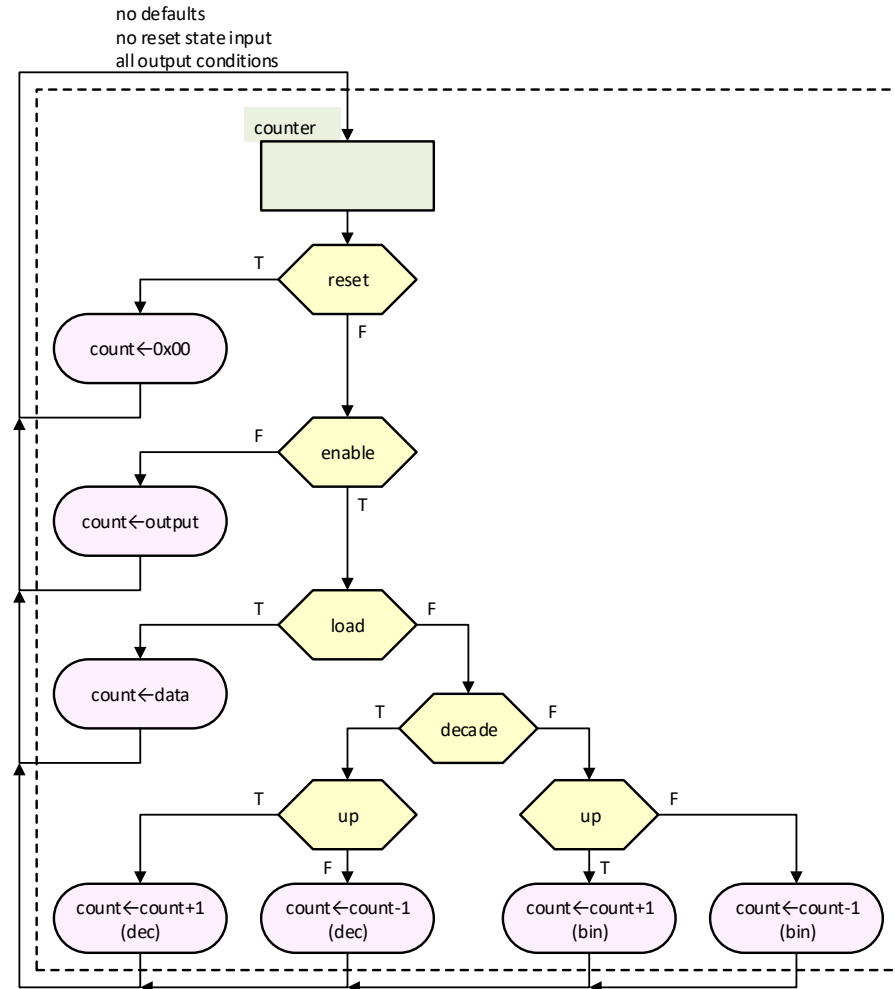- What type of conditional statement is most suited?
  - Count conditions and outputs..


 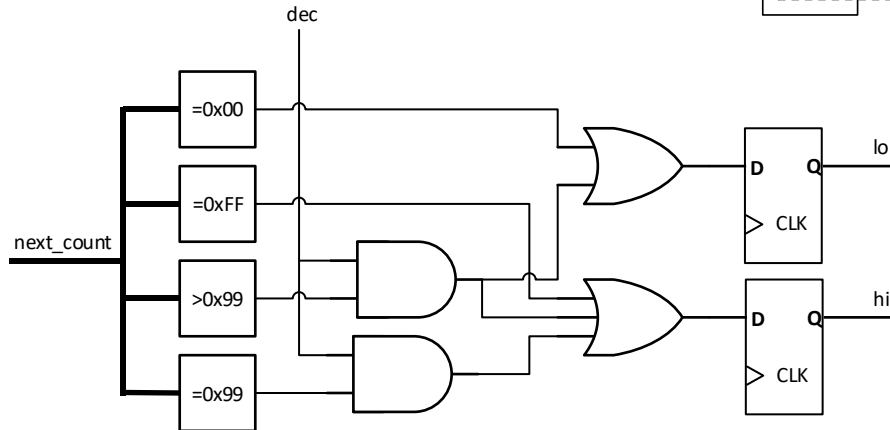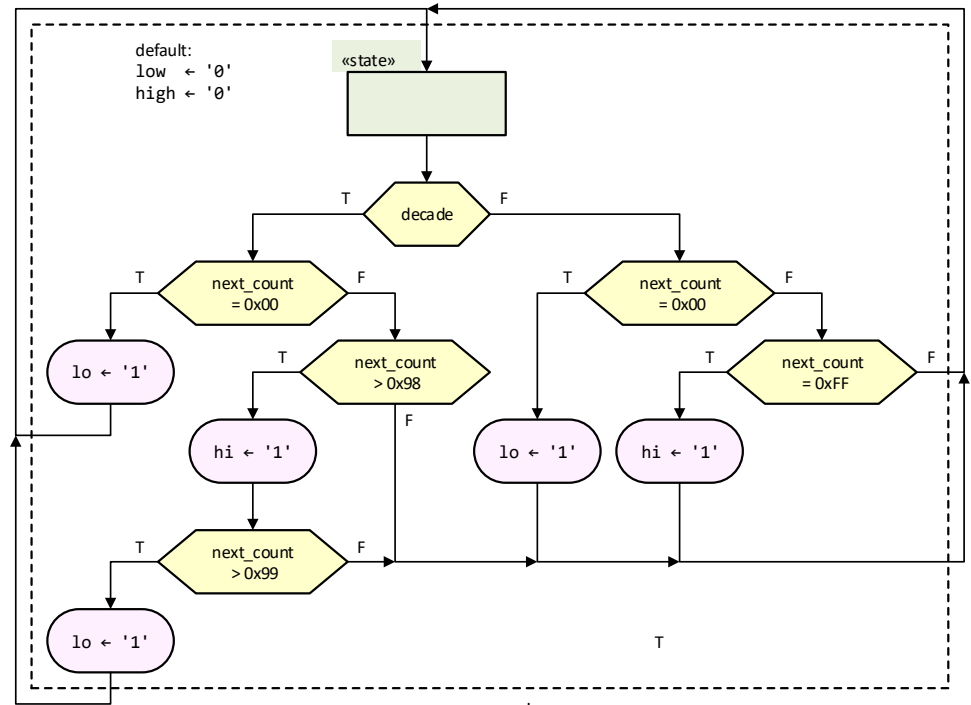
# Decade counter : hi/ lo signals

- Various level of detail
  - *Do we need unwrap all details?*



```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;
```

```
entity dec_count is
generic(
COUNT_WIDTH : natural := 8);
port(
clk, reset, enable, load, decade, up : in std_logic;
data : in std_logic_vector(COUNT_WIDTH-1 downto 0);
hi, lo : out std_logic;
count : out std_logic_vector(COUNT_WIDTH-1 downto 0)
);
end entity dec_count;
```

```
architecture RTL of dec_count is
constant DEC_MAX : unsigned(3 downto 0) := "1001";
constant ZERO_NIBBLE : unsigned(3 downto 0) := "0000";
constant NIBBLES : integer := COUNT_WIDTH/4;


signal next_count : unsigned(count'range);
signal next_hi, next_lo : std_logic;

alias upper : unsigned(3 downto 0) is next_count(next_count'high downto next_count'high - 3);
alias lower : unsigned(3 downto 0) is next_count(3 downto 0);
```

```
begin
-- registry update
count <= std_logic_vector(next_count) when rising_edge(clk);
hi <= std_logic(next_hi) when rising_edge(clk);
lo <= std_logic(next_lo) when rising_edge(clk);
```


```
-- non generic part -- -- can also be processed in a loop --
next_hi <= '1' when (and next_count = '1') or ( (decade = '1') and ((lower>8) and (upper >8)) ) else '0';
next_lo <= '1' when (nor next_count = '1') or ( (decade = '1') and ((lower>9) or (upper >9)) ) else '0';
```
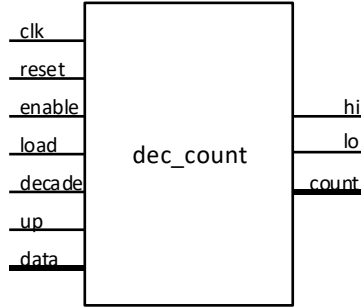
# Decade counter example: entity + constants and register storage




decade	count	high	low
X	0x00	0	1
0	0x01-0xFE	0	0
0	0xFF	1	0
1	0x01-0x98	0	0
1	0x99	1	0
1	0xA0-0xFF	1	1

• Do we need both?

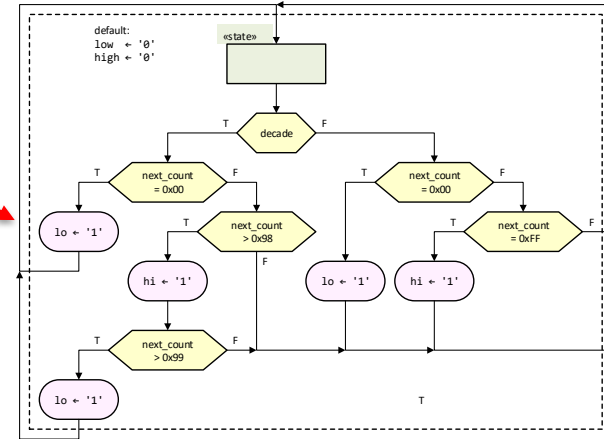

- Reset not part of register storage when synchronous.
- When checking multiple arguments
  - => break down to boolean clauses with >, <, = or /=

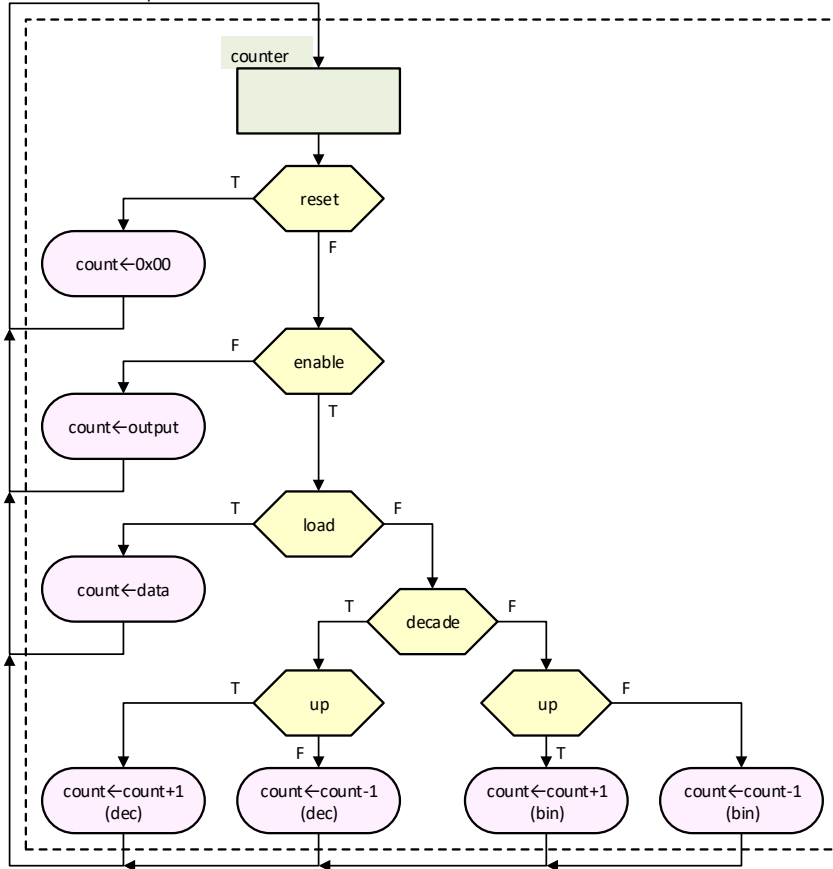no defaults  
no reset state input  
all output conditions



- Decision tree: one output, several conditions => when else
- *There are many ways of performing decade counting*
  - Indexing requirements = obstacle when reading.
  - Use mod or rem will be OK but still 4 bit nibble

```

COUNTING: process(all) is
function count_dec(up: std_logic; dec : unsigned(count'range)) return unsigned is
variable i_count : unsigned(count'range);
variable acc : integer;
variable criteria, nibble : unsigned(3 downto 0);
begin
acc := 1          when up else -1;
criteria := DEC_MAX  when up else ZERO_NIBBLE;
nibble := ZERO_NIBBLE when up else DEC_MAX;
i_count := dec; -- by default use the old value.
for i in 0 to NIBBLES-1 loop
if dec(i*4+3 downto i*4) = criteria then
i_count(i*4+3 downto i*4) := nibble;
next;
else
i_count(i*4+3 downto i*4) := dec(i*4+3 downto i*4) + acc;
exit;
end if;
end loop;
return i_count;
end function;
begin
next_count <=
( (others => '0')
unsigned(count)
unsigned(data)
count_dec(up, unsigned(count))
unsigned(count) + 1
unsigned(count) - 1;
end process;
end architecture RTL;
    
```

Note: SW-like trick to create priority.. (Works in synthesis)

Before going into function details:  
ASM style decision tree is normally easy to implement  
Here: up/down used as parameter in function

## Suggested reading

- Diagrams
  - These and earlier lecture notes.
- Reset circuits
  - Steve Kilts: Advanced FPGA Design: Architecture, Implementation and Optimization, 2007, chapter 10.
    - download from university library  
Semesterside for IN3160->“Pensum/litteratur i Leganto”