



UiO : **Department of Informatics**
University of Oslo

IN 3160, IN4160

Interconnect, Memory

Yngve Hafting



In this course you will learn about the **design of advanced digital systems**. This includes programmable logic circuits, a hardware design language and system-on-chip design (processor, memory and logic on a chip). Lab assignments provide practical experience in how real design can be made.

After completion of the course you will:

- understand important **principles for design** and testing of digital systems
- understand the relationship between behaviour and different construction criteria
- be able to describe advanced digital systems at different levels of detail
- be able to perform simulation and synthesis of digital systems.


Goals for this lesson:

- Know terms and structure
 - Interconnect types
 - buses
 - crossbar switches
 - interconnect networks
- Know typical structures for memory address decoding
 - Bit slicing
 - Banking
 - Tiling

Overview

- Interconnect
 - bus
 - crossbar
 - network
- Memory
 - SRAM
 - DRAM
- Memory organization
 - Banking
 - Slicing
 - Tiling


Interconnect

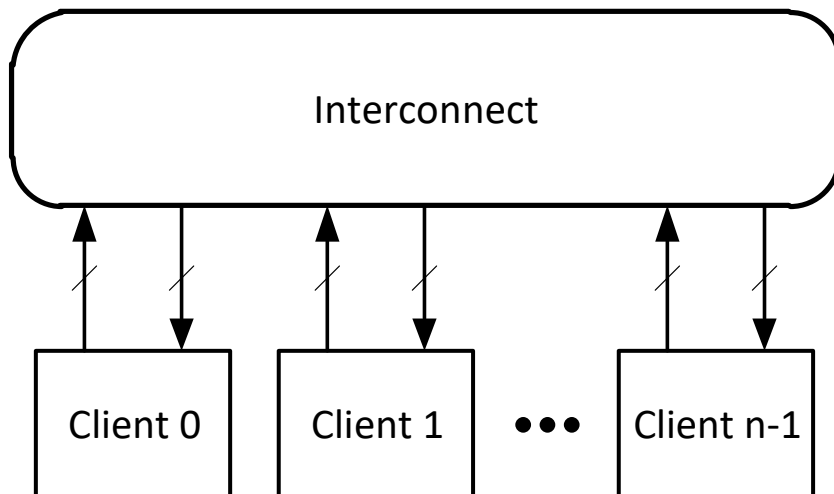

- Many clients need to communicate
- Ad-hoc point-to-point wiring or shared interconnect
- Like a telephone exchange



Bus

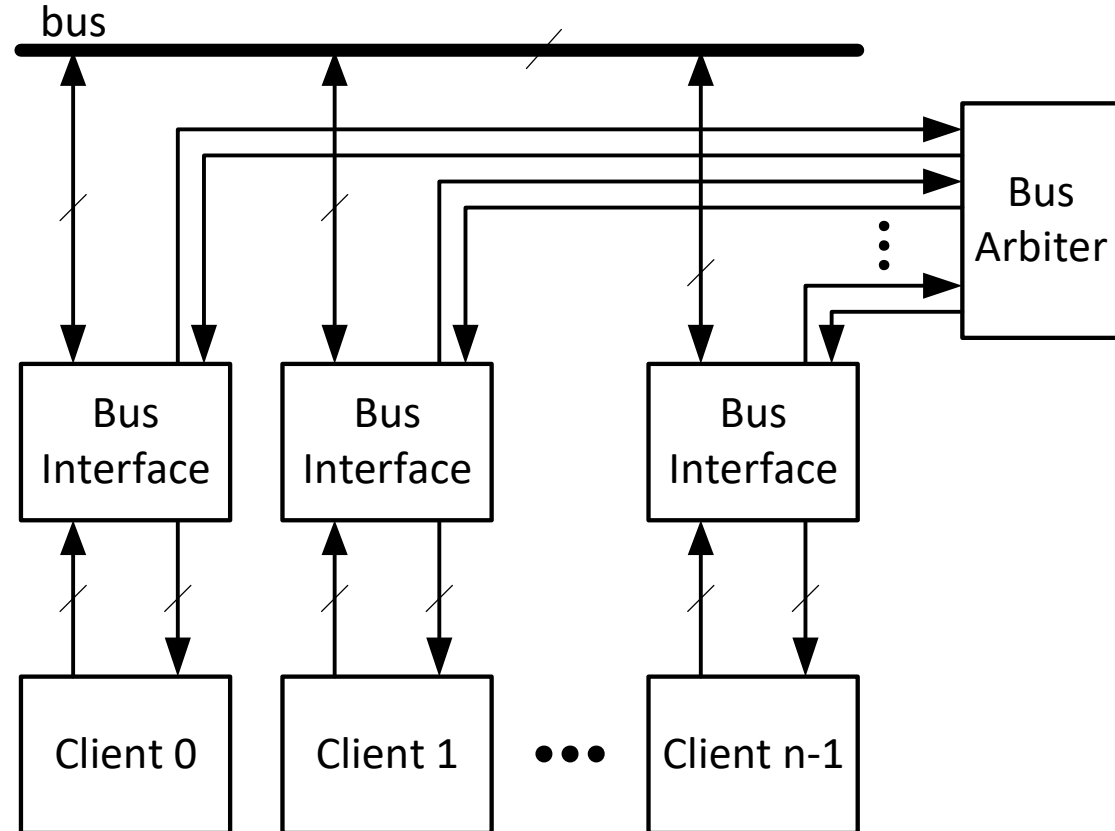- interconnect with (multiple) clients connected to one (often multiple bit) data line.
- Only one client can send data at a time, but there can be multiple receivers.
- The bus arbiter selects which client is allowed to use the bus.
- External buses:
 - tristate
- Internal buses
 - or'ing of client signals



VHDL for a simple bus interface

(c) 2005-2012 W. J. Dally

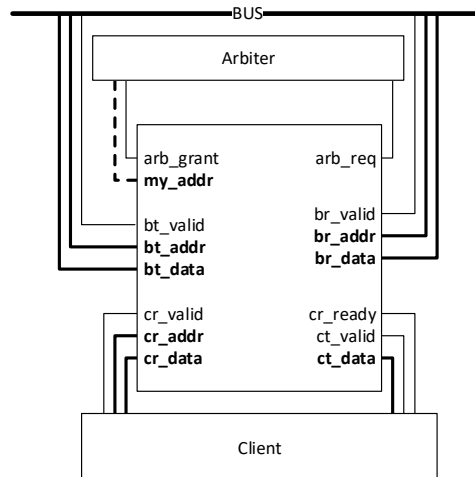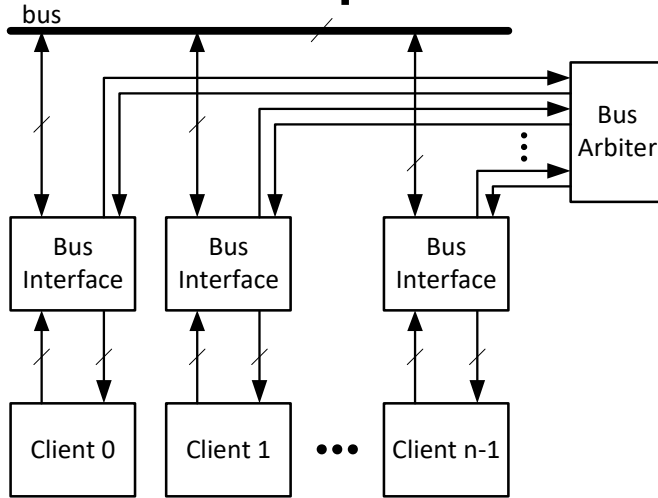

```
-- Combinational Bus Interface
-- t (transmit) and r (receive) in signal names are from the
-- perspective of the bus
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity BusInt is
  generic( aw: integer := 2; -- address width
           dw: integer := 4 ); -- data width
  port( cr_valid, arb_grant, bt_valid: in std_logic;
        cr_ready, ct_valid, arb_req, br_valid: out std_logic;
        cr_addr, bt_addr, my_addr: in std_logic_vector(aw-1 downto 0);
        br_addr: out std_logic_vector(aw-1 downto 0);
        cr_data, bt_data: in std_logic_vector(dw-1 downto 0);
        br_data, ct_data: out std_logic_vector(dw-1 downto 0) );
end BusInt;
```

```
architecture impl of BusInt is
```


```
begin
  -- arbitration
  arb_req <= cr_valid;
  cr_ready <= arb_grant;
```

```
  -- bus drive
  br_valid <= arb_grant;
  br_addr <= cr_addr when arb_grant else (others => '0');
  br_data <= cr_data when arb_grant else (others => '0');
```


```
  -- bus receive
  ct_valid <= '1' when (bt_valid = '1') and (bt_addr = my_addr) else '0';
  ct_data <= bt_data ;
end impl;
```

Crossbar Switch

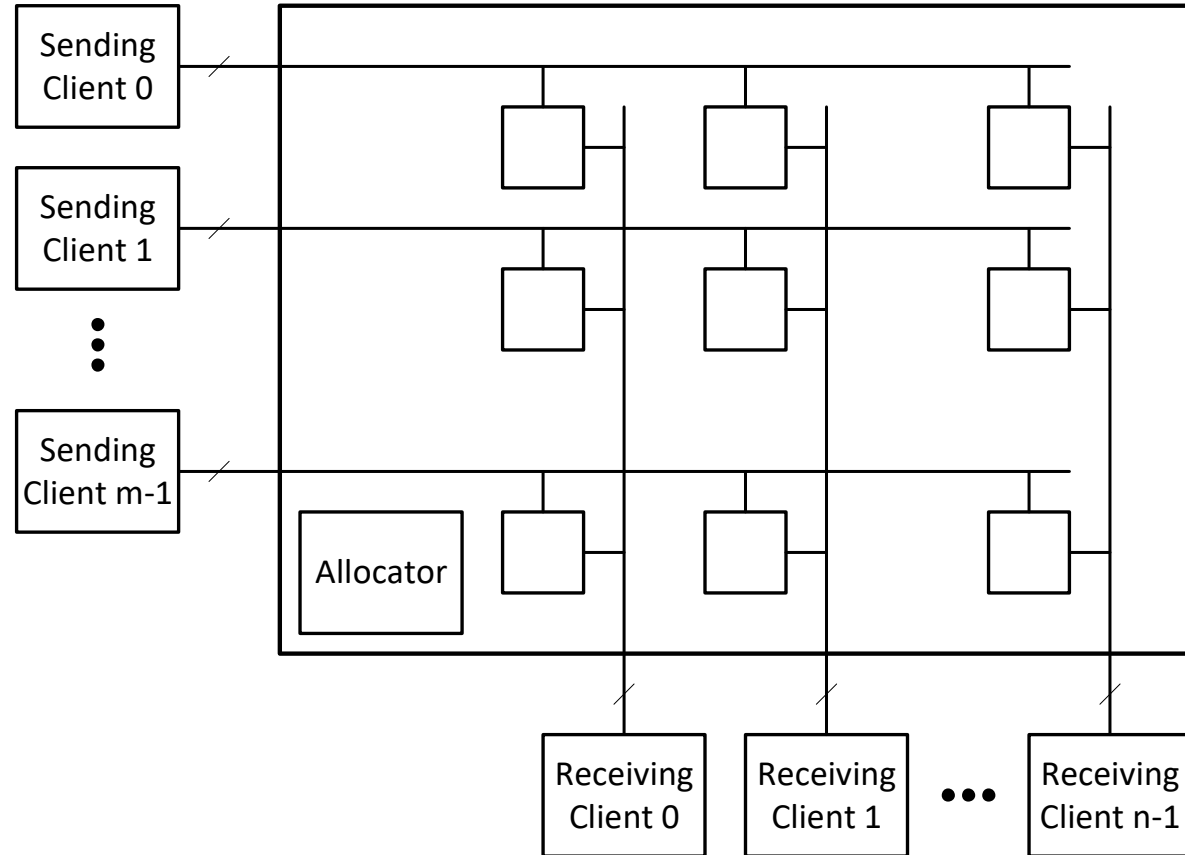- interconnect with multiple senders and receivers.
- Several senders may be active at a time, as long as a unique path can be allocated to each receiver.
- Throughput *can* be increased by allowing buffering at each crosspoint..



Crossbar Switch 2x2 example

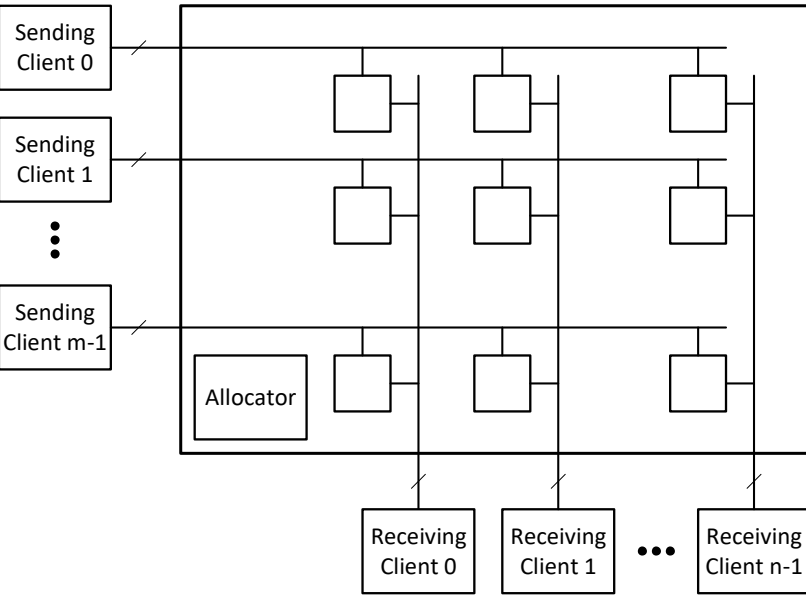

```
architecture impl of Xbar22 is
    signal req00, req01, req10, req11: std_logic;
    signal grant00, grant01, grant10, grant11: std_logic;
begin
    -- request matrix
    req00 <= '1' when not c0r_addr and c0r_valid else '0';
    req01 <= '1' when c0r_addr and c0r_valid else '0';
    req10 <= '1' when not c1r_addr and c1r_valid else '0';
    req11 <= '1' when c1r_addr and c1r_valid else '0';
```

```

-- arbitration 0 wins
grant00 <= req00;
grant01 <= req01;
grant10 <= req10 and not req00 ;
grant11 <= req11 and not req01 ;


-- connections
c0t_valid <= (grant00 and c0r_valid) or (grant10 and c1r_valid);
c0t_data <= (c0r_data and (dw-1 downto 0 => grant00)) or
            (c1r_data and (dw-1 downto 0 => grant10));
c1t_valid <= (grant01 and c0r_valid) or (grant11 and c1r_valid);
c1t_data <= (c0r_data and (dw-1 downto 0 => grant01)) or
            (c1r_data and (dw-1 downto 0 => grant11));

-- ready
c0r_ready <= (grant00 and c0t_ready) or (grant01 and c1t_ready);
c1r_ready <= (grant10 and c0t_ready) or (grant11 and c1t_ready);
end impl;
```


```
entity Xbar22 is
    generic( dw: integer := 4 ); -- data width
    port(
        c0r_valid, c0t_ready, c1r_valid, c1t_ready: in std_logic;
        c0r_ready, c0t_valid, c1r_ready, c1t_valid: out std_logic;
        c0r_addr, c1r_addr: in std_logic;
        c0r_data, c1r_data: in std_logic_vector(dw-1 downto 0);
        c0t_data, c1t_data: out std_logic_vector(dw-1 downto 0) );
end Xbar22;
```


Interconnection Networks

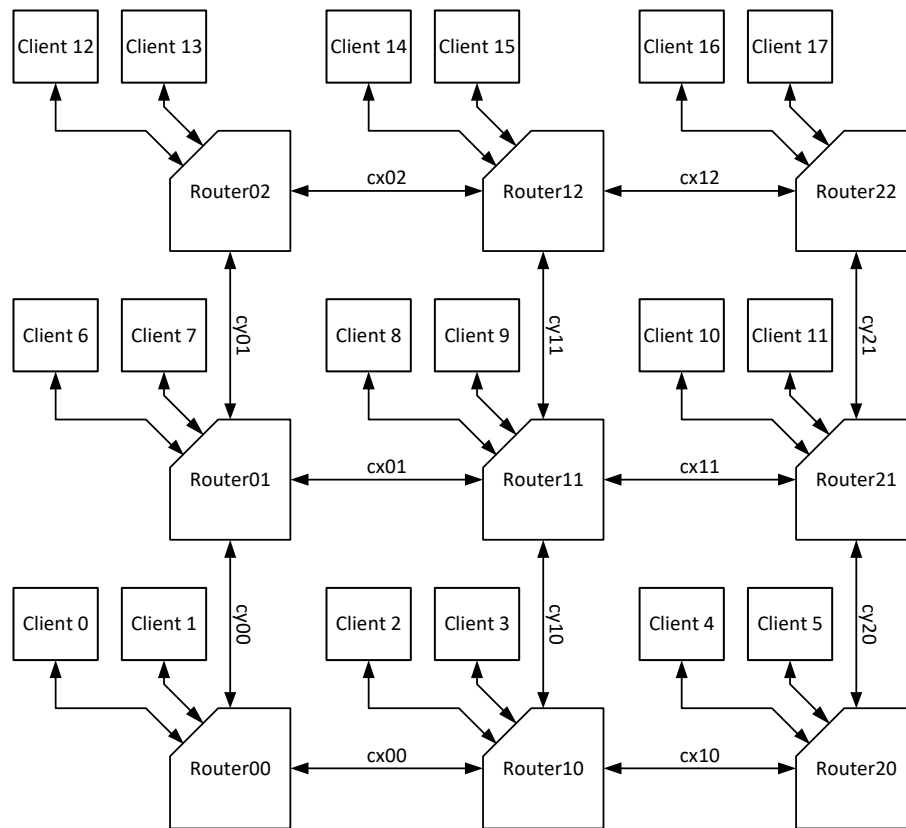- multiple senders and receivers.
- Packets are buffered by routers that transfer the packet in the direction of the recipient.
- Routing algorithm will be depending on the network topology.
 - star/tree topology (LAN)
 - ring topology
 - mesh topology




Interconnection Networks

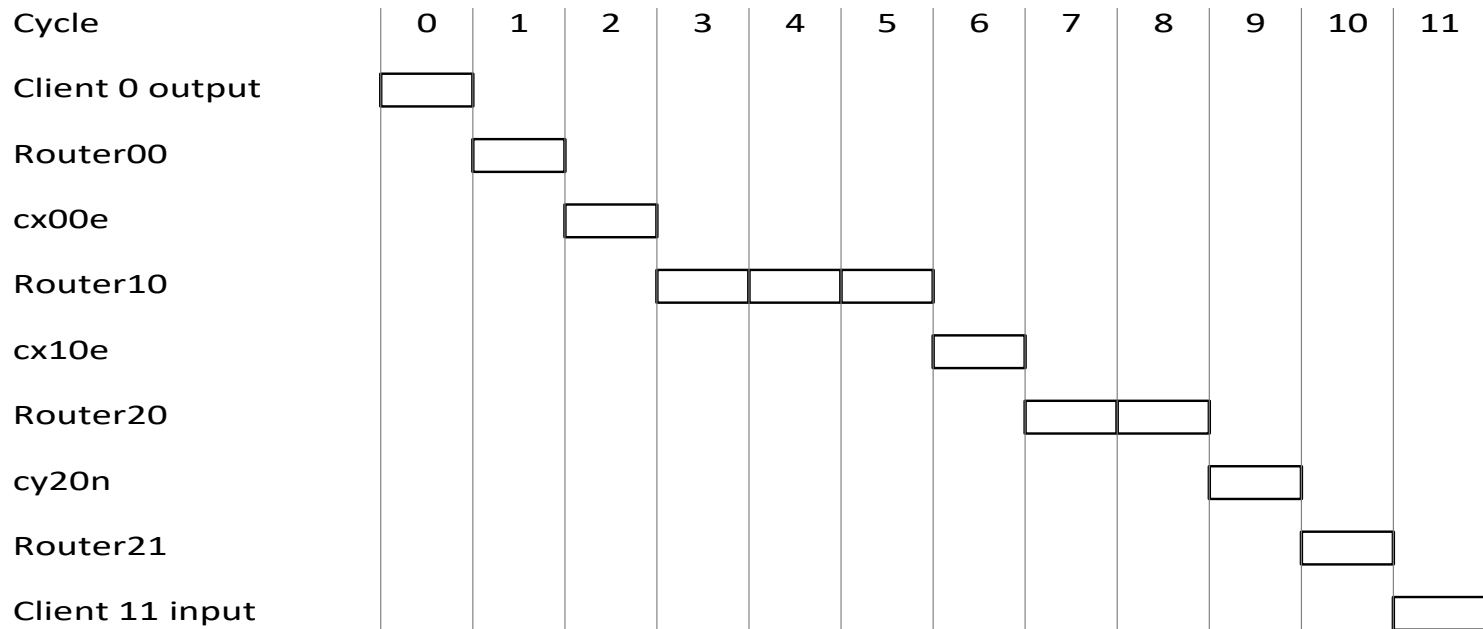

Memory


 
- Row of decoders, column multiplexers
- Typical restriction of array size
 - $256 \times 256 = 65536 = 64\text{k bit} = 8\text{k Byte}$
 - electrical restriction
- Larger memory need to be multiples of arrays at the maximum size



Capacity
Bandwidth
Latency
Granularity


SRAM

  - Both asynchronous and synchronous versions exist
- Stored bit is (weakly) upheld by the inverters.
- When wordline is activated
 - bitline either
 - propagates the weak value or
 - sets the bit value if it is driven (strong)
- The physical layout can be more complex, including transistors for precharging bitlines etc.



DRAM Operation

 - For each read, the stored capacitor charge is removed, and thus need to be re-written to remain stored.
- Several columns in one row can be read before rewrite.
- Rewrite (D&H: precharge operation) takes a certain time
 - DRAM stores bit as charge on capacitors.
- RAM cells need periodically refresh that performs read/write




UiO : **Department of Informatics**
University of Oslo

What if you need more memory or more bandwidth than one primitive?




Bit-Slicing

 - Several slices shares the same address
- Data is read from a row of slices in parallel.




Banking

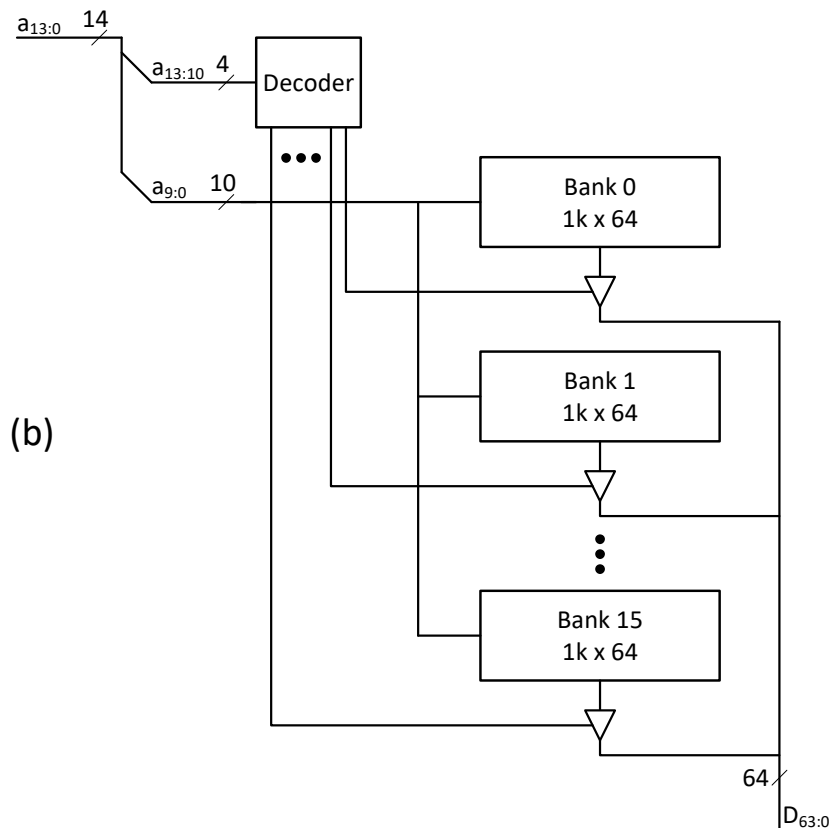- Banked memory is organized in columns of array banks
- Parts of the address is decoded to enable output from the selected bank only.
 - May be used to have the other banks idle and save power.




Tiling = Bit slicing & banking

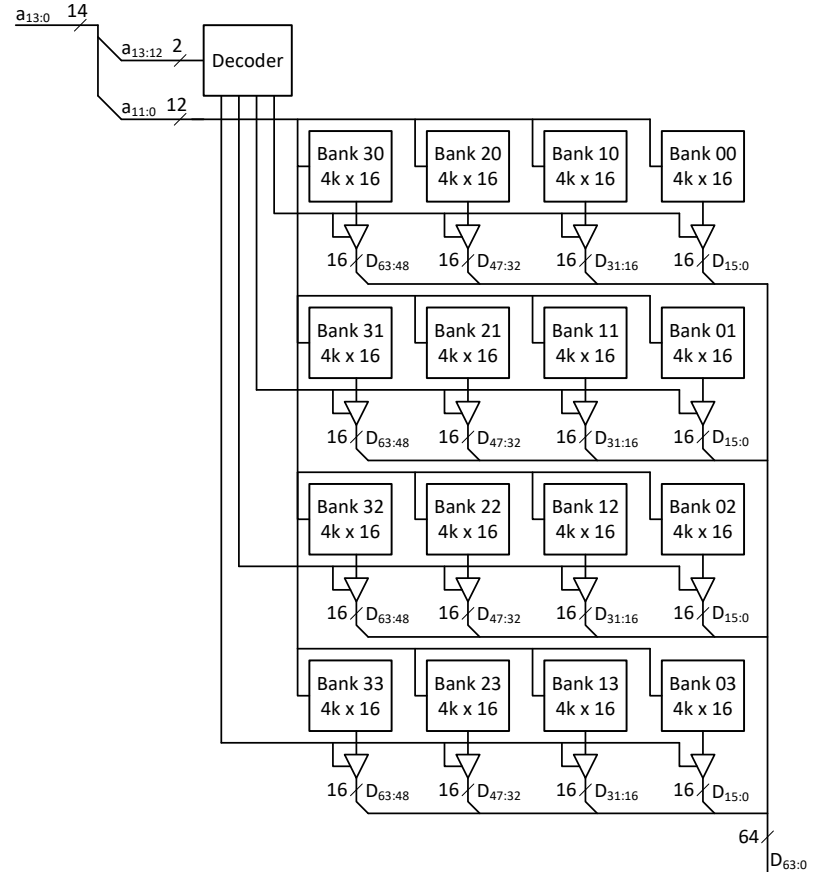


Interleaving

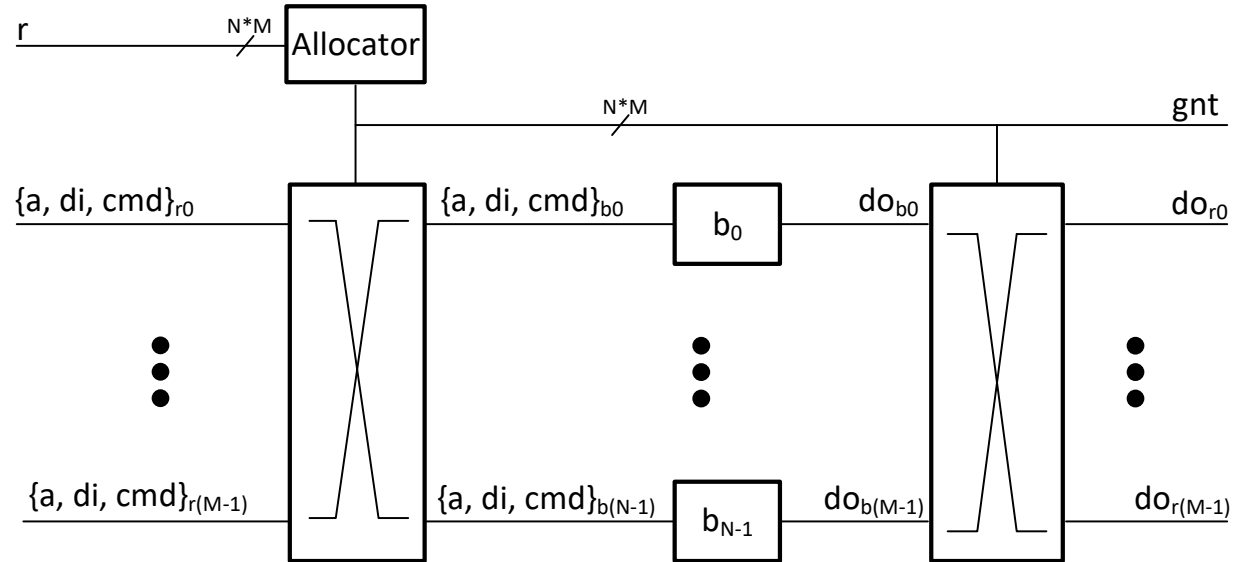- Using a crossbar switch for a tiled set of banks
- Allow for multiple read or writes during the same cycle
- Ex: Quad data rate (QDR) RAM



Hierarchy (->IN2060)

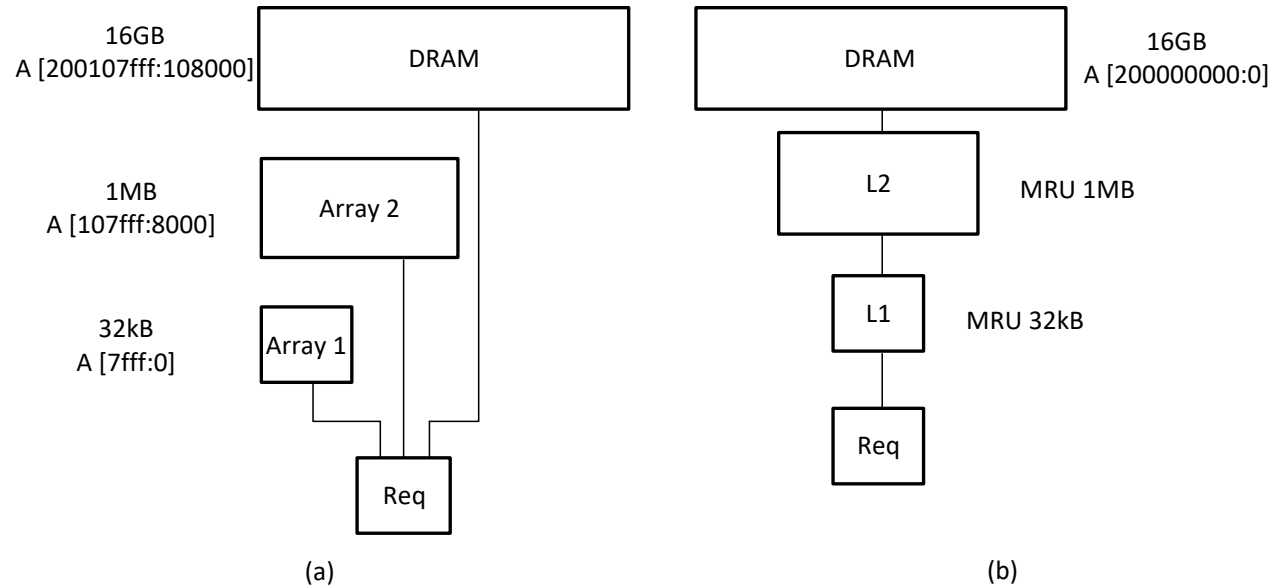

Summary

- DHA
 - 24-25.3, p 521-540
 - (25.4 can be read to connect the dots from IN2060)