

IN 3160, IN4160

VHDL conditional statements and loops

Yngve Hafting



Messages

- Implement?
 - Oblig 1
 - yes
 - Oblig 2
 - yes
- Demonstrate / show lab supervisor?
 - Yes:
 - Simplifies approval and feedback process
 - If not possible...
 - Video -> filesender. Can be used to show the same
 - *Feedback in canvas only*
 - ...
- Remote access:
 - https://robin.wiki.ifi.uio.no/Remote_access
 - *4 PCs, same setup as LISP + camera*

In this course you will learn about the design of advanced digital systems. This includes programmable logic circuits, a hardware design language and system-on-chip design (processor, memory and logic on a chip). Lab assignments provide practical experience in how real design can be made.

After completion of the course you will:

- understand important principles for design and testing of digital systems
- **understand the relationship between behaviour and different construction criteria**
- **be able to describe advanced digital systems at different levels of detail**
- **be able to perform simulation and synthesis of digital systems.**

Goals for this lesson:

- Know the basic structure and function of widely used combinational structures.
 - how to implement these structures using VHDL
 - *If, case, when-else, select*
 - *Loops*
 - *Type casting*
 - *Shift operators*
 - *Dataflow vs RTL descriptions*
- Know how to generate complex structures in VHDL
 - generate

Section overview

- VHDL:
 - Sensitivity list
 - Signals and variables example
 - If, case, when-else, select
 - Loops
 - Structural coding
 - Generate
 - Generics

Next lesson: Building blocks

Decoders vs encoders

Decoder

Multiplexer

Encoders

Arbiters

Shifters

Comparators

ROM

RAM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity My_thing is
  port(A: in STD_LOGIC;
       F: out STD_LOGIC
       );
end entity My_thing;
```

```
architecture Behavioral of My_thing is
  signal b : STD_LOGIC;
begin
  signal_update: process(a)
  begin
    if A = '1' then b <= '1';
    else b <= '0';
    end if;

    if b = '1' then F <= '1';
    else F <= '0';
    end if;

  end process;
end architecture Behavioral;
```

Sensitivity list

What happens with F?

Assume a changes from '0' to '1'

```
signal_update: process(a,b)
begin
  if a = '1' then
    b <= '1';
  else
    b <= '0';
  end if;
  if b = '1' then
    f <= '1';
  else
    f <= '0';
  end if;
end process;
```




Signals vs. variables (sequential logic example)

- Exercise:
- Assume all signals are 0, then
 - signal a changes from 0 to 1.
- On which clock cycles does f and g change value; first, second, third?

Try for 1 minute, answers can be written in chat...

Time's up...

```
signal_var_update : process (clk)
    variable c : std_logic;
begin
    if rising_edge (clk) then
        if a = '1' then
            b <= '1';
            c := '1';
        else
            b <= '0';
            c := '0';
        end if;
        if b = '1' then
            f <= '1';
        else
            f <= '0';
        end if;
        if c = '1' then
            g <= '1';
        else
            g <= '0';
        end if;
    end if;
end process;
```

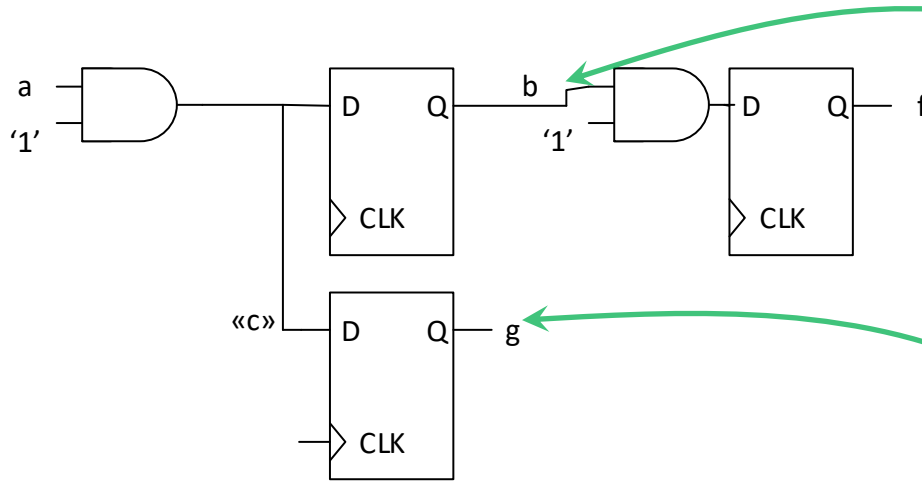

NOTE: c *could* be assigned multiple places in the process.


How would that affect the diagram..?

Variables update «immediately»
Signals are assigned «where» the process ends
when the process statement updates as a whole

```
signal_var_update :  
process (clk)  
    variable c : std_logic;  
begin  
    if rising_edge (clk) then  
        if a = '1' then  
            b <= '1';  
            c := '1';  
        else  
            b <= '0';  
            c := '0';  
        end if;  
        if b = '1' then  
            f <= '1';  
        else  
            f <= '0';  
        end if;  
        if c = '1' then  
            g <= '1';  
        else  
            g <= '0';  
        end if;  
    end if;  
end process;
```

Digression:

- Simplified...

 

```
signal_var_update :  
process (clk)  
  variable c : std_logic;  
begin  
  if rising_edge (clk) then  
    b <= a;  
    c := a;  
    f <= b;  
    g <= c; -- g <= a  
  end if;  
end process;
```

```
signal_var_update :  
process (clk)  
  variable c : std_logic;  
begin  
  if rising_edge (clk) then  
    if a = '1' then  
      b <= '1';  
      c := '1';  
    else  
      b <= '0';  
      c := '0';  
    end if;  
    if b = '1' then  
      f <= '1';  
    else  
      f <= '0';  
    end if;  
    if c = '1' then  
      g <= '1';  
    else  
      g <= '0';  
    end if;  
  end if;  
end process;
```


Default values in processes

```
: architecture Sequential2 of priority is
: begin
:   process (a) is
:   begin
:     valid <= '1';
:     if a(3)='1' then
:       y <= "11";
:     elsif a(2)='1' then
:       y <= "10";
:     elsif a(1)='1' then
:       y <= "01";
:     elsif a(0)='1' then
:       y <= "00";
:     else
:       valid <= '0';
:       y <= "00";
:     end if;
:   end process;
: end architecture Sequential2;
```

- Ensures we always have an output value (*avoiding latches*).
- Be reasonable with use of “default” values in a process
 - Does only change where it’s necessary
 - This works because processes are compiled sequentially...
 - The *last assignment* within the *process* will take precedence
 - Don’t bury default values within nested ifs...
 - Readability and maintainability suffer if you do..
- Default values are commonly used for state machine outputs
 - typically active in one state only...

Signals and variables

- Signals and variables can be used to hold data
- Signals
 - A signal can be used within the whole architecture
 - Connect to other architectures through the entity ports
 - Changes value when a process terminates in simulation
- Variables
 - Variables are declared and *only used locally* within a process (function or procedure)
 - Assigned using “:=“ (Ex: var := ‘1’ ;)
 - Unlike a signal the variable changes value **immediately** in simulation
 - Immediately = based on position
 - *can hold multiple values* within one process.
 - Variables are useful to keep intermediate results in algorithms
 - Subprograms initialize variables every run.
 - Process variables initialize once, *when simulation starts*

Rule of thumb:

- **Signal** for all registers (FFs)
“out is a **signal** that can be read outside the entity”
- «when others»:
 - use **variable** if possible...

If and case in **VHDL Processes**

- ***if*** and ***case*** are used much like in other programming languages like C, Java etc.
 - In if-tests we can test on different signals/variables
 - if-tests have a built in priority
 - In case-tests we are only testing in one signal (with one or more bit)
 - No built in priority because the same signal are being used everywhere in the test

If

- Must be in process
 - **Multiple conditions**
 - **Multiple targets**
 - prioritizes
- First option has priority
 - (think of two-input multiplexers)
 - Can be used to infer latches and Flipflops
 - FF when edge triggered (rising_edge)
 - **Latch when not sufficiently specified**
 - This is a trap, avoid this!
 - Can be nested using «elsif»
 - And replace case statements...
 - Consider using case...
 - Avoid deep nesting
 - 4 degrees should be maximum...

If example (*all input specified*):

inp1	inp2	a	b
1	1	1	1
1	0	1	0
0	1	0	Latched
0	0	0	Latched


```
process(all) is
begin
  if inp1 then
    if inp2 then
      a <= '1';
      b <= '1';
    else
      a <= '1';
      b <= '0';
    end if;
  else
    a <= '0';
  end if;
end process;
```

```
process(all) is
begin
  if inp1 then
    a <= '1';
    b <= inp2;
  else
    a <= '0';
    -- b ass. missing
  end if;
end process;
```

Always specify all outputs for all conditions of inputs!

```
entity My_thing is
  port(A,B,J,K,L: in STD_LOGIC;
        OUTPUT: out STD_LOGIC);
end entity My_thing;
```

 
```
architecture prioritized of My_thing is
begin
  process(all)
  begin
    if A = '1' then
      OUTPUT <= J;
    elsif B = '1' then
      OUTPUT <= K;
    else
      OUTPUT <= L;
    end if;
  end process;
end architecture prioritized;
```



if../case..

```
entity My_thing is
  port(A : in STD_LOGIC_VECTOR(1 downto 0);
        J,K,L: in STD_LOGIC;
        OUTPUT: out STD_LOGIC);
end entity My_thing;

 architecture nonpri of My_thing is
begin
  case A is
    when "01" =>
      OUTPUT <= J;
    when "10" =>
      OUTPUT <= K;
    when others =>
      OUTPUT <= L;
  end case;
end architecture nonpri;
```



If nesting vs. chaining (*using elsif*)

```
process(all) is
begin
  if (input = 4d"1") then
    isprime <= '1';
  else
    if (input = 4d"2") then
      isprime <= '1';
    else
      if (input = 4d"3") then
        isprime <= '1';
      ...
    end if;
  end if;
  else isprime <= '0';
  end if;
end process;
```

```
process(all) is
begin
  if (input = 4d"1") then isprime <= '1';
  elsif (input = 4d"2") then isprime <= '1';
  elsif (input = 4d"3") then isprime <= '1';
  ...
  else isprime <= '0';
  end if;
end process;
```

If nesting for priority – danger zone

Sometimes it can make sense to use nesting

- clocked processes and state machines
- It is easy infer latches
 - When not all input options are covered
 - When some output is not covered for all options

Consider other options when creating CL

- *improve readability*
- *Reduce risk for latches*
- *It is OK to nest other statements within if...*
 - *select ...*
 - *when ... else*
 - *case ...*

```
process(all) is
begin
  if (inp1 = a) then
    if (inp2 = b) then
      if (inp3 = c) then
        <statement 1>
      <statement 2>
    else
      <statement 3>
    end if;
  end if;
else
  <statement 4>
end if;
end process;
```


Example

```
library ieee;
use ieee.std_logic_1164.all;

entity latches is
port(
  invec : in std_logic_vector(1 downto 0);
  outvec : out std_logic_vector(3 downto 0);

  input : in std_logic;
  out1, out2 : out std_logic
);
end entity latches;
```

- Nesting if-statements will conceal these errors easily, thus providing an endless source of errors

```
architecture poor of latches is
begin
  -- if invec = "11" => outvec is latched
  missing_input: process(all) is
  begin
    if invec = "00" then
      outvec <= "0000";
    elsif invec = "01" then
      outvec <= "1110";
    elsif invec = "10" then
      outvec <= "0110";
    end if;
  end process;

  -- if input='1' then out2 is latched.
  -- if input='0' then out1 is latched.
  missing_output: process(all) is
  begin
    if input then
      out1 <= '1';
    else
      out2 <= '0';
    end if;
  end process;
end architecture poor;
```

Case

- Must be in process
 - **single input vector**
 - **Multiple targets**
 - Every alternative has same priority
-
- Every option for *input* must be declared
 - ‘**when others**’ can be used
 - be wary of changes in input *type*...
 - Can infer latches too...
 - When not defining all outputs for all inputs
 - Matching case- «case?»
 - Allowes for don't care's


```
process(input) is
begin
  case input is
    when x"1" | x"2" | x"3" | x"5" | x"7" |x"b" | x"d" =>
      isprime <= '1';
    when others => isprime <= '0';
  end case;
end process;
```

The typical use-case for case is state machines.


Case is excellent when you want to set several output vectors depending on one state vector.

Case creating latches:

 Default values can be a good solution when using case statements.



 'null' statement should only be used in CL when using default values for all outputs.



```
process(input) is
begin
  isprime <= '0';
  isfour <= '0';
  case input is
    when x"1" | x"2" | x"3" | x"5" | x"7" | x"b" | x"d" =>
      isprime <= '1';
      isfour <= '0';
    when x"4" =>
      isprime <= '0';
      isfour <= '1';
    when others =>
      null;
  end case;
end process;
```



= latch inferred

When ... else

- Can be used concurrently (outside processes).
- **Multiple conditions**
- **Single target**
- prioritizes

- Can replace if statements for *single target*
- Can infer FF's/latches
- Compact
 - Suitable when complexity is low

```
isprime <=
  '1' when input = x"1" else
  '1' when input = x"2" else
  '1' when input = x"3" else
  '1' when input = x"5" else
  '1' when input = x"7" else
  '1' when input = x"b" else
  '1' when input = x"d" else
  '0';
```

```
q <= '0' when reset else 'd' when rising_edge(clk);
```

```
a <= b when en;
```

^^ always keep 'else' in mind...

With ... select

- Can be used concurrently
- **single input vector**
- **Single target**
 - Must have all input cases defined

- Can also infer latches
 - *Least likely*
 - Feedback obvious 😊
- Compact and readable

```
with input select isprime <=  
  '1' when x"1" | x"2" | x"3" | x"5" | x"7" | x"b" | x"d",  
  '0' when others;
```

```
with a select g <=  
  16d"1" when 16d"1",  
  16d"4" when 16d"2",  
  16d"8" when 16d"3",  
  g when others;
```

If, case, when ... else, with select - summary

- When in doubt...
 - Try **‘with...select’**
 - This will force you to make visible choices.
- *Only* use **‘if’**...
 - When you need to prioritize conditions...
 - and have multiple targets
 - Typically used for clocked processes.
- It is fine to **use select...** or **when/else** inside **if** and **case**
 - *Do you need if inside if?..*
 - *Case inside case? ..*
 - Readability suffers when nesting several levels of if or case

Statement	Targets	Conditions	Process
if	<i>Multiple</i>	<i>Multiple</i>	Required
case	<i>Multiple</i>	Single	Required
when ... else	Single	<i>Multiple</i>	Optional
with ... select	Single	Single	Optional

Whatever you choose,
keep the following in mind:

define

- all outputs *for*
- all conditions

Loops in VHDL

- Both simulation and synthesizable code
- Three types
 - Simple loop- until exit
 - While- loop condition is true
 - For loop
 - Counted
 - Numbers or elements/ ‘range’
 - Loop parameter static
 - Can be increased using ‘next’
 - ‘next when <condition>’
- ‘exit’+(optional loop_label)
 - Can be used in all loops
 - Innermost loop is default
 - Nested loops: use label

```
--SIMPLE LOOP--  
variable i: integer := 0;  
...  
loop  
    statements;  
    i := i + 1;  
    exit when i = 10;  
end loop  
  
--WHILE LOOP--  
variable i: integer := 0;  
...  
while i < 10 loop  
    statements;  
    i := i + 1;  
end loop  
  
--FOR LOOP--  
for i in 1 to 10 loop  
    statements;  
end loop;  
  
--FOR LOOP2--  
type frukt_type is (eple, pære, banan);  
...  
frukt_loop: for f in frukt_type loop  
    statements;  
    when <condition1> next frukt_loop;  
    when <condition2> exit frukt_loop;  
end loop;
```


Entity/architecture

- Entity and architecture are the two most fundamental building blocks in VHDL
- Entity
 - Connection to the surroundings
 - Port description
 - Input/output/bi-directional signals
- Architecture
 - Describes behavior
 - An entity can have many architectures
 - Can be used to describe the circuit on several levels of abstraction:
 - Behavioral (for simulation)
 - RTL (Register Transfer Level)
 - Dataflow
 - Structural
 - Post synthesis (netlist)
 - Post Place & Route (netlist + timing)



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

 entity My_thing is
    generic(width: integer := 8);
    port(INA, INB : in STD_LOGIC;
         INC : in STD_LOGIC_VECTOR(width-1 downto 0);
         OUT1: out STD_LOGIC;
         OUT2: out STD_LOGIC_VECTOR( width/2 - 1 downto 0)
    );
end entity My_thing;
```



Generics

- In addition to the port description an entity can have a generic description
- **Generics** can be used to make parameterized components (generic)
 - can be used for structural information
 - both synthesis and simulation
 - can be used for timing information
 - for simulation only
 - Example 1:
 - Time delay can vary between circuits, but the behavior is the same
 - Example 2:
 - The number of bits can vary between circuits, but the behavior is the same

```

24: entity And2 is
25:   generic (delay : DELAY_LENGTH := 10 ns);
26:   port (x, y : in BIT; z: out BIT);
27: end entity And2;
28:
29: architecture ex2 of And2 is
30: begin
31:   z <= x and y after delay;
32: end architecture ex2;

```


```

architecture Structural of My_tb is
  component And2
  .. port( x,y : in BIT; z : out BIT);
  end component;
  signal a,b,c : BIT;
begin
  MY_COMP1: And2
  .. generic map(delay => 1 us);
  .. port map(x=>a, y=>b, z=>c);
end architecture Structural;

```

DELAY_LENGTH is a subtype of the type time from the predefined (always in use) package “std”


Structural design

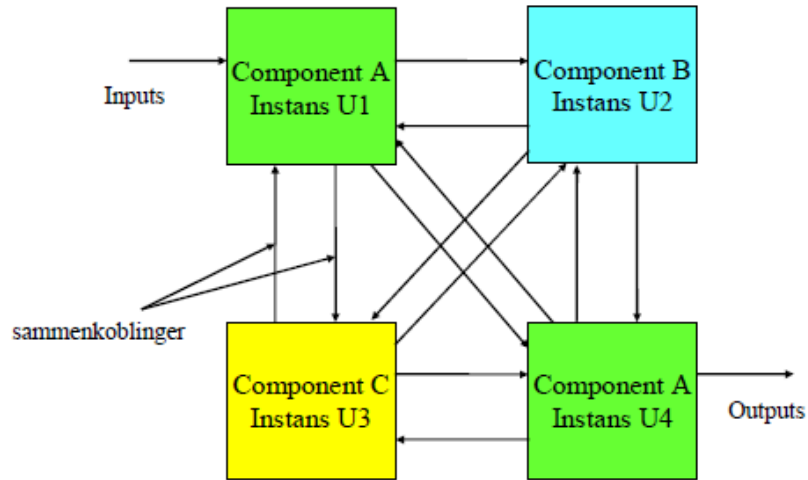

- Every Component instance has an underlying Entity/architecture pair
- We can easily re-use «entities»
- We *can* make a hierarchic design with as many levels we want
 - Try keep design hierarchy manageable...

Structural design

- Reuse of modules (entities and architectures)
- Generic modules (generics)
 - For example scalable bus widths
 - Configurable functionality
- Breaking up big designs to smaller and more manageable building blocks
 - Think functional blocks
 - Connection of functional blocks (entities/components/modules)
- Easier to collaborate within a design team
 - Well defined interface between modules
- Any entity-/architecture pair can be used as a building block in a structural description
 - Pairing of components

 

Structural design (netlist)


```
25: architecture netlist2 of comb_function is
26:
27:   component And2 is
28:     port (x, y : in BIT; z: out BIT);
29:   end component And2;
30:
31:   component Or2 is
32:     port (x, y : in BIT; z: out BIT);
33:   end component Or2;
34:
35:   component Not1 is
36:     port (x : in BIT; z: out BIT);
37:   end component Not1;
38:
39:   signal p, q, r : BIT;
40:
41: begin
42:   g1: Not1 port map (a, p);
43:   g2: And2 port map (p, b, q);
44:   g3: And2 port map (a, c, r);
45:   g4: Or2 port map (q, r, z);
46: end architecture netlist2;
```

- A netlist is a description of components used, and their connections
 - Synthesizing *is* creating a netlist using the available primitives for a (PL/ASIC) device.
 - The top level in larger designs is often purely structural, although with design elements and not device primitives
- Here we pick up the entities from the «working» library
- The last compiled architecture are being used
- Port mapping:
 - «Association» *can* be done by position
 - named association is less error prone.
(ex: **g1: Not1 port map (x => a, z=>p);**)

Structural design with generate statement

- ***generate*** is can build multiple components in a small loop.
 - Requires indexable parameters in connected signals
- Example: Bidirectional bus
 
```
bidir_bus_inst: for i in 0 to 15 generate  
  buft_inst: buft port map (data(i),en,din(i));  
  ibuf_inst: ibuf port map (dint(i),data(i));  
end generate;
```



Suggested reading

- D&H 7.1- 7.3 p129-153