



UiO • **Institutt for informatikk**
Det matematisk-naturvitenskapelige fakultet

IN3160, IN4160

Introduction to VHDL
+Basic layout for VHDL

Yngve Hafting



Messages:

- Questions before we start?

Course Goals and Learning Outcome

<https://www.uio.no/studier/emner/matnat/ifi/IN3160/index-eng.html>

In this course you will learn about the **design of advanced digital systems**. This includes programmable logic circuits, a **hardware design language** and system-on-chip design (processor, memory and logic on a chip). **Lab assignments provide practical experience in how real design can be made.**

After completion of the course you will:

- understand important **principles for design** and testing of digital systems
- understand the **relationship between behavior and different construction criteria**
- be able to **describe advanced digital systems** at different levels of detail
- be able to perform simulation and synthesis of digital systems.

Goals for this lesson:

- Know the basic structure of VHDL
 - Know which design entities there are
 - Know how assignment and statements works
 - Know the basic functionality of processes
 - Be able to create designs using VHDL
 - Know the relation between physical signals and their declaration.
 - Know the difference between basic coding styles
- Know basic layout principles
 - Guidelines for capital letters
 - Basic layout types
 - Principles for indentation, commenting, naming, punctuations

Overview

- Repetition
- VHDL Structure (Partly repetition from IN2060)
 - Design entities
 - Statements
 - Signals, variables, vectors
 - Processes
 - Libraries
 - STD_LOGIC
 - Operators
 - String literals
- Code layout principles
- Next lesson: Combinational logic
 - Assignments and suggested reading for this week

HDL

- VHDL = VHSIC HDL:
 - Very High Speed Integrated Circuit Hardware Description Language
 - **The purpose is to generate digital circuits, and verify their function through simulation.**
 - **Synthesizable (realizable) code generates circuits that are always on = work concurrently (in parallel).**
 - Code for simulation include things such as file I/O which cannot be synthesized.
 - Testbenches can and will use some synthesizable elements, but will in general look more like other sequential languages, and use sequential statements.
This may be confusing at times...


REPETITION

HDL

Code for generating and parsing simulation data (Test benches)

code for generating multiple instances or variants of entities

Synthesizable code

 


VHDL structure

- Design entities
- Architecture styles
- Ports and signals
- Vectors
- Assignment
- Libraries
- STD_LOGIC data type
- Operators


Design entities in VHDL

- 5 types of design entities
 - Entity
 - Architecture *body*
 - Package
 - Package body
 - Configuration
- Each entity can have its own file...

Design-entities: Entity and architecture



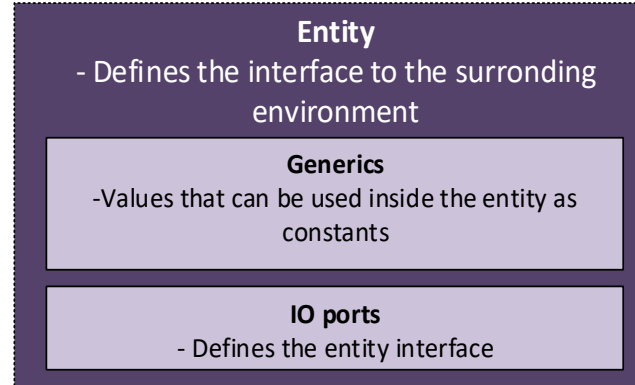


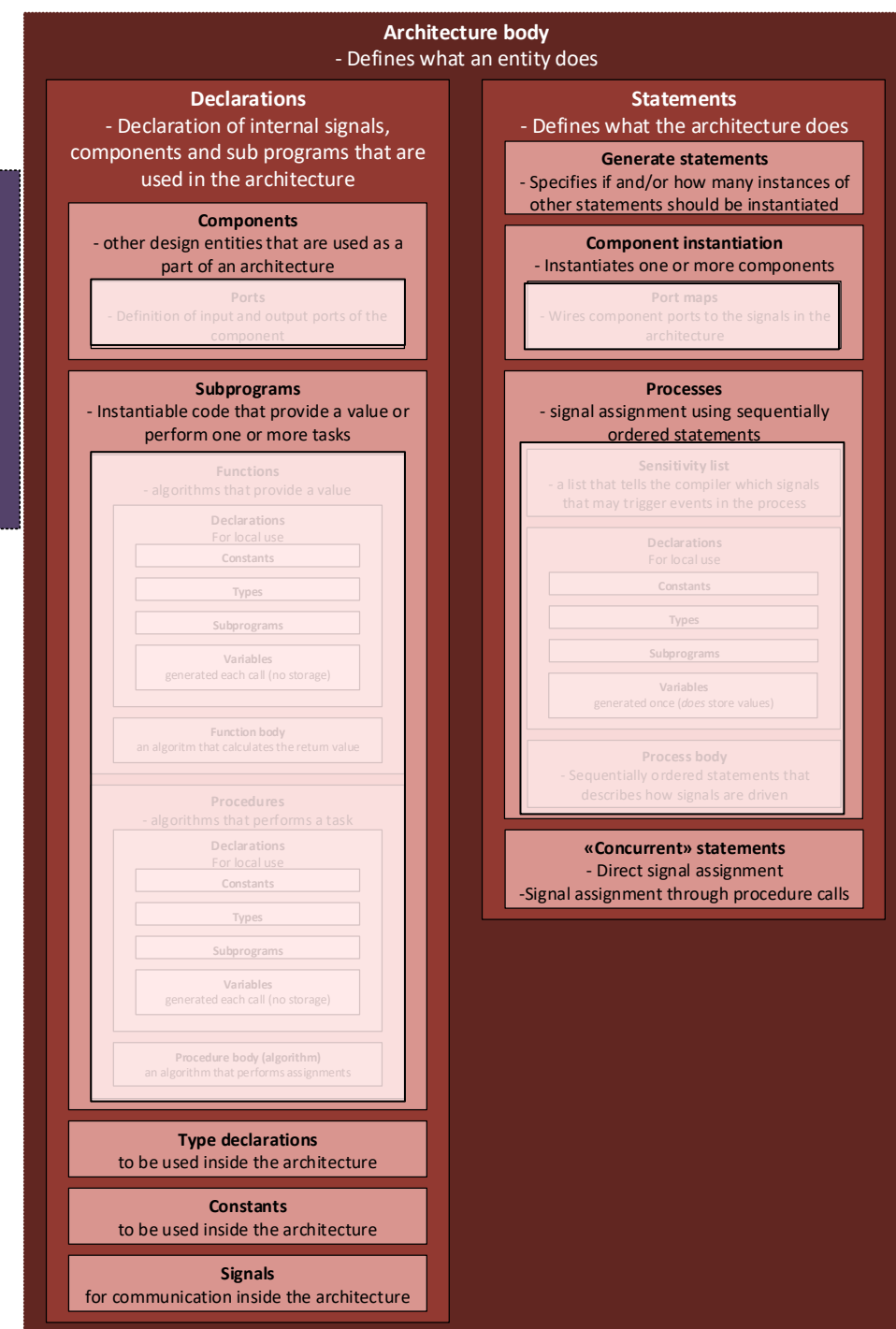- E. and A. is often put into the same file
- In larger designs these may be separated, several architectures can be used for one entity.
 - Simulation vs modules for synthesis
- *Details will be revealed later..*




Design entities: Package, P.body, Configuration

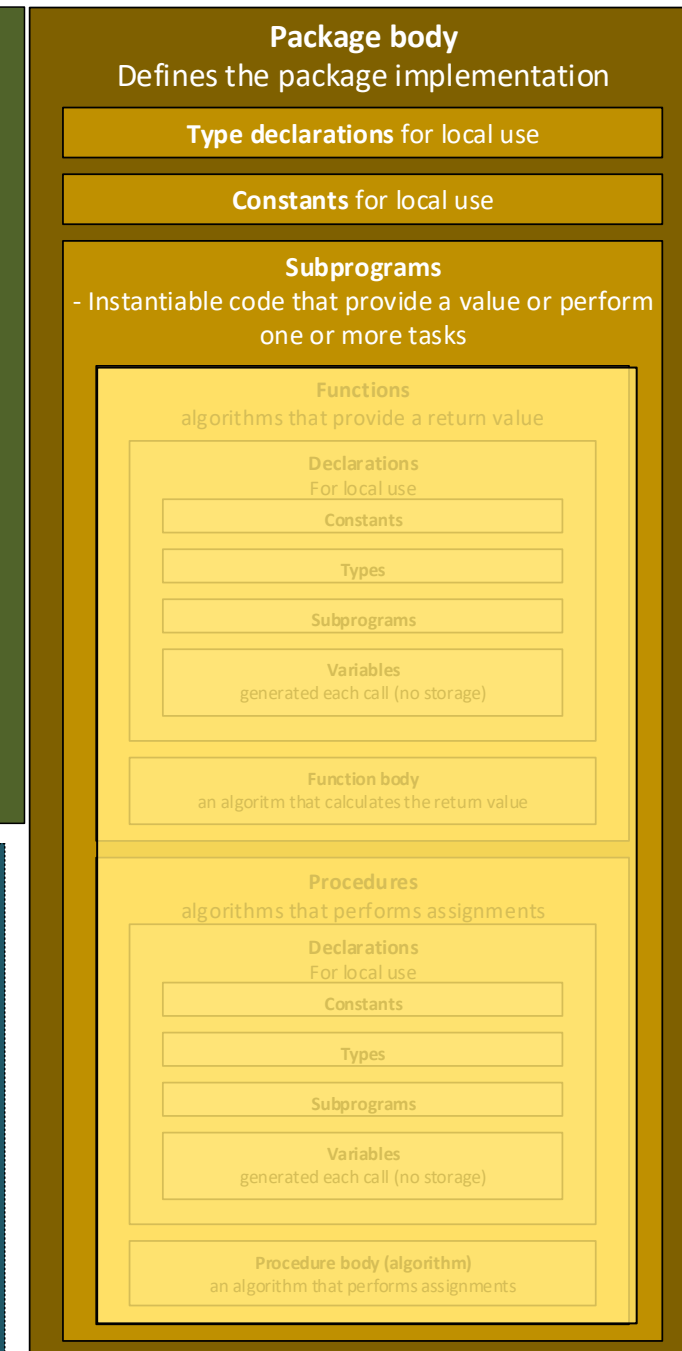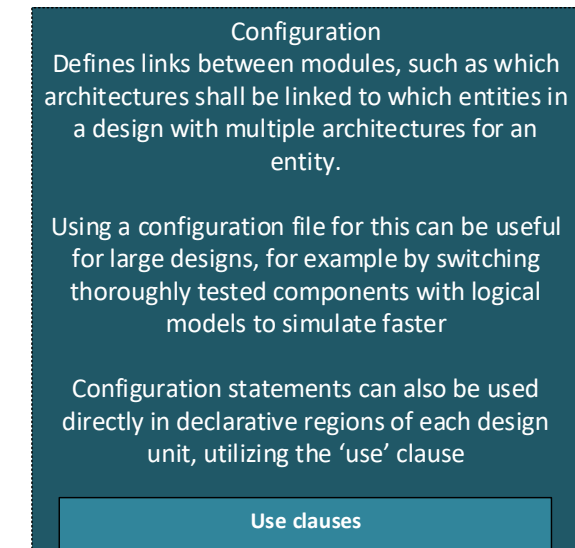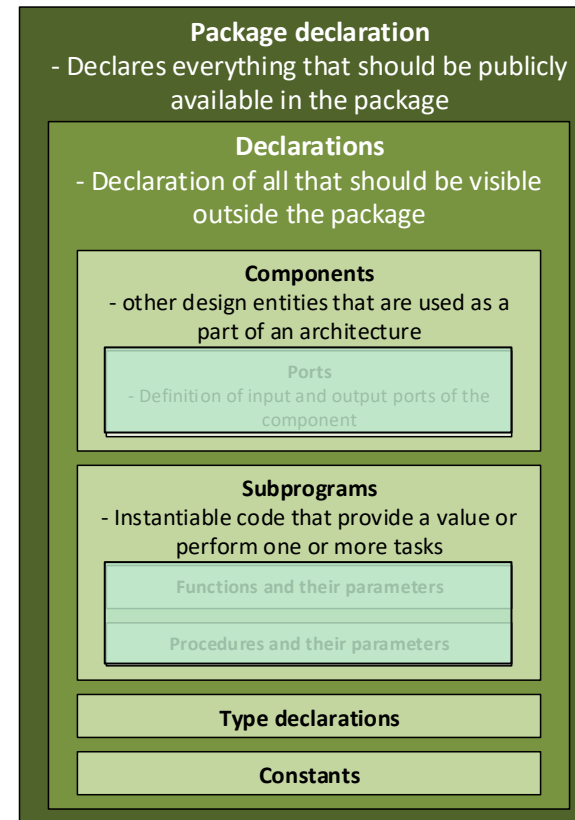- VHDL uses and can be used to create packages
- We will almost always use packages in precompiled libraries.
- Configuration files can be used to specify which components or architectures that shall be used in (large) designs
 - (Not a primary concern for in3160)



VHDL Entity and Architecture


 
- Entity defines Input and Output ports in the design
 - There is only one entity in a vhdl file..
- Architecture defines what the design does.
 - There can be several architectures for an entity
 - Architectures, may be defined using different styles (next slide)
 - “RTL” and “Dataflow” are names providing information;
 - changing these names would not change function.



```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
```

```
entity D_flipflop is
port(
    clk: in std_logic;
    D : in std_logic;
    Q : out std_logic
);
end entity D_FLIPFLOP;
```
  
```
architecture RTL of D_flipflop is
begin
    process (clk) is
    begin
        if rising_edge(clk) then
            Q <= 'D';
        end if;
    end process;
end architecture RTL;
```



```
architecture data_flow of D_flipflop is
    signal e, f, g, h, i, j, k, l: std_logic;
begin
    -- concurrent statements
    e <= NOT (D AND clk);
    f <= NOT (e AND clk);
    g <= NOT (e AND h);
    h <= NOT (f AND g);
    i <= NOT (g AND NOT clk);
    j <= NOT (h AND NOT clk);
    k <= NOT (l AND i);
    l <= NOT (k AND j);
    Q <= k;
end architecture data_flow;
```

4 main abstraction levels

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
```

```
entity D_flipflop is
port(
  clk: in std_logic;
  D: in std_logic;
  Q: out std_logic
);
end entity D_flipflop;
```

```
architecture RTL of D_flipflop is
begin
  process (clk) is
  begin
    if rising_edge(clk) then
      Q <= 'D';
    end if;
  end process;
end architecture RTL;
```

```
architecture data_flow of D_flipflop is
  signal e, f, g, h, i, j, k, l: std_logic;
begin
  -- concurrent statements
  e <= not (D and clk);
  f <= not (e and clk);
  g <= not (e and h);
  h <= not (f and g);
  i <= not (g and not clk);
  j <= not (h and not clk);
  k <= not (l and i);
  l <= not (k and j);
  Q <= k;
end architecture data_flow;
```

RTL, register transfer level

- high level
- easy to read
- describes registers and what happens between them
- «default» for sequential logic

Data Flow

- typically used for optimization
- will easily become unreadable if used extensively.
- *Use higher level code unless absolutely necessary*

Behavioral

- *Simulation models only = Software*
- Not for synthesis or implementation

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity my_thing is
port (
  A: in std_logic;
  B: in std_logic_vector(5 downto 0);
  C, D, E, F: in std_logic;
  G: out std_logic;
  H: out std_logic_vector(64 downto 0);
  I: out std_logic
);
end entity my_thing;
```

```
architecture structural of my_thing is
  signal js: std_logic;
  signal ks: std_logic_vector(64 downto 0);
  signal ls: std_logic;

  component apple is
  port (
    A: in std_logic;
    B: in std_logic_vector(5 downto 0);
    C: out std_logic;
    D: out std_logic_vector(64 downto 0)
  );
end component;

  component pear is
  port (
    A, B, C: in std_logic;
    D, E: out std_logic
  );
end component;

  component banana is
  port (
    smurf: in std_logic_vector(64 downto 0);
    cat, dog, donkey: in std_logic;
    horse: out std_logic;
    monkey: out std_logic_vector(64 downto 0)
  );
end component;


begin -- port map (component => My_thing)
  U1: apple port map(
    A => A,
    B => B,
    C => js,
    D => ks
  );

  U2: pear port map(
    A => D,
    B => E,
    C => F,
    D => ls,
    E => I
  );

  U3: banana port map(
    smurf => ks,
    cat => js,
    dog => C,
    donkey => ls,
    horse => G,
    monkey => H
  );
end architecture structural;
```

Structural

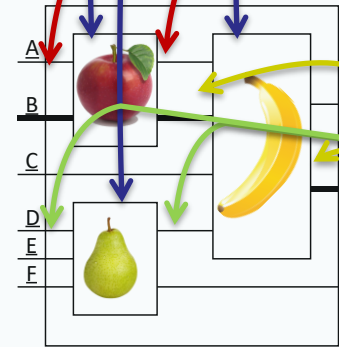- Ties components together
- Typically used in test benches, and when using predefined components




```
begin -- port map (component => My_thing)
  U1: apple port map(
    A => A,
    B => B,
    C => js,
    D => ks
  );

  U2: pear port map(
    A => D,
    B => E,
    C => F,
    D => ls,
    E => I
  );

  U3: banana port map(
    smurf => ks,
    cat => js,
    dog => C,
    donkey => ls,
    horse => G,
    monkey => H
  );
end architecture structural;
```

Ports and signals

- Ports define the entity interface
 - IN:
 - *can only be read*
 - cannot be driven or assigned internally
 - OUT:
 - *can only be driven*
 - (In VHDL 2008, output ports can be read as an internal signal).
 - Should be assigned in the architecture
 - It is bad practice not to do so.
 - INOUT
 - *Can be both driven and read*
(typical use is for buses)
- Signals are internal
 - For connecting internal modules, subprograms and processes.

 

```
library IEEE;
  use IEEE.std_logic_1164.all;

entity my_entity is
  port(
    Ain      : in      std_logic;
    Binout   : inout   std_logic;
    Cout     : out     std_logic
  );
end entity my_entity;

architecture dataflow of my_entity is
  signal enb, s1, s2, s3, s4 : std_logic;

begin
  -- ...

  s1 <= Ain;
  Cout <= s2;
  -- reading INOUT is OK
  s3 <= Binout;
  -- setting INOUT should implement tri-state
  Binout <= s4 when enb else 'Z';

end architecture dataflow;
```

Ports continued


INOUT is for tying input and output to the same pin

- **should** implement tristate functionality.
- 'Z' means it is not driven (tristate)
- Typically to be used when connecting a bus with multiple drivers.

DO NOT use INOUT for convenience!

- The compiler will not alert you if you are driving from two sources simultaneously.
 - *May cause electrical faults*
- INOUT may infer inferior structures (long delays)

 use an extra signal unless you need to assign both input and output to the same physical pin (location).



```
library IEEE;
use IEEE.std_logic_1164.all;

entity my_entity is
  port(
    Ain      : in    std_logic;
    Binout   : inout std_logic;
    Cout     : out   std_logic
  );
end entity my_entity;

architecture dataflow of my_entity is
  signal enb, s1, s2, s3, s4 : std_logic;

begin
  -- ...

  s1 <= Ain;
  Cout <= s2;
  -- reading INOUT is OK
  s3 <= Binout;
  -- setting INOUT should implement tri-state
  Binout <= s4 when enb else 'Z';

end architecture dataflow;
```

Statements and assignments

- Statements and processes
 - defines how a digital circuit works
 - assign drivers to signals
 - All statements must be valid at all times
 - A circuit may have sequential behavior...
 - But all logic is present and functional at all times
 - Processes are complex statements
 - Assigns values to one or more signals
 - Can have local variables.. (more on those later)
 - A signal can only be assigned once in an architecture
 - We do not want two circuits to apply voltage on the same wire...



Examples:

```
with input select isprime <=
  '1' when x"1" | x"2" | x"3" | x"5" | x"7" | d"11" | x"d",
  '0' when others;
```



```
process(Reset, Clock) is
  variable Q : Unsigned(7 downto 0);
begin
  if Reset = '0' then
    Count <= zero_byte;
  elsif rising_edge(Clock) then
    Q :=
      unsigned(Count)    when Enable else
      unsigned(Data)     when not Load else
      unsigned(Count) + 1 when not Mode else
      dec_count(unsigned(Count));
    Count <= std_logic_vector(Q);
  end if;
end process;
```

«Vectors»

- `signal my_sig std_logic;`

  

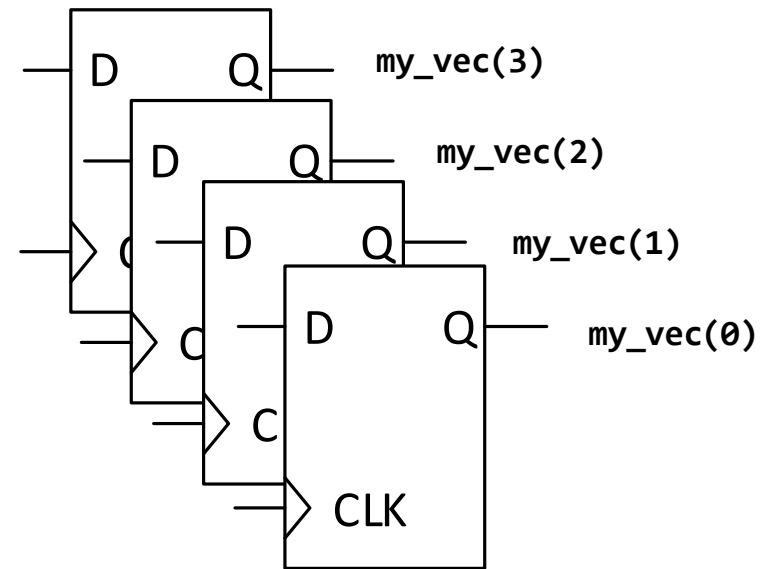 - `signal my_vec std_logic_vector(3 downto 0);`



Signals and variables

- Signals are for inter-architecture communication
 - Between processes, modules and subprograms
- Variables are subprogram(or process)-internal
 - To make code clearer, and more local.
- Example note:
 - placement of s&v declarations
 - Signal assignment order is irrelevant outside processes

```
architecture example of sigvar is
  -- (signal) declarations
  signal S, T : std_logic;

begin
  -- statements
  S <= A and B;

  process (A,B) is
    -- (variable) declarations
    variable V : std_logic;
  begin
    -- process body
    V := '0';
    -- ...

  end process;

  X <= S XOR T;
end architecture;
```


Signal and variable assignment

- Signals are assigned concurrently in statements
 - both in and outside processes
 - Signals are assigned using <=
 - Signals uses event based updates
 - ie after a process is complete.
- Variables can only be used inside processes and subprograms
 - Variables are assigned using :=
 - Variables are updated immediately in simulation
 - *Processes can have variables store values*
 - *Initialized at the beginning of simulation*
 - *Subprograms (procedure, function) can not have variables store values*
 - *initialized on every call*


```
A <= B; -- A reads B, or A is assigned to B's ouput,  
        -- (A is a signal)
```

```
C := B; -- C is given B's value, C is a variable  
        -- variables are used internally in processes.
```

```
D(6 downto 0) <= E(3 downto 1) & (others => '0');  
        -- D is a vector having 7 input signals  
        -- D(6) <= E(3)  
        -- D(5) <= E(2)  
        -- D(4) <= E(1)  
        -- D(3 downto 0) <= "0000"
```

Processes

- A process is one (concurrent) statement
 - Ensures one driver for each signal by using priority.
 - "Signals are only updated only once"..
 - The process body has sequential *priority*
 - Last assignment takes precedence over previous.
 - Variables *can* be assigned multiple times within a process body(!)
 - They *can* act as several signals
 - » Generally this should be avoided
 - sensitivity list
 - determines when the process body is invoked *during simulation*
 - *Event triggered*
 - *Can* be used to make sequential logic
 - Clocked events infers flipflops (or latches)

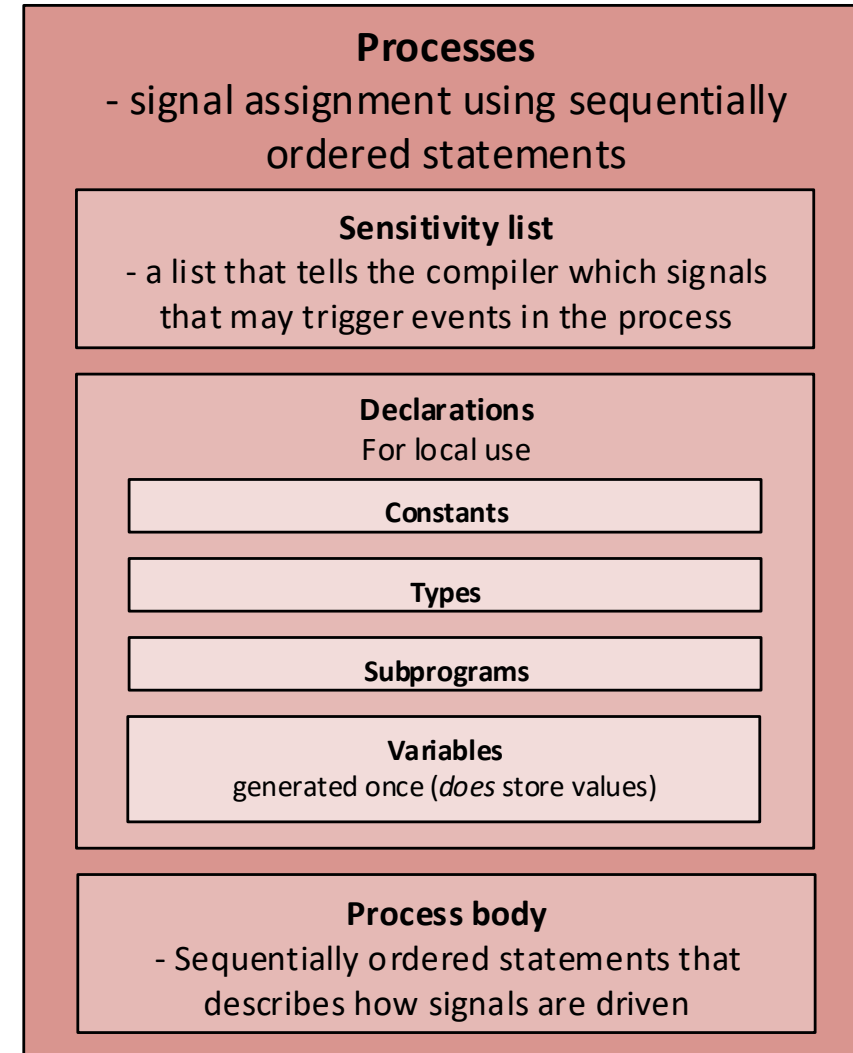

Process example

(this example \neq good code)

```
library IEEE;
use IEEE.std_logic_1164.all;

entity sigvar is
  port(
    A, B : in  std_logic;
    X    : out std_logic
  );
end entity sigvar;
```

- The use of V would not be allowed a signal outside a process.
- A variable can be used in place of multiple physical signals within a process. (= bad practice...)
- Signals will be assigned one driver in a process.

```
architecture example of sigvar is
  -- declarations
  signal S, T : std_logic;

begin
  -- statements
  S <= A and B;

  process (A,B) is
    -- decalarations
    variable V : std_logic;

  begin
    -- process body
    V := '0';
    if (A = '1') then
      V := '1';
    end if;
    if (B = '1') then
      V:= '1';
    end if;
    T <= V;
  end process;

  X <= S XOR T;
end architecture;
```


Libraries and Data types

- VHDL is built upon use of libraries and packages.
- You can both use existing ones, and create your own.
- Most used is the IEEE library, which contains the most used data types and functions
 - The built-in standard (std) package, containing:
 - bit, integer, natural, positive, boolean, string, character, real, time, delay_length
 - std_logic_1164 (which defines the STD_LOGIC type)
 - numeric_std (numeric operations for std_logic_vectors)
 - std_logic_textio (to provide IO during simulation)
 - numeric_bit (numeric operations for bit vectors)
 - etc.




STD_LOGIC TYPE (requires std_logic_1164 package from IEEE library)

- **STD_LOGIC** is a **type** that has the following possible values
 - ‘U’ Uninitialized (Typically seen in simulation before initializing values)
 - ‘X’ Unknown (typically when a signal is driven to both 0 and 1 simultaneously)
 - ‘0’ **Driven low**
 - ‘1’ **Driven High**
 - ‘Z’ **Tristate**
 - ‘W’ Weak unknown (when driven by two different weak drivers)
 - ‘L’ Weak ‘0’ (Typically for simulating a pulldown resistor)
 - ‘H’ Weak ‘1’ (Typically for simulating a pullup resistor)
 - ‘_’ Don’t care (Typically for assessing results in simulator).
- **You will only *assign* synthesizable signals to ‘0’, ‘1’ and ‘Z’**
- Type **STD_LOGIC_VECTOR** is array (NATURAL range <>) of **STD_LOGIC**
 - STD logic vector is used for hardware. For simulation, other types (such as integer) may be faster. Thus we use **STD_LOGIC** for hardware interactions, and other types when possible for test bench code.

std_logic -- values

 


Value	Name	Usage
'U'	Uninitialized state	Used as a default value
'X'	Forcing unknown	Bus contentions, error conditions, etc.
'0'	Forcing zero	Transistor driven to GND
'1'	Forcing one	Transistor driven to VCC
'Z'	High impedance	3-state buffer outputs
'W'	Weak unknown	Bus terminators
'L'	Weak zero	Pull down resistors
'H'	Weak one	Pull up resistors
'_'	Don't care	Used for synthesis and advanced modeling

   


-- multiple drivers

signal c : std_logic;

 

Signal A/B	'U'	'X'	'0'	'1'	'Z'	'W'	'L'	'H'	'_'
'U'	'U'	'U'	'U'	'U'	'U'	'U'	'U'	'U'	'U'
'X'	'U'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	'X'
'0'	'U'	'X'	'0'	'X'	'0'	'0'	'0'	'0'	'X'
'1'	'U'	'X'	'X'	'1'	'1'	'1'	'1'	'1'	'X'
'Z'	'U'	'X'	'0'	'1'	'Z'	'W'	'L'	'H'	'X'
'W'	'U'	'X'	'0'	'1'	'W'	'W'	'W'	'W'	'X'
'L'	'U'	'X'	'0'	'1'	'L'	'W'	'L'	'W'	'X'
'H'	'U'	'X'	'0'	'1'	'H'	'W'	'W'	'H'	'X'
'_'	'U'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	'X'

Tri-state buffer

 

- Hardware can only read '0' or '1'
- We can set tristate (high impedance) to allow other sources to drive a bus.
- Simulation tools can use all possible `STD_LOGIC` values.

```
A <= B when EN = '1' else 'Z';
```

```
-- ekvivalent med  
TRISTATE:  
process (B,EN)  
begin  
    if EN = '1' then  
        A <= B;  
    else  
        A <= 'Z';  
    end if;  
end process;
```


VHDL operator priority

- Functions are interpreted from left to right (in reading order).
- **Use paranthesis to govern priority!**

Prioritet	Operator klasse	Operatorer
1 (first)	miscellaneous	** , abs, not
2	multiplying	* , /, mod, rem
3	sign	+ , -
4	adding	+ , -, &
5	Shift	sll, srl, sla, sra, rol, ror
6	relational	=, /=, <, <=, >, >=, ?=, ?/=, ?<, ?<=, ?>, ?>=
7	logical	And, or, nand, nor, xor, xnor
8 (last)	condition	??

Examples (elaboration on next page):

a <= a **or** b **and** c; **==** a <= (a **or** b) **and** c;


z <= a **and not** b **and** c; **==** z <= a **and** (**not** b) **and** c; **==** z <= c **and** (a **and** (**not** b));

y <= a **and not** (b **and** c); **-- z=1 kun for a=1, b=0, c=1. y=1 for a=1 og (b eller c)=0.**


VHDL operator priority

 Examples:

`x <= a or b and c;` == `x <= (a or b) and c;`




(What you might want)

 

(what you actually will get)

Try

`a := '1'`
`b := '1'`
`c := '0'`

 

`z <= a and not b and c;` == `z <= a and (not b) and c;` == `z <= c and (a and (not b));`
`y <= a and not (b and c);`



Bit operators and reduction operator

- **and**, **or**, **not**, **xor**, **xnor** operators will work at bit level when they are placed between two signals or vectors.

- $y1 \leftarrow a \text{ and } b$; -- is equal to the lines below

$y1(3) \leftarrow a(3) \text{ and } b(3)$;

$y1(2) \leftarrow a(2) \text{ and } b(2)$;



$y1(1) \leftarrow a(1) \text{ and } b(1)$;

$y1(0) \leftarrow a(0) \text{ and } b(0)$;

- In VHDL2008 (not earlier) these operators can be used for reduction

$y \leftarrow \text{and } a$; -- is equal to the figure ->

  - **xor** can be used this way to generate (even) parity for a signal.



VHDL Bit String Literals

Binary, Decimal, hexadecimal, Octal, Unsigned, Signed

<ant bit><U/S><B/D/O/X><numbers of type B/D/O/X >

B"1111_1111_1111" -- Equivalent to the string literal

"111111111111".

X"FFF" -- Equivalent to B"1111_1111_1111".

O"777" -- Equivalent to B"111_111_111".

X"777" -- Equivalent to B"0111_0111_0111".

B"XXXX_01LH" -- Equivalent to the string literal

"XXXX01LH"

UO"27" -- Equivalent to B"010_111"

UO"2X" -- Equivalent to B"011_XXX"

SX"3W" -- Equivalent to B"0011_WWWW"

D"35" -- Equivalent to B"100011"

12UB"X1" -- Equivalent to B"0000_0000_00X1"

12SB"X1" -- Equivalent to B"XXXX_XXXX_XXX1"

12UX"F-" -- Equivalent to B"0000_1111_----"

12SX"F-" -- Equivalent to B"1111_1111_----"

12D"13" -- Equivalent to B"0000_0000_1101"

12UX"000WWW" -- Equivalent to B"WWW_WWW_WWW"

12SX"FFFC00" -- Equivalent to B"1100_0000_0000"

12SX"XXXX00" -- Equivalent to B"XXXX_0000_0000"

8D"511" - Error (> 2^8)

8UO"477" - Error (>2^8)

8SX"0FF" - Error (cannot have 255 using 8 bit signed)

8SX"FXX" - Error (cannot extend beyond 8 bit)

IN3160

Code Layout (15 min)



Overview

- Why bother thinking about layout?
- What constitutes a good layout scheme?
- Basic layout types
- Indentation
- Paragraphs and spaces

Why bother thinking of layout?

```
pRoCeSS(clock,reset) bEGIn iF resET then oUTpuT <="0000"; eISE IF RiSiNG_eDge  
(ClOck) tHEN cASe s Is WhEn 1=>outPUT<= "0001"; wHEN 2046=> oUTpuT <="0010";WhEn  
31=>OutPut<="0100";when OTHERs=>OUTput <= «1111"; end cASe; END if;END proCESS; --  
Q.E.D.
```

A good layout scheme...

1. ...accurately matches the structure of the code
2. ...improves readability
3. ...affords changes
4. ...is consistent (few exceptions)
5. ...is simple (few rules)
6. ...is easy to use
7. ...is economic

Basic layout types

Block layout



Endline layout



Column layout



Block layout (What you should use *most of the time*)

- Accurately matches structure
- relatively tidy
- readable,
- easy to maintain, etc.

```
process (clock, reset)
begin
  if reset then
    output <= "0000";
  else if rising_edge(clock) then
    case s is
      when 1 => output <= "0001";
      when 2046 => output <= "0010";
      when 31 => output <= "0100";
      when others => output <= "1111";
    end case;
  end if;
end process;
```

Endline layout (*avoid this*)

- Harder to maintain when code changes.
- Looks tidier, but isn't faster than pure block
- Will get messy- poor match of code hierarchy
- Long lines..!

```
process (clock, reset)
begin
  if reset then output <= "0000";
  else if rising_edge(clock) then case s is
    when 1 => output <= "0001";
    when 2046 => output <= "0010";
    when 31 => output <= "0100";
    when others => output <= "1111";
  end case;
  end if;
end process;
```

Column layout (use sparingly)

- Can be easier to read than pure block layout (scanning vertically)
- Harder to maintain.
- Best to use when columns are unlikely to change, and statements are related.
 - Typically used for 2D arrays.

```
process (clock, reset)
begin
  if reset then
    output <= "0000";
  else if rising_edge(clock) then
    case s is
      when 1 => output <= "0001";
      when 2 => output <= "0010";
      when 333 => output <= "0100";
      when others => output <= "1111";
    end case;
  end if;
end process;
```

Indentation

- *Use indentation to match code hierarchy*
- 2-4 spaces has been proven most efficient
 - *Along with a monospace font, such as courier, consolas..*
- Use space rather than tabulator sign.
 - Tabulator spaces may be interpreted differently in different editors.
 - Most editors can be set up for this.
- Example:

```
entity ent_name is
  generic (
    generic_declaration_1;
    generic_declaration_2;
  );
  port(
    port_declaration_1;
    port_declaration_2;
  );
end entity ent_name;
.
.
.
process (sensitivity_list)
  declaration_1;
  declaration_2;
begin
  statement_1;
  statement_2;
end process;
```

Paragraphs and comments

- Paragraphs should be used to separate chunks that does not need to be read all at once.
- Paired with comments that this make for good readability
- Comments should be indented as according to the code it is referring to.

```
-- Find character in text RAM corresponding to x, y
text_ram_x := pixel_x / FONT_WIDTH;
text_ram_y := pixel_y / FONT_HEIGHT;
display_char := text_ram(text_ram_x, text_ram_y);

-- Get character bitmap from ROM
ascii_code := character'pos(display_char);
char_bitmap := FONT_ROM(ascii_code);

-- Get pixel value from character bitmap
x_offset := pixel_x mod FONT_WIDTH;
y_offset := pixel_y mod FONT_HEIGHT;
pixel := char_bitmap(x_offset)(y_offset);
```

Line length and wrapping

- Try to keep line length within reasonable limits
 - 80, 100 and 120 characters is widely used.
- When wrapping lines:
 - break at a point that clearly shows it is incomplete, such as
 - after opening paranthesis
 - after operators or commas (&, +, -, *, /)
 - after keywords such as «and» or «or»
 - consider one item per line...

```
-- one item/line + named association
Paddle <= update_sprite(
  sprite => paddle,
  sprite_x => paddle_position.x + paddle_increment.x,
  sprite_y => paddle_position.x + paddle_increment.y,
  raster_x => vga_raster_x,
  raster_y => vga_raster_y,
  sprite_enabled => true
);
```

```
-- several items/line
paddle <= update_sprite(paddle, paddle_position.x + paddle_increment.y,
  paddle_position.y + paddle_increment.y, vga_raster_x, vga_raster_y, true);
```

Spaces

- Punctuation symbols
(comma, colon, semicolon)

- use spaces as you would in regular prose:
 - Never add space before punctuation symbols
 - Always add space after punctuation symbols
- *no exceptions*

- Parentheses

- Add a space before opening parenthesis.
- Add a space or punctuation symbol after closing parenthesis
- Except:
 - array indices and routine parameters;
 - *expressions*.

```
-- too much
function add ( addend : signed ; augend : signed ) return signed ;

-- better
function add(addend: signed; augend: signed) return signed;
```

```
-- consider this expression:
a + b mod c sll d;

-- better
(a + (b mod c)) sll d;
```

```
-- consider
(-b+sqrt(b**2-4*a*c))/2*a;

-- better
(-b + sqrt(b**2 - 4*a*c)) / 2*a;

-- too much
( - b + sqrt( b ** 2 - 4 * a * c ) ) / 2 * a;
```


Naming conventions - Letter case and underscores

```
noconventionnaming -- don't go there
UpperCamelCase -- OK used consequently
lowerCamelCase -- OK used consequently
snake_case or underscore_case
SCREAMING_SNAKE_CASE or ALL_CAPS
```

- Do not use ALL_CAPS too frequently.
- Use editor colors/ **bold** for highlighting **keywords**
- Try to avoid mixing snakes_andCamels.
- Treat acronyms/ abbreviations as words
 - "UDPHDRFromIPPacket" **vs**
"UdpHdrFromIpPacket" **vs**
"udp_hdr_from_ip_packet"
- VHDL packages tend to favour snake_case and ALL_CAPS
- *Suggestion:*
 - Use snake_case for all **names** except **constants** and **generics** that use ALL_CAPS

Suggested reading, Mandatory assignments

- D&H:
 - 1.5 p 13-16
 - 3.6 p 51-54
 - 6.1 p 105-106
- Oblig 1: «Design Flow»
- Oblig 2: «VHDL»
 - See canvas for further instruction.

(Layout is lecture only)