

Oblig 4

Structural code using component instantiation

IN3160 / IN4160

Version 2.2 2023-02-02

In this exercise, we will look at instantiation of components. The attached code in `dff.vhd` is a bit-register (flipflop) with synchronous reset. The register will receive the next value on each rising edge of the `clk`, and this value will either be 0 when `rst_n` is active (low) or `din` when the reset signal is inactive. For this exercise, the `dff` component shall be used *without modifications*.

The shift registers implemented in this assignment should have *serial input and both parallel and serial output* (both “SIPO” and “SISO” functionality). The shift registers shall have single bit input, there is no need to construct parallel input¹.

 


Figure 1: 8 bit shift register with serial input and parallel output

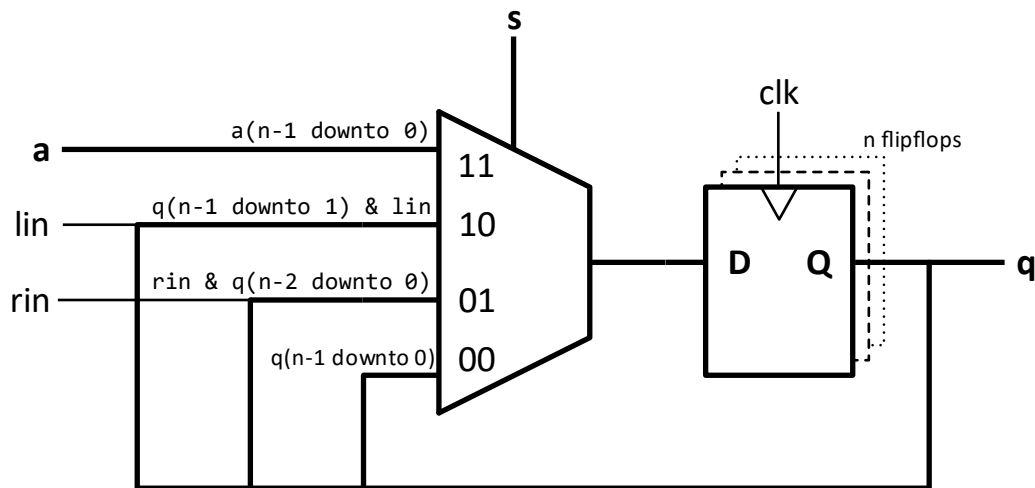


Figure 2: Bi-directional shift register with parallel load capability

¹ Shift registers are typically used for serial transceivers. Most known is “UART” - Universal Asynchronous Receiver Transmitter. Fast board-to-board communication are normally never parallel, although you may have several serial transmitters working in parallel, each transmitter works individually to perform fast transfer rates and error correction.

a)

Create an 8-bit shift register by instantiating the component `dff` 8 times, and call this component `shift8`. Use named association in `port map`. Create a test bench that simulates the shift register.

b)

Create a 32-bit shift register by means of the component `dff` and generate the statement. Name this component `shift32`. Use named association in `port map`. Create a test bench that simulates the shift register.

When using python testbenches with cocotb and GHDL, generics in the top level module can be given new values using `SIM_ARGS += -g<GENERIC>` in the makefile.

Example that sets generic "width" to 5:

```
SIM_ARGS +=-gWIDTH=5
```

As long as `+=` is used with `SIM_ARGS`, multiple generics can be set by duplicating the statement for each generic parameter.

c)

Create an n-bit shift register by means of a generic statement. Name this component `shiftn`. Create a test bench that simulates an instantiation of `shiftn` with the length set at 64 bit.

Approval:

VHDL source files and python test bench for the individual questions.