

# IN3170/4170 2021 notes on solutions of the Inspira exam

**These notes are published due to popular demand by the students and are not to be taken as a quality controlled set of solutions** *Make sure that your copy of this examination paper is*

*complete before answering.*

## Abstract

These notes on the IN3170/4170 2021 online exam are published due to popular demand by the students and are not to be taken as either a quality controlled set of solutions nor as being nicely presented and formatted. I just did my best to quickly dump the notes of the online system here together with the tasks.

## Chapter 5

### Solution task 1

$\lambda = 0.05$  with  $\pm 0.002$  tolerance

### Solution task 2

$$v_{GS} = [1.40, 1.41]\text{V}$$

$$V_{sat} = [0.75, 0.76]\text{V}$$

## Chapter 6/7

### Solution task 3

$$R_O = (r_o + R_2) \parallel R_1 = \frac{(r_o + R_2) \cdot R_1}{R_1 + R_2 + r_o}$$

$$G_M = g_m \frac{r_o}{r_o + R_2}$$

$$A = G_M \cdot R_O = g_m \cdot \frac{R_1 \cdot r_o}{R_1 + R_2 + r_o}$$

### Solution task 4

$$g_m = [1000, 1100]\mu\text{A/V}$$

$$r_o = [24500, 25500]\Omega$$

$$A_0 = [26, 27]\text{V/V}$$

$$W = [10.1, 10.2]\mu\text{m}$$

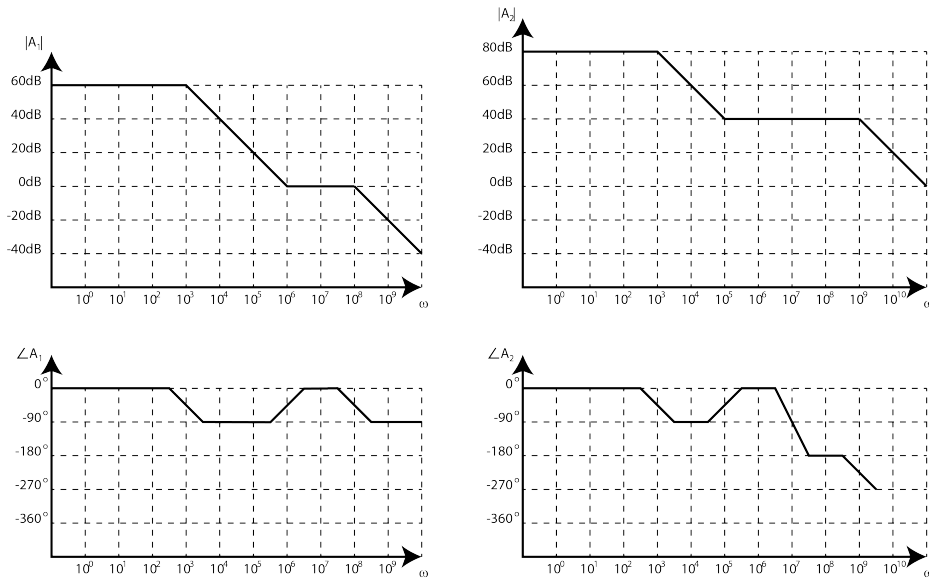


Figure 1: Solution task 7

## Chapter 8

### Solution task 5

$$A = [44, 45] \text{V/V}$$

## Chapter 9/10 and Bode Plots

### Task 6

#### Solution task 6

$$A_{DC} = 30 \text{V/V}$$

$$C_{gd} = [62, 66] \text{fF}$$

### Task 7

#### Solution task 7

See figure 1

## Chapter 15 and Combinational Logic Circuits

### Solution task 8

fastest to slowest: (3,4,2,1)

### Solution task 9

PUN5

### **Solution task 10**

See figure 2

### **Solution task 11**

See figure 3

## **Sequential Logic**

### **Solution task 12**

See figure 4

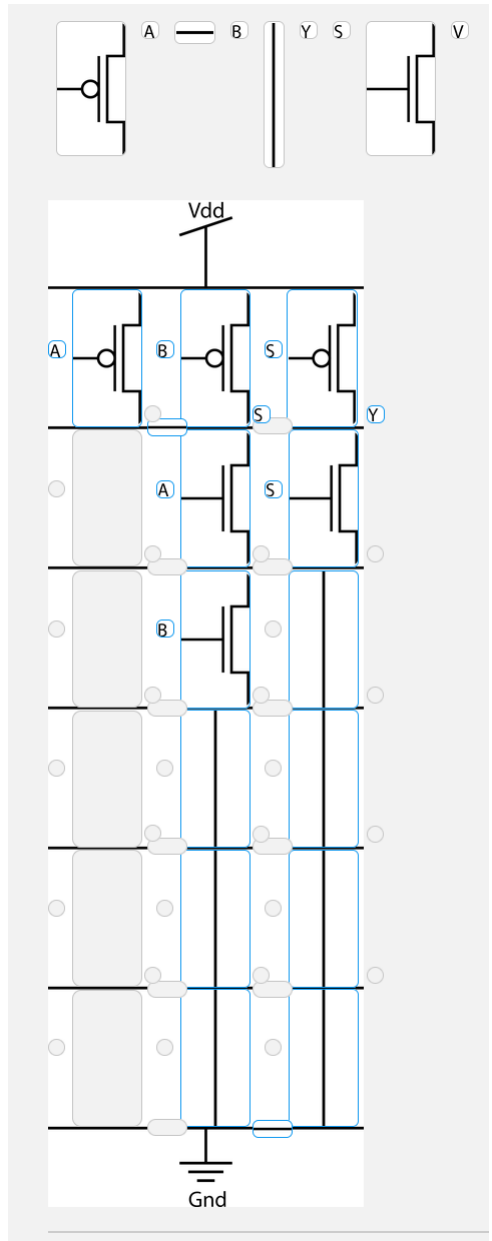


Figure 2: Solution task 10 (one of many correct possibilities)


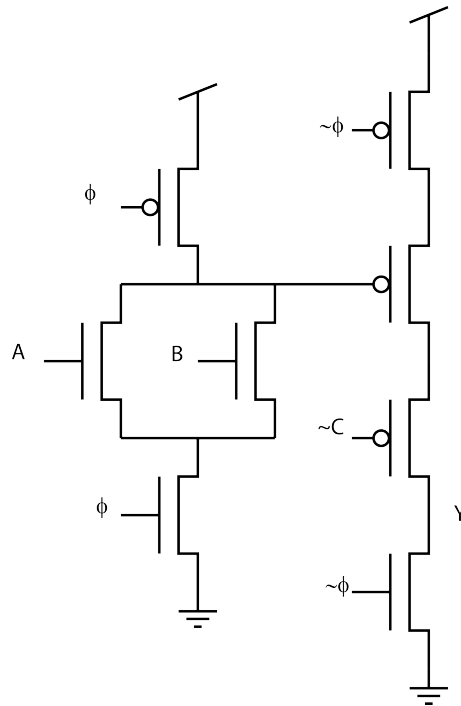
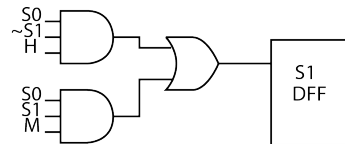
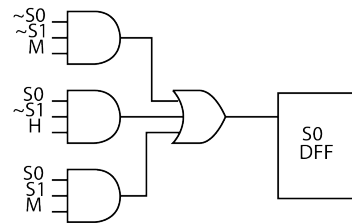


Figure 3: Solution task 11

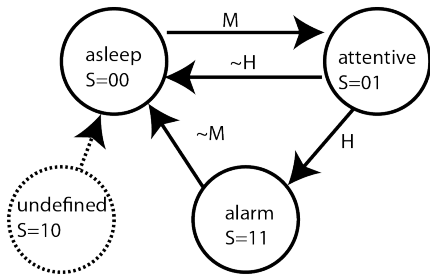

S	M	H	S <sub>next</sub>
00	0	X	00
00	1	X	01
01	X	0	00
01	X	1	11
11	1	X	11
11	0	X	00
10	X	X	00

$$S0 = (\sim S0 * \sim S1 * M) + (S0 * \sim S1 * H) + (S1 * S0 * M)$$

$$S1 = (S0 * \sim S1 * H) + (S0 * S1 * M)$$

Figure 4: Solution task 12