



**UiO** : **Department of Informatics**  
University of Oslo

**IN5230**

**Electronic noise – estimates and countermeasures**

# **Lecture 4**

## **Grounding (Ott3)**



## 3 Grounding (Ott 3)

3.1 AC power distribution and safety grounds

3.2 Signal grounds

3.3 Equipment grounding

3.4 Ground loops

3.5 Low-frequency analysis of common-mode choke

3.6 High-frequency analysis of common-mode choke

3.7 Single ground reference for a circuit

# Types of grounding

- Two kinds of grounding:
  - Power ground (heavy current/safety ground)
  - Signal ground

# 3.1 AC POWER DISTRIBUTION AND SAFETY GROUNDS

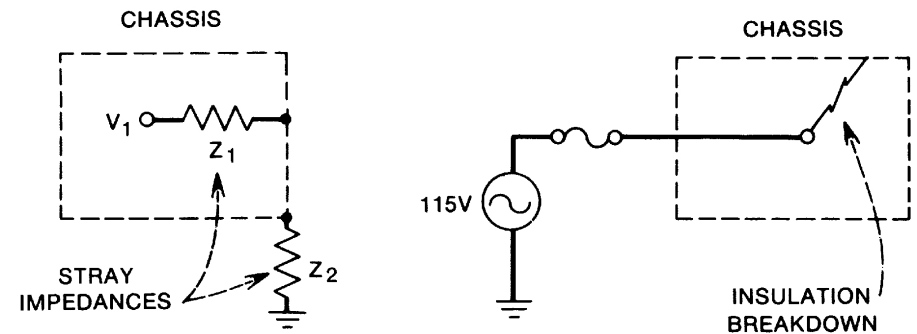


Figure 3-1. Chassis should be grounded for safety. Otherwise, it may reach a dangerous voltage level through stray impedances (left) or insulation breakdown (right).

**Assume the chassis is not grounded ( $Z_2 \gg 0\Omega$ ):**

$V_1$  is an internal point at a high voltage connected to the high voltage mains. The voltage potential on the chassis can be

expressed as:

$$V_{chassis} = \left( \frac{Z_2}{Z_1 + Z_2} \right) V_1$$

Typically  $Z_1$  and  $Z_2$  are both large while the ratio between them may be arbitrary. That means that the voltage on the chassis may be close to  $V_1$ . If an electrically grounded person is touching the chassis he/she may experience an unpleasant electrical shock even though the current is small (small current due to large  $Z_1$ ).


The right side of figur 3-1 shows a more dangerous situation. The figure illustrates an example where the isolation is broken so that  $Z_1$  is close to  $0\Omega$ . Hence the chassis may have a voltage of  $V_1$ . The chassis may deliver a maximum current decided by the fuse. If an electrically grounded person touches the chassis the entire current may pass through his/her body with fatal consequences.

If, on the other hand the chassis was grounded

- The current would pass through the ground cable instead of the person.
- The cable would be low ohmic resulting in a high current making the fuse go within short time with the result that the chassis lose the voltage.
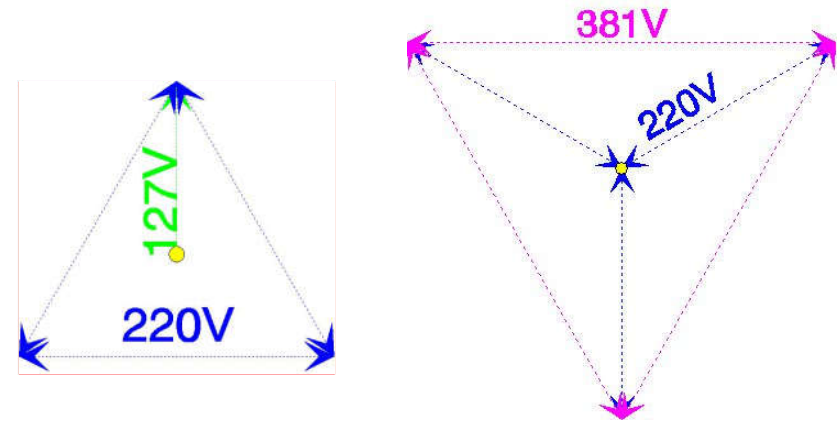
# Mains power systems:

- Norwegian (220V(310V))
- American (115V/220V)



## (Old) Norwegian system (IT- *Isolée Terre*):

The traditional Norwegian system has three phases with 120 degrees between the phases. Ground is in the middle and not used for anything else than security. Loads are connected between pairs of the phases (3 combinations). 220Vrms between two phases (Approx. 127Vrms between all phases and ground.)

Colours: Green or Yellow/Green for ground. Black, white and blue for the three phases. Brown after a switch. Red is not common and should not be used.

## European (and new Norwegian) system (TN-*Terra Neutral*):

The voltage between ground and the three phases are increased to 220V for standard use. The voltage between the phases (381V) are used for more power hungry equipment. This system are used in larger buildings. (Not hospitals!)

Colours: Brown, (black, and grey) for phases (L1,L2, L3), blue for neutral (N) (conducting ground/null-leader) and green/yellow for protective earth (PE).

## American system:

Ground used both for security ground and as fixed current return but in two different cables. Supply phase 115V from ground.

### 115V system:

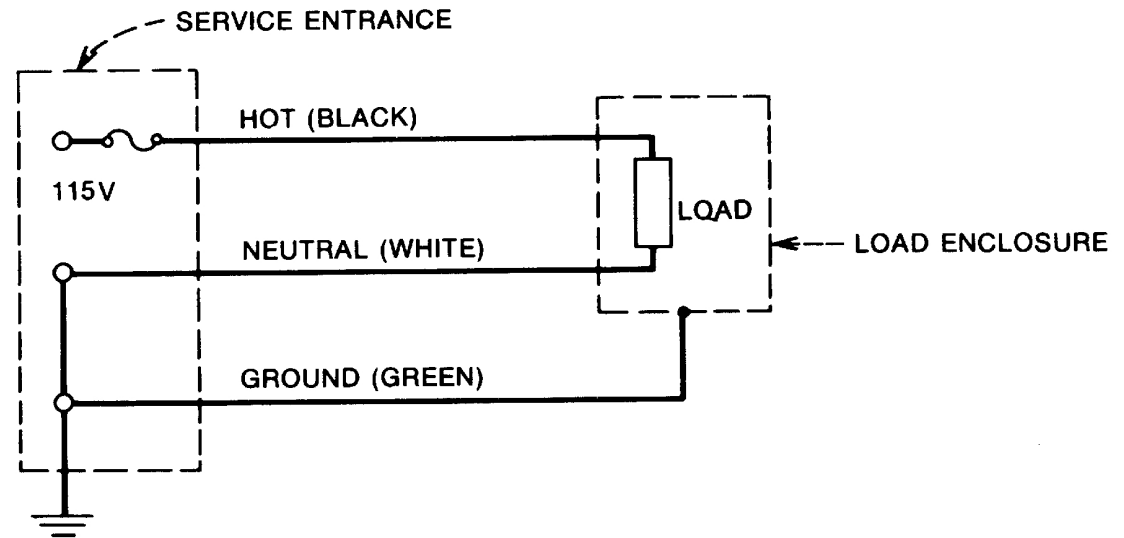


Figure 3-2. Standard 115-V ac power distribution circuit has three leads.

Fuse only on the 115V phase. Ground for return current and security ground connected in local transformer station. Current in ground indicates isolation breakdown and that the equipment has to be inspected. RCD's (Residual-Current Device) (UK), GFCI (Ground Fault Circuit Interrupter) (USA), jordfeilbryter (NO) are automated fuses/switches that breaks the electrical power if the ground current is above **30mA**. Now a requirement in all new wat rooms.

230V system:


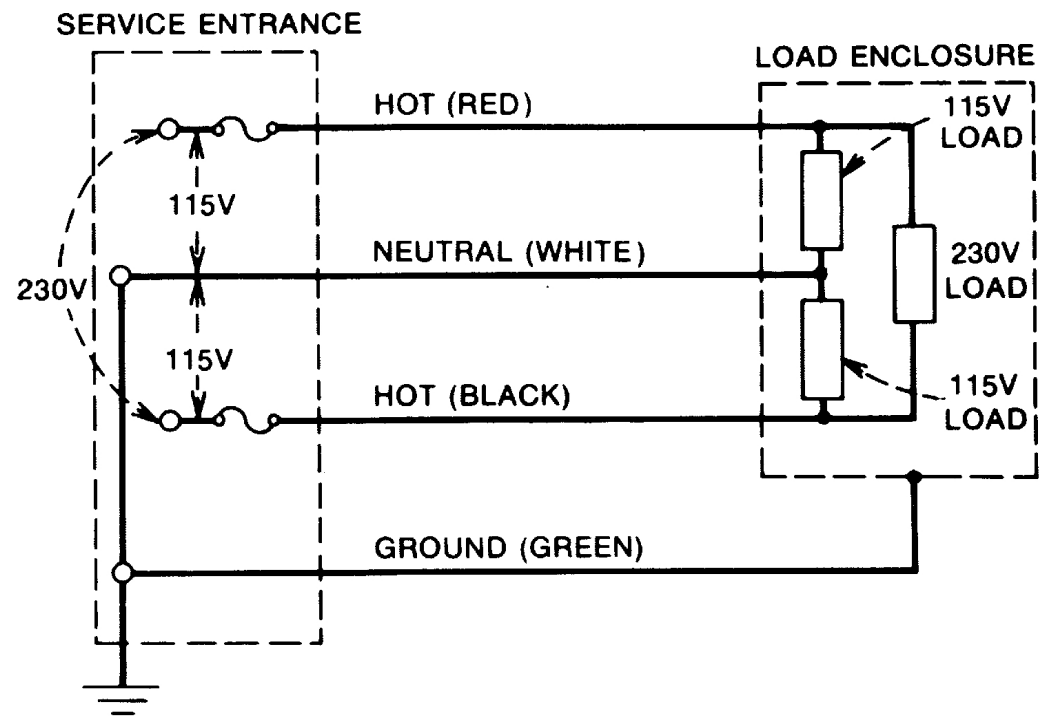


Figure 3-3. Combination 115/230-V ac power distribution circuit has four leads.

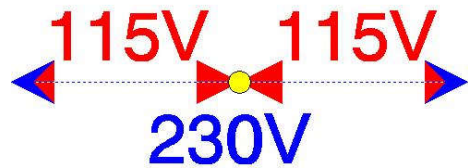

# Ungrounded and grounded safety ground (1/2).

Socket(/outlet/stikkontakt/female) and plug(/støpsel/male).



- A) Ungrounded system. Single isolated. Earlier in «non-conducting rooms» i.e. rooms without water, radiators, preferably upstairs, linoleum floors etc.



- B) Earth/grounded system. Single isolated but grounded shields and grounded conducting materials (metal etc.). Wet rooms (kitchen, bathroom), basement/ground floor, outside, room with doors out on the ground level.




- C) Euro-system. Double isolated. Can be used everywhere.

## Ungrounded and grounded safety ground (2/2).


- Some large rooms may have both, typically a living room with a mini kitchen.
- Now all new installations has to be grounded.
- Grounded plug in ungrounded outlet.
  - If the room is still «non-conducting».
  - Not if the manufacturer requires ground either due to safety or EMC.
- Ungrounded plug in grounded outlet
  - Requires adapter
  - If the equipment does not have a conducting surface. (If it has, it has to be electrically isolated.)
  - Care has to be taken.

## 3.2 SIGNAL GROUND

A low impedance path for return current.

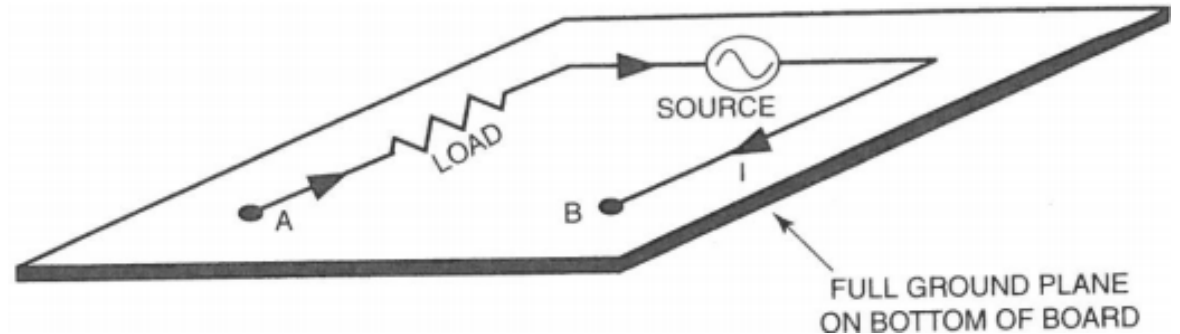

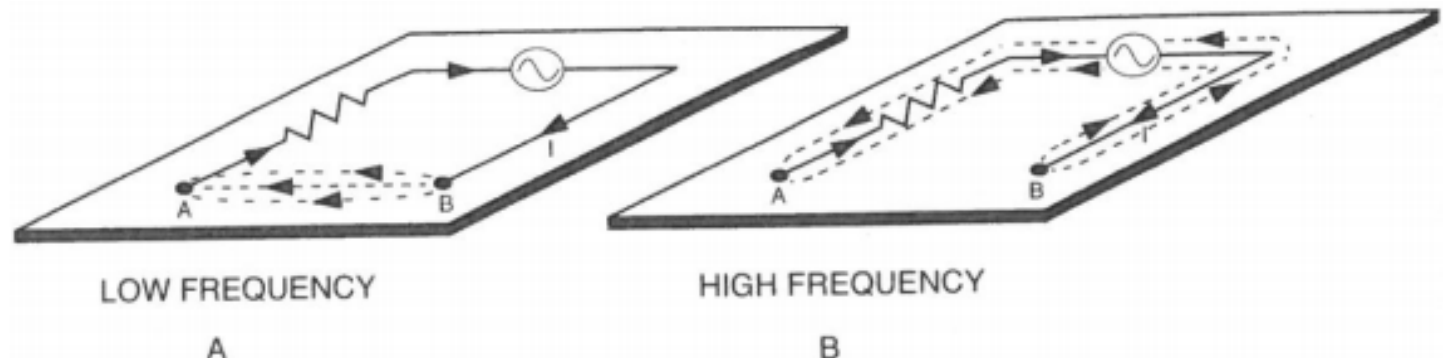A two plane board with signals on top and a ground plane on the bottom plane. At low frequencies the current follows the shortest path while at high frequencies it follows close to the signal path



# Single and multipoint ground

(A low impedance path for return current.)

Three alternative architectures:

1) One point ground, 2) Multi point ground, 3) Hybrid ground

## 1. One point ground

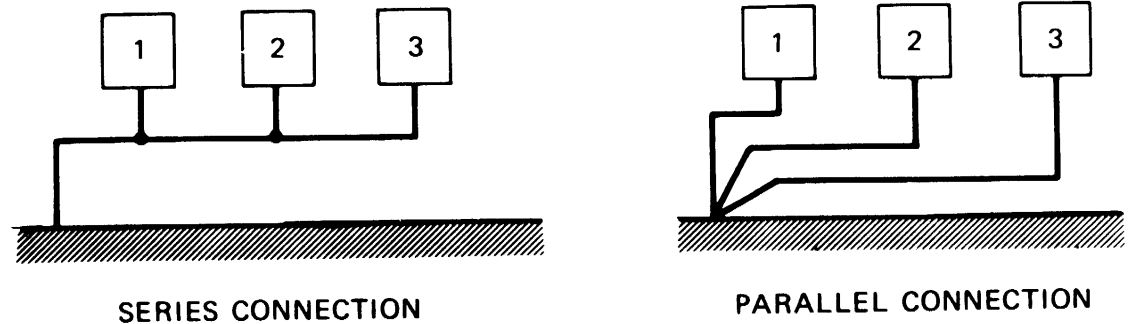


Figure 3-4. Two types of single-point grounding connections.

The serial routing is the most common but also the most noisy.

## 2. Multi point ground


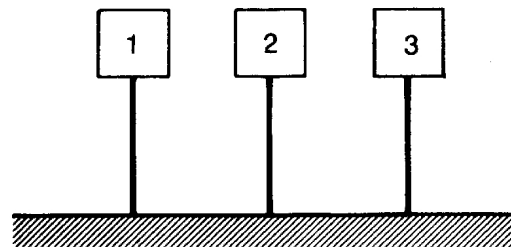


Figure 3-5. Multipoint grounding connections.

# One point ground - serial

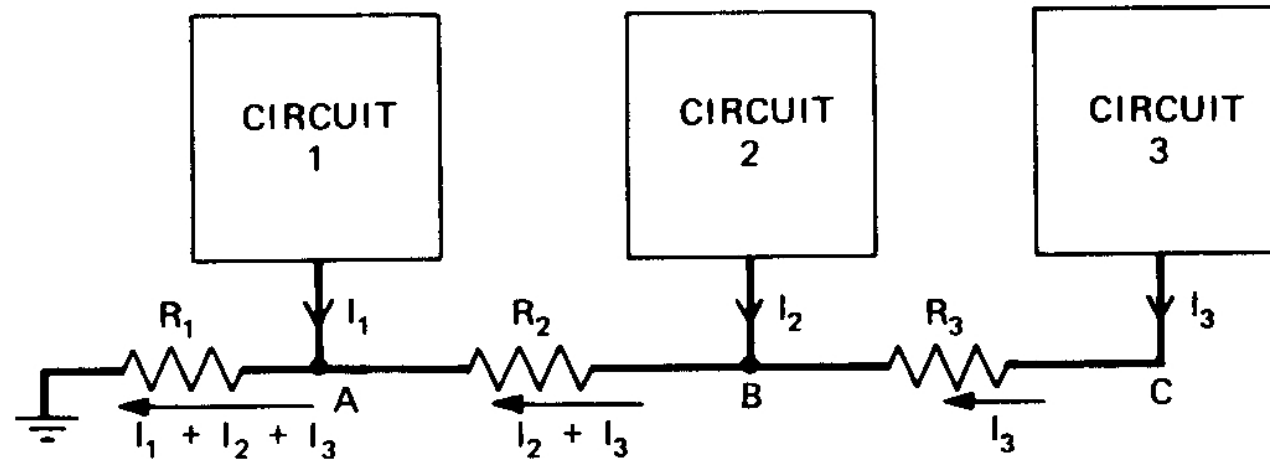


**Figure 3-6.** Common ground system is a series ground connection and is undesirable from a noise standpoint but has the advantage of simple wiring.

$$V_A = (I_1 + I_2 + I_3)R_1$$

$$V_C = (I_1 + I_2 + I_3)R_1 + (I_2 + I_3)R_2 + I_3R_3$$

Single line with significant common noise.

# One point ground - parallel

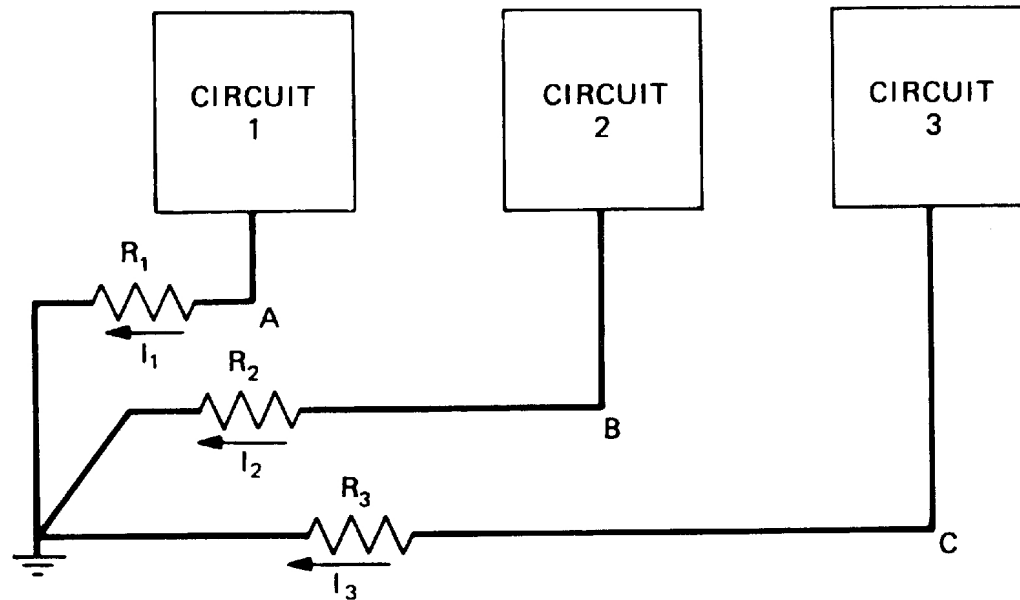

**Figure 3-7.** Separate ground system is a parallel ground connection and provides good low-frequency grounding but is mechanically cumbersome.

$$V_A = I_1 R_1$$

$$V_C = I_3 R_3$$

Less noise current but more wiring.

Not suitable for longer lines and higher frequencies.


$$L \ll \lambda/20.$$

# Serial or parallel one-point?

- Should we use the routing area for a wider, low resistance/low inductance path?
- Or should we use the available area for independent but higher resistive, higher inductive multiple paths?
- If the noise contributions are very different between the loads, they should be split. If they are similar, one wide connector may be better.

One wide wire:					
				R	dl_tot
Three split wires:					
				>3R	dl <(1/3) dl_tot
				>3R	dl <(1/3) dl_tot
				>3R	dl <(1/3) dl_tot
				>3R	dl <(1/3) dl_tot

# Multi point ground

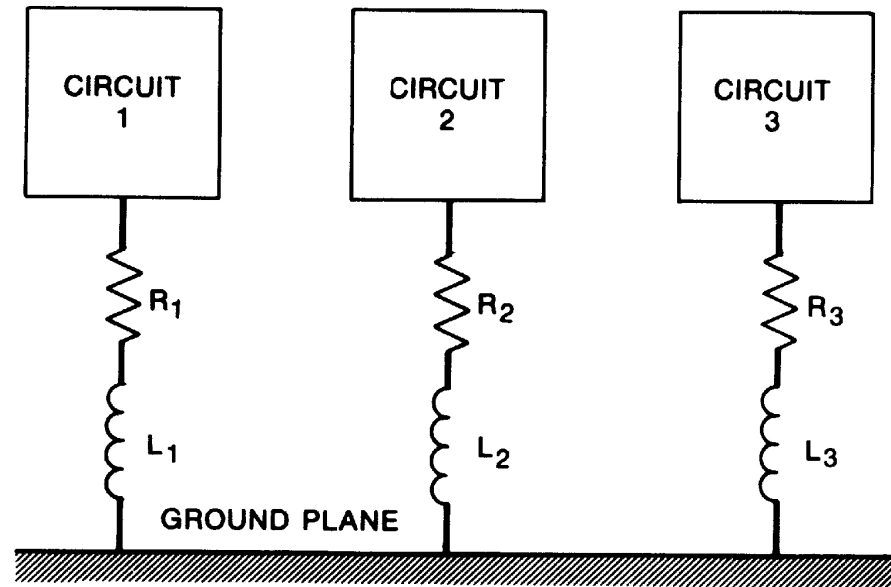


**Figure 3-8.** Multipoint ground system is a good choice at frequencies above 10 MHz. Impedances  $R_1$ – $R_3$  and  $L_1$ – $L_3$  should be minimized.

Used for higher frequencies ( $>10\text{MHz}$ ) and in digital designs when it is important to reduce the inductance because  $\omega L$  may be significant. At lower frequencies when the resistance (say in the ground plane) is more essential than the inductance, this solution should not be used. Instead an one point parallel solution should be selected.




# Hybrid ground (#1/2)

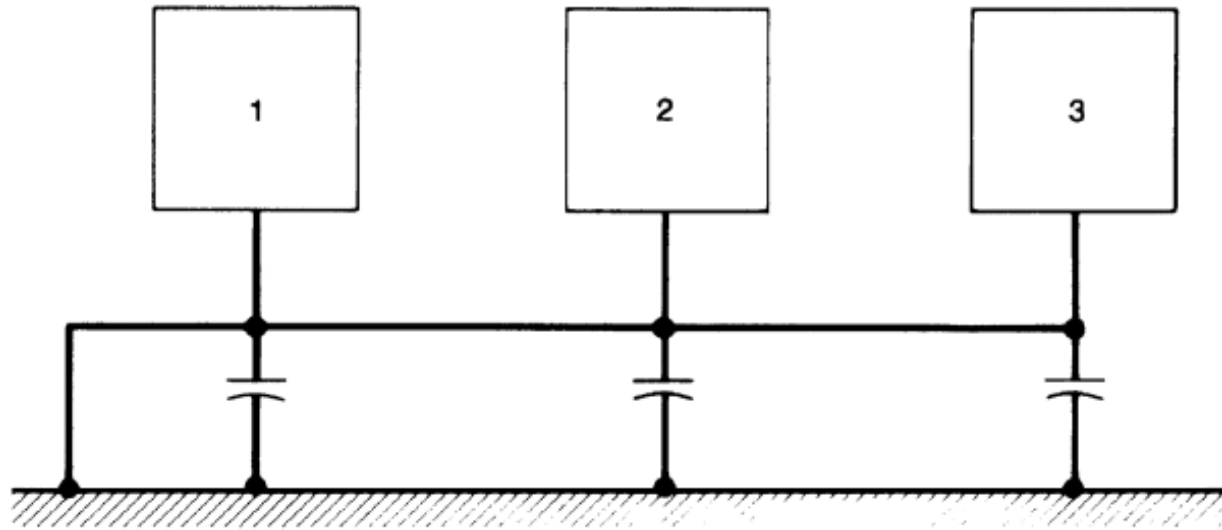

**Figure 3-9.** *A hybrid ground connection that acts as a single-point ground at low frequencies and a multipoint ground at high frequencies.*

Fig. 3.9: Behave as a one point ground at lower frequencies and a multipoint ground at higher frequencies. Used to ground cables and/or shields.

## Hybrid ground (#2/2)

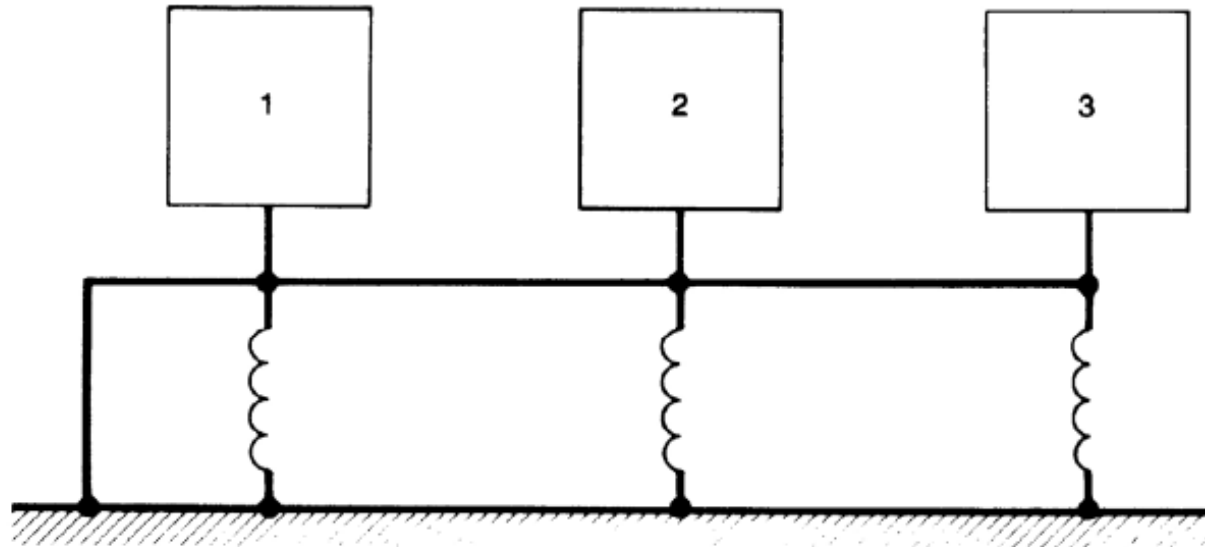


**Figure 3-10.** *A hybrid ground connection that acts as a multipoint ground at low frequencies and a single-point ground at high frequencies.*

Fig. 3.10: Multi point grounding at lower frequencies and one point grounding at higher frequencies. Used, say, when a low frequency coupling to the security ground for the mains is needed for each module at the same time as we want a single point grounding at the higher frequencies.

## 3.3 EQUIPMENT GROUNDING

# Example 1:

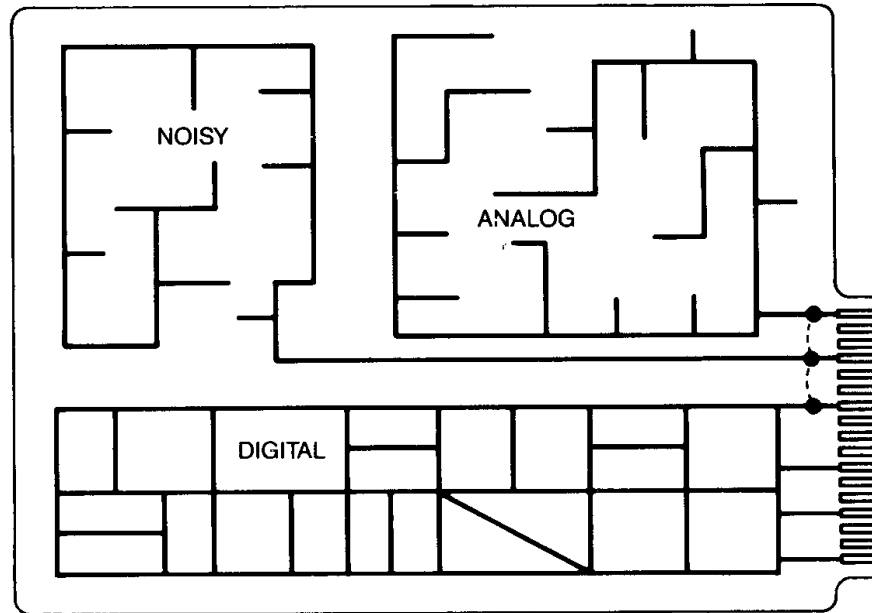

**Figure 3-11.** A printed wiring board with three separate ground systems, one for the digital logic, one for the low-level analog circuits, and one for the “noisy” circuits.


Here we have separated routing to avoid common impedance. Multi point grounding for the digital part, one point serially for the “noisy” part and one point parallel for the “analogue” part.

The chosen layout is a compromise between

- Design for low noise requiring more space and
- Design accepting more noise and requiring less space.

An example of a common grounding strategy is one line for each of three classes:

- Noise sensitive modules
- Noise generating modules
- Cabinet, chassis

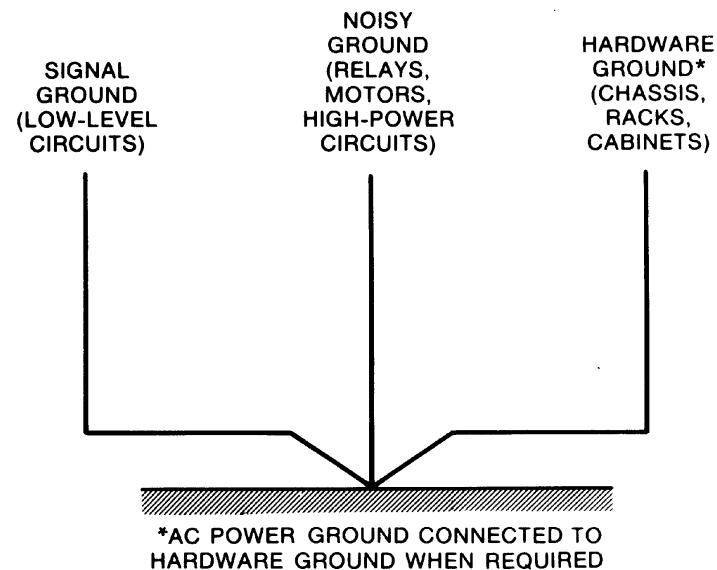

**Figure 3-12.** *These three classes of grounding connections should be kept separate to avoid noise coupling.*

## Example 2:

The common connection point for the ground lines should be as close as possible to the power supply.


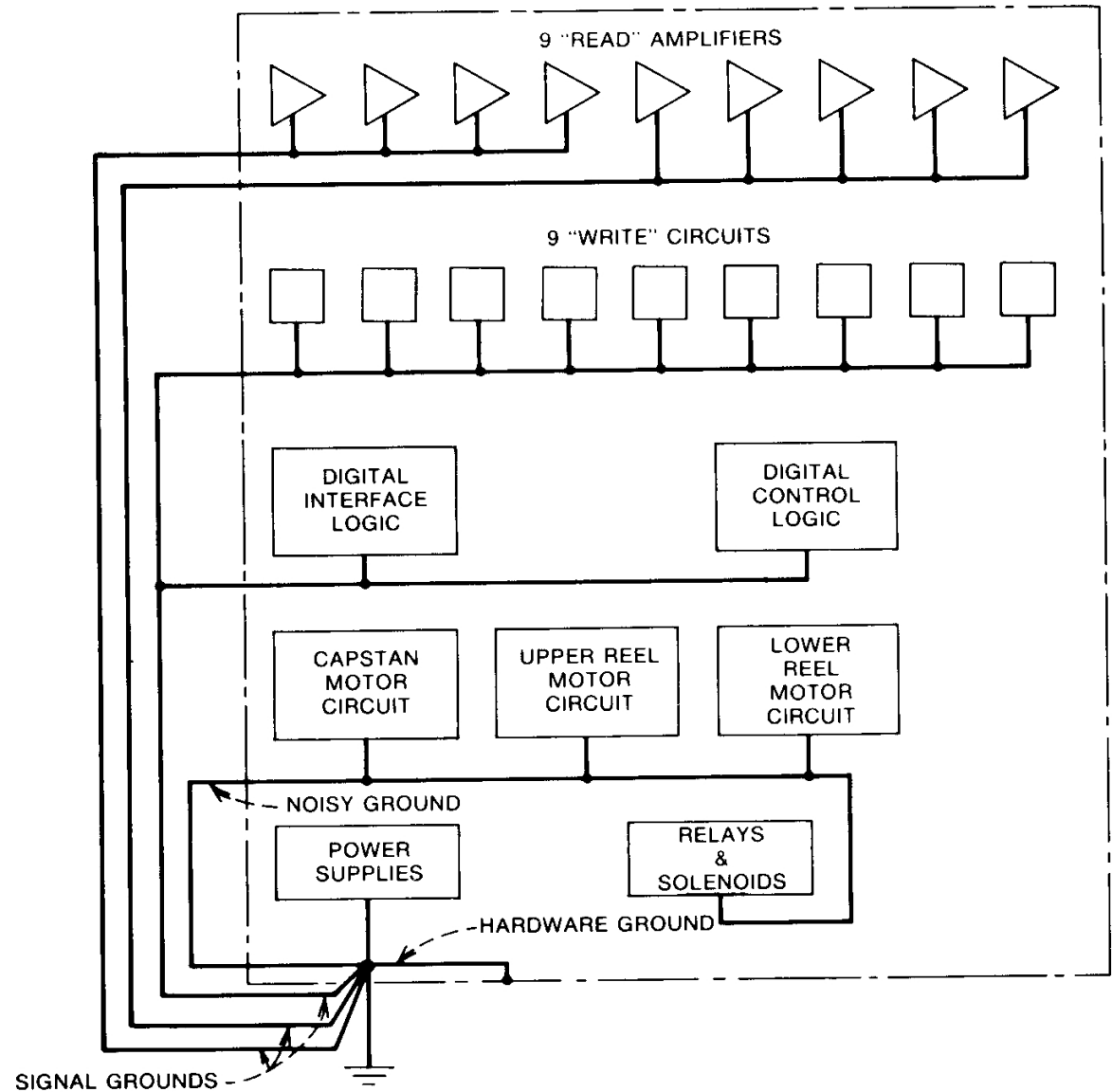


Figure 3-13. Typical grounding system for nine-track digital tape recorder.

# Example 3

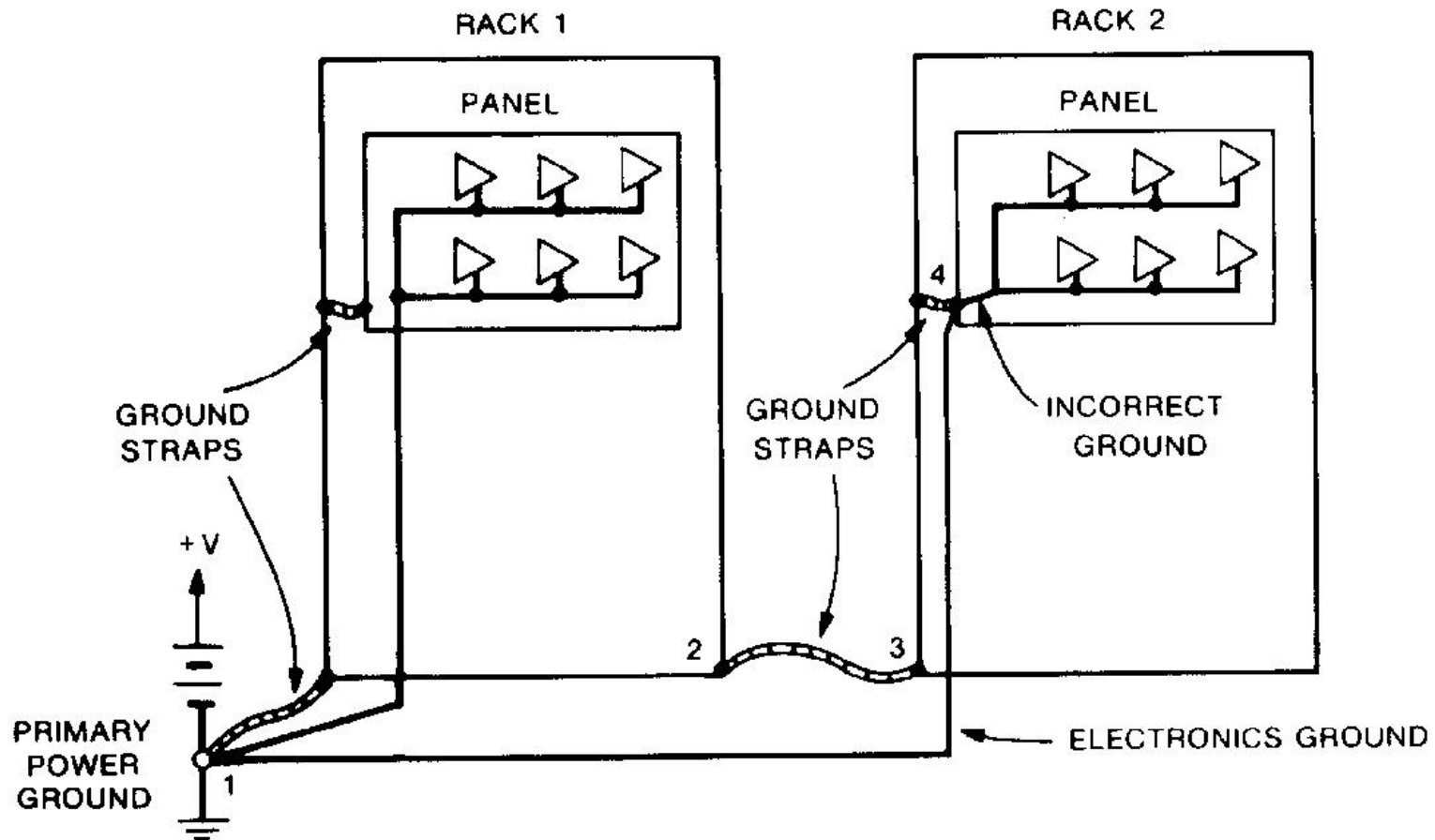

**Figure 3-14.** *Electronic circuits mounted in equipment racks should have separate ground connections. Rack 1 shows correct grounding; rack 2 shows incorrect grounding.*

# One contra two points grounding of a sensor- amplifier system.

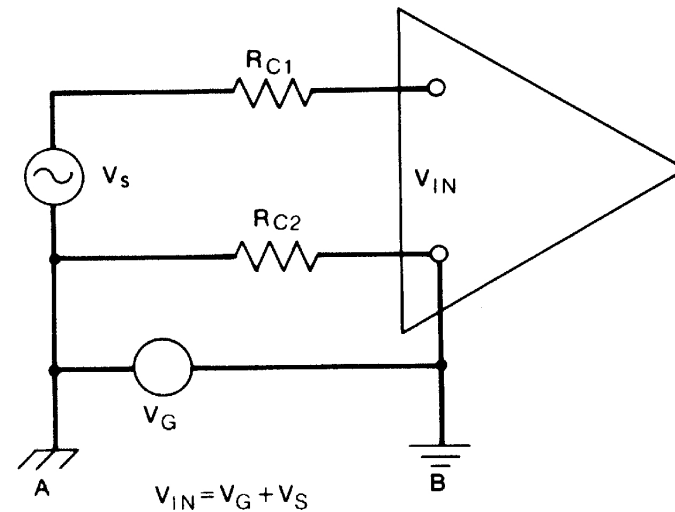


Figure 3-15. Noise voltage  $V_G$  will couple into the amplifier if the circuit is grounded at more than one point.

$V_s$  is the wanted source signal.

$V_G$  is the unwanted voltage difference between the two ground points. A and B is both ground points that is connected together and that ideally should have the same potential. However for different possible reasons there is a minor difference in potential between these two ground points. This is illustrated by using different ground symbols for the two points.



# Alternative 1: Two ground connections

When

$$R_{C2} \ll R_S + R_{C1} + R_L$$

we have that

$$V_N = \left[ \frac{R_L}{R_L + R_{C1} + R_S} \right] \left[ \frac{R_{C2}}{R_{C2} + R_G} \right] V_G$$

**Example:**

$$V_G = 10A \cdot 0.01\Omega = 100mV$$


$V_G$  may be due to magnetic coupling or due to passing currents running in ground.

$$R_S = 500\Omega,$$

$$R_{C1} = R_{C2} = 1\Omega,$$

$$R_L = 10k\Omega,$$

$$\Rightarrow V_N = 95mV.$$

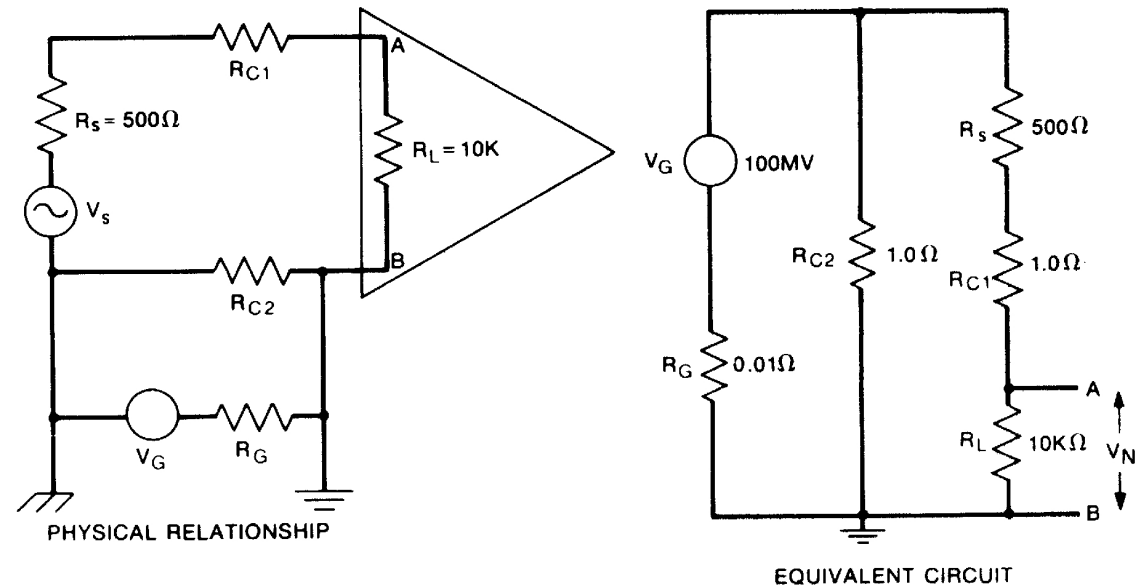

**Figure 3-16.** With two ground connections, much of the ground-potential difference appears across the load as noise.

# Alternative 2: One ground connection

Signal source is not grounded (almost):  $Z_{SG}$  is a parasitic large impedance.

When


$$R_{C2} \ll R_S + R_{C1} + R_L$$

and

$$Z_{SG} \gg R_{C2} + R_G$$

we have that

$$V_N = \left[ \frac{R_L}{R_L + R_{C1} + R_S} \right] \left[ \frac{R_{C2}}{Z_{SG}} \right] V_G$$

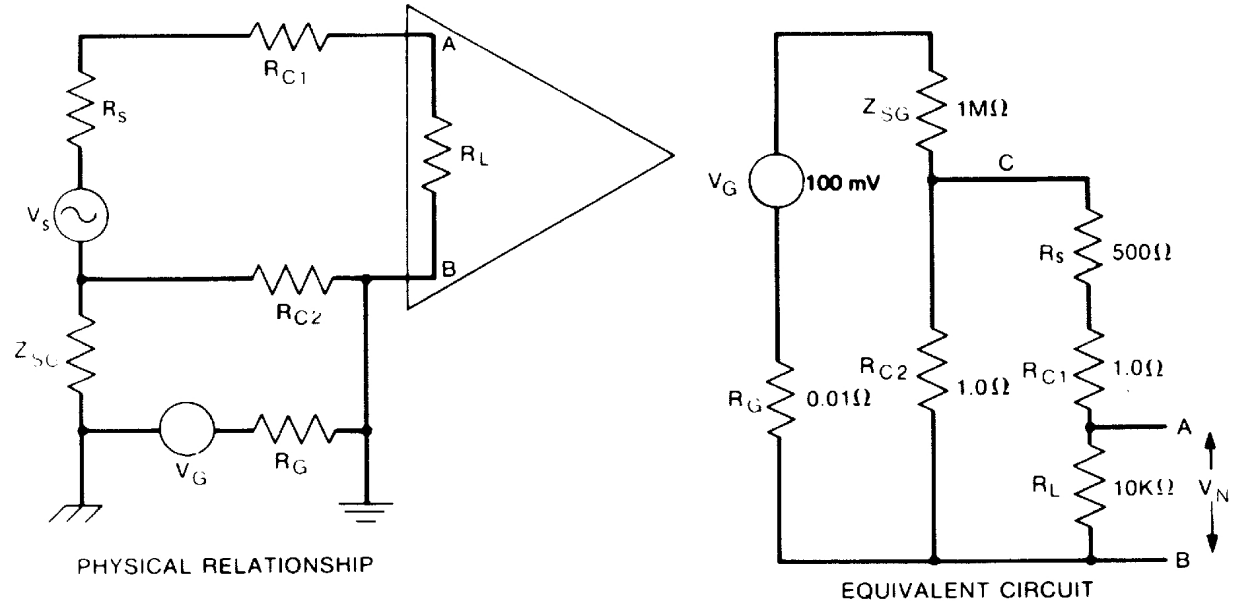

**Figure 3-17.** A large impedance between the source and ground keeps most of the ground-potential difference away from the load and reduces noise.

**Example:**

Same values as in the previous example plus:

$$Z_{SG} = 1 \text{ M}\Omega$$

$$\Rightarrow V_N = 0.095 \mu\text{V}$$

# Shielded, packaged amplifiers

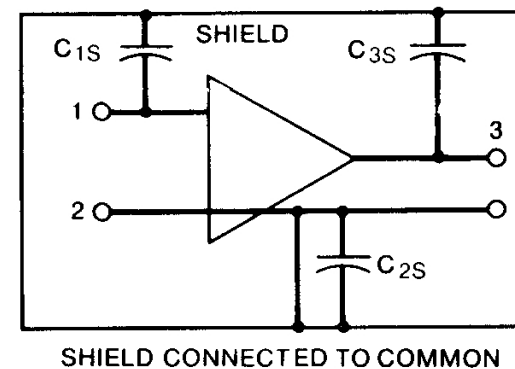
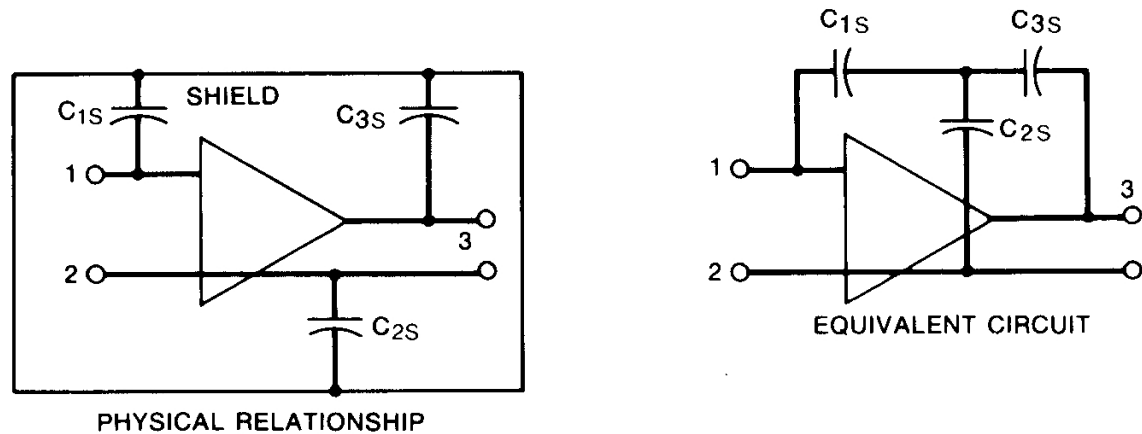


Figure 3-18. Amplifier shield should be connected to the amplifier common.

If the package house is not properly grounded it may be a part of a unwanted feedback and result in instability. Proper grounding is illustrated at the bottom figure. Here the package house is coupled to the common input/output reference ground.

# How to ground the shield?

**Case 1: When only the AMP is grounded.**

A: Shield noise will return through one of the signal wires. This is the worst case.

Prioritised order:  
C, D, B, and A.

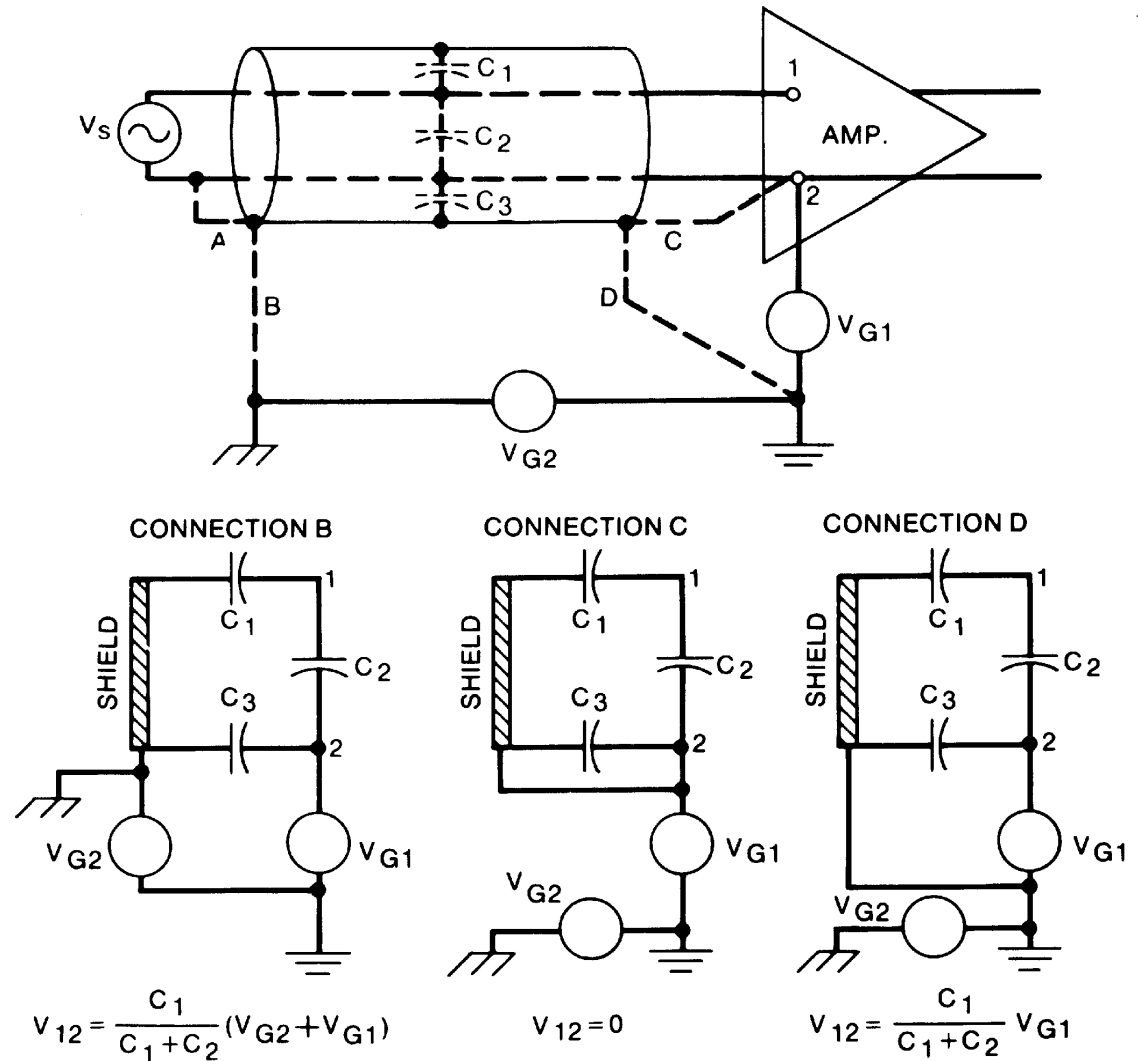



Figure 3-19. When amplifier is grounded, the best shield connection is C, with shield connected to amplifier common.

# How to ground the shield?

**Case 2: When only the signal source is grounded.**


C: Shield noise will return through one of the signal wires. This is the worst case in this setup.

Prioritised order: A, B, D and C.

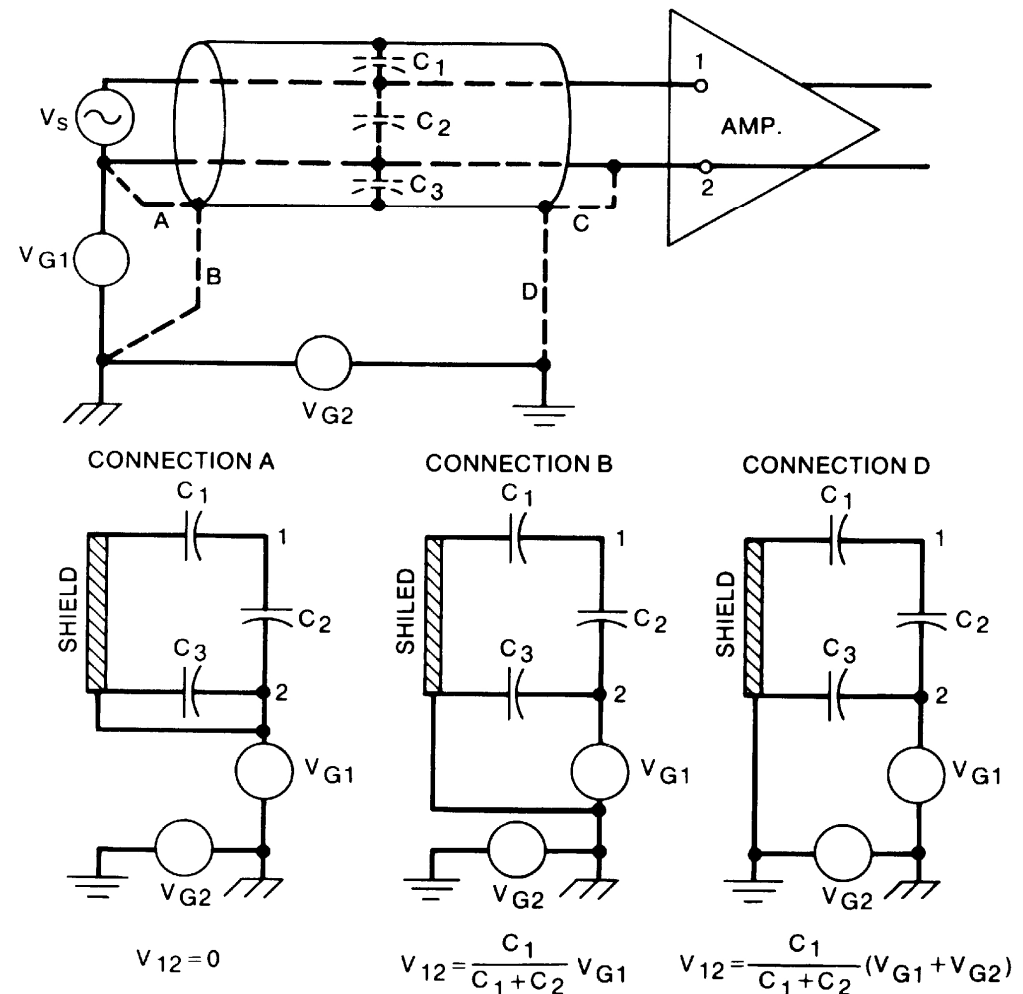

**Figure 3-20.** When source is grounded, the best shield connection is A, with shield connected to the source common. The configuration can also be used with a differential amplifier.

## 3.4 GROUND LOOPS

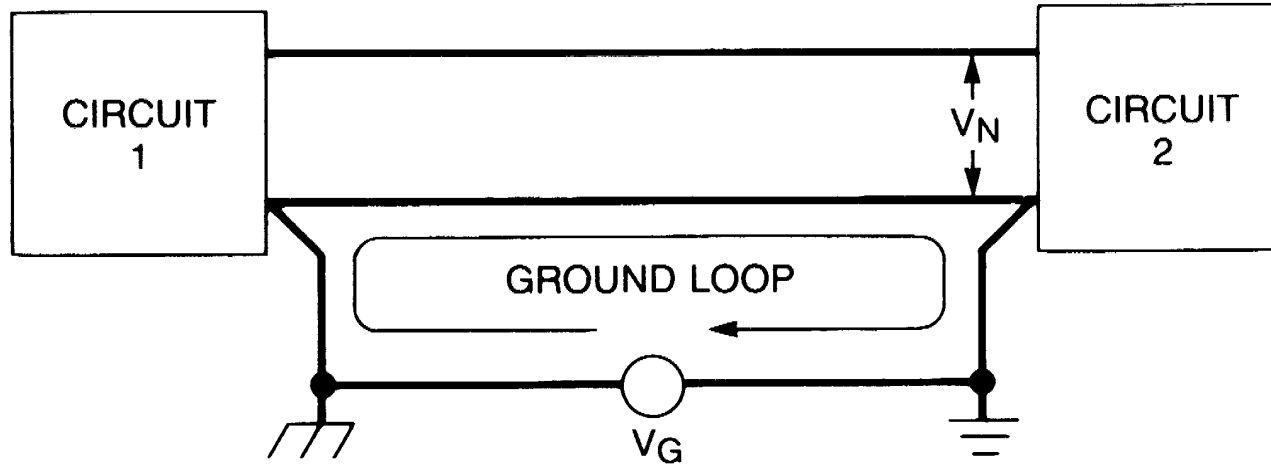

**Figure 3-22.** *A ground loop between two circuits.*

By “ground loop” we mean a closed loop where the potential ideally should have been at ground all over the loop. However there may be running a current in this loop influencing significantly on the electronic circuitry. There are two main causes for currents in ground loops: The current may be due to magnetic fields or due to large passing currents in part of the ground loop, say in a ground plan.


## Countermeasures depending on cause:

1. Reduce the size of the loop (if magnetic cause)
2. Route the current in a different direction (if passing current).

## Cause independent countermeasures:

1. Change the system to only one ground connection.
2. "Split" the loop electronically
  - a) transformer
  - b) common mode choke
  - c) optical coupler
  - d) balanced circuit
  - e) frequency selective grounding (hybrid ground).

## a) Transformer

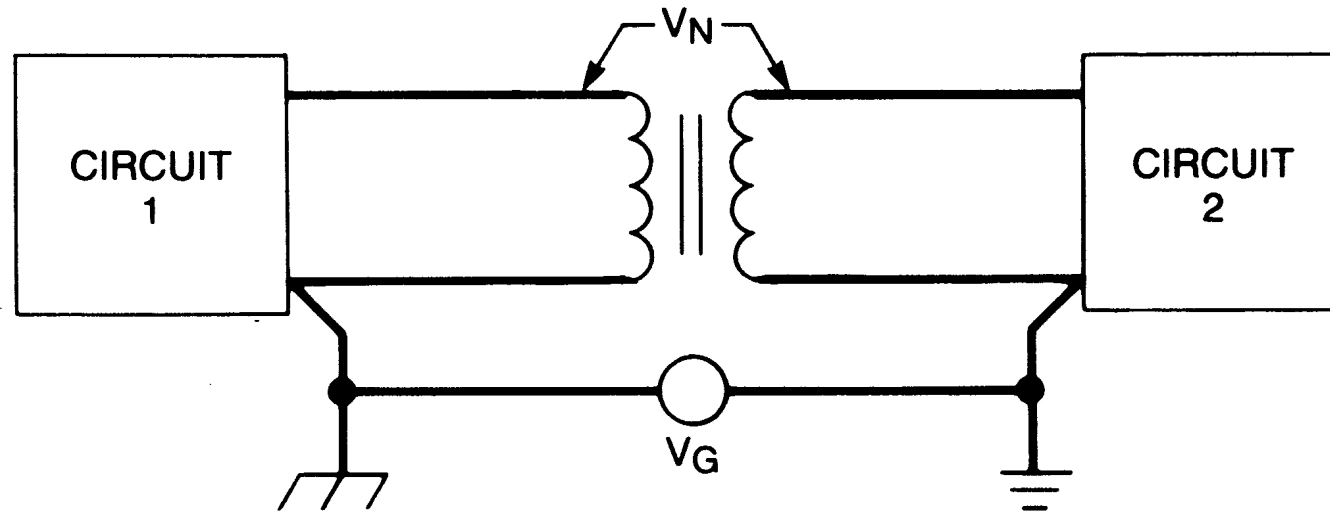


**Figure 3-23.** *A ground loop between two circuits can be broken by inserting a transformer.*

The noise is over the trafo and will not influence on the differential voltage. Capacitive coupling may give some noise infection. This coupling may be reduced by shielding the trafo.




## b) Common mode choke

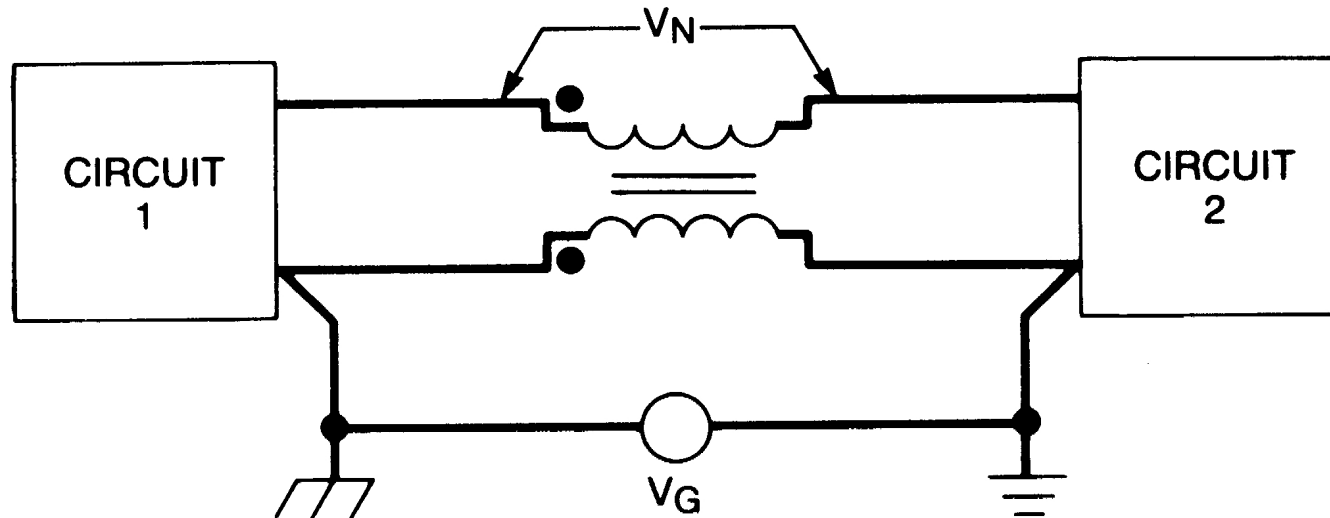

**Figure 3-24.** A ground loop between two circuits can be broken by inserting a common-mode choke.

(To be discussed in detail a little later.)


## c) Optical coupler

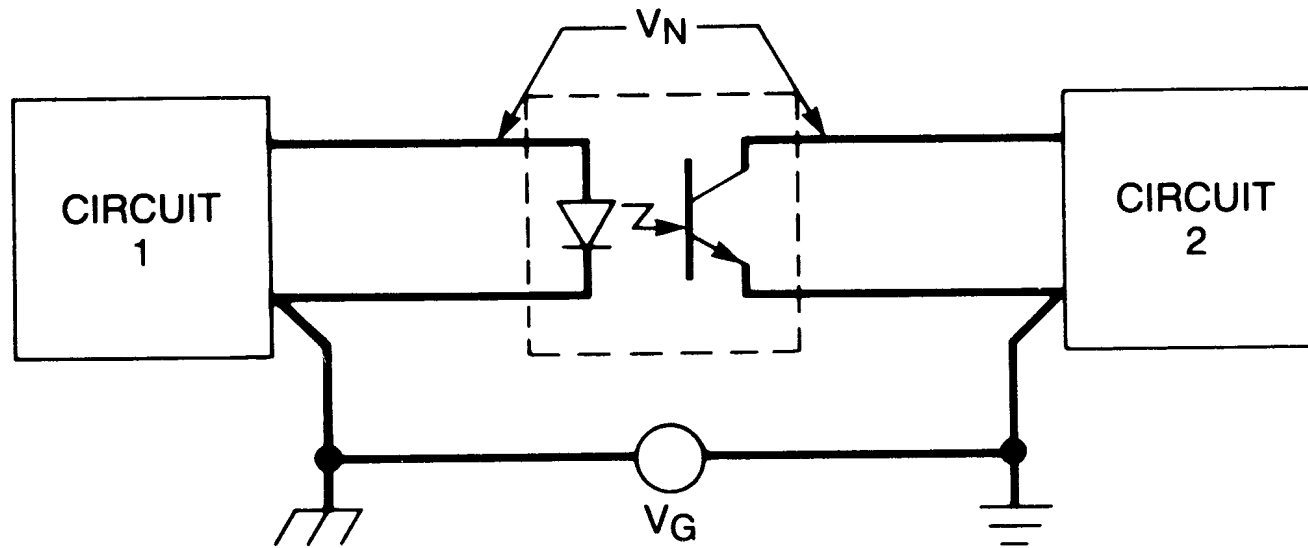

**Figure 3-25.** *An optical coupler can be used to break the ground loop between two circuits.*

An attractive alternative when the ground voltage difference is very large. It is better suited for digital circuitry than analogue circuitry due to bad linearity.

## d) Balanced circuit

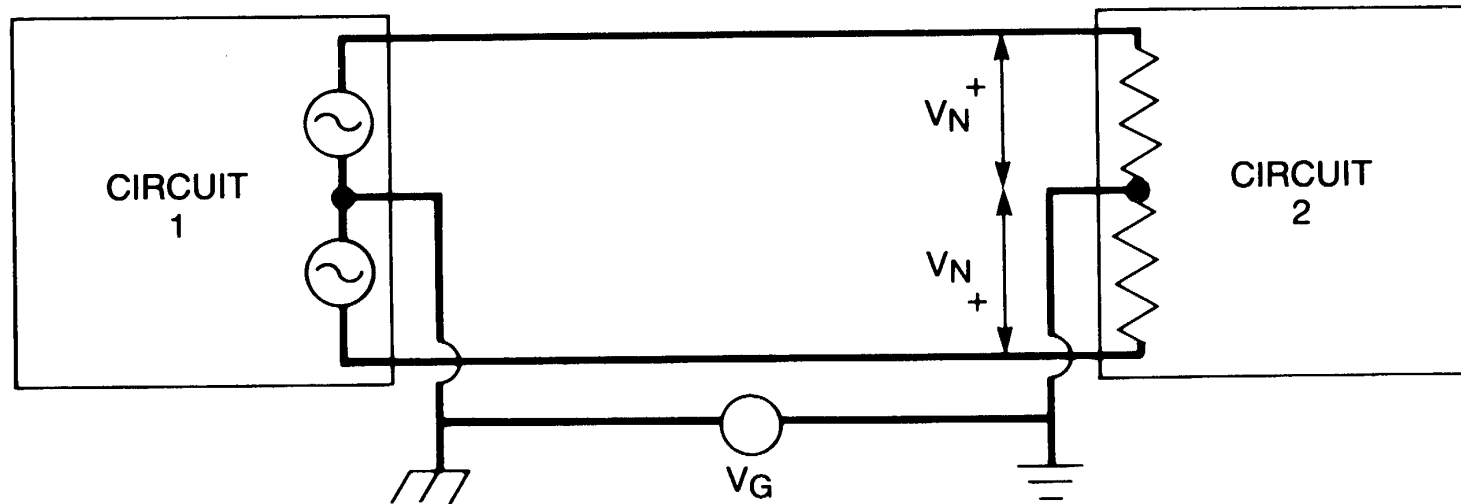

**Figure 3-26.** *A balanced circuit can be used to cancel out the effect of a ground loop between two circuits.*

If the ground current is equally divided into the two differential lines, the noise will be eliminated in the receiver. Hence the efficiency will depend on how well symmetry we manage to achieve.

## 3.5 LOW-FRQUENCY ANALYSIS OF COMMON-MODE CHOKE

Other names used:  
longitudinal choke,  
neutralizing transformer,  
balun.

**Signal current:** Current in  
opposite directions in the  
differential pair. Low  
impedance.

**Common mode current:**  
Current in the same direction  
in both differential conductors.  
High impedance.

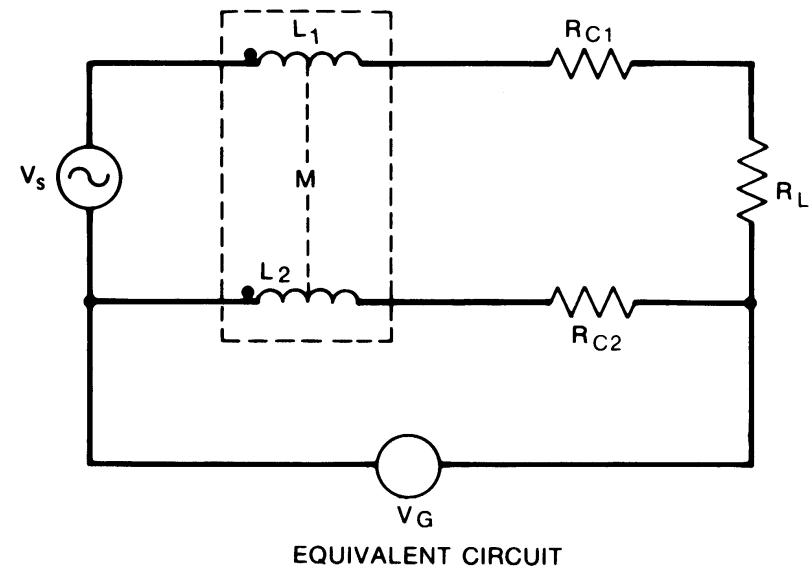
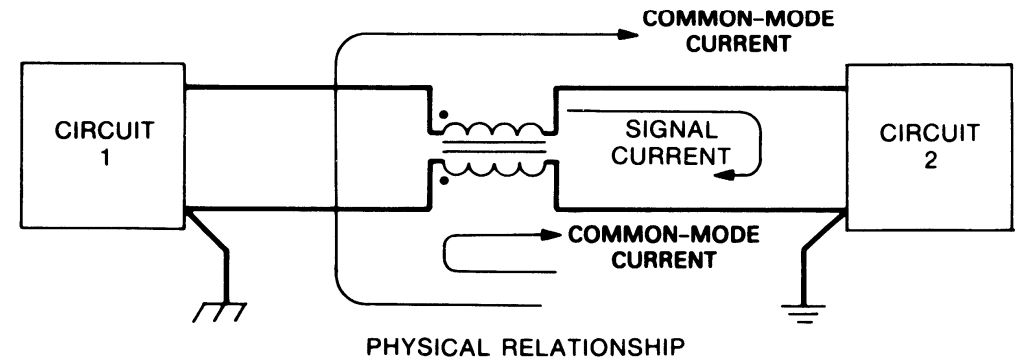


Figure 3-27. When dc or low-frequency continuity is required, a common-mode choke can be used to break a ground loop.

# Calculation of signal current

(Ref: similarities with previous equation (2-22))

When  $f$  is over  $R_{C2}/L_2$  most of the return current will pass through the other differential conductor (2). When  $f$  is over  $5R_{C2}/L_2$  we have that approximately all current passes through the other line and nothing through ground.

Now we can put up the following equation:

$$V_S = j\omega(L_1 + L_2)I_S - 2j\omega MI_S + (R_L + R_{C2})I_S$$

If the coils are approximately equal and are on the same kernel, we have that:  $L_1 = L_2 = M$

Then we have:  $I_S = \frac{V_S}{R_L + R_{C2}} \approx \frac{V_S}{R_L}$  given that  $R_L \gg R_{C2}$

*NB! Without choke we get the same expression.*

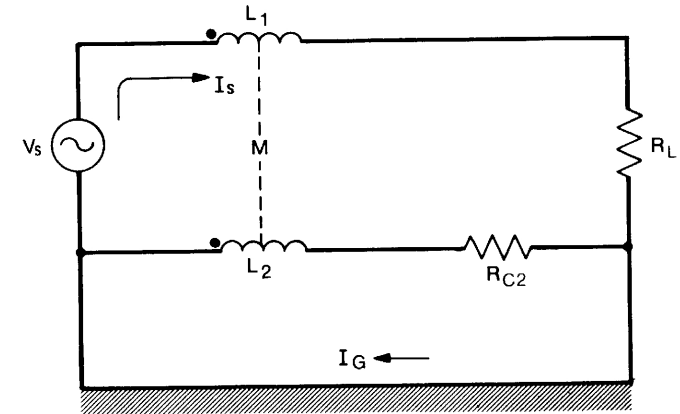


Figure 3-28. Equivalent circuit for Fig. 3-27 for analysis of response to signal voltage  $V_s$ .

I.e. the choke does not have any influence on the signal current when the frequency is over  $5R_{C2}/L_2$ . Hence we will try to choose  $R_{C2}$  and  $L_2$  so that the corner frequency becomes lower than the lowest possible signal frequency.

# Estimates of common noise current

The voltage in the outer loop is:  
 $V_G = j\omega L_1 I_1 + j\omega M I_2 + I_1 R_L$   
 while the voltage in the inner loop is:

$$V_G = j\omega L_2 I_2 + j\omega M I_1 + R_{C2} I_2$$

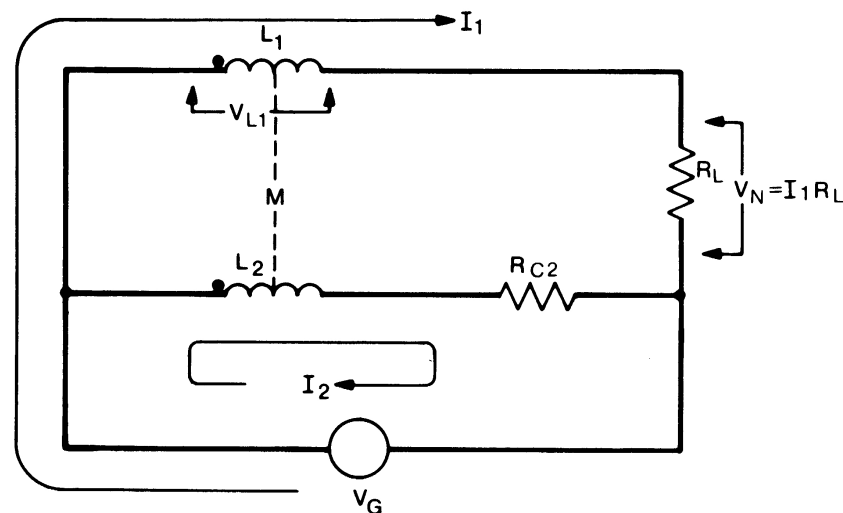


Figure 3-29. Equivalent circuit for Fig. 3-27 for analysis of response to common-mode voltage  $V_G$ .

We find  $I_2$  from the last expression:

$$I_2 = \frac{V_G - j\omega M I_1}{j\omega L_2 + R_{C2}}$$

We still assume  $L_1 = L_2 = M$  and include the last expression in the expression for the outer loop and achieve:

$$I_1 = \frac{V_G R_{C2}}{j\omega L (R_{C2} + R_L) + R_{C2} R_L}$$

$$I_1 = \frac{V_G R_{C2}}{j\omega L(R_{C2} + R_L) + R_{C2}R_L}$$

The noise voltage  $V_N$  is equal to  $I_1 R_L$ . Since  $R_{C2}$  typically is much less than  $R_L$  we may remove the first term in the parenthesis and ends up with:

$$V_N = \frac{V_G R_{C2} / L}{j\omega + R_{C2} / L}$$

To minimize the part of the noise voltage that reaches the "receiver",  $R_{C2}$  should be as small as possible and the choke inductance should be so that  $L \gg \frac{R_{C2}}{\omega}$  where  $\omega$  is the frequency of the noise.


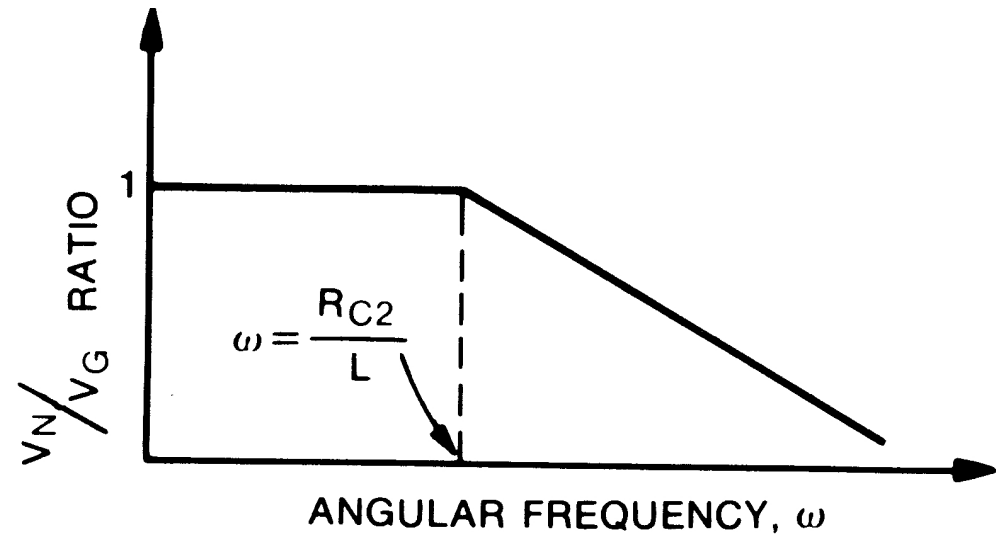


Figure 3-30. Noise voltage may be significant if  $R_{C2}$  is large.

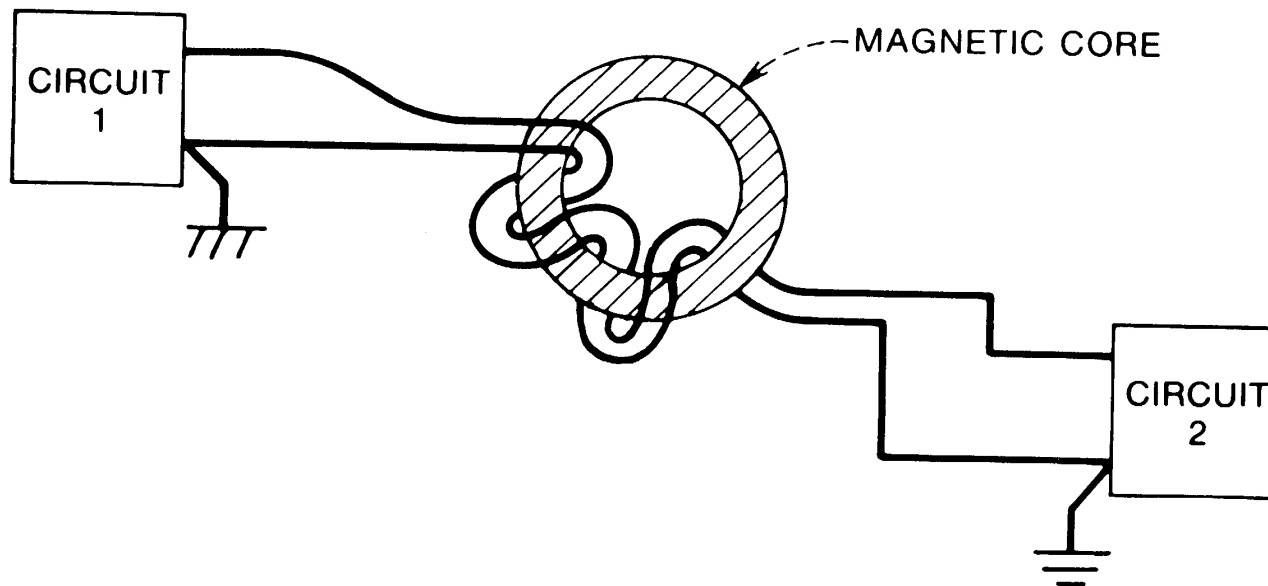

The figure below shows an example of how this can be done.



**Figure 3-31.** *An easy way to place a common-mode choke in the circuit is to wind both conductors around a toroidal magnetic core. A coaxial cable may also be used in place of the conductors shown.*

# Differential amplifiers

- Differential amplifiers (top figure) have less sensitivity to common mode noise. It is also possible to achieve this with a single sided amplifier if connected as shown in the bottom figure.
- Both the real differential and the one based on the single sided amplifier can be represented by the same equivalent schematic and the same equation.

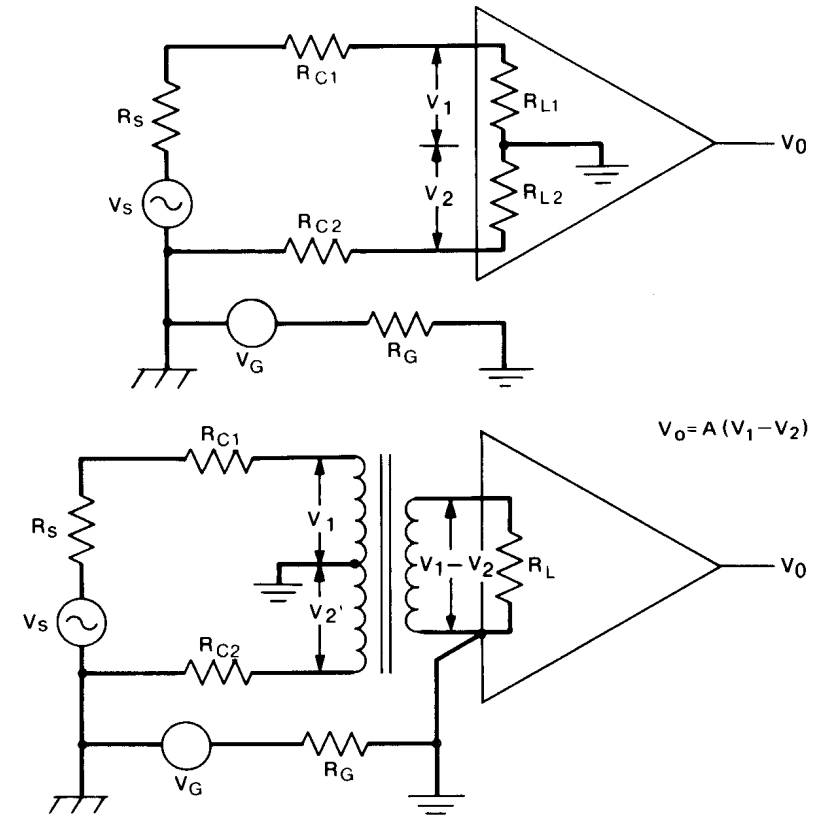


Figure 3-35. A differential amplifier—or a single-ended amplifier with transformer—can be used to reduce the effects of a common-mode noise voltage.

If we assume that  $R_{L2}$  is much larger than  $R_G$  we can simplify to the following equation:

$$V_N = V_1 - V_2 = \left( \frac{R_{L1}}{R_{L1} + R_{C1} + R_S} - \frac{R_{L2}}{R_{L2} + R_{C2}} \right) V_G$$

**Example:**

$$V_G = 100\text{mV}$$

$$R_G = 0.01\Omega$$

$$R_S = 500\Omega$$

$$R_{C1} = R_{C2} = 1\Omega$$

$$\text{If } R_{L1} = R_{L2} = 10\text{k}\Omega \text{ then } V_N = 4.6\text{mV}$$

$$\text{If } R_{L1} = R_{L2} = 100\text{k}\Omega \text{ then } V_N = 0.5\text{mV}$$

Larger  $R_L$  and/or smaller  $R_S$  is attractive

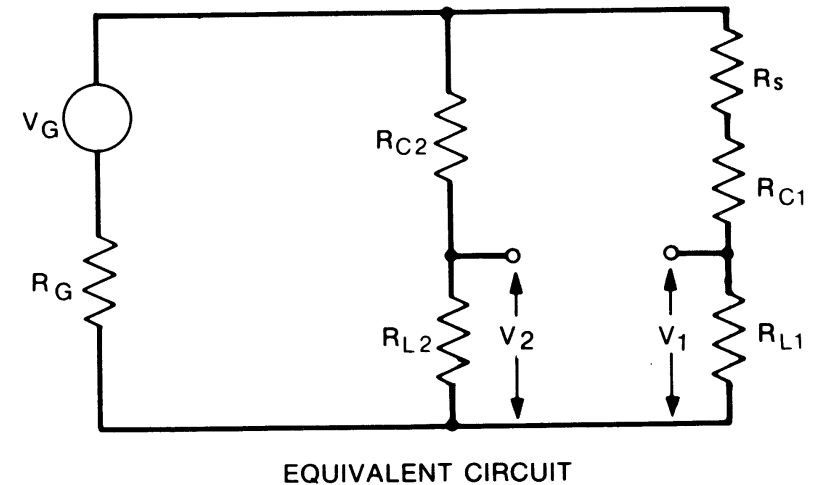


Figure 3-36. Equivalent circuit for analysis of differential-amplifier circuit.

It is possible to increase the input impedance for the common mode signal without increasing the impedance experienced by the differential signal. This can be achieved by inserting a resistance  $R$  as drawn in the figure.

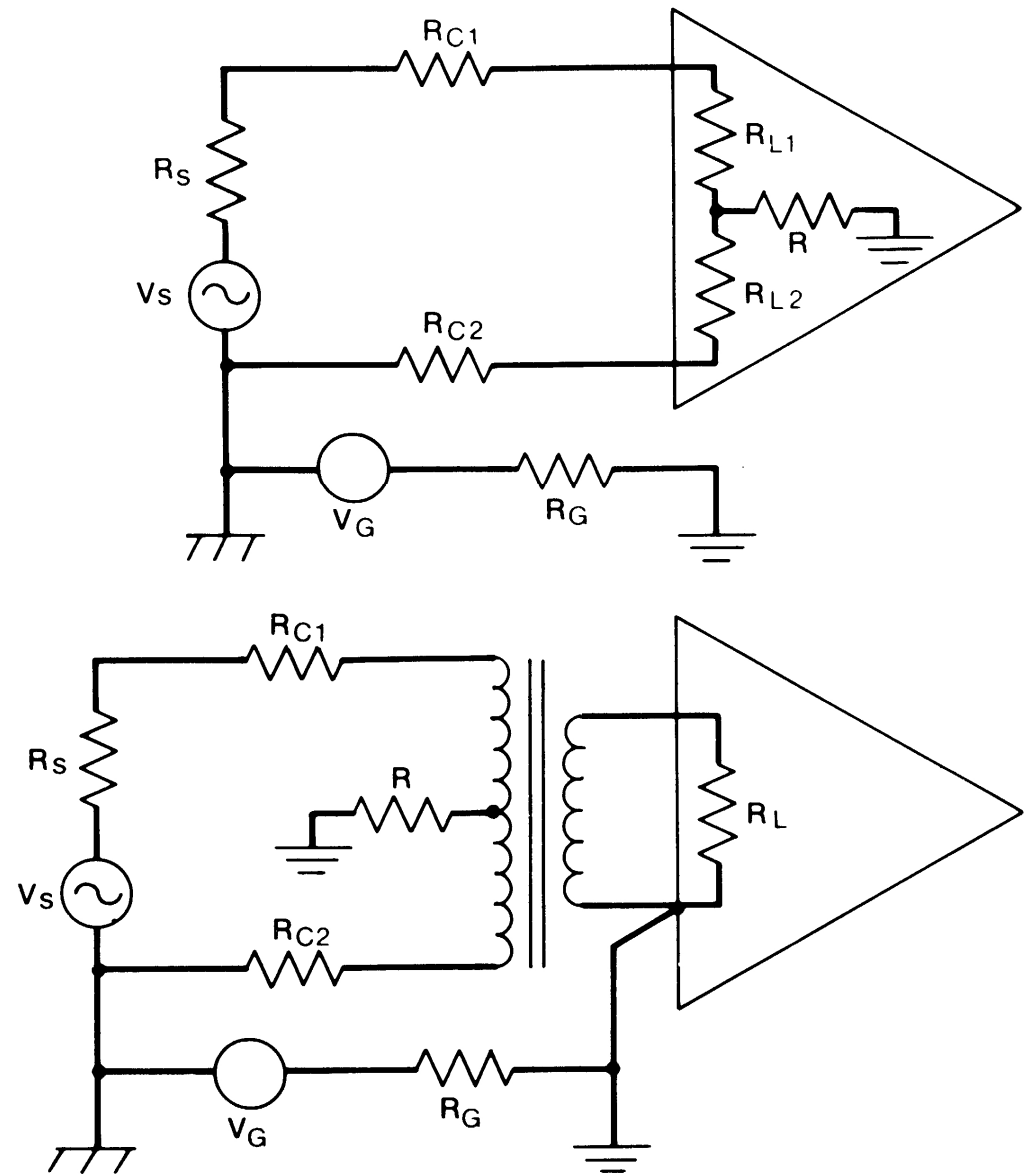


Figure 3-37. Insertion of resistance  $R$  into ground lead decreases the noise voltage.

# Guard shields

In general we have that  $(R_S + R_1 + X_{C_{1G}}) \ll (R_2 + X_{C_{2G}})$ . The difference in the ground potential  $V_G$  will result in two different currents through the differential pair and thus two different voltage drops over  $X_{C_{1G}}$  and  $X_{C_{2G}}$  even though  $X_{C_{1G}}$  and  $X_{C_{2G}}$  are equal.


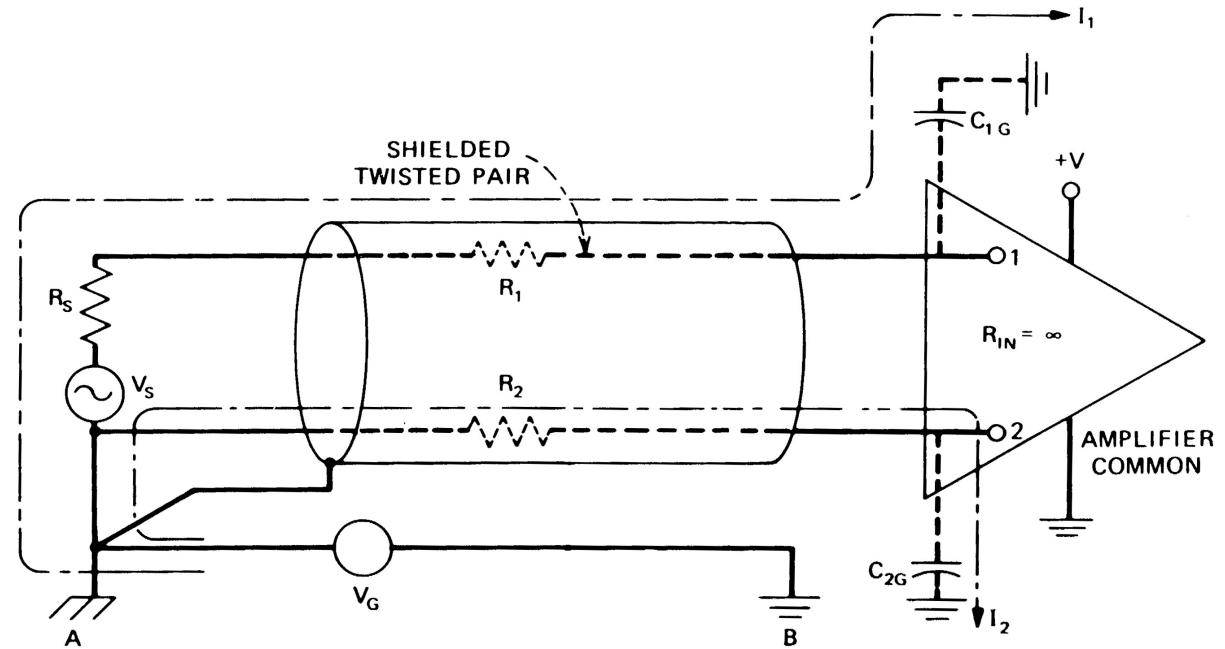


Figure 3-39. Amplifier and a grounded source are connected by a shielded twisted pair.

To make the currents equal  $(R_S + R_1 + X_{C_{1G}})$  has to be equal to  $(R_2 + X_{C_{2G}})$  at the same time as  $X_{C_{1G}} = X_{C_{2G}}$ .

$$V_{in}(x) = \frac{Z_{in}(x)}{Z_{in}(x) + Z_{rest}(x)} V_{common\_noise}$$

A much more realistic solution is to try to make the voltage drop over the differential wires equal to 0V. If so the voltage drop over the inputs become equal (i.e. 0Volt).

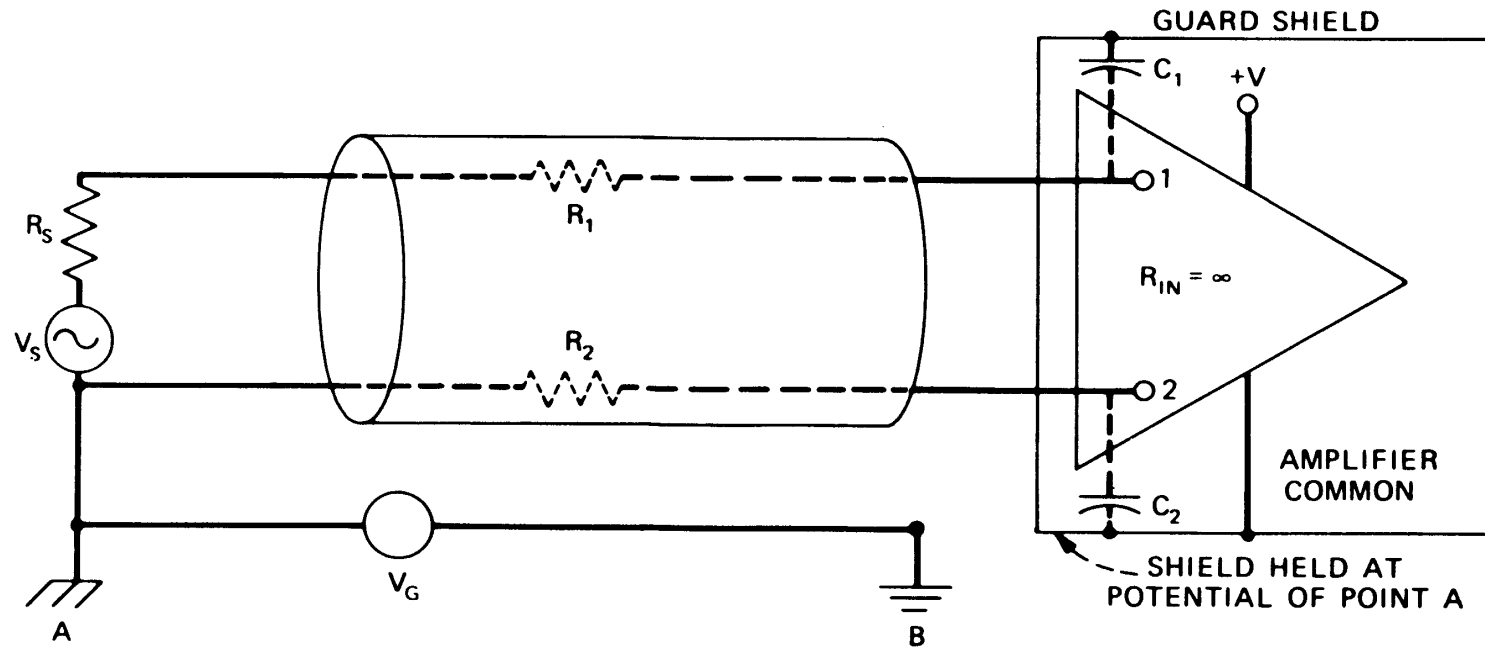

**Figure 3-40.** *Guard shield at potential of point A eliminates noise currents.*

In the solution drawn above we have a screen encapsulating the amplifier. The shield is connected so that it has the same ground potential as the source (point A). In this way the ground voltage drop will be zero from point A, through the differential wires and through the amplifier input towards the shield.

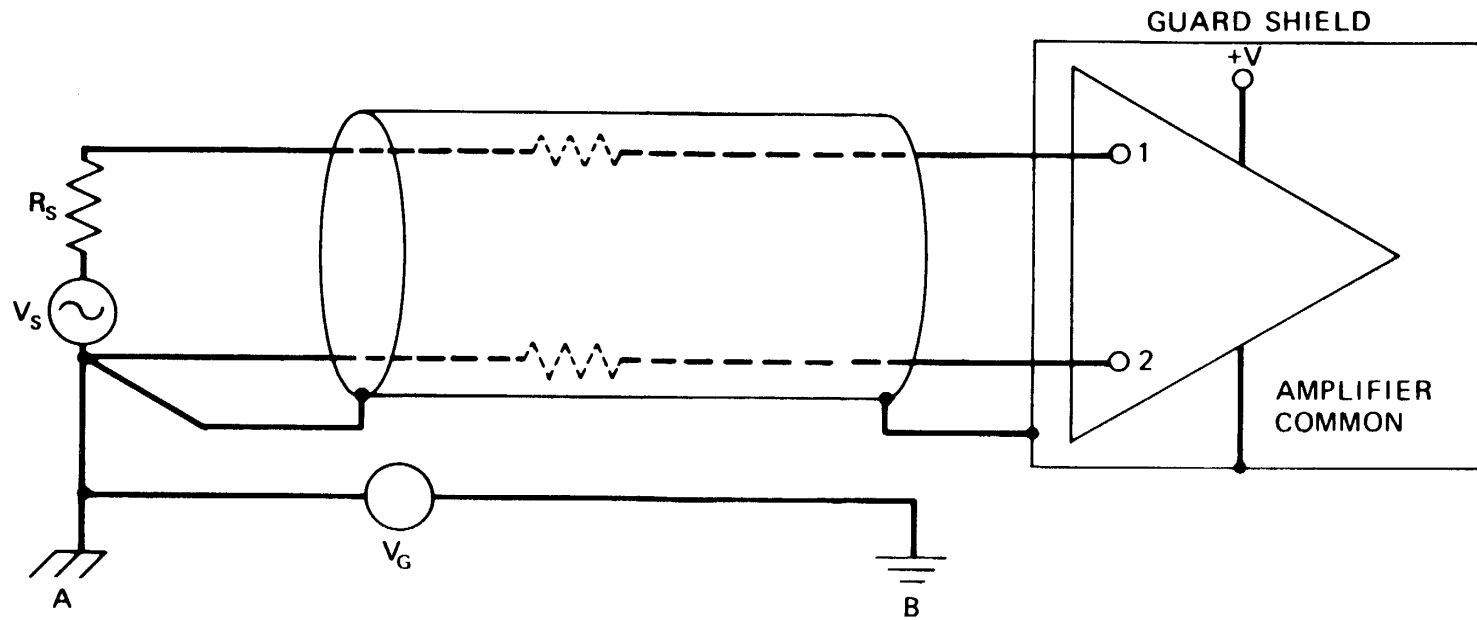


Figure 3-41. Guard shield is connected to point A through the cable shield.

The figure illustrates how the amplifier shield can be connected to point A via the cable shield.

The amplifier power source can not refer to point B. Possible power options are via cable from A, having an independent power source (for example a battery) or coupled via a galvanic element to the power source on the right side.

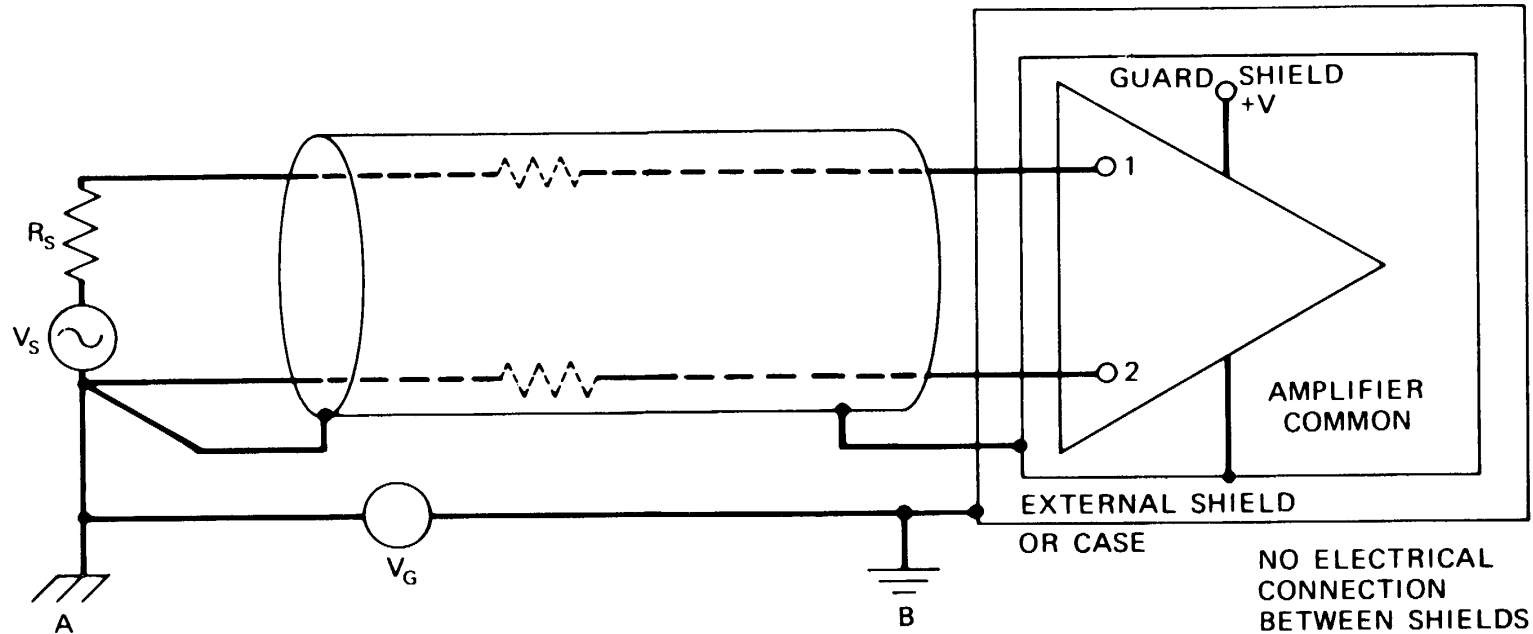


Figure 3-42. Practical circuit often has a second shield around the guard shield.

If it is likely/a possibility that the screen encapsulating the amplifier can pick up noise from the surroundings, a double shield may be a possibility. In this case the outer shield is grounded locally and it is also important that the impedance between the two shields are high enough compared with the other influencing impedances in the system.



## Example:

$V_G = 100\text{mV}$  at 60Hz,  $R_1 = R_2 = 0$ ,  $R_S = 2.6\text{k}\Omega$ ,

$C_{1G} = C_{2G} = 100\text{pF} \Rightarrow X_C = 26\text{M}\Omega$  at 60Hz

a) Without amplifier shield

$$V_N = \left( \frac{R_S + R_1}{R_S + R_1 + Z_{1G}} - \frac{R_2}{R_2 + Z_{2G}} \right) V_G$$

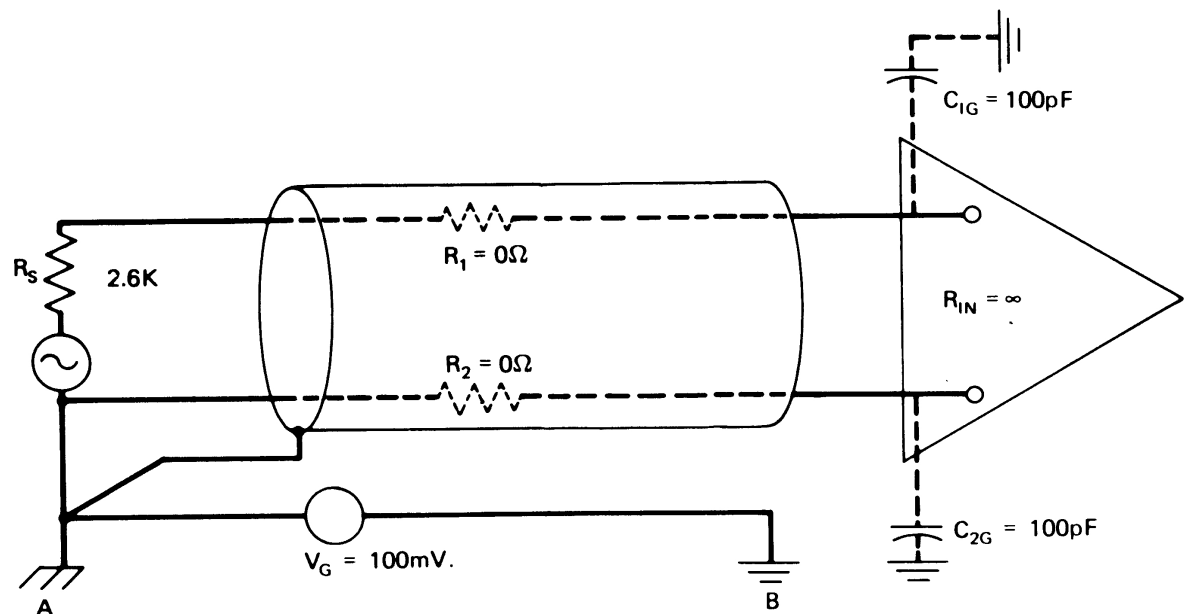


Figure 3-43. Numerical example to illustrate need for guard shield.

Given the values above we achieve:  $V_N = 10\mu\text{V}$

b) With amplifier shield:

Assume that the shield results in a change of  $C_{1G}$  and  $C_{2G}$  from 100pF to 2pF. We may use the same expression as above and now have:  $V_N=0.2\mu\text{V}$   
i.e. now an attenuation of -34 dB

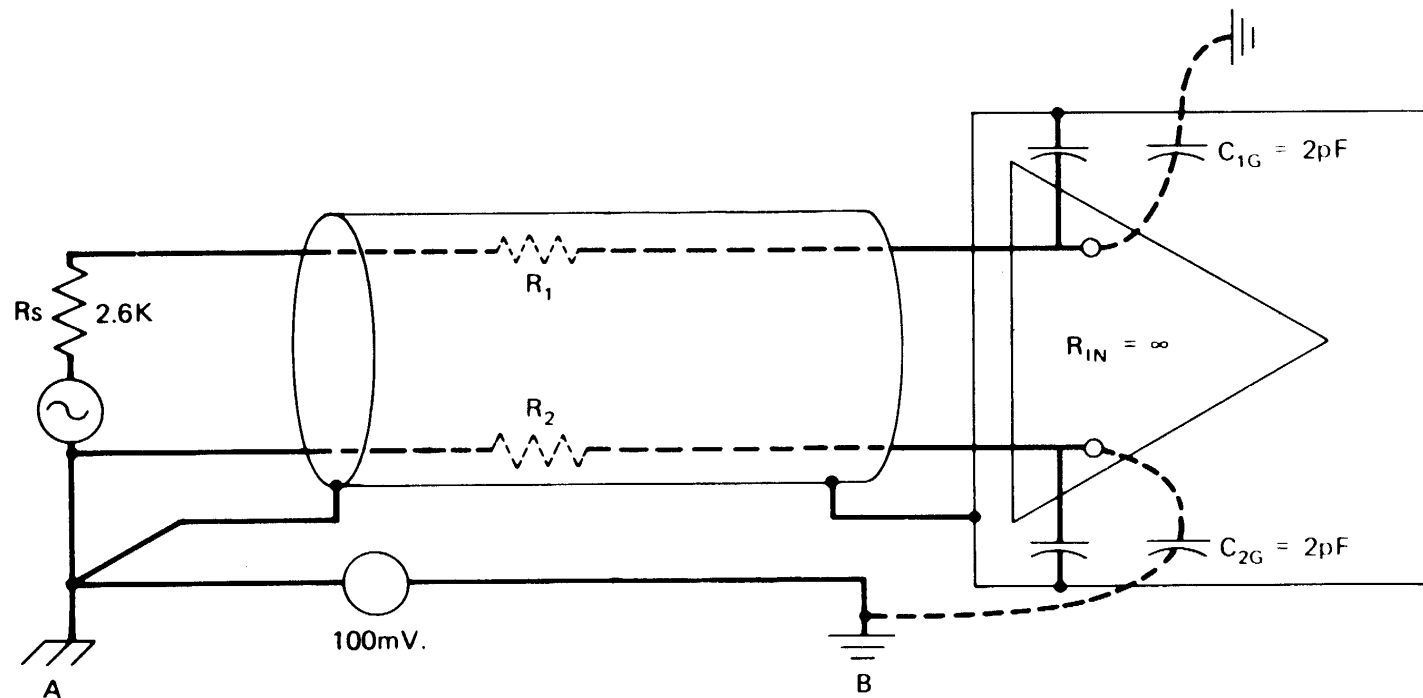


Figure 3-44. Guard shield reduces line capacitance to ground and therefore noise voltage.

# Measuring apparatus with "Guard". Discussion of alternative connections

How to  
connect  
"Guard"  
to  
achieve the  
best  
possible  
measuring  
results?



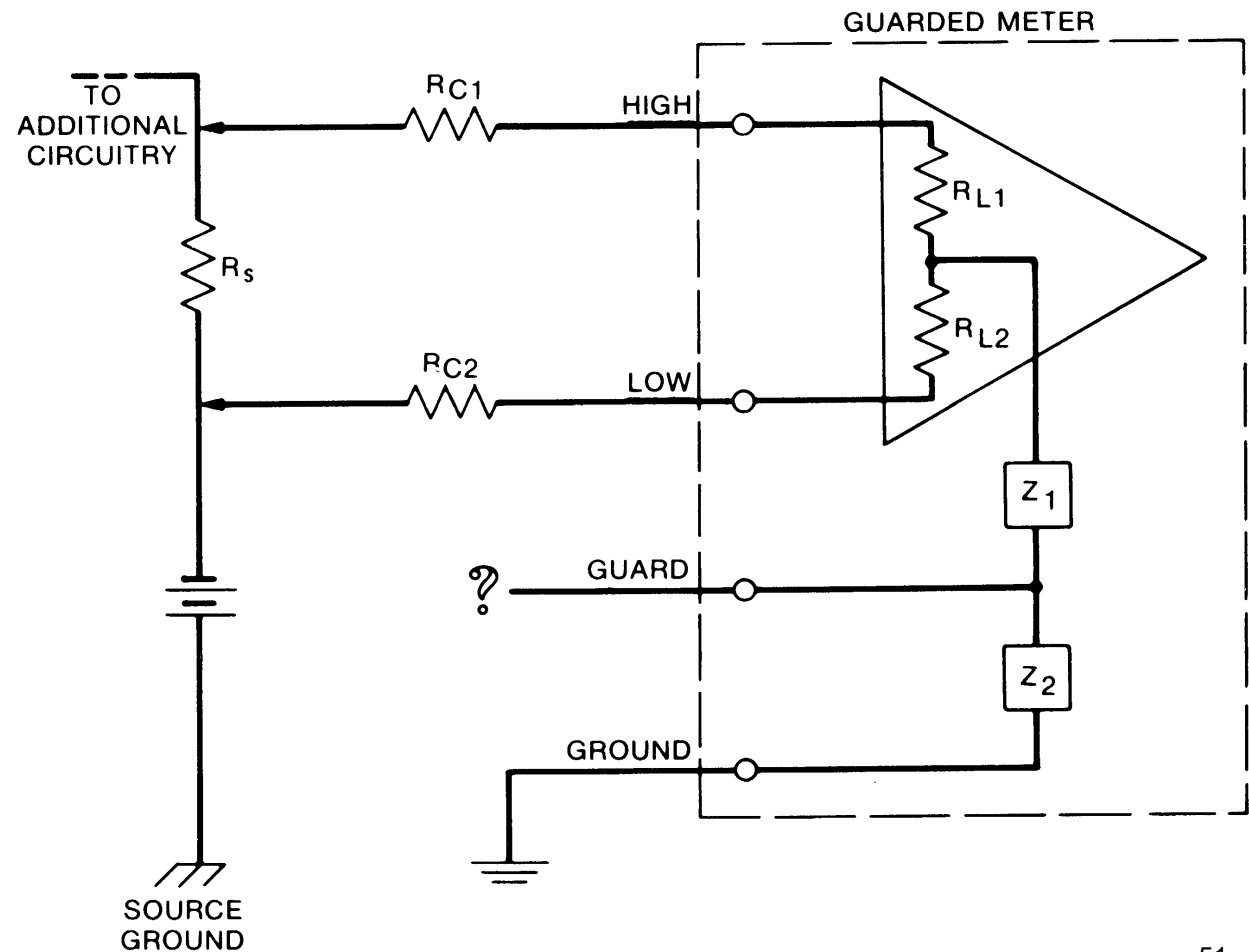



Figure 3-45. When a guarded meter is used, a common problem is where to connect the guard terminal.

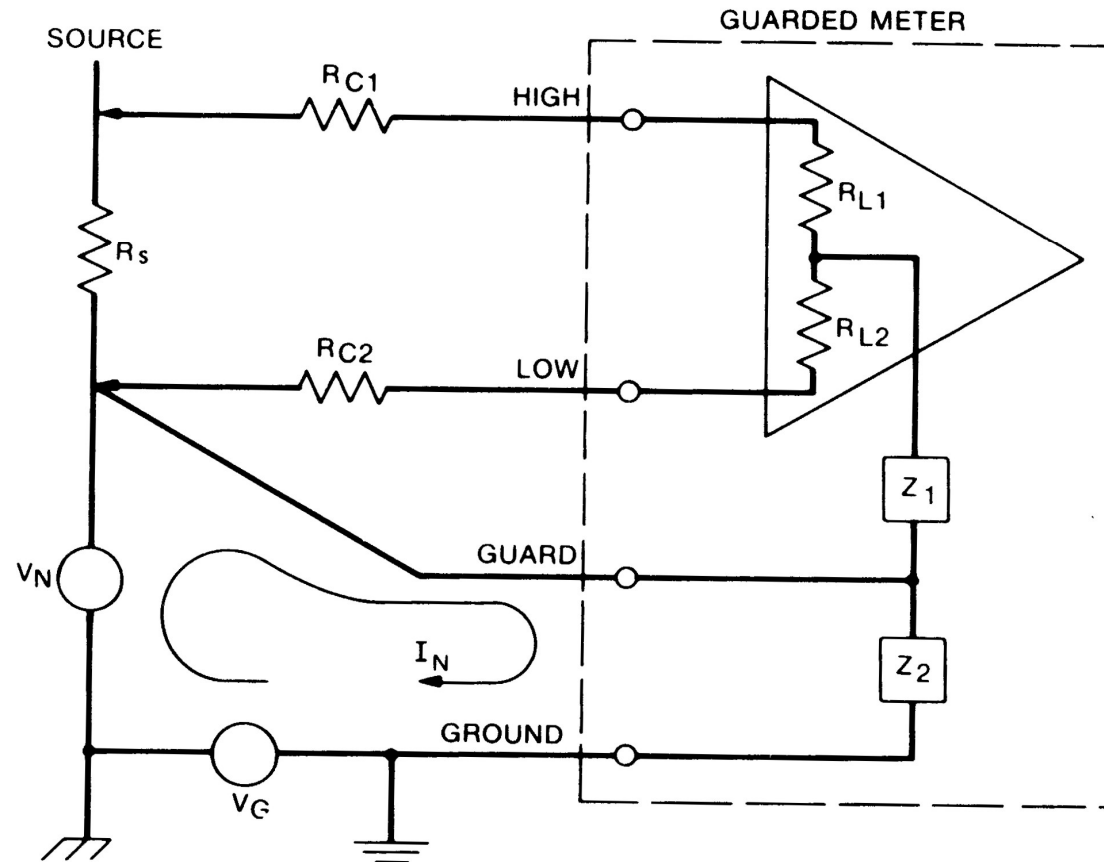


**Figure 3-46.** When measuring voltage across  $R_s$ , best connection for the guard is to the low-impedance side of  $R_s$ ; noise current does not affect amplifier.

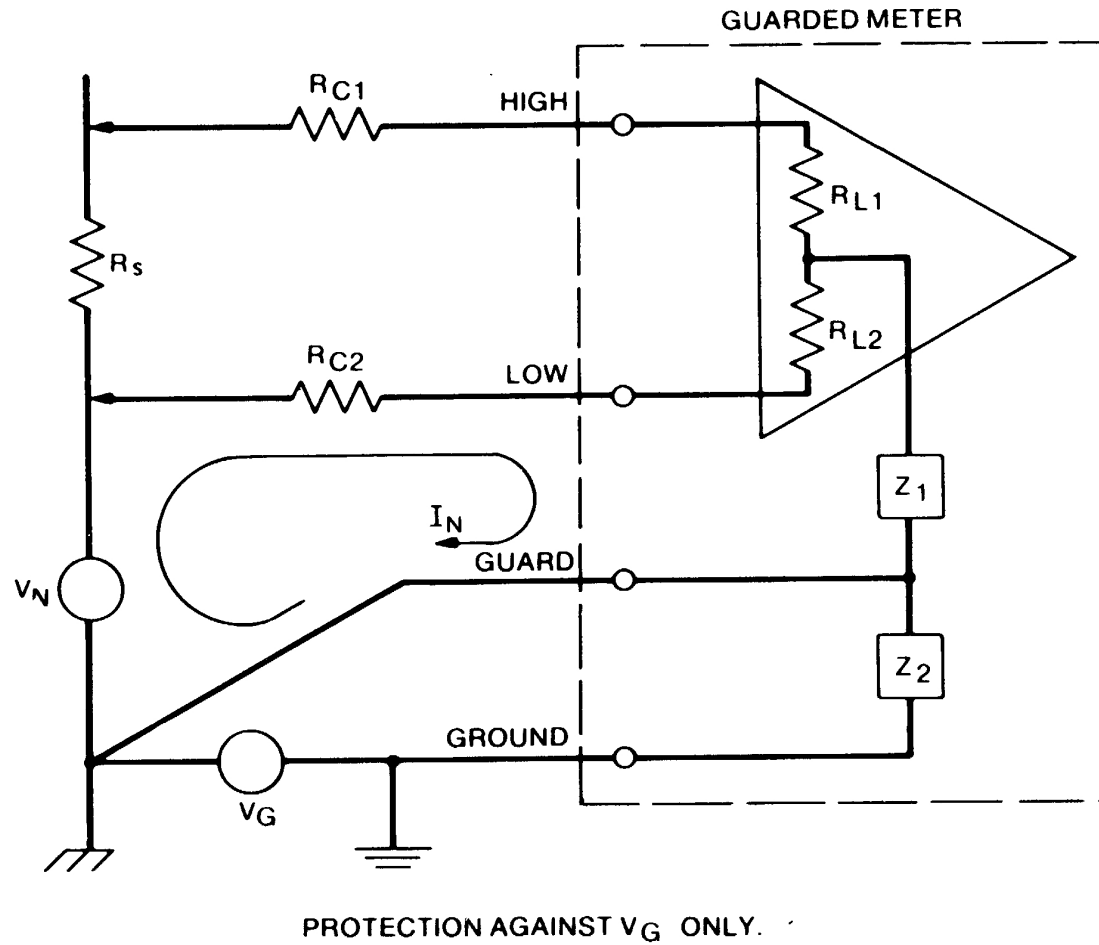


**Figure 3-47.** Guard connected to source ground gives no protection against  $V_N$ .

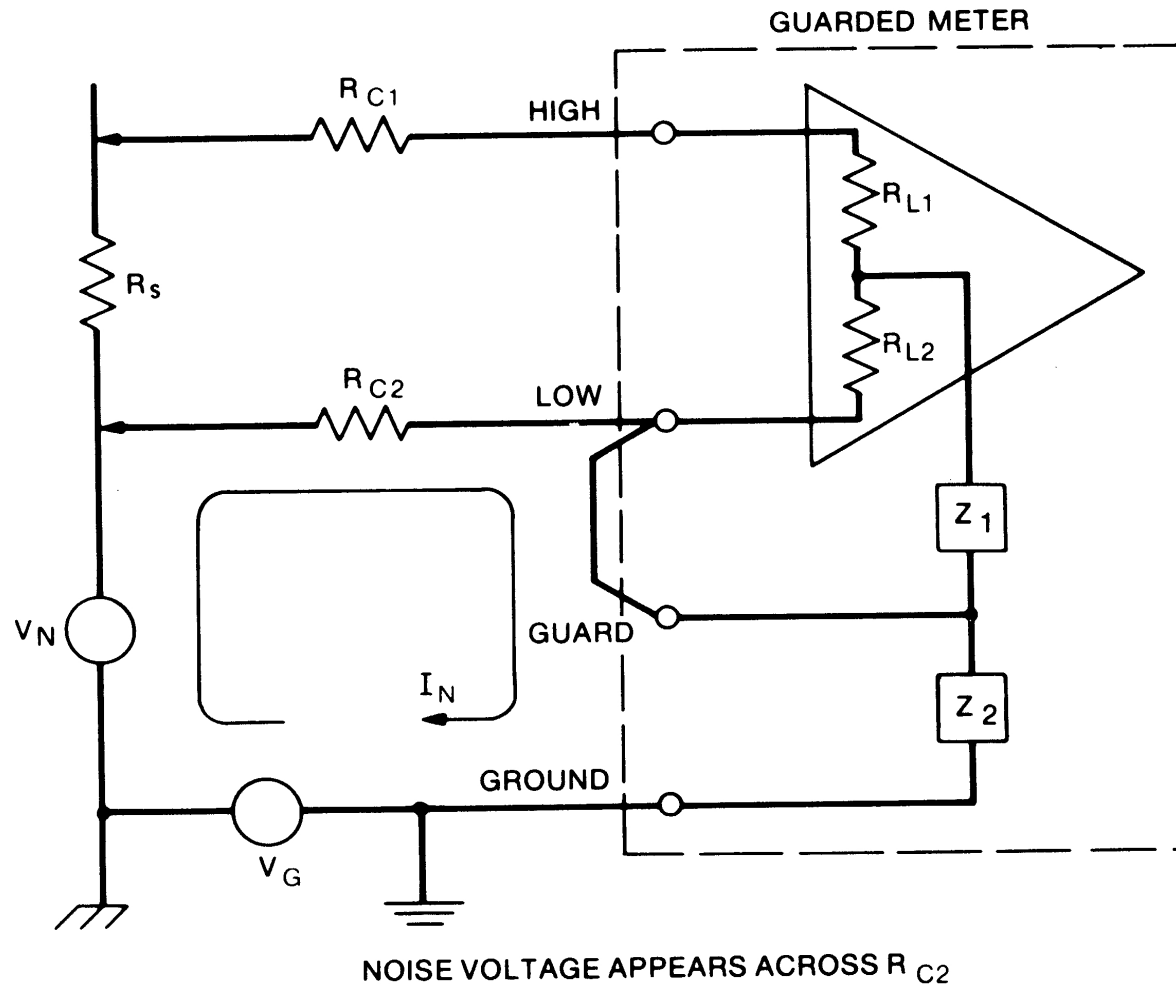

**Figure 3-48.** Guard connected to low side of meter allows noise current to flow in line resistance  $R_{C2}$ .

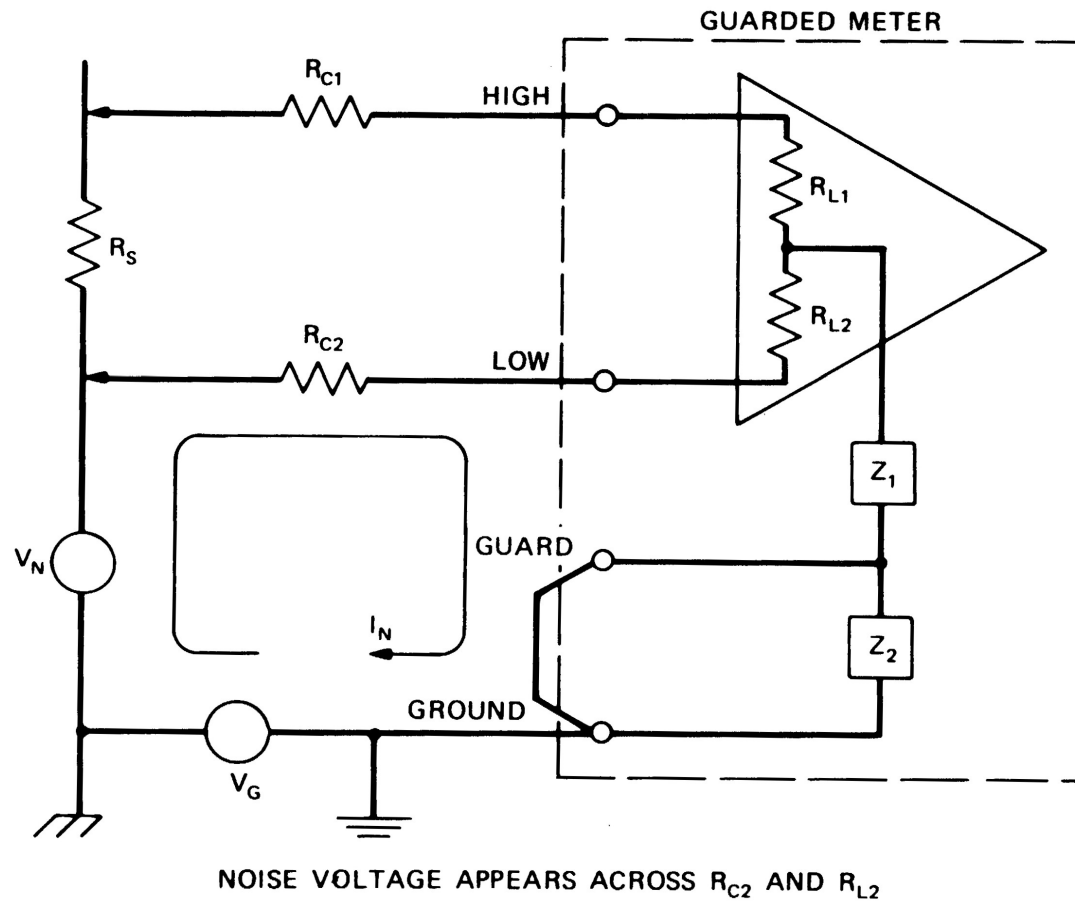

**Figure 3-49.** Guard connected to local ground is ineffective; noise current flows through  $R_{C2}$ ,  $R_{L2}$ , and  $Z_1$ .

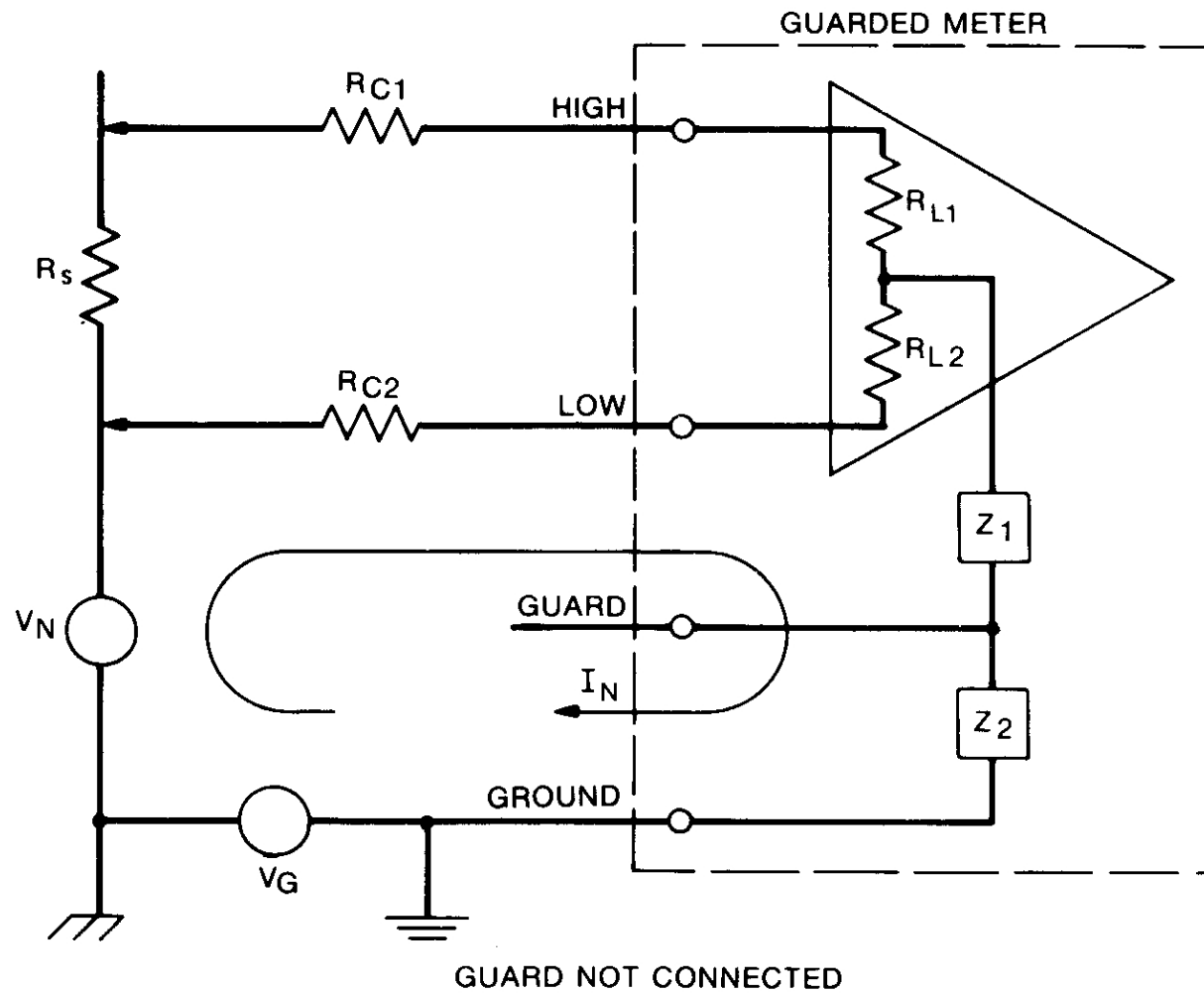

**Figure 3-50.** Guard not connected; noise currents due to  $V_N$  and  $V_G$  flow through  $R_{C2}$ ,  $R_{L2}$ ,  $Z_1$ , and  $Z_2$ .