



**UiO** : **Department of Informatics**  
University of Oslo

**IN5230**

**Electronic noise –  
Estimates and countermeasures**

## **Lecture 13 (Mot 10)**


# **Amplifier Architectures**


 
# Miller capacitance

Before we look at the transistor configurations we need a fast repetition of the Miller effect.

- When a capacitor is connected between a signal line and a stable potential the signal line will experience a capacitance according to the standard formula ( $C=\epsilon A/t$ ).
- If the potential on the other side are in phase a smaller capacitance will be experienced. If the signal is exactly equal the capacitance will "disappear".
- If the signal is in opposite phase the experienced capacitance will be larger. If it is in opposite phase and exactly equal the capacitance will be double.



# Transistor configurations:

- There are mainly three alternatives for placing a FET/BJT in an architecture:

**CS/CE** has both voltage and current amplification resulting in the highest gain. But it has also the highest input capacitance (due to the Miller effect)

**CD/CC** has a high current gain but a voltage gain close to one. It has a low input capacitance (from the Miller effect) resulting in a high input impedance. It also has low output impedance.

**CG/CB** is used to achieve low input impedance and high output impedance.

FET	BJT	
<b>CS:</b> Common Source	<b>CE:</b> Common Emitter	
<b>CD:</b> Common Drain	<b>CC:</b> Common Collector	
<b>CG:</b> Common Gate	<b>CB:</b> Common Base	

**RED**

# 10-2 Common Emitter

The schematic shows a transistor that is biased for low noise operation between 10Hz and 10kHz.

The noise values are as follows:

	10Hz	10kHz
$E_n$	2nV	2nV
$I_n$	2pA	0.3pA
$R_0$	1000 $\Omega$	6700 $\Omega$
NF@ $R_0$	1.8dB	0.3dB

The noise schematic shows a hybrid- $\pi$  model together with passive bias elements.

Note that when  $V_{EE}$  and  $V_{CC}$  are stable DC-sources, they are merged together with ground during noise analysis.


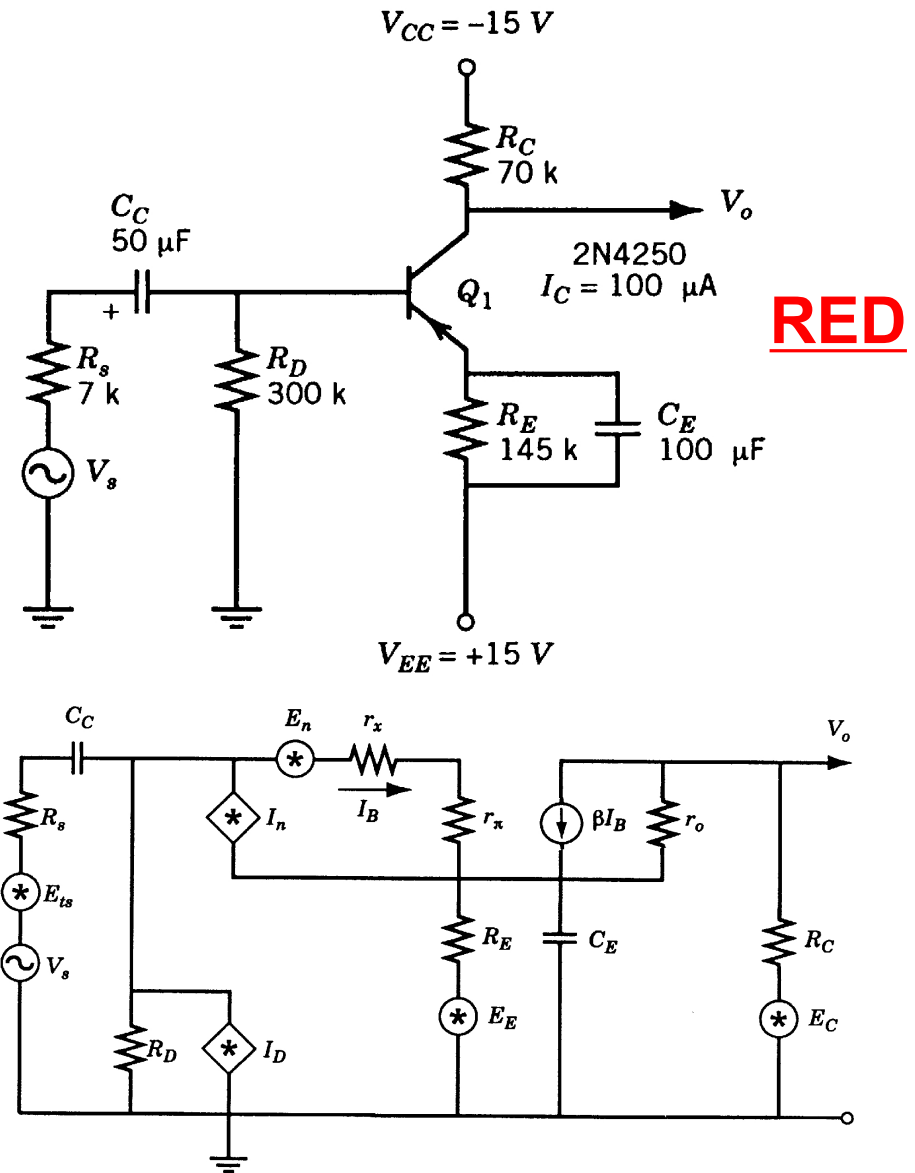


Figure 10-2 Noise and small-signal equivalent circuit for CE stage. 4

**YELLOW**
 
# The voltage gain $K_t$ :

$$K_t \cong \left( \frac{-\beta R_L}{Z_i} \right) \left( \frac{Z_i \parallel R_D}{Z_S + Z_i \parallel R_D} \right)$$



$K_t$  is the voltage gain from  $V_s$  to  $V_o$ . The first parenthesis is the voltage gain within the transistor ( $\beta$  is  $I_{CE}/I_{BE}$ ) while the second parenthesis is the network in front of the base.

$$Z_i = r_x + r_\pi + (\beta + 1)Z_E$$

The input resistance  $Z_i$  includes the resistance you can see through the base towards emitter.

$$R_L \cong R_C \parallel r_o \parallel R_{i2}$$

The load resistance consists of the collector bias resistance, the transistor internal resistance and the input resistance of the next stage:  $R_{i2}$ .

$$Z_E = R_E \parallel -jX_E$$

The emitter impedance consists of a real part and an imaginary part (a resistance and a capacitance in parallel).

$$Z_S = R_S - jX_C$$

The source impedance is a resistance in series with a capacitor.

If we assume ignorable loss in biasing, coupling and feedback we can simplify the expression for  $K_t$  to:

$$K_t \cong - \frac{\beta R_L}{Z_S + r_x + r_\pi + \beta Z_E}$$

If  $Z_S \ll r_\pi$  and  $Z_E \ll r_e$  the expression is simplified to:

$$K_t \cong - \frac{R_L}{r_e} = -g_m R_L$$

If we simplify and ignore the external load we have:

$$K'_t = K_t \quad \text{for} \quad R_L = R_C$$

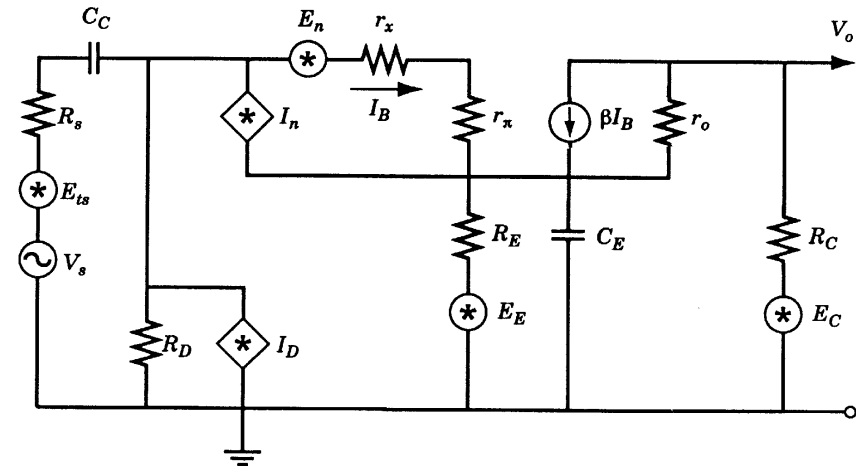


Figure 10-2 Noise and small-signal equivalent circuit for CE stage.

We will then have the following expression for the equivalent input noise:

$$E_{ni}^2 \cong E_{ns}^2 + E_n^2 \left( \frac{R_S + R_D}{R_D} \right)^2 + (I_n^2 + I_D^2)(R_S - jX_C)^2 + \frac{E_E^2}{1 + (\omega R_E C_E)^2} + \left( \frac{E_C}{K'_t} \right)^2.$$

In the expression, we recognise the first part (say from section. 7.3). Last term is also known. The second last term, however, needs some comments. The noise voltage over  $R_E$  will not be  $E_E$  for higher frequencies, because  $C_E$  will "attempt to short-circuit" this. To find the expression we first model the thermal noise in  $R_E$  as a current noise of size  $I_E = E_E / R_E$ . The noise current over  $R_E$  and  $C_E$  will be:


$$E'_E{}^2 = I_E^2 \cdot (C_E \parallel R_E) = \frac{E_E^2}{R_E^2} \left| \frac{R_E}{j\omega R_E C_E + 1} \right|^2 = \frac{E_E^2}{1 + (\omega R_E C_E)^2}$$

**YELLOW**

# Common-emitter with one voltage supply

Here a point A is established supplying a stable DC potential for the base. The point A is AC-wise short circuited to ground through  $C_B$ .


**YELLOW**

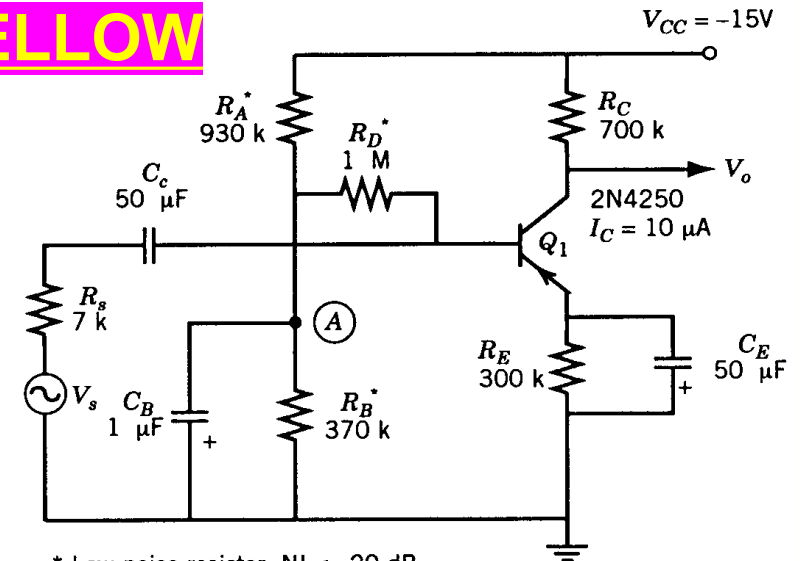

\* Low-noise resistor, NI < -20 dB

(a)

	10Hz	10kHz
$E_n$	4.5nV	4.5nV
$I_n$	0.3pA	0.1pA
$R_0$	10k $\Omega$	45k $\Omega$
NF@ $R_0$	0.68dB	0.35dB
Kt	280	
Ri	780	

 


(b)


 
# Noise in cascaded stages

We have previously studied the noise figure for cascaded amplifiers. We will now look at the equivalent input noise:



The expression for equivalent input noise can be expressed as follows

$$E_{ni}^2 = E_{ns}^2 + E_{n1}^2 + I_{n1}^2 R_s^2 + \frac{E_{n2}^2 + I_{n2}^2 r_{o1}^2}{K_{t1}^2} + \frac{E_{n3}^2 + I_{n3}^2 r_{o2}^2}{K_{t1}^2 K_{t2}^2} + \dots$$

**YELLOW**

Here  $r_{o1}$  is the output resistance of stage 1. Similarly for  $r_{o2}$ ,  $r_{o3}$  etc.

$K_{ti}$  is as earlier the voltage gain.

As previously if the gain is large enough in the first stage, noise from subsequent stages can be ignored.