



UiO : **Department of Informatics**
University of Oslo

IN5230

**Electronic noise –
Estimates and countermeasures**

Lecture X (Razavi 7)

Noise – Razavi – Chapter 7




MOSFET Thermal Noise⁽²⁹⁾

- MOS transistors exhibit thermal noise with the most significant source being the noise generated in the channel
- For long-channel MOS devices operating in saturation, the channel noise can be modelled by a current source connected between the drain and source terminals with a spectral density

$$\overline{I_n^2} = 4kT \gamma g_m$$


**Red:
Equation**

 - The coefficient ‘ γ ’ (Not body effect coefficient!) is derived to be 2/3 for long-channel transistors and is higher for submicron MOSFETs
- As a rule of thumb, Razavi assume $\gamma=1$



**Red:
Figure**

MOSFET Thermal: Example

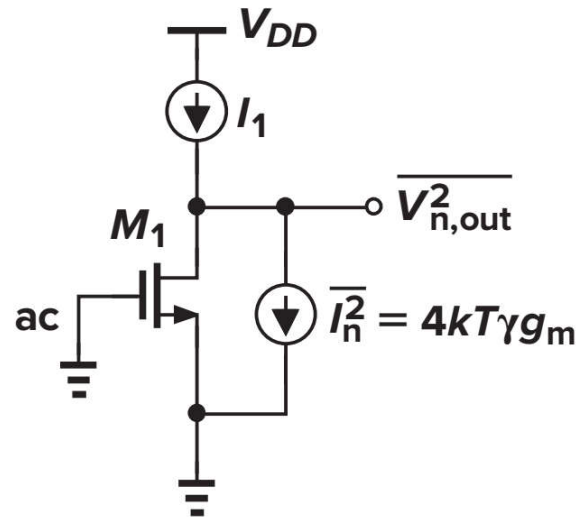


- The maximum output noise occurs if the transistor sees only its own output impedance as the load, i.e., if the external load is an ideal current source
- Output noise voltage spectrum is given by (7.29,7.30)

$$S_{out}(f) = S_{in}(f) |H(f)|^2$$


$$\overline{V_n^2} = \overline{I_n^2} r_O^2 = (4kT\gamma g_m) r_O^2$$

MOSFET Thermal Noise

 


- Ohmic sections of a MOSFET have a finite resistivity and exhibit thermal noise
- For a wide transistor, source and drain resistance is negligible whereas the gate distributed resistance may become noticeable.

□ = contact

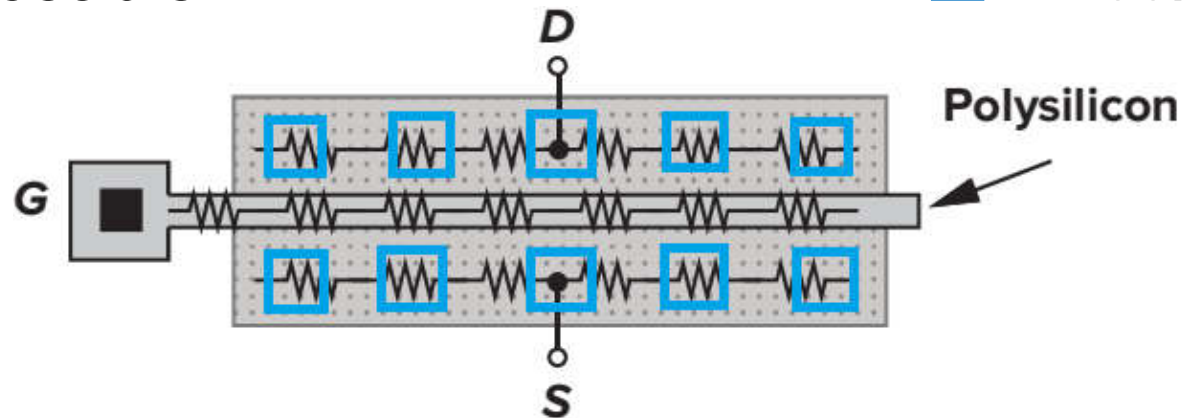


MOSFET Thermal Noise

 

- In the noise model (left fig), the lumped resistance R_1 represents the distributed gate resistance
- In the distributed structure of the right figure, unit transistors near the left end see the noise of only a fraction of R_G whereas those near the right end see the noise of most of R_G
- It can be proven that $R_1 = R_G/3$ and hence the noise generated by gate resistance is $\overline{V_{nRG}^2} = 4kT R_G/3$


**Red:
Equation**

MOSFET Thermal Noise

 

- Effect of R_G can be reduced by proper layout
- In left fig, the two ends of the gate are shorted by a metal line, reducing the distributed resistance from R_G to $R_G/4$
- Alternatively, the transistor can be folded as in the right figure so that each gate “finger” exhibits a resistance of $R_G/4$ for composite transistor

MOSFET Thermal Noise: Example

 

$$\overline{V_{n,RG}^2} = 4kT \frac{R_G}{3}$$


- If the total distributed gate resistance is R_G , the output noise voltage due to R_G is given by (7.32)

$$\overline{V_{n,out}^2} = 4kT \frac{R_G}{3} (g_m r_O)^2$$

- For the gate resistance noise to be negligible, we must ensure (7.33)

$$\frac{R_G}{3} \ll \frac{\gamma}{g_m} \quad \text{Yellow: Equation}$$

Flicker Noise⁽³⁶⁾

 

Yellow:
Figure

- At the interface between the gate oxide and silicon substrate, many “dangling” bonds appear, giving rise to extra energy states
- Charge carriers moving at the interface are randomly trapped and later released by such energy states, introducing “flicker” noise in the drain current
- Other mechanisms in addition are believed to generate flicker noise


Flicker Noise

- Average power of flicker noise cannot be predicted easily
- It varies depending on cleanness of oxide-silicon interface and from one CMOS technology to another
- Flicker noise is more easily modelled as a voltage source in series with the gate and in saturation region, is roughly given by

$$\overline{V_n^2} = \frac{K}{C_{ox}WL} \cdot \frac{1}{f} \quad \text{Red: Equation}$$

- K is a process-dependent constant on the order of $10E-25V^2F$


Flicker Noise

 

- The noise spectral density is inversely proportional to frequency
 - Trap and release phenomenon occurs at low frequencies more often
- Flicker noise is also called “1/f” noise
- To reduce 1/f noise, device area must be increased
- Generally, **PMOS devices exhibit less 1/f noise than NMOS transistors**
 - Holes are carried in a “buried” channel, at some distance from the oxide-silicon interface

Flicker Noise Corner Frequency

 - At low frequencies, the flicker noise power approaches infinity
- At very slow rates, flicker noise becomes indistinguishable from thermal drift or aging of devices
 - Noise component below the lowest frequency in the signal of interest does not corrupt it significantly
- Intersection point of thermal noise and flicker noise spectral densities is called “corner frequency” f_c



Yellow:
Figure

Nanometer Design Notes


- $W/L = 5\mu\text{m}/40\text{nm}$,
- $I_D = 250\mu\text{A}$

- Low frequencies: Flicker noise
- High frequencies: Thermal noise


- \Rightarrow PMOS exhibit less noise than NMOS (and PNP less than NPN)

- \Rightarrow NMOS noise corner at several hundred MHz

Yellow:
Figure

 

Input-Referred Noise: Example 3/9

 


- For the simple CS stage, the input-referred noise voltage is given by (7.45,7.46,7.47)
$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2}$$

$$= \left(4kT \gamma g_m + \frac{K}{C_{ox} WL} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2 \frac{1}{g_m^2 R_D^2}$$

$$= 4kT \frac{\gamma}{g_m} + \frac{K}{C_{ox} WL} \cdot \frac{1}{f} + \frac{4kT}{g_m^2 R_D}$$

- First and third terms combined can be viewed as thermal noise of an equivalent resistance R_T , so that the equivalent input-referred thermal noise is $4kTR_T$

Common-Source Stage: Example 3/4

 


- Since the voltage gain is equal to $g_{m1}(r_{O1} \parallel r_{O2})$, total noise voltage referred to the gate of M_1 is (7.77,7.78)

$$\overline{V_{n,in}^2} = 4kT(\gamma g_{m1} + \gamma g_{m2}) \frac{1}{g_{m1}^2} = 4kT\gamma \left(\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$

- Thus, g_{m2} must be minimized because M_2 serves as a current source rather than a transconductor

Common-Source Stage: Example 4/4

 

- Total output noise with C_L is (7.79,7.80)

$$\overline{V_{n,out,tot}^2} = \int_0^\infty 4kT \gamma (g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})^2 \frac{df}{1 + (r_{O1} \parallel r_{O2})^2 C_L^2 (2\pi f)^2}$$

$$\overline{V_{n,out,tot}^2} = \gamma (g_{m1} + g_{m2})(r_{O1} \parallel r_{O2}) \frac{kT}{C_L}$$

- A low-frequency input sinusoid of amplitude V_m yields an output amplitude equal to $g_{m1}(r_{O1} \parallel r_{O2})V_m$ with an output SNR of (7.81,7.82)



$$\text{SNR}_{out} = \left[\frac{g_{m1}(r_{O1} \parallel r_{O2})V_m}{\sqrt{2}} \right]^2 \cdot \frac{1}{\gamma (g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})(kT/C_L)}$$

Yellow:

Equation

$$= \frac{C_L}{2\gamma kT} \cdot \frac{g_{m1}^2 (r_{O1} \parallel r_{O2})}{g_{m1} + g_{m2}} V_m^2$$

Source Followers: Thermal Noise 2/2

  

- The voltage gain is

$$A_v = \frac{\frac{1}{g_{mb1}} \parallel r_{O1} \parallel r_{O2}}{\frac{1}{g_{mb1}} \parallel r_{O1} \parallel r_{O2} + \frac{1}{g_{m1}}}$$


- Total input-referred noise voltage is (7.110,7.111)

$$\overline{V_{n,in}^2} = \overline{V_{n1}^2} + \frac{\overline{V_{n,out}^2}|_{M2}}{A_v^2} = 4kT\gamma \left(\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$

Yellow:
Equation

- Source followers add noise to the input signal and provide a voltage gain less than unity

Noise in five-transistor OTA

 

- The noise current of M_3 primarily circulates through the diode-connected impedance $1/g_{m3}$, producing a voltage at the gate of M_4 with spectral density $4kT\gamma/g_{m3}$



- This noise is multiplied by g_{m4}^2 as it emerges from the drain of M_4 ; the noise current of M_4 also flows directly through the output short-circuit thus $\overline{I_{n,out}^2} = 4kT\gamma(2g_{m1,2} + 2g_{m3,4})$
- Multiplying this noise by $R_{out}^2 \approx (r_{O1,2} || r_{O3,4})^2$ and dividing the result by $A_v^2 = G_m^2 R_{out}^2$ the total input-referred noise is

$$\overline{V_{n,in}^2} = 8kT\gamma \left(\frac{1}{g_{m1,2}} + \frac{g_{m3,4}}{g_{m1,2}^2} \right)$$

Yellow:
Equation


Noise in Op Amps^{9.12}

- How to analyse for noise in more complex amplifier structures?
 - ⇒ Find which gate voltages that influence most on the output!
 - ⇒ Analyse manually or by simulation!
-
- Upper right: Telescopic
 - Lower left: Folded cascode
 - Lower right: Two-stage opamp

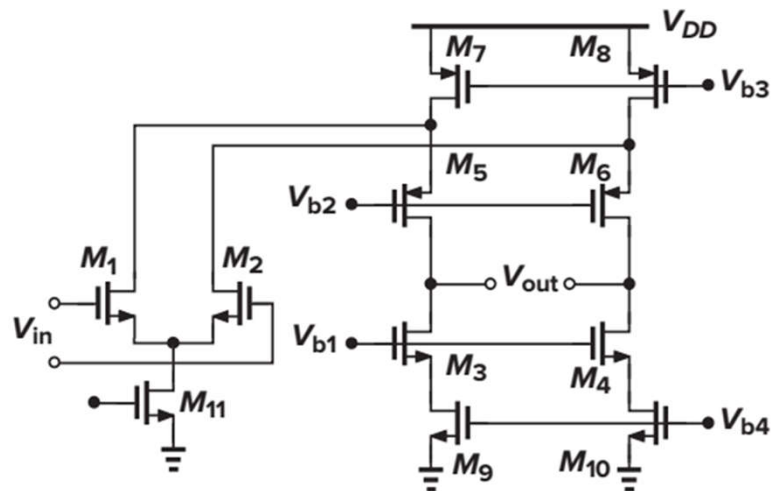 

IN5230

Noise in field effect transistors

 


Noise in Op Amps^{9.12}

Telescopic

- M7-M8 give a coarse regulation of current while M5-M6 gives fine tuning i.e. M7-M8 has larger influence
- M1-M2 is the signal inputs, obviously more sensitive than M3-M4.
- \Rightarrow M1-M2 and M7-M8 are the most noise sensitive.
- Resulting expression below:

$$\overline{V_n^2} = 4kT \left(2 \frac{\gamma}{g_{m1,2}} + 2 \frac{\gamma g_{m7,8}}{g_{m1,2}^2} \right) + 2 \frac{K_N}{(WL)_{1,2} C_{ox} f} + 2 \frac{K_P}{(WL)_{7,8} C_{ox} f} \frac{g_{m7,8}^2}{g_{m1,2}^2}$$

YELLOW: Figure

 

Noise in Op Amps^{9.12}

Folded-cascode

- The gate voltage of M1-M2, M7-M8, M9-M10 will give the largest influence on the output and are hence most noise sensitive. (We test by making a small step on M7 and keep the others fixed etc.)
- We calculate (thermal) noise from M7-M8 and M9-M10 to output.


$$\overline{V_{n,out}^2} |_{M7,8} = 2 \left(4kT \frac{\gamma}{g_{m7,8}} g_{m7,8}^2 R_{out}^2 \right)$$

$$\overline{V_{n,out}^2} |_{M9,10} = 2 \left(4kT \frac{\gamma}{g_{m9,10}} g_{m9,10}^2 R_{out}^2 \right)$$

- Then we add M1-M2 contribution and calculate back to the input V_{in}


$$\overline{V_{n,int}^2} = 8kT \left(\frac{\gamma}{g_{m1,2}} + \gamma \frac{g_{m7,8}}{g_{m1,2}^2} + \gamma \frac{g_{m9,10}}{g_{m1,2}^2} \right)$$

YELLOW: Figure

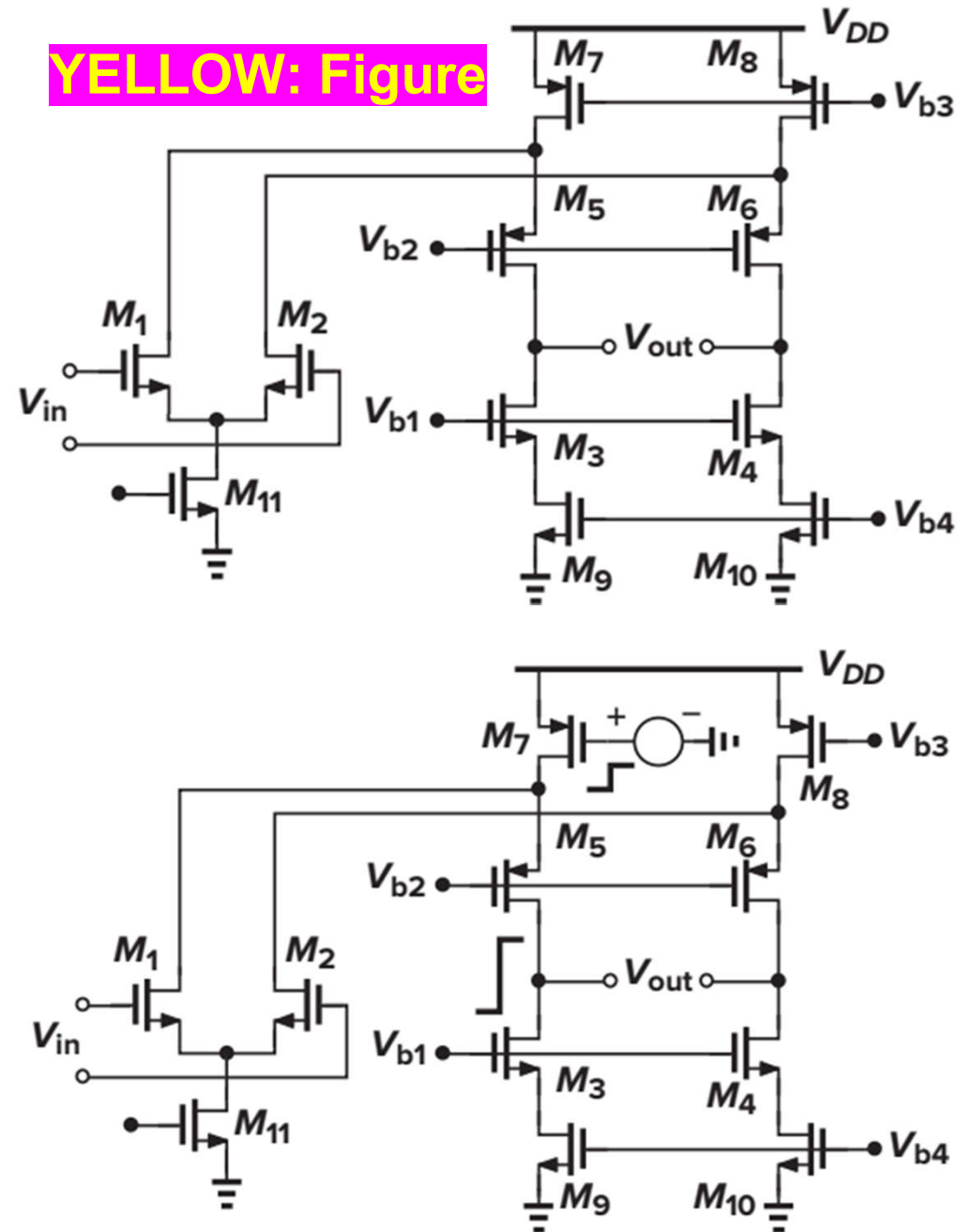

Noise in Op Amps^{9.12}

Two-stage opamp

 

YELLOW: Figure

- Gain to Vout1:

$$g_{m1}(r_{O1} \parallel r_{O3}) \times g_{m5}(r_{O5} \parallel r_{O7})$$

- Noise from M5-M8 on input

$$\overline{V_n^2} \Big|_{M5-8} = 2 \times 4kT \gamma (g_{m5} + g_{m7})(r_{O5} \parallel r_{O7})^2 \frac{1}{g_{m1}^2 (r_{O1} \parallel r_{O3})^2 g_{m5}^2 (r_{O5} \parallel r_{O7})^2} = 8kT \gamma \frac{g_{m5} + g_{m7}}{g_{m1}^2 g_{m5}^2 (r_{O1} \parallel r_{O3})^2}$$

- Noise from M1-M4 on input

$$\overline{V_n^2} \Big|_{M1-4} = 2 \times 4kT \gamma \frac{g_{m1} + g_{m3}}{g_{m1}^2}$$


- Total noise on input

$$\overline{V_{n,tot}^2} = 8kT \gamma \frac{1}{g_{m1}^2} \left[g_{m1} + g_{m3} + \frac{g_{m5} + g_{m7}}{g_{m5}^2 (r_{O1} \parallel r_{O3})^2} \right]$$

YELLOW: Equation

Bandgap - Speed and Noise Issues^{12.6}

 
- The bandgap reference generates a stable voltage on P independent of temperature variations. This is used to generate stable currents on M5, M6 etc.
- An unwanted voltage spike on N may be transferred to P and further on to M6 and other parts using the reference.
- In a low power implementation the amplifier will be slow and this makes it less resistant towards noise



YELLOW: Figure


Bandgap - Speed and Noise Issues^{12.6}

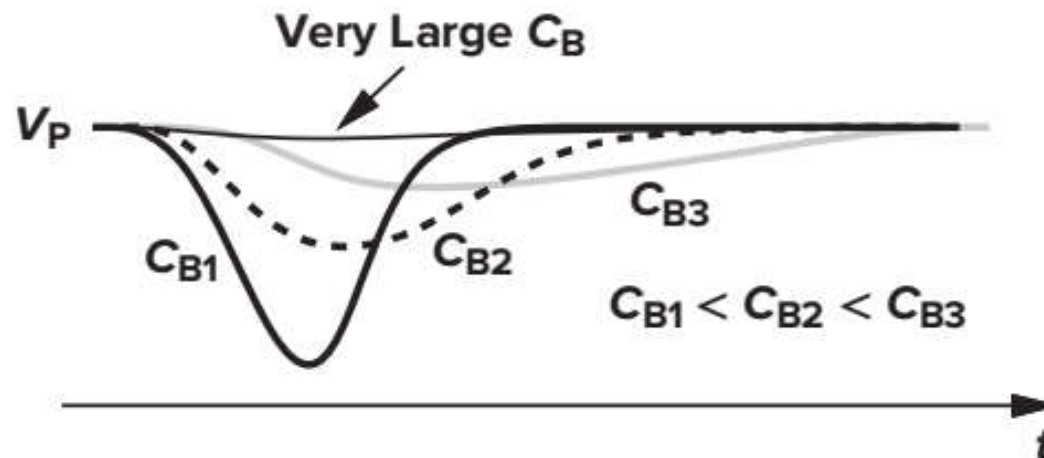- Using a faster amplifier will reduce the noise but increase the power consumption
- An alternative is to add a capacitor C_B in node P. A large C_B reduces the noise spike but makes it last for a longer time. It also increases the time before the circuit is settled after power on. This is a disadvantage in particular when the reference is normally off and only turned on when it should be used.



Bandgap - Speed and Noise Issues^{12.6}

 
- Whether a fast amplifier or large capacitance (or a combination) should be used will depend on the application.
- The noise resistivity towards this type of noise can be modelled by adding a voltage pulse on a capacitor connected to the generated reference voltage.



RED: Figure


Reduction of Noise by Offset Cancellation^{14.2.3}

 - DC-offset \approx low frequency
- Periodic cancellation?



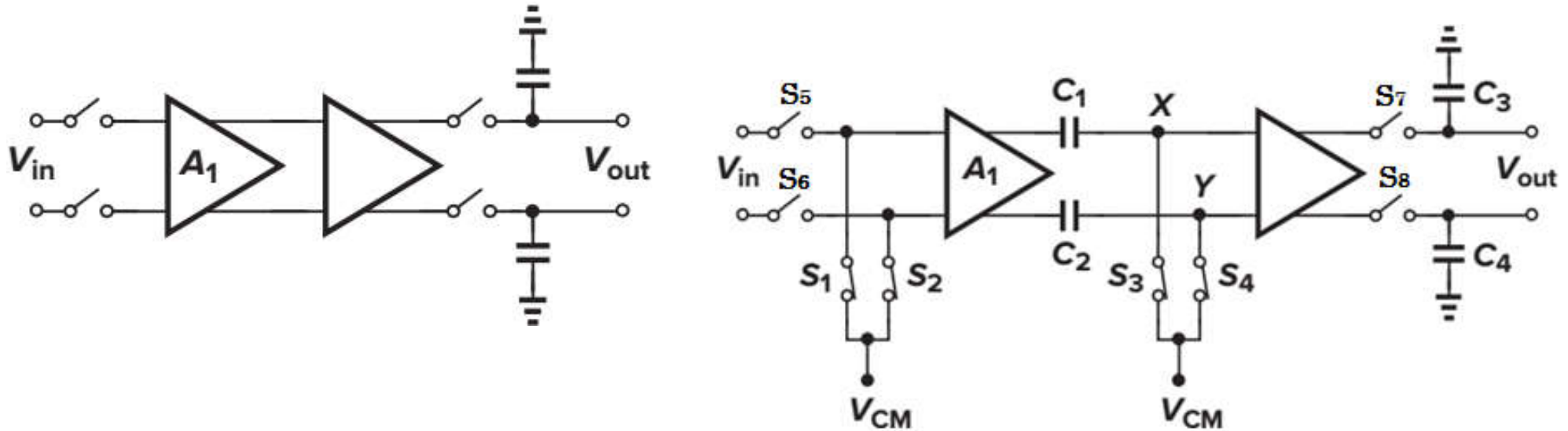- Problem: Noise of A_1 corrupts V_{in}


Reduction of Noise by Offset Cancellation^{14.2.3}



- Offset cancellation before every sampling
- CDS: Correlated Double Sampling
 - (Leads to aliasing of wideband noise)

Reduction of Noise by Offset Cancellation^{14.2.3}

YELLOW: Figure

 

1. S1-S4 closed, S5-S8 open: Offset of A_1 stored on C_1 and C_2
2. S1-S4 open, S5-S8 closed: Input sets C_3 and C_4
3. (S1-S6 closed, S5-S6 open), S7-S8 open: C_3 and C_4 keeps sampled value

Reduction of Noise by Offset Cancellation^{14.2.3}

- $\Delta t = t_2 - t_1 = 10 \text{ ns}$
- Offset/noise under $1/\Delta t$ is suppressed
- Sinus maximum slew rate: $2\pi fA$, maximum voltage change: $\Delta V = 2\pi fA\Delta t$.
- 1MHz: $\Delta V_1/A = 6.3\%$
- 10MHz: $\Delta V_1/A = 63\%$
- Low frequency has not time to change

