

INF2270, counter with synchronous load

P. Häfliger

April 6, 2010

Synchronous Counter with load

Figure 1 shows one possible solution. Remember that a JK flipflop works like a T-flipflop if J and K are shorted. This is the case if $LD=0$ since the same signal is routed to both J and K through the multiplexers and the circuit becomes equivalent to the synchronous counter without a LD control signal.

When $LD=1$, on the other hand, K receives the inverted J signal and J is shorted to the input. Thus, on the next clock edge, the value I is loaded into the counter.

 


Figure 1: A counter with LD and CE control signals