



inf

INF2270 — Spring 2010

Philipp Häfliger

Lecture 3: Sequential Logic



UNIVERSITETET
I OSLO

content

Flip-Flops

Finite State Machines

Selected Sequential Logic
Counters
Shift Registers

Binary Addition

content

Flip-Flops

Finite State Machines

Selected Sequential Logic
Counters
Shift Registers

Binary Addition

Flip-Flop


Flip-flops are digital circuits with two stable states that are used as storage elements for 1 bit. The term 'flip-flop' is in the more recent use of the language more specifically used for synchronous binary memory cells (e.g. D-flip-flop, JK-flip-flop, T-flip-flop), whereas the term 'latch' (e.g. SR-latch) is used for the simpler more basic asynchronous 'transparent' storage elements, but this is not necessarily consequently applied throughout the literature.

Characteristic Table and Equation

The behaviour of a flip-flop can be expressed with a *characteristic table*: a truth table expressing the relation between the input and the present state, and the next state. An alternative is the *characteristic equation* which defines the dependency of the next state on the input and present state as a Boolean expression. Examples follow on the next slides.

Flip-Flop Principle: Positive Feedback

 The simplest Flip Flop: Gated D-Latch/Transparent Latch




Characteristic Equation:

$$Q = D \wedge E \vee \overline{E} \wedge Q$$

When the feedback loop is connected the state is maintained

SR-Latch

 

Characteristic

Equation:

$$Q = S \vee \bar{R} \wedge Q \text{ (illegality of}$$

input (1,1) not covered!)


Characteristic Table

S	R	Q	Q_{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	?
1	1	1	?


Abbreviated:

S	R	Q
0	0	Q
0	1	0
1	0	1
1	1	?

Clock Signal

 

JK-Flip-Flop

 

Characteristic
Equation:

$$Q = J \wedge \bar{Q} \vee \bar{K} \wedge Q$$


Characteristic Table

J	K	Q_t	Q_{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

abbreviated:

J	K	Q_{t+1}
0	0	Q_t
0	1	0
1	0	1
1	1	\bar{Q}_t

T-Flip-Flop

 

Characteristic
Equation:
 $Q = T \oplus Q$


Characteristic Table

T	Q_t	Q_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

abbreviated:

T	Q_{t+1}
0	Q_t
1	\bar{Q}_t

D-Flip-Flop

 

Characteristic
Equation:
 $Q = D$

Characteristic Table

D	Q_t	Q_{t+1}
0	0	0
0	1	0
1	0	1
1	1	1

Abbreviated:

D	Q_t	Q_{t+1}
0	X	0
1	X	1

or simply:

D	Q_{t+1}
0	0
1	1

content

Flip-Flops

Finite State Machines

Selected Sequential Logic
Counters
Shift Registers


Binary Addition

Finite State Machines


Finite State Machines (FSM) are a formal model suited to describe sequential logic, i.e. logic circuits whose output does not only depend on the present input but on internal memory and thus, on the history or sequence of the inputs.

Specifying a FSM with a state transition graph

Example: Traffic Light

 

Moore and Mealy Machine

 

In a *Moore* FSM, the output depends solely on the state/memory, in contrast to the *Mealy model*, where outputs also depend on the inputs directly. The latter sometimes allows to reduce the number of states, but is more demanding to design.

Synchronous and Asynchronous FSM

- ▶ *Synchronous* FSMs include an implicit positive transition of a global *clock* signal as transition condition for all state changes. Synchronous FSMs realized as sequential logic circuits use synchronous flip-flops as memory elements, e.g. D-flip-flops. They are generally simpler to implement and easier to verify and test. The clock frequency needs to be slow enough to allow the slowest combinational transition condition to be computed.
- ▶ *Asynchronous* FSMs change state at once if the explicit transition condition is met. They can be very fast but are much harder to design and verify.

content

Flip-Flops


Finite State Machines

Selected Sequential Logic
Counters
Shift Registers

Binary Addition

Deducing a Synchronous 3-bit Counter from a FSM

 Counters are a frequently used building block in digital electronics. A counter increases a binary number with each clock edge.



For the design of this simple counter variant, state transitions are unconditional, i.e. they happen in every case at every positive clock edge.

State Transition Table

We chose to represent the 8 states in D-flip-flops with the corresponding binary numbers. Thus, there is in a first instance no output combinational logic necessary. (Note that output combinational logic will be necessary if the numbers should, for example, appear on an LED-display)

present			in	next		
S_2	S_1	S_0	NA	S_2	S_1	S_0
0	0	0		0	0	1
0	0	1		0	1	0
0	1	0		0	1	1
0	1	1		1	0	0
1	0	0		1	0	1
1	0	1		1	1	0
1	1	0		1	1	1
1	1	1		0	0	0

Karnaugh Maps

		$S_{2_{next}}$	
		S_0	S_1
S_2	S_1	0	1
00	0	0	0
01	0	0	1
11	1	1	0
10	1	1	1

		$S_{1_{next}}$	
		S_0	S_1
S_2	S_1	0	1
00	0	0	1
01	1	1	0
11	1	1	0
10	0	0	1

		$S_{0_{next}}$	
		S_0	S_1
S_2	S_1	0	1
00	1	1	0
01	1	1	0
11	1	1	0
10	1	1	0


$$\begin{aligned}S_{2_{next}} &= (S_2 \wedge \overline{S_1}) \vee (S_2 \wedge \overline{S_0}) \vee (\overline{S_2} \wedge S_1 \wedge S_0) \\ &= S_2 \wedge (\overline{S_1} \vee \overline{S_0}) \vee (\overline{S_2} \wedge (S_1 \wedge S_0)) \\ &= S_2 \wedge (\overline{S_1 \wedge S_0}) \vee \overline{S_2} \wedge (S_1 \wedge S_0) \\ &= S_2 \oplus (S_1 \wedge S_0)\end{aligned}$$

General Synchronous Counter Element

$$S_{n_{next}} = S_n \oplus \left(\bigwedge_{k=0}^{n-1} S_k \right) \quad (1)$$

\Rightarrow T-flip-flop where $T = \bigwedge_{k=0}^{n-1} S_k$
(Compare characteristic equation of the T-flip-flop!)


3 bit Synchronous Counter

 

Useful extensions:

- ▶ Possibility for loading an initial number (control signal LD and an input bus)
- ▶ Reset to zero (control signal RES)
- ▶ Switching between up and down counting (control signal UpDown)

3 bit Ripple Counter

 

A simple and popular asynchronous variant (only the first T-flip-flop is clocked with the global clock) of a counter. A possible disadvantage is that the output signal 'ripples' from the lowest to the highest bit, i.e. the highest bits are updated with a delay. This must be taken into account, if this kind of counter is used.

content

Flip-Flops

Finite State Machines


Selected Sequential Logic

Counters

Shift Registers

Binary Addition

Registers

 

The Clock signal is implicit and usually not drawn for most higher level synchronous logic

- ▶ Memory cells composed of an array of flip-flops that are accessed in parallel (e.g. as memory blocks in a CPU) are called registers
- ▶ Most commonly D-flip-flops and additional control combinational logic are used, e.g. a write enable (WE or LD) is 'AND'ed with the global clock for the D-flip-flop clock
- ▶ They are sized to store convenient unit of memory (Byte, Word ...)
- ▶ They are sometimes equipped with some extra functions beyond storage




Shift Register

- ▶ Shift registers are registers that can shift the bits by one position per clock cycle
- ▶ The last bit 'falls out' of the register when shifting
- ▶ The first bit that is 'shifted in' can for example:
 - ▶ be set to zero
 - ▶ be connected to the last bit (cycling/ring counter)
 - ▶ be connected to a serial input for serial loading
- ▶ Typical control signals are:
 - ▶ load (LD, for parallel loading)
 - ▶ shift enable (SE, to enable or stop the shifting)
 - ▶ left shift (LS, for controlling the direction of the shift)
- ▶ A left shift of a binary number corresponds to a multiplication with 2, a right shift to a division with 2

Shift Register State Transition Table

control			next		
LD	SE	LS	O_2	O_1	O_0
1	X	X	I_2	I_1	I_0
0	0	X	O_2	O_1	O_0
0	1	0	RSin	O_2	O_1
0	1	1	O_1	O_0	LSin

Shift Register Schematics

   

Uses for Shift Registers

- ▶ Parallel to Serial Conversion
- ▶ Binary Multiplication
- ▶ Ring 'one-hot' code counters/scanners
- ▶ Pseudo random number generators
- ▶ ...

content

Flip-Flops

Finite State Machines

Selected Sequential Logic
Counters
Shift Registers

Binary Addition

Half Adder

Truth table
for a 1-bit half
adder:


a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

S is the result
and C is the carry
bit, i.e. a bit
indicating if
there is an
overflow and an
additional bit is
necessary to
represent the
result.

Example:

$$\begin{array}{r} 0001 \\ + 0011 \\ \hline = 0100 \end{array}$$

Schematics:

 

Full Adder (1/2)

A half adder cannot be cascaded to a binary addition of an arbitrary bit-length since there is no carry input. An extension of the circuit is needed.

Full Adder truth table:

C_{in}	a	b	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder (2/2)

Schematics:

