

INF2270, exercise on combinational logic:
solution

P. Häfliger

January 28, 2011

A

$$[a \oplus b] \vee [(b \wedge c) \oplus (c \wedge a)] \quad (1)$$

Truth table:

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Karnaugh map:

$bc \setminus a$	0	1
00	0	1
01	0	1
11	1	0
10	1	0

Resulting Boolean function:

$$(a \wedge \bar{b}) \vee (\bar{a} \wedge b) \quad (2)$$

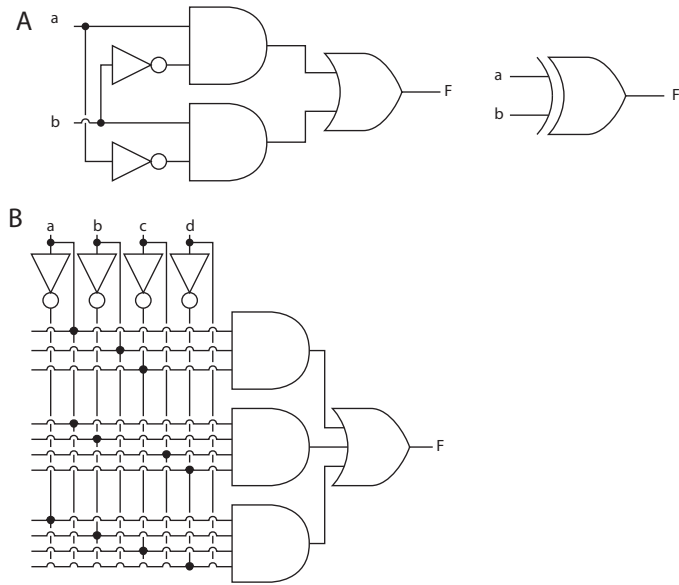


Figure 1: The resulting simplified circuits

B

Boolean function:

$$[((a \wedge b) \vee c) \vee (c \wedge (b \vee d))] \oplus [(c \wedge (b \vee d)) \oplus ((b \vee d) \vee a)] \quad (3)$$

Truth table:

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Karnaugh map:

cd \ ab	00	01	11	10
00	1	0	1	0
01	0	0	1	0
11	0	0	0	0
10	0	0	0	1

Resulting Boolean function:

$$(a \wedge b \wedge \bar{c}) \vee (a \wedge \bar{b} \wedge c \wedge \bar{d}) \vee (\bar{a} \wedge \bar{b} \wedge \bar{c} \wedge \bar{d}) \quad (4)$$