


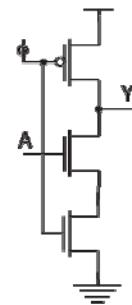
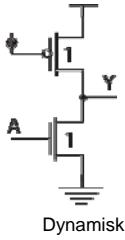


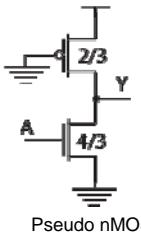


Introduksjon til dynamisk CMOS

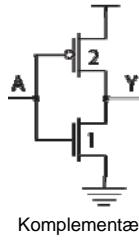

2007

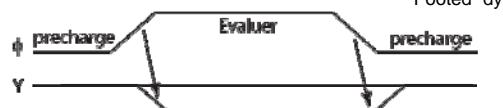


Dynamiske invertere:

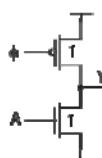

$$g_d = \frac{1}{3}$$

$$P_d = \frac{2}{3}$$

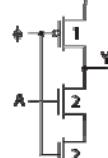

$$g_d = \frac{2}{3}$$

Ikke-footed inverter:

$$\begin{aligned} g_d &= \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n}\right)^{-1}} \\ &= \frac{W_n}{3W_n} \\ &= \frac{1}{3} \end{aligned}$$

$$\begin{aligned} P_d &= \frac{1}{W_n} \cdot R \cdot (W_p + W_n) \cdot C \\ &= 1R \cdot 2C \\ &= 2RC \\ &= \frac{2}{3} \tau \end{aligned}$$

Footed inverter:


$$\begin{aligned} g_d &= \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}} \\ &= \frac{W_n}{3\left(\frac{2}{W_n}\right)^{-1}} \\ &= \frac{2}{3} \end{aligned}$$

$$\begin{aligned} P_d &= \left(\frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n) \cdot C \\ &= \left(\frac{1}{2} + \frac{1}{2}\right) R \cdot (1+2)C \\ &= 3RC \\ &= 1\tau \end{aligned}$$

2007



Dynamiske NAND2:

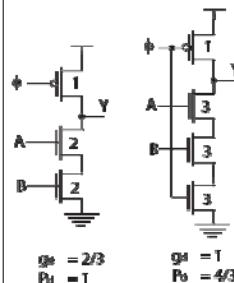

Ikke-footed NAND2:

$$g_d = \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}}$$

$$= \frac{W_n}{3\left(\frac{2}{W_n}\right)^{-1}}$$

$$= \frac{2}{3}$$

$$P_d = \left(\frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n) \cdot C$$

$$= \left(\frac{1}{2} + \frac{1}{2}\right) R \cdot (1+2)C$$

$$= 3RC$$

$$= 1\tau$$

Footed NAND2:

$$g_d = \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}}$$

$$= \frac{W_n}{3\left(\frac{3}{W_n}\right)^{-1}}$$

$$= 1$$

$$P_d = \left(\frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n) \cdot C$$

$$= \left(\frac{1}{3} + \frac{1}{3} + \frac{1}{3}\right) R \cdot (1+3)C$$


$$= 4RC$$

$$= \frac{4}{3}\tau$$

2007

3/23

Dynamiske NOR2:

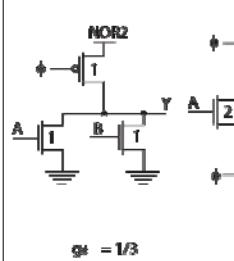

Ikke-footed NOR2:

$$g_d = \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n}\right)^{-1}}$$

$$= \frac{W_n}{3\left(\frac{1}{W_n}\right)^{-1}}$$

$$= \frac{1}{3}$$

$$P_d = \left(\frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n + W_n) \cdot C$$

$$= \left(\frac{1}{2} + \frac{1}{2}\right) R \cdot (1+1+1)C$$

$$= 3RC$$

$$= 1\tau$$

Footed NOR2:

$$g_d = \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}}$$

$$= \frac{W_n}{3\left(\frac{2}{W_n}\right)^{-1}}$$

$$= \frac{2}{3}$$

$$P_d = \left(\frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n + W_n) \cdot C$$

$$= \left(\frac{1}{2} + \frac{1}{2}\right) R \cdot (1+2+2)C$$

$$= 5RC$$

$$= \frac{5}{3}\tau$$


2007

4/23

Oppgave 6.27

Tegn transistorskjema for dynamisk footed 3inngangs NAND og NOR porter. Angi bredde p'a transistorene. Hva blir logisk effekt for portene?

Dynamiske NAND3:

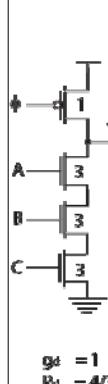

$$g_d = 1$$

$$P_d = 4/3$$

Ikke-footed NAND3:

$$\begin{aligned} g_d &= \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}} \\ &= \frac{W_n}{3\left(\frac{3}{W_n}\right)^{-1}} \\ &= 1 \\ P_d &= \left(\frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n) \cdot C \end{aligned}$$

$$\begin{aligned} &= \left(\frac{1}{3} + \frac{1}{3} + \frac{1}{3}\right) R \cdot (1+3)C \\ &= 4RC \\ &= \frac{4}{3}\tau \end{aligned}$$

$$g_d = 4/3$$

$$P_d = 5/3$$

Footed NAND3:

$$\begin{aligned} g_d &= \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}} \\ &= \frac{W_n}{3\left(\frac{4}{W_n}\right)^{-1}} \\ &= \frac{4}{3} \\ P_d &= \left(\frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n) \cdot C \\ &= \left(\frac{1}{4} + \frac{1}{4} + \frac{1}{4} + \frac{1}{4}\right) R \cdot (1+4)C \\ &= 5RC \\ &= \frac{5}{3}\tau \end{aligned}$$

2007


5/23

Dynamiske NOR3:



$$g_d = 1/3$$

$$P_d = 4/3$$

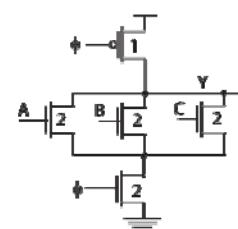

$$g_d = 2/3$$

$$P_d = 7/3$$

Ikke-footed NOR3:

$$\begin{aligned} g_d &= \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n}\right)^{-1}} \\ &= \frac{W_n}{3\left(\frac{1}{W_n}\right)^{-1}} \\ &= \frac{1}{3} \end{aligned}$$

$$\begin{aligned} P_d &= \left(\frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n + W_n + W_n) \cdot C \\ &= \left(\frac{1}{2} + \frac{1}{2}\right) R \cdot (1+1+1+1)C \\ &= 4RC \\ &= \frac{4}{3}\tau \end{aligned}$$

Footed NOR3:


$$\begin{aligned} g_d &= \frac{W_n}{\left(1 + \frac{\mu_n}{\mu_p}\right) \cdot \left(\frac{1}{W_n} + \frac{1}{W_n}\right)^{-1}} \\ &= \frac{W_n}{3\left(\frac{2}{W_n}\right)^{-1}} \\ &= \frac{2}{3} \\ P_d &= \left(\frac{1}{W_n} + \frac{1}{W_n}\right) \cdot R \cdot (W_p + W_n + W_n + W_n) \cdot C \\ &= \left(\frac{1}{2} + \frac{1}{2}\right) R \cdot (1+2+2+2)C \\ &= 7RC \\ &= \frac{7}{3}\tau \end{aligned}$$

2007

6/23



Domino logikk

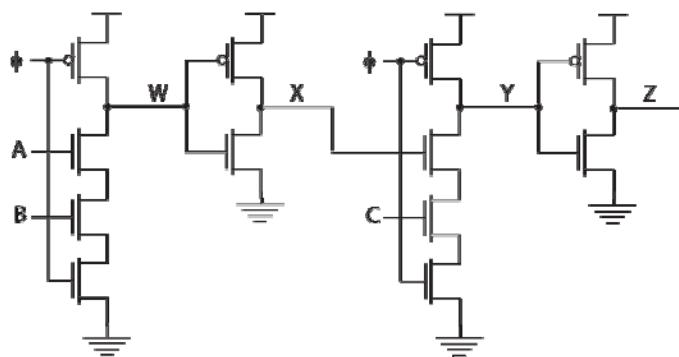


2007

7/23

INF3400/4400 våren 2007 Dynamisk CMOS





Domino multiplexer:

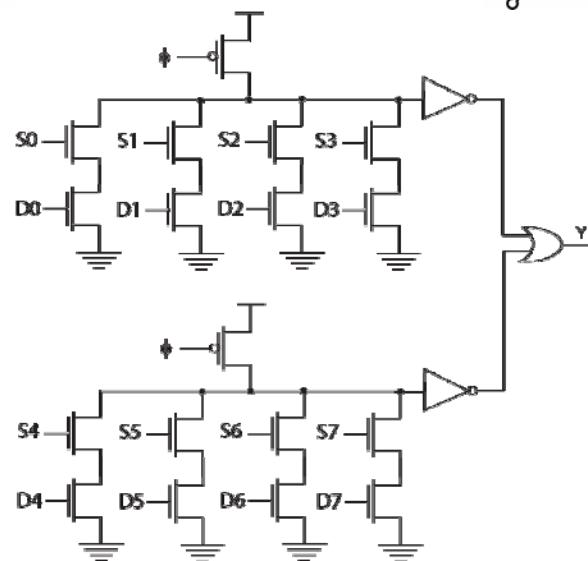

2007


8/23

INF3400/4400 våren 2007 Dynamisk CMOS

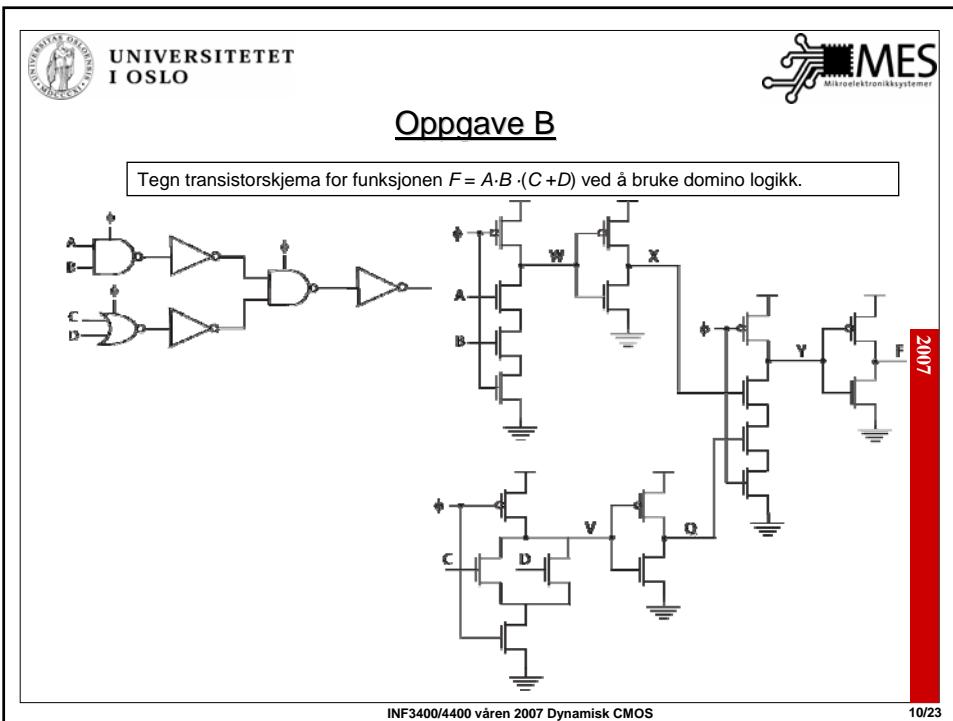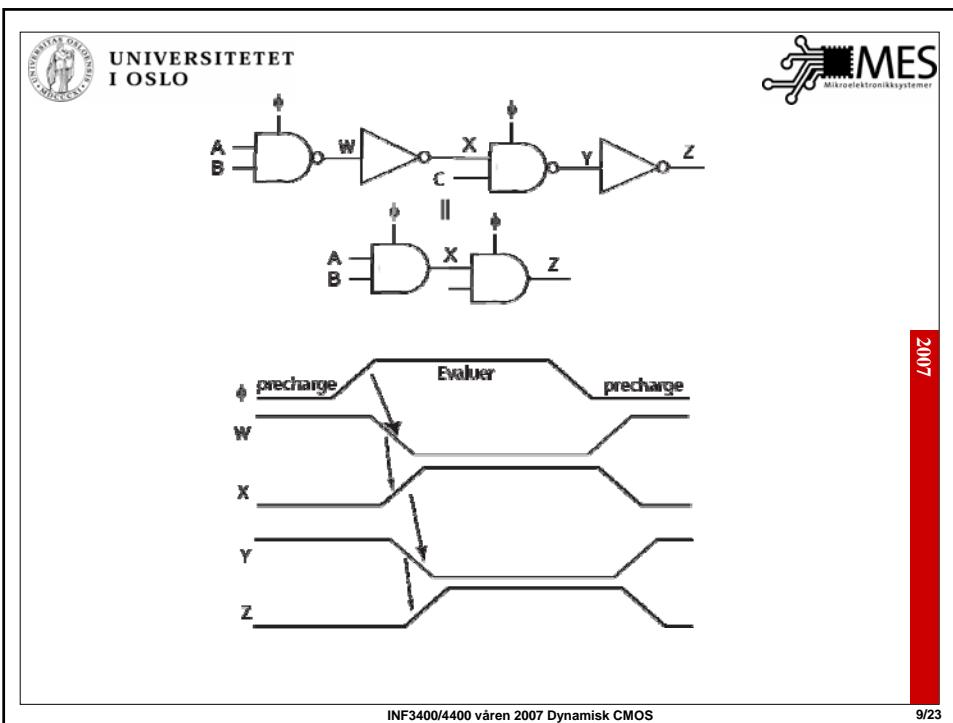



Dual-rail domino logikk

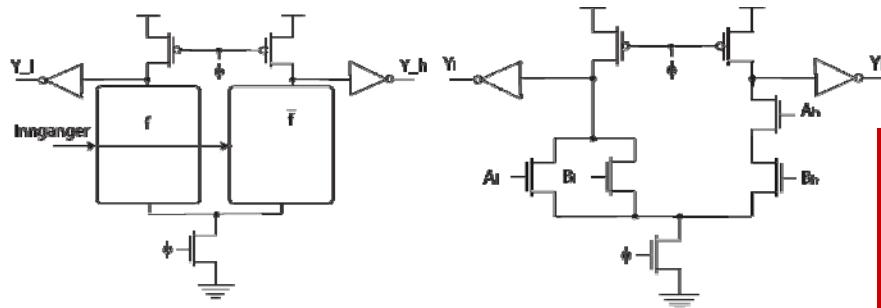

2007


INF3400/4400 våren 2007 Dynamisk CMOS

11/23



Oppgave 6.28

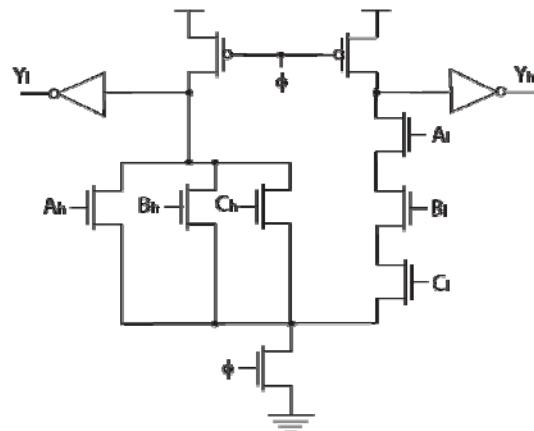
Tegn transistorskjema for en 3inngangs dual-rail domino OR/NOR port.



2007

INF3400/4400 våren 2007 Dynamisk CMOS

12/23

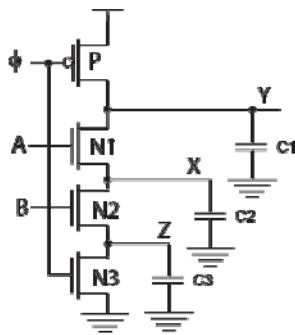
Ladningsdeling



Endring pga. ladningsdeling:

$$\Delta V = \left(1 - \frac{C_1}{C_1 + C_2}\right) \cdot V_{DD}$$

$$V_Y = V_{DD} - \Delta V$$

$$V_X \approx V_Y$$

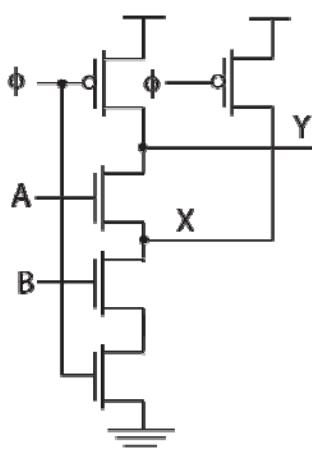Precharge av interne nodert

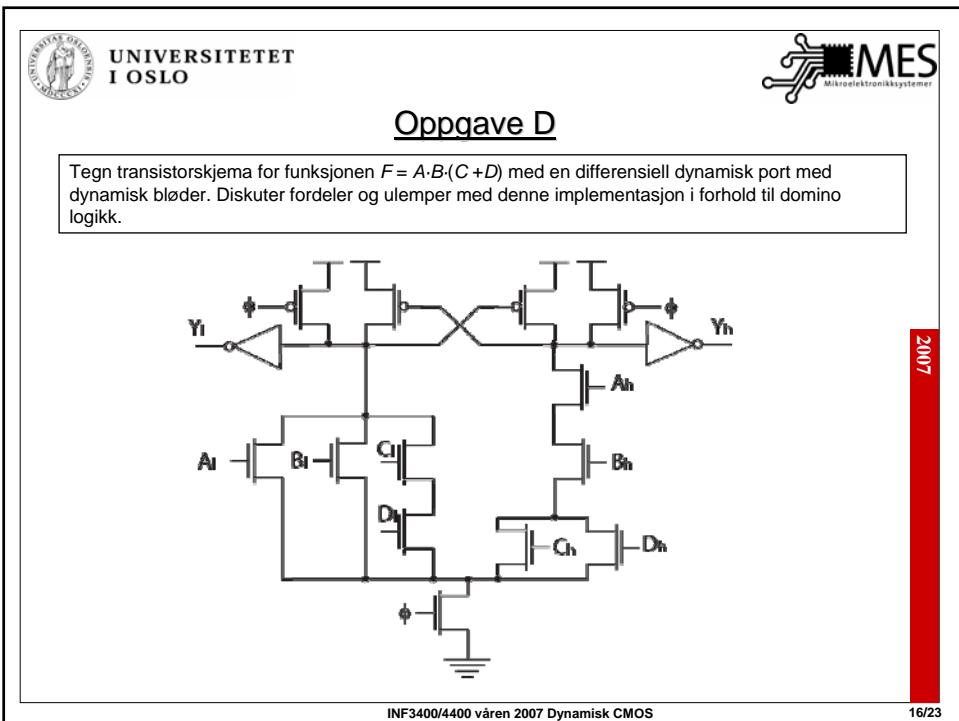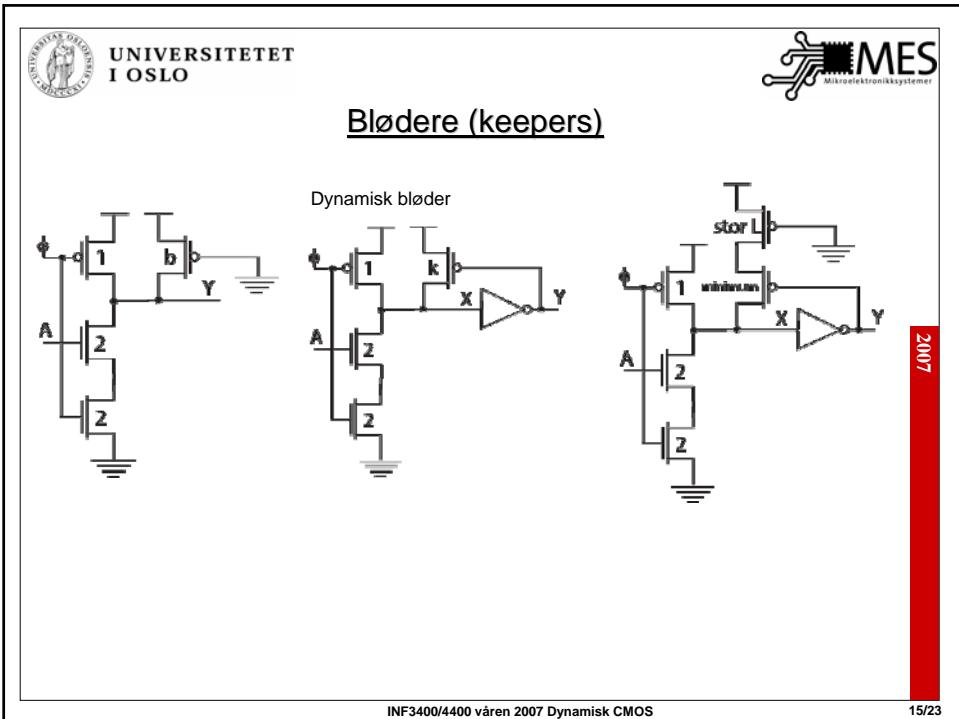



Logisk effekt i dynamiske kjeder


Ikke-footed:

$$G_u = \frac{1}{3} \cdot \frac{5}{6}$$

$$= \frac{5}{18}$$

$$G_d = \frac{2}{3} \cdot \frac{5}{3}$$

$$= \frac{10}{9}$$

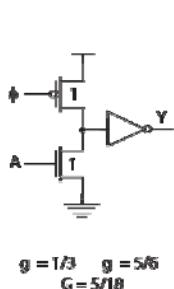


Footed:

$$G_u = \frac{2}{3} \cdot \frac{5}{6}$$

$$= \frac{5}{9}$$

$$G_d = \frac{4}{3} \cdot \frac{5}{3}$$


$$= \frac{20}{9}$$

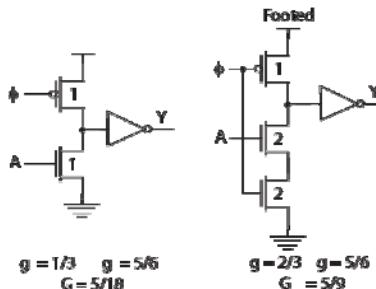

2007



Eksempel:

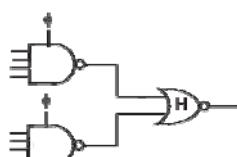

$$G_u = \frac{5}{3} \cdot \frac{3}{2}$$

$$= \frac{5}{2}$$

$$P_u = (5C + C) \cdot R + \left(4C + 2 \cdot \frac{1}{2}C\right) \cdot R$$

$$= 11RC$$

$$= \frac{11}{3}\tau$$

$$N = 2$$

$$f' = F^{\frac{1}{2}}$$

$$= (G \cdot 1 \cdot H)^{\frac{1}{2}}$$

$$= \sqrt{\frac{5H}{2}}$$

Tidsforsinkelse i kjeden:


$$D = NF^{\frac{1}{N}} + P_u$$

$$= 2\sqrt{\frac{5H}{2}} + \frac{11}{3}$$

2007



Eksempel:

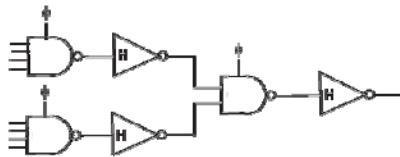

$$N = 4$$

$$f' = F^{\frac{1}{4}}$$

$$= (G \cdot 1 \cdot H)^{\frac{1}{4}}$$

$$= \left(\frac{125H}{108} \right)^{\frac{1}{4}}$$

2007

$$G_u = \frac{5}{3} \cdot \frac{5}{6} \cdot 1 \cdot \frac{5}{6}$$
$$= \frac{125}{108}$$

$$P_u = (5C + C) \cdot R + \left(2 + \frac{1}{2} \right) C \cdot R + (3C + C) \cdot R + \left(2 + \frac{1}{2} \right) C \cdot R$$
$$= 15RC$$
$$= 5\tau$$


Tidsforsinkelse i kjeden:

$$D = NF^{\frac{1}{N}} + P_u$$

$$= 4 \cdot \left(\frac{125H}{108} \right)^{\frac{1}{4}} + 5$$




2007

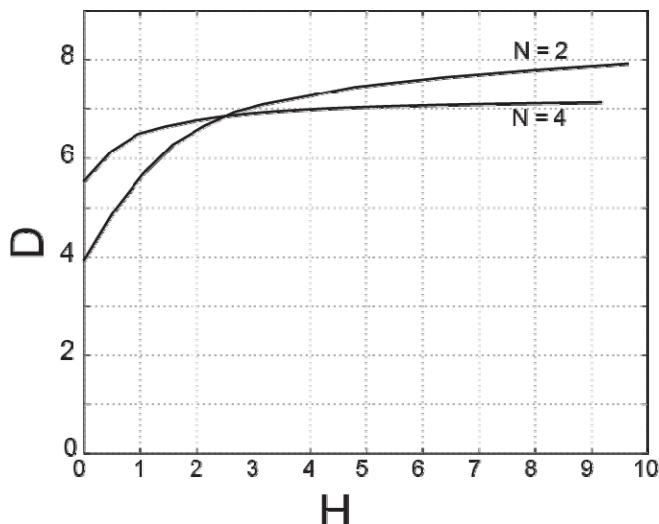



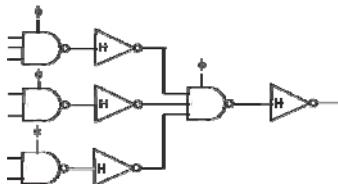Finn tidsforsinkelse i den dynamiske kjeden som er vist i Figuren.



$$\begin{aligned} G_u &= \frac{4}{3} \cdot \frac{5}{6} \cdot \frac{4}{3} \cdot \frac{5}{6} \\ &= \frac{100}{81} \\ P_u &= 5RC + \left(2 + \frac{1}{2}\right)C \cdot R + 5RC + \left(2 + \frac{1}{2}\right)C \cdot R \\ &= 15RC \\ &= 5\tau \end{aligned}$$

$$N = 4$$

$$\begin{aligned} f' &= F^{\frac{1}{4}} \\ &= (G \cdot 1 \cdot H)^{\frac{1}{4}} \\ &= \left(\frac{100H}{81}\right)^{\frac{1}{4}} \end{aligned}$$

Tidsforsinkelse i kjeden:

$$\begin{aligned} D &= NF^{\frac{1}{N}} + P_u \\ &= 4 \cdot \left(\frac{100H}{81}\right)^{\frac{1}{4}} + 5 \end{aligned}$$


2007

21/23

Eksamensoppgave 2005

Hva blir parasittisk tidsforsinkelse for nedtrekket for 3inngangsdynamisk footed NAND porten?

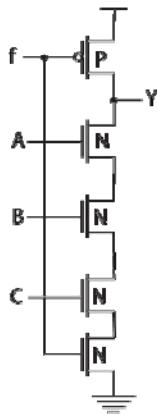Velger N=4 som gir effektiv motstand i nedtrekket lik R:




$$\begin{aligned} P_d &= R(1+4)C \\ &= 5RC \\ &= \frac{5}{3}\tau \end{aligned}$$

2007

22/23



NP (og Zipper domino)

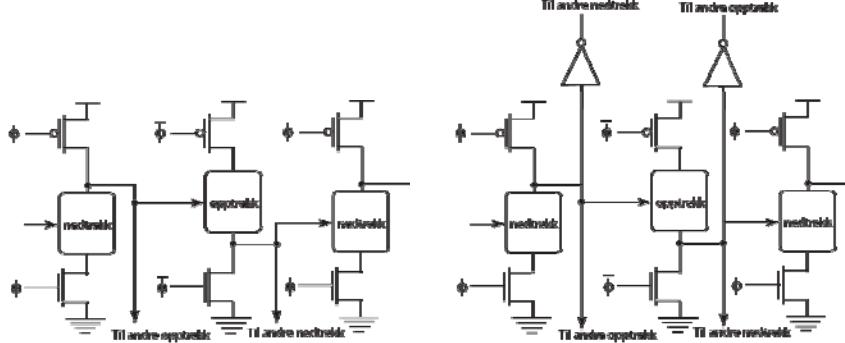

2007