


ifi

Sample and Hold Circuits
(chapter 8)


Tuesday 2nd of February, 2010

Snorre Aunet, sa@ifi.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

 UNIVERSITETET
I OSLO

Last time – Tuesday 26th of January

 - Practical issues
- Learning goals
- Design project, tools and methods
- Syllabus
- Very brief introduction to various circuit building blocks (sample-and-holds, bandgap references, switched capacitor circuits, nyquist- and oversampling data converters, phase-locked loops)




Sample and Holds (S/H) – What are the purposes?

- Mainly used in Analog-to-Digital Converters (ADC)
 - Samples analog input signal and holds value between clock cycles
 - Stable input value is required in many ADC-topologies
 - Reduces ADC-error caused by internal ADC delay variations
- Sometimes referred to as Track and Hold (T/H)
- Important parameters for S/H's
 - Hold step: Voltage error during S/H-transition
 - Signal isolation in hold mode
 - Input signal tracking speed in sample mode
 - Droop rate in hold mode: Small change in output voltage
 - Aperture jitter: Sampling time uncertainty



 
Overview of signal spectra – conceptual and physical realizations



- An **anti-aliasing** filter (not shown) is assumed to band limit the continuous time signal, $x_c(t)$.
- **DSP** ("discrete-time signal processing") may be accomplished using fully digital processing or discrete-time analog circuits (ex.: SC-circ.)





Basic S/H-topology

 

- Hold step:
 - Switch charge injection causes signal dependent hold step
- Aperture jitter:
 - Sampling-time variations causes signal dependent errors



Basic S/H-topology

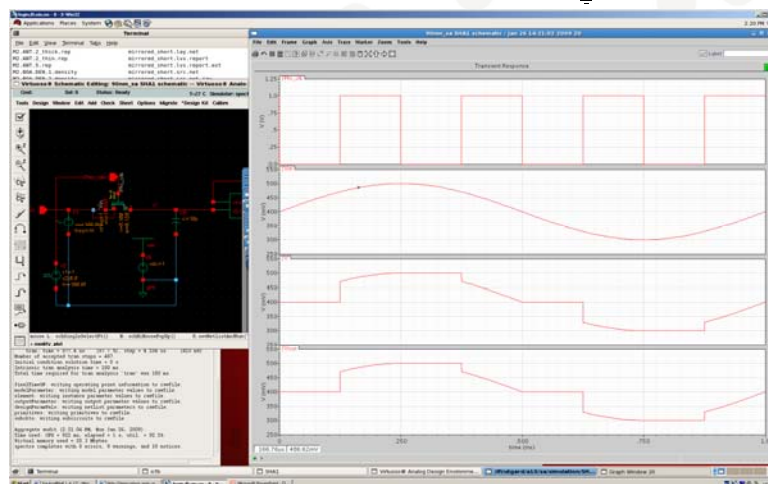 



Charge injection due to channel capacitance

When ϕ_{clk} goes low, the channel charge of Q_1 is equally distributed between source and drain, leaving 50% of the charge across C_{hld} :

$$\Delta Q_{C_{hld}} = \frac{Q_{CH}}{2} = \frac{C_{ox}WL V_{eff-1}}{2}$$

$$V_{eff-1} = V_{GS1} - V_{tn} = V_{DD} - V_{tn} - V_{in}$$
  
$$\Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{ox}WL(V_{DD} - V_{tn} - V_{in})}{2C_{hld}}$$




- $\Delta V'$ is linearly related to V_{in} , resulting in a **gain error** for the S/H. There is also a linear relationship to V_{tn} , which is nonlinearly related to V_{in} (through V_{sb}) resulting in **distortion** for the overall S/H.

Charge injection due to the gate overlap capacitance:


-
 
$$\Delta V' \cong -\frac{C_{ox}WL_{ov}(V_{DD} - V_{SS})}{C_{hld}}$$



- (See eq. 7.8) This component is usually **smaller** than that due to the channel charge, and appears as an **offset**, since it's signal independent. Thus it **may be removed** in most systems.
- The clock signal should be relatively noise free, as the power-supply rejection of this S/H might be poor. (if for example clock signal comes from an inverter with common V_{dd} and V_{ss})

Hold step reduction

 


CMOS transmission gate

Dummy switch


- **Transmission gate** reduces charge injection since the charge carriers in the NMOS and PMOS have inverted polarity -> The negative charge from the NMOS cancels the positive charge from the PMOS
 - PMOS and NMOS are however hard to match in size, reducing the benefit.
- A NMOS **dummy switch** (S and D short-circuited) of half channel area clocked on inverted clock may be used to absorb charge
 - Hold step reduced by approximately 80%
 - The dummy switch clock must be slightly delayed to ensure that no charge leaks through Q1 while it is still open

Aperture jitter

 

- If the input voltage is lower than the capacitor voltage, V_{in} is the source of the transistor used as a switch
- V_{gs} is then depending on V_{in} . For high values of V_{in} , the switch turns off too fast while for low values of V_{in} it turns off too late causing **distortion**

S/H (fig. 8.7)

 


- **Advantages:**

- High input impedance
- Buffer offset voltage is divided by the gain of the input opamp, due to negative feedback. Simple voltage follower may be used at the output.


- **Disadvantages:**

- Errors due to finite clock rise- and fall-times (PMOS and NMOS are not switched off at the same time)
- Signal dependent charge injection -> Distortion
- Feedback loop and need for stability limit maximum speed
- In Hold mode, the first opamp output goes to either rail. Must slew back

Sample-and-Hold from fig. 8.7

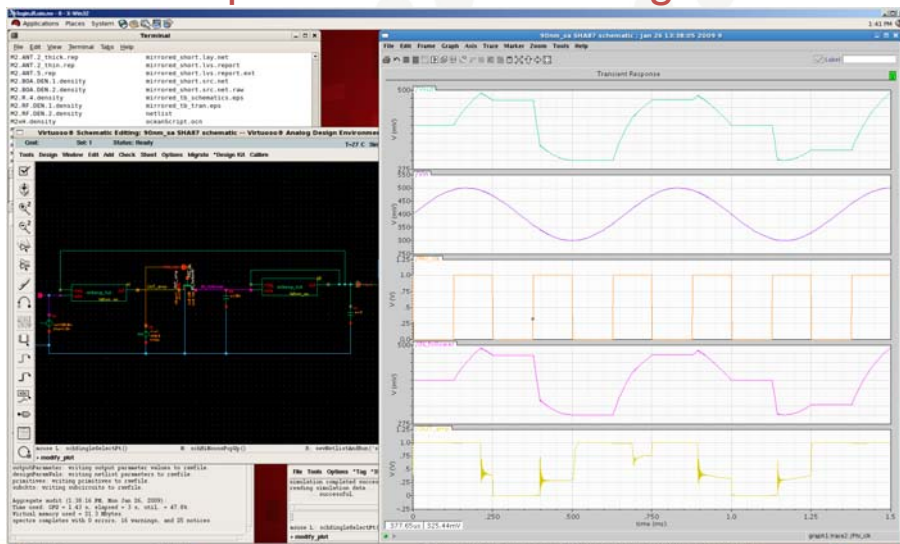


Increased speed (fig. 8.8)

 


- During hold mode the opamp output is tracking the input
 - Leads to increased speed
- Disadvantages in common with the previous circuit

SAMPLE (= Track) / HOLD modes (fig 8.8)

 


Sample-and-Hold from fig. 8.8

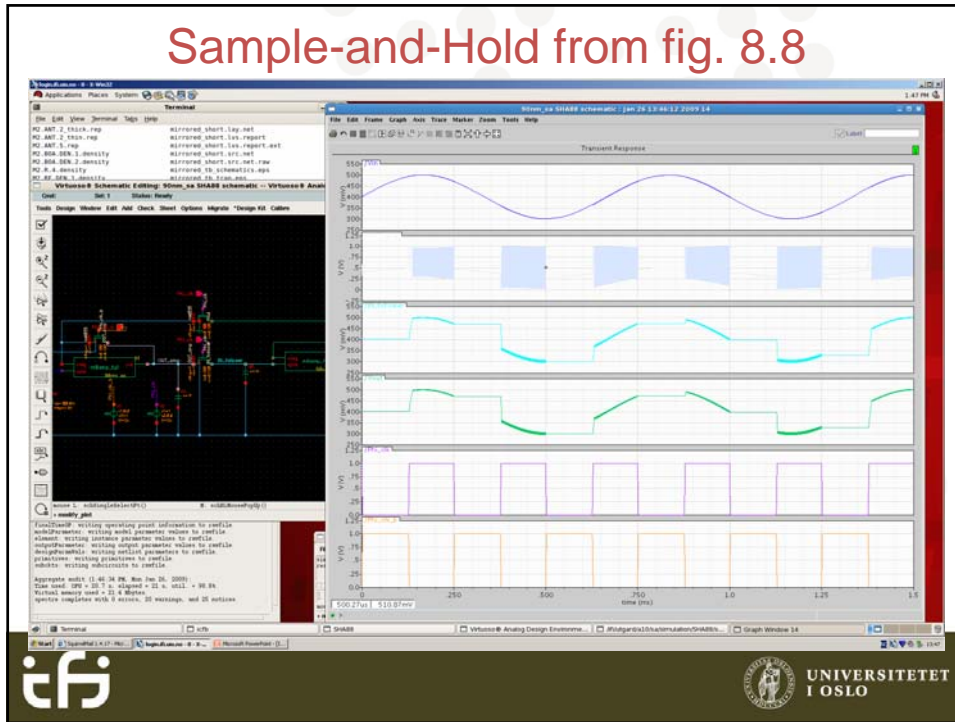


Another S/H: Fig 8.9 (Improved version of the S/H from fig 8.8)

Fig. 8.9:

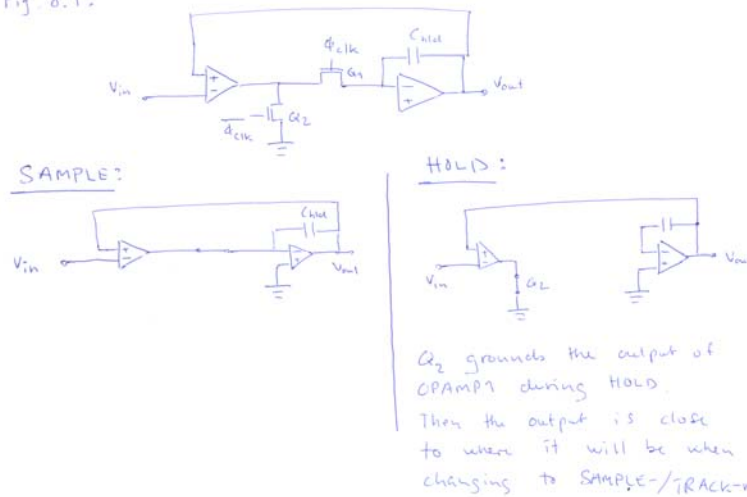


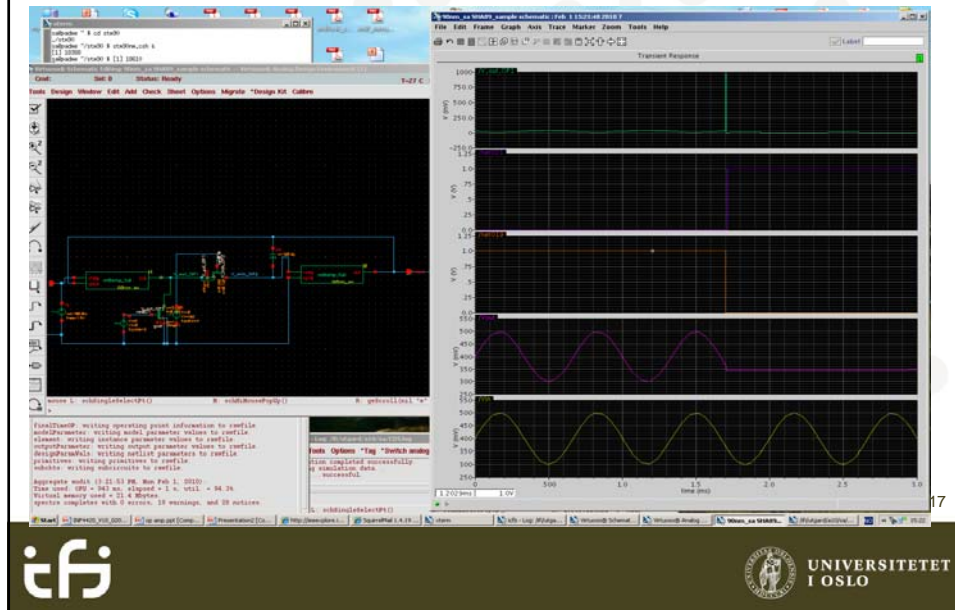3. februar 2010

Sample (track) mode to Hold mode (the S/H in fig. 8.9) signals, from top: $V_{\text{outopamp1}}$, $V_{(Q2)}$, $V_{(Q1)}$, V_{out} , V_{in}




 S/H with hold step independent of input signal (fig. 8-9)



- + : Both sides of Q_1 are nearly signal independent, so that the charge injection is (nearly) signal independent, provided a sufficient gain in the 2nd Opamp. The charge injection on C_{hld} causes the **output** of the 2nd Opamp to have a positive **hold step**, which is just a dc offset, with **no signal distortion**, and **signal independent**.
- + : Sampling time will not change due to finite slopes of the sampling clock \rightarrow less aperture jitter / aperture uncertainty \rightarrow sample value closer to the ideal one.

 S/H with hold step independent of input signal (fig. 8-9)



- + : Q_2 ground the output of OPAMP1 in hold mode, meaning that it's close to (and quickly getting to) the voltage it should have in S. mode, which improves speed.
- Preventing instability **reduces speed**
 - Worsened due to two opamps in the feedback loop
- More relevant information: K. R. Stafford, P. R. Gray, R. A. Blanchard: "A Complete Monolithic Sample/Hold Amplifier", IEEE Journal of Solid-State Circuits, Dec. 1974. (available from <http://ieeexplore.ieee.org> , when on UiO IP-address)



"New(er) architecture"

FIGURE 9. Closed-Loop Architecture with Integrator Output

 


FIGURE 10. Current Multiplexed Architecture

A new architecture which combines the speed of the open-loop configuration and the accuracy of the closed-loop configuration is the current-multiplexed architecture shown in Figure 10. The LF6197, National's High Performance VIP™ Sample-and-Hold Amplifier used this architecture. This architecture provides for a cancellation of charge injection, allowing one to use a small hold capacitor to get high speeds without the disadvantage of a large hold step.

Specifications and Architectures of Sample-and-Hold Amplifiers

National Semiconductor
Application Note 775
July 1992



Continuous efforts to improve S/H circuits..

A Sample/Hold Circuit for 80MSPS 14-bit A/D Converter

Xiao Kunguang^{1,2}, Wang Yuxing^{1,2}, Xu Minyuan^{1,2}, and Zhu Chan^{1,2}

454

IEEE JOURNAL OF SELECTED TOPICS IN SIGNAL PROCESSING, VOL. 3, NO. 3, JUNE 2009

Digital Calibration of a Nonlinear S/H

Patrick Satarzadeh, *Student Member, IEEE*, Bernard C. Levy, *Fellow, IEEE*, and Paul J. Hurst, *Fellow, IEEE*

A High-Speed Highly-Linear CMOS S/H Circuit

Mahmoud Sadollahy^{1,2}, Khayrollah Hadidi¹

¹Acad Islamic University, Safian Branch

²Microelectronic Research Laboratory, Urmia University
st_madollahy@matl.urmia.ac.ir

978-1-4244-1692-9/08/\$25.00 ©2008 IEEE

 


Figure 1. Sample and hold architectures.

 



Figure 2. Proposed open loop S/H architecture.

- IEEEExplore may provide State-of-the-Art solutions

3. februar 2010

21

Reduced DC-error (fig. 8-10)

 

- Improved version of previous circuit (in fig. 8.9)
- By placing a copy of Q1 and Chld in parallel between ground and the positive input of the second opamp, the voltage change due to charge injection will be equal on both inputs. Error is cancelled by [opamp CMRR](#).
The **common-mode rejection ratio** (CMRR) of a differential amplifier (or other device) measures the tendency of the device to reject input [signals](#) common to both input leads.

Additional Background Litterature, S/H circuits


- A. S. Sedra, K. C. Smith: "Microelectronic Circuits", Saunders College Publishing, 1991.
- R. Gregorian, G. C. Temes: "Analog MOS Integrated Circuits for signal processing", Wiley, 1986.
- K. R. Stafford, P. R. Gray, R. A. Blanchard: "A Complete Monolithic Sample/Hold Amplifier", IEEE Journal of Solid-State Circuits, Dec. 1974.
- F. F. Kuo: "Network Analysis and Synthesis", Wiley, 1966.
- S. Soma: "Grunnbok i elektronikk", Universitetsforlaget, 1979.
- National Semiconductor: "Specifications and Architectures of Sample-and-Hold Architectures", App. Note 775, July 1992.
- S. Aunet: "BiCMOS Sample-and-Hold for Satelittkommunikasjon", hovedfagsoppgave, UiO, 1993.

3. februar 2010

23



S/H stuff..

 

Unfortunately, V' will have a negative going hold step, caused by channel charge from transistor Q_1 .
 If Q_{ch} is turned off fast, the channel charge, Q_{ch} , will flow equally into both junctions. The charge flowing to V' is then
 given by: $\Delta Q_{ch} = \frac{Q_{ch}}{2}$
 $(C_{ox} W L) \Delta V = \frac{Q_{ch}}{2}$
 $\Delta V = \frac{Q_{ch}}{2 C_{ox} W L}$
 The change in V' is:
 $\Delta V = \frac{Q_{ch}}{2 C_{ox} W L} = \frac{(C_{ox} W L) (V_{in} - V_{th})}{2 C_{ox} W L} = \frac{V_{in} - V_{th}}{2}$
 ΔV is known as $V_{in} - V_{th}$ GAIN ERROR

$$\Delta V' = \frac{C_{ox} W L (V_{in} - V_{th} - V_{in})}{2 C_{ox}}$$

$\Delta V'$ is also linearly related to V_{in} , which is unfortunately related to the input signal, V_{in} , due to variations in the source-substrate voltage (turning the substrate is tied to one of the voltage rails)

∴ This nonlinear relationship with V_{in} results in distortion for the overall sample-and-hold circuit.

Additional charge in V' due to the gate overlap capacitance.

Using a derivation similar to that used to find (9.7), we have:
 $\Delta V' = \frac{C_{ox} W L (V_{in} - V_{th})}{C_{ox}}$ (9.7.10)

This component is usually smaller than the one due to the channel charge, and speed independent. This means it can be removed.



3. februar 2010

24

