


ifj

PLLs, report writing

Tuesday 13th of April, 2009, 9:15 – 11:00


Snorre Aunet, sa@ifi.uio.no
 Nanoelectronics Group, Dept. of Informatics
 Office 3432

 UNIVERSITETET
I OSLO

Last time – and today, Tuesday 13th of April:

March the 23rd:

 - 14.2 Oversampling with noise shaping
- 14.3 System Architectures
- 14.4 Digital Decimation Filters
- 14.5 Higher-Order Modulators
- (14.6 Bandpass Oversampling Converters)
- 14.7 Practical Considerations
- 14.8 Multi-bit oversampling converters
- 2nd order sigma delta design example
- 16.1 Basic Phase Locked Loop Architecture



Today:

- 16.1 Linearized small-signal analysis of general PLLs
- 16.2 PLLs with charge-pump phase comparators
- 16.3 Voltage controlled oscillators
- 16.4 Computer Simulations of PLLs
- About writing the report

PLL Basic Architecture

- In general, output may be V_{ctrl} or V_{osc}

University of Toronto
 3 of 26
© D. Jidari, E. Maria, 1997

PLL linear model applying to almost every PLL

- Combining above 2 equations ...

$$\frac{V_{ctrl}(s)}{\phi_{in}(s)} = \frac{s K_{pd} K_{lp} H_{lp}(s)}{s + K_{pd} K_{lp} K_{osc} H_{lp}(s)}$$
- This is a highpass response from input phase to control voltage
- Can also be written as

$$\frac{\phi_{osc}(s)}{\phi_{in}(s)} = \frac{K_{pd} K_{lp} K_{osc} H_{lp}(s)}{s + K_{pd} K_{lp} K_{osc} H_{lp}(s)}$$
- This is a lowpass response from input phase to output phase
- Differences between PLLs are determined only by what is used for the LP-filter ($H_{lp}(s)$), the Phase Detector (K_{pd}) or the oscillator (K_{osc}).

$$V_{ctrl}(s) = K_{pd} K_{lp} H_{lp}(s) [\phi_{in}(s) - \phi_{osc}(s)]$$

$$\phi_{osc}(s) = \frac{K_{osc} V_{ctrl}(s)}{s}$$

$$H_{lp}(s) = \frac{1 + s\tau_z}{1 + s\tau_p}$$

University of Toronto
 4

More on the 2nd order PLL model

2nd order transfer functions are often written in the form:

$$H(s) = \frac{N(s)}{D(s)}$$

$$D(s) = 1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}$$

ω_0 : resonant frequency

Transient time for the complete loop:

$$\tau_{pll} \approx \frac{1}{\omega_0}$$

12. Q : Q-factor, damping factor

Good settling: $Q = 0.5$

max. flat group delay: $Q = \frac{1}{\sqrt{3}} = 0.577$

max. flat amplitude resp.: $Q = \frac{1}{\sqrt{2}} = 0.707$

$$\omega_0 = \frac{K_{pll}}{\sqrt{\tau_p}} \quad (16.32)$$

$$Q = \frac{\sqrt{\tau_p}}{\frac{1}{K_{pll}} \tau_z K_{pll}}$$

$$K_{pll} = \sqrt{K_{pd} \cdot K_{lp} \cdot K_{oc}}$$

Usually, when $\omega_0 \ll \omega_{fr}$:

$$Q \approx \frac{1}{\omega_0 \tau_z} = \frac{\sqrt{\tau_p}}{\tau_z K_{pll}} \quad (16.35)$$

When $Q = 0.5$:

$$\tau_z = \frac{2\sqrt{\tau_p}}{K_{pll}} = \frac{2}{\omega_0}$$

5

TET

Capture range, lock range, false lock

- The maximum difference between the input signal's frequency and the oscillator's free-running frequency where lock can eventually be attained is defined as the **capture range**
- Once lock is attained, as long as the input signal's frequency changes only slowly it will remain in lock over a range that is much larger than the capture range
- When a multiplier is used for the phase detector the loop may lock to harmonics (multiple of the frequency) of the input signal. This is called a **false lock**.

Exclusive-OR Phase comparators

V_{in}	V_{osc}	V_{pd}
0	0	0
0	1	1
1	0	1
1	1	0

put given by $V_{pd} = V_{in} \oplus V_{osc}$, where the amplitudes of the signals are determined by the logic levels. Some typical waveforms are shown in Fig. 16.6. It is seen that


 


Fig. 16.6 Typical waveforms when an exclusive-OR gate is used as a phase comparator

- When the waveforms are **90 degrees** out of phase the output is a waveform at **twice the frequency** of the input signal and has a **50 percent duty cycle**.
- If all waveforms are symmetric about 0 volts the average value extracted by the low-pass filter would be zero.

EXOR phase comp

 

- When the waveforms become **more out of phase**, the average value of the output signal is **positive**; whereas when they become **more in phase**, the **average value** of the output signal is **negative**

CHARGE-PUMP COMPARATOR

- no false lock, attains lock quickly
- V_{in} and V_{osc} are exactly in phase when the system is in lock.
- injects, leaves alone, or subtracts charge on the capacitor in the LP-filter, depending on P_u and P_d .
- S_1 closed: I_{ch} increases the control voltage into the VCO
- S_2 closed: I_{ch} flows out of the LP-filter, decreasing the control voltage.
- S_1 and S_2 open: steady state
- P_u and P_d are digital signals
- IF V_{in} goes to 1 before V_{osc} , then P_u will be 1 during the time that the signals are different. \Rightarrow injecting charge ELSE if V_{osc} goes to 1 before V_{in} , P_d will be 1 during the time that the inputs are

different $\Rightarrow S_2$ will be closed, removing charge from the loop-filter and decreasing the VCO frequency.

OBS: Notice that P_u only goes high at the leading edges and is insensitive to the falling edges.

Fig. 16.1 The basic architecture of a phase-locked loop.

Small-Signal Model of the Charge-Pump PLL

In average the current from the CP is: $I_{avg} = \frac{\Delta\phi_{in}}{2\pi} I_{ch}$

The transfer function from the loop filter is (C2 ignored):

$$H_{lp}(s) = \frac{V_{lp}(s)}{I_{avg}(s)} = R + \frac{1}{sC_1} = \frac{1 + sRC_1}{sC_1}$$

$$\frac{\phi_{osc}(s)}{\phi_{in}(s)} = \frac{(1 + sRC_1)}{1 + sRC_1 + \frac{s^2 C_1}{K_{pd} K_{osc}}}$$

$$\omega_0 = \frac{1}{\tau_{pll}} = \sqrt{\frac{I_{ch} K_{osc}}{2\pi C_1}}$$

$$Q = \frac{1}{RC_1 \omega_0} = \frac{1}{R} \sqrt{\frac{2\pi}{C_1 I_{ch} K_{osc}}}$$

Ex. 16.4

Ex. 16.4 $K_{osc} = 2\pi \times 50 \text{ Mrad/V}$
 $I_{ch} = 10 \mu\text{A}$, $\omega_{tr} = 50 \text{ MHz}$
 and the loop has a time constant of 100 cycles, or $2 \mu\text{s}$.
 Design the components of the LP-filter in fig. 16.7

fig. 16.7

Let $C_2 = \frac{C_2}{10} = 200 \text{ pF}$
 Let $Q = 0.4$
 From 16.61:
 $Q = \frac{1}{R C_1 \omega_0} = \frac{1}{R} \sqrt{\frac{2\pi}{C_1 I_{ch} K_{osc}}}$
 $R = \frac{1}{Q} \sqrt{\frac{2\pi}{2 \text{ nF} \cdot 10 \mu\text{A} \cdot 2\pi \times 50 \text{ Mrad/s}}}$
 $= 2.5 \text{ k}\Omega$

$\omega_0 = \frac{1}{2 \mu\text{s}} = 500 \text{ k rad/s}$


$\omega_0 = \sqrt{\frac{K_{pd} \cdot K_{osc}}{C_1}} \wedge K_{pd} = \frac{I_{ch}}{2\pi} \text{ (16.61, 16.56)}$

$\omega_0^2 = \frac{K_{pd} \cdot K_{osc}}{C_1} \Leftrightarrow C_1 = \frac{K_{pd} \cdot K_{osc}}{\omega_0^2}$

$C_1 = \frac{I_{ch}}{2\pi} \cdot \frac{K_{osc}}{\omega_0^2}$
 $= \frac{10 \mu\text{A}}{2\pi} \cdot \frac{2\pi \times 50 \text{ Mrad/s}}{(500 \text{ k rad/s})^2} = 2 \text{ nF}$


$C_1 = 10 \text{ nF}$
 $C_2 = 200 \text{ pF}$

Phase Frequency Detector (PFD)

 

- Most commonly used sequential phase detector is the Phase Frequency Detector (PFD).
- This circuit handles phase differences up to 2π .


Phase Frequency Detector (PFD)

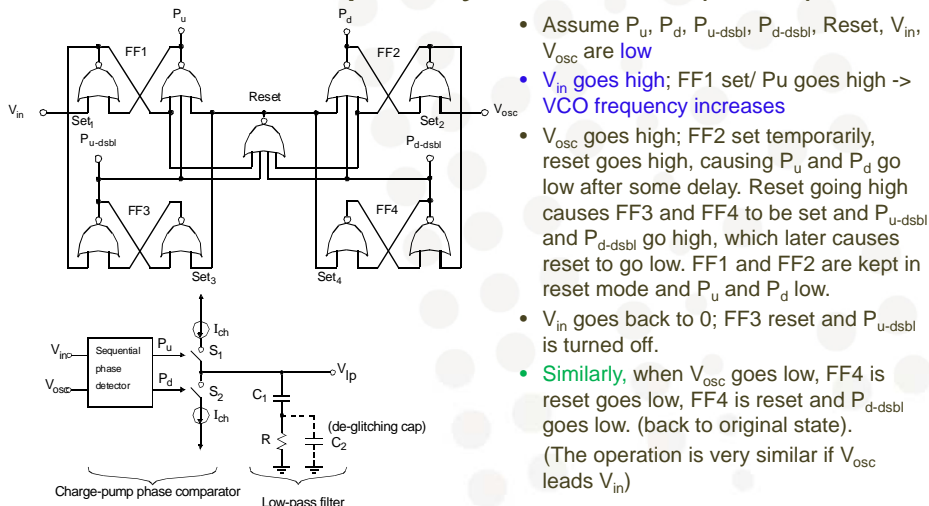


- Assume P_u , P_d , P_{u-dsbl} , P_{d-dsbl} , Reset, V_{in} , V_{osc} are low
- V_{in} goes high; FF1 set/ P_u goes high -> VCO frequency increases
- V_{osc} goes high; FF2 set temporarily, reset goes high, causing P_u and P_d go low after some delay. Reset going high causes FF3 and FF4 to be set and P_{u-dsbl} and P_{d-dsbl} go high, which later causes reset to go low. FF1 and FF2 are kept in reset mode and P_u and P_d low.
- V_{in} goes back to 0; FF3 reset and P_{u-dsbl} is turned off.
- Similarly, when V_{osc} goes low, FF4 is reset goes low, FF4 is reset and P_{d-dsbl} goes low. (back to original state). (The operation is very similar if V_{osc} leads V_{in})



 
PFD waveforms – when V_{in} has a much higher frequency than V_{osc}



- Whenever a positive going edge of V_{in} occurs, P_u goes high causing the VCO frequency to increase, and stays high until both V_{in} and V_{osc} go to 1. Then reset goes high, setting both P_{u-dsbl} and P_{d-dsbl} , and causing P_u and P_d to go low. The next time V_{in} goes to 0, FF1 is reset, which resets FF3, turning P_{u-dsbl} off.
- Most of the time (here) P_u is high, causing V_{osc} to quickly increase in frequency until lock is achieved.
- No false lock
- Only suitable for digital (non-sine) inputs

 


Voltage controlled oscillators (VCO)

 

- Sinusoidal output oscillators usually realized some frequency selective or tuned circuit in feedback configuration, while square-wave output oscillators are usually realized using a nonlinear feedback config.
- The tuned oscillators offers better frequency stability, but limited tuning range.



Ring oscillators

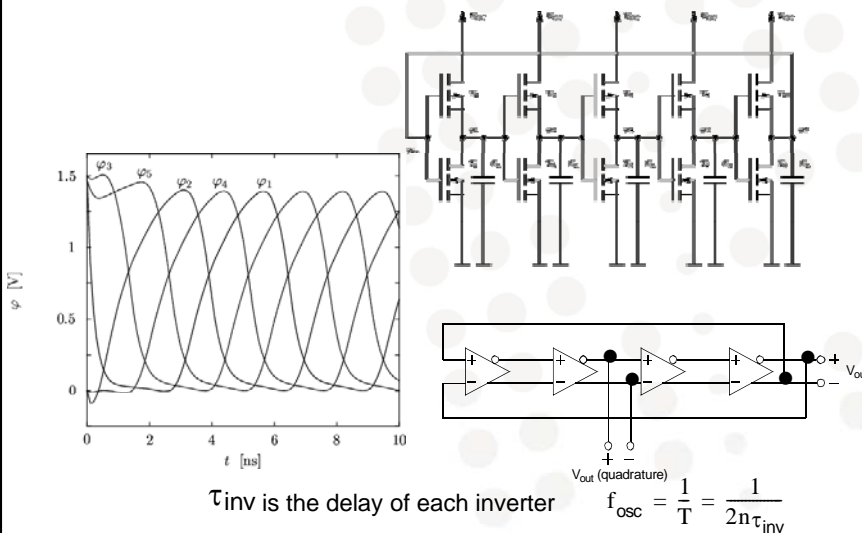

0.2 V subthreshold VCO

 


Figure 3. RVCO transfer function for a 5 stage RVCO simulated in Cadence

 


Figure 4. Sensitivity of the RVCO illustrates a nonlinearity of 0.5 %

Linearity of Bulk-Controlled Inverter Ring VCO in Weak and Strong Inversion

Ulrik Wisnar*, Dag Wisland**, Pietro Andreani*


*Centre for Physical Electronics, OrstedDTU, Technical University of Denmark, DK-2800 Kgs. Lyngby, Denmark

**Microelectronic Systems, Department of Informatics, University of Oslo, N-0316 Oslo, Norway



UNIVERSITETET
I OSLO

Differential inverter

 


- Programmable delay
- Cascode transistors Q3, Q4 to increase output impedance of programmable current sources for better PSRR
- $I_B = K_{bias} V_{ctrl}$ (proportional)
- τ proportional to C_L / g_m , f_{osc} proportional to $\sqrt{V_{ctrl}}$; nonlinear



UNIVERSITETET
I OSLO

Bias circuit

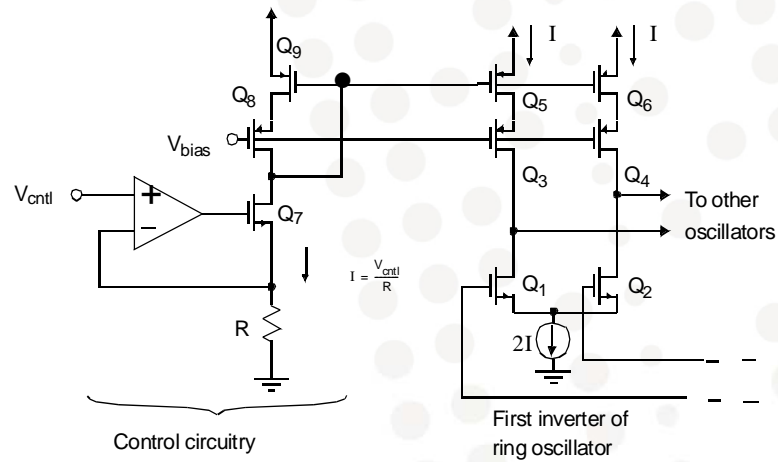



Computer simulations of PLLs

- **Nontrivial** due to often very wide range of time constants present in PLLs.
- **SPICE** simulations **only** may be highly **impractical** and take too long time.
- **Possible approach:**
 - Simulate the **individual components** using **SPICE** over a few periods of the VCO's output waveform before simulating the **complete system** using simplified models where continuous time components are replaced by **approximately equivalent difference-equation models**;
 - Simulink in Matlab (easy, don't need much expertise)
 - or** custom difference equations using for example C. (fast and may be modified for greater accuracy)

Additional litterature

- Ulrik Wismar, Dag T. Wisland, Pietro Andreani: *Linearity of Bulk-Controlled Inverter Ring VCO in weak and strong inversion*, Proceedings of IEEE Norchip Conference, 2005.
- <http://www.eecg.toronto.edu/~johns/nobots/Book/book.html>
- <http://www.iue.tuwien.ac.at/phd/grasser/node83.html> (Ring osc.)

  Remember: Grading is based on the contents of the report



Some pointers

- <http://www.idi.ntnu.no/~lasse/DM/SkriveTips.php>
- **Preface**
- **(Acknowledgement)**
- **1 Introduction**
- **2 Theoretical background**
- **(2.1 Various approaches to Nifty Gadgets)**
- **2.2 Nifty Gadgets my way**
- **3 My implementation of a Nifty Gadget**
- **4 Nifty Gadget results**
- **5 Discussion**



UNIVERSITETET
I OSLO

Nifty Gadget / DAC chapter 3

- **3 My implementation of a Nifty Gadget**
- Can you describe your implementation in detail?
Why did you use this technology?
How does the theory relate to your implementation?
What are your underlying assumptions?
What did you neglect and what simplifications have you made?
What tools and methods did you use?
Why use these tools and methods?



UNIVERSITETET
I OSLO

Nifty Gadget / DAC chapter 4

- **4 Nifty Gadget results**
- Did you actually build it?
 - How can you test it?
 - How did you test it?
 - Why did you test it this way?
 - Are the results satisfactory?
 - Why should you (not) test it more?
 - What compensations had to be made to interpret the results?
 - Why did you succeed/fail?



UNIVERSITETET
I OSLO

Nifty Gadget / DAC chapter 5

- **5 Discussion**
- Are your results satisfactory?
 - Can they be improved?
 - Is there a need for improvement?
 - Are other approaches worth trying out?
 - Will some restriction be lifted?
 - Will you save the world with your Nifty Gadget?



UNIVERSITETET
I OSLO

Guide to writing a thesis

Guide to Writing a Thesis Page 1 of 4

Guide to Writing a Thesis

*Department of Applied Electronics
Last updated 1997-03-12*

Original manuscript written by Øyvind Mattsson

The Design and Implementation of a Nifty Gadget

Tobias Lis Book
April 12, 1992

Abstract
What is all this about?
Why should I read this thesis?
Is it any good?
What's new?

Preface
Have you done anything that doesn't have to do with your research?
Have you published parts of this work before?

Acknowledgement
Who is your advisor?
Did anyone help you?
Who funded this work?
What's the name of your favorite pet?

1 Introduction
What is the use of a Nifty Gadget?
What is the problem?
How can it be solved?
What are the previous approaches?
Why do it this way?
What are your results?
Why is this better?
Is this a new approach?
Why hasn't anyone done it before?
or
Why do you reiterate previous work?
What is your contribution to the field of Nifty Gadgets?

Guide to Writing a Thesis Page 2 of 4

2 Theoretical background
What is the required background knowledge?
Where can I find it?

2.1 Various approaches to Nifty Gadgets
What is the relevant prior work?
Where can I find it?
Why should it be done differently?
Has anyone attempted your approach previously?
Where is that work reported?

2.2 Nifty Gadgets my way
What is the outline of your way?
Have you published it before?

3 My implementation of a Nifty Gadget
Can you describe your implementation in detail?
Why did you use this technology?
How does the theory relate to your implementation?
What are your underlying assumptions?
What did you neglect and what simplifications have you made?
What tools and methods did you use?
Why use these tools and methods?

4 Nifty Gadget results
Did you actually build it?
How was your own it?
How did you test it?
Why did you test it this way?
Are the results satisfactory?
Why should you have tested it more?
What compensations had to be made to interpret the results?
Why did you succeed fail?

5 Discussion
Are your results satisfactory?
Can they be improved?
Is there a need for improvement?
Are other approaches worth trying out?
Will some restriction be lifted?
Will you save the world with your Nifty Gadget?

6 References
What is the background reading list?

Guide to writing a thesis

Guide to Writing a Thesis Page 3 of 4

Where is the related work?
Where is the prior work?
Where can I find supporting material?

Appendix A
Can you outline familiar calculus or whatever complicated theory or results you are using that will obscure the text?

Appendix B
A thesis should discuss the following topics:

- **Introduction**
Presentation of the problem or phenomenon to be addressed, the situation where the problem or phenomenon occurs, and references to earlier relevant research.
Common errors
Problem is not properly specified or formulated, insufficient references to earlier work.
- **Purpose**
What can be gained by more knowledge about the problem or phenomenon.
Common errors
The purpose is not mentioned, not connected to earlier research, or not in line with what the actual contents of the thesis.
- **Problem/Hypothesis**
Questions that need to be answered to reach the goal and/or hypothesis formulated by means of underlying theories.
Common errors
Missing problem description, deficiencies in the connections between questions, badly formulated hypothesis.
- **Method**
Choice of an adequate method with respect to the purpose and problem/hypothesis.
Common errors
An inappropriate method is used, for example due to lack of knowledge about different methods; erroneous use of chosen method.
- **Result**
Answers to the forwarded questions by means of the achieved results.
Common errors
The results are not properly connected to the problem, hasty presentation, the results are inter-

Guide to Writing a Thesis Page 4 of 4

mixed with discussion.

- **Discussion**
Discussion of the accuracy and relevance of the results; comparison with other researchers results.
Common errors
Too few reaching conclusions; guesswork; not supported by the data; introduction of a new problem and a discussion around this.
- **Conclusion**
Consequences of the achieved results, for example for new research, theory and applications.
Common errors
The conclusions are too far reaching with respect to the achieved results, the conclusions do not correspond with the purpose.

[Home Page for the Department of Applied Electronics](#)

$\begin{matrix} A & B & C \\ 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 1 \end{matrix}$

Assume (unrealistic) no delay in wires - just gate delays

VERSITY ISLO
 A gate delay after reset goes high, P_u and P_d go low.

1

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

2
 V_{in} goes high

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

3a)
 V_{osc} goes high
 FF2 is set temporarily

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

3b)
 Reset goes high (just after V_{osc})

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

3c)

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

3d)
 After another delay P_u -dsbl and P_d -dsbl go high

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

3e)
 P_u -dsbl and P_d -dsbl cause Reset go low after another gate delay (guarantee P_u and P_d low)

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

4)
 V_{in} goes low
 FF1 goes low

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

Increasing freq on VCO

4b)
 after a gate delay P_u -dsbl turned off

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

5
 V_{osc} goes low

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

FF4 reset
 (after similar chain of events as when V_{in} went low) and P_u -dsbl goes low.
 (BACK IN ORIGINAL STATE)

 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

VERSITY ISLO

Ex. 16.2

Ex. 16.2

Assume the same conditions as in example 16.1. Design a LP-filter for the loop so that the loop time constant is approximately 10 periods at 10 MHz, $Q = \frac{1}{2}$

Equation 16.34: $K_{pll} = \sqrt{K_{pd} \cdot K_{lp} \cdot K_{osc}}$

$$= \sqrt{0.1406 \frac{\text{rad}}{\text{rad}} \cdot 1 \cdot 6.28 \cdot 10^7 \frac{\text{rad}}{\text{s}}} = \sqrt{8829680 \frac{\text{rad}}{\text{s}}} = 2972 \text{ s}^{-1/2}$$

Having a loop-time constant of 10 periods:

$$\omega_0 = \frac{1}{2\tau_{pll}} = \frac{10^7}{100} \text{ s}^{-1} = 10^5 \text{ s}^{-1}$$

16.32: $\omega_0 = \frac{K_{pll}}{\sqrt{C_1}} \Leftrightarrow \tau_p = \left(\frac{K_{pll}}{\omega_0}\right)^2 = 0.883 \text{ ms}$

The pole is located at $f_p = \frac{\omega_p}{2\pi} = \frac{1}{2\pi \tau_p} = \frac{1}{2\pi \cdot 0.000883} = 180 \text{ Hz}$

$Q = \frac{1}{1 + \tau_z \cdot K_{pll}}$

$$\tau_z = \frac{\sqrt{C_1}}{2K_{pll}} = 19.87 \mu\text{s}$$

$V_{pd} \xrightarrow{862k\Omega} V_{lp} \xrightarrow{C_1 = 10nF} \text{LP-filter} \xrightarrow{1.99k\Omega} R_2$

Choose $C_1 = 10 \text{ nF}$

$$R_2 = \frac{\tau_z}{C_1} = \frac{19.87 \cdot 10^{-6}}{10 \cdot 10^{-9}} = 1.99 \text{ k}\Omega$$

$$R_1 = \frac{\tau_p}{C_1} - R_2 = \frac{0.883 \text{ ms}}{10 \text{ nF}} - 1.99 \text{ k}\Omega = 88.3 \text{ k}\Omega - 1.99 \text{ k}\Omega = 86.3 \text{ k}\Omega$$

NIVERSITET
OSLO

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.9 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.9 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.9 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.9 A phase-frequency sequential phase detector based on NAND gates.

UNIVERSITET
I OSLO