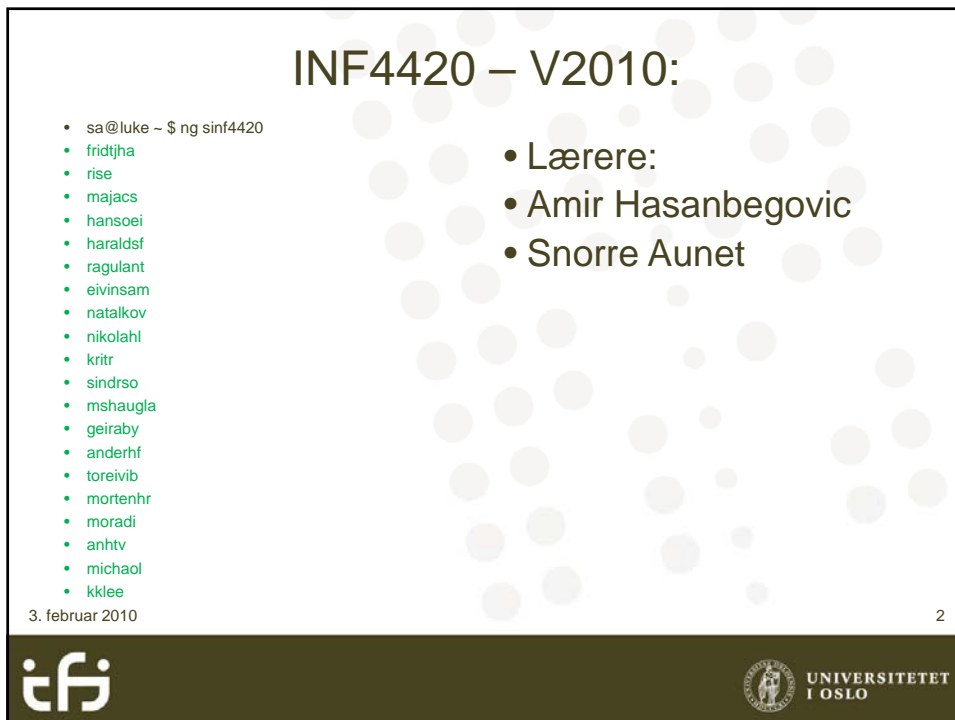





The cover slide features a background image of a person's hands typing on a laptop keyboard. In the top left corner, the 'ifi' logo is displayed in white. The main text is centered and reads: 'Welcome to INF4420 Projects in Analog and mixed signal CMOS design !', 'Introduction, Tuesday 26th of January, 2010', and 'Snorre Aunet, sa@ifi.uio.no', 'Nanoelectronics Group, Dept. of Informatics', 'Office 3432'. In the bottom right corner, the University of Oslo logo and the text 'UNIVERSITETET I OSLO' are visible.



The slide has a light background with a pattern of grey circles of varying sizes. The title 'INF4420 – V2010:' is centered at the top. Below the title, there are two bulleted lists. The first list on the left contains names: sa@luke, \$ ng sinf4420, fridtjha, rise, majacs, hansoei, haraldsf, ragulant, eivinsam, natakov, nikolahl, kritr, sindrso, mshaugla, geiraby, anderhf, toreivib, mortenhr, moradi, anhtv, michael, and kklee. The second list on the right is titled 'Lærere:' and lists Amir Hasanbegovic and Snorre Aunet. At the bottom left, the date '3. februar 2010' is shown, and at the bottom right, the number '2' is displayed. The 'ifi' logo and 'UNIVERSITETET I OSLO' are at the bottom of the slide.

Outline – Tuesday 20th of January



 
- Practical issues
- Learning goals
- Design project, tools and methods
- Syllabus
- Very brief introduction to various circuit building blocks (sample-and-holds, bandgap references, switched capacitor circuits, Nyquist- and oversampling data converters, phase-locked loops)



UNIVERSITETET
I OSLO


CMOS Integrated Circuits?

   - Digital circuits exploit mainly transistors and interconnect
- Mixed-Signal (Digital AND Analog) also use resistors, capacitors and inductors
- Work-horse of modern Information Technology



UNIVERSITETET
I OSLO

 Moore's law: exponential increase in components per area



http://www.uio.no/studier/emner/matnat/ifi/INF4420/

INF4420 - Prosjekt i analog/mixed-signal CMOS konstruksjon

Kort om emnet
 Kurset vil gi nødvendig kunnskap og ferdigheter for å konstruere analoge og "mixed-signal" integrerte kretsmoduler med moderne programverktøy. Hovedfokus i kurset vil være komplekse systemer som dataformere (A/D, D/A) og ferdigste sløyer (PLL). Det vil bli gitt en innføring i CMOS-teknologi og metoder for å implementere passive komponenter som motstander, kondensatorer og spoler i tillegg til matching, optimalisering og styring av viktige aspekter. Gjennomføring av prosjektoppgaver vil stå sentralt i undervisningen.

Hva lærer du?
 Å gi studenterne nødvendige ferdigheter for å kunne konstruere en integrert "mixed signal" krets i CMOS ved hjelp av moderne designverktøy.

Opptak og adgangsgodkjenning
 Studenter med studierett på program eller enkeltfag må hvert semester seke [undersøkningsopptak til emnet](#) i [Studentweb](#). Dersom du ikke allerede har studierett ved UiO, kan du lete om [studietilbud og opptak til program](#) eller om muligheten for [opptak til enkeltfag](#) med [lignende fag](#).

Forkunnskaper
Anbefalte forkunnskaper
 Det er anbefalt at man har tatt [EE1400 - Digital teknolog](#) / [RF130](#)
 Emnet bygger på [RF3400 - Digital mikroelektronikk](#) / [EE4400 - Digital mikroelektronikk](#), [RN241](#) og [RF3410 - Analog mikroelektronikk](#) / [4410](#)

Overlapping
 10 studiepoeng mot [EE3420 - Prosjekt i analog/mixed signal CMOS konstruksjon](#); 6 studiepoeng mot [RF 219](#) og 3 studiepoeng mot [RF 238](#).

Undervisning
 3 timer forelesning og 2 timer øvelse per uke. Noe av undervisningen vil stå i form av veiledning på terminarbeid. Det kreves gjennomføring av obligatoriske øvelser.

Vurdering og eksamen
 Individuell vurdering av prosjektoppgave (ca. 50%) med mellevering i midten av semesteret. Avsluttende muntlig skriftlig 3 timers eksamen (ca. 50%). Bokstavs karakter (A-F).

Adgang til utsett eller ny eksamen/vurdering
 Dette emnet tilbyr ikke ny eksamen i begynnelsen av påfølgende semester til kandidater som styrker eller trekker seg under ordinær eksamen. For generelle opplysninger om ny og utsett eksamen, se [www.uio.no/studier/studieremner/oppkvalifikasjonsreguleringer](#)

Annet
 Det er obligatorisk oppgatte på første forelesning. Ved pålegg gjelder 3-gangers regel og skal emnet sees i sammenheng med [RF3420](#).
 Tilsvarensensor for emnet er: Per Dag Falv.

Fakta om emnet:

Studiepoeng	10
Undervises	Hvert våsemester
Eksamen	Hvert våsemester
Undervisningspråk	Norsk
Tilbys ved	Institutt for informasjons (B)

Semestersider (undervisningsleder, eksamenstidspunkt, pensum m.m.)

- Vår 2010
- Vår 2009
- Vår 2008
- Vår 2007
- Vår 2006
- Vår 2005
- Vår 2004
- Vår 2003





Why ASICs (Application Specific Integrated Circuits) ??

- Advantages:

- Reduced size
- Improved performance and functionality
- Easier to hide "company secrets"
- Reduced cost
- Reduced power consumption
- Less radiated noise




- Disadvantages:

  - Increased start-up cost
- High power density - Heat
- Hard to find top competence
- Time consuming development and production
- Time-to-market



What is an integrated circuit?

 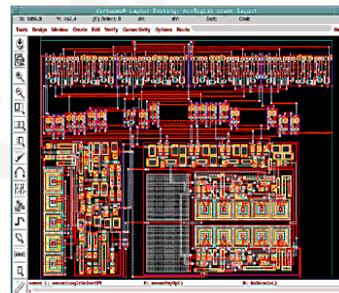 
- Transistors
 - Several options
- Capacitors
 - How to implement
 - Linearity
- Resistors
 - How to implement
 - Area
- Inductors
 - How to implement
 - Quality factor
- Parasitic components
 - Calculate
 - Minimize



Design methods; digital from HDL, full custom analog

- Digital systems:
 - Automatic synthesis
 - VHDL
 - Schematic

 - Analog systems:
 - Module based
 - Full-custom



Low Power..

KISEL ELLER MJUKVARA
 Och till slut – är pendeln på väg att svänga från mjukvara till hårdvara? Idag handlar allt om energiförbrukning och i valet mellan programmerbara system och "hårda" ASIC-lösningar är det ingen större rökkan om vad som är energieffektivast. Och det blir samtidigt allt lättare att konstruera med hjälp av färdiga IP-block.
 Om det här hade jag ett långt och intressant samtal med Kathryn Krause, vd för EDA-företaget Jasper. Kathryn Krause hävdar med bestämdhet att hon ser allt fler halvledarkonstruktioner, inte färre. Till och med företag som inte tidigare gjort egna kretsar tar nu steget till kisel för att klara sina krav.
 Det här är något som vi snart kommer att återkomma till. Ännu så länge saknas hårda data, men de exploderande mjukvarukostnaderna gör att hårdvara inte nödvändigtvis är dyrare än mjukvara. Hårdvarukonstruktionens disciplin och effektiva verifiering kanske gör att det till slut lönar sig med hårdvara.
 Men det återstår att se. ■ ■ ■
Gösta Fagerfjäll

The collage features several advertisements:

- NORDIC SEMICONDUCTOR**: Promoting **µBlue™** Micro ampere Bluetooth® wireless technology.
- ENERGY**: Advertising **EFM32** as "the world's most energy friendly microcontrollers".
- ASD**: Promoting **Impulse Radio Technology** with features like "Single chip Impulse radar" and "Impulse Radio Communication".
- AVR**: Advertising "8- and 32-bit low power, high performance MCUs".

3. februar 2010

10



Mandatory design project

- Design and implement mixed-mode circuit:
 - Example: ADC, SC-filter, PLL, DAC (2008)
 - System for automatic removal of mismatch (2009)
 - Milestones during the process
 - Teaching assistant, Amir Hasanbegovic, will follow up
- Write a project report
 - LaTeX or similar
- Submission: Early/Mid May
- Counts 40 % in the final grading (exam 60%)

Challenge in 2008: Digital-to-Analog Converter ("DAC")

INF 4420 - Prosjektoppgave: Digital til Analog Omformer - 2008

1 Introduksjon

Det skal lages en data konverter av typen "Two-stage balanced current DAC", illustrert i figur lengre ned.

- DAC'en skal ha en oppløsning tilsvarende minimum 6 bit.
- Anta i utgangspunktet at maksimalt et en spenningsreferanse og en strømkilde er tilgjengelig, og dermed ikke trenger konstrueres.
- Digitalt ord inn (input) skal være på følgende form, forutsatt 6 bit oppløsning: 00..0, 00..1, ..., 11..1.
- Utgangsspillet skal være nedad begrenset til 0.3 V og oppad begrenset til 0.7 V.
- Positiv forsyningspennig ("VSP") er 1.0 V. Negativ forsyningspennig ("VSN") er 0 V.
- Maksimal CLK: +1..1.58
- Kretsen slik den er i kretsdiagrama mangler buffer, for eksempel i form av en spenningsfølger, som går inn i stand til å drive en kapasitiv last i form av VO-celle ("pad"). Det er frivillig evt å lage et slikt buffer, ikke påkrevd.
- Søk en best mulig konstruksjon ut fra effektivitet og areal.

2 Målepåler

For å sikre gjennomføring innenfor tidsrammen settes det delmål med oppgitte frister. Studentene har ansvaret for å få disse delmålene godkjent av gruppelærer.

11/2-08 Det skal leveres inn et dokument på inntil 2 sider som beskriver hvordan dere har forstått oppgaven, og skisserer hvordan dere har tenkt å løse den.

25/3-08 Testbenk for systemet skal være ferdig.

05-08 Design og simuleringarbeidet for hele kretsen skal være ferdig for både skjema og utlegg, og LVS inkludert. Gruppelærer skal eventuelt godkjenne at kretsen fungerer tilfredsstillende på bakgrunn av demonstrasjon.

3 Krav til prosjektgjennomføring

3. februar 2010

Måsetingen er å lage en digital-til-analog omformer ("DAC") med minimum 6 bit nøyaktighet. Gruppens medlemmer må i fellesskap gå gjennom oppgaven og fordele arbeidsoppgaver, men samtidig skal kunne stå inne for og redde seg for konstruksjonen. Arbeidsfordelingen mellom deltakere i prosjektet skal rapporteres. Under følger noen tilleggsopplysninger og nærmere spesifisering.

3.1 Trykktid arbeid

1. komplette skjema, ned til transistornivå, skal tegnes. Det skal legges symboler for de ulike byggeblokkene som inngår i det komplette systemet som utgår dataomformeren.

2. Berytt statistiske ("Monte-Carlo") simuleringer for å verifisere funksjonalitet under prosessvariasjoner.

3. Når simuleringresultatene er tilfredsstillende skal det tegnes fysisk utlegg ("layout") for hver av byggeblokkene, som til slutt settes sammen til den komplette kretsen.

4. Det er en del spesielle utfordringer i forbindelse med design av systemer som inneholder mixed-signal (analoge og digitale) byggeblokker. Identifiser slike utfordringer og foreslå tiltak for å løse disse.

5. Berytt Layout Versus Schematic ("LVS") for delkreter og totalsystem, for å verifisere samsvare mellom kretsdiagram og tilsvarende utlegg, og lette konstruksjonen. Resultatene fra LVS skal vedlegges prosjektrapporten.

4. Krav til rapport.

Sertrakt i bedømmingen av arbeidet vektlegges rapportens kvalitet. Skriv den i LaTeX eller tilsvarende program. De ulike fasene av prosjektet skal dokumenteres. Dette inkluderer sia plott av skjematikk samt simuleringresultater som demonstrerer funksjonalitet hos de ulike byggeblokkene. LVS rapporter fra Cadence harer også hjemme her. Begynn og dokumenter de ulike valgene dere har gjort. Dette inkluderer blant annet dimensjonering av aktive og passive komponenter, problematik omkring matching, tiltak mot støy, samt layout.

Husk at bidrag fra de ulike gruppelemmene skal være identifiserbare.

Rapporten skal også inneholde informasjon om hvor Cadence-filer ligger tilgjengelige for etterkontroll av resultater.

Sensor bedømmer rapporten. Derfor er det viktig at denne er mest mulig forståelig for sensor.

5. Frister for innlevering.

Prosjektet skal være avsluttet og rapport innlevert senest 05-2008 kl. 12:00. Alle gruppene må presentere resultatene av prosjektet etter innlevering. Følg med på fagens hjemmeside for evt. andre beskjeder. Vurdering baseres på en bedømming

av arbeidets kvalitet, og rapportens kvalitet, slik dette framgår av sistnevnte. En prosentuell score vektles inn i endelig karakter for faget.

 


Fig 4.6 Diagram, two-stage balanced current DAC.

Fra "High-Speed Data Converters Fully Integrated in CMOS", Leif Hanssen, dr. scient. avhandling, IFU, 1990.

Lykke til!!

12

INF4420 Project 2009 (1/2)

INF4420 project description

Some years from now, you have been hired by an undisclosed chip maker as their mixed signal designer, partly because of your achievements in the INF4420 course. The company is currently working hard towards finishing their new flagship product. The system designers in your group already have very promising high level simulation results of the product. From these simulations they have derived the specifications for each building block.

The OTAs are central components in this system, as a lot of the specifications for the final product relies on OTA performance. Your group's analog designer already have a working folded cascode OTA which almost meets the spec, except for the offset voltage. This is not easily correctable in the layout because the required transistor sizing would be impractical and incur other unacceptable side effects.

At the next meeting, you suggest doing a digital calibration loop¹ for the OTA's offset voltage. The OTA's designer advise you that the trimming can be done easily by drawing a compensation current from the input-stage differential pair.

For this product, timing is not tight so you should have plenty of time for running the calibration. However, if you can make it faster, it will be much easier to apply to future products, without having to go through an expensive redesign.

1 Measuring the OTA performance

The existing OTA is available from `/ben/sjorgensen/cadence.atm99/INF4420`. Use the library manager to add this path (Edit → Library path...). Using an ideal 100 pF capacitor as load, connect the OTA in a closed loop unity gain feedback, and measure the following:

- Gain-bandwidth product (GBW)
- Phase margin (PM)
- If you like, you can also measure
 - Noise
 - Slow rate (how does this compare to the theory?)
 - Output swing
 - Settling behaviour
 - Or other relevant parameters

3. februar 2010

¹The workings of the calibration loop will be described later.

 


Figure 1: Digital trimming of the OTA's offset voltage (All NMOS are 0.5/0.5 μm)

Next, set up a testbench to find the variation in offset voltage. Use a monte-carlo (MC) analysis with 100 runs.

- What is the standard deviation, σ , of the offset voltage?
 - If we cover for variation, how many percent of the manufactured OTAs will function to spec?
 - What is the 6σ value?
- Remembering that β_{eff} is the transistor parameter that relates a change in gate voltage to a change in drain current, we can find the maximum required compensation current as $I_{bias} = \beta_{eff} \times \Delta V_{GS}$. To find the β_{eff} you can use an operating point analysis (remember to save operating point) and the results browser which you find under the tools menu in ADE.
- What is the value of g_m of transistor M1 or M2 in the OTA?
 - What is the value of I_{bias} ?

2 Simulating the calibration loop

It's now time to simulate the entire calibration loop using the supplied components `OTA_crisin`, `DAC_ideal`, and `SAR_OTA_crisin` in the same as OTA but with an added current-mode trimming port. `DAC_ideal` is an ideal 7 bit DAC, constructed with radix 1.77 (sub-binary resolution).

If we run the OTA in open loop, an offset voltage will cause the output to rail (assuming sufficient gain). We can use this to detect if the offset voltage is too high or low. To properly buffer the output to a clean digital level, we can add inverters as buffers.

The DAC outputs a differential current approximately proportional to the input word (it does have some redundancy). This current is applied to the trimming port of



INF4420 project 2009 (2/2)

 


Figure 2: M3M DAC schematics (all PMOS are 0.5/0.2 μm)

the OTA through a current mirror. Thus, we now have a digital input for trimming the OTA's offset voltage. To find the suitable digital correction word, we will use a successive approximation register (SAR). The SAR sets each bit, starting at the MSB. If the OTA output swings above the common mode output voltage, the next bit is cleared. After testing each bit, the SAR signals that it is done, and that normal system operation can resume. Thus, this signal can be used to switch the OTA between open loop and closed loop unity gain feedback.

- Simulate the system to verify its functionality
 - What is the offset voltage after calibration?
 - What is the σ of the offset voltage now?
- Make a testbench and measure how the added trimming circuitry affect the performance of the OTA.
- Is the performance different compared to your previous measurements?
 - What can be done to counter this?

3 DAC design

• Draw ideal transfer functions for a radix 2 converter and a radix 1.77 converter in the same plot.

Figure 3 depicts the schematics of a so-called M3M DAC. The nodes are all in the triode region.

- How does this structure compare to the more familiar B2R DAC?
- Make a testbench where you compare the transfer function of the ideal DAC with the M3M DAC.

Replace the ideal DAC in your calibration loop test bench with the M3M DAC.

- How does this affect the performance of the calibration loop?

Draw layout for the M3M DAC and the current mirror, remember to verify its correctness using DRC and LVS. Finally, do a parasitic extraction of the layout.

- Simulate the calibration loop with the extracted netlists.

4 Project requirements

The transistor sizing given in this document are reasonable guidelines to get you started. You are free to change this if necessary.

Document everything, including but not limited to, all relevant schematics, layout, and simulation results. Discuss the choices you have made in designing and testing. Everything should be clear just from reading the documentation.

5 Deliverables

1. Do the first part of the project, described in Sect 1. Deadline March 19.
2. Do the second part of the project, described in Sect 2. Deadline April 2.
3. Finalize the project by completing the third and final part of the project, described in Sect 3, and write your final report. Deadline May 11.

In the first two deliverables, write a short report observing the guidelines in Sect 4. The final report must be comprehensive and document the entire project (i.e. include all deliverables). Only this final report will contribute towards your final grade. Please make all schematics and layout available for inspection.

IAM, February 12, 2009




Cadence (<http://www.cadence.com/>)

- Widely used IC design tool worldwide, both in companies and academia
- Very large system
 - PCB-design
 - IC-design
 - Synthesis
 - Schematic entry
 - Simulator (Analog Environment / Spectre)
 - Layout (Virtouso)
- DRC and LVS performed by Calibre (Mentor)



Full-custom ("handmade") design flow

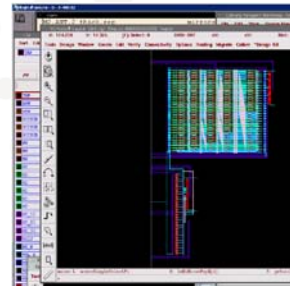- Design and calculation
 - Design equations
 - Dimensioning for matching
- Schematic entry
 - Simulations on cells and top level
 - Several interactions
- Layout
 - Module interface
 - Symmetry/hierarchy
 - Post Layout Simulations on critical modules
- Next module....




Cadence forts.


- Start-up:
 - Web manual
- Standard libraries:
 - tsmcN90rf
 - analogLib
- Design views:
 - Symbol
 - Schematic
 - Layout



 Schematic entry and simulations in Cadence



Symbol, schematic and layout (Cadence)

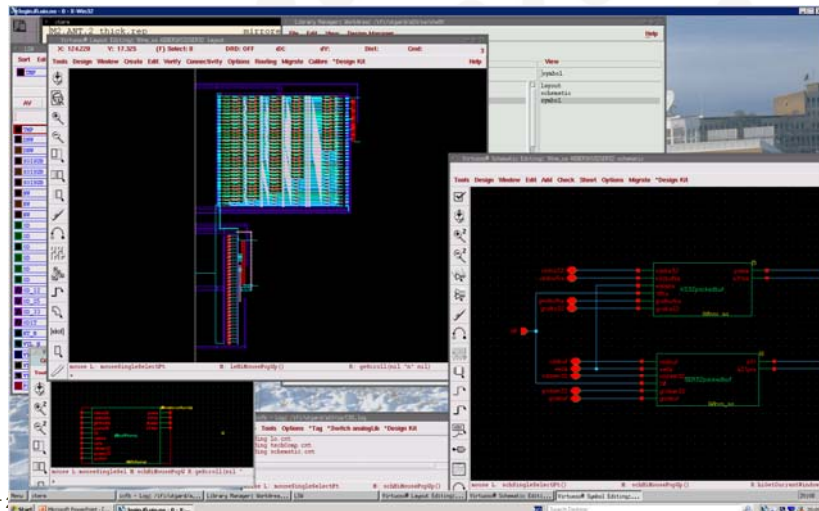

3. februar


19



Process

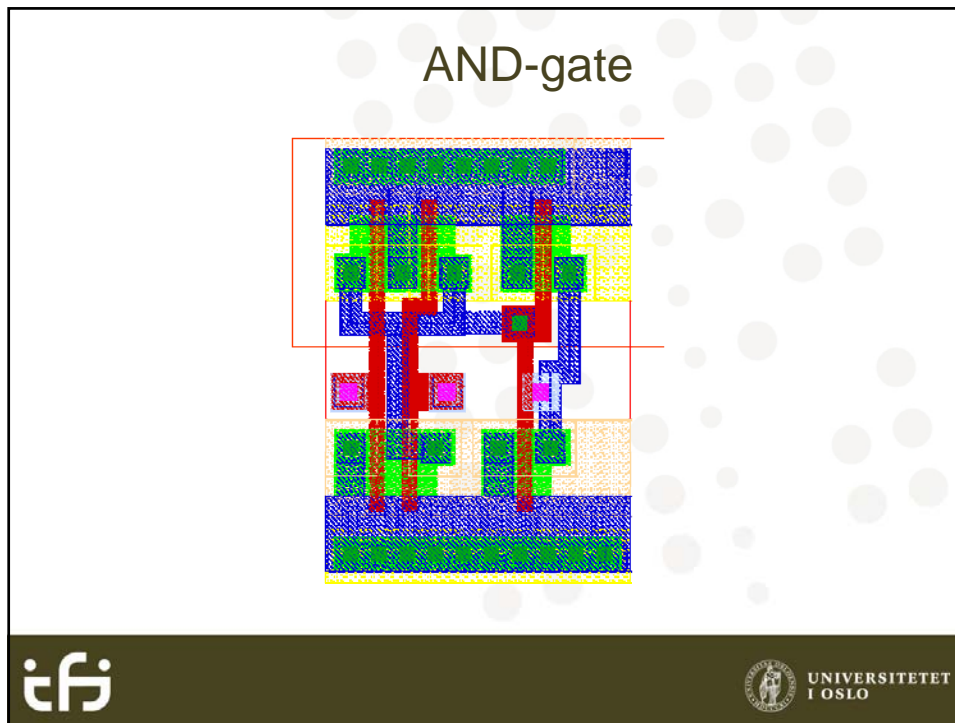
- TSMC 90 nm **low power** CMOS:
 - Minimum gate length: 90nm
 - 1 Poly-layer
 - 9 Metal-layers
 - True triple well
 - Three different threshold voltages
 - Supply voltage: 1.2 V typ.
 - Very advanced process





Challenges regarding the project

 - Project administration
- Theoretical analysis and circuit design
- Design errors
 - LVS
- Parasitic components
 - Extraction and Post Layout Simulation (PLS)
- Process variations
 - Simulations (Corner + Monte-Carlo)
- Noise
 - Component and crosstalk
- Good layout practice / Symmetry



Practical information

- Lectures:
 - Tuesdays . 9.15 – 11.00 (should not collide with FYS3240).
 - From. 26/2: Tuesday . 9.15 – 12.00 (Might be 9:15 – 11:00 in most cases)
- Syllabus:
 - Johns and Martin: Analog Integrated Circuit design (Kap. 2, 8-14, 16. Not bipolar)
 - Selected additional material and lecture notes
 - LTH: Cadence 4.4
 - IFI: Lokal guide til Cadence
- Exercises
 - 2 hours per week – Time will be set next week. Amir Hasanbegovic, amirh@ifi.uio.no
- Projectsupervision/design lab
 - 2/4 hours each week – Time may be adjusted. Amir H., amirh@ifi.uio.no .
 - Room 3217 (?)
- Software:
 - Cadence 5.00 or 6.00 ((?))
 - TSMC 90 nm design kit
- Where to run the software:
 - Win PC running X-Win connected to Linux server /remote desktop and Linux
 - Linux computer
- Student reference group
 - 1-2 students



UNIVERSITETET
I OSLO

What do we expect from you?


- The course is demanding
- Theoretical background
 - INF3410 analog microelectronics, or similar
 - FYS3220 linear circuit theory, or similar
 - INF3440 signal processing, or similar
- Prepare for the lectures
- Exercises
- Use the reference group and course evaluations to provide feedback



UNIVERSITETET
I OSLO

Final exam – a few words

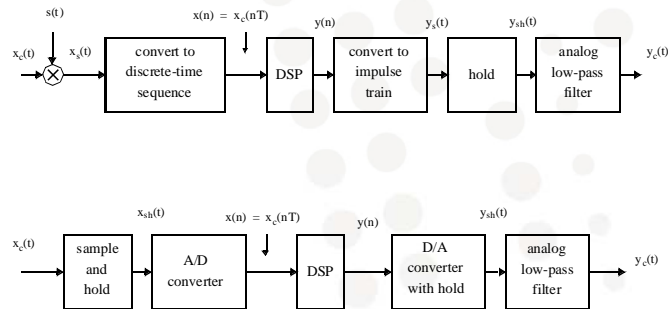- Thursday **3rd of June**, starting **14:30** (3 hours)
- Problems usually related to every single of the relevant chapters in the book (2,8,9,...,14,16), and material from the lectures





Syllabus; chapters 2,8,9,10,11,12,13,14,16

- Chapter 2 Processing and layout
- Chapter 8 **Sample and Holds, Voltage references**, and translinear circuits
- Chapter 9 **Discrete-Time Signals**
- Chapter 10 **Switched-capacitor circuits**
- Chapter 11 **Data converter fundamentals**
- Chapter 12 **Nyquist-rate D/A converters**
- Chapter 13 **Nyquist-rate A/D converters**
- Chapter 14 **Oversampling converters**
- Chapter 16 **Phase-locked loops**



(in lectures, tuesdays)

Syllabus; chapter 2

  


- CMOS processing
- Relative matching far better than absolute accuracy in CMOS
- CMOS layout and design rules
- *"Matching is the Achilles heel of analog"* C. Diorio, Impinj / Washington State University
- A bad layout can ruin about any analog circuit.




Chapter 8 Sample and Holds, Voltage References

 - Performance of S/H
- S/H basics
- Bandgap voltage reference basics
- Circuits for bandgap references




Chapter 9 Discrete-Time Signals

 - Signal spectra
- Laplace transform of discrete-time signals
- Z-transform
- Downsampling and upsampling
- Discrete-time filters
- S/H response





Chapter 10 Switched-Capacitor Circuits

 - Building blocks
- Operation and analysis
- First-order filters
- Biquad filters


  
$$\Delta Q = C_1(V_1 - V_2) \text{ every clock period}$$




$$R_{eq} = \frac{T}{C_1}$$



Chapter 11 Data converter fundamentals

 - Ideal D/A and A/D
- Quantization noise
- Signed codes
- Performance limitations




ifi

UNIVERSITETET
I OSLO

Chapter 12 Nyquist-Rate D/A Converters

 - Decoder-based converters
- Binary-scaled converters
- Thermometer-code converters
- Hybrid conv.




ifi

UNIVERSITETET
I OSLO

Chapter 13 Nyquist-Rate A/D Converters

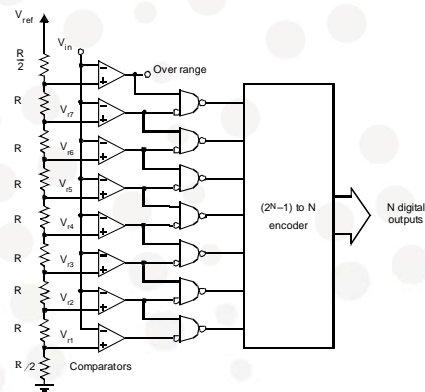- Integrating converters
- Successive approx. converters
- Algorithmic converters
- Flash (parallell) conv.
- Two-step, interpolating,
- Folding, pipelined conv.



ifj



UNIVERSITETET
I OSLO

Two consequences of the Nyquist-theorem and anti-aliasing filters (Wikipedia):

- If the highest frequency B in the original signal is known, the theorem gives the lower bound on the sampling frequency for which perfect reconstruction can be assured. This lower bound to the sampling frequency, $2B$, is called the [Nyquist rate](#).
- If instead the sampling frequency is known, the theorem gives us an upper bound for frequency components, $B < fs/2$, of the signal to allow for perfect reconstruction. This upper bound is the [Nyquist frequency](#), denoted fN .
- An **anti-aliasing filter** is a filter used before a signal sampler, to restrict the bandwidth of a signal to approximately satisfy the [sampling theorem](#). Since the theorem states that unambiguous interpretation of the signal from its samples is possible only when the power of frequencies outside the Nyquist bandwidth is zero, the anti-aliasing filter would have to have perfect stop-band rejection to completely satisfy the theorem. Every realizable anti-aliasing filter will permit some [aliasing](#) to occur; the amount of aliasing that does occur depends on how good the filter is.


ifj



UNIVERSITETET
I OSLO

Chapter 14 Oversampling Converters

 - Oversampling ($\gg 2$ Nyquist bandwidth) relaxes requirements for matching
- High resolution, low to medium speed
- Noise shaping & oversampling
- N+1 order modulator gives a certain SNR for lower OSR than N-order mod.
- 24 bit Audio conv.




ifj

UNIVERSITETET
I OSLO

Chapter 16 Phase-locked loops

 - Application examples:
- clock multiplication,
- Freq. generation: The PLL output is a signal with frequency N times the input frequency where N may be a fractional number
- FM demodulation (The input is a FM signal (IF) The output is the demodulated baseband signal)
- Products: TV and wireless



ifj

UNIVERSITETET
I OSLO

www.akademika.no / www.gnist.no / www.amazon.co.uk

3. februar 2010 37


ifi UNIVERSITETET I OSLO

Next week:

- Sample and Hold circuits (chapter 8)
- Questions: sa@ifi.uio.no



ifi UNIVERSITETET I OSLO

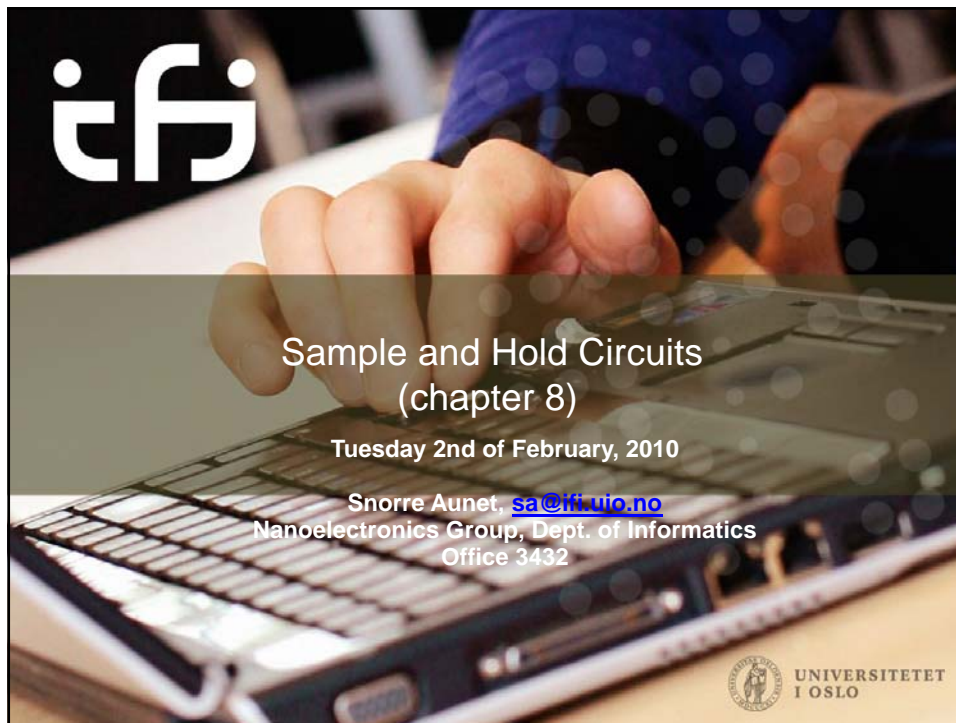


ifi

Sample and Hold Circuits (chapter 8)


Tuesday 2nd of February, 2010

Snorre Aunet, sa@ifi.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

 UNIVERSITETET
I OSLO

Last time – Tuesday 26th of January

 - Practical issues
- Learning goals
- Design project, tools and methods
- Syllabus
- Very brief introduction to various circuit building blocks (sample-and-holds, bandgap references, switched capacitor circuits, nyquist- and oversampling data converters, phase-locked loops)




Sample and Holds (S/H) – What are the purposes?

- Mainly used in Analog-to-Digital Converters (ADC)
 - Samples analog input signal and holds value between clock cycles
 - Stable input value is required in many ADC-topologies
 - Reduces ADC-error caused by internal ADC delay variations
- Sometimes referred to as Track and Hold (T/H)
- Important parameters for S/H's
 - Hold step: Voltage error during S/H-transition
 - Signal isolation in hold mode
 - Input signal tracking speed in sample mode
 - Droop rate in hold mode: Small change in output voltage
 - Aperture jitter: Sampling time uncertainty



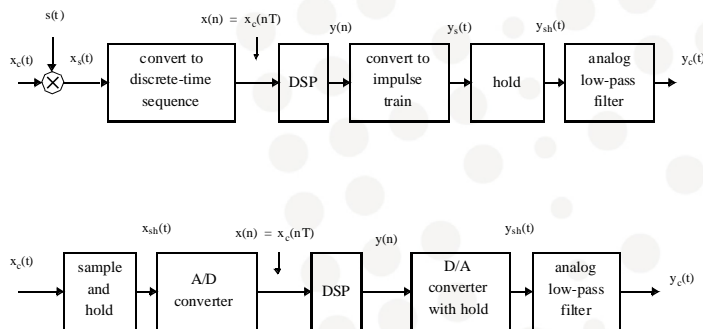
Overview of signal spectra – conceptual and physical realizations



- An **anti-aliasing** filter (not shown) is assumed to band limit the continuous time signal, $x_c(t)$.
- **DSP** ("discrete-time signal processing") may be accomplished using fully digital processing or discrete-time analog circuits (ex.: SC-circ.)





Basic S/H-topology

 

- Hold step:
 - Switch charge injection causes signal dependent hold step
- Aperture jitter:
 - Sampling-time variations causes signal dependent errors



Basic S/H-topology

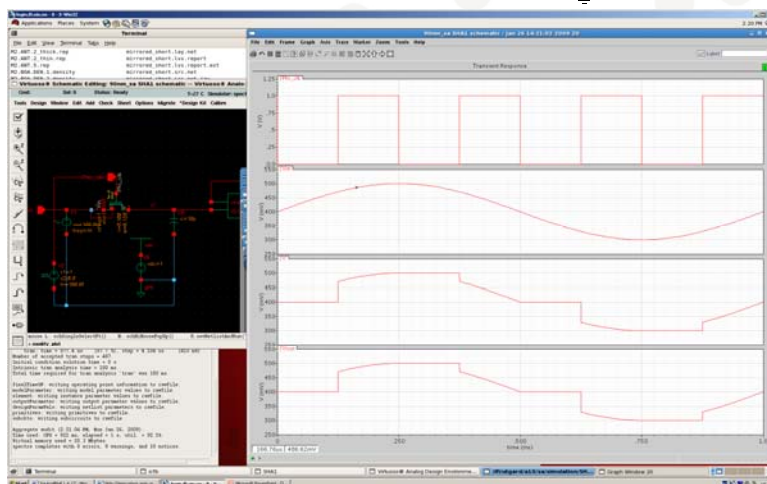 



Charge injection due to channel capacitance

When ϕ_{clk} goes low, the channel charge of Q_1 is equally distributed between source and drain, leaving 50% of the charge across C_{hld} :

$$\Delta Q_{C_{hld}} = \frac{Q_{CH}}{2} = \frac{C_{ox}WL V_{eff-1}}{2}$$

$$V_{eff-1} = V_{GS1} - V_{tn} = V_{DD} - V_{tn} - V_{in}$$
  
$$\Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{ox}WL(V_{DD} - V_{tn} - V_{in})}{2C_{hld}}$$




- $\Delta V'$ is linearly related to V_{in} , resulting in a **gain error** for the S/H. There is also a linear relationship to V_{tn} , which is nonlinearly related to V_{in} (through V_{sb}) resulting in **distortion** for the overall S/H.

Charge injection due to the gate overlap capacitance:


-
 
$$\Delta V' \cong -\frac{C_{ox}WL_{ov}(V_{DD} - V_{SS})}{C_{hld}}$$



- (See eq. 7.8) This component is usually **smaller** than that due to the channel charge, and appears as an **offset**, since it's signal independent. Thus it **may be removed** in most systems.
- The clock signal should be relatively noise free, as the power-supply rejection of this S/H might be poor. (if for example clock signal comes from an inverter with common V_{dd} and V_{ss})

Hold step reduction

 


CMOS transmission gate

Dummy switch


- **Transmission gate** reduces charge injection since the charge carriers in the NMOS and PMOS have inversed polarity -> The negative charge from the NMOS cancels the positive charge from the PMOS
 - PMOS and NMOS are however hard to match in size, reducing the benefit.
- A NMOS **dummy switch** (S and D short-circuited) of half channel area clocked on inverted clock may be used to absorb charge
 - Hold step reduced by approximately 80%
 - The dummy switch clock must be slightly delayed to ensure that no charge leaks through Q1 while it is still open

Aperture jitter

 

- If the input voltage is lower than the capacitor voltage, V_{in} is the source of the transistor used as a switch
- V_{gs} is then depending on V_{in} . For high values of V_{in} , the switch turns off too fast while for low values of V_{in} it turns off too late causing **distortion**

S/H (fig. 8.7)

 


- **Advantages:**

- High input impedance
- Buffer offset voltage is divided by the gain of the input opamp, due to negative feedback. Simple voltage follower may be used at the output.


- **Disadvantages:**

- Errors due to finite clock rise- and fall-times (PMOS and NMOS are not switched off at the same time)
- Signal dependent charge injection -> Distortion
- Feedback loop and need for stability limit maximum speed
- In Hold mode, the first opamp output goes to either rail. Must slew back

Sample-and-Hold from fig. 8.7

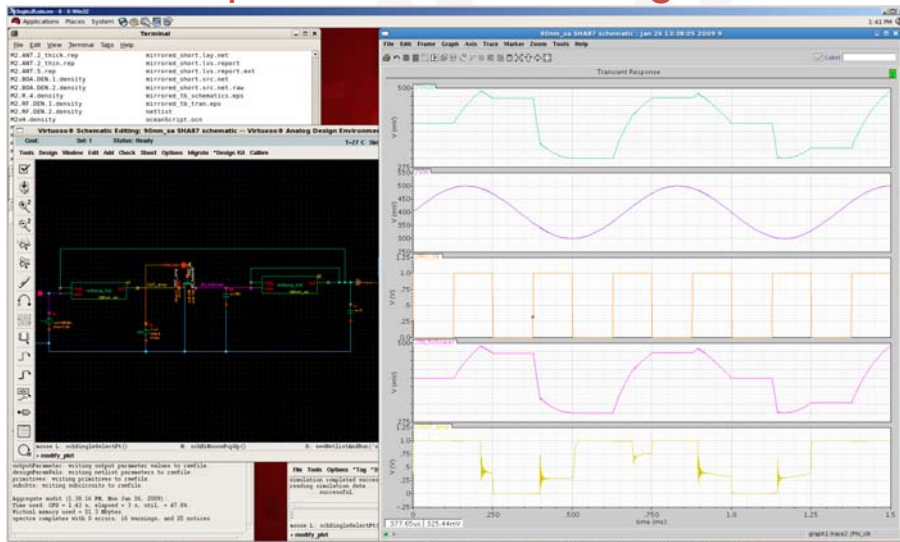


Increased speed (fig. 8.8)

 


- During hold mode the opamp output is tracking the input
 - Leads to increased speed
- Disadvantages in common with the previous circuit

SAMPLE (= Track) / HOLD modes (fig 8.8)

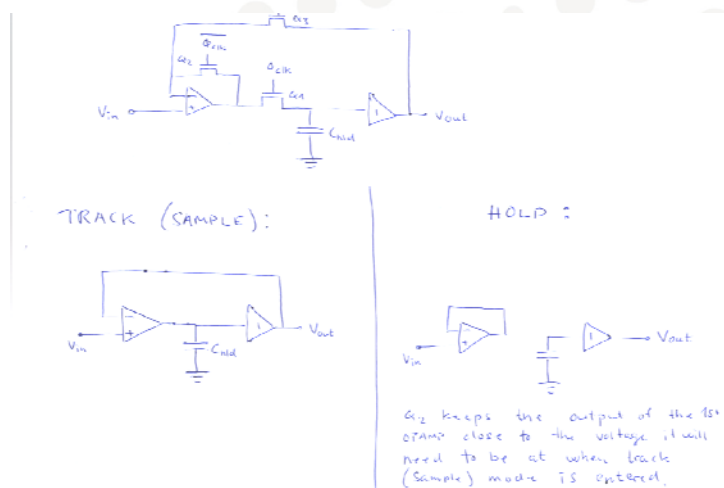


Sample-and-Hold from fig. 8.8

 


Another S/H: Fig 8.9 (Improved version of the S/H from fig 8.8)

Fig. 8.9:

 

SAMPLE:

 

HOLD:




ϕ_2 grounds the output of OPAMP2 during HOLD. Then the output is close to where it will be when changing to SAMPLE-/TRACK-mode.

 3. februar 2010

Sample (track) mode to Hold mode (the S/H in fig. 8.9) signals, from top: $V_{\text{outopamp1}}$, $V_{(Q2)}$, $V_{(Q1)}$, V_{out} , V_{in}




S/H with hold step independent of input signal (fig. 8-9)



- + : Both sides of Q_1 are nearly signal independent, so that the charge injection is (nearly) signal independent, provided a sufficient gain in the 2nd Opamp. The charge injection on C_{hld} causes the **output** of the 2nd Opamp to have a positive **hold step**, which is just a dc offset, with **no signal distortion**, and **signal independent**.
- + : Sampling time will not change due to finite slopes of the sampling clock \rightarrow less aperture jitter / aperture uncertainty \rightarrow sample value closer to the ideal one.

 S/H with hold step independent of input signal (fig. 8-9)



- + : Q_2 ground the output of OPAMP1 in hold mode, meaning that it's close to (and quickly getting to) the voltage it should have in S. mode, which improves speed.
- Preventing instability **reduces speed**
 - Worsened due to two opamps in the feedback loop
- More relevant information: K. R. Stafford, P. R. Gray, R. A. Blanchard: "A Complete Monolithic Sample/Hold Amplifier", IEEE Journal of Solid-State Circuits, Dec. 1974. (available from <http://ieeexplore.ieee.org> , when on UiO IP-address)

"New(er) architecture"

FIGURE 9. Closed-Loop Architecture with Integrator Output

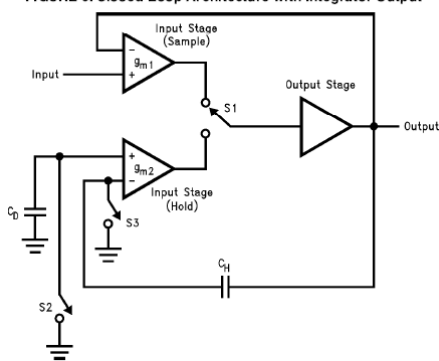


FIGURE 10. Current Multiplexed Architecture

A new architecture which combines the speed of the open-loop configuration and the accuracy of the closed-loop configuration is the current-multiplexed architecture shown in Figure 10. The LF6197, National's High Performance VIP™ Sample-and-Hold Amplifier used this architecture. This architecture provides for a cancellation of charge injection, allowing one to use a small hold capacitor to get high speeds without the disadvantage of a large hold step.

Specifications and Architectures of Sample-and-Hold Amplifiers

National Semiconductor
Application Note 775
July 1992

Continuous efforts to improve S/H circuits..

A Sample/Hold Circuit for 80MSPS 14-bit A/D Converter

Xiao Kunguang^{1,2}, Wang Yuxing^{1,2}, Xu Minyuan^{1,2}, and Zhu Chan^{1,2}

454

IEEE JOURNAL OF SELECTED TOPICS IN SIGNAL PROCESSING, VOL. 3, NO. 3, JUNE 2009

Digital Calibration of a Nonlinear S/H

Patrick Satarzadeh, *Student Member, IEEE*, Bernard C. Levy, *Fellow, IEEE*, and Paul J. Hurst, *Fellow, IEEE*

A High-Speed Highly-Linear CMOS S/H Circuit

Mahmoud Sadollahy^{1,2}, Khayrollah Hadidi¹

¹Acad Islamic University, Safian Branch

²Microelectronic Research Laboratory, Urmia University
st_madollahy@matl.urmia.ac.ir

978-1-4244-1692-9/08/\$25.00 ©2008 IEEE

 


Figure 1. Sample and hold architectures.

 



Figure 2. Proposed open loop S/H architecture.

- IEEEExplore may provide State-of-the-Art solutions

3. februar 2010

21

Reduced DC-error (fig. 8-10)

 

- Improved version of previous circuit (in fig. 8.9)
- By placing a copy of Q1 and Chld in parallel between ground and the positive input of the second opamp, the voltage change due to charge injection will be equal on both inputs. Error is cancelled by [opamp CMRR](#).
The **common-mode rejection ratio** (CMRR) of a differential amplifier (or other device) measures the tendency of the device to reject input [signals](#) common to both input leads.

Additional Background Litterature, S/H circuits

- A. S. Sedra, K. C. Smith: "Microelectronic Circuits", Saunders College Publishing, 1991.
- R. Gregorian, G. C. Temes: "Analog MOS Integrated Circuits for signal processing", Wiley, 1986.
- K. R. Stafford, P. R. Gray, R. A. Blanchard: "A Complete Monolithic Sample/Hold Amplifier", IEEE Journal of Solid-State Circuits, Dec. 1974.
- F. F. Kuo: "Network Analysis and Synthesis", Wiley, 1966.
- S. Soma: "Grunnbok i elektronikk", Universitetsforlaget, 1979.
- National Semiconductor: "Specifications and Architectures of Sample-and-Hold Architectures", App. Note 775, July 1992.
- S. Aunet: "BiCMOS Sample-and-Hold for Satelittkommunikasjon", hovedfagsoppgave, UiO, 1993.

3. februar 2010

23



S/H stuff..



See p.22
 When $\phi_{in} = 1$, V^+ follows V_{in}
 When $\phi_{in} = 0$, V^+ stays constant, being a value equal to V_{in} at the instance ϕ_{in} went low.
 If $\phi_{in} > V_{in}$, equal number of positive and negative charges are injected into the node.
 $I_{avg} = \frac{C_{load} \Delta V}{T}$

Unfortunately, V^+ will have a negative going hold step, caused by channel charge from transistor Q_1 .

If Q_{ch} is turned off fast, the channel charge, Q_{ch} , will flow equally into both junctions. The charge flowing to V^+ is then given by: $\Delta Q_{ch} = \frac{Q_{ch}}{2}$

$(C_{ox} W L) \Delta V_{ch} = \frac{Q_{ch}}{2}$
 $\Delta V_{ch} = \frac{Q_{ch}}{2 C_{ox} W L}$

The change in V^+ is:
 $\Delta V^+ = \frac{\Delta Q_{ch}}{C_{load}} = \frac{(C_{ox} W L) \Delta V_{ch}}{2 C_{load}}$
 ΔV^+ is turning method to V_{in} = GAIN ERROR

$$\Delta V^+ = \frac{C_{ox} W L (V_{in} - V_{ch} - V_{ch})}{2 C_{load}}$$

ΔV^+ is also linearly related to V_{in} , which is unfortunately related to the input signal, V_{in} , due to variations in the source-substrate voltage (turning the substrate is tied to one of the voltage rails)

∴ This nonlinear relationship with V_{in} results in distortion for the overall sample-and-hold circuit.

Additional charge in V^+ due to the gate overlap capacitance.

Using a derivation similar to that used to find (9.7), we have:
 $\Delta V^+ = \frac{C_{ov} W L (V_{in} - V_{ch})}{C_{load}}$ (9.7.10)

This component is usually smaller than the one due to the channel charge, and speed independent. This means it can be removed.



3. februar 2010

24



ifi

Bandgap References and Discrete Time Signals
(chapter 8 + 9)

Tuesday 9th of February, 2010

Snorre Aunet, sa@ifi.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

UNIVERSITETET
I OSLO

Last time – Tuesday 2nd of February, and today, February the 9th:

- 8.1 performance of Sample-and-Hold Circuits
- 8.2 MOS Sample-and-Hold circuits
- 8.3 Examples of CMOS S/H circuits
- 8.5 Bandgap Voltage Reference Basics
- 8.6 Circuits for Bandgap References
- Chapter 9 Discrete-Time Signals
- 9.1 Overview of some signal spectra
- 9.2 Laplace Transforms of Discrete-Time Signals
- 9.3 Z-transform

ifi

UNIVERSITETET
I OSLO


Voltage references (chapter 8.5)

- Purpose:
 - Generate a **constant on-chip voltage** which is independent of temperature, supply voltage, aging etc.
- Different approaches:
 - 1) **Breakdown** voltage of a reverse-biased **zener** diode
 - **Too high voltage** for CMOS
 - 2) Threshold voltage difference between CMOS enhancement and **depletion transistors**
 - Depletion-mode transistors **unavailable** in most CMOS processes
 - 3) **Bandgap references**: Canceling the negative temperature dependence of a forward-biased pn-junction (CTAT) with a positive temperature dependence (PTAT) (proportional-to-absolute-temperature) circuit
 - Most commonly used
 - CTAT: Conversely proportional to temperature
 - PTAT: Proportional to temperature

More about today's Bandgap Reference agenda (including, but not limited to):

- About the fundamental equations giving the relationship between the output voltage of a bandgap reference and temperature.
- How to design a bandgap reference for a "most stable" reference voltage at a particular temperature.
- How to estimate temperature dependence at another temperature that the BG reference was designed for.
- Practical implementations

Basic principle

 

- The voltage V_{BE} is CTAT
- The voltage ΔV_{BE} is PTAT
- ΔV_{BE} is scaled by K to get the same slope as V_{BE}
- By adding V_{BE} and $K \Delta V_{BE}$, the output V_{ref} becomes independent of temperature



Bandgap reference example

A High Precision Curvature Compensated Bandgap Reference without Resistors

Jianghua Chen*, Xuewen Ni, Bangxian Mo and Zhanfei Wang
 Institute of Microelectronics, Peking University, Beijing 100871, P.R. China
 * Email: chenjianghua@ime.pku.edu.cn

A High Precision Curvature Compensated Bandgap Reference with
 Jianghua Chen; Xuewen Ni; Bangxian Mo; Zhanfei Wang;
 Solid-State and Integrated Circuit Technology, 2006, ICSICT'06, 8th Intl
 23-26 Oct. 2006 Page(s):1748 - 1750
 Digital Object Identifier 10.1109/ICSICT.2006.306414
[AbstractPlus](#) | Full Text: [PDF \(124 KB\)](#) [IEEE CNF](#)
[Rights and Permissions](#)

 


Figure 4 Output reference V_{ref} vs. temperature.

 


Figure 1 General bandgap reference architecture.

 


Figure 5 Output reference V_{ref} vs. power supply V_{dd} .

9. februar 2010



Theory

- Collector current

$$I_C = I_s e^{V_{BE}/(kT/q)}$$

- Solved with respect to V_{BE} :

$$V_{BE} = V_{G0} \left(1 - \frac{T}{T_0}\right) + V_{BE0} \frac{T}{T_0} + \frac{mkT}{q} \ln\left(\frac{T}{T_0}\right) + \frac{kT}{q} \ln\left(\frac{J_C}{J_{C0}}\right)$$

- The junction current equals the **effective area of the base-emitter junction** times the **junction current density, J_c** :

$$I_C = A_E J_C$$

The difference between two base-emitter junctions biased at different densities (proportional to temperature):

$$\Delta V_{BE} = V_2 - V_1 = \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right)$$




Example 8.3

Ex. 8.3 Assume two trans. biased at current-density ratio of 10:1 at 300 °K. What is the difference in their base-emitter voltages and what is its temperature dependence?

likn. 8.12: $\Delta V_{BE} = \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right)$ ← eq. 8.12 p. 354
 
$$= \frac{1.38 \cdot 10^{-23} (300)}{1.602 \cdot 10^{-19}} \ln(10) = 59.5 \text{ mV}$$



$$V_{ref} = V_{BE2} + K \Delta V_{BE}$$

Since this voltage is proportional to absolute temperature, after a 1°K temp. increase, the voltage difference will be $\Delta V_{BE} = 59.5 \text{ mV} \cdot \frac{301}{300} = 59.7 \text{ mV}$

Thus, the voltage dependence is $59.5 \text{ mV}/300^\circ\text{K}$ or $0.198 \text{ mV}/^\circ\text{K}$.

Since the temperature dependence of a single V_{BE} is $-2 \text{ mV}/^\circ\text{K}$, if it is desired to cancel the temp. dependence of a single V_{BE} then ΔV_{BE} should be amplified by about a factor of 10.



Theory

- Assuming that:

$$\frac{J_i}{J_{i0}} = \frac{T}{T_0}$$

- V_{ref} can then be written as:

$$\begin{aligned} V_{ref} &= V_{BE2} + K \Delta V_{BE} \\ &= V_{G0} + \frac{T}{T_0} (V_{BE0.2} - V_{G0}) + (m-1) \frac{kT}{q} \ln\left(\frac{T_0}{T}\right) + K \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right) \end{aligned}$$

- For a given temperature V_{ref} may be independent of changes in the temperature if a proper value of K is assigned
- This (equation 8.16) is the **fundamental equation giving the relationship between the output voltage of a bandgap voltage reference and temperature.**

From V_{BE} as a function of collector current and temperature to V_{out} for BG ref. (part 1 of 2)

$$\frac{PP\ 354-355}{V_{BE} = V_{G0} \left(1 - \frac{T}{T_0}\right) + V_{BE0} \frac{T}{T_0} + \frac{mkT}{q} \ln\left(\frac{T_0}{T}\right) + \frac{kT}{q} \ln\left(\frac{J_c}{J_{c0}}\right) \quad (8.10)$$

↑ (using $\frac{J_c}{J_{c0}} = \frac{T}{T_0}$)

$$V_{BE} = V_{G0} - V_{G0} \frac{T}{T_0} + V_{BE0} \frac{T}{T_0} + \frac{mkT}{q} \ln\left(\frac{T_0}{T}\right) + \frac{kT}{q} \ln\left(\frac{T}{T_0}\right)$$

↑

$$V_{BE} = V_{G0} + \frac{T}{T_0} (V_{BE0} - V_{G0}) + \frac{mkT}{q} [\ln T_0 - \ln T] + \frac{kT}{q} [\ln T - \ln T_0]$$

↑

$$V_{BE} = V_{G0} + \frac{T}{T_0} (V_{BE0} - V_{G0}) + \frac{mkT}{q} \ln T_0 - \frac{mkT}{q} \ln T + \frac{kT}{q} \ln T - \frac{kT}{q} \ln T_0$$

↑

$$V_{BE} = V_{G0} + \frac{T}{T_0} (V_{BE0} - V_{G0}) + \frac{mkT}{q} \ln T_0 - \frac{mkT}{q} \ln T - \left(\frac{kT}{q} \ln T_0 - \frac{kT}{q} \ln T\right) \quad \left[\ln\left(\frac{T}{T_0}\right) = \ln a - \ln b = -\ln b + \ln a = -(\ln b - \ln a)\right]$$

↑

$$V_{BE} = V_{G0} + \frac{T}{T_0} (V_{BE0} - V_{G0}) + \frac{mkT}{q} \ln T_0 - \frac{mkT}{q} \ln T - \frac{kT}{q} \ln \frac{T_0}{T}$$

↑

$$V_{BE} = V_{G0} + \frac{T}{T_0} (V_{BE0} - V_{G0}) + \frac{mkT}{q} \ln \frac{T_0}{T} - \frac{kT}{q} \ln \frac{T_0}{T}$$

↑

$$V_{BE} = V_{G0} + \frac{T}{T_0} (V_{BE0} - V_{G0}) + (m-1) \frac{kT}{q} \ln \frac{T_0}{T} \Rightarrow$$

SIMILAR TO ALL BUT LAST PART OF EQ 8.16.

From V_{BE} as a function of collector current and temperature to V_{out} for BG ref. (part 2 (of 2))

$$\begin{aligned} 8.16 \quad V_{ref} &= V_{BE2} + K \Delta V_{BE} \\ &= V_{60} + \frac{T}{T_0} (V_{BE0-2} - V_{60}) + (m-1) \frac{kT}{q} \ln\left(\frac{I_0}{T}\right) \quad (8.16) \\ &\quad + K \left[\frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right) \right] \quad (\text{using 8.12}) \end{aligned}$$

This equation (8.16) is the fundamental equation giving the relationship between the output voltage of a bandgap reference and temperature.

9. februar 2010

11

UNIVERSITETET
I OSLO

Differentiating eq. 8.16 with respect to temperature, getting eq. 8.17

$$\begin{aligned} & \left[V_{60} + \frac{T}{T_0} (V_{BE0-2} - V_{60}) + (m-1) \frac{kT}{q} \ln\left(\frac{I_0}{T}\right) + K \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right) \right]' \\ &= (V_{60})' + \left(\frac{T}{T_0}\right)' (V_{BE0-2} - V_{60}) + \frac{T}{T_0} (V_{BE0-2} - V_{60})' + (m-1) \left[\frac{kT}{q} \ln\left(\frac{I_0}{T}\right) \right]' + (m-1) \left[\frac{kT}{q} \ln\left(\frac{I_0}{T}\right) \right]' \\ & \quad + \left(K \frac{kT}{q} \right)' \ln\left(\frac{J_2}{J_1}\right) + K \frac{kT}{q} \left(\ln\left(\frac{J_2}{J_1}\right) \right)' \end{aligned}$$

$y = uv, y' = u'v + uv'$
 $y = \ln x, y' = \frac{1}{x}$

$$\frac{\partial V_{ref}}{\partial T} = \left(\frac{T}{T_0}\right)' (V_{BE0-2} - V_{60}) + \underbrace{(m-1) \left[\frac{kT}{q} \ln\left(\frac{I_0}{T}\right) \right]'}_A + \underbrace{\left(K \frac{kT}{q} \right)' \cdot \ln\left(\frac{J_2}{J_1}\right)}_B$$

Noen mellomregninger: A

$$\left(\frac{T}{T_0}\right)' = \left(T \cdot \frac{1}{T_0}\right)' = 1 \cdot \frac{1}{T_0} + T \cdot 0 = \frac{1}{T_0}$$

$$\ln \frac{I_0}{T} = \ln I_0 - \ln T \quad y' = (\ln I_0)' - (\ln T)' = -\frac{1}{T}$$

$$A = (m-1) \cdot \left(\frac{kT}{q}\right)' \cdot \ln\left(\frac{I_0}{T}\right) + \frac{kT}{q} \left(\ln \frac{I_0}{T}\right)' = (m-1) \frac{k}{q} \cdot \ln\left(\frac{I_0}{T}\right) + \frac{kT}{q} \left(-\frac{1}{T}\right) = (m-1) \frac{k}{q} \cdot \ln\left(\frac{I_0}{T}\right) - \frac{k}{q}$$

$$B = \left[\left(K \frac{k}{q}\right)' \cdot T + K \frac{k}{q} \cdot T' \right] \cdot \ln\left(\frac{J_2}{J_1}\right) = K \frac{k}{q} \cdot \ln\left(\frac{J_2}{J_1}\right)$$

$$\therefore \frac{\partial V_{ref}}{\partial T} = \frac{1}{T_0} (V_{BE0-2} - V_{60}) + K \frac{k}{q} \ln\left(\frac{J_2}{J_1}\right) + (m-1) \frac{k}{q} \left[\ln\left(\frac{I_0}{T}\right) - 1 \right] \quad \text{eq. 8.17}$$

UNIVERSITETET
I OSLO

Setting equation 8.17 = 0, and $T = T_0$ getting eq. 8.18, giving the needs for zero temperature dependence at the reference temp.

$$\begin{aligned} \text{Set } \frac{\partial V_{ref}}{\partial T} &= 0 \quad \wedge \quad T = T_0 \quad \boxed{\ln 1 = 0} \\ 0 &= \frac{1}{T_0} (V_{BE0-2} - V_{BE0}) + K \frac{k}{q} \ln \left(\frac{J_2}{J_1} \right) + (n-1) \frac{k}{q} \left[\ln \left(\frac{T_0}{T_0} \right) - 1 \right] \\ 0 &= \frac{1}{T_0} (V_{BE0-2} - V_{BE0}) + K \frac{k}{q} \ln \left(\frac{J_2}{J_1} \right) + (n-1) \frac{k}{q} (-1) \\ 0 &= (V_{BE0-2} - V_{BE0}) + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) + (n-1) \frac{k T_0}{q} (-1) \\ V_{BE0-2} + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) &= V_{BE0} - (n-1) \frac{k T_0}{q} (-1) \\ V_{BE0-2} + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) &= V_{BE0} + (n-1) \frac{k T_0}{q} \quad (8.18) \end{aligned}$$

Setting $T=T_0$ in eq. 8.16 gives the left side of eq. 8.18

$$\begin{aligned} \text{8.16 : } V_{ref} &= V_{BE2} + K \Delta V_{BE} \\ &= V_{BE0} + \frac{T}{T_0} (V_{BE0-2} - V_{BE0}) + (n-1) \frac{kT}{q} \ln \left(\frac{T_0}{T_0} \right) + K \frac{kT}{q} \ln \left(\frac{J_2}{J_1} \right) \\ \text{Letting } T &= T_0 : \\ V_{ref} &= V_{BE0} + \frac{T_0}{T_0} (V_{BE0-2} - V_{BE0}) + (n-1) \frac{k T_0}{q} \ln \left(\frac{T_0}{T_0} \right) + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) \\ &= V_{BE0} + (V_{BE0-2} - V_{BE0}) + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) \\ &= V_{BE0-2} + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) \end{aligned}$$

For $T=T_0$, the left side of eq. 8.18 equals the result above.

$$\text{8.18 ; } \quad \underline{V_{BE0-2} + K \frac{k T_0}{q} \ln \left(\frac{J_2}{J_1} \right) = V_{BE0} + (n-1) \frac{k T_0}{q}}$$

For zero temperature dependence at $T=T_0$. At **300 K** (8.18, 8.19, 8.20):

$$V_{\text{beo-2}} + K \frac{kT_0}{q} \ln\left(\frac{J_2}{J_1}\right) = V_{\text{beo}} + (m-1) \frac{kT_0}{q} \quad (8.18) \quad \begin{array}{l} [^{\circ}\text{C}] = [\text{K}] - 273.15 \\ 300[\text{K}] - 273.15[\text{K}] \\ \approx 27^{\circ}\text{C} \end{array}$$

The left side of eq 8.18 is the output voltage V_{ref} at $T=T_0$ (as we have shown).

For zero temperature dependence at $T=T_0$, we need

$$V_{\text{ref-0}} = V_{\text{beo}} + (m-1) \frac{kT_0}{q} \quad (8.19)$$

For the special case of $T_0 = 300\text{ K}$ and $m = 2.3$ (8.19) implies that, for zero temperature dependence

$$\begin{aligned} V_{\text{ref-0}} = V_{\text{beo}} &= 1.206\text{ V} + (2.3-1) \cdot \frac{1.38 \times 10^{-23} (300)}{1.602 \times 10^{-19}} \\ &= 1.206\text{ V} + 1.3 \times 25.8\text{ mV} \\ &= \underline{1.24\text{ V}} \end{aligned}$$

Note that this value is independent of the current densities chosen.



UNIVERSITETET
I OSLO

Required value for K at 300K (eq. 8.21):

From eq (8.20) we got $V_{\text{ref-0}} = 1.24\text{ V}$ for zero temp. dependence at 300K. This value is independent of the current densities chosen.

K from equation 8.18:

$$K = \frac{V_{\text{beo}} + (m-1) \frac{kT_0}{q} - V_{\text{beo-2}}}{\frac{kT_0}{q} \ln\left(\frac{J_2}{J_1}\right)} = \frac{1.24\text{ V} - V_{\text{beo-2}}}{25.8\text{ mV} \cdot \ln\left(\frac{J_2}{J_1}\right)}$$

The output of a bandgap reference is given by the bandgap voltage, V_{beo} , plus a small correction to account for 2nd-order effects.




UNIVERSITETET
I OSLO

Output voltage for temperatures different from the reference; get (8.22) and then differentiate ...

The fundamental equation giving the relationship between the output voltage of a bandgap reference and temperature is equation 8.16, page 355:

$$V_{ref} = V_{BE2} + K \Delta V_{BE}$$
 
$$= V_{60} + \frac{T}{T_0} (V_{BE0-2} - V_{60}) + (m-1) \frac{kT}{q} \ln\left(\frac{T_0}{T}\right) + K \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right)$$



The output voltage of the reference for temperatures different from the reference is found after backsubstituting (8.18) and (8.19) into (8.16) and some manipulation:

$$V_{ref} = V_{60} + (m-1) \frac{kT}{q} \left[1 + \ln\left(\frac{T_0}{T}\right) \right] \quad (8.22)$$

ifi

UNIVERSITETET
I OSLO

(8.22) differentiated with respect to T, getting (8.23):

Differentiating 8.22: $\log_a\left(\frac{u}{v}\right) = \log_a u - \log_a v$ $y = uv$ $y' = u'v + uv'$ $y = \ln x$ $y' = \frac{1}{x}$

$$\frac{\partial V_{ref}}{\partial T} = (V_{60})' + \underbrace{\left[(m-1) \frac{kT}{q} \right]'}_u \underbrace{\left[1 + \ln\left(\frac{T_0}{T}\right) \right]}'_v + \underbrace{(m-1) \frac{kT}{q}}_u \underbrace{\left[1 + \ln\left(\frac{T_0}{T}\right) \right]}'_{v'}$$

$$= (m-1) \frac{k}{q} \left[1 + \ln\left(\frac{T_0}{T}\right) \right] + (m-1) \frac{kT}{q} \cdot \left(-\frac{1}{T} \right)$$

$$= \text{---} \parallel \text{---} + (-m+1) \frac{k}{q}$$

$$= \text{---} \parallel \text{---} \div (m-1) \frac{k}{q}$$

$$= (m-1) \frac{k}{q} \left[1 + \ln\left(\frac{T_0}{T}\right) - 1 \right] = (m-1) \frac{k}{q} \ln\left(\frac{T_0}{T}\right) \quad (8.23)$$

Equations 8.22 and 8.23 may be used to estimate the temperature dependence at temperatures different from the reference temperature

ifi

UNIVERSITETET
I OSLO

Example 8.4

Ex. 8.4 Estimate the temperature dependence at 0°C
p. 757 for a bandgap reference that was designed
to have zero temperature dependence at 20°C.
Present the result as ppm/°K.

Using eq. 8.23 :
$$\frac{\partial V_{ref}}{\partial T} = (n-1) \frac{k}{q} \ln\left(\frac{T_0}{T}\right)$$

°K corresponds to -273°C. $T_0 = 293\text{°K}$, $T = 273\text{°K}$

$$\frac{\partial V_{ref}}{\partial T} = (2.3-1) \frac{1.38 \cdot 10^{-23}}{1.6 \cdot 10^{-19}} \ln\left(\frac{293}{273}\right) \left[\frac{\mu\text{V}}{\text{°K}}\right] = 8 \mu\text{V}/\text{°K}$$


For a reference voltage of 1.24 V, a dependency of
8 $\mu\text{V}/\text{°K}$ results in $\frac{8 \mu\text{V}/\text{°K}}{1.24 \text{ V}} = 6.5 \cdot 10^{-6}$ parts/°K

$$= 6.5 \text{ ppm}/\text{°K}$$

"ppm": parts per million


NB! Ideally: 0 ppm/°K, typically $4 \cdot 10 \times$ the
value here.

CMOS Bandgap References

 

- Vertical CMOS well transistors in an n-well and p-well process (pnp in -well, npn in p-well)

CMOS BGR Circuits

 

- CMOS bandgap references implemented with well transistors



Design equations, BG ref.

DESIGN EQUATIONS

The voltage drop due to I_1 :

$$V_{ref} = V_{EB1} + V_{R1} \quad (8.35)$$

Since $V_{R1} = V_{R3}$, assuming an ideal op-AMP:

$$V_{R2} = V_{EB1} - V_{EB2} = \Delta V_{EB} \quad (8.26)$$

I_2 runs through both R_2 and R_3 , so that

$$(8.37) \quad V_{R3} = \frac{R_3}{R_2} V_{R2} = \frac{R_3}{R_2} \Delta V_{EB} \quad (V_{R2} = \Delta V_{EB})$$

Substituting (8.37) into (8.35):

$$V_{ref} = V_{EB1} + V_{R1} = V_{EB1} + V_{R3} = V_{EB1} + \frac{R_3}{R_2} \Delta V_{EB} \quad (8.38)$$


In integrated realizations the bipolar transistors are often taken the same size, and different current densities are realized by taking $R_3 > R_1$, causing $I_1 > I_2$. In this case

$$\frac{I_1}{I_2} = \frac{R_3}{R_1} \quad (8.39)$$


Recalling from 8.12 that $\Delta V_{EB} = V_{EB1} - V_{EB2} = \frac{kT}{q} \ln \frac{I_1}{I_2} \quad (8.40)$

$$(8.39) \text{ into } (8.38): V_{ref} = V_{EB1} + \frac{R_3}{R_2} \frac{kT}{q} \ln \left(\frac{R_3}{R_1} \right) \quad K = \frac{R_3}{R_2} \quad (8.42)$$

FIG. 8.27

 
 
$$\ln x = \frac{x}{1.6} - 0.5 \ln \frac{1}{x} + 0.12 \ln x$$




Design Equations

$$V_{\text{ref}} = V_{\text{EB1}} + V_{\text{R1}}$$

$$V_{\text{R2}} = V_{\text{EB1}} - V_{\text{EB2}} = \Delta V_{\text{EB}}$$

$$V_{\text{R3}} = \frac{R_3}{R_2} V_{\text{R2}} = \frac{R_3}{R_2} \Delta V_{\text{EB}}$$
 
$$V_{\text{ref}} = V_{\text{EB1}} + \frac{R_3}{R_2} \Delta V_{\text{EB}}$$




Design Equations

$$\frac{J_1}{J_2} = \frac{R_3}{R_1}$$

$$\Delta V_{\text{EB}} = V_{\text{EB1}} - V_{\text{EB2}} = \frac{kT}{q} \ln\left(\frac{J_1}{J_2}\right)$$


$$V_{\text{ref}} = V_{\text{EB1}} + \frac{R_3 kT}{R_2 q} \ln\left(\frac{R_3}{R_1}\right)$$

$$K = \frac{R_3}{R_2}$$

 

 EXAMPLE 8.5

Find the resistances of a bandgap reference based on fig. 8.27 a), where $I_1 = 80 \mu\text{A}$, $I_2 = 8 \mu\text{A}$, and $V_{EB1-0} = 0.65\text{V}$ at $T = 300^\circ\text{K}$



Assuming that the sizes of Q_1 and Q_2 are the same

$$\Delta V_{EB} = \frac{kT_0}{q} \ln \frac{I_1}{I_2} = \frac{kT_0}{q} \cdot 2.30259 = 59.4 \text{ mV}$$

$$R_2 = \frac{V_{R2}}{I_2} = 7.44 \text{ k}\Omega = \frac{59.4 \text{ mV}}{8 \mu\text{A}}$$

From (8.20) we know that $V_{ref-0} = 1.24 \text{ V}$ at $T_0 = 300^\circ\text{K}$

From (8.35) we get $V_{R1} = V_{ref-0} - V_{EB1-0} = 1.24\text{V} - 0.65\text{V}$

$$\underline{V_{R1} = 0.59 \text{ V}} \quad \underline{R_1 = \frac{0.59 \text{ V}}{80 \mu\text{A}} = 7.38 \text{ k}\Omega}, \quad \underline{R_3 = \frac{0.59 \text{ V}}{8 \mu\text{A}} = 73.8 \text{ k}\Omega}$$

ifi

UNIVERSITETET
I OSLO

Example 8.5 (2)

$V_{R2} = \Delta V_{EB} = \frac{kT}{q} \ln(10)$, since the sizes of Q_1 and Q_2 are assumed to be the same. (equations 8.36 and 8.40)

$$\therefore V_{R2} = \frac{1.38 \cdot 10^{-23}}{1.62 \cdot 10^{-19}} (300) \cdot \ln(10) = 59.5 \text{ mV} \quad (V_{R2} = \Delta V_{EB})$$

$$U = RI \Rightarrow R = \frac{59.5 \text{ mV}}{8 \mu\text{A}} = 7.44 \text{ k}\Omega \quad \underline{R_2 = 7.44 \text{ k}\Omega}$$

Remember from 8.20 that for 300°K and $m = 2.3$, (8.19) implies that $V_{ref-0} = V_{e0} + (m-1) \frac{kT_0}{q} = 1.24 \text{ V}$ ($V_{e0} = 1206 \text{ mV}$)

Then we can get K from (8.21):

$$K = \frac{V_{e0} + (m-1) \frac{kT_0}{q} - V_{EB1-0}}{\frac{kT_0}{q} \ln\left(\frac{I_1}{I_2}\right)} = \frac{1.24 \text{ V} - 0.65 \text{ V}}{0.0258 \ln(10)} = 9.93$$

$$8.42 \text{ say that } K = \frac{R_3}{R_2} \Rightarrow \underline{R_3 = K \cdot R_2 = 73.9 \text{ k}\Omega}$$

$$8.39: \frac{I_1}{I_2} = \frac{R_3}{R_1} \left(= \frac{I_1}{I_2} \right) \Rightarrow \frac{R_3}{R_1} = \frac{8 \mu\text{A}}{80 \mu\text{A}} \Rightarrow R_1 = \frac{R_3}{10} = \underline{7.39 \text{ k}\Omega}$$

ifi

UNIVERSITETET
I OSLO




9. februar 2010 27



ifi  UNIVERSITETET I OSLO

Chapetr 9; Discrete-time signals

- Discrete-time signal processing is heavily used in the design and analysis of **oversampling A/D and D/A converters** as well as **switched capacitor filtering** ;"SC-circuits".
- Switched Capacitor filters are classified as analog, since they use continuous time analog values.

ifi  UNIVERSITETET I OSLO

  
Overview of signal spectra – conceptual and physical realizations



- An **anti-aliasing** filter (not shown) is assumed to band limit the continuous time signal, $x_c(t)$.
- **DSP** ("discrete-time signal processing") may be accomplished using fully digital processing or discrete-time analog circuits (ex.: SC-circ.).




Signals in time, and frequency spectra

 

- $S(t)$: periodic impulse train with period T ($T=1/f_s$)
- $x_s(t)$ has the same frequency spectrum as $x_c(t)$, but the baseband spectrum repeats every f_s (assuming no aliasing)
- $x(n)$ has the same frequency spectrum as $x_c(t)$, but the sampling frequency is normalized to 1
- The frequency spectrum of $x_{sh}(t)$ is equal to that of $x_s(t)$ multiplied by the $\sin(x)/x$ response of the S/H.



 Laplace Transform of Discrete-Time Signals (1/3)



- The signal must be defined for all time
- For $t=nT$:

$$x_s(nT) = \frac{x_c(nT)}{\tau}$$
- τ is chosen such that the area under $x_s(nT)$ equals the value of $x_c(nT)$
- As τ approaches 0, the height of $x_s(nT)$ goes to ∞



Laplace Transform of Discrete-Time Signals (2/3)

- A single pulse at $t=nT$ may be defined as:

• $g(t)$ is the step function:
$$g(t) \equiv \begin{cases} 1 & (t \geq 0) \\ 0 & (t < 0) \end{cases}$$

- $x_s(t)$ may then be rewritten as a linear combination of a series of pulses, $x_{sn}(t)$, where $x_{sn}(t)$ is zero everywhere except for a single pulse at nT :

$$x_{sn}(t) = \frac{x_c(nT)}{\tau} [g(t-nT) - g(t-nT-\tau)]$$

$x_s(t)$ is now defined for all time:

$$x_s(t) = \sum_{n=-\infty}^{\infty} x_{sn}(t)$$



Laplace Transform of Discrete-Time Signals (3/3)

- The Laplace transform for $x_{sn}(t)$ is:

$$X_{sn}(s) = \frac{1}{\tau} \left(\frac{1 - e^{-s\tau}}{s} \right) x_c(nT) e^{-snT}$$

- Since there is a linear relationship between $x_s(t)$ and $x_{sn}(t)$, the Laplace transform of $x_s(t)$ is:

$$X_s(s) = \frac{1}{\tau} \left(\frac{1 - e^{-s\tau}}{s} \right) \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT}$$

- When τ approaches 0, the term before the sum equals 1 (eq. 9.7):

$$X_s(s) = \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT} \quad z \equiv e^{sT}$$

$$X(z) = \sum_{n=-\infty}^{\infty} x_c(nT) z^{-n}$$



UNIVERSITETET
I OSLO

Spectra of Discrete-Time Signals (1/2)

- The frequency spectrum of $x_s(t)$ may be found by replacing s by $j\omega$ in the Laplace transform (eq. 9.7).
- Another more intuitive approach is to use the property that **multiplication in the time domain equals convolution in the frequency domain**. Using this and $\tau \rightarrow 0$, $X_s(t)$ can be rewritten

$$x_s(t) = x_c(t)s(t)$$

- Define a pulse-train:

- The sampled signal is now: $s(t) = \sum_{n=-\infty}^{\infty} \delta(t - nT)$

- The Fourier-transform of $s(t)$ is: $S(j\omega) = \frac{2\pi}{T} \sum_{k=-\infty}^{\infty} \delta(\omega - k\frac{2\pi}{T})$



UNIVERSITETET
I OSLO

Spectra of Discrete-Time Signals ^(2/2)

- Writing (9.8) in the frequency domain:

$$X_s(j\omega) = \frac{1}{2\pi} X_c(j\omega) \otimes S(j\omega)$$

- The frequency spectrum of $x_s(t)$ is then (eq. 9.12):

$$X_s(j\omega) = \frac{1}{T} \sum_{k=-\infty}^{\infty} X_c(j\omega - \frac{jk2\pi}{T})$$


which is periodic with period f_s (9.13:).

No aliasing occurs if $f < f_s/2$

$$X_s(f) = \frac{1}{T} \sum_{k=-\infty}^{\infty} X_c(j2\pi f - jk2\pi f_s)$$



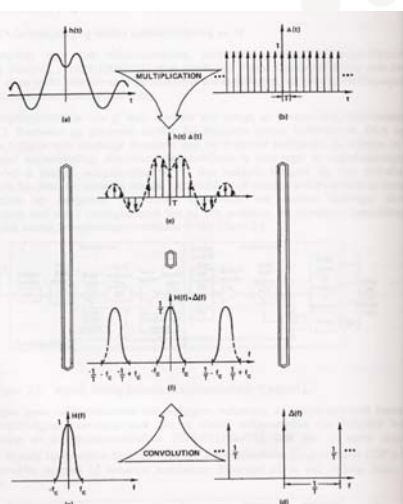Multiplication in the time domain equals convolution in the frequency domain




Figur 2.7: Sammenhengen mellom sampling i tids- og frekvensdomenet. Produktet av $h(t)$, figur 2.7 a), og $\Delta(t)$, i figur b), er lik den samplede kurveformen i figur c). Fouriertransformene av $h(t)$ og $\Delta(t)$ er gitt i henholdsvis figur 2.7 c) og d). Frekvenskonvolusjonssteoretet er illustrert ved at Fouriertransformen av $h(t)\Delta(t)$ er lik $h(f)\Delta(f)$ [Brig74].

- Figure from E. O. Brigham: "The Fast Fourier Transform", Prentice Hall Inc., 1974., in S. Aunet: "BiCMOS sample-and-hold for satellitt-kommunikasjon", Cand. Scient. Thesis, University of Oslo, 1993.
- Wikipedia; Convolution:
- In [mathematics](#) and, in particular, [functional analysis](#), **convolution** is a mathematical [operation](#) on two [functions](#) f and g , producing a third function that is typically viewed as a modified version of one of the original functions. Convolution is similar to [cross-correlation](#).
- Computing the inverse of the convolution operation is known as [deconvolution](#).
- In [mathematics](#), the **Fourier transform** (often abbreviated **FT**) is an operation that [transforms](#) one [complex-valued function](#) of a [real variable](#) into another. In such applications as [signal processing](#), the domain of the original function is typically [time](#) and is accordingly called the [time domain](#). That of the new function is [frequency](#), and so the Fourier transform is often called the [frequency domain representation](#) of the original function. It describes which frequencies are present in the original function.




Sampling at different frequencies

2.2 Signaler i tids- og frekvensdomenet, for ulike samplingsfrekvenser

 

Figur 2.4: Sampling ved ulike frekvenser, sett i tidsdomenet. f_s er samplingsfrekvensen, også kalt samplingsraten, mens f_a er frekvensen for det analoge signalet som samples. [Kest91].

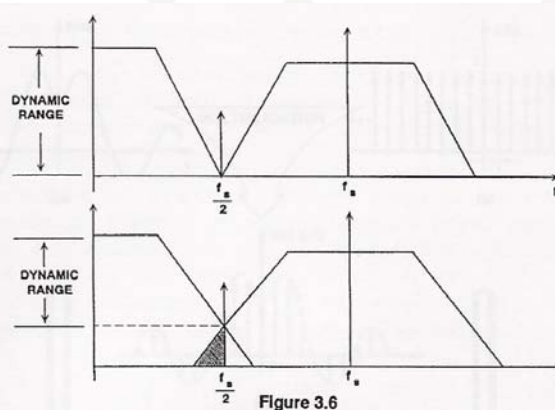Aliasing and potential degrading of signal / noise



Figur 2.6: Aliasing og dynamisk område [Kest91] I det øverste tilfellet samples det slik at det dynamiske området beholdes. I det andre tilfellet overlapper frekvensspektrerne slik at dynamisk område, eller signal/støy -forhold, reduseres.

Z-Transform

- Discrete-time systems are most often analyzed using the z-transform which is equivalent to the Laplace-transform with the following substitution:

- Then the z-transform is defined as :

$$z \equiv e^{sT}$$

$$X(z) \equiv \sum_{n=-\infty}^{\infty} x_c(nT)z^{-n}$$



Z-Transform

- Two important properties of the z-transform:
 - 1) If $x(n) \leftrightarrow X(z)$, then $x(n-k) \leftrightarrow z^{-k}X(z)$
 - 2) Convolution in the time-domain is equal to multiplication in the freq. domain (If $y(n)=h(n) \otimes x(n)$, then $Y(z) = H(z)X(z)$. Similarly, multiplication in the time-domain equals convolution in the frequency domain
 - $X(z)$ is only related to the sampled sequence of numbers, while $X_s(s)$ is the Laplace transform of $x_s(t)$ when $\tau \rightarrow 0$
 - The frequency response of $X_s(f)$ is related to $X(\omega)$ the following way:

$$X_s(f) = X\left(\frac{2\pi f}{f_s}\right)$$

- Thus, the following scaling has been applied:

$$\omega = \frac{2\pi f}{f_s}$$






Z-Transform

- Important observation:
 - Discrete-time signals have ω in units of radians/sample
 - The original continuous-time signal have frequency units of cycles/second (Hertz) or radians / second. (2π Radians \sim 360 degrees)
- Example:
 - A continuous-time sinusoidal signal of 1kHz when sampled at 4 kHz will change by $\pi/2$ radians between each sample. In such case the discrete time signal is defined to have a frequency of $\pi/2$ radians per sample

Next time, Tuesday 16th of February

  - Chapter 9; 9.4 – 9.6
- Chapter 10; Switched Capacitor Circuits






ifi

Discrete Time Signals and Switched Capacitor Circuits
(rest of chapter 9 + 10.1, 10.2)

Tuesday 16th of February, 2010


Snorre Aunet, sa@ifi.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

 UNIVERSITETET
I OSLO


Last time – Tuesday 9th of February, and today, February the 16th:

- 8.5 Bandgap Voltage Reference Basics
- 8.6 Circuits for Bandgap References
- Chapter 9 Discrete-Time Signals
- 9.1 Overview of some signal spectra
- 9.2 Laplace Transforms of Discrete-Time Signals

- 9.2 -9.6
- 10.1-10.2 (10.3((?)))

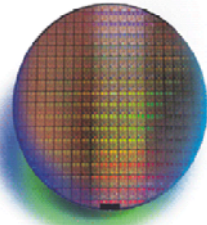

ifi

 UNIVERSITETET
I OSLO

9.2 LAPLACE - TRANSFORM OF DISCRETE TIME SIGNALS

The sampled signal, $x_s(t)$ is related to the continuous-time signal, $x_c(t)$, as shown in Fig. 9.3.

Conceptual (See fig. 9.1)


 



Fig. 9.3:

 


In Fig. 9.3 $x_s(t)$ is scaled by $\frac{1}{T}$ such that the area under the pulse equals the value of $x_c(nT)$.

At $t = nT$ we then have $x_s(nT) = \frac{x_c(nT)}{T}$ such that the area

Fig. 9.2:

 

 under the pulse, $\int x_s(t) dt$, equals $x_c(nT)$. As $T \rightarrow 0$, the height of $x_s(t)$ at time nT goes to ∞ .



The single-pulse signal, $x_{sn}(t)$, can be written

$$x_{sn}(t) = \frac{x_c(nT)}{T} [\psi(t-nT) - \psi(t-nT-T)]$$

see that we can now write $x_s(t)$ as


$$x_s(t) = \sum_{n=-\infty}^{\infty} x_{sn}(t)$$

$\int x_s(t)$ plotted

$\psi(t)$ is defined to be the step function given by

$$\psi(t) = \begin{cases} 1 & (t \geq 0) \\ 0 & (t < 0) \end{cases}$$

 $x_s(t)$ can be represented as a linear combination of a series of pulses, $x_{sn}(t)$, where $x_{sn}(t)$ is zero everywhere except for a single pulse at nT .



These signals are defined for all time so that the LAPLACE-transform may be found for $x_s(t)$ in terms of $x_c(t)$.

Laplace transform $X_{sn}(s)$

for $x_{sn}(t)$:

$$X_{sn}(s) = \frac{1}{T} \left(\frac{1 - e^{-sT}}{s} \right) x_c(nT) e^{-snT}$$

Since $x_s(t)$ is a linear combination of $x_{sn}(t)$, we also have

$$X_s(s) = \frac{1}{T} \left(\frac{1 - e^{-sT}}{s} \right) \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT}$$

When $T \rightarrow 0$ the term before the summation goes to unity, so in this case:

(eq 9.7):
$$X(s) = \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT}$$

pp. 376

SPECTRA OF DISCRETE-TIME SIGNALS

↳ **convolution**

9.97:
$$X_s(s) = \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT}$$

The spectrum of the sampled signal, $x_s(t)$, can be found by replacing s by $j\omega$ in (9.7).

A more intuitive approach is to recall that **if $y(n) = h(n) \otimes x(n)$, then $Y(z) = H(z) \cdot X(z)$**

Using this fact, for $T \rightarrow 0$, $x_s(t)$ can be written as the product

$$x_s(t) = x_c(t) s(t) \quad (9.8)$$

where $s(t)$ is a periodic pulse train, or

$$s(t) = \sum_{n=-\infty}^{\infty} \delta(t - nT)$$

where $\delta(t)$ is the impulse function (Dirac delta func.)

It is well known that the Fourier transform of a periodic impulse train is another periodic impulse train.

$$(9.10) \quad S(j\omega) = \frac{2\pi}{T} \sum_{k=-\infty}^{\infty} \delta(\omega - k \frac{2\pi}{T})$$

(spectrum of $s(t)$)

Writing (9.8) in the frequency domain:

$$(9.11) \quad X_s(j\omega) = \frac{1}{2\pi} x_c(j\omega) \otimes S(j\omega)$$

UNIVERSITET I OSLO

$$X_s(j\omega) = \frac{1}{2\pi} X_c(j\omega) \otimes S(j\omega)$$

By performing this convolution either mathematically or graphically, the spectrum of $X_s(j\omega)$ can be seen to be given by

$$X_s(j\omega) = \frac{1}{T} \sum_{k=-\infty}^{\infty} X_c(j\omega - jk\frac{2\pi}{T}) \quad (9.12)$$

or equivalently

$$X_s(f) = \frac{1}{T} \sum_{k=-\infty}^{\infty} X_c(j2\pi f - jk2\pi f_s) \quad (9.13)$$

9.12 and 9.13 show that the spectrum for the sampled signal, $x_s(t)$, equals a sum of shifted spectra of $x_c(t)$. No aliasing occurs if $X_c(j\omega)$ is bandlimited to $\frac{f_s}{2}$.

Figur 2.10: Grafisk fremstilling av sampling, i tids- og frekvensdomenet.

(9.13) confirms the example spectrum for $X_s(f)$, shown in Fig. 9.2.

Note that, for a discrete-time signal, $X_s(f) = X_c(f + kf_s)$, where k is an arbitrary integer as seen by substitution in (9.13).

9.3 Z-TRANSFORM pp 377 in J&M⁴

(9.7): $X(z) = \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT} \quad \wedge \quad z = e^{sT}$

(9.15) $X(z) \equiv \sum_{n=-\infty}^{\infty} x_c(nT) z^{-n}$; the z-transform of the samples $x_c(nT)$

TWO PROPERTIES, deduced from Laplace-tr. properties:

- 1) If $x(n) \leftrightarrow X(z)$ then $x(n-k) \leftrightarrow z^{-k} \cdot X(z)$
- 2) Conv. in the time domain equals mult. in the freq domain
 Mult. ——— || ——— || ——— || ——— || ———
 If $y(n) = h(n) \otimes x(n)$ then $Y(z) = H(z) \cdot X(z)$


Note that $X(z)$ is not a function of the sampling rate but only to the numbers $x_c(nT)$.

The signal $x(n)$ is simply a series of numbers that may (or may not) have been obtained by sampling

" $x(n)$ is simply a series of numbers..." (p. 377)

One way of thinking about this series of numbers is that the original sample time, T , has been effectively normalized to 1.

 The scaling justifies the spectral relation between $X_s(f)$ and $X(\omega)$ shown in Fig. 9.2



Relationship between $X_s(f)$ and $X(\omega)$:

~~$X_s(f) = \frac{2\pi f}{f_s}$~~ (9.16)

Alternatively:

$$\omega = \frac{2\pi f}{f_s}$$

At Nyquist rate:


$$\omega = \frac{2\pi f}{f_s} = \frac{2\pi f}{2f} = \pi \left[\frac{\text{radians}}{\text{Sample}} \right]$$

f : cycles/second (Hz)

ω : radians/sample


See fig. 9.4

 Normally discrete-time signals are defined to have frequency components only between $-\pi$ and π rad/sample




$f = 1 \text{ kHz}$, $f_s = 4 \text{ kHz}$

 
The signal changes $\frac{\pi}{2}$ radians between each sample. Such a discrete-time signal is defined to have a frequency of $\frac{\pi}{2}$ rad/sample




0 rad/sample = 0 cycles/sample

 

 $\pi/8$ rad/sample = $1/16$ cycles/sample



$\pi/4$ rad/sample = $1/8$ cycles/sample

 

$\pi/2$ rad/sample = $1/4$ cycles/sample


Note: Discrete-time signals are not unique since the addition of 2π results in the same signal.

(For example, a discrete-time signal having a freq. of $\frac{\pi}{4}$ rad/sample is identical to that of $\frac{9\pi}{4}$ rad/sample)

 9.4 Downsampling AND Upsampling

Downsampling to reduce the sample rate (without inform. loss)
 Upsampling to increase — L —.

Downsampling:
 achieved by
 keeping every
 L th sample and
 discarding the
 others.




Noninteger
 rates can be
 achieved, but
 here L being
 integer is
 considered only.

FREQUENCY DOMAIN:



original spectra expanded by L :



 


(See
 fig. 9.6
 pp. 379)

SIGNAL MUST
 BE BAND
 LIMITED TO $\frac{\pi}{L}$
 BEFORE DOWNS.
 TO AVOID
 ALIASING


Upsampling - increasing the effective f_s (pp 379)

   Upsampling is accomplished by inserting $L-1$ zero values
 between samples (as shown in fig. 9.7)



- The spectra of the resulting upsampled signal are identical to the original signal but with a renormalization along the frequency axis.
- When a signal is upsampled by L , the frequency axis is scaled by L such that 2π now occurs where $L2\pi$ occurred in the original signal.

 9.5 Discrete-Time Filters (pp. 382 in "J&M")



- An input series of numbers is applied to a filter to create a **modified output series of numbers**
- Discrete-time filters are most often **analyzed and visualized in terms of the z-transform**
- In this figure (Fig. 9.9) the output signal is defined to be the impulse response, $h(n)$, when the input, $u(n)$, is an impulse (i.e. 1 for $n = 0$ and 0 otherwise. **Transfer function; $H(z)$ being the z-transform of the impulse response, $h(n)$.**



UNIVERSITETET
I OSLO

Continuous time LP-filter

pp 382 "Johns & Martin"


The transfer function for discrete-time filters appear similar to those for continuous-time filters, except that, instead of polynomials in s , polynomials in z are obtained. For example, the transfer function of a low-pass, continuous time filter, $H_c(s)$ might appear as

$$H_c(s) = \frac{4}{s^2 + 2s + 4}$$

$$s = \frac{-2 \pm \sqrt{2^2 - 4 \cdot 1 \cdot 4}}{2 \cdot 1} = \frac{-2 \pm \sqrt{-3 \cdot 4}}{2} = \frac{-2 \pm 2\sqrt{-3}}{2}$$

$$s = -1 \pm j\sqrt{3}, \text{ roots of the denominator.}$$

 $ax^2 + bx + c$
 $x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$



This LP-filter is also defined to have to zeros at ∞ since the denominator polynomial is two orders higher than the numerator polynomial. To find the frequency response of $H_c(s)$ the poles and zeros may be plotted (Fig. 9.10 a)

1


14

TETET

Discrete-Time Transfer Function

- Assume the following (LP-) transfer function:

 
$$H(z) = \frac{0,05}{z^2 - 1,6z + 0,65}$$



- Poles:** Complex conjugated at $0.8 \pm 0.1j$
- Zeros:** **Two zeros at infinity** (Defined). The number of zeros at infinity reflects the difference in order between denominator and nominator
- In the discrete time somain $z=1$ corresponds to the freq. response at both **dc** ($\omega=0$) and $\omega = 2\pi$.
- The frequency respons need only be plotted for $0 \leq \omega \leq \pi$ (frequency response repeats every 2π).
- The unit circle, $e^{j\omega}$, is used to determine the frequency response of a system that has it's input and output as a series of numbers.
- (The magnitude is represented by the product of the lengths of the zero-vectors divided by the product of the lengths of the pole-vectors).
- The phase is calculated using addition and subtraction)




Frequency response

 

- The frequency **response of discrete-time filters are similar to the response of continuous-time filters**. The poles and zeroes are located in the z-plane instead of the s-plane
- DC/ 2π equals $z=1$, $fs/2$ equals $z=-1$
- The response is periodic with period 2π



Stability of Discrete-Time Filters

 

- The filters are described by finite difference equations

$$y(n+1) = bx(n) + ay(n)$$

- In the z-domain:

$$zY(z) = bX(z) + aY(z)$$

$$H(z) = \frac{Y(z)}{X(z)} = \frac{b}{z-a}$$

- $H(z)$ has a pole in $z=a$. $a \leq 1$ to ensure stability
- In general a LTI system is stable if all the poles are located inside or on the unit circle



Test for stability

- Let the input, $x(n)$ be an impulse signal (i.e. 1 for $n=0$, and 0 otherwise), which gives the following output signal, according to 9.25, $y(0) = k$, where k is some arbitrary initial state for y .
- $y(n+1) = bx(n) + ay(n)$
- $y(0+1) = b x(0) + a y(0) = b \cdot 1 + ak = b + ak$,
- $y(2) = b x(1) + a y(1) = b \cdot 0 + a(b + ak) = ab + a^2k$
- $y(3) = b x(2) + a y(2) = b \cdot 0 + a(ab + a^2k) = a^2b + a^3k$
- $y(4) = a^3b + a^4k$
- Response, $h(n) = 0$ for $(n < 0)$,
- k for $(n=0)$
- $(a^{n-1}b + a^n k)$ for $n \geq 1$
- This response remains bounded only when $|a| \leq 1$ for this 1st order filter, and unbounded otherwise.
- In general, an arbitrary, time invariant, discrete time filter, $H(z)$, is stable if, and only if, all its poles are located within the unit circle.



IIR and FIR Filters

- **Infinite Impulse Response (IIR)** filters are discrete-time filters whose outputs remain non-zero when excited by an impulse:
 - Can be more efficient
 - Finite precision arithmetic may cause limit-cycle oscillations
- **Finite Impulse Response (FIR)** filters are discrete-time filters whose outputs goes precisely to zero after a finite delay:
 - Poles only in $z=0$
 - Always stable
 - Exact linear phase filters may be designed
 - High order often required



UNIVERSITETET
I OSLO

Bilinear transform

Bilinear transform

In many cases it is desirable to convert a continuous-time filter into a discrete-time filter or vice versa.

Assuming that $H_c(p)$ is a continuous time transfer function (where p is the complex variable equal to $\sigma_p + j\Omega$), the bilinear transform is defined to be given by

$$p = \frac{z-1}{z+1}$$

Finding the inverse transformation:

$$\begin{aligned} p(z+1) &= z-1 & z &= \frac{-(p+1)}{p-1} \\ p z + p &= z-1 & z &= \frac{-(1+p)}{p-1} \\ p z - z &= -1-p & z &= \frac{-(1+p)}{p-1} \\ z(p-1) &= -1-p & z &= \frac{1+p}{1-p} \\ z &= \frac{-(p+1)}{p-1} & z &= \frac{1+p}{1-p} \end{aligned}$$

z -plane locations of 1 and -1 (i.e. dc and $f_s/2$) are mapped to p -plane locations of 0 and ∞ , respectively.

The bilinear transform also maps the unit circle, $z = e^{j\omega}$ in the z -plane to the entire $j\Omega$ -axis in the p -plane. To see the mapping:

$$p = \frac{e^{j\omega} - 1}{e^{j\omega} + 1} = \frac{e^{j\frac{\omega}{2}}(e^{j\frac{\omega}{2}} - e^{-j\frac{\omega}{2}})}{e^{j\frac{\omega}{2}}(e^{j\frac{\omega}{2}} + e^{-j\frac{\omega}{2}})}$$

$$= \frac{2j \sin(\frac{\omega}{2})}{2 \cos(\frac{\omega}{2})} = j \tan(\frac{\omega}{2})$$

Points on the unit circle in the z -plane are mapped to locations on the $j\Omega$ -axis in the p -plane, and we have $\Omega = \tan(\omega/2)$.

$$\begin{aligned} \cos \theta &= \frac{e^{j\theta} + e^{-j\theta}}{2} \\ \sin \theta &= \frac{e^{j\theta} - e^{-j\theta}}{2j} \end{aligned}$$



ET

Bilinear Transform

- In many cases it is desirable to convert a continuous-time filter into a discrete-time filter or vice-versa.
- $H_c(p)$ is a CT transfer function with $p = \sigma_p + j\Omega$. Then

$$p = \frac{z-1}{z+1} \quad z = \frac{1+p}{1-p}$$

- The bilinear transforms map the z-plane locations of 1 (DC) and -1 (fs/2) to the p-plane locations 0 and ∞ .



Bilinear Transform

- The unit-circle $z = e^{j\omega}$ in the z-plane is mapped to the entire $j\Omega$ -axis in the p-plane:

$$\begin{aligned} p &= \frac{e^{j\omega} - 1}{e^{j\omega} + 1} = \frac{e^{j(\omega/2)}(e^{j(\omega/2)} - e^{-j(\omega/2)})}{e^{j(\omega/2)}(e^{j(\omega/2)} + e^{-j(\omega/2)})} \\ &= \frac{2j \sin(\omega/2)}{2 \cos(\omega/2)} = j \tan(\omega/2) \end{aligned}$$

- The following frequency mapping occurs:

$$\Omega = \tan(\omega/2)$$

- Then $H(z) \equiv H_c((z-1)/(z+1))$ and $H(e^{j\omega}) = H_c(j \tan(\omega/2))$



Sample-and-Hold Response (1/3)

- A sampled and held signal is related to the sampled continuous-time signal as follows:

$$x_{sh}(t) = \sum_{n=-\infty}^{\infty} x_c(nT)[g(t-nT) - g(t-nT-T)]$$

- Taking the Laplace-transform:

$$\begin{aligned} X_{sh}(s) &= \frac{1-e^{-sT}}{s} \sum_{n=-\infty}^{\infty} x_c(nT)e^{-snT} \\ &= \frac{1-e^{-sT}}{s} X_c(s) \end{aligned}$$



UNIVERSITETET
I OSLO

Sample-and-Hold Response (2/3)

- The hold transfer function $H_{sh}(s)$ is due to the previous result equal to:

$$H_{sh}(s) = \frac{1-e^{-sT}}{s}$$

- The spectrum is found by setting $s=j\omega$:

$$H_{sh}(j\omega) = \frac{1-e^{-j\omega T}}{j\omega} = T \times e^{-j\frac{\omega T}{2}} \times \frac{\sin\left(\frac{\omega T}{2}\right)}{\left(\frac{\omega T}{2}\right)}$$

- Finally the magnitude is given by:


$$|H_{sh}(j\omega)| = T \frac{\left|\sin\left(\frac{\omega T}{2}\right)\right|}{\left|\frac{\omega T}{2}\right|} \qquad |H_{sh}(f)| = T \frac{\left|\sin\left(\frac{\pi f T}{2}\right)\right|}{\left|\frac{\pi f T}{2}\right|}$$

- This response $\sin(x)/x$ is usually referred to as the *sinc-response*.




UNIVERSITETET
I OSLO

Sample-and-Hold Response (3/3)

 

 - Shaping only occurs for continuous-time signals, since a sampled signal will not be affected by the hold function.
- A S/H before an A/D converter **does not reduce the demand of an anti-aliasing filter** preceding the A/D-converter, but simply allow the A/D to have a **constant input value during the conversion**.



ifj

UNIVERSITETET
I OSLO


Tuesday 16th of February:

- Discrete Time Signals
(from chapter 9)

Today: as far as we get with:

10.1 Basic building blocks (Opamps,
Capacitors, Switches,
Nonoverlapping clocks)

 10.2 Basic operation and analysis
(Resistor equivalence of a Switched
Capacitor, Parasitic Insensitive
Integrators)



ifj

UNIVERSITETET
I OSLO

Properties of SC circuits

- Popular due to **accurate frequency response**, **good linearity and dynamic range**
- Easily analyzed with z-transform
- Typically require aliasing and smoothing filters
- Accuracy is obtained since filter coefficients are determined from **capacitance ratios**, and relative **matching** is good in CMOS
- The overall **frequency response** remains a function of the **clock**, and the frequency may be set very precisely through the use of a **crystal oscillator**
- **SC-techniques** may be used to realize other signal processing blocks like for **example gain stages, voltage-controlled oscillators and modulators**



UNIVERSITETET
I OSLO


Basic building blocks in SC circuits; **Opamps**, capacitors, switches, clock generators (chapter 10.1)

- **DC gain** typically in the order of 40 to 80 dB (100 – 10000 x)
- **Unity gain** frequency should be $> 5 \times$ clock speed (rule of thumb)
- **Phase margin** > 70 degrees (according to Johns & Martin)
- Unity-gain and phase margin highly dependent on the load capacitance, in SC-circuits. In single stage opamps a doubling of the load capacitance halves the unity gain frequency and improve the phase margin
- The finite **slew rate** may limit the upper clock speed.
- Nonzero **DC offset** can result in a high output dc offset, depending on the topology chosen, especially if correlated double sampling is not used




UNIVERSITETET
I OSLO

 
Basic building blocks in SC circuits; Opamps, capacitors, switches, clock generators



cross-section view

 


equivalent circuit

 

- Typically constructed between two polysilicon layers
- Parasitics; C_{p1} , C_{p2} .
- Parasitic C_{p2} may be as large as 20 % of the desired, C_1
- C_{p1} typically 1- 5 % of C_1 . Therefore, the equivalent model contain 3 capacitors



 
Basic building blocks in SC circuits; Opamps, capacitors, switches, clock generators



- Desired: very **high off-resistance** (to avoid leakage), relatively **low on-resistance** (for fast settling), no offset
- Phi, the **clock signal**, switches between the **power supply levels**
- Convention: Phi is high means that the switch is on (shorted)
- Transmission gate switches may increase the signal range
- Some nonideal effects: nonlinear capacitance on each side of the switch, charge injection, capacitive coupling to each side



 Basic building blocks in SC circuits; Opamps, capacitors, switches, **clock generators**



- Must be **nonoverlapping**; at no time both signals can be high
- Convention in "Johns & Martin"; sampling numbers are integer values
- Location of **clock edges** need only be **moderately controlled** (assuming low-jitter sample-and-holds on input and output of the overall circuit)
- Delay elements above can be an even number of inverters or an RC network



SC Resistor Equivalent (1/2)



$$Q_x = C_x V_x$$

C_1 is first charged to V_1 and then charged to V_2 during one clock cycle

$$\Delta Q_1 = C_1(V_1 - V_2)$$



The average current is then given by the change in charge during one cycle

$$I_{\text{avg}} = \frac{C_1(V_1 - V_2)}{T}$$

Where T is the clock period ($1/f_s$)



SC Resistor Equivalent (2/2)

  

The current through an equivalent resistor is given by:

Combining the previous equation with **avg**:

$$I_{\text{eq}} = \frac{V_1 - V_2}{R_{\text{eq}}}$$

The resistor equivalence is valid when f_s is much larger than the signal frequency. In the case of higher signal frequencies, z-domain analysis is required :

$$R_{\text{eq}} = \frac{T}{C_1} = \frac{1}{C_1 f_s}$$




Example of resistor implementation

- What is the resistance of a 5 pF capacitance sampled at a clock frequency of 100 kHz?
- Note the large resistance that can be implemented. Implemented in CMOS it would take a large area for a resistor of the same resistance

$$R_{\text{eq}} = \frac{1}{(5 \times 10^{-12})(100 \times 10^3)} = 2\text{M}\Omega$$



An inverting integrator

 

Transfer function for simple discrete time integrator in chapter 10.2

SC:

RC-int.

$Q = C \cdot V$
 $f = \frac{1}{T} \dots$

ref.: Nils Haakeim, "Analog (MS)", Universitetet i Trondheim - NTH, 1994

Svitsjen er ved tidspunkt $t = (n-1)T$ i posisjon 1, og det blir tatt en punktprøve ("et sampel") av $u_1(t)$, da C_1 blir ladet til:

$$q_1[(n-1)T] = C_1 \cdot u_1[(n-1)T]$$

Ladningen på C_2 er (samtidig):

$$q_2[(n-1)T] = C_2 \cdot u_2[(n-1)T]$$

Ved tidspunkt $t = n \cdot T$ blir ladningen på C_1 overført til C_2 ved at svitsjen er i posisjon 2. Hele ladningen på C_1 blir ført over til C_2 fordi operasjonsforst. tvinger spenningen over C_1 til å bli null.

Ladn. på C_1 subtraheres dermed fra ladn. på C_2 .
 Ladn. på C_2 ved $t = nT$ blir dermed:

$$q_2[nT] = q_2[(n-1)T] - q_1[(n-1)T]$$

$$C_2 \cdot u_2[nT] = C_2 \cdot u_2[(n-1)T] - C_1 \cdot u_1[(n-1)T]$$


$$u_2[nT] = u_2[(n-1)T] - \frac{C_1}{C_2} \cdot u_1[(n-1)T]$$

Kan benytte z-transformen
 osv. If $x(n) \leftrightarrow X(z)$, then $x(n-k) \leftrightarrow z^{-k} X(z)$

$$U_2(z) = U_2(z) \cdot z^{-1} - \frac{C_1}{C_2} U_1(z) z^{-1}$$

$$H(z) = \frac{U_2(z)}{U_1(z)} = -\frac{C_1}{C_2} \cdot \frac{z^{-1}}{(1-z^{-1})}$$

 
Example waveforms. $H(z)$ rewritten to eliminate terms of z having negative powers. Equation representative just before end of phi1 only



Frequency response (Low frequency)

$$H(z) = -\left(\frac{C_1}{C_2}\right) \frac{z^{-1/2}}{z^{1/2} - z^{-1/2}}$$

$$z = e^{j\omega T} = \cos(\omega T) + j\sin(\omega T)$$

$$z^{1/2} = \cos\left(\frac{\omega T}{2}\right) + j\sin\left(\frac{\omega T}{2}\right)$$

$$z^{-1/2} = \cos\left(\frac{\omega T}{2}\right) - j\sin\left(\frac{\omega T}{2}\right)$$

$$H(e^{j\omega T}) = -\left(\frac{C_1}{C_2}\right) \frac{\cos\left(\frac{\omega T}{2}\right) - j\sin\left(\frac{\omega T}{2}\right)}{j2\sin\left(\frac{\omega T}{2}\right)}$$

Example 10.2 (2/2)

- Assuming low frequency i.e. $\omega T \ll 1$:

$$\omega T \ll 1$$


- The gain-constant is depending only on the capacitor-ratio and clock frequency:

$$H(e^{j\omega T}) \cong -\left(\frac{C_1}{C_2}\right) \frac{1}{j\omega T}$$

$$K_I \cong \frac{C_1}{C_2 T}$$



 Parasitics reducing accuracy and performance




- Parasitics added
- C_{p1} the one that is harmful, as accurate discrete-time frequency responses depends on precise matching of capacitors, (sometimes down to 0.1 percent)
- C_{p1} 1-5 % of C_1 (page 396)
- Gain coefficient related to C_{p1} which is not well controlled and partly

$$H(z) = -\left(\frac{C_1 + C_{p1}}{C_2}\right) \frac{1}{z-1}$$



Effect of parasitic capacitors
 
$$H(z) = -\left(\frac{C_1 + C_{p1}}{C_2}\right) \frac{1}{z-1}$$




- The gain coefficient depends on the parasitic and possibly non-linear capacitance

ifj

UNIVERSITETET
I OSLO

Parasitic-Insensitive Integrator

 


- The following parasitics does not influence:
 - C_{p2} is either connected to virtual ground or physical ground
 - C_{p3} is connected to virtual ground
 - C_{p4} is driven by the output
 - C_{p1} is charged between $v_i(n)$ and gnd.

ifj

UNIVERSITETET
I OSLO

Parasitic-Insensitive Integrator

 

- Two additional switches removes sensitivity to parasitics:
 - Improved linearity
 - More well-defined and accurate transfer-functions



Transfer function not dependent on Cp1:

"Non-inverting delaying discrete-time int." (J of M p. 4.5)

$Q = C \cdot V$

Remember, from chapter 1:
If $x(n) \leftrightarrow X(z)$ then $x(n-k] \leftrightarrow z^{-k} X(z)$

using $Q = C \cdot V$:

$$C_2 V_{out}[nT] = C_2 V_{out}[(n-1)T] + C_1 V_{in}[(n-1)T]$$

\uparrow z-transf. \uparrow z-transf.

$$C_2 V_{out}(z) = C_2 V_{out}(z) \cdot z^{-1} + C_1 V_{in}(z) \cdot z^{-1}$$

$$C_2 V_{out}(z) - C_2 V_{out}(z) \cdot z^{-1} = C_1 V_{in}(z) \cdot z^{-1}$$


$$C_2 V_{out}(z) (1 - z^{-1}) = C_1 V_{in}(z) \cdot z^{-1}$$

$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}}$$


At time $t = (n-1)T$, in ϕ_1 , a "sample" of the input voltage is taken, and C_1 gets charged:
 $q_{c1}[(n-1)T] = C_1 \cdot v_{in}[(n-1)T]$

At the same time, there is a charge on C_2 :
 $q_{c2}[(n-1)T] = C_2 \cdot v_{out}[(n-1)T]$

 At time $t = nT$ the charge on C_1 is transmitted to C_2 :
 $q_{c2}[nT] = q_{c2}[(n-1)T] + q_{c1}[(n-1)T]$



 Parasitic-Insensitive Integrator (fig. 10.9)



$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = \left(\frac{C_1}{C_2}\right) \frac{1}{z-1}$$

- Note that **the integrator** is now **positive**
- C_1 and C_2 no longer need to be much larger than parasitics
- A remaining limitation is the lateral stray capacitance between the lines leading to the electrodes of C_1 and C_2 . This can be reduced by inserting a grounded line between the leads. In any case the **minimum permissible C_1 and C_2 values are reduced by a factor 10 – 50 if the stray-insensitive configuration is used**, hence reducing the area required by the capacitors is reduced by the same factor [GrTe86]. Price is proportional to area.
- **While parasitics do not affect the discrete time difference equation (or $H(z)$), they may slow down settling time behaviour.**



$H(z)$ for inverting, delay-free integrator

Inverting, delay-free integrator (fig. 10.12 in JDM⁴)
 $C_2 = C \cdot V$

Charge on C_2 at the end of ϕ_1 is equal to its old value minus the charge needed to charge C_1 to $V_{in}(nT)$:

$$C_2 V_{out}(nT) = C_2 V_{out}[(n-1)T] - C_1 V_{in}[nT]$$

Dividing by C_2 and switching to discrete-time variables:

$$V_{out}(n) = V_{out}(n-1) - \frac{C_1}{C_2} V_{in}(n)$$


z -transf.:

$$V_{out}(z) = V_{out}(z) \cdot z^{-1} - V_{in}(z) \cdot \frac{C_1}{C_2}$$

$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C_1}{C_2} \frac{1}{1-z^{-1}}$$

$V_{in}(nT)$ occurs in the difference equation rather than $V_{in}[(n-1)T]$, since the charge on C_2 at the end of ϕ_1 is related to $V_{in}(nT)$ at the same time \rightarrow "DELAY-FREE"

 Inverting delay-free integrator (fig. 10.12)



- Equations similar to previous slide, but with clocking- and timing convention as in fig. 10.3:


$$C_2 v_{co}(nT - T/2) = C_2 v_{co}(nT - T)$$

$$C_2 v_{co}(nT) = C_2 v_{co}(nT - T/2) - C_1 v_{ci}(nT)$$

- $H(z)$ having z^{-1} removed: $H(z) = \frac{V_o(z)}{V_i(z)} = -\left(\frac{C_1}{C_2}\right) \frac{z}{z-1}$

Next time, Tuesday the 23rd

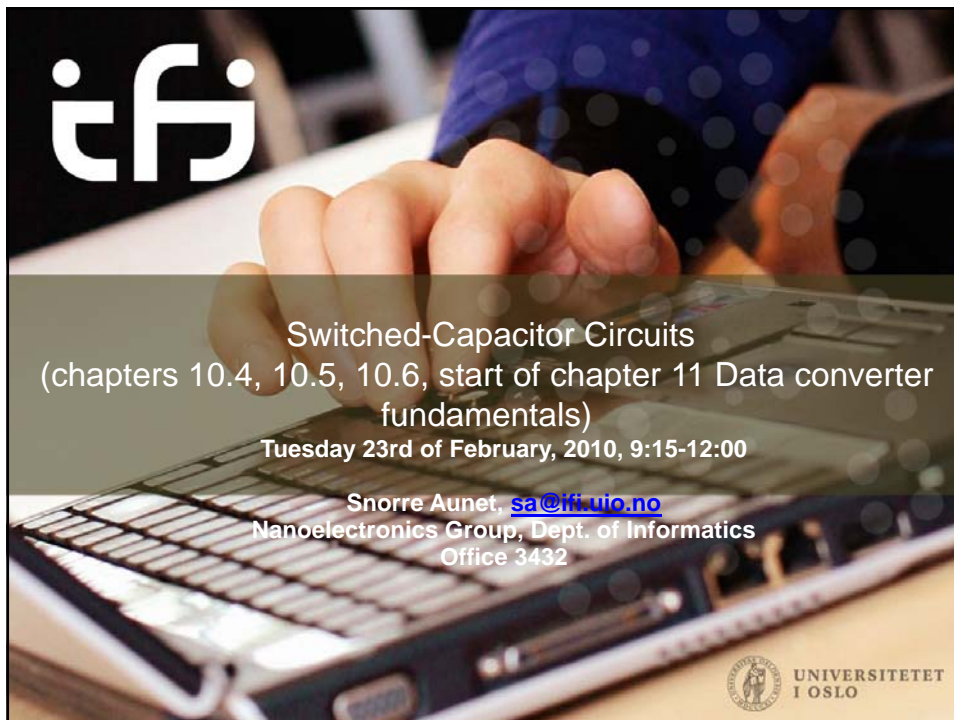- Rest of chapter 10. (10.3, 10.4, 10.5, 10.7)
- Chapter 11, Data Converter Fundamentals




ifi

Switched-Capacitor Circuits
(chapters 10.4, 10.5, 10.6, start of chapter 11 Data converter fundamentals)

Tuesday 23rd of February, 2010, 9:15-12:00

Snorre Aunet, sa@ifi.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

 UNIVERSITETET
I OSLO


Last time – and **today**, Tuesday 23rd of February:

9.2 Laplace Transform of Discrete Time Signals
9.3 z-transform
9.4 downsampling and Upsampling
9.5 Discrete Time Filters
9.6 Sample-and-Hold Response


10.1 Switched Capacitor Circuits
10.2 Basic Operation and Analysis

Today:

 
10.3 First-order filters
10.4 Biquad filters (high-Q)
10.5 Charge injection
10.7 Correlated double sampling techn
11.1 Ideal D/A converter
11.2 Ideal A/D converter
11.3 quantization noise
11.4 signed codes



Signal-flow-graph analysis (p. 407)

 

 - Applying charge equations is tedious for larger circuits. Using some rules and **signal-flow-graph analysis** simplifies analysis and design of SC-circuits.
- Superposition (Wikipedia) In a linear system, the net response at a given place and time caused by two or more independent stimuli is the sum of the responses which would have been caused by each stimulus individually.



Individual contributions:

$$\frac{V_o(z)}{V_1(z)} = -\frac{C_1}{C_A} \quad (10.28) \quad (\text{See lecture notes from 1/2})$$

$$\frac{V_o(z)}{V_2(z)} = \frac{C_2}{C_A} \frac{z^{-1}}{1-z^{-1}} \quad (10.29) \quad (\text{Non-inverting delaying integrator See eq. 10.26})$$

$$\frac{V_o(z)}{V_3(z)} = -\frac{C_3}{C_A} \frac{1}{1-z^{-1}} \quad (10.30) \quad (\text{delay-free int., see eq. 10.25})$$



Getting the transfer function..

Multiplying each of the equations (10.28), (10.29), (10.30) by their respective input voltages, on each side:

$$V_o(z) = -\frac{C_1}{C_A} \cdot V_1(z)$$

$$V_o(z) = \frac{C_2}{C_A} \frac{z^{-1}}{1-z^{-1}} \cdot V_2(z)$$

$$V_o(z) = -\frac{C_3}{C_A} \frac{1}{(1-z^{-1})} \cdot V_3(z)$$

Adding the contributions:

$$V_{out}(z) = -\frac{C_1}{C_A} \cdot V_1(z) + \frac{C_2}{C_A} \frac{z^{-1}}{1-z^{-1}} V_2(z) + -\frac{C_3}{C_A} \frac{1}{(1-z^{-1})} \cdot V_3(z)$$

22

As powers of z:

$$V_{out}(z) = -\frac{C_1}{C_A} \cdot V_1(z) + \frac{C_2}{C_A} \frac{1}{z-1} V_2(z) - \frac{C_3}{C_A} \frac{z}{z-1} V_3(z) \quad (10.31)$$

4



TET


Signal Flow Graph (Fig. 10.13 in "J & M")

SIGNAL FLOW GRAPH IN FIG 10.13


(10.30)

$$V_{out}(z) = -\frac{C_1}{C_A} \cdot V_1(z) + \frac{C_2}{C_A} \frac{z^{-1}}{1-z^{-1}} V_2(z) - \frac{C_3}{C_A} \frac{1}{1-z^{-1}} V_3(z)$$

$$= -\frac{C_1}{C_A} \frac{(1-z^{-1})}{(1-z^{-1})} \cdot V_1(z) + \frac{C_2}{C_A} \frac{z^{-1}}{1-z^{-1}} V_2(z) - \frac{C_3}{C_A} \frac{1}{1-z^{-1}} V_3(z)$$

 See that $\frac{1}{C_A(1-z^{-1})}$ is a common factor

First-Order Filters

 

- Select a known Active-RC circuit
- Replace resistors by SC-equivalents
- Analyze using discrete-time methods

Making 1st order SC-filter from active RC equivalent

1st order filters via inverting delay-free SC (See fig 10.12) (See eq 10.25)

Superposition

$$V_{out}(z) = -\frac{C_2}{C_A} \frac{z^{-1}}{1-z^{-1}} \cdot V_{in}(z) - \frac{C_3}{C_A} \frac{1}{1-z^{-1}} \cdot V_{out}(z) - \frac{C_1}{C_A} V_{in}(z)$$

$$V_{out}(z) \cdot C_A (1-z^{-1}) = -C_2 \cdot V_{in}(z) - C_3 \cdot V_{out}(z) - C_1 (1-z^{-1}) \cdot V_{in}(z)$$

$$V_{out}(z) \cdot C_A (1-z^{-1}) + C_3 V_{out}(z) = -C_2 \cdot V_{in}(z) - C_1 (1-z^{-1}) V_{in}(z)$$

$$V_{out}(z) [C_A (1-z^{-1}) + C_3] = -V_{in}(z) [C_2 + C_1 (1-z^{-1})]$$

$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = -\frac{[C_2 + C_1 (1-z^{-1})]}{[C_A (1-z^{-1}) + C_3]} = \frac{\frac{C_2}{C_A} z + \frac{C_1}{C_A} (z-1)}{1-z^{-1} + \frac{C_3}{C_A}} = \frac{\frac{C_2}{C_A} z + \frac{C_1}{C_A} (z-1)}{z-1 + \frac{C_3}{C_A} z} = \frac{\frac{C_2}{C_A} z + \frac{C_1}{C_A} z - \frac{C_1}{C_A}}{z + \frac{C_3}{C_A} z - 1}$$

eq 10.33:


$$= \frac{\left(\frac{C_1+C_2}{C_A}\right)z - \frac{C_1}{C_A}}{\left(1 + \frac{C_3}{C_A}\right)z - 1}$$

POLES?
 Equating the denominator to zero, in $H(z)$:

$$\left(1 + \frac{C_3}{C_A}\right)z - 1 = 0$$

$$z_p = \frac{C_A}{C_A + C_3}$$

 For positive capacitance values this pole is restricted to the real axis between zero and one



In this case the circuit is always stable.

The case of $C_3 = 0$:

$$z_p = \frac{C_A}{C_A + C_3} = \frac{C_A}{C_A} = 1$$

ZEROS?
 Numerator in $H(z) = 0$

$$\left(\frac{C_1 + C_2}{C_A}\right)z - \frac{C_1}{C_A} = 0$$

$$\left(\frac{C_1 + C_2}{C_A}\right)z = \frac{C_1}{C_A} \Rightarrow z = \frac{C_1}{C_1 + C_2}$$

For positive capacitances the zero is located to the real axis between 0 and 1.

DC-gain ($z=1$):

$$H(1) = -\frac{\left(\frac{C_1+C_2}{C_A}\right)z - \frac{C_1}{C_A}}{\left(1 + \frac{C_3}{C_A}\right)z - 1} = -\frac{\frac{C_1}{C_A} + \frac{C_2}{C_A} - \frac{C_1}{C_A}}{1 + \frac{C_3}{C_A} - 1}$$

$$= -\frac{\frac{C_2}{C_A}}{\frac{C_3}{C_A}} = -\frac{C_2}{C_3}$$



Switch sharing (p. 413)

in ϕ_1 : C_2 top plate Switched to (virtual) ground
 C_3 ————— || —————


in ϕ_2 : C_2 ————— || ————— ground
 C_3 ————— || —————

Connecting the top plates and letting them share one "switch-pair":

Top plates of C_2 and C_3 can be connected together and one pair of switches eliminated


Fig. 10.16 in "J&M"

 Fully Differential Filters (p. 414 (1/3))



- The signal is represented by the difference of two voltages
- Most SC-designs are fully differential, typically operating around a dc common-mode voltage halfway between the supply voltages
- Reduced common-mode noise
- Cancellation of even-order harmonic distortion, if the nonlinearity is memoryless

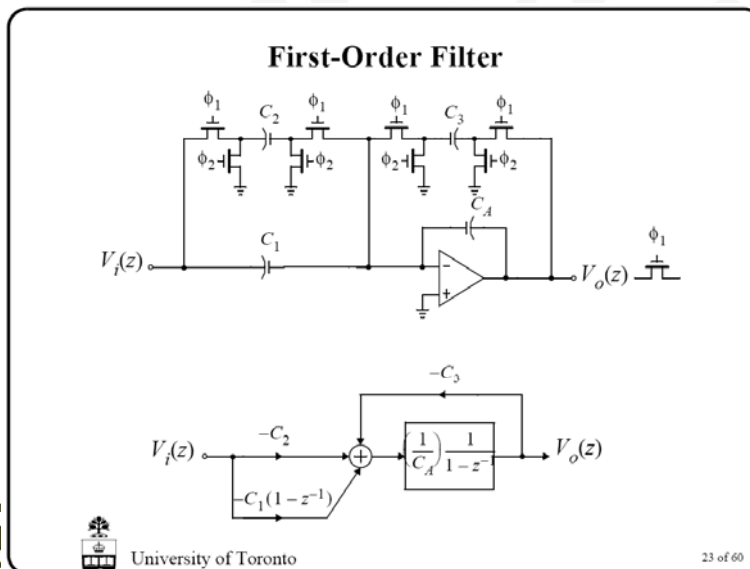SFG based on superposition, similar as in fig 10.13.



22. februar

11




University of Toronto

23 of 60

© D. Johns, K. Martin, 1997

UNIVERSITET

 Differential implementation (fig. 10.18 p. 415)



UNIVERSITET
I OSLO

Example: Fully differential SC-sigma-delta ADC published May 2007

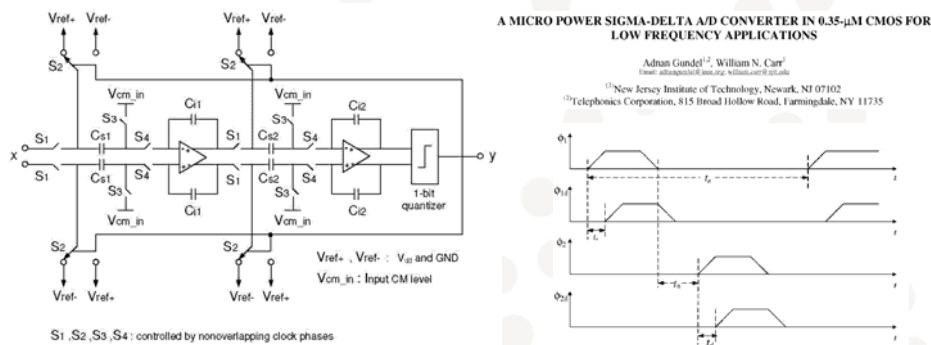


Figure 4. Nonoverlapping clock phases.

- Downloaded from IEEEXplore (<http://ieeexplore.ieee.org/Xplore/dynhome.jsp>)




Properties of Fully Differential Filters, compared to single-ended solutions

- Requires two copies of a single-ended filter except from the Opamp which is shared
- Common-mode feedback circuitry is required
- The input- and output signal amplitude are doubled. The same dynamic range can be achieved with half-sized capacitors:
 - Area reduction and less power consumption
 - Reduced size of switches (less charge)
- More wires are required
- Improved performance with respect to noise and distortion



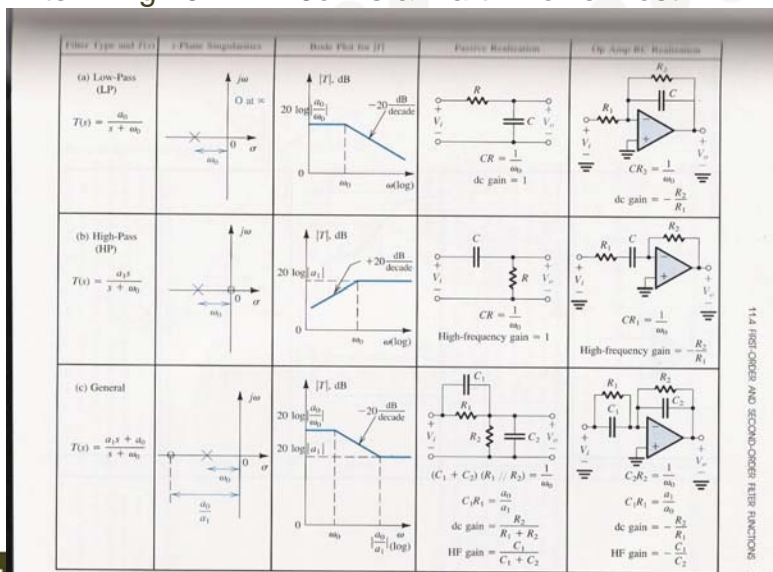
Some Active RC 1st order filters (Sedra & Smith p. 779).
Filter in fig 10.14 in "Johns & Martin" lowermost.



Additional literature


- Adnan Gundel, William N. Carr: A micropower sigma-delta A/D converter in 0.35 um CMOS for low-frequency applications, Proceedings of IEEE Long Island Systems, Applications and Technology Conference, IEEE 2007
- [GrTe86]: Roubik Gregorian, Gabor C. Temes: Analog MOS Integrated Circuits for signal processing, Wiley, 1986.
- [Haah94]: Nils Haaheim: Analog CMOS, Universitetet i Trondheim, Norges Tekniske Høgskole, 1994.
- Adel S. Sedra, Kenneth C. Smith: Microelectronic Circuits, Saunders College Publ., 1989.
- Kenneth R. Laker, Willy M. C. Sansen: Design of analog integrated circuits and systems, McGraw-Hill, 1994.

High-Q Biquad active RC-filter

 

- Another circuit is required for high Q-values and small capacitor spread
- Q-damping is obtained by adding a capacitor around both integrators instead of a resistive feedback around the last integrator

 High-Q Switched-capacitor biquad filter (Fig. 10.25, p. 421) by changing the resistors with SC-equivalents



High-Q Biquad Filter

- General transfer function:

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = \frac{K_3 z^2 + (K_1 K_5 + K_2 K_5 - 2K_3)z + (K_3 - K_2 K_5)}{z^2 + (K_4 K_5 + K_5 K_6 - 2)z + (1 - K_5 K_6)}$$

- The function can be rewritten as:

$$H(z) = \frac{a_2 z^2 + a_1 z + a_0}{z^2 + b_1 z + b_0}$$

- The coefficients are then:

$$K_1 K_5 = a_0 + a_1 + a_2$$

$$K_2 K_5 = a_2 - a_0$$

$$K_3 = a_2$$

$$K_4 K_5 = 1 + b_0 + b_1$$

$$K_5 K_6 = 1 - b_0$$

- A signal-flow-graph approach is used to find the transfer function. There is some freedom in choosing the coefficients as there is one less equation than the number of coefficients. $K_4 = K_5 = \text{SQR}(1 + b_0 + b_1)$ defines the other ratios.



Ex 10.5 1) BP-filter, peak gain 5 near $f_s/10$ and Q of about 10

... \rightarrow max gain = 5, $Q = 10$

$H(z) = -\frac{0.288(z-1)}{z^2 - 1.5722z + 0.9429}$ 10.6 BP: $H(z) = -\frac{a_2 z^2 + a_1 z + a_0}{z^2 + b_1 z + b_0}$

Find the largest to smallest capacitor ratio if this transfer function is realized using the high-Q biquad circuit. Let $C_1 = C_2$.

(10.74) $K_4 = K_5 = \sqrt{1 + b_0 + b_1} = \sqrt{1 + 0.9429 + 1.572}$
 $= \sqrt{0.3709} = 0.6090$

$K_5 \cdot K_6 = 1 - b_0 \Rightarrow K_6 = \frac{(1 - b_0)}{K_5}$
 (10.71) $K_3 = a_2 = 0$ (see 10.6P) $= \frac{1 - 0.9429}{0.6090} = 0.0591$

(10.69) $K_1, K_2 = a_0 + a_1 + a_2 = 0.0938$

$K_1 = (a_0 + a_1 + a_2) / K_5$
 $= \frac{-0.288 + 0.288}{0.6090} = 0$

(10.70) $K_2 \cdot K_5 = a_2 - a_0 \Rightarrow K_2 = \frac{0 + 0.288}{0.6090} = 0.4729$

$C_1 = C_2 = 1$

$K_1 \cdot C_1 = 0$
 $K_2 \cdot C_1 = 0.4729 \cdot C_1$
 $K_3 \cdot C_1 = 0$
 $K_4 \cdot C_1 = 0.6090 \cdot C_1$
 $K_5 \cdot C_1 = 0.6090 \cdot C_1$
 $K_6 \cdot C_1 = 0.0938 \cdot C_1$

$\frac{C_1}{K_6 \cdot C_1} = \frac{1}{0.0938} = 10.66$

Max. capacitance spread is 10.66

22. febr.

20



TET

Charge Injection (chapter 10.5)

 


Figure 4. Nonoverlapping clock phases.

- To reduce the effects of charge injection in SC circuits, realize all switches connected to ground or virtual ground as n-channel switches only, and turn off the switches connected to ground or virtual ground first. Such an approach will minimize distortion and gain error as well as keeping DC offset low.
- In this case θ_{1a} and θ_{2a} are turned off first to prevent other switches affecting the output voltage of the circuit.



CHARGE INJ.
Ch. 10.5

$Q_{CH} = -WLC_{ox}(V_{DS} - V_{th}) \quad (10.82)$

When a_7 and a_4 are on, $V_{DS} = V_{DD}$, and since their source remain at 0 volts, their V_{th} 's remain constant (neglected).
 THE CHARGE INJECTED BY a_3, a_4 IS THE SAME FROM ONE CLOCK CYCLE TO THE NEXT AND CAN BE CONSIDERED AS A DC OFFSET.
 Unfortunately this is not the case for a_1 and a_6 . Ex $a_1: Q_{CH1} = -W_1L_1C_{ox}(V_{DD} - V_{th1} - V_{in})$
 In this case one portion of the channel charge is linearly related to V_{in} . The V_{th} changes in a nonlinear relationship (bulk effect). Q_{CH1} has a lin. and nonlin. relationship to V_{in} and would cause a gain error and distortion if a_1 were turned off early.



INJECTING CONSTANT CHARGE: a_3, a_4
 a_2, a_5

a_3 and a_4 connect to ground or virtual ground, respectively, meaning that when they are turned on ($a_{2a} = V_{DD}$ or $a_{1a} = V_{DD}$) they need only pass a signal near the ground node ($V_{SS} = 0V$).
 These two switches can be realized using single n-channel transistors. A 2nd important reason for this is that the charge injections due to a_3 and a_4 are not signal dependent (a_3 will be seen).

Channel charge of an NMOS in triode, (chapter 7): $Q_{CH} = -WLC_{ox} \cdot V_{eff}$

TO MINIMIZE DISTORTION, GAIN ERR. AND DC OFFS:
 TO REDUCE THE EFFECTS OF CHARGE-INJECTION IN SC-CIRCUITS, REALIZE ALL SWITCHES CONNECTED TO GROUND OR VIRTUAL GROUND AS n-CHANNEL SWITCHES, AND TURN OFF THE SWITCHES NEAR THE VIRTUAL GROUND OF THE CAPS FIRST.

Ex. 10.6 (1/2)

  

Assume an ideal opamp. Estimate the amount of dc offset at the output due to channel-charge injection when $C_1=0$ and $C_2=C_A=10$ $C_3=10$ pF. $V_{th}=0.8$ V, $W=30$ μ m, $L=0.8$ μ m. $V_{dd}=\pm 2.5$ V. $C_{ox}=3.9 \cdot 10^{-3}$ pF/(μ m)². Q_3 and Q_4 are advanced, and contribute with channel charge.

$$Q_{CH3} = Q_{CH4} = (-30 \cdot 10^{-6}) (0.8 \cdot 10^{-6}) 1.9 \cdot 10^3 \cdot \frac{10^{-12}}{(10^{-5})^2} (2.5 - 0.8) C$$

$$= -30 \cdot 0.8 \cdot 0.0019 \cdot 1.7 \text{ pC} = 0.07752 \text{ pC}$$


22. februar 2




The dc feedback will keep the virtual input of the opamp at 0 volts. All feedback current is charge transferred through C_3 .

Ex. 10.6 (2/2)


 
When ϕ_{1a} turns off, half the charge, Q_{CH4} , goes to virtual ground, while half of Q_{CH4} is placed on the node between Q_3 and Q_4 :



 When Q_{2a} goes high, the 2nd charge escapes to ground:



  When Q_{2a} goes low half of it's channel ch. is left between Q_3 and Q_4 :



DC offset on the output is affected by the sizes of the capacitors, switch sizes and Vdd.


NON-OVERLAPPING CLOCKS, PP=598 ns

At "last" when ϕ_{1a} goes high again, the previously mentioned charge is passed into the virtual ground:

$$\frac{1}{2} Q_{CH3} \text{ to virtual gnd} = 38.75 \text{ pC}$$

$$V_{out} = \frac{Q_{C3}}{-C_3} = \frac{Q_{C3}}{C_3} = \frac{77.5 \cdot 10^{-3} \text{ pC}}{1 \text{ pF}} = 77.5 \text{ mV}$$

CHARGE INJECTION AND HIGHER FREQUENCIES

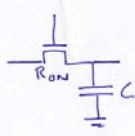

$Q = CV$
 $v = \frac{Q}{C}$

The smaller the R_{on} and smaller the C , the higher the frequency of switching (possible)

$$H(s) = \frac{1}{1 + \tau s} \quad \tau = RC$$

To decrease R_{on} the size of the switch increases, and thus the charge injection.

Will derive a simple formula that gives the upper bound on the frequency of operation of an SC circ. for a max. voltage change due to charge inj.: (ignore overlap capacitance)

MOST SC CIRC. HAVE 2 SERIES SWITCHES PER CAPACITOR. AS A RULE OF THUMB, FOR GOOD SETTLING, THE SAMPLING CLOCK HALF PERIOD MUST BE GREATER THAN 5 TIME CONST.

$$\frac{T}{2} > 5 R_{on} \cdot C \Leftrightarrow f_{clk} < \frac{1}{10 R_{on} C} \quad (10.89)$$

$f_{clk} = \frac{1}{T}$

$$R_{on} = \frac{1}{\mu_n C_{ox} \cdot \frac{W}{L} \cdot V_{eff}} \quad (10.88)$$

Using (10.83) the charge change due to the channel charge caused by turning an n-channel switch off is approximated by

$$|\Delta V| = \frac{1}{2} Q_{ch} \cdot \frac{1}{C} = \frac{W L C_{ox} V_{eff}}{2C}$$

For a specified $|\Delta V|_{max}$

$$C = \frac{W L C_{ox} V_{eff}}{2 |\Delta V|_{max}}$$

Substituting in (10.89):

$$f_{clk} < \frac{1}{10 \cdot \frac{W L C_{ox} V_{eff}}{\mu_n C_{ox} \frac{W}{L} V_{eff}} \cdot \frac{W L C_{ox} V_{eff}}{2 |\Delta V|_{max}}}$$


$$f_{clk} < \frac{\mu_n |\Delta V|_{max}}{5 L^2}$$

\therefore UPPER FREQ. LIMIT INVERSELY PROPORTIONAL TO L^2 . IT IGNORES OVERLAP CAP AND IS SOMEWHAT OPTIMISTIC

Correlated Double Sampling ("CDS")

- Used to realize highly accurate gain amplifiers, sample-and-hold circuits and integrators to reduce errors due to offset voltages, $1/f$ noise and finite opamp gain.
- Method: During a calibration phase the input voltage of an opamp is sampled and stored (across a C) and later subtracted from the signal in the operational phase (when the output is being sampled), by appropriate switching of the capacitors.
- A detailed description is beyond the scope of the text in "J & M". The interested reader may check: C. G. Themes, C. Enz: "Circuit techniques for reducing the effects of opamp imperfections: Autozeroing, Correlated Double Sampling, and Chopper Stabilization", Proceedings of the IEEE, Nov. 1996.

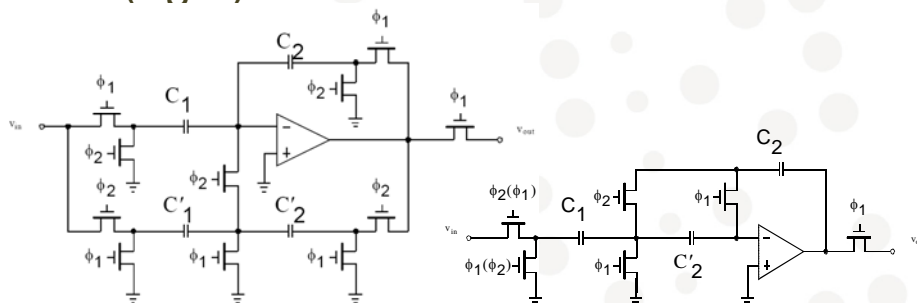SC amplifier (left) and SC integrator with CDS (right)



- For the **amplifier**: During θ_2 the error is sampled and stored across C_1 and C_2
- The stored error is then subtracted during θ_1
- For the **integrator**: During θ_1 the error is sampled and stored across $C'2$
- The stored error is then subtracted during θ_2



CORRELATED DOUBLE SAMPLING

The opamp input error voltage is sampled during ϕ_1 . Next, during ϕ_2 , C_2 is connected in series with the opamp's inverting input and greatly minimizes the effects of these errors (by a factor of the inverse of the opamp's gain over what would otherwise occur at frequencies substantially less than the sampling frequency).

CORRELATED DOUBLE SAMPLING (CDS)

Integrator, fig. 10.35

An additional capacitor, C_2' samples the opamp input error voltage during ϕ_1 .

During ϕ_2 , C_2' is connected in series with the opamp's inverting input and greatly minimizes the effects of these errors

- Reducing errors by a factor of the inverse of the opamp's gain over what would otherwise occur at frequencies substantially less than the sampling frequency
- When CDS is used, the opamps should be designed to minimize thermal noise rather than $1/f$ noise.
- When used in SC-filters only a couple among the stages typically need CDS
- Very useful in over-sampling A/D converters

22. februar 2010 29

UNIVERSITETET I OSLO

SC-integrator with CDS ("J & M" page 434)

- During Phi1 the error is sampled and stored accross C2

UNIVERSITETET I OSLO

Johns & Martin" page 434

$V_{out} \approx -\frac{C_1}{C_2} \cdot V_{in}$


Errors due to finite-offset voltage, $\frac{1}{f}$ noise and gain are included. At the same time the finite opamp input voltage caused by these errors is sampled and stored across C_1 and C_2 .

Next, during ϕ_1 , this input error voltage is subtracted from the signal (applied to the opamp input) at that time. Assuming that the input voltage and the opamp input error voltages did not change appreciably from ϕ_1 to ϕ_2 errors due to them will be significantly reduced.

22. februar 2010 32

UNIVERSITETET I OSLO

Data Converter Fundamentals (chapter 11)

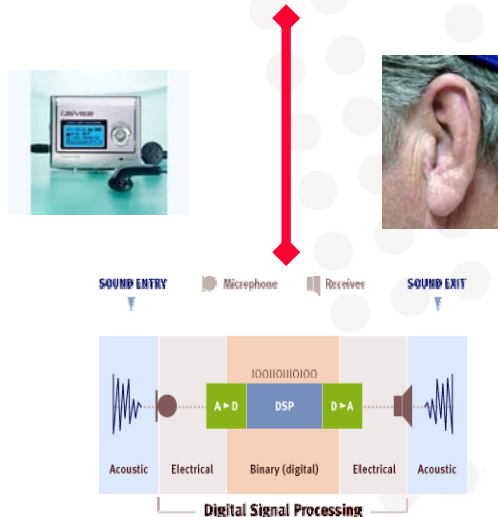

Main data converter types:

- Nyquist-rate converters:
 - Each value has a one-to-one correspondence with a single input
 - The sample-rate must be at least equal to twice the signal frequency (Typically somewhat higher)
- Oversampled converters:
 - The sample-rate is much higher than the signal frequency, typically 20 – 512 times.
 - The extra samples are used to increase the SNR
 - Often combined with noise shaping

Flash ADC from 1926 (Analog Digital Conversion handbook, Analog Devices)

The first documented flash converter was part of Paul M. Rainey's electro-mechanical PCM facsimile system described in a relatively ignored patent filed in 1921 (Reference 5—see further discussions in Chapter 1 of this book). In the ADC, a current proportional to the intensity of light drives a galvanometer which in turn moves another beam of light which activates one of 32 individual photocells, depending upon the amount of galvanometer deflection (see Figure 3.49). Each individual photocell output activates part of a relay network which generates the 5-bit binary code.


 


Figure 3.49: A 5-Bit Flash ADC Proposed by Paul Rainey
Adapted from Paul M. Rainey, "Facsimile Telegraph System," U.S. Patent 1,608,527, Filed July 20, 1921, Issued November 30, 1926

11.1 Ideal D/A converter

 

$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}$$

$$V_{out} = V_{ref}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N})$$

Example 11.1 : 8-bit D/A converter

An ideal D/A converter has

$$V_{\text{ref}} = 5 \text{ V}$$

Find V_{out} when

$$B_{\text{in}} = 10110100$$

$$B_{\text{in}} = 2^{-1} + 2^{-3} + 2^{-4} + 2^{-6} = 0,703125$$

$$V_{\text{out}} = V_{\text{ref}} B_{\text{in}} = 3,516 \text{ V}$$


Find

$$V_{\text{LSB}}$$

$$V_{\text{LSB}} = 5/256 = 19,5 \text{ mV}$$


$$V_{\text{LSB}} \equiv \frac{V_{\text{ref}}}{2^N}$$

$$1 \text{ LSB} = \frac{1}{2^N}$$

 

UNIVERSITETET
I OSLO

11.2 Ideal A/D converter (Fig. 11.3)

 

$$V_{\text{ref}}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}) = V_{\text{in}} \pm V_x$$


where

$$-\frac{1}{2} V_{\text{LSB}} \leq V_x < \frac{1}{2} V_{\text{LSB}}$$



UNIVERSITETET
I OSLO


 
Ideal transfer curve for a 2-bit A/D converter (Fig. 11.4)



- A range of input values produce the same output value (QA range of input values produce the same output value (Quantization error))
- Different from the D/A case




11.3 Quantization noise

  


$$V_Q = V_1 - V_{in}$$



Quantization noise model

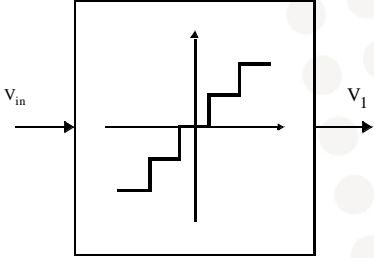

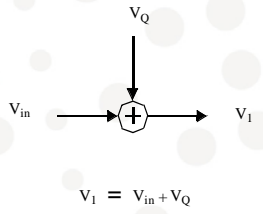

Quantizer



Model

$V_1 = V_{in} + V_Q$

- The model is exact as long as V_Q is properly defined
- V_Q is most often assumed to be white and uniformly distributed between $\pm V_{LSB}/2$



UNIVERSITETET
I OSLO

Quantization noise



- The rms-value of the quantization noise can be shown to be:

$$V_{Q(rms)} = \frac{V_{LSB}}{\sqrt{12}}$$


- Total noise power is independent of sampling frequency
- In the case of a sinusoidal input signal with p-p amplitude of $V_{ref}/2$

$$SNR = 20 \log \left(\frac{V_{in(rms)}}{V_{Q(rms)}} \right) = 20 \log \left(\frac{V_{ref}/(2\sqrt{2})}{V_{LSB}/(\sqrt{12})} \right)$$

$$SNR = 6,02N + 1,76 \text{ dB}$$



UNIVERSITETET
I OSLO

 Quantization noise



- Signal-to Noise ratio is highest for maximum input signal amplitude



11.4 Signed codes

Table 11.1 Some 4-bit signed digital representations

Number	Normalized number	Sign magnitude	1's complement	Offset binary	2's complement
+7	+7/8	0111	0111	1111	0111
+6	+6/8	0110	0110	1110	0110
+5	+5/8	0101	0101	1101	0101
+4	+4/8	0100	0100	1100	0100
+3	+3/8	0011	0011	1011	0011
+2	+2/8	0010	0010	1010	0010
+1	+1/8	0001	0001	1001	0001
+0	+0	0000	0000	1000	0000
(-0)	(-0)	(1000)	(1111)		
-1	-1/8	1001	1110	0111	1111
-2	-2/8	1010	1101	0110	1110
-3	-3/8	1011	1100	0101	1101
-4	-4/8	1100	1011	0100	1100
-5	-5/8	1101	1010	0011	1011
-6	-6/8	1110	1001	0010	1010
-7	-7/8	1111	1000	0001	1001
-8	-8/8			0000	1000

- Unipolar / bipolar
- Common signed digital repr.: sign magnitude, 1's complement, 2's compl.
- Sign. M.: 5:0101, -5:1101, two repr. Of 0, 2^N-1 numb.
- 1's compl.: Neg. Numbers are complement of all bits for equiv. Pos. Number: 5:0101, -5:1010
- Offset bin: 0000 to the most neg., and then counting up..
+ : closely related to unipolar through simple offset



2's complement

A3a2a1a0	Sign magnitude	2's complement
0111	+7	+7
0110	+6	+6
0101	+5	+5
0100	+4	+4
0011	+3	+3
0010	+2	+2
0001	+1	+1
0000	+0	+0
1000	-0	-8
1001	-1	-7
1010	-2	-6
1011	-3	-5
1100	-4	-4
1101	-5	-3
1110	-6	-2
1111	-7	-1

- $5_{10} : 0101 = 2^2 + 2^0$

- $-5_{10} : (0101)' + 1 = 1010 + 1 = 1011$

- Addition of positive and negative numbers is straightforward, using addition, and requires little hardware
- 2's complement is most popular representation for signed numbers when arithmetic operations have to be performed



UNIVERSITETET
I OSLO

$7_{10} - 6_{10}$ via addition using two's complement of -6

- $0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 00111_2 = 7_{10}$
 - $0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 00110_2 = 6_{10}$
 - *Subtraction uses addition: The appropriate operand is **negated** before being added*
 - *Negating a two's complement number: Simply invert every 0 and 1 and add one to the result. Example:*
 - $0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0110_2$ becomes
 - $1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1001_2$
- $$\begin{array}{r}
 + \\
 \\
 \hline
 = 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1010_2 \\
 \\
 + 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1010_2 \\
 = 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0001_2
 \end{array}$$



UNIVERSITETET
I OSLO

11.5 performance limitations

- Resolution
- Offset and gain error
- Accuracy
- Integral nonlinearity (INL) error
- Differential nonlinearity (DNL) error
- Monotonicity
- Missing codes
- A/D conversion time and sampling rate
- D/A settling time and sampling rate
- Sampling time uncertainty
- Dynamic range
- NB!! Different meanings and definitions of performance parameters sometimes exist. → Be sure what's meant in a particular specification or scientific paper.. There are also more than those mentioned here.



UNIVERSITETET
I OSLO

Resolution

- Resolution usually refers to the number of bits in the input (D/A) or output (ADC) word, and is often different from the accuracy.
- Analog-Digital Conversion Handbook, Analog Devices, 3rd Edition, 1986: *An n -bit binary converter should be able to provide $2n$ distinct and different analog output values corresponding to the set of n binary words. A converter that satisfies this criterion is said to have a resolution of n bits.*

A Cost-Efficient High-Speed 12-bit Pipeline ADC
in 0.18- μm Digital CMOS

Yiqin Huo, Andrew, Ronald, James, Michael, IEEE, John, Benjamin, Frank, Sotirov,
Mikael, Eriksson, Member, IEEE, Thomas, E. Brunschwiler, and Olivier, Makris

TABLE I
KEY DATA FOR THE ADC

Nominal sampling rate	110MS/s
Technology	0.18 μm digital CMOS
Nominal supply voltage	1.8V
Resolution	12bit
Full scale analog input	$2V_{DD}$
Area	0.86mm ²
Power consumption	97mW
DNL	± 1.2 LSB
INL	-1.5 ± 1 LSB
SNR ($f_{in}=10\text{MHz}$)	67.1 dB
SNDR ($f_{in}=10\text{MHz}$)	64.2 dB
SFDR ($f_{in}=10\text{MHz}$)	69.4 dB
ENOB ($f_{in}=10\text{MHz}$)	10.4 bit

 


Fig. 8. SFDR, SNR, and SNDR versus conversion rate. The input frequency and signal swing is 10 MHz and $2V_{DD}$, respectively.



Next Tuesday (2/3-10):

- Chapter 12 Nyquist DACs

Du er her: [LSP](#) > [Studier](#) > [Fagser](#) > [Matematikk og naturvitenskap](#) > [Informasjon](#) > [INF4420 - 210](#)

Undervisningsplan (INF4420 - Vår 2010)

Dato	Undervises av	Sted	Tema	Kommentarer / ressurser
26.01.2010	Snorre Aunet ("SA")	Lille Auditorium, III	Introduksjon til INF4420	Slides , Slides , two per page
02.02.2010	SA, Amir Hasanbegovic ("AH")	Lille Auditorium, III	From chapter 8 i "Johns & Martin". + SW intro (Cadence)	Slides , Slides , two per page , other relevant material
09.02.2010	SA	Lille Aud.	from chapters 8 and 9 in "Johns & Martin".	Slides , Slides , two per page
16.02.2010	SA	Lille Aud.	9.2-9.6, 10.1-10.2	Slides , Slides , two per page
23.02.2010	SA	Lille Aud.	Chapter 10.3, --> beg. of chapter 11.	
02.03.2010	SA	Lille Aud.	chapter 12: Nyquist-rate DACs	
09.03.2010	SA	Lille Aud.	chapter 13: Nyquist-rate ADCs I	
16.03.2010	SA	Lille Aud.	chapter 13: Nyquist-rate ADCs II	
23.03.2010	SA	Lille Aud.	Chapter 14: Oversampling Converters	
30.03.2010				No teaching in week 13.
06.04.2010				No teaching in week 14, due to Easter holidays.
13.04.2010	SA	Lille Aud.	chapter 16, PLLs	
20.04.2010	SA, AH	Lille Aud.	"project meeting"	
27.04.2010	SA	Lille Aud.	To be defined.	In case..
10.05.2010	AH	Lille Aud.	Selected problems relevant for the exam.	
11.05.2010	SA, AH	Lille Aud.	presentation of the project work.	

Redaksjon: [Redaksjon for informasjon om studietilbudet ved IUP](#)

Dokument opprettet: 26.12.2009, endret: 17.02.2010



UNIVERSITETET
I OSLO

Additional literature:

1506

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 40, NO. 7, JULY 2005

A Cost-Efficient High-Speed 12-bit Pipeline ADC in 0.18- μ m Digital CMOS

Terje Nortvedt Andersen, Bjørnar Hernes, *Member, IEEE*, Atle Briskemyr, Frode Telsto, Johnny Bjørnsen, *Member, IEEE*, Thomas E. Bonnerud, and Øystein Moldsvor

ANALOG-DIGITAL CONVERSION

Walt Kester

Editor



High speed data converters
fully integrated in CMOS

by
Leif Hanssen



UNIVERSITETET
I OSLO




22. februar 2010

51

ifj



UNIVERSITETET
I OSLO




ifi

Nyquist Rate D/A Converters (12.1-12.4)

Tuesday 2nd of March, 2010, 9:15-11:00

Snorre Aunet, sa@ifi.uio.no
 Nanoelectronics Group, Dept. of Informatics
 Office 3432

 UNIVERSITETET
I OSLO


Last time – and today, Tuesday 2nd of March:

Last time:

- 10.3 First-order filters
- 10.4 Biquad filters (high-Q)
- 10.5 Charge injection
- 10.7 Correlated double sampling techniques
- 11.1 Ideal D/A converter
- 11.2 Ideal A/D converter
- 11.3 quantization noise
- 11.4 signed codes


Today:

 - 11.5 Performance Limitations
- 12.1 Decoder-based converters
- 12.2 Binary-scaled converters
- 12.3 Thermometer-code converters
- 12.4 Hybrid converters
- 10:55 : 5 minute survey by "Micro"



Offset and gain error

- In a D/A converter ("DAC") the **offset error** is defined to be the output that occurs for the input code that should provide zero output. For an A/D converter ("ADC") the **offset error** is the deviation of $V_{0...01}$ from $\frac{1}{2}$ LSB.
- The **gain error** is the difference at the full scale value between ideal and actual curves when the offset has been reduced to zero. For a DAC it is given in units of LSBs.

 

ADC:

given by

$$E_{\text{gain(A/D)}} = \left(\frac{V_{1...1}}{V_{\text{LSB}}} - \frac{V_{0...01}}{V_{\text{LSB}}} \right) - (2^N - 2) \quad (11.25)$$



Integral nonlinearity error (INL)


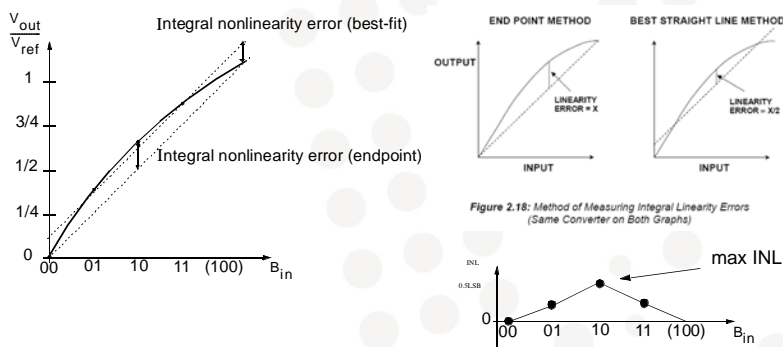


Figure 2.18: Method of Measuring Integral Linearity Errors (Same Converter on Both Graphs)

 - After both offset and gain errors have been removed, the **integral nonlinearity (INL) error** is defined to be the deviation from a straight line. Possible straight lines: endpoints of the converters transfer respons, best-fit straight line such that the difference (or mean squared error) is minimized.



Differential nonlinearity error (DNL)




- Ideally, each analog step size is equal to 1 LSB. **DNL is variation in step size from V_{LSB} (after removal of gain and offset errors).** Ideally DNL is 0 for all digital values. DNL is in “J & M” defined for each digital word, whereas other sometimes refer to DNL as the maximum magnitude of DNL values.



UNIVERSITETET
I OSLO

Monotonicity in DACs

- A monotonic DAC is one in which the output always increases as the input increases (slope of the transfer response is of only one sign.)
- If the maximum DNL error is less than 1 LSB, the DAC is guaranteed to be monotonic.
- A converter is guaranteed to be monotonic if maximum DNL is < 1 LSB (or if INL is less than $\frac{1}{2}$ LSB).
- 3-bit nonmonotonic example in the figure is from Analog-Digital conversion handbook by Analog Devices

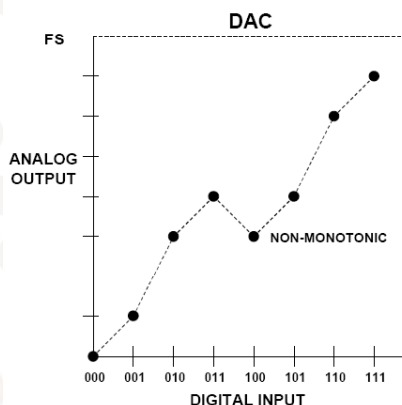

UNIVERSITETET
I OSLO

D/A (DAC) settling time and sampling rate

- In a DAC the **settling time** is defined as the time it takes for the converter to settle within some specified amount of the final value (usually 0.5 LSB).
- The **sampling rate** is the rate at which samples can be continuously converted and is typically the **inverse of the settling time**.
- Different combinations of input vectors give different settling times.

 



Fig 3.9 Risettime 6 bit DAC, input 0 to 128. (Xdivision = 50ns)

Picture from "High-speed data converters fully integrated in CMOS", dissertation for the dr. scient. degree by Leif Hanssen, Ifi, UiO, 1990.



Nyquist Rate D/A Converters

 - 12.1 Decoder-based converters
 - resistor string conv.
 - folded resistor string conv.
 - multiple R-string converters
- 12.2 Binary-Scaled converters
 - binary-weighted resistor converters
 - reduced resistance-ratio ladders
 - R-2R-based converters
 - charge-redistribution switched-capacitor conv.
 - current-mode conv.
- 12.3 Thermometer-code converters
 - thermometer-code current-mode D/A converters
 - single-supply positive-output converters
 - dynamically matched current sources
- 12.4 Hybrid converters
 - resistor-capacitor hybrid converters
 - segmented converters



Some systems exploiting data converters, "Allen & Holberg"


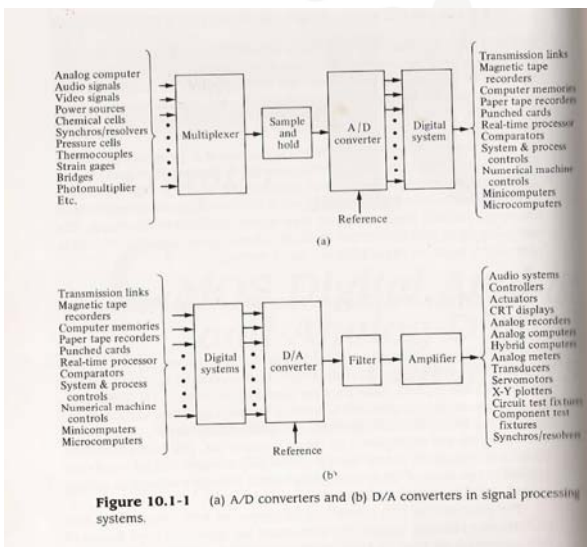


Figure 10.1-1 (a) A/D converters and (b) D/A converters in signal processing systems.

 

Ideal D/A converter




$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}$$

$$V_{out} = V_{ref}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N})$$



Ideal D/A converter

 


12.1 Decoder-Based Converters

- Creates 2^N reference signals and passes the appropriate signal to the output, depending on the digital input word.
- The switching network produces one, and only one, low impedance path between the resistor string and the input of the buffer
- Relatively compact switches if n-channel devices are used instead of transmission gates.




Resistor String Converters (12.1)

 

- Only one path between resistor string and D/A-output
- Guaranteed monotonicity, provided that the voltage follower does not have too large offset
- Compact design when using only n-transistors (no contacts)
- Polysilicon resistors may give resolution up to 10 bit
- Delay through switch network is the major speed limitation of the circuit
- 2^N resistors are required (when only one resistor string is included)

Resistor String Converters (12.1)

 

- High-speed implementation (when compared to the previous one), due to maximum of one switch in series →
- Less resistance through switches
- The switches are controlled by digital logic
- More area for the decoder compared to the previous DAC
- Larger capacitance on the buffer input, due to the 2^N transistors connected to it
- Pipelining may be applied for "moderate speed"
- 2^N resistors are required

Estimating the time constant for n resistors and capacitors in series (ex. 12.2)

Estimating the time constant for n resistors and capacitors in series (ex. 12.2)

time constant due to the first capacitor: RC

1st ———— 2nd ———— 2RC
 1st ———— nth ———— nRC

total: $\tau = RC + 2RC + \dots + nRC = RC(1 + 2 + \dots + n)$

K. Rothman, S. 111: $\sum_{k=1}^{n} k = \frac{n(n+1)}{2}$ (Formelsammlung)

$\tau = RC \left[\frac{(n+1)n}{2} \right]$ für großen $n \rightarrow \tau = RC \left(\frac{n^2}{2} \right)$

n	1	5	10	50	100
$\frac{(n+1)n}{2}$	1	15	55	1275	5050
$\frac{n^2}{2}$	$\frac{1}{2}$	12.5	50	1250	5000


$V_{out} \approx (1 - e^{-t/\tau}) V_p$

$V_{out} = 0.999 V_p$: about 7. τ is needed




Folded Resistor-String Converters 12.1

- Reducing size of digital circuitry and capacitive loading
- 2^N resistors are required
- b_1b_2 : Most significant bits in the 4 bit case (selects one single word line.)
- Structure similar to what can be found in digital memories.
- OBS! NMOS switches here
- Number of transistor junctions connected to the output line is now $2 \sqrt{2^N}$, instead of 2^N
- 4 bit case: 8 instead of 16
- 8 bit case: 32 instead of 256
- 10 bit case: 64 instead of 1024
- When a word line goes high, all the bit lines must be pulled to new levels, limiting speed (no increase equal to the ratio $(2 \sqrt{2^N}) / 2^N$)

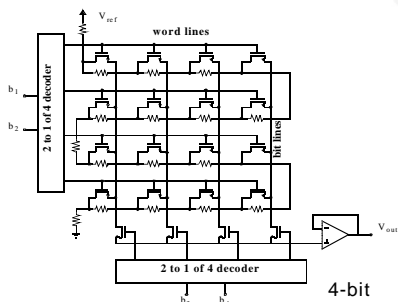


Multiple R-String Converters (12.1)

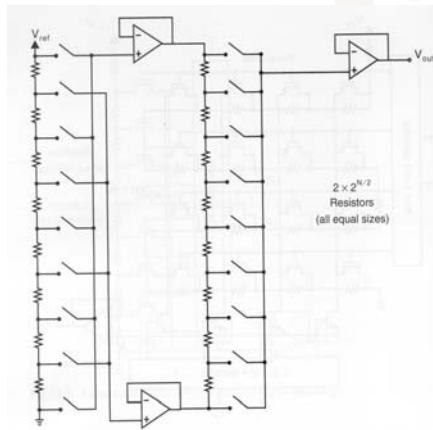


- A second tapped resistor string is connected between buffers whose inputs are two adjacent nodes of the first resistor string, as shown.
- In this 6-bit case the 3 MSBs determine the two adjacent nodes. The 2nd (“fine”) string linearly interpolates between the two adjacent voltages from the first (“coarse”) resistor string
- Additional logic needed to handle polarity switching, related to which intermediate buffer has the highest voltage on the input
- Guaranteed monotonicity assuming matched opamps and voltage insensitive offset voltages
- $2 \times 2^{N/2}$ resistors are required
- Relaxed matching requirements for the 2nd resistor string.
- Ex.: 10 bit, 4 bits for the 1st string, matched to 0.1 %. Requirements for 2nd string? $2^4 \times 0.1 \% = 1.6 \%$

 12.2 Binary-Scaled Converters

- Combining a set of signals that are related in a binary fashion
- Typically currents (resistors or plain current) or binary weighted arrays of charges
- Example: 4-bit binary-weighted resistor DAC:



 Binary-Weighted Resistor Converters (12.2)



4-bit

$$V_{\text{out}} = -R_F V_{\text{ref}} \left(-\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} - \dots \right)$$

- Few switches and resistors
- Large resistor and current ratios (2^N)
- Monotonicity not guaranteed
- Prone to glitches for high-speed operation

Glitches –from Analog Digital Conversion Handbook

Glitch Impulse Area

Ideally, when a DAC output changes it should move from one value to its new one monotonically. In practice, the output is likely to overshoot, undershoot, or both (see Figure 2.94). This uncontrolled movement of the DAC output during a transition is known as a *glitch*. It can arise from two mechanisms: capacitive coupling of digital transitions to the analog output, and the effects of some switches in the DAC operating more quickly than others and producing temporary spurious outputs.

 


Figure 2.94: DAC Transitions (Showing Glitch)

Capacitive coupling frequently produces roughly equal positive and negative spikes (sometimes called a *doublet glitch*) which more or less cancel in the longer term. The glitch produced by switch timing differences is generally unipolar, much larger and of greater concern.

- Glitches waste energy and make noise

Glitches waste energy and produce noise

- Glitches can be seen as unwanted transitions on the output, instead of a monotonous move from one output value to the next
- Mainly the result of different delays occurring when switching different signals
- Potential cures:
 - Exact **matching** in time (difficult)
 - Reducing the bandwidth by placing **C** across R_f in a circuit similar to the one in fig. 12.13
 - Add **S/H** to the output
 - Modify some or all of the digital word from binary to **thermometer code** (most popular)


decimal	Binary b1b0b1	Thermometer code d1d2d3d4d5d6d7
0	000	0000000
1	001	0000001
2	010	0000011
3	011	0000111
4	100	0001111
5	101	0011111
6	110	0111111
7	111	1111111

22. mai 2010

21



Reduced-Resistance-Ratio Ladders (12.2)

 

- Reducing the large resistor ratios (compared to Fig. 12.7, left) in a binary weighted array by introducing a series resistor (right).
- Same relationship to the digital binary signals as in the previous case, but with **one-fourth the resistance ratio** (4/2 - not 16/2)
Somewhat similar to the R-2R ladder structure..



R-2R ladder

R-2R - based structure

V_{ref} is applied to the left end of the ladder. The ladder consists of a series of resistors R and $2R$. At each node, a $2R$ resistor is connected to ground.


Calculations:
 $R'_4 = 2R$
 $R_4 = \frac{2R \cdot 2R}{2R + 2R} = \frac{4R^2}{4R} = R$
 $R'_3 = R + R_4 = R + R = 2R$
 $R_3 = 2R \parallel R'_3 = \frac{2R \cdot 2R}{4R} = R$
 $R'_2 = R + R_3 = R + R = 2R$
 $R_2 = 2R \parallel R'_2 = R$
 $R'_1 = R + R_2 = R + R = 2R$
 $R_1 = 2R \parallel R'_1 = R$
 $R'_i = 2R \text{ for all } i$

Currents and Voltages:
 Therefore: $I_1 = \frac{V_{ref}}{2R}$
 From ②: The voltage at node ② is half of the voltage at ①:
 $I_2 = \frac{V_2}{2R} = \frac{\frac{1}{2} V_{ref}}{2R} = \frac{V_{ref}}{4}$
 $I_3 = \frac{V_3}{2R} = \frac{\frac{1}{2} \cdot \frac{1}{2} V_{ref}}{2R} = \frac{V_{ref}}{8R}$
 And so on...

Resistor Matching:
 Resistors of size $2R$ are used on each node to match the size R resistors to improve matching.



R-2R-Based Converters (12.2)

 

- Only two resistor values
- Improved matching
- → smaller size and better accuracy

$$R'_4 = 2R$$


$$R_4 = 2R \parallel 2R = R$$

$$R'_3 = R + R_4 = 2R$$

$$R_3 = 2R \parallel R'_3 = R$$




4-bit R-2R Resistor Ladder (12.2)

 

- The current is scaled by controlling the switches
- Important to scale the switches accordingly
 - Ensuring equal voltage drop across the switches
- Suited for fast operation
 - V_{out} is the only changing voltage



 R-2R Resistor Ladder with equal current through all switches (12.2)



- Not necessary to scale switch sizes (Equal current)
- Slower due to changing node voltages



Binary weighted current mode DAC (12.2)(fig. 12.13)

 


Fig. 12.13 Binary-weighted current-mode D/A converter.


- Current-mode DACs are very similar to resistor-based converters, but intended for higher speed applications
- The output current is converted to a voltage through the use of R_F



Parallel charge sharing DAC principle

PARALLEL CHARGE SCALING DAC

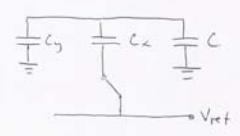
DAC operation based on capacitive voltage division Example: 4-bit DAC, Charge Scaling




$$V_{out} = \frac{C_x}{C_x + C_y + C} V_{ref}$$

→ Make C_x & C_y function of incoming DAC digital word

Reset phase:

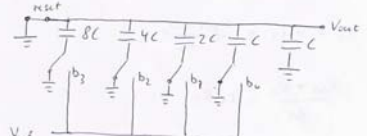

Charge-phase:
input-code 1110:

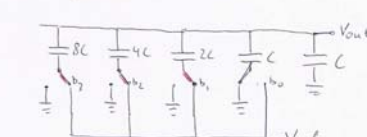


$$V_{out} = \frac{2^3 C + 2^2 C + 2^1 C}{2^4 C} V_{ref} = \frac{(2+4+8)}{16} C \cdot V_{ref}$$



Capacitance ratios defining voltage gain

SWITCHED CAPACITOR GAIN STAGES

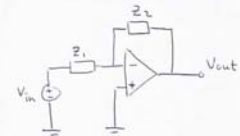


The input-output relation:

$$\frac{V_{out}}{V_{in}} = - \frac{Z_2}{Z_1}$$

If $Z_2 = k \cdot Z_1$, where k is a constant, a (fixed) gain is achieved.

One of the most common functions in analog signal processing is voltage amplification, as shown left (most often used way...)

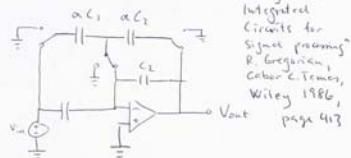Analog MOS Integrated Circuits for Signal Processing
R. Gregorian, Gabriel L. Temes, Wiley 1986, page 413



SC voltage amplifier


$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = - \frac{C_1}{C_2}$$

$H(z)$ is a frequency independent constant.

By switching in different C , the voltage gain may change, depending on dig. input



 Charge-Redistribution Switched Capacitor Converter (12.2) (fig. 12.12)




- By replacing the input capacitor of an SC gain amplifier by a programmable capacitor array (PCA) a charge based converter is obtained
- Employs correlated double sampling (CDS) – insensitive to $1/f$ noise, input-offset voltage and finite amplifier gain.
- An additional sign bit may be realized by interchanging the clock phases
- Carefully generated clock waveforms and a deglitching capacitor are required
- Digital codes must change only when the input-side of the capacitors are connected to ground

Thermometer-Code Converters (Chapter 12.3)- number of 1s represents the decimal value

- + compared to binary counterpart:
- Lower DNL errors
- Reduced glitching noise
- Guaranteed monotonicity
- - compared to binary counterp.:
- Need $2^N - 1$ digital inputs to represent 2^N input values


decimal	Binary b1b2b3	Thermometer code d1d2d3d4d5d6d7
0	000	0000000
1	001	0000001
2	010	0000011
3	011	0000111
4	100	0001111
5	101	0011111
6	110	0111111
7	111	1111111

Thermometer Based 3-bit DAC (12.3)

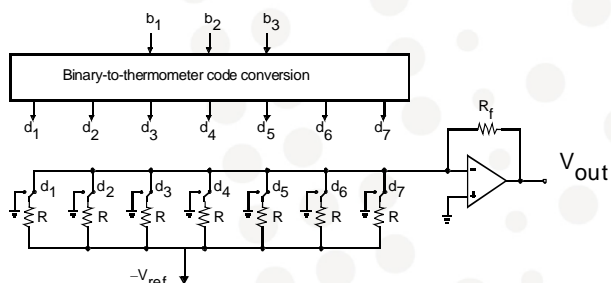


- Equal resistor sizes
- Equal switch sizes
- 2^N resistors required

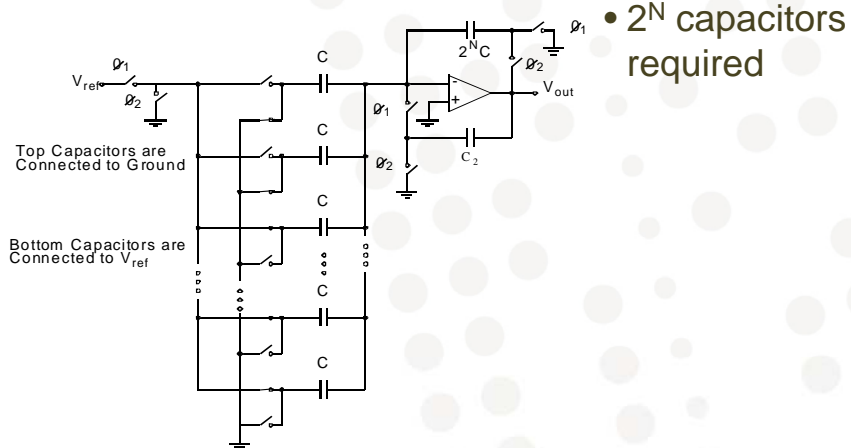Thermometer-Code Charge-Redistribution DAC (12.3) (Fig. 12.16)



Thermometer-code Current-Mode D/A-Converter (12.3)

- Thermometer-code decoder in both row and column, for inherent monotonicity and good DNL
- Current is switched to the output when both row and column lines for a cell are high
- Cascode current source used for improved current matching
- Suited for high speed, with output fed directly into a resistor (50 or 75 Ohms), instead of an output opamp.
- The delay to all switches must be equal (suppress glitching)
- Important that the edges of d_i and d'_i are synchronized

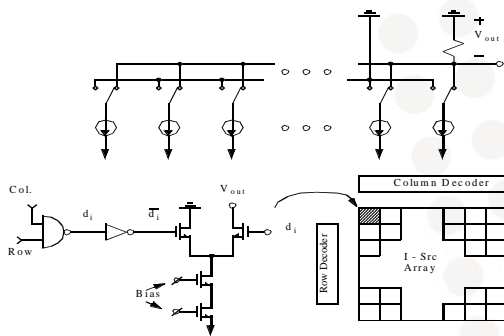

Thermometer-code Current-Mode DAC - example

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. SC-21, NO. 6, DECEMBER 1986

An 80-MHz 8-bit CMOS D/A Converter

TAKAHIRO MIKI, YASUYUKI NAKAMURA, MASAO NAKAYA, SOTOJU ASAI, YOICHI AKASAKA, AND YASUTAKA HORIBA

- Cascode current sources
- Latches connected to decoding
- One gate in the differential pair may be put to a dc level, to improve speed.

 


Fig. 2. Two-step decoding.

 


Fig. 3. High-speed decoding circuit.

 


Fig. 4. Circuit diagram of the LSB current source.

 



Fig. 5. Configuration of current source. (a) Single-transistor configuration. (b) Cascode configuration.

TABLE I
CHARACTERISTICS OF THE DAC

Resolution	8 bit
Settling Time	12.5 ns
Rise/Fall Time	5.5 ns
Integral Linearity Error (DC)	0.38 LSB (Typ.)
Differential Linearity Error (DC)	0.22 LSB (Typ.)
Glitch Energy	100 pJ
Power Consumption	145 mW
Chip Size	1.85 mm x 2.05 mm



Single-Supply Positive-Output Converters

 

- For fast single-supply positive-output
- **One side of each current-steering pair connected to V_{bias} , rather than the inversion of the bit signal**, to maintain current matching. When the current is steered to the output through Q2, the drain-source voltage across the current source, Q3, remains mostly constant if V_{out} stays close to zero, such that Q2 remains in the active region.
- Thus, Q2 and Q3 effectively form a **cascode current source** when driving current to the output.
- Does not need d_1 and d_2 ; reduces complexity and **removes the need for precisely timed edges** to avoid glitches.



UNIVERSITETET
I OSLO

Dynamically Matched Current Sources

(12.3)

- for high resolution

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 23, NO. 6, DECEMBER 1988

A Low-Power Stereo 16-bit CMOS D/A Converter for Digital Audio

HANS J. SCHOUWENAARS, SENIOR MEMBER, IEEE, D. WOUTER J. GROENEVELD,
AND HENK A. H. TERMEER

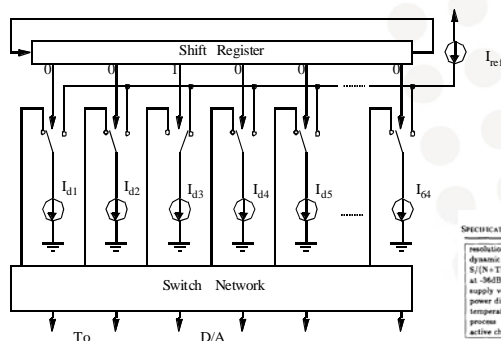


TABLE II
SPECIFICATIONS OF THE D/A CONVERTER

resolution	16 bit
dynamic range	95 dB
S/(N+THD) at 0dB	79 dB
at -50dB	69 dB
supply voltage range	2.5 to 5 V
power dissipation	15 mW at 5 V
temperature range	-20 to 85°C
process	2µm CMOS
active chip area	5 mm ²


- Current sources are **periodically being regulated to ideally the same value (matched) during normal operation**, to ensure proper resolution.
- A “once and for all” matching of each current source is not enough due to mechanisms including temperature drift and gate leakage.



UNIVERSITETET
I OSLO

Dynamically Matched Current Sources

(12.3)

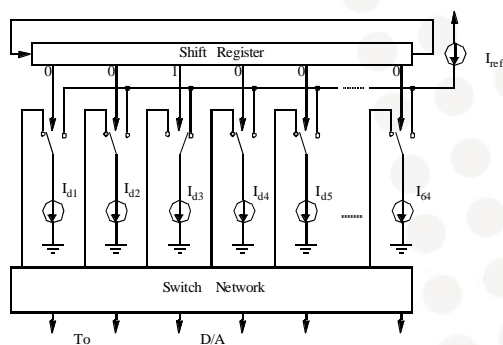


- 6 MSB realized using a thermometer code. (binary array for the remaining bits)
- All currents are matched against I_{ref} , one after one, to get the same precise value on all I_{di} .
- One extra current source is included to provide continuous operation, even when one of the sources is being calibrated.

ifi

 UNIVERSITETET
I OSLO

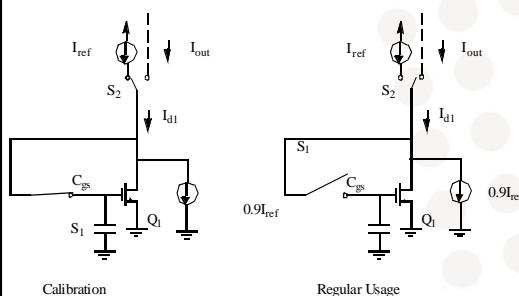Dynamic matched current sources – method for calibration




- I_{di} is connected to I_{ref} during calibration. This places whatever voltage is necessary across the parasitic C_{gs} so that I_{di} equals I_{ref} . When S_i is opened I_{di} remains nearly equal to I_{ref} .
- Major limitation in matching the 64 current sources is due to differences in clock feedthrough and charge injection of the switches S_i . → have relatively large C_{gs} and V_{gs} (large V_{gs} so that a certain voltage difference will cause a smaller current deviation.)
- Using $0.9I_{ref}$ in parallel makes Q_1 need only to source a current near $0.1 I_{ref}$. With such an arrangement a large low-transconductance device can be used (ex.: $W/L=1/8$)

ifi

 UNIVERSITETET
I OSLO

Segmented Converters (12.4)

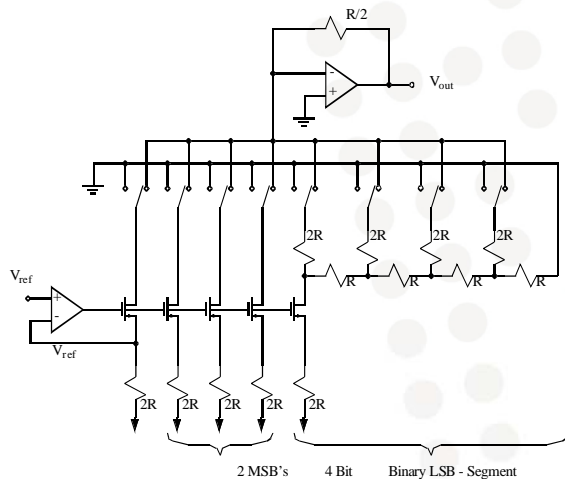

- Combination of thermometer- and binary
- 2 MSB's are thermometer (reduces glitches)
- 4 LSB's are binary
- High bits switched to the output, low bits to ground

A few published DACs

Publication year	SFDR @Nyquist [dB]	ENOB @ Nyquist	Nyquist update rate, [Ms/s]	Power consumpt. [mW]	Area [mm ²]	Supply voltage [V]	Technology [nm]	other	Reference
2009	>60dB	9.7	1000	188			65	Current steering	Lin et al., ISSCC '09
2008	80	12.9	11	119	0.8	1.8	180	"current steering"	Radulov, APPCAS '08
2007	59	9.5	200 @3.3 V	56	2.25	3.3	180	"current steering"	Mercer, JSSC, Aug. '07
2004	40	6	250	23	0.14	1.8	180	"binary weighted"	Deveugele, JSSC, July '04
2001	61	9.84	1000	110	0.35	3.0	350	"current steering"	Van den Bosch, JSSC, Mar. '01
1988	95	15.45	0.044	15	5	2.5-5	2000		Schouwenars, JSSC, Dec. '88

Next Tuesday (9/3-08):

- Chapter 13 Nyquist Analog-to-Digital Converters



UNIVERSITETET
I OSLO

Additional literature

- Phillip E. Allen, Douglas R. Holberg: **CMOS Analog Circuit Design**, Holt Rinehart Winston, 1987.
- R. Gregorian, G. Temes: **Analog MOS Integrated Circuits for Signal Processing**, Wiley, 1986
- Leif Hanssen: High Speed Data Converters Fully Integrated in CMOS, dissertation for the dr. scient. Degree, University Of Oslo, 1990.
- A/D , D/A Conversion Handbook, Analog Devices.
- Lecture Notes, University of California, Berkeley, EE247 Analog Digital Interface Integrated Circuits, Fall 07;<http://inst.eecs.berkeley.edu/~ee247/fa07/>



UNIVERSITETET
I OSLO



ifj

Nyquist Rate Analog-to-Digital Converters

Tuesday 9th of March, 2009, 9:15 – 11:00

Snorre Aunet, sa@ifj.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

 UNIVERSITETET
I OSLO

Last time – and today, Tuesday 9th of March:

Last time:

- 12.1 Decoder-Based Converters
- 12.2 Binary-Scaled Converters
- 12.3 Thermometer-Code Converters
- 12.4 Hybrid Converters

Today – from the following chapters:

- 13.1 Integrating Converters
- 13.2 Successive-Approx. Converters
- 13.3 Algorithmic (or cyclic) A/D Converters
- 13.4 Flash (or parallel) converters
- 13.5 Two-Step A/D converters
- 13.6 Interpolating A/D Converters (16/3-10)
- 13.7 Folding A/D Converters (16/3-10)
- 13.8 Pipelined A/D Converters
- 13.9 Time-Interleaved A/D Converters



Different A/D Converter Architectures

Low-to-Medium Speed High Accuracy	Medium Speed Medium Accuracy	High Speed Low-to-Medium Accuracy
Integrating	Successive approximation	Flash
Oversampling	Algorithmic	Two-Step
		Interpolating
		Folding
		Pipelined
		Time-interleaved



Different ADCs depending on needs

 


Figure 1. ADC architectures, applications, resolution, and sampling rates.

 


Fig. 2. ADC sample rate vs. ENOB from 1987 to 2005.

Which ADC Architecture Is Right for Your Application?


By Walt Kester [walt.kester@analog.com]

IEEE 2005 CUSTOM INTEGRATED CIRCUITS CONFERENCE
Scaling of Analog-to-Digital Converters into Ultra-Deep-Submicron CMOS

Y. Chin¹, B. Nikolic², and P. R. Gray²
¹ Electrical and Computer Engineering, University of Illinois at Urbana-Champaign
² Electrical Engineering and Computer Sciences, University of California at Berkeley



A/D-conversion – Basic Principle

 


$$V_{ref}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}) = V_{in} \pm x$$

$$\text{where } \left(-\frac{1}{2}V_{LSB} < x < \frac{1}{2}V_{LSB}\right)$$

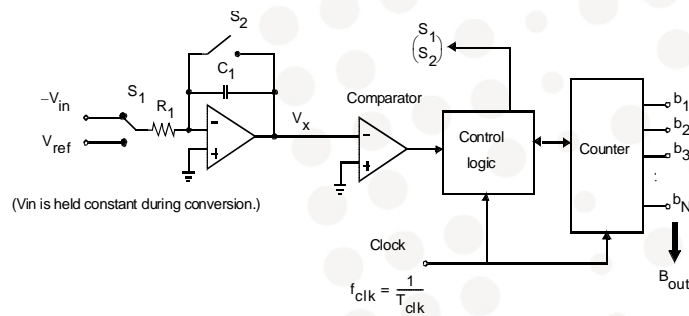- The analog input value is mapped to discrete digital output value
 - Quantization error is introduced



Integrating Converters (13.1)



- $V_x(t) = V_{in} t / RC$ (V_x ramp derivative depending on V_{in})
- High linearity and low offset/gain error
- Small amount of circuitry
- Low conversion speed
 - $2^{N+1} * 1/T_{clk}$ (Worst case)



Integrating Converters

- The digital output is given by the count at the end of T_2
- The digital output value is independent of the time-constant RC

Dual slope ADC

POSITIVE INTEGRATOR USED IN DUAL-SLOPE ADCS

$$i_1 = i_2$$
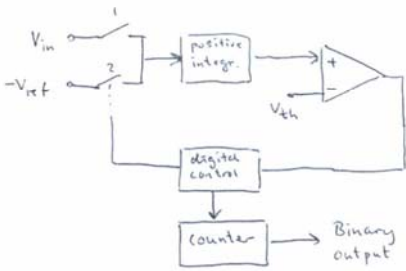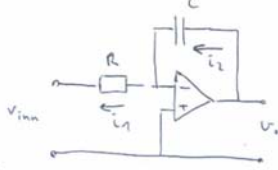
$$\frac{V_{in}}{R} = C \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{dt} = \frac{V_{in}}{RC}$$

$$V_{out} = \frac{1}{RC} \int_0^t V_{in} dt$$

$$= \frac{V_{in}}{RC} t$$

Example: 16-bit two-slope ADC with $V_{in} = 3V$, $V_{max} = 4V$ and $T_1 = 20\mu s$. $RC = \text{constant? Clock?}$

$$f_{clk} = \frac{1}{T_{clk}} = \frac{2^{16}}{20\mu s} \approx 3.28 \text{ MHz}$$


equation (17.15):

$$V_x = \frac{V_{in} T_1}{RC} \Leftrightarrow 4V = \frac{3V \cdot 20\mu s}{RC}$$

$$\uparrow$$

$$RC = 15 \mu s$$

 
Integrating Converters – careful choice of T_1 can attenuate frequency components superimposed on the input signal



- In the above case, 60 Hz and harmonics are attenuated when T_1 is an integer multiple of $1/60$ Hz.
- Sinc-response with rejection of frequencies multiples of $1/T_1$



Successive approx ADC algorithm (13.2)

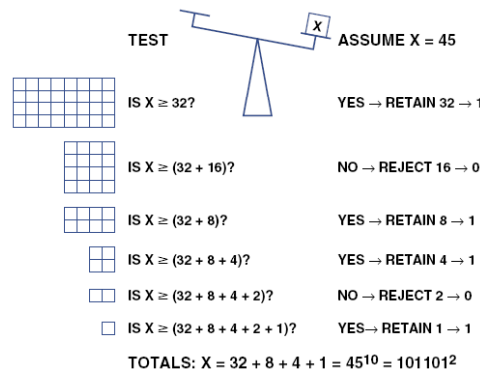

- If we have weights of 1 kg, 2 kg, 4 kg, 8 kg, 16 kg, 32 kg and will find the weight of an unknown X assumed to be 45 kg.

• 101101_2

$$= 1 \cdot 32 + 0 \cdot 16 + 1 \cdot 8 + 1 \cdot 4 + 0 \cdot 2 + 1 \cdot 1$$

$$= 45_{10}$$


Figure 4. Successive-approximation ADC algorithm using balance scale and binary weights.

Which ADC Architecture Is Right for Your Application?

By Walt Kester [walt.kester@analog.com]




Successive-Approximation Converters

 



- Uses **binary-search** algorithm
- Accuracy of 2^N requires N steps
- The digital signal accuracy is within $\pm 0.5 V_{ref}$
- Medium speed
- Medium resolution
- Relatively moderate complexity

DAC-Based Successive Approximation

 

- $V_{D/A}$ is adjusted until the value is within 1LSB of V_{in}
- Starts with MSB and continues until LSB is found
- Requires DAC, S/H, Comparator and digital logic
- The DAC is typically limiting the resolution

Succ. Approx ADC, example 13.2

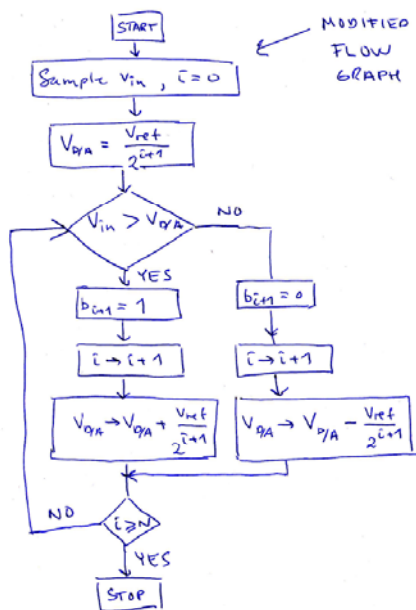 

EX. 13.2 $V_{ref} = 8V$, $V_{in} = 2.831V$

$V_{D/A} = \frac{V_{ref}}{2^{i+1}} = \frac{8V}{2^1} = 4V$

$V_{in} > V_{D/A} \Leftrightarrow 2.831V > 4V? \rightarrow \text{NO!}$
 $b_{i+1} = b_{0+1} = b_1 = 0$
 $i \rightarrow i + 1 = 0 + 1 = 1$
 $V_{D/A} \rightarrow 4V - \frac{8}{2^2}V = 4V - 2V = 2V$
 $i = 1 \geq 3? \rightarrow \text{NO}$

$V_{in} > V_{D/A} \Leftrightarrow 2.831V > 2V? \rightarrow \text{YES!}$
 $b_{i+1} = b_{1+1} = b_2 = 1$; $b_2 = 1$
 $i \rightarrow i + 1 = 1 + 1 = 2$
 $V_{D/A} \rightarrow V_{D/A} + \frac{V_{ref}}{2^{i+1}} = 2V + \frac{8}{2^3}V = 2V + 1V = 3V$
 $i = 2, 2 \geq 3? \rightarrow \text{NO!}$

$V_{in} > V_{D/A} \Leftrightarrow 2.831V > 3V? \rightarrow \text{NO!}$
 $b_3 = 0$
 $i \rightarrow 2 + 1$
 $V_{D/A}$ update, $3 \geq 3 \Rightarrow \text{STOP}$

Charge-Redistribution A/D-Converter (unipolar)

- Instead of using a separate DAC and setting it equal to the input voltage (within 1 LSB) as for the DAC based converter from figure 13.5, one can use the error signal equaling the difference between the input signal, V_{in} , and the DAC output, $V_{D/A}$

 


Fig. 13.6 Flow graph for a modified successive approximation (divided remainder).



Numbers from 13.2 setting an error signal V equal to $V_{in} - V_{D/A}$ – modified succ. approx as in fig. 13.6


EXAMPLE 13.2 USING MODIFIED SUCCL. APPROX (DIVIDED REMINDER)
 Error signal, $V = V_{in} - V_{D/A}$

Fig. 13.6

page 494:
 The error signal, V , equals the difference between the input signal, V_{in} , and the D/A output

$V = +2.831V - 4V = -1.169V$
 $-1.169 > 0?$ NO, $b_1 = 0$
 $V \rightarrow -1.169V + 2V = 0.831V$
 $i = i + 1 = 2$
 $i = 2 > 3?$ NO
 $0.831V > 0?$
 YES
 $b_2 = 1$
 $V \rightarrow (0.831 - 8/8)V = -0.169V$
 $i = 2 + 1 = 3$
 $i > 3?$ NO
 $-0.169V > 0?$
 NO $\rightarrow b_3 = 0$
 $b_1 b_2 b_3 = 010$
 (like in ex. 13.2)

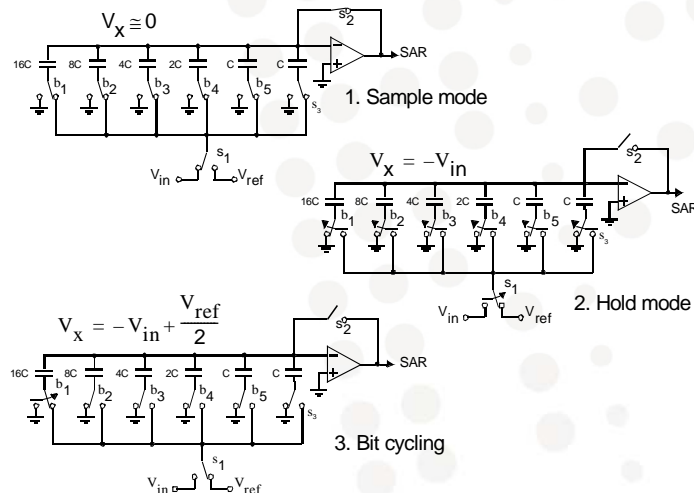Unipolar Charge-Redistribution A/D-Converter



ifi

UNIVERSITETET
I OSLO

Charge-Redistribution A/D-Converter

- Sample mode:
 - All capacitors charged to V_{in} while the comparator is reset to its threshold voltage through S_2 . The capacitor array is performing S/H operation.
- Hold mode:
 - The comparator is taken out of reset by opening S_2 , then all capacitors are switched to ground. V_x is now equal to $-V_{in}$. Finally S_1 is switched so that V_{ref} can be applied to the capacitors during bit-cycling.
- Bit-cycling:
 - The largest capacitor is switched to V_{ref} . V_x goes to $-V_{in} + V_{ref}/2$. If V_x is negative, then V_{in} is greater than $V_{ref}/2$ and the MSB capacitor is left connected to V_{ref} . Otherwise the MSB capacitor is disconnected and the same procedure is repeated N times

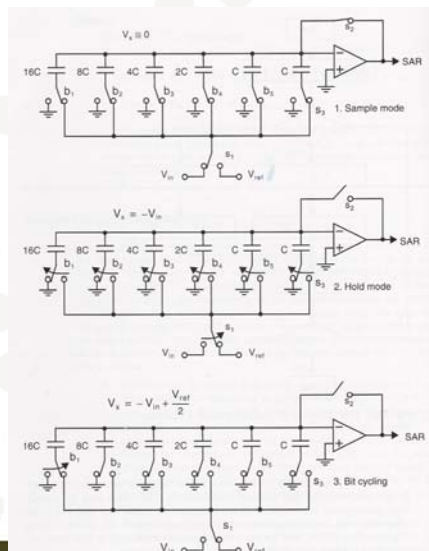


Fig. 13.7 A 5-bit unipolar charge-redistribution A/D converter.

ifi

UNIVERSITETET
I OSLO

EX. 13.3 pp. 497

Find intermediate node voltages at V_x during the operation of the 5-bit charge-redistribution conversion shown in fig. 13.7. Assume $8C$ as a parasitic cap. at V_x . $V_{ref} = 5V$, $V_{in} = 1.23V$

SAMPLE MODE :

$V_x = 0$

Top-plates to V_{ref} to minimize parasitic capacitance at node V_x .

$$V_{out} = \frac{C_x}{C_x + C_y + C} \cdot V_{ref}$$

C_x and C_y functions of digital word/switching

- 1) Sample mode
- 2) Hold mode
- 3) Bit-cycling

HOLD MODE :

$V_x = \frac{32}{32+8} \cdot (-V_{in})$

$V_x = \frac{32}{40} \cdot (-1.23V) = -0.984V$

pp. 396:

$C_{x1} < C_{x2}$

22. mai 2010 19

BIT CYCLING

$V_{ref} = 5V$

- b_1 IS Switched, controlling the $16C$ capacitor:

$$V_x = -0.984V + \frac{16}{(32+8)} \cdot 5V$$

$$= -0.984V + 2V = 1.016V$$

$$V_x > 0 \Rightarrow \underline{b_1 = 0}$$
- b_2 IS Switched:

$$V_x = -0.984V + \frac{8}{(32+8)} \cdot 5V$$

$$V_x = -0.984V + 1V = 0.016V$$

When b_2 is switched $V_x > 0$, so $b_2 = 0$ and V_x IS set back to $-0.984V$ by switching b_2 back to gnd.
- b_3 IS Switched:

$$V_x = -0.984V + \frac{4}{40} \cdot 5V = -0.484V$$

V_x IS now $< 0 \Rightarrow \underline{b_3 = 1}$ and b_3 left connected to V_{ref} .

22. mai 2 20 20

$V_{ref} = 5V$

b_1 b_2 b_3 b_4 b_5

$b_{out} = b_1 b_2 b_3 b_4 b_5 = 00111$

$\frac{5V}{2^5} = \frac{5V}{32} = 0.15625V$

DAL: $V_{out} = V_{ref} (b_1 \cdot 2^{-1} + b_2 \cdot 2^{-2} + b_3 \cdot 2^{-3} + b_4 \cdot 2^{-4} + b_5 \cdot 2^{-5})$
 $= 5V (0.125V + 0.0625V + 0.03125V) = 5V (0.21875) = 1.09375V$

• b_4 is switched:

$$V_x = -0.984V + \frac{6}{40} \cdot 5V = -0.984V + 0.75V = -0.234V$$

$V_{x4} < 0 \Rightarrow b_4 = 1$

• b_5 is switched:

$$V_{x5} = -0.234V + \frac{1}{40} \cdot 5V = -0.109V$$

$V_{x5} < 0 \Rightarrow b_5 = 1$

May also be expressed from the drawings and the orig. Step-plot with:

$$\frac{32}{32+8} (-V_{in}) + \frac{7}{32+8} \cdot 5V = -0.984V + 0.875V = -0.109V$$

$V_A = 1.09375V = 1.23V = -0.12625V$

22. mai



Succ. Approx. Approach flow graph

EX. 13.3 VIEWED IN ANOTHER WAY, AND WITHOUT PARASITICS.

$V_{in} = 1.23V$
 $V_{ref} = 5V$

$b_1=0$ $b_2=0$ $b_3=1$ $b_4=1$ $b_5=1$

$5V : 2 = 2.5V$
 $2.5V : 2 = 1.25V$
 $1.25V : 2 = 0.625V$
 $0.625 + 0.3125V = 0.9375V$
 $5V : 32 = 0.15625V$
 $(0.625 + 0.3125 + 0.15625)V = 1.09375V$


```

graph TD
    Start([Start]) --> Sample[Sample V_in, V_DA = 0, i = 1]
    Sample --> Decision{V_in > V_DA}
    Decision -- No --> Bi0[b_i = 0]
    Decision -- Yes --> Bi1[b_i = 1]
    Bi0 --> UpdateDA[V_DA -> V_DA - (V_ref / 2^i)]
    Bi1 --> UpdateDA[V_DA + V_ref / 2^i]
    UpdateDA --> IncI[i -> i + 1]
    IncI --> DecisionI{I >= N}
    DecisionI -- No --> Decision
    DecisionI -- Yes --> Stop([Stop])
    
```

22. mai 2010




Signed Charge redistribution A/D

 

(Fig. 13.8)

- Resembling the unipolar version (Fig. 13.7)
- Assuming V_{in} is between $\pm V_{ref}/2$
- Disadvantage: V_{in} attenuated by a factor 2, making noise more of a problem for high resolution ADCs
- Any error in the MSB capacitor causes both offset and a sign-dependent gain error, leading to INL errors

 Resistor-Capacitor Hybrid (figure 13.9 in "J & M")



- First all capacitors are charged to V_{in} before the comparator is being reset.
- Next a succ. approx. conversion is performed to find the two adjacent resistor nodes having voltages larger and smaller than V_{in}
- One bus will be connected to one node while the other is connected to the other node. All of the capacitors are connected to the bus having the lower voltage.
- Then a successive approximation using the capacitor-array network is done, starting with the largest capacitor...

Speed estimate for charge-redistribution converters


 


Fig. 13.12 Simplified model of a capacitor array during the sampling time.

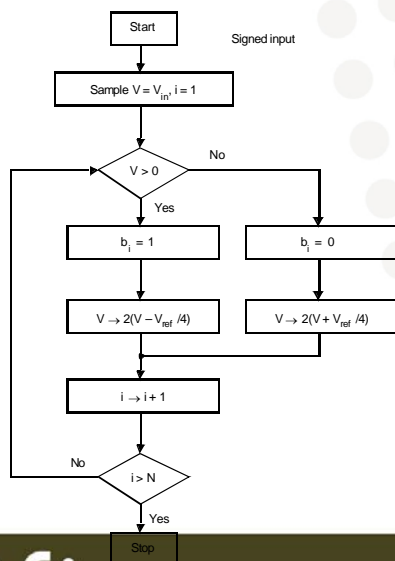- RC time constants often limit speed
 - Individual time constant due to the 2C cap.: $(R_{s1}+R+R_{s2})2C$
 - (R ; bit line)
 - $\tau_{eq}=(R_{s1}+R+R_{s2})2^N C$, for the circuit in fig. 13.12
 - For better than 0.5 LSB accuracy: $e^{-T/\tau_{eq}} < 1/(2^{N+1})$, T = charging time
 - $T > \tau_{eq} (N+1) \ln 2$
- $$= 0.69(N+1)\tau_{eq}$$
- 30 % higher than from Spice simulations ("J & M")




Algorithmic (or Cyclic) A/D Converter (13.3)



- Similar to the Successive approximation converter
- Constant V_{ref}
- Doubles the error each cycle, instead of halving the reference voltage in each cycle, like succ. approx. conv.
- Requires an accurate multiply-by-2 amplifier
- Accuracy can be improved by operating in four cycles (instead of two)
- compact




Ratio-Independent Algorithmic Converter

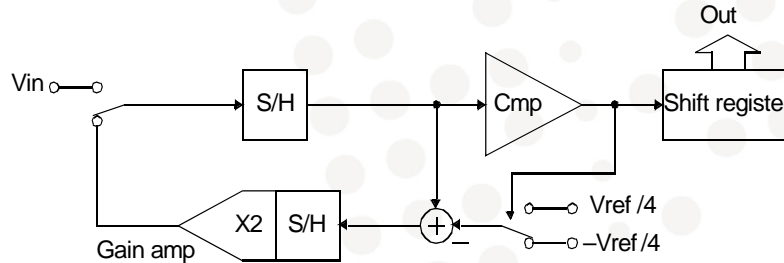


- Simple circuitry
- Due to the cyclic operation the circuitry are reused in time
- Fully differential circuits normally used

Ratio-Independent Algorithmic Converter

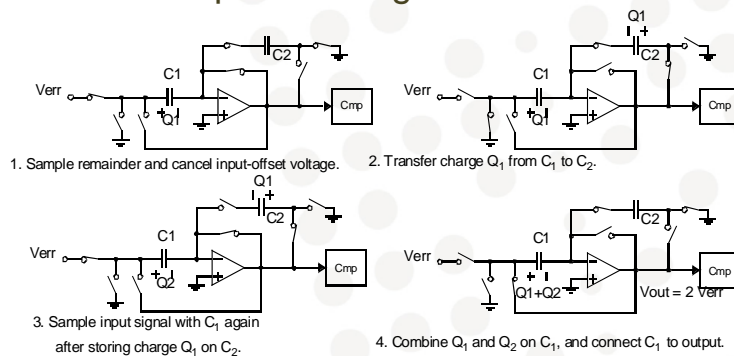


- The basic idea is to sample the input signal twice using the same capacitor. During the 2nd sampling the charge from the 1st capacitor is stored on a 2nd capacitor whose size is unimportant. After the 2nd sampling both charges are recombined into the 1st capacitor which is then connected between the opamp input and output.
- Does not rely on capacitor matching, is insensitive to amplifier offset.

Flash (Parallel) Converters (13.4)

 

- High speed – among the fastest
- 2^N comparators in parallel, each connected to different nodes – area consuming
- High power consumption
- Thermometer-code output fed into decoder
- NANDs used for simpler decoding and error detection (bubble error)
- Differential comparator required to ensure sufficient PSSR
- Top and bottom resistors chosen to create the 0.5 LSB offset in an A/D converter

Flash converter

 

One NAND-gate will have a 0 output. All other NAND-gate outputs will be 1. This also allows for error checking by checking for more than one 0 output.

(See fig 13.16 page 508)

Any comparator connected to a resistor string node where V_{ref} is larger than V_{in} will have a 1 output.

Clocked CMOS comparator

 



Fig. 13.17 A clocked CMOS comparator.

- When the clock ("phi") is high, the inverter is set to its bistable point, $V_{in} = V_{out} (= V_{DD}/2)$. The other (left) side of C is charged to V_{ri} .
- When the clock ("phi") goes low, the inverter switches, depending on the voltage difference between V_{ri} and V_{in} . ($V_{ri} > V_{in}$; 1 output, $V_{ri} < V_{in}$; 0 output from inv.)
- Differential inverters helps poor PSRR with this simple comparator solution.

Issues in Designing Flash A/D Converters

- **Input Capacitive Loading:** The large number of comparators connected to V_{in} results in a large capacitive load on at the input node which increases power and reduces speed
- **Comparator Latch-to-Track Delay:** The internal delay in the comparator when going from latch to track mode
- **Signal and/or Clock Delay:** Differences in signal/clock delay between the comparators may cause errors. Example: A250-MHz, 1-V peak input-sinusoid converted with 8-bit resolution requires a precision of 5ps. Can be reduced by matching the delays and capacitive loads on the signal/clock.
- **Substrate and Power-Supply Noise:** For a 8-bit converter with $V_{ref}=2V$ only 7.8mV of noise injection is required to introduce an error of 1LSB. The problem can be reduced by proper layout (Shielding, Differential clocks, Separate power supplies, and symmetrical layout)
- **Bubble Error Removal:** Comparator metastability may introduce wrong thermometer code (a single 1 or 0 in between opposite values)
- **Flashback:** Caused by latched comparators. When the comparator is switched from track to latch mode a charge glitch is introduced at the input. The problem is reduced by using a preamplifier and input impedance matching

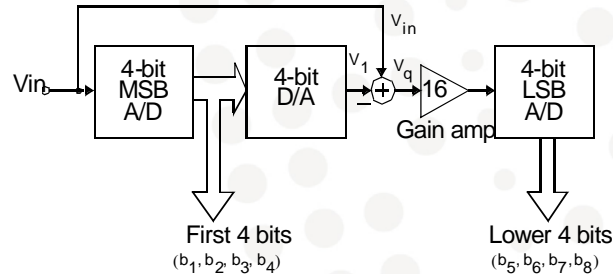
Two-Step (Subranging) A/D Converters (13.5)



- Popular choice for **high-speed medium accuracy** converters (8-10 b)
- Less area and power consumption than a Flash ADC
- The MSB's are converted during the first step. In the next step the remaining error is converted into the LSB's
- Speed is limited by the Gain Amplifier
- Requires N-bit accuracy for all components (May be relaxed by using Digital Error Correction)



 Digital Error Correction for two-step A/D



- The accuracy requirements on the input ADC is relaxed due to the error corr.. 4-bit for MSb converter



Pipelined ADCs (13.5) Once the first stage has completed it's work it immediately starts working on the next sample

- Small area

The pipelined ADC has its origins in the *subranging* architecture, first used in the 1950s. A block diagram of a simple 6-bit, two-stage subranging ADC is shown in Figure 11.


 


Figure 11. 6-bit, two-stage subranging ADC.

The output of the SHA is digitized by the first-stage 3-bit sub-ADC (SADC)—usually a flash converter. The coarse 3-bit MSB conversion is converted back to an analog signal using a 3-bit sub-DAC (SDAC). Then the SDAC output is subtracted from the SHA output, the difference is amplified, and this “residue signal” is digitized by a second-stage 3-bit SADC to generate the three LSBs of the total 6-bit output word.

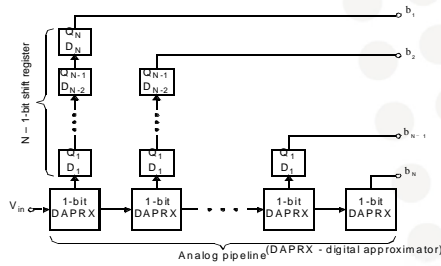

Pipelined ADC -example

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 40, NO. 7, JULY 2005

A Cost-Efficient High-Speed 12-bit Pipeline ADC in 0.18- μ m Digital CMOS

Terje Nortvedt Andersen, Bjørnar Hernes, Member, IEEE, Atle Briskemyr, Frode Telsto, Johnny Bjørnsen, Member, IEEE, Thomas E. Bonnerud, and Øystein Moldsvor

 
 
 


Fig. 9. SFDR, SNR, and SNDR versus input frequency. The conversion rate and signal swing are 110 MS/s and 75 mV_{rms}, respectively.

 


Fig. 7. Power dissipation versus conversion rate. The input frequency and signal swing are 10 MHz and 75 mV_{rms}, respectively.

Nominal sampling rate	110 MS/s
Technology	0.18 μ m digital CMOS
Nominal supply voltage	1.8 V
Resolution	12 bit
Full scale analog input	$2V_{FS}$
Area	0.86 mm ²
Power consumption	97 mW
DNL	± 1.2 LSB
INL	± 1.5 LSB
SNR ($f_c=10$ MHz)	67.1 dB
SNDR ($f_c=10$ MHz)	64.2 dB
SFDR ($f_c=10$ MHz)	69.4 dB
ENOB ($f_c=10$ MHz)	10.4 bit



 


Fig. 12. Figure of Merit (FOM) versus $1/A$ for 12-bit ADCs. f_{IN} is given in MS/s, A is given in mm² and f_{IN} is given in mW.

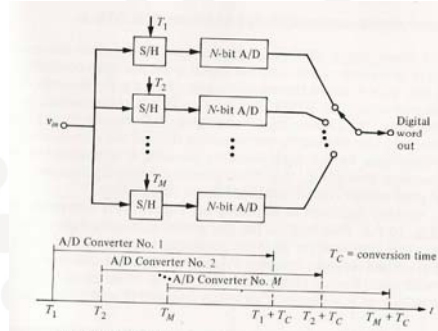

Time-Interleaved A/D-converter (13.9)

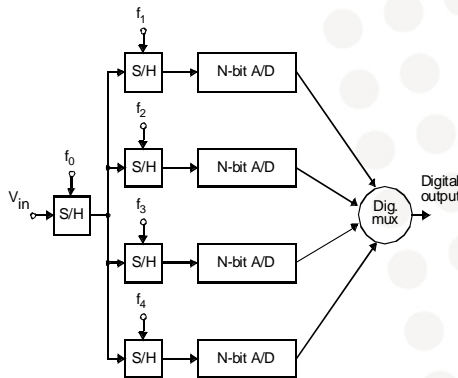

- Very high speed (figure to the right from “Allen & Holberg”)
- f_0 is four times higher than $f_1 - f_4$, which in addition is slightly delayed
- Only the S/H and the MUX must run on the highest frequency
- Tones are introduced at multiples of f_0/N



Time-Interleaved – best compromise between complexity and sampling rate – may be used for different architectures [Elbjornsson '05]


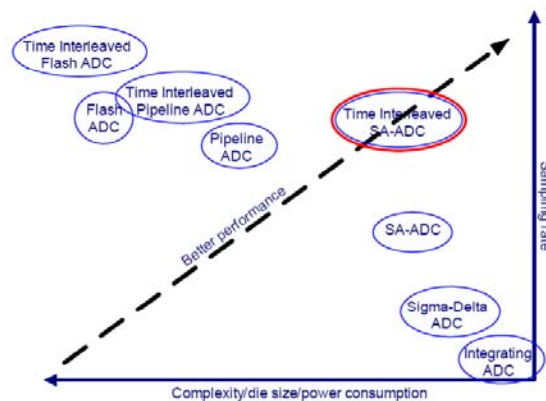


Figure 7 Comparison between ADC architectures. The time interleaved successive approximation ADC gives the best compromise between complexity and sampling rate.

 

Dynamic range


- Dynamic range is defined as the power of the maximum input signal range divided by the total power of the quantization noise and distortion
- Often referred to as **Signal-to-Noise-and-Distortion** range
- $S/(N+D)$
- SINAD



ifi

UNIVERSITETET
I OSLO

 Analog and digital supply voltages are reduced as technology scales



Some ADC trends:

- Limited dynamic range at low supply voltages remains the utmost challenge for **high-resolution** Nyquist converters.
- Oversampling converters will dominate this arena in the future
- Linearity correction with **digital correction** is becoming prevalent

Fig. 1. Scaling of supply and threshold voltages.

IEEE 2005 CUSTOM INTEGRATED CIRCUITS CONFERENCE

22. mai 2010

Scaling of Analog-to-Digital Converters into Ultra-Deep-Submicron CMOS

40

ifi

Y. Chiu¹, B. Nikolic², and P. R. Gray²

¹ Electrical and Computer Engineering, University of Illinois at Urbana-Champaign
² Electrical Engineering and Computer Sciences, University of California at Berkeley

UNIVERSITETET
I OSLO

Nyquist ADCs at ISSCC; FOM, Effective Number of Bits

$$FOM = \frac{P}{2^{2ENOB} f_s}$$

 


Fig. 22. FOM as a function of effective number of bits and technology.

- FOM: Figure of Merit
- High-resolution conv.: FOM minimum at about $10^{-17}J/step$
- 6-bit ADCs : FOM about 4 orders of magnitude worse than 14 bit converters, suggesting that there is much to be gained by designing more efficient 6-bit ADCs
- Better ENOB reported for 350 nm than 250 nm, 180 nm and 130 nm
- Data from ISSCC up to 2005.

Analog Circuit Design in Nanoscale CMOS Technologies

Classic analog designs are being replaced by digital methods, using nanoscale digital devices, for calibrating circuits, overcoming device mismatches, and reducing bias and temperature dependence.

By LARRY L. LEWIS, Life Senior Member IEEE, TAOHONG YU, Senior Member IEEE, CARSTEN WULF, Member IEEE, and KENNETH MARTIN, Fellow IEEE

22. mai 2010

41



Nyquist ADCs at ISSCC; FOM, Sampling rate

$$FOM = \frac{P}{2^{2ENOB} f_s}$$

 


Fig. 23. FOM cliff for Nyquist ADCs in ISSCC 2000-2007.

Vol. 97, No. 10, October 2009 | PROCEEDINGS OF THE IEEE

- Maximum Sampling frequency (Usually faster is better) and FOM.
- ISSCC 2000-2007 (90 nm, 130 nm, 180 nm technologies)
- Small improvement in sampling frequency in going to finer technologies, mainly due to reduced capacitance.

22. mai 2010

Analog Circuit Design in Nanoscale CMOS Technologies

Classic analog designs are being replaced by digital methods, using nanoscale digital devices, for calibrating circuits, overcoming device mismatches, and reducing bias and temperature dependence.

By LARRY L. LEWIS, Life Senior Member IEEE, TAOHONG YU, Senior Member IEEE, CARSTEN WULF, Member IEEE, and KENNETH MARTIN, Fellow IEEE

42



Publication year	SFDR @Nyquist [dB]	ENOB @ Nyquist	Nyquist update rate, [Ms/s]	Power consumpt. [mW]	Area [mm ²]	Supply voltage [V]	Technology [nm]	other	Reference
2006	55	8.5	1000	250	3.5	1.2	130	Time interleaved	Gupta et al IEEE JSSC '06
2007		4	2500	24	0.057	1.2	130	"Pipelined flash"	Wang et al, IEEE Trans. Instr. Meas.
2007		5	500	6	0.9	1.2	65	Time interleaved succ. approx	Ginsburg et al IEEE JSSC '07
2007		8	100	30	2.04	1.0	180	Switched opamp pipelined	Wu et al, IEEE JSSC '07
2008		10	30	22	0.7	1.8	180	pipelined	Li et al, IEEE JSSC '08
2009	81	13		0.073		0.7	180	Delta-sigma	Chae, JSSCC Feb. '09
2009	27.5	4.3	1750	2.2	0.02	1.0	90	"folding flash"	Verbruggen, JSSCC, Mar. '09
2009	10		1.2	12.2	0.354	3.3	350	Continuous time sigma delta	TCAS-II, Jan. '09

22. mai 2010

43



UNIVERSITETET I OSLO

Sampling-time uncertainty

- Variation in output voltage caused by variations in the time of sampling

Consider the following input signal: $V_{in} = \frac{V_{ref}}{2} \sin(2\pi f_{in} t)$

If the variation in sampling time is Δt , following equation must be satisfied to keep ΔV less than 1LSB

$$\Delta t < \frac{V_{LSB}}{\pi f_{in} V_{ref}} = \frac{1}{2^N \pi f_{in}}$$



UNIVERSITETET I OSLO

Additional literature

- Phillip E. Allen, Douglas Holberg: *CMOS Analog Circuit Design*, Holt Rinehart Winston, 1987.
- Jonas Elbornsson: *White paper on parallel successive approximation ADC*, Mathcore Engineering AB, 2005.
- R. Gregorian, G. Temes: *Analog MOS Integrated Circuits for Signal Processing*, Wiley, 1986
- D. M. Gingrich Lecture Notes, University of Alberta, Canada
<http://www.piclist.com/images/ca/ualberta/phys/www/http/~gingrich/phys395/notes/phys395.html>
- Walt Kester: Which ADC is right for your application?
- Y. Chiu, B. Nicolic, P. R. Gray: *Scaling of Analog-to-Digital Converters into Ultra-Deep-Submicron CMOS*, Proceedings of Custom Integrated Circuits Conference, 2005.
- Lecture Notes, University of California, Berkeley,
EE247 Analog Digital Interface Integrated Circuits, Fall 07; <http://inst.eecs.berkeley.edu/~ee247/fa07/>
- Lanny L. Lewyn, Trond Ytterdal, Carsten Wulff, Kenneth Martin: "Analog Circuit Design in Nanoscale CMOS Technologies", Proceedings of the IEEE, October 2009.
- James L. McCreary, Paul R. Gray: "All-MOS Charge Redistribution Analog-to-Digital Conversion Techniques – part 1", IEEE Journal of Solid-State Circuits, December 1975.

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 40, NO. 7, JULY 2005

A Cost-Efficient High-Speed 12-bit Pipeline ADC in 0.18- μm Digital CMOS

Terje Nortvedt Andersen, Bjørnar Hernes, Member, IEEE, Atle Briskemyr, Frode Teilsto, Johnny Bjørnsen, Member, IEEE, Thomas E. Bonnerud, and Øystein Moldvør



Next Tuesday (10/3-08):

Rest of chapter 13.

- Chapter 14 Oversampling Converters

 


Figure 1. ADC architectures, applications, resolution, and sampling rates.


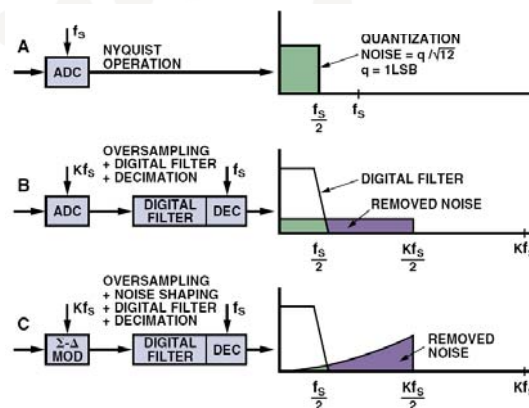


Figure 6. Noise-spectrum effects of the fundamental concepts used in Σ - Δ : oversampling, digital filtering, noise shaping, and decimation.

 

Analog Layout - mismatch



- "...The ratio between two similar components on the same integrated circuit can be controlled to better than $\pm 1\%$, and in many cases, to better than $\pm 0.1\%$. Devices specifically constructed to obtain a known, constant ratio are called **matched devices**."
- "Matching – the Achilles Heel of Analog" (Chris Diorio)

22. mai 2010

47

Some companies located in Norway, doing (or that have done) full custom data converter designs:

- Analog Concepts (Trondheim)
- Arctic Silicon Devices (Trondheim)
- Atmel Norway (Trondheim)
- Energy Micro (Oslo)
- GE Vingmed Ultrasound (Horten)
- Nordic Semiconductors (Trondheim, Oslo)
- Novelda (Oslo)
- Micrel (Oslo)
- Sintef (Trondheim, Oslo)
- Texas Instruments (Oslo)




22. mai 2010

48

Metastability in FFs (<http://www.asic-world.com/tidbits/metastability.html>) To avoid M. in comparators: Make gain high, increase current levels.

What is metastability?

Whenever there are setup and hold time violations in any flip-flop, it enters a state where its output is unpredictable: this state is known as metastable state (quasi stable state). At the end of metastable state, the flip-flop settles down to either '1' or '0'. This whole process is known as metastability. In the figure below T_{su} is the setup time and T_h is the hold time. Whenever the input signal D does not meet the T_{su} and T_h of the given D flip-flop, metastability occurs.

 

When a flip-flop is in metastable state, its output oscillate between '0' and '1' as shown in the figure below (here the flip-flop output settles down to '0'). How long it takes to settle down, depends on the technology of the flip-flop.

The approximate equation which describes the output voltage, $V_Q(t)$ is given by:

$$V_Q(t) = \Delta V_{IN} A e^{-t/\tau} \quad \text{Eq. 1}$$

where ΔV_{IN} = the differential input voltage at the time of latching, A = the gain of the preamp at the time of latching, τ = regeneration time constant of the latch, and t = the time that has elapsed after the comparator output is latched (see References 2 and 3).

For small differential input voltages, the output takes longer to reach a valid logic level. If the output data is read when it lies between the "valid logic 1" and the "valid logic 0" region, the data can be in error. If the differential input voltage is exactly zero, and the comparator is perfectly balanced at the time of latching, the time required to reach a valid logic level can be quite long (theoretically infinite). However, comparator hysteresis and input noise makes this condition highly unlikely. The effects of invalid logic levels out of the comparator are different depending upon how the comparator is used in the actual ADC.

From a design standpoint, comparator metastability can be minimized by making the gain (A) high, minimizing the regeneration time constant (τ) by increasing the gain-bandwidth of the latch, and allowing sufficient time (t), for the output of the comparator to settle to a valid logic level. It is not the purpose of this discussion to analyze the complex tradeoffs between speed,

22. mai 2010

49



ifj

Interpolating ADCs, Folding ADCs and Oversampling Converters

Tuesday 16th of March, 2009, 9:15 – 11:00

Snorre Aunet, sa@ifj.uio.no
Nanoelectronics Group, Dept. of Informatics
Office 3432

 UNIVERSITETET
I OSLO

Last time – and today, **Tuesday 16th** of March:


Last time:

- 13.1 Integrating Converters
- 13.2 Successive-Approx. Converters
- 13.3 Algorithmic (or cyclic) A/D Converters
- 13.4 Flash (or parallel) converters
- 13.5 Two-Step A/D converters
- 13.8 Pipelined A/D Converters
- 13.9 Time-Interleaved A/D Converters





Today – from the following chapters:

 - 13.6 Interpolating A/D Converters
- 13.7 Folding A/D Converters
- 14.1 Oversampled converters



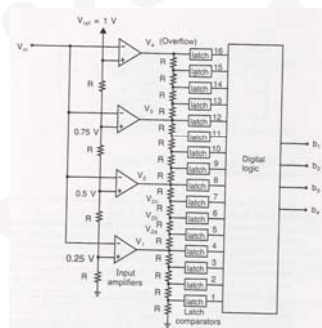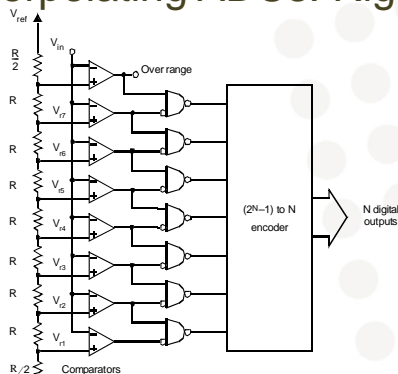Interpolating ADCs. Rightmost interpol.=4 (1/4)



- Reduced complexity compared to Flash ADCs → reduced input capacitance and slightly reduced power.
- In the [mathematical](#) subfield of [numerical analysis](#), **interpolation** is a method of constructing new data points within the range of a [discrete set](#) of known data points.

Interpolating ADCs (2/4)


 
 


Fig. 13.24 Possible transfer characteristics of an interpolating ADC.

- Uses input amplifiers behaving as **linear amplifiers near their threshold voltages**, allowed to saturate for moderately large input signals
- Thus **"noncritical" latches** need only determine the sign of the amplifier outputs

Interpolating ADCs (3/4)

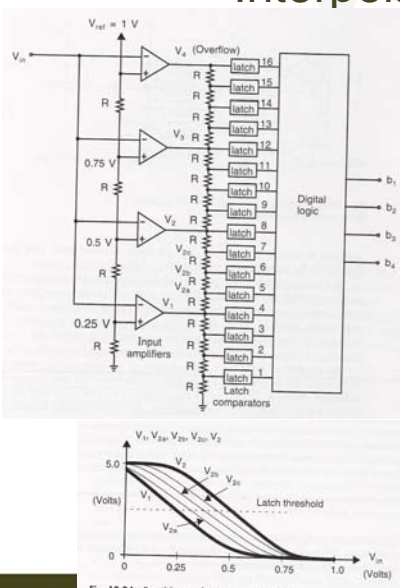

- Amplifier outputs V_1 and V_2 as well as their interpolated values are shown lowermost (fig. 13.24)
- The reference points created from interpolated values (for example V_{2a}, V_{2b}, V_{2c}) have latches potentially triggering in order, for increasing (or decreasing) input.
- For good linearity the interpolated signals need only cross the latch threshold at the correct points



Interpolating ADCs (4/4)

 


Fig. 13.24 Possible transfer characteristics of an interpolating ADC.


 


Fig. 13.25 Adding series resistors to equalize delay times to the latch comparators.

 - To achieve good linearity V_1 and V_2 need to be linear between their own thresholds. In figure 13.24 this linear region corresponds to $0.25 < V_{in} < 0.5$ (horizontally)
- For fast operation the delays to each of the latches must be made to equal each other as much as possible. In fig. 13.25 this is done using resistors.



Example, based on Fig. 13.23 (1/2)



• $V_{in} = 0.4 \text{ V}$, gain of -10, logic levels of 0 and 5 volts. \rightarrow

- $V_4 = 5 \text{ V}$
- $V_3 = 5 \text{ V}$
- $V_2 = 3.5 \text{ V}$
- $V_1 = 1.0 \text{ V}$


 


Fig. 13.24 Possible transfer characteristics for a 4-bit interpolating ADC.

 

Example – interpolating ADC (2/2)



LATCH THRESHOLD = $\frac{5 \text{ volt}}{2} = 2.5 \text{ V}$


 



Fig. 13.24 Possible transfer characteristics for a 4-bit interpolating ADC.

16. mars 2010


8

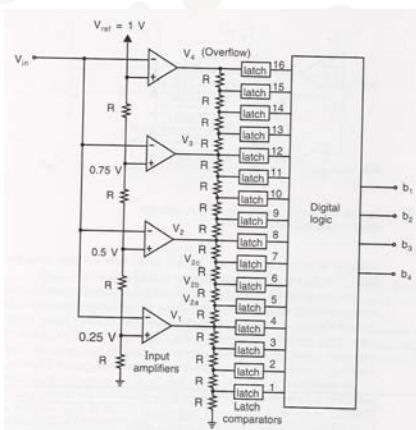


Folding A/D Converters (13.7)

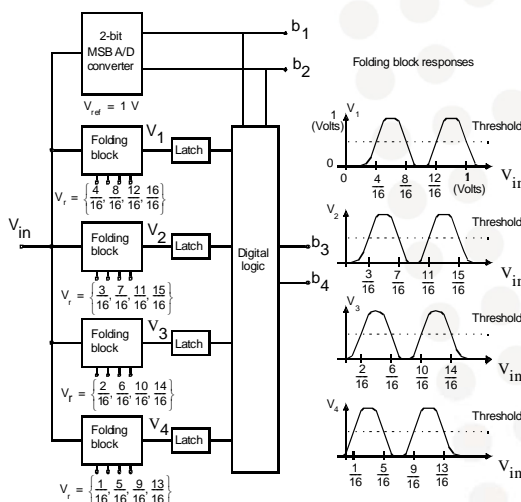

- The number of latches is reduced compared to the interpolating ADC, and even more from FLASH
- The figure shows a 4 bit converter with folding rate of 4
- A group of LSBs are found separately from a group of MSBs.
- The MSB converter determines whether the input signal, V_{in} , is in one of four voltage regions (between 0 and $\frac{1}{4}$, $\frac{1}{4}$ and $\frac{1}{2}$, $\frac{1}{2}$ and $\frac{3}{4}$, or $\frac{3}{4}$ and 1)
- V_1 to V_4 produce a thermometer code for each of the four MSB regions

 

 
Similar to folding block responses on previous slide..




- Bipolar folder outputs
- Ex: Input 1.05:
- $F_1 > \text{threshold} = 0 \rightarrow "1"$
- $F_2 > \text{threshold} = 0 \rightarrow "1"$
- $F_3 > \text{threshold} = 0 \rightarrow "1"$
- $F_4 < \text{threshold} = 0 \rightarrow "0"$
- Thermometer code produced for each of the four MSB regions (between 0 and $\frac{1}{4}$, $\frac{1}{4}$ and $\frac{1}{2}$, $\frac{1}{2}$ and $\frac{3}{4}$, or $\frac{3}{4}$ and 1 for previous slide)
- (in certain respects related to interpolation in Fig 13.24)

16. mars 2010

10

 

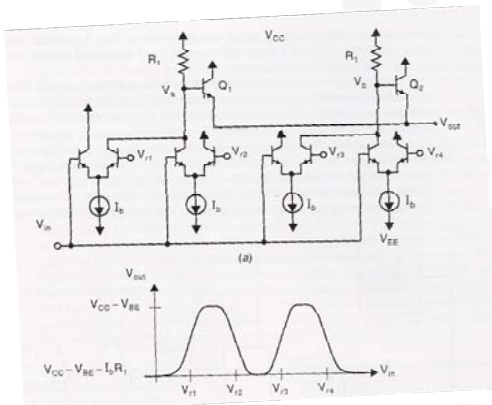
Folding block with a folding rate of four




- Input-output response for the cross-coupled differential pair is shown lowermost
- Vout is low if, and only if, both V_a and V_b are low, otherwise high
- The output from a folding block is at a much higher frequency than the input signal, limiting the practical folding rate.
- Differential solutions in practice



Folding and Interpolating ADC

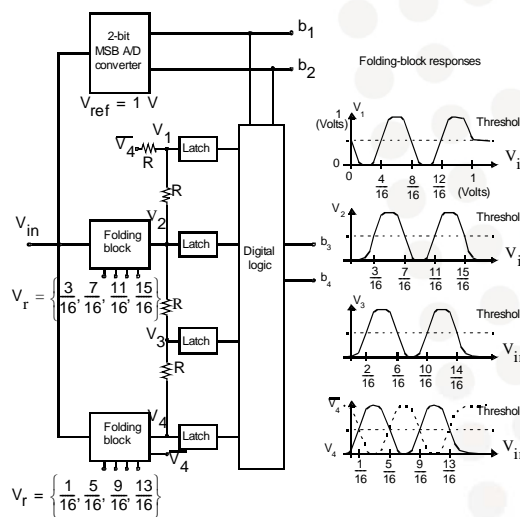

 - By introducing interpolation, the number of folding blocks is reduced
- Input capacitance is reduced (if both folding and interpolating is combined)
- Folding-rate of four and interpolate-by-two
- (Literature references on page 523)



Interpolating and folding and interpolating ADCs

Resolution	Sampling rate	ENOB	Power dissip.	Supply voltage	architecture	reference
8 bit	100 MHz	6.5 bit@5V, 7.1 bit@8V	1.2W@5V	5 or 8 V	interpolating	Steyaert , Roovers, Craninckx, CICC 1993
5 bit	5 GHz	4 bit at 5GHz	113 mW@1V	1 V	interpolating	Wang, Liu, VLSI-DAT '2007
6 bit	200 MHz	5.35 bit	35 mW@3.3V	3.3V	folding and interpolating	Yin, Wang, Liu, ICSICT, 2008
6 bit	200 MHz	5.5 bit	78.8 mW@2.5V	2.5V	folding and interpolating	Silva, Fernandes, ISCAS, 2003


16. mars 2010

13

UNIVERSITETET
I OSLO

Oversampling converters (chapter 14 in "J & M")


- For **high resolution, low-to-medium-speed** applications like for example digital audio
- **Relaxes requirements placed on analog** circuitry, including matching tolerances and amplifier gains
- **Simplify requirements placed on the analog** anti-aliasing **filters** for A/D converters and smoothing filters for D/A converters.
- Sample-and-Hold is usually not required on the input
- **Extra bits of resolution can be extracted from converters that samples much faster than the Nyquist-rate.** Extra resolution can be obtained with lower oversampling rates by exploiting **noise shaping**

 

UNIVERSITETET



Resolution and clock cycles per sample

 

Dependence of achievable resolution and required clock cycles per sample for various ADC systems.


IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 27, NO. 10, OCTOBER 1992

A Gigasample/Second 5-b ADC with On-Chip Track and Hold Based on an Industrial 1- μ m GaAs MESFET E/D Process

Richard Hagelauer, Member, IEEE, Frank Oehler, Günter Rohmer, Josef Sauerer, and Dieter Seitzler, Senior Member, IEEE



Nyquist Sampling and Oversampling

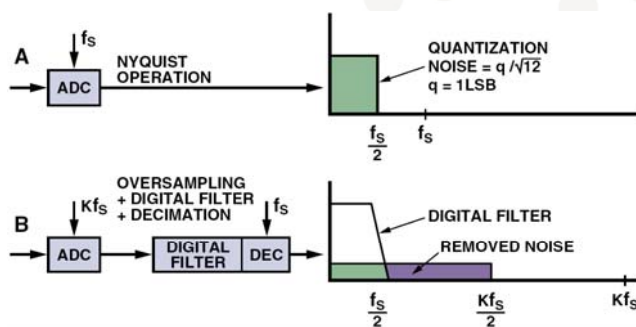

- Figure from [Kest05]
- Straight oversampling gives an SNR improvement of 3 dB / octave
- $f_s > 2f_0$ ($2f_0 =$ Nyquist Rate)
- $OSR = f_s/2f_0$
- $SNR_{max} = 6.02N + 1.76 + 10\log(OSR)$



Oversampled converters; High resolution and relatively low speed

 


Figure 1. ADC architectures, applications, resolution, and sampling rates.

 


Fig. 2. ADC sample rate vs. ENOB from 1987 to 2005.

Which ADC Architecture Is Right for Your Application?

By Walt Kester [walt.kester@analog.com]


IEEE 2005 CUSTOM INTEGRATED CIRCUITS CONFERENCE
Scaling of Analog-to-Digital Converters into Ultra-Deep-Submicron CMOS

Y. Chiu¹, B. Nikolic², and P. R. Gray¹
¹ Electrical and Computer Engineering, University of Illinois at Urbana-Champaign
² Electrical Engineering and Computer Sciences, University of California at Berkeley



QUANTIZATION NOISE (p. 532-533 in "J & M")

 The quantization noise is the difference between the input and output values.




This model is exact under the assumption that the quantization error is strongly related to the input signal ("J & M" p. 532). The model becomes approximate when assumptions are made about the statistical properties of $e(n)$, such as $e(n)$ being an independent white-noise signal. This model leads to a simpler understanding of $\Sigma\Delta$ and with some exceptions is usually reasonably accurate.


- If $x(n)$ is very active, $e(n)$ can be approximated as an independent random number uniformly distributed between $\pm \frac{\Delta}{2}$, where Δ equals the difference between two adjacent

quantization levels. Thus, the quantization noise power equals $\frac{\Delta^2}{12}$ (Sec. 11.3) and is independent of the sampling frequency, f_s .

 The spectral density of $e(n)$, $S_e(f)$ is white (constant over freq.) and all its power within $\pm f_s/2$, as shown in the figure:



 The spectral density height is calculated by noting that the total noise power is $\Delta^2/12$ and with a two-sided def. of power equals the area under $S_e(f)$ within $\pm f_s/2$.



14.1 Output and quantization errors for two quantizers

$x(n) = \{0.01, 0.31, -0.11, 0.80, 0.52, -0.70\}$

Quantizer 1:

$y_1(n) = \{0.0, 0.5, 0, 1.0, 0.5, -0.5\}$

Quantizer 2:

$y_2(n) = \{1.0, 1.0, -1.0, 1.0, 1.0, -1.0\}$

$e_1(n) = \{-0.01, 0.19, -0.11, -0.30, -0.02, 0.20\}$

$e_2(n) = \{0.99, 0.69, -0.89, 0.20, 0.48, -0.30\}$

Expected power and power density spectra?

$e(n)$ is approximated as an independent random number uniformly distributed between $\pm \frac{\Delta}{2}$, where Δ equals the difference between two adjacent quantization levels.

$P_e = \frac{\Delta^2}{12}$

quant 1: $\frac{\Delta^2}{12} = \frac{(0.5)^2}{12} = 0.0208\bar{3} [w]$

quant 2: $\frac{\Delta^2}{12} = \frac{1^2}{12} = 0.08\bar{3} [w]$

$S_e(f)$

Quantizer I:

Quantizer II:

OVERSAMPLING IS BASED ON THE ASSUMPTION THAT AN ADC'S TOTAL QUANTIZATION NOISE POWER (VARIANCE) IS THE SQUARED VALUE OF THE CONVERTER'S LEAST SIGNIFICANT BIT (LSB) VOLTAGE DIVIDED BY 12 (1/12ths' rule)

$S_{e1}^2(f) = \frac{0.0208\bar{3}}{2\pi} \left[\frac{w}{rad/sample} \right] = 0.0033 \frac{w}{rad/sample}$

$S_{e2}^2(f) = \frac{0.08\bar{3}}{2\pi} \left[\frac{w}{rad/sample} \right] = 0.013 \frac{w}{rad/sample}$

OVERSAMPLING ADVANTAGE p. 535

Signal of interest is bandlimited to f_0 .

If the input is sinusoidal, its maximum peak value without clipping is $2^N (\Delta/2)$. For this wave the signal power P_s has a power equal to $P_s = \left(\frac{\Delta 2^N}{2} \frac{1}{\sqrt{2}} \right)^2 = \frac{\Delta^2 2^{2N}}{8}$.

The power of the input signal within $y_1(n)$ remains the same as before since we assumed the signal's frequency content is below f_0 .

HOWEVER, THE QUANTIZATION NOISE POWER IS REDUCED TO

$P_e = \int_{-f_s/2}^{f_s/2} S_e^2(f) |H(f)|^2 df = \int_{-f_0}^{f_0} k_n^2 df$

$= \frac{2f_0}{f_s} \cdot \frac{\Delta^2}{12} = \frac{\Delta^2}{12} \left[\frac{1}{OSR} \right]$

THEREFORE, DOUBLING OSR DECREASES THE QUANTIZATION NOISE POWER BY ONE-HALF, OR EQUIVALENTLY, 3 dB (or equiv. 0.5 bits)

$SNR_{max} = 10 \log \left(\frac{P_s}{P_e} \right) = 10 \log \left(\frac{3}{2} 2^{2N} \right) + 10 \log (OSR)$

$= 6.02N + 1.76 + 10 \log (OSR) [dB]$

due to N-bit quantizer due to over-sampling

After quantization, $y_1(n)$ is filtered by $H(f)$ to create $y_2(n)$ that eliminates quantization noise (together with any other signals) greater than f_0 .

$$SNR_{max} = 10 \log \left(\frac{P_s}{P_e} \right) \quad \wedge \quad P_s = \frac{\Delta^2 \cdot 2^{2N}}{8} \quad \wedge \quad P_e = \frac{\Delta^2}{12} \cdot \frac{1}{OSR}$$

$$SNR_{max} = 10 \log \left[\frac{\frac{\Delta^2 \cdot 2^{2N}}{8}}{\frac{\Delta^2}{12} \cdot \frac{1}{OSR}} \right] = 10 \log \left[\frac{\Delta^2 \cdot 2^{2N} \cdot 3 \cdot OSR}{8 \cdot \Delta^2} \right] = 10 \log \left(\frac{3}{2} \cdot 2^{2N} \cdot OSR \right)$$

$$= 10 \log \frac{3}{2} \cdot 2^{2N} + 10 \log OSR$$

$$= 10 \log \frac{3}{2} + 10 \log 2^{2N} + 10 \log OSR$$

$$= 10 \log 2^{2N} + 1.76 + 10 \log OSR$$


$$= 10 \cdot 2N \cdot \log 2 + 1.76 + 10 \log OSR$$

$$= 10 \cdot 2 \cdot N \cdot 0.301 + 1.76 + 10 \log OSR$$


$$= 6.02 N + 1.76 + 10 \log (OSR) \quad [dB]$$

(14.13) pp. 54
i. J. & M.

16. mars 2010 21

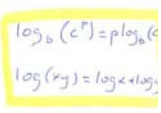

Oversampling (without noise shaping)

 


• Total støy er gitt av:

$$P_e = \int_{-f_0}^{f_0} S_e^2(f) df = \frac{\Delta^2}{12} \cdot \frac{1}{OSR}$$

- Doubling of the sampling frequency increases the dynamic range by 3 dB = 0.5 bit.
- To get a high SNR a very high fs is needed → high power consumption.
- Oversampling usually combined with noise shaping and higher order modulators, for higher increase in dynamic range per octave ("OSR")

SNRmax = 6.02N+1.76+10log(OSR) [dB]
 SNR improvement 0.5 bits / octave

 

Ex. 14.3

EXAMPLE 14.3


Given that a 1-bit A/D converter has a 6-dB SNR, what sample rate is required using oversampling (no noise shaping) to obtain a 96-dB SNR (i.e., 16 bits) if $f_b = 25$ kHz? (Note that the input into the A/D converter has to be very active for the white-noise quantization model to be valid—a difficult arrangement when using a 1-bit quantizer with oversampling without noise shaping).

Solution

Oversampling (without noise shaping) gives 3 dB/octave where 1 octave implies doubling the sampling rate. We require 90 dB divided by 3 dB/octave, or 30 octaves. Thus, the required sampling rate, f_s , is

$$f_s = 2^{30} \times 2f_b \approx 54,000 \text{ GHz!}$$

 This example shows why noise shaping is needed to improve the SNR faster than 3 dB/octave, since 54,000 GHz is highly impractical.



Advantages of 1-bit A/D converters (p.537 in "J&M")

- Oversampling improves signal-to-noise ratio, but not linearity
- Ex.: 12-bit converter with oversampling needs component accuracy to match better than 16-bit accuracy if a 16-bit linear converter is desired
- Advantage of 1-bit D/A is that it is **inherently linear**. Two points define a straight line, so no laser trimming or calibration is required
- Many audio converters presently use 1-bit converters for realizing 16- to 18-bit linear converters (with noise shaping).



UNIVERSITETET
I OSLO

Problems with some 1-bit converters ((?))

Why 1-Bit Sigma-Delta Conversion is Unsuitable for High-Quality Applications

by

Stanley P. Lipshitz and John Vanderkooy
Audio Research Group, University of Waterloo
Waterloo, Ontario N2L 3G1, Canada

ABSTRACT

Single-stage, 1-bit sigma-delta converters are in principle imperfectible. We prove this fact. The reason, simply stated, is that, when properly dithered, they are in constant overload. Prevention of overload allows only partial dithering to be performed. The consequence is that distortion, limit cycles, instability, and noise modulation can never be totally avoided. We demonstrate these effects, and using coherent averaging techniques, are able to display the consequent profusion of nonlinear artefacts which are usually hidden in the noise floor. Recording, editing, storage, or conversion systems using single-stage, 1-bit sigma-delta modulators, are thus inimical to audio of the highest quality. In contrast, multi-bit sigma-delta converters, which output linear PCM code, are in principle infinitely perfectible. (Here, multi-bit refers to at least two bits in the converter.) They can be properly dithered so as to guarantee the absence of all distortion, limit cycles, and noise modulation. The audio industry is misguided if it adopts 1-bit sigma-delta conversion as the basis for any high-quality processing, archiving, or distribution format to replace multi-bit, linear PCM.



Audio Engineering Society
Convention Paper 5395

Presented at the 110th Convention
2001 May 12-15 Amsterdam, The Netherlands



UNIVERSITETET
I OSLO

Oversampling with noise shaping (14.2)

- Oversampling combined with noise shaping can give much more dramatic improvement in dynamic range each time the sampling frequency is doubled.
- The sigma delta modulator converts the analog signal into a noise-shaped low-resolution digital signal.
- The decimator converts to a high resolution digital signal


 



Fig. 14.5 Block diagram of an oversampling A/D converter.

Multi-order sigma delta noise shapers (Sangil

Park, Motorola)

 

Note: Higher order Noise Shaper has less baseband noise

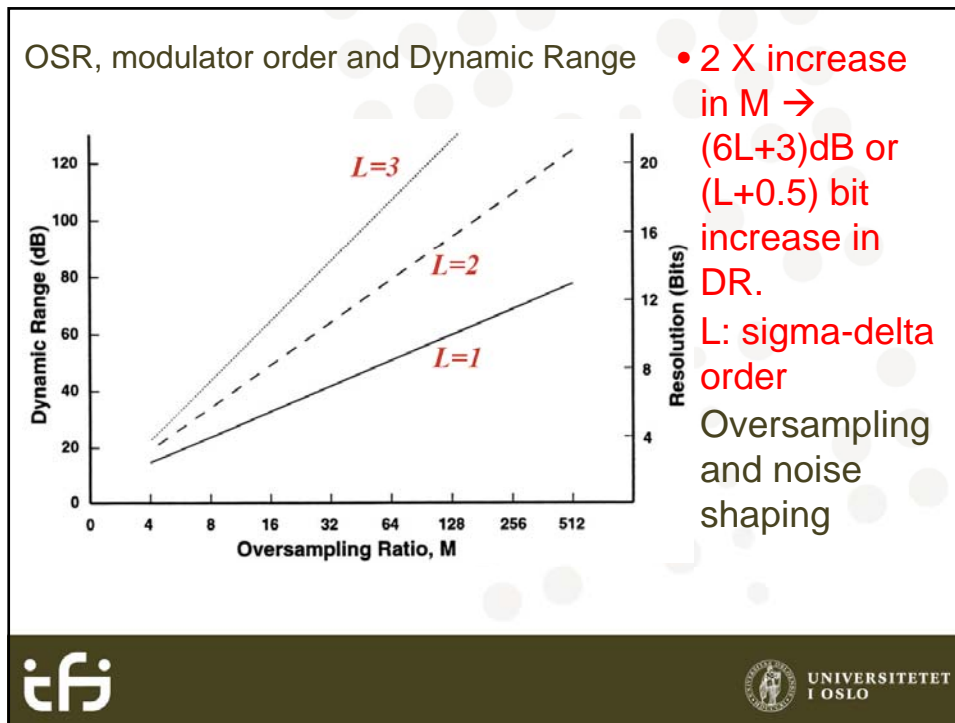

Ex. 14.5

- Given that a 1-bit A/D converter has a 6 dB SNR, which sample rate is required to obtain a 96-dB SNR (or 16 bits) if $f_0 = 25$ kHz for straight oversampling as well as first- and second-order noise shaping?
- **Oversampling with no noise shaping:** From ex. 14.3 we know that straight oversampling requires a sampling rate of 54 THz.
- $(6.02N + 1.76 + 10 \log(\text{OSR})) = 96$
 $\Leftrightarrow 6 + 10 \log \text{OSR} = 96$
 $\Leftrightarrow 10 \log \text{OSR} = 90$

Ex. 14.5

$$\text{SNR}_{\text{max}} = 6.02N + 1.76 - 5.17 + 30 \log(\text{OSR}) \quad (14.25)$$

We see here that doubling the OSR gives an SNR improvement for a first-order modulator of 9 dB or, equivalently, a gain of 1.5 bits/octave. This result should be compared to the 0.5 bits/octave when oversampling with no noise shaping.

 


Fig. 14.7 A first-order noise-shaped interpolative modulator.

- Oversampling with 1st order noise shaping:

- $6 - 5.17 + 30 \log(\text{OSR}) = 96$ $\text{OSR} = f_s / 2f_0$

- $30 \log(\text{OSR}) = 96 - 6 + 5.17 = 95.17$

A doubling of the OSR gives an SNR improvement of 9 dB / octave for a 1st order modulator;

$$95.17 / 9 = 10.57 \quad 2^{10.56} \times 2 \times 25 \text{ kHz} = 75.48 \text{ MHz}$$

OR: $\log(\text{OSR}) = 95.17 / 30 = 3.17 \rightarrow \text{OSR} = 1509.6$

$$1509.6 \times (2 \times 25 \text{ kHz}) = 75.48 \text{ MHz}$$

 


Ex. 14.5

$$\text{SNR}_{\text{max}} = 6.02N + 1.76 - 12.9 + 50 \log(\text{OSR}) \quad (14.3)$$

We see here that doubling the OSR improves the SNR for a second-order modulator by 15 dB or, equivalently, a gain of 2.5 bits/octave.

The realization of the second-order modulator using switched-capacitor techniques is straightforward and is left as an exercise for the interested reader.

Fig. 14.10 Second-order $\Delta\Sigma$ modulator.

- Oversampling with 2nd order noise shaping:

- $6 - 12.9 + 50 \log(\text{OSR}) = 96$ $\text{OSR} = f_s / 2f_0$


- $50 \log(\text{OSR}) = 96 - 6 + 12.9 = 102.9$

A doubling of the OSR gives an SNR improvement of 15 dB / octave for a 2nd order modulator;

$$102.9 / 15 = 6.86 \quad 2^{6.86} \times 2 \times 25 \text{ kHz} = 5.81 \text{ MHz}$$



Ex. 14.5 "point":

 

- 2 X increase in M → (6L+3)dB or (L+0.5) bit increase in DR.
- L: sigma-delta order
- 6 db Quantizer, for 96 dB SNR:
- Plain oversampling: $f_s=54$ GHz
- 1st order : $f_s=75.48$ MHz
- 2nd order: $f_s= 5.81$ MHz
- Exam problem (INF4420) below

3 a) (Weight 10 %)

16. mars 2010

A sampled signal is bandlimited to $f_b = 22$ kHz. What is the sampling frequency, f_s , for an oversampling ratio ("OSR") of 128?

A 1-bit analog-to-digital converter ("ADC") has an inherent 6-dB SNR. Which maximum SNR is acquired by combining it with strict oversampling and an OSR of 128, if no noise shaping is used? What is the maximum SNR in the similar case exploiting 2nd order noise shaping?

If a 1-bit ADC using 3rd order noise shaping has a maximum SNR of 125 dB for an OSR of 128, what is the expected maximum SNR if the OSR is reduced to 32?



Sigma Delta converters, ISSCC 2008

- ISSCC- Foremost global forum
- "CT": continous time

ΣΔ DATA CONVERTERS		27.5 A 28mW Spectrum-Sensing Reconfigurable 28MHz 72dB-SNR 70dB-SNDR DT ΣΔ ADC for 802.11a/WiMax Receivers	
Chair: Zhongyuan Chang, IDT Technology, Shanghai, China			10:45 AM
Associate Chair: Yannis Manoli, University of Freiburg, Freiburg, Germany		P. Maly ^{1,2} , H. Lakdawala ¹ , K. Koravajala ³ , K. Soumyanath ¹	
27.1 A 108dB-SNR 1.1mW Oversampling DAC with a Three-Level DEM Technique	8:30 AM	¹ Intel, Hillsboro, OR	
K. Nguyen, A. Bandyopadhyay, S. Adams, K. Svedand, P. Bajkowski		² Cornell University, Ithaca, NY	
Analog Devices, Wilmington, MA		³ Georgia Institute of Technology, Atlanta, GA	
A multi-bit audio DAC in a 0.18µm CMOS process uses a three-level DEM scheme and an ISI-free output stage to achieve 108dB SNR while consuming a total of 1.1mW per channel from a 1.8V supply.		A reconfigurable MASH 2-2 ΣΔ ADC, fabricated in 90nm CMOS, has an OSR of 19.5 and uses a 1.2V supply. It achieves SNRs of 72, 62, 60, and 54dB with a 20MHz BW while consuming 20, 20, 15, and 12mW, respectively. The configuration and, therefore, power are determined by signal and blocker power. SNRs of 73, 77, and 79dB are achieved for BWs of 10, 5, 2.5MHz, respectively.	
27.2 A 0.7V 30µW 85dB-DR Audio ΣΔ Modulator Using a Class-C Inverter	9:00 AM	27.5 A 100mW 10MHz-BW CT ΣΔ Modulator with 87dB DR and -91dBc IMD	11:15 AM
Y. Chae, I. Lee, G. Han		W. Yang, W. Schofield, H. Shibus, S. Koravajala, A. Shaikh, N. Abuskhroun, D. Ribner	
Yonsei University, Seoul, Korea		Analog Devices, Wilmington, MA	
An audio ΣΔ modulator is realized in a standard 0.18µm CMOS process, exploiting the possibility of substituting a class-C inverter for an OTA. The measurement results from the fabricated chip demonstrate 81dB SNDR, 84dB SNR, and 85dB DR for a 20kHz signal bandwidth. The chip consumes 36µW from a 0.7V supply.		A 3 rd -order CT ΣΔ modulator with a hybrid feedback-feedforward topology and 9-bit quantization is implemented in a 0.18µm CMOS process. When clocked at 640MHz, the modulator achieves 87dB DR, 92dB peak SNDR, and -91dBc IMD over a 10MHz BW. The modulator occupies 0.7mm ² and consumes 100mW from a 1.8V supply.	
27.3 An Inverter-Based Hybrid ΣΔ Modulator	9:30 AM	27.7 A 65nm CMOS CT ΣΔ Modulator with 81dB DR and 8MHz BW Auto-Tuned by Pulse Injection	11:45 AM
R. Weichow, R. Ruten, L. Breems		Y.-S. Zhu ¹ , S.-S. Song ¹ , K. Razvanic ²	
IXP Semiconductors, Eindhoven, Netherlands		¹ University of California, San Diego, CA	
A hybrid ΣΔ modulator with 1 st -order analog filter, 5th quantizer, 2 nd -order digital filter, 1b quantizer, and 1b DAC is presented. The active circuitry is implemented solely with inverter circuits and standard digital cells. The 65nm CMOS modulator achieves a peak SNR of 77dB in 200kHz. Power consumption is 950µW at 1.2V and the area is 0.03mm ² .	Break 10:00 AM	² Cosensart Systems, Palm Bay, FL	
27.4 A Noise-Coupled Time-Interleaved ΣΔ ADC with 4.2MHz BW, -95dB THD, and 79dB SNDR	10:15 AM	Active filters for CT ΣΔ modulators are calibrated by injecting a binary pulse dither and nulling it with an LMS algorithm. A 3 rd -order 4b prototype in 65nm CMOS occupies 0.5mm ² and consumes 50mW at 1.2V. At 25MS/s (OSR=16), the DR is 81dB with a 2.4µV full-scale range. SNR and SNDR of -148FS and 76 and 70dB, respectively.	
K. Lee ¹ , J. Choi ¹ , M. Anjo ² , K. Hamashita ² , K. Takasaki ² , S. Takeuchi ² , G. Temes ¹		27.8 A CT ΣΔ ADC for Voice Coding with 92dB DR in 45nm CMOS	12:00 PM
¹ Oregon State University, Corvallis, OR		L. Dornik, F. Kutzak, A. Sattari, C. Kropf, T. Ptaschitz, T. Hartig	
² Acacia Kasei, Atsugi, Japan		Infineon, Villach, Austria	
A two-channel time-interleaved noise-coupled ΣΔ ADC is realized in 0.18µm CMOS technology. Time interleaving doubles the effective clock rate while noise coupling raises the effective order of the noise-shaping loops, implements dithering, and also prevents tone generation in all loops. Using a 1.5V supply, the device achieved SFDR=100dB, THD=-95dB, and an SNDR of 79dB in a 4.2MHz signal band.		A 2 nd -order CT multi-bit (4b) ΣΔ ADC for voice coding is implemented in a 45nm CMOS process. The input operational amplifier is chopped to eliminate flicker noise and offset. The quantizer, a power-efficient 3-comparator tracking ADC with a capacitive voltage reference DAC, is suitable for low-voltage designs and high clock rates. Over a bandwidth of 20kHz, the DR is 86dB. The ADC consumes 1.2mW from a 1.1V supply when clocked at 12MHz.	



ISSCC VISION STATEMENT
The International Solid-State Circuits Conference is the foremost global forum for presentation of advances in solid-state circuits and systems-on-chip. The Conference offers a unique opportunity for engineers working at the cutting edge of IC design and application to maintain technical currency and to network with leading experts.



UNIVERSITETET I OSLO

2nd order sigma delta modulator

 


Fig. 1. Block diagram of second-order $\Sigma\Delta$ modulator with decimator.

 


Fig. 10. Second-order $\Sigma\Delta$ modulator implementation.

 


Fig. 13. Measured SNR for a sampling frequency of 4 MHz and a signal frequency of 1.02 kHz.


 


Fig. 14. Maximum operating frequency.

 

15. Dynamic range as a function of the oversampling ratio for a sampling frequency of 4 MHz.

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 23, NO. 6, DECEMBER 1988

The Design of Sigma-Delta Modulation Analog-to-Digital Converters

BERNHARD E. BOSER, STUDENT MEMBER, IEEE, AND BRUCE A. WOOLLEY, FELLOW, IEEE

Additional litterature

- Stanley P. Lipshitz, John Vanderkooy: *Why 1-bit Sigma Delta Conversion is Unsuitable for High Quality Applications*, Journal of the audio engineering society, 2001.
- Y. Chiu, B. Nolicic, P. R. Gray: *Scaling of Analog-to-Digital Converters into Ultra-Deep-Submicron CMOS*, Proceedings of Custom Integrated Circuits Conference, 2005.
- Richard Hagelauer, Frank Oehler, Gunther Rohmer, Josef Sauerer, Dieter Seitzer: *A GigaSample/Second 5-b ADC with On-Chip Track-And-Hold Based on an Industrial 1 um GaAs MESFET E/D Process*, IEEE Journal of Solid-State Circuits ("JSSC"), October 1992.
- Walt Kester: *Which ADC Architecture is right for your application?*, Analog Dialogue, Analog Devices, 2005.
- Richard Lyons, Randy Yates: *"Reducing ADC Quantization Noise"*, MicroWaves & RF, 2005
- Sangil Park: *"Principles of sigma-delta modulators for analog to digital converters"*, Motorola
- B. E. Boser, B. A. Wooley: *"The design of sigma delta modulation analog to digital converters*, IEEE JSSC, 1988.
- John P. Bentley: *Principles of Measurement Systems*, 2nd ed., Bentley, 1989.
- Lecture Notes, University of California, Berkeley,
EE247 Analog Digital Interface Integrated Circuits, Fall 07; <http://inst.eecs.berkeley.edu/~ee247/fa07/>

Next Time, 23/3-10:

- More from Chapter 14; Oversampling Converters (14.2, 14.3, 14.4, 14.5, 14.7)
- Beginning of chapter 16; Phase-Locked Loops (16.1)

Guide to writing a thesis / report: The Design and implementation of a Nifty Gadget (page 1 and 2)

Guide to Writing a Thesis

Department of Applied Electronics
Last updated 1997-03-12

Original manuscript written by Svein Mattiazon

The Design and Implementation of a Nifty Gadget

Tekst- Lir Book

April 12, 1992

Abstract

What is all this about?
Why should I read this thesis?
Is it any good?
What's new?

Preface

Have you done anything that doesn't have to do with your research?
Have you published parts of this work before?

Acknowledgement

Who is your advisor?
Did anyone help you?
Who funded this work?
What's the name of your favorite pet?

1 Introduction

What is the use of a Nifty Gadget?
What is the problem?
How can it be solved?
What are the previous approaches?
What is your approach?
Why do it this way?
What are your results?
Why is this better?
Is this a new approach?
Why haven't anyone done it before?

1

<http://www.tde-bk.uio.no/education/wafby.html>

04.07.2006

or
Why do you reiterate previous work?
What is your contribution to the field of Nifty Gadgets?

2 Theoretical background

What is the required background knowledge?
Where can I find it?

2.1 Various approaches to Nifty Gadgets

What is the relevant prior work?
Where can I find it?
Why should it be done differently?
Has anyone attempted your approach previously?
Where is that work reported?

2.2 Nifty Gadgets my way

What is the outline of your way?
Have you published it before?

3 My implementation of a Nifty Gadget

Can you describe your implementation in detail?
Why did you use this technology?
How does the theory relate to your implementation?
What are your underlying assumptions?
What did you neglect and what simplifications have you made?
What tools and methods did you use?
Why use these tools and methods?

4 Nifty Gadget results

Did you actually build it?
How- can you test it?
How did you test it?
Why did you test it this way?
Are the results satisfactory?
Why should you (not) test it more?
What comparisons had to be made to interpret the results?
Why did you succeed/fail?

5 Discussion

Are your results satisfactory?
Can they be improved?
Is there a need for improvement?

38

"Nifty Gadget" page 3 and 4

Are other approaches worth trying out?
Will some restriction be lifted?
Will you save the world with your Nifty Gadget?

6 References

What is the background reading list?
Where is the related work?
Where is the prior work?
Where can I find important material?

Appendix A

Can you outline futility calculus or whatever complicated theory or results you are using that will obscure the text?

Appendix B

A thesis should discuss the following topics:

- **Introduction**

Presentation of the problem or phenomenon to be addressed, the situation where the problem or phenomenon occurs, and references to earlier relevant research.

Common errors
Problem is not properly specified or formulated; insufficient references to earlier work.

- **Purpose**

What can be gained by more knowledge about the problem or phenomenon.

Common errors
The purpose is not mentioned, not connected to earlier research, or not in line with what the actual contents of the thesis.

- **Problem/Hypothesis**

Questions that need to be answered to reach the goal and/or hypothesis formulated by means of underlying theories.

Common errors
Missing problem description; deficiencies in the connections between questions; badly formulated hypothesis.

- **Method**

Choice of an adequate method with respect to the purpose and problem/hypothesis.

Common errors

An inappropriate method is used, for example due to lack of knowledge about different methods; erroneous use of chosen method.

- **Result**

Answers to the forwarded questions by means of the achieved results.

Common errors

The results are not properly connected to the problem; blurry presentation; the results are inter-mixed with discussion.

- **Discussion**

Discussion of the accuracy and relevance of the results; comparison with other researchers results.

Common errors

Too far reaching conclusions; guesswork not supported by the data; introduction of a new problem and a discussion around this.

- **Conclusion**

Consequences of the achieved results, for example for new research, theory and applications.

Common errors

The conclusions are too far reaching with respect to the achieved results; the conclusions do not correspond with the purpose.

[Home Page for the Department of Applied Electronics](#)

39



ifj

Oversampling Converters and PLLs

Tuesday 23rd of March, 2010, 9:15 – 11:10

Snorre Aunet, sa@ifi.uio.no
 Nanoelectronics Group, Dept. of Informatics
 Office 3432

 UNIVERSITETET
I OSLO



Last time – and today, Tuesday 16th of March:

Last time:

- 13.6 Interpolating A/D Converters
- 13.7 Folding A/D Converters
- 14.1 Oversampled converters


Today:

  - 14.2 Oversampling with noise shaping
- 14.3 System Architectures
- 14.4 Digital Decimation Filters
- 14.5 Higher-Order Modulators
- (14.6 Bandpass Oversampling Converters)
- 14.7 Practical Considerations
- 14.8 Multi-bit oversampling converters
- 2nd order sigma delta design example
- 16.1 Basic Phase Locked Loop Architecture



the relative phase angles of the input signal and the output of the oscillator
 Fig. 16.3

 
Nyquist Sampling, Oversampling, Noise Shaping



- Figure from [Kest05]
- Straight over-sampling gives an SNR improvement of 3 dB / octave
- $f_s > 2f_0$ ($2f_0 =$ Nyquist Rate)
- $OSR = f_s/2f_0$
- $SNR_{max} = 6.02N + 1.76 + 10\log(OSR)$



OSR, modulator order and Dynamic Range

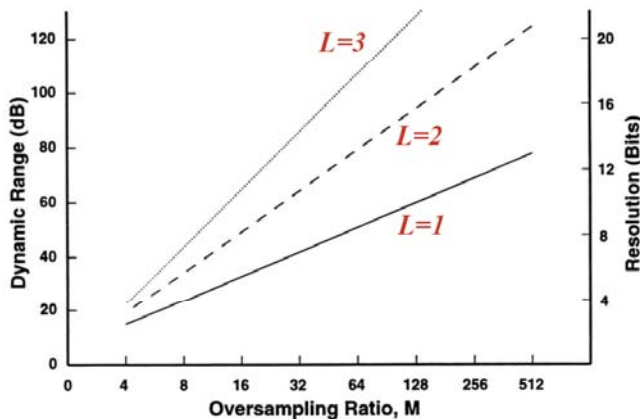

- 2 X increase in $M \rightarrow (6L+3)\text{dB}$ or $(L+0.5)$ bit increase in DR.
- L : sigma-delta order
- Oversampling and noise shaping



14.2 Oversampling with noise shaping


 


Fig. 14.5 Block diagram of an oversampling A/D converter.

- The anti aliasing filter bandlimits the input signals less than $f_s/2$.
- The continuous time signal $x_c(t)$ is sampled by a S/H (not necessary with separate S/H in Switched Capacitor impl.)
- The **Delta Sigma modulator** converts the analog signal to a noise shaped low resolution digital signal
- The **decimator** converts the oversampled low resolution digital signal into a high resolution digital signal at a lower sampling rate usually equal to twice the desired bandwidth of the desired input signal (conceptually a low-pass filter followed by a downsampler).

 


Noise shaped Delta Sigma Modulator





The linear model can be treated as having two independent inputs (which is an approximation).

Signal:

 

Noise:

  

Signal transfer function, $S_{TF}(z)$:

$$S_{TF}(z) \equiv \frac{Y(z)}{U(z)} = \frac{H(z)}{1 + H(z)}$$

Noise transfer function, $N_{TF}(z)$:

$$N_{TF}(z) \equiv \frac{Y(z)}{E(z)} = \frac{1}{1 + H(z)}$$

The output is the combination of the input and noise: $Y(z) = S_{TF}(z)U(z) + N_{TF}(z)E(z)$

TET

CHAP. 16 BLOCK DIAGRAMS AND SIGNAL FLOW GRAPHS 291

General remarks. So long as the generator is operated approximately $f_0 \ll f_c$, and the transfer function between v_1 and v_2 is simply a constant:

$$\frac{V_2(s)}{V_1(s)} = K_{eff} \quad (16.1)$$

Fisher's rule. If the series combination of the resistor field inductor and the reference-controlled resonant inductor is much larger than R_0 , then voltage division is valid and the transfer function relating v_2 to v_1 is

$$\frac{V_2(s)}{V_1(s)} = \frac{R_0}{R_0 + K_1 T_c s} \quad (16.2)$$

The above transfer functions and summer signal have been used to form the (mathematical) block diagram of Fig. 16-2.

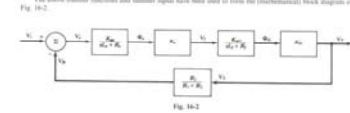


Fig. 16-2

16.2 BLOCK DIAGRAM ALGEBRA

For a control system of any complexity, the block diagram will contain many transfer functions in series and parallel arrangements. It is expedient to reduce the block diagram to more tractable form by applying the rules of block diagram algebra, as summarized in Table 16-1.

Rule	Original System	Reduced System
1. Cascaded blocks		
2. Parallel paths		
3. Moving a pick-off point		

292 BLOCK DIAGRAMS AND SIGNAL FLOW GRAPHS [CHAP. 16]

Table 16-1 (cont.)

Rule	Original System	Reduced System
4. Mating a summer		
5. Eliminating a feedback loop		

The original system of Rule 5 exhibits the canonical form into which any control system with feedback can be transformed.

Example 16.2. Reduce the block diagram of Fig. 16-3(a) to a single block.

Solution. Move the pick-off point for feedback signal $W(s)$ from the left to the right of block $C(s)$, using Rule 3. The result is shown in Fig. 16-3(b). Combine cascaded series-connected blocks in the forward and feedback paths by Rule 1, giving the reduced block diagram of Fig. 16-3(c). Finally, the single negative feedback loop is obtained by Rule 5, to yield the diagram of Fig. 16-3(d).


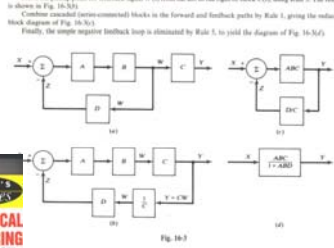


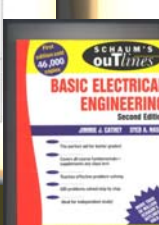

Fig. 16-3



23. mars 2010





UNIVERSITETET
I OSLO

First-Order Noise Shaping (Figures from Schreier & Temes '05)

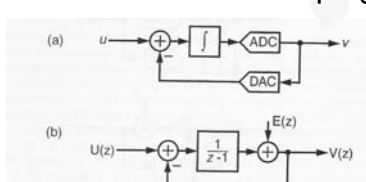


Figure 1.4: (a) A delta-sigma modulator used as an ADC and (b) its linear z-domain model.

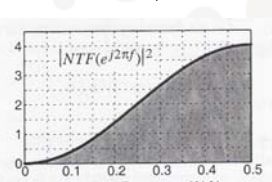




Figure 1.5: Noise-shaping function for the $\Delta\Sigma$ modulator shown in Fig. 1.4.

- $S_{TF}(z) = [H(z)/1+H(z)]$ (eq. 14.15) $N_{TF}(z) = [1/1+H(z)]$
- $Y(z) = S_{TF}(z) U(z) + N_{TF}(z) E(z)$
- $H(z) = 1/z-1$ (discrete time integrator) gives 1st order noise shaping
- $S_{TF}(z) = [H(z)/1+H(z)] = 1/(z-1)/[1+1/(z-1)] = z^{-1}$
- $N_{TF}(z) = [1/1+H(z)] = 1/[1+1/(z-1)] = (1 - z^{-1})$
- The signal transfer function is simply a delay, while the noise transfer function is a discrete-time differentiator (i.e. a high-pass filter)

23. mars 2010





UNIVERSITETET
I OSLO

14.2 Oversampling with noise shaping

$$N_{TF}(f) = 1 - e^{-j2\pi f/f_s} = (e^{j\pi f/f_s} - e^{-j\pi f/f_s}) \cdot e^{-j\pi f/f_s} = (e^{j\pi f/f_s} - e^{-j\pi f/f_s}) \cdot 2j \cdot e^{-j\pi f/f_s}$$

$$= 2j \sin\left(\frac{\pi f}{f_s}\right) \cdot e^{-j\pi f/f_s}$$

$$|N_{TF}(f)| = 2 \sin\left(\frac{\pi f}{f_s}\right) \quad (\text{high-pass})$$

$$\cos z = \frac{e^{jz} + e^{-jz}}{2}$$

$$\sin z = \frac{e^{jz} - e^{-jz}}{2j}$$

Quantization noise power over the frequency band 0 to f_0 is now given by

$$P_e = \int_{-f_0}^{f_0} S_e^2(f) \cdot |N_{TF}(f)|^2 df = \int_{-f_0}^{f_0} \left(\frac{\Delta^2}{12}\right) \frac{1}{f_s} \left[2 \sin\left(\frac{\pi f}{f_s}\right)\right]^2 df \quad (14.23)$$

Making the approximation that $f_0 \ll f_s$ ($OSR \gg 1$) so that $\sin\left(\frac{\pi f}{f_s}\right) \approx \frac{\pi f}{f_s}$:

$$P_e \approx \left(\frac{\Delta^2}{12}\right) \left(\frac{\pi^2}{3}\right) \left(\frac{2f_0}{f_s}\right)^3 = \frac{\Delta^2 \pi^2}{36} \left(\frac{1}{OSR}\right)^3 \quad OSR = \frac{f_s}{2f_0}$$

It is assumed that the maximum signal power is the same as obtained before, in equation 14.11 ($P_s = \Delta^2/8$), making maximum SNR:

$$SNR_{max} = 10 \log\left(\frac{P_s}{P_e}\right) = 10 \log\left(\frac{3}{2} \cdot 2^{2N}\right) + 10 \log\left[\frac{3}{\pi^2} (OSR)^3\right], \text{ or:}$$

$$SNR_{max} = 6.02N + 1.76 - 5.17 + 30 \log(OSR)$$

Doubling the OSR gives an SNR improvement for a 1st order modulator of 9 dB/octave or, equiv. 1.5 bits/octave.

Quantization noise power for linearized model of a general $\Delta\Sigma$ modulator

$$P_e = \int_{-f_0}^{f_0} S_e^2(f) |N_{TF}(f)|^2 df = \int_{-f_0}^{f_0} \left(\frac{\Delta^2}{12}\right) \frac{1}{f_s} \left[2 \sin\left(\frac{\pi f}{f_s}\right)\right]^2 df \quad (14.23)$$

Using the approximation that $f_0 \ll f_s$ (i.e. $OSR \gg 1$)

so that we may approximate $\sin\left(\frac{\pi f}{f_s}\right)$ to be $\frac{\pi f}{f_s}$:

$$P_e = \int_{-f_0}^{f_0} \frac{\Delta^2}{12} \frac{1}{f_s} \left[2 \frac{\pi f}{f_s}\right]^2 df = \int_{-f_0}^{f_0} \frac{\Delta^2}{12} \frac{1}{f_s} \frac{4\pi^2}{f_s^2} \cdot f^2 df$$

$$\text{Letting } K = \frac{\Delta^2}{12} \frac{1}{f_s} \frac{4\pi^2}{f_s^2}$$

$$P_e = K \int_{-f_0}^{f_0} f^2 df = \frac{K}{3} (f_0^3 - (-f_0)^3) = \frac{K}{3} \cdot 2 f_0^3$$

$$= \frac{\Delta^2}{12} \frac{1}{f_s} \frac{4\pi^2}{f_s^2} \cdot \frac{2}{3} \cdot f_0^3 = \frac{\Delta^2}{12} \frac{\pi^2}{3} \cdot \frac{2 \cdot 2 \cdot 2}{f_s^3} \cdot f_0^3 = \frac{\Delta^2}{12} \frac{\pi^2}{3} \left(\frac{2f_0}{f_s}\right)^3$$

23. mars 2010


Using $OSR = \frac{f_s}{2f_0} \Leftrightarrow \frac{2f_0}{f_s} = \frac{1}{OSR}$: $P_e = \frac{\Delta^2 \pi^2}{36} \left(\frac{1}{OSR}\right)^3 \quad (14.24)$

if

10

TET

Second-order noise shaping

 

The above modulator realizes 2nd order noise shaping.

The signal transfer function is given by

$$S_{TF}(f) = z^{-1}$$

The noise transfer function is given by

$$N_{TF}(f) = (1 - z^{-1})^2$$

Magnitude: $|N_{TF}(f)| = [2 \sin(\frac{\pi f}{f_c})]^2$

The quantization noise power over the frequency band of interest:

$$P_e \approx \frac{\Delta^2 \pi^4}{60} \left(\frac{1}{OSR}\right)^5$$



Max SNR:

$$SNR_{max} = 10 \log\left(\frac{P_s}{P_e}\right) = 10 \log\left(\frac{3}{2} 2^{2N}\right) + 10 \log\left[\frac{5}{\pi^4} (OSR)^5\right]$$

or:

$$SNR_{max} = 6.02N + 1.76 - 12.9 + 50 \log(OSR) \quad (14.32)$$

Doubling the OSR improves the SNR for a 2nd order mod. by 15dB.

  

Ex. 14.5 p. 545:
 1-bit A/D, 6-bit SNR, $f_0 = 25 \text{ kHz}$
 96 dB SNR is the goal.
 Sample rate needed?
 - oversampling: 54 THz
 - 1st order n.s.: 7.5 MHz
 - 2nd order n.s.: 5.8 MHz

ETET

14.3 System Architectures (A/D)



 


Fig. 14.14 Block diagram of an oversampling A/D converter.

 

- $X_c(t)$ is sampled and held, resulting in $x_{sh}(n)$.
- $x_{sh}(n)$ is applied to an A/D Sigma Delta modulator which has a 1-bit output, $x_{dsm}(n)$. The 1-bit signal is assumed to be linearly related to the input $X_c(t)$ (accurate to many orders of resolution), although it includes a large amount of out-of-band quantization noise (seen to the right).
- A digital LP filter removes any high frequency content, including out of band quantization noise, resulting in $X_{ip}(n)$
- Next, $X_{ip}(n)$ is resampled at $2f_0$ to obtain $X_s(n)$ by keeping samples at a submultiple of the OSR

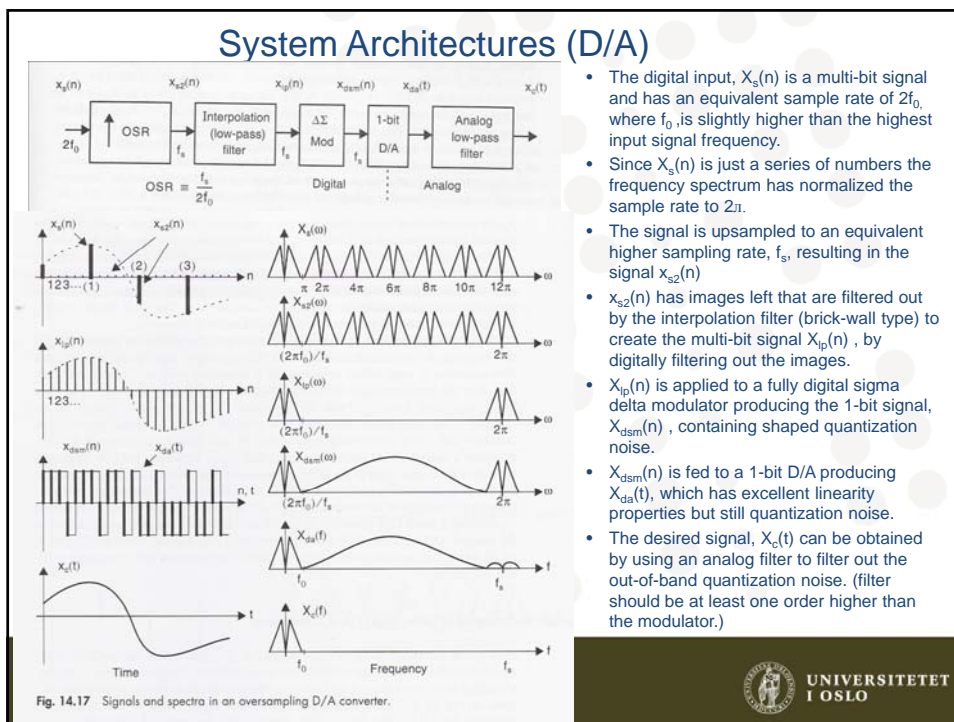

14.4 Digital decimation filters

 


Fig. 14.18 Multi-stage decimation filters: (a) sinc followed by an IIR filter; (b) sinc followed by halfband filters.

- Many techniques
- a) FIR filter removes much of the quantization noise, so that the output can be downsampled by a 2nd stage filter which may be either IIR type (as in a), uppermost) or a cascade of FIR filters (as in b), below)
- In b) a few halfband FIR filters in combination with a sinc compensation FIR-filter are used.

In some applications, these halfband and sinc compensation filters can be realized using no general multi-bit multipliers [Saramaki, 1990]

14.5 Higher-Order Modulators – Interpolative structure

 


Fig. 14.20 A block diagram of a fifth-order modulator.

- L th order noise shaping modulators improve SNR by $6L+3\text{dB/octave}$.
- Typically a single high-order structure with feedback from the quantized signal.
- In figure 14.20 a **single-bit D/A** is used for feedback, **providing excellent linearity**.
- Unfortunately, modulators of order two or more can go unstable, especially when large input signals are present (and may not return to stability)
Guaranteed stability for an interpolative modulator is nontrivial.

Multi-Stage Noise Shaping architecture ("MASH")

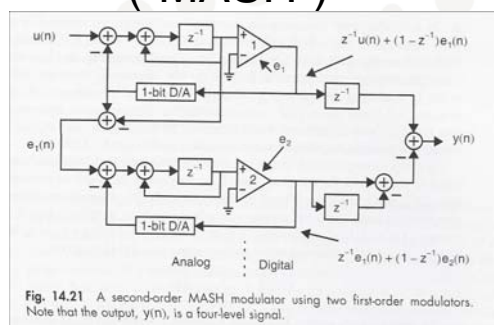


Fig. 14.21 A second-order MASH modulator using two first-order modulators. Note that the output, $y(n)$, is a four-level signal.

- Overall higher order modulators are constructed using lower-order, more stable, ones \rightarrow more stable overall system.
- Fig. 14.21: 2nd order using two first-order modulators.
- Higher order noise filtering can be achieved using lower-order modulators.
- Unfortunately sensitive to finite opamp gain and mismatch

14.7 Practical considerations

- Stability
- Linearity of two-level converters
- Idle tones
- Dithering
- Opamp gain

For this case, the output sequence becomes
 $y(n) = \{1, 1, -1, 1, 1, -1, 1, 1, -1, 1, 1, -1, 1, 1, -1, 1, -1, \dots\}$ (14.47)
 The period of this output pattern is now 16 cycles long and has some power at $f_s/16$. With an oversampling ratio of eight (i.e., $f_s = f_s/16$), the post low-pass filter will not attenuate the signal power at $f_s/16$ since that frequency is just within the frequency band of interest. In other words, a dc level of 3/8 into this modulator will produce the correct dc output signal.

 


Fig. 14.26 Adding dithering to a delta-sigma modulator. Note that the dithered signal is also noise shaped.



Design example, 14b 2nd order Sigma-Delta mod

BOSER AND WOOLEY: SIGMA-DELTA MODULATION ANALOG-TO-DIGITAL CONVERTERS

 
 


Fig. 1. Block diagram of second-order $\Sigma\Delta$ modulator with decimator.

 


Fig. 2. Modified architecture of second-order $\Sigma\Delta$ modulator.

- 16 bit, 24 kHz , OSR as powers of two, and allowing for increased baseband noise due to nonidealities: OSR 512 was chosen



Design example, 14b 2nd order Sigma-Delta mod

• Among most relevant nonidealities:

- Finite DC gain
- Bandwidth,
- Slew rate
- Swing limitation
- Offset voltage
- Gain nonlinearity
- Flicker noise
- Sampling jitter
- Voltage dependent capacitors
- Switch on-resistance
- Offset voltage and settling time for comparators


 


Fig. 15. Dynamic range as a function of the oversampling ratio for a sampling frequency of 4 MHz.

 

Design example, 14b 2nd order Sigma-Delta mod

4.1 Specification of modulator functions

- SYSTEM
 - Technology: CMOS 0.8 micron
 - Power supply: VSS = -2.5 V, GND = 0 V, VDD = 2.5 V
 - Temperature: 0 to 70 degrees C
- OPERATIONAL AMPLIFIER
 - Gain: 1000 (60 dB)
 - Unity-Gain Bandwidth: 100 MHz
 - Phase Margin: 60°
 - Maximum capacitive load: several pF
 - Input voltage swing: 4 V
 - Diff. output voltage swing: ≥ 6V
 - Slew rate: at least $300 \frac{V}{\mu s}$
- SWITCH
 - $R_{on} < 440\Omega$
- CAPACITORS
 - Type:
 - C_1 : 1 pF
 - C_2 : 2 pF
- LATCH
 - D-type, able to settle within 20 ns.
- COMPARATOR
 - Hysteresis: < 0.5 V
 - Settling time: < 20 ns

 


Figure 11: Dummy switch charge injection compensation circuit.


 



Fig. 1. Fully differential folded-cascode amplifier (after [4]).

 

- Noninverting parasitic insensitive integrator (fig 10.9) was used (fully differential implementation)



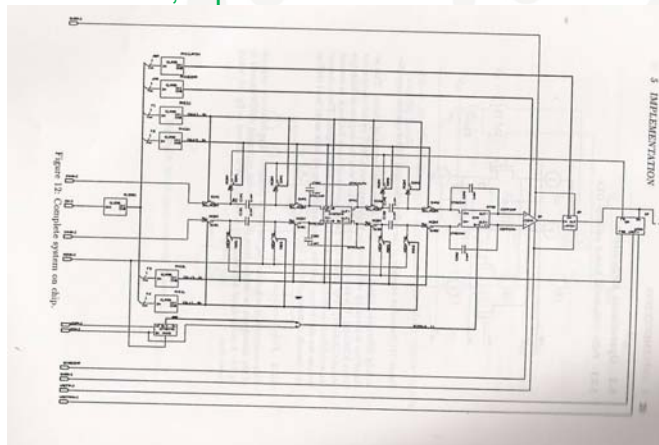2nd order modulator; top level schematics





- Two-phase clock generator, switches, chopper stabilized OTA (1st int.), OTA (2nd int.- fully differential folded cascode), comparator, latch, two-level DAC. Biasing circuit. Functional after test.

Phase-locked loops (chapter 16)

- **Phase-locked loop**
- From Wikipedia, the free encyclopedia
- A **phase-locked loop** or **phase lock loop** (PLL) is a [control system](#) that generates a [signal](#) that has a fixed relation to the [phase](#) of a "reference" signal. A phase-locked loop circuit responds to both the frequency and the phase of the input signals, automatically raising or lowering the frequency of a controlled [oscillator](#) until it is matched to the reference in both frequency and phase. A phase-locked loop is an example of a control system using negative [feedback](#).
- Phase-locked loops are widely used in [radio](#), [telecommunications](#), [computers](#) and other electronic applications. They may generate stable frequencies, recover a signal from a noisy communication channel, or distribute clock timing pulses in digital logic designs such as [microprocessors](#). Since a single [integrated circuit](#) can provide a complete phase-locked-loop building block, the technique is widely used in modern electronic devices, with output frequencies from a fraction of a cycle per second up to many gigahertz.

Phase-locked loops (chapter 16)

 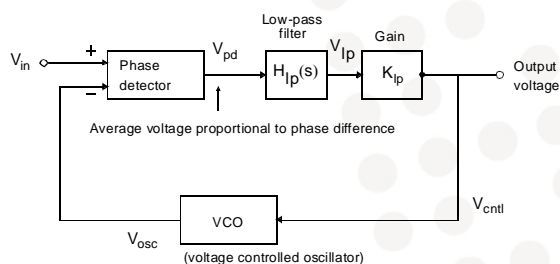

- Clock multiplication:
 - The input signal is reference oscillator with fixed frequency
 - The PLL output is a signal with frequency N times the input frequency where N is an integer
- Data recovery and clock resynchronization:
 - The input signal is a digital signal containing data
 - The output is digital data at a certain clock rate
 - The system clock is recovered from the digital input signal
- Frequency synthesis (ex: to select channels in television or wireless communication systems):
 - The input signal is reference oscillator with fixed frequency
 - The PLL output is a signal with frequency N times the input frequency where N may be a fractional number
- FM demodulation:
 - The input is a FM signal (IF)
 - The output is the demodulated baseband signal

Phase-Locked Loop, typical architecture


 


Fig. 16.1 The basic architecture of a phase-locked loop.

- The *phase detector* ("PD") normally has an output voltage with an average value proportional to the phase difference between the input signal and the output of the VCO ("Voltage Controlled Oscillator").
- The *low-pass filter* is used to extract the average value from the output of the PD.
- The average value is amplified by the *Gain* block and used to drive the VCO.
- The negative feedback of the loop results in the output of the VCO being synchronized with the input signal.

Phase-locked loop example (p. 649)

 

- The input signal, V_{in} , is assumed to be a sinusoid with known amplitude.
- The phase detector is realized as an analog multiplier with $V_{pd} = K_M \cdot V_{in} \cdot V_{osc}$ \wedge K_M : multiplication constant.
- $H_{lp}(s) = \frac{1+s\tau_z}{1+s\tau_p}$, $\tau_z \ll \tau_p$; first-order LEAD-LAG filter.
- $V_{in} = E_{in} \cdot \sin(\omega t)$
- $V_{osc} = E_{osc} \sin(\omega t - \Phi_d + 90^\circ) = E_{osc} \cos(\omega t - \Phi_d)$

23. mars 2010 Φ_d represents the phase difference between the input signal and the output of the oscillator. The reason for the 90° offset is that the PD (analog mult.) has a zero average output for a phase difference of zero.

V_{in} and V_{osc} exactly in phase when $\Phi_d=90^\circ$

- $V_{in} = E_{in} \sin(\omega t)$,
- $V_{osc} = E_{osc} \sin(\omega t - \Phi_d + 90^\circ) = E_{osc} \sin(\omega t - 90^\circ + 90^\circ) = E_{osc} \sin(\omega t)$
- The input signal and the output of the oscillator will be exactly in phase, and the output from the phase detector ("PD") is found to be the amplitudes of the two sinusoids multiplied together and divided by 2, resulting in

$$V_{ctrl} = K_p K_M E_{in} E_{osc} / 2 \quad (\text{Eq. 16.5, p 650 in J\&M})$$

Fig. 16.2, below, shows the output from the PD when V_{in} and V_{osc} are nearly in phase.


 
 


Fig. 16.1 The basic architecture of a phase-locked loop.

26

 Examples of different waveforms, as a function of different Φ_d ,
(J&M p 650-651 ,fig. 16.3)

- $V_{osc} = E_{osc} \sin(\omega t - \Phi_d + 90^\circ) = E_{osc} \cos(\omega t - \Phi_d)$ (16.4)
- $\Phi_d > 0$ corresponds to waveforms that are more in phase.
- When the input signal and VCO output have a 90° phase diff. ($\Phi_d = 0$), they are uncorrelated and the output of the LP-filter will be zero.)



the relative phase angles of the input signal and the output of the oscillator.
Fig. 16.3

 


Fig. 16.1 The basic architecture of a phase-locked loop.

27



Some relevant mathematical relationships from 16.1, pages 650-652 in "J&M"

- The output of the phase detector:
 - $V_{pd} = K_M V_{in} V_{osc} = K_M E_{in} E_{osc} \sin(\omega t) \cos(\omega t - \Phi_d)$ (16.6)
 - Using $\sin(A)\cos(B) = (1/2)[\sin(A+B) + \sin(A-B)]$ we have
 $V_{pd} = K_M V_{in} V_{osc} / 2 [\sin(\Phi_d) + 2\sin(2\omega t - \Phi_d)]$ (16.8)
 - The LP-filter removes the second term at twice the frequency of the input signal, so V_{cntl} is therefore given by
 $V_{cntl} = K_{lp} K_M (E_{in} E_{osc} / 2) \sin(\Phi_d)$ (16.9)
 - Since V_{cntl} is either a dc value or slowly varying, for small Φ_d the following approximation for (16.9) may be used:
 $V_{cntl} \approx K_{lp} K_M (E_{in} E_{osc} / 2) \Phi_d = K_{lp} K_{pd} \Phi_d$ (16.10)
- Thus, the output of the LP-filter is approximately proportional to the phase difference between the output of the oscillator and the input signal, assuming the 90° offset bias is ignored. The approximation is used in analyzing the PLL to obtain a linear model. The constant of proportionality is called K_{pd} and is given by
- $$K_{pd} = K_M (E_{in} E_{osc} / 2)$$
- (16.11)

23. mars 2010

 



Fig. 16.1 The basic architecture of a phase-locked loop.

28



More on PLL operation (p. 652-653)

- Assume that the VCO has a free-running frequency ω_{fr} when it's input is zero, and that the input signal is initially equal to ω_{fr} and the system has $\Phi_d = 0$ (in lock).
- NEXT, assume the **input frequency** slowly **increases**. Now, with $\Phi_d > 0$, the two waveforms will become more in phase (See fig. 16.3). After a short time the output of the LP-filter will go positive. Since the two waveforms are at slightly different frequencies, the output of the LP-filter will slowly increase. Since the VCO frequency is proportional to V_{cntl} , this increase will cause the VCO frequency to increase until it is the same of that of the input signal again, which will keep the two signals in synchronism (i.e. **locked**). (The opposite would occur for a **decrease** in the input signal frequency.)

 

The relative phase angles of the input signal and the output of the oscillator.

Fig. 16.3

 



Fig. 16.1 The basic architecture of a phase-locked loop.

 23. mars 2010



More on PLL operation (p. 652-653)

- At a new input frequency, ($\neq \omega_{fr}$) which does not equal the free-running frequency, we can find the new phase difference for the two locked signals by noting that the frequency of the oscillator's output signal is given by $\omega_{osc} = K_{osc} V_{cntl} + \omega_{fr}$ (16.12). K_{osc} is a constant relating the change in frequency to control voltage ratio. The output voltage of the amplified LP-filter is now given by $V_{cntl} = (\omega_{in} \omega_{fr}) / K_{osc}$ (16.13) where ω_{in} is the frequency of the input signal, which is equal to the frequency of the oscillator's output. From (16.10): $\Phi_d = V_{cntl} (K_{ip} K_{pd}) = (\omega_{in} - \omega_{fr}) / K_{ip} K_{pd} K_{osc}$ (16.14)



The relative phase angles of the input signal and the output of the oscillator.

Fig. 16.3


 


Fig. 16.1 The basic architecture of a phase-locked loop.

23. mars 2010

 

Ex. 16.2



Ex. 16.1 problem to the right

$$\Phi_d = \frac{V_{cntl}}{K_{lp} \cdot K_{pd}} = \frac{\omega_{in} - \omega_r}{K_{lp} \cdot K_{pd} \cdot K_{osc}} \quad (16.14)$$

K_{pd} and K_{osc} are needed in 16.14:

The phase detector realized as an analog multiplier has the following relationship:

$$V_{pd} = K_M \cdot V_{in} \cdot V_{osc} \quad (16.1)$$

$$K_M = \frac{2.0V}{2.0V \cdot 2.0V} = \left(= \frac{V_{pd}}{V_{in} \cdot V_{osc}} \right) \Leftrightarrow K_M = 0.5 \frac{1}{V}$$

$$K_{pd} = K_M \cdot \frac{E_{in} - E_{osc}}{2} = 0.5 \frac{1}{V} \cdot \frac{0.75V - 0.75V}{2} = 0.140625 V$$

Using 16.14: $\Phi_d = \frac{2\pi(11MHz - 10MHz)}{K_{lp} \cdot K_{pd} \cdot K_{osc}} = 0.7112 rad = 40.8^\circ$

EX. 16.1

Consider a PLL where the amplitudes of the inp. signal and the oscillator output are both at a 0.75 V peak. The analog mult. which would have 2V output when both inputs are DC values of 2V. The VCO free-running frequency is 10 MHz, and would decrease to zero for $V_{cntl} = -1V$. The gain block is unity, i.e. $K_{lp} = 1$. When in lock, what is the phase difference between the input and osc. output when $f_{in} = 11 MHz$? What is the phase difference when the input is 9 MHz? How does the phase difference change if $K_{lp} = ?$?


Control voltage ratio: $\frac{\Delta \omega_{osc}}{\Delta V_{cntl}} = \frac{2\pi \cdot 10^6 rad/s}{7V}$
 Counting in 90° offset: $90 - 40.8 = 49.2^\circ$

23. mars

31



Ex. 16.1

 

$f_{in} = 11 MHz$: The phase difference between the input and oscillator output becomes $90^\circ - 40.8^\circ = 49.2^\circ$.

$f_{in} = 9 MHz$: $\Phi_d = -40.8^\circ \Rightarrow$ phase difference of $90^\circ - (-40.8^\circ) = 130.8^\circ$


For $K_{lp} = 2$, half the phase difference results in the same VCO control voltage, V_{cntl} . So, for $\omega_{in} = 11 MHz$, $\Phi_d = \frac{40.8^\circ}{2} = 20.4^\circ$, and for $9 MHz$, $\Phi_d = -20.4^\circ$. (Since $\Phi_d = \frac{\omega_{in} - \omega_r}{K_{lp} \cdot K_{pd} \cdot K_{osc}}$)

23. mars

32



Linear model of the PLL – when in lock

 

$$V_{\text{ctrl}}(s) = K_{\text{pd}} K_{\text{lp}} H_{\text{lp}}(s) [\phi_{\text{in}}(s) - \phi_{\text{osc}}(s)]$$

$$\phi_{\text{osc}}(s) = \frac{K_{\text{osc}} V_{\text{ctrl}}(s)}{s}$$

PLL transfer functions

- Combining equations from previous slide:

$$\frac{V_{\text{ctrl}}(s)}{\phi_{\text{in}}(s)} = \frac{s K_{\text{pd}} K_{\text{lp}} H_{\text{lp}}(s)}{s + K_{\text{pd}} K_{\text{lp}} K_{\text{osc}} H_{\text{lp}}(s)}$$

- This is a highpass response from input phase to the control voltage.
- Rewriting gives:

$$\frac{\phi_{\text{osc}}(s)}{\phi_{\text{in}}(s)} = \frac{K_{\text{pd}} K_{\text{lp}} K_{\text{osc}} H_{\text{lp}}(s)}{s + K_{\text{pd}} K_{\text{lp}} K_{\text{osc}} H_{\text{lp}}(s)}$$

- This is a lowpass response from the input phase

Additional litterature

- **Walt Kester**: *Which ADC Architecture is right for your application?*, Analog Dialogue, Analog Devices, 2005.
- **Behzad Razavi**: "Design of Analog CMOS Integrated Circuits", McGraw-Hill, reprint 2009.
- **Jimmy J. Cathey, Syed A. Nasar**: *Basic Electrical Engineering*, Schaum's Outlines, McGraw Hill 1997.
- **Richard Schreier, Gabor C. Temes**: *Understanding Delta-Sigma Data Converters*, IEEE Press / Wiley Interscience, 2005
- **Tapio Saramaki et. Al**: *Multiplier-Free Decimator Algorithms for Super-Resolution Oversampled Converters*, IEEE International Symposium on Circuits and Systems, 1990.
- **Bernhard A. Boser, Bruce A. Wooley**: *The Design of Sigma-Delta Modulation Analog-to-Digital Converters*, IEEE Journal of Solid-State Circuits, December 1988.
- **Sudhir M. Mallya, Joseph H. Nevin**: *Design Procedures for a Fully Differential Folded-Cascode CMOS Operational Amplifier*, IEEE Journal of Solid-State Circuits, December 1989.
- <http://www.wikipedia.org> (on PLLs)
- **Snorre Aunet**: *Second-Order Sigma Delta Modulator*, Nordic VLSI, May 4, 1994.

Next Time, 13/4-10:


- More from Chapter 16; PLLs
- About report writing

23.03.2010	SA	Lille Aud.	Chapter 14; Oversampling Converters	preliminary... Slides Slides, two per page
30.03.2010				No teaching in week 13.
06.04.2010				No teaching in week 14, due to Easter holidays.

13.04.2010	SA	Lille Aud.	chapter 16; PLLs	Later... Slides Slides, two per page
------------	----	------------	------------------	--




TRANSFER

 


Johns & Martin are treating the linear model as having two independent inputs.


SIGNAL

 

Eliminating the feedback loop:

 

ORIGINAL

 

REDUCED








23. mars 2010

37



NOISE

     

$$S_{TF}(z) \equiv \frac{Y(z)}{V(z)} \quad (14.15)$$


$$N_{TF}(z) \equiv \frac{Y(z)}{E(z)} \quad (14.16)$$

THE OUTPUT SIGNAL CAN BE WRITTEN AS A COMBINATION OF THE INPUT SIGNAL AND THE NOISE SIGNAL EACH BEING FILTERED BY THE CORRESPONDING TRANSFER FUNCTION,

23. mars 2010

38



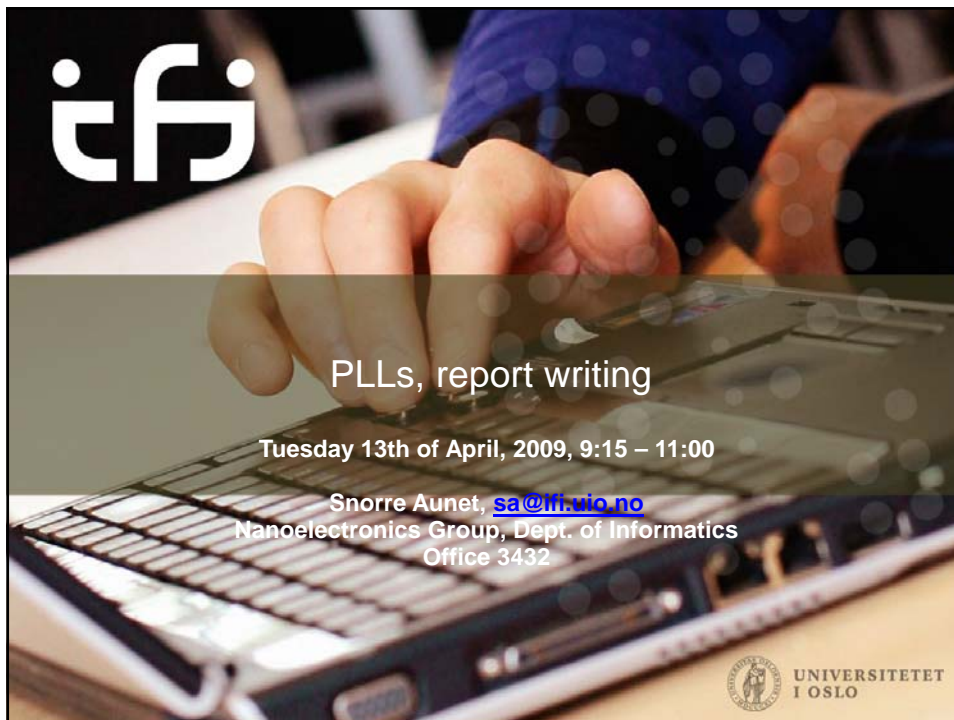


ifj

PLLs, report writing

Tuesday 13th of April, 2009, 9:15 – 11:00


Snorre Aunet, sa@ifi.uio.no
 Nanoelectronics Group, Dept. of Informatics
 Office 3432

 UNIVERSITETET
I OSLO

Last time – and today, Tuesday 13th of April:

March the 23rd:

 - 14.2 Oversampling with noise shaping
- 14.3 System Architectures
- 14.4 Digital Decimation Filters
- 14.5 Higher-Order Modulators
- (14.6 Bandpass Oversampling Converters)
- 14.7 Practical Considerations
- 14.8 Multi-bit oversampling converters
- 2nd order sigma delta design example
- 16.1 Basic Phase Locked Loop Architecture




Today:

- 16.1 Linearized small-signal analysis of general PLLs
- 16.2 PLLs with charge-pump phase comparators
- 16.3 Voltage controlled oscillators
- 16.4 Computer Simulations of PLLs
- About writing the report

PLL Basic Architecture

- In general, output may be V_{ctrl} or V_{osc}

 PLL linear model applying to almost every PLL



$$V_{ctrl}(s) = K_{pd}K_{lp}H_{lp}(s)[\phi_{in}(s) - \phi_{osc}(s)]$$

$$\phi_{osc}(s) = \frac{K_{osc}V_{ctrl}(s)}{s}$$

$$H_{lp}(s) = \frac{1 + s\tau_z}{1 + s\tau_p}$$

- Combining above 2 equations ...

$$\frac{V_{ctrl}(s)}{\phi_{in}(s)} = \frac{sK_{pd}K_{lp}H_{lp}(s)}{s + K_{pd}K_{lp}K_{osc}H_{lp}(s)}$$

- This is a highpass response from input phase to control voltage

- Can also be written as

$$\frac{\phi_{osc}(s)}{\phi_{in}(s)} = \frac{K_{pd}K_{lp}K_{osc}H_{lp}(s)}{s + K_{pd}K_{lp}K_{osc}H_{lp}(s)}$$

- This is a lowpass response from input phase to output phase

- Differences between PLLs are determined only by what is used for the LP-filter ($H_{lp}(s)$), the Phase Detector (K_{pd}) or the oscillator (K_{osc}).

More on the 2nd order PLL model

2nd order transfer functions are often written in the form:

$$H(s) = \frac{N(s)}{D(s)}$$

$$D(s) = 1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}$$

ω_0 : resonant frequency

Transient time for the complete loop:

$$\tau_{pll} \approx \frac{1}{\omega_0}$$

12. Q : Q-factor, damping factor

Good settling: $Q = 0.5$

max. flat group delay: $Q = \frac{1}{\sqrt{3}} = 0.577$

max. flat amplitude resp.: $Q = \frac{1}{\sqrt{2}} = 0.707$

$$\omega_0 = \frac{K_{pll}}{\sqrt{\tau_p}} \quad (16.32)$$

$$Q = \frac{\sqrt{\tau_p}}{\frac{1}{K_{pll}} \tau_z K_{pll}}$$

$$K_{pll} = \sqrt{K_{pd} \cdot K_{lp} \cdot K_{oc}}$$

Usually, when $\omega_0 \ll \omega_{fr}$:

$$Q \approx \frac{1}{\omega_0 \tau_z} = \frac{\sqrt{\tau_p}}{\tau_z K_{pll}} \quad (16.35)$$

When $Q = 0.5$:

$$\tau_z = \frac{2\sqrt{\tau_p}}{K_{pll}} = \frac{2}{\omega_0}$$

5

TET

Capture range, lock range, false lock

- The maximum difference between the input signal's frequency and the oscillator's free-running frequency where lock can eventually be attained is defined as the **capture range**
- Once lock is attained, as long as the input signal's frequency changes only slowly it will remain in lock over a range that is much larger than the capture range
- When a multiplier is used for the phase detector the loop may lock to harmonics (multiple of the frequency) of the input signal. This is called a **false lock**.

Exclusive-OR Phase comparators

V_{in}	V_{osc}	V_{pd}
0	0	0
0	1	1
1	0	1
1	1	0

put given by $V_{pd} = V_{in} \oplus V_{osc}$, where the amplitudes of the signals are determined by the logic levels. Some typical waveforms are shown in Fig. 16.6. It is seen that


 


Fig. 16.6 Typical waveforms when an exclusive-OR gate is used as a phase comparator

 - When the waveforms are **90 degrees** out of phase the output is a waveform at **twice the frequency** of the input signal and has a **50 percent duty cycle**.
- If all waveforms are symmetric about 0 volts the average value extracted by the low-pass filter would be zero.



EXOR phase comp



90° degrees out of phase
50% duty cycle

 


Fig. 16.1 The basic architecture of a phase-locked loop.

- When the waveforms become **more out of phase**, the average value of the output signal is **positive**; whereas when they become **more in phase**, the **average value** of the output signal is **negative**



CHARGE-PUMP COMPARATOR

- no false lock, attains lock quickly
- V_{in} and V_{osc} are exactly in phase when the system is in lock.
- injects, leaves alone, or subtracts charge on the capacitor in the LP-filter, depending on P_u and P_d .
- S_1 closed: I_{ch} increases the control voltage into the VCO
- S_2 closed: I_{ch} flows out of the LP-filter, decreasing the control voltage.
- S_1 and S_2 open: steady state
- P_u and P_d are digital signals
- IF V_{in} goes to 1 before V_{osc} , then P_u will be 1 during the time that the signals are different. \Rightarrow injecting charge ELSE if V_{osc} goes to 1 before V_{in} , P_d will be 1 during the time that the inputs are

different $\Rightarrow S_2$ will be closed, removing charge from the loop-filter and decreasing the VCO frequency.

OBS: Notice that P_u only goes high at the leading edges and is insensitive to the falling edges.

Fig. 16.1 The basic architecture of a phase-locked loop.

Small-Signal Model of the Charge-Pump PLL

In average the current from the CP is: $I_{avg} = \frac{\Delta\phi_{in}}{2\pi} I_{ch}$

The transfer function from the loop filter is (C2 ignored):

$$H_{lp}(s) = \frac{V_{lp}(s)}{I_{avg}(s)} = R + \frac{1}{sC_1} = \frac{1 + sRC_1}{sC_1}$$

$$\frac{\phi_{osc}(s)}{\phi_{in}(s)} = \frac{(1 + sRC_1)}{1 + sRC_1 + \frac{s^2 C_1}{K_{pd} K_{osc}}}$$

$$\omega_0 = \frac{1}{\tau_{pll}} = \sqrt{\frac{I_{ch} K_{osc}}{2\pi C_1}}$$

$$Q = \frac{1}{RC_1 \omega_0} = \frac{1}{R} \sqrt{\frac{2\pi}{C_1 I_{ch} K_{osc}}}$$

Ex. 16.4

Ex. 16.4 $K_{osc} = 2\pi \times 50 \text{ Mrad/V}$
 $I_{ch} = 10 \mu\text{A}$, $\omega_{tr} = 50 \text{ MHz}$
 and the loop has a time constant of 100 cycles, or $2 \mu\text{s}$.
 Design the components of the LP-filter in fig. 16.7

fig. 16.7

Let $C_2 = \frac{C_2}{10} = 200 \text{ pF}$
 Let $Q = 0.4$
 From 16.61:
 $Q = \frac{1}{R C_1 \omega_0} = \frac{1}{R} \sqrt{\frac{2\pi}{C_1 I_{ch} K_{osc}}}$
 $R = \frac{1}{Q} \sqrt{\frac{2\pi}{2 \text{ nF} \cdot 10 \mu\text{A} \cdot 2\pi \times 50 \text{ Mrad/s}}}$
 $= 2.5 \text{ k}\Omega$

$\omega_0 = \frac{1}{2 \mu\text{s}} = 500 \text{ k rad/s}$


$\omega_0 = \sqrt{\frac{K_{pd} \cdot K_{osc}}{C_1}} \wedge K_{pd} = \frac{I_{ch}}{2\pi} \text{ (16.6.14.56)}$

$\omega_0^2 = \frac{K_{pd} \cdot K_{osc}}{C_1} \Leftrightarrow C_1 = \frac{K_{pd} \cdot K_{osc}}{\omega_0^2}$

$C_1 = \frac{I_{ch}}{2\pi} \cdot \frac{K_{osc}}{\omega_0^2}$
 $= \frac{10 \mu\text{A}}{2\pi} \cdot \frac{2\pi \times 50 \text{ Mrad/s}}{(500 \text{ k rad/s})^2} = 2 \text{ nF}$


$C_1 = 10 \text{ nF}$
 $C_2 = 200 \text{ pF}$

Phase Frequency Detector (PFD)

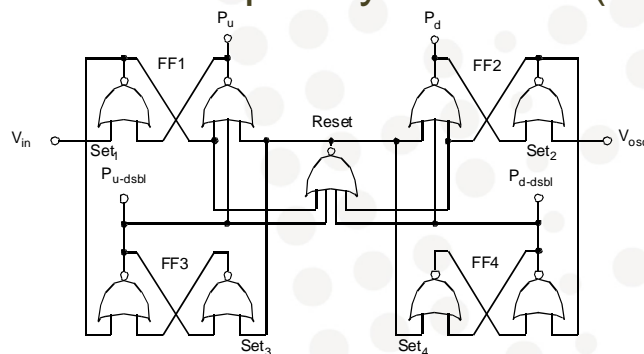

- Most commonly used sequential phase detector is the Phase Frequency Detector (PFD).
- This circuit handles phase differences up to 2π .


Phase Frequency Detector (PFD)

 


- Assume P_u , P_d , P_{u-dsbl} , P_{d-dsbl} , Reset, V_{in} , V_{osc} are low
- V_{in} goes high; FF1 set/ P_u goes high -> VCO frequency increases
- V_{osc} goes high; FF2 set temporarily, reset goes high, causing P_u and P_d go low after some delay. Reset going high causes FF3 and FF4 to be set and P_{u-dsbl} and P_{d-dsbl} go high, which later causes reset to go low. FF1 and FF2 are kept in reset mode and P_u and P_d low.
- V_{in} goes back to 0; FF3 reset and P_{u-dsbl} is turned off.
- Similarly, when V_{osc} goes low, FF4 is reset goes low, FF4 is reset and P_{d-dsbl} goes low. (back to original state). (The operation is very similar if V_{osc} leads V_{in})



 
PFD waveforms – when V_{in} has a much higher frequency than V_{osc}



- Whenever a positive going edge of V_{in} occurs, P_u goes high causing the VCO frequency to increase, and stays high until both V_{in} and V_{osc} go to 1. Then reset goes high, setting both P_{u-dsbl} and P_{d-dsbl} , and causing P_u and P_d to go low. The next time V_{in} goes to 0, FF1 is reset, which resets FF3, turning P_{u-dsbl} off.
- Most of the time (here) P_u is high, causing V_{osc} to quickly increase in frequency until lock is achieved.
- No false lock
- Only suitable for digital (non-sine) inputs

 


Voltage controlled oscillators (VCO)

 

- Sinusoidal output oscillators usually realized some frequency selective or tuned circuit in feedback configuration, while square-wave output oscillators are usually realized using a nonlinear feedback config.
- The tuned oscillators offers better frequency stability, but limited tuning range.



Ring oscillators

 

0.2 V subthreshold VCO

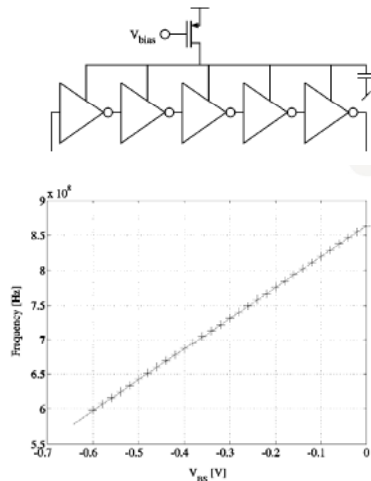


Figure 3. RVCO transfer function for a 5 stage RVCO simulated in Cadence

 


Figure 4. Sensitivity of the RVCO illustrates a nonlinearity of 0.5 %

Linearity of Bulk-Controlled Inverter Ring VCO in Weak and Strong Inversion

Ulrik Wisnar*, Dag Wisland**, Pietro Andreani*


*Centre for Physical Electronics, OrstedDTU, Technical University of Denmark, DK-2800 Kgs. Lyngby, Denmark

**Microelectronic Systems, Department of Informatics, University of Oslo, N-0316 Oslo, Norway



UNIVERSITETET
I OSLO

Differential inverter

 


- Programmable delay
- Cascode transistors Q3, Q4 to increase output impedance of programmable current sources for better PSRR
- $I_B = K_{bias} V_{ctrl}$ (proportional)
- τ proportional to C_L / g_m , f_{osc} proportional to $\sqrt{V_{ctrl}}$; nonlinear



UNIVERSITETET
I OSLO

Bias circuit

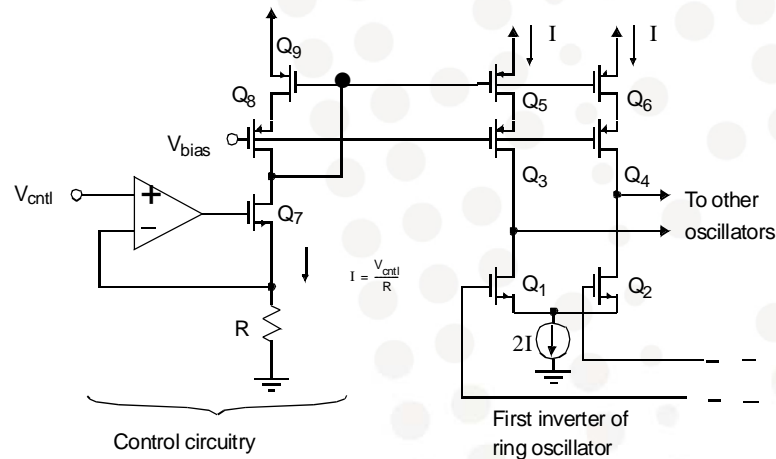



Computer simulations of PLLs

- **Nontrivial** due to often very wide range of time constants present in PLLs.
- **SPICE** simulations **only** may be highly **impractical** and take too long time.
- **Possible approach:**
 - Simulate the **individual components** using **SPICE** over a few periods of the VCO's output waveform before simulating the **complete system** using simplified models where continuous time components are replaced by **approximately equivalent difference-equation models**;
 - Simulink in Matlab (easy, don't need much expertise)
 - or** custom difference equations using for example C. (fast and may be modified for greater accuracy)

Additional litterature

- Ulrik Wismar, Dag T. Wisland, Pietro Andreani: *Linearity of Bulk-Controlled Inverter Ring VCO in weak and strong inversion*, Proceedings of IEEE Norchip Conference, 2005.
- <http://www.eecg.toronto.edu/~johns/nobots/Book/book.html>
- <http://www.iue.tuwien.ac.at/phd/grasser/node83.html> (Ring osc.)

  Remember: Grading is based on the contents of the report



Some pointers

- <http://www.idi.ntnu.no/~lasse/DM/SkriveTips.php>
- **Preface**
- **(Acknowledgement)**
- **1 Introduction**
- **2 Theoretical background**
- **(2.1 Various approaches to Nifty Gadgets)**
- **2.2 Nifty Gadgets my way**
- **3 My implementation of a Nifty Gadget**
- **4 Nifty Gadget results**
- **5 Discussion**

UNIVERSITETET
I OSLO

Nifty Gadget / DAC chapter 3

- **3 My implementation of a Nifty Gadget**
- Can you describe your implementation in detail?
Why did you use this technology?
How does the theory relate to your implementation?
What are your underlying assumptions?
What did you neglect and what simplifications have you made?
What tools and methods did you use?
Why use these tools and methods?

UNIVERSITETET
I OSLO

Nifty Gadget / DAC chapter 4

- **4 Nifty Gadget results**
- Did you actually build it?
 - How can you test it?
 - How did you test it?
 - Why did you test it this way?
 - Are the results satisfactory?
 - Why should you (not) test it more?
 - What compensations had to be made to interpret the results?
 - Why did you succeed/fail?



UNIVERSITETET
I OSLO

Nifty Gadget / DAC chapter 5

- **5 Discussion**
- Are your results satisfactory?
 - Can they be improved?
 - Is there a need for improvement?
 - Are other approaches worth trying out?
 - Will some restriction be lifted?
 - Will you save the world with your Nifty Gadget?



UNIVERSITETET
I OSLO

Guide to writing a thesis

Guide to Writing a Thesis Page 1 of 4

Guide to Writing a Thesis

*Department of Applied Electronics
Last updated 1997-03-12*

Original manuscript written by Øyvind Mattsson

The Design and Implementation of a Nifty Gadget

Tobias Lis Book
April 12, 1992

Abstract
What is all this about?
Why should I read this thesis?
Is it any good?
What's new?

Preface
Have you done anything that doesn't have to do with your research?
Have you published parts of this work before?

Acknowledgement
Who is your advisor?
Did anyone help you?
Who funded this work?
What's the name of your favorite pet?

1 Introduction
What is the use of a Nifty Gadget?
What is the problem?
How can it be solved?
What are the previous approaches?
Why do it this way?
What are your results?
Why is this better?
Is this a new approach?
Why hasn't anyone done it before?
or
Why do you restate previous work?
What is your contribution to the field of Nifty Gadgets?

Guide to Writing a Thesis Page 2 of 4

2 Theoretical background
What is the required background knowledge?
Where can I find it?

2.1 Various approaches to Nifty Gadgets
What is the relevant prior work?
Where can I find it?
Why should it be done differently?
Has anyone attempted your approach previously?
Where is that work reported?

2.2 Nifty Gadgets my way
What is the outline of your way?
Have you published it before?

3 My implementation of a Nifty Gadget
Can you describe your implementation in detail?
Why did you use this technology?
How does the theory relate to your implementation?
What are your underlying assumptions?
What did you neglect and what simplifications have you made?
What tools and methods did you use?
Why use these tools and methods?

4 Nifty Gadget results
Did you actually build it?
How was it done?
How did you test it?
Why did you test it this way?
Are the results satisfactory?
Why should you trust test it more?
What compensations had to be made to interpret the results?
Why did you succeed fail?

5 Discussion
Are your results satisfactory?
Can they be improved?
Is there a need for improvement?
Are other approaches worth trying out?
Will some restriction be lifted?
Will you save the world with your Nifty Gadget?

6 References
What is the background reading list?

Guide to writing a thesis

Guide to Writing a Thesis Page 3 of 4

Where is the related work?
Where is the prior work?
Where can I find supporting material?

Appendix A
Can you outline familiar calculus or whatever complicated theory or results you are using that will obscure the text?

Appendix B
A thesis should discuss the following topics:

- **Introduction**
Presentation of the problem or phenomenon to be addressed, the situation where the problem or phenomenon occurs, and references to earlier relevant research.
Common errors
Problem is not properly specified or formulated, insufficient references to earlier work.
- **Purpose**
What can be gained by more knowledge about the problem or phenomenon.
Common errors
The purpose is not mentioned, not connected to earlier research, or not in line with what the actual content of the thesis.
- **Problem/Hypothesis**
Questions that need to be answered to reach the goal and/or hypothesis formulated by means of underlying theories.
Common errors
Missing problem description, deficiencies in the connections between questions, badly formulated hypothesis.
- **Method**
Choice of an adequate method with respect to the purpose and problem/hypothesis.
Common errors
An inappropriate method is used, for example due to lack of knowledge about different methods; erroneous use of chosen method.
- **Result**
Answers to the forwarded questions by means of the achieved results.
Common errors
The results are not properly connected to the problem, hasty presentation, the results are inter-

Guide to Writing a Thesis Page 4 of 4

mixed with discussion.

- **Discussion**
Discussion of the accuracy and relevance of the results; comparison with other researchers results.
Common errors
Too few reaching conclusions; guesswork; not supported by the data; introduction of a new problem and a discussion around this.
- **Conclusion**
Consequences of the achieved results, for example for new research, theory and applications.
Common errors
The conclusions are too far reaching with respect to the achieved results, the conclusions do not correspond with the purpose.

[Home Page for the Department of Applied Electronics](#)

$\begin{matrix} X & Y & H & R \\ 0 & 0 & 1 & 0 \\ 0 & 1 & 1 & 0 \\ 1 & 0 & 1 & 0 \\ 1 & 1 & 1 & 0 \end{matrix}$

Assume (unrealistic) no delay in wires - just gate delays

VERSITY ISLO
 A gate delay after reset goes high, P_u and P_d go low.

1
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

2
 V_{in} goes high
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

V_{osc} goes high
3a)
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates. FF2 is set temporarily

3b)
 Reset goes high (just after V_{osc})
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates.

3c)
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates. After another delay P_u-dsbl and P_d-dsbl go high

3d)
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates. After another delay P_u-dsbl and P_d-dsbl cause Reset to go low after another gate delay (guarantee P_u and P_d low)

4)
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates. V_{in} goes low
 FF1 goes low

PD
 V_{in}
 V_{osc}
 I_{ch}
 I_{ca}
 I_{cl}

4b)
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates. after a gate delay P_u-dsbl turned off

5
 Fig. 18.7 A phase-frequency separated phase detector based on VCO gates. V_{osc} goes low
 FF4 reset (after similar chain of events as when V_{in} went low) and P_u-dsbl goes low.
 (BACK IN ORIGINAL STATE)

VERSITY ISLO

Ex. 16.2

Ex. 16.2

Assume the same conditions as in example 16.1. Design a LP-filter for the loop so that the loop time constant is approximately 10 periods at 10 MHz, $Q = \frac{1}{2}$

Equation 16.34: $K_{pll} = \sqrt{K_{pd} \cdot K_{lp} \cdot K_{osc}}$

$$= \sqrt{0.1406 \frac{\text{rad}}{\text{rad}} \cdot 1 \cdot 6.28 \cdot 10^7 \frac{\text{rad}}{\text{s}}} = \sqrt{8829680 \frac{\text{rad}}{\text{s}}} = 2972 \text{ s}^{-1/2}$$

Having a loop-time constant of 10 periods:

$$\omega_0 = \frac{1}{2\tau_{pll}} = \frac{10^7}{100} \text{ s}^{-1} = 10^5 \text{ s}^{-1}$$

16.32: $\omega_0 = \frac{K_{pll}}{\sqrt{C_1}} \Leftrightarrow \tau_p = \left(\frac{K_{pll}}{\omega_0}\right)^2 = 0.883 \text{ ms}$

The pole is located at $f_p = \frac{\omega_p}{2\pi} = \frac{1}{2\pi \tau_p} = \frac{1}{2\pi \cdot 0.000883} = 180 \text{ Hz}$

$Q = \frac{1}{1 + \tau_z \cdot K_{pll}}$

$$\tau_z = \frac{\sqrt{C_1}}{2K_{pll}} = 19.87 \mu\text{s}$$

$V_{pd} \xrightarrow{862k\Omega} V_{lp} \xrightarrow{C_1 = 10nF} \text{LP-filter} \xrightarrow{1.99k\Omega} R_2 \rightarrow \text{Output}$

Choose $C_1 = 10 \text{ nF}$

$$R_2 = \frac{\tau_z}{C_1} = \frac{19.87 \cdot 10^{-6}}{10 \cdot 10^{-9}} = 1.99 \text{ k}\Omega$$

$$R_1 = \frac{\tau_p}{C_1} - R_2 = \frac{0.883 \text{ ms}}{10 \text{ nF}} - 1.99 \text{ k}\Omega = 88.3 \text{ k}\Omega - 1.99 \text{ k}\Omega = 86.3 \text{ k}\Omega$$

NIVERSITET
OSLO

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

 


Fig. 16.7 A phase-frequency sequential phase detector based on NAND gates.

UNIVERSITET
I OSLO