

# UNIVERSITY OF OSLO

## Faculty of Mathematics and Natural Sciences

**Exam in: INF9425 Projects in Analog / Mixed Signal CMOS Construction**

**Day of exam: Thursday, June the 3rd, 2010.**

**Exam hours: 14:30 – 17:30.**


**This examination paper consists of 5 pages.**

**Appendices: None.**

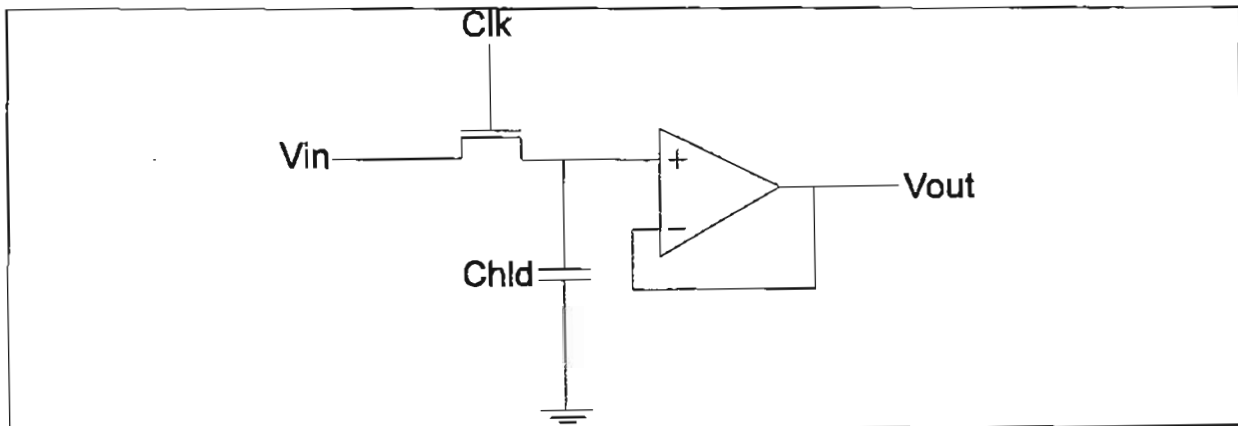**Permitted materials: Any written material and calculator.**

*Make sure that your copy of this examination paper is complete before answering.*

**Oppgave 1** (Problem 1 has a weight of 17 % out of the total exam.)




**1 a) (weight 6 %)**

Consider the Sample-and-Hold circuit above, with  $C_{OX} = 1.92 \text{ fF}/(\mu\text{m})^2$ ,  $V_m = 0.5 \text{ V}$ , and  $W/L = 2 \mu\text{m} / 0.5 \mu\text{m}$ , supply-voltages  $\pm 2.5 \text{ V}$  and the input signal varying between  $-0.5 \text{ V}$  and  $0.5 \text{ V}$ . The switch introduces a hold step. What is the minimum size of  $C_{hd}$  if the absolute value of the offset due to charge injection should be no larger than  $5 \text{ mV}$ ?

 **1 b) (weight 6 %)**

For the bandgap reference shown below, we have:  $V_{EB1-0} = 0.65 \text{ V}$ ,  $T = 300 \text{ K}$ ,  $I_t = 100 \mu\text{A}$ .  $\Delta V_{EB} = 59 \text{ mV}$ ,  $J_1 / J_2 = 10$ . Find the values of  $R_1$ ,  $R_2$  and  $R_3$ .



1 c) (weight 5 %)

Based on problem 1 b), what is the value of  $K$ ? You may make relevant assumptions based on "Johns & Martin".

**Problem 2** (Problem 2 has a weight of 21 % out of the total exam.)

2 a) (weight 6 %)

The following relationships are given for an SC-circuit with input voltage  $u_1$ , output voltage  $u_2$  and the capacitances  $C_1$  and  $C_2$ :

$$C_2 u_2[nT] = C_2 u_2[(n-1)T] - C_1 u_1[(n-1)T]$$

The signal at the input is sampled with the help of an ideal NMOS switch at time,  $t = (n-1)T$ . The clock signal for this switch is low at  $T = nT$ . Use the z-transform and write a transfer function for the circuit, in the z-plane.

2 b) (weight 10 %)


Given a SC-implementation of the following transfer function:

$$H(z) = U_2(z) / U_1(z) = (-C_1/C_2)(1/z-1)$$

Draw schematics for an SC-implementation of  $H(z)$ , as well as the similar RC-filter implementation.



2 c) (weight 5 %)

 Consider the illustration below, providing a relation between dynamic range and oversampling rate for an oversampling data converter. Which order,  $N$ , ( $N$  is a natural number) of the converter is probably belonging to the illustration. Explain your answer.



 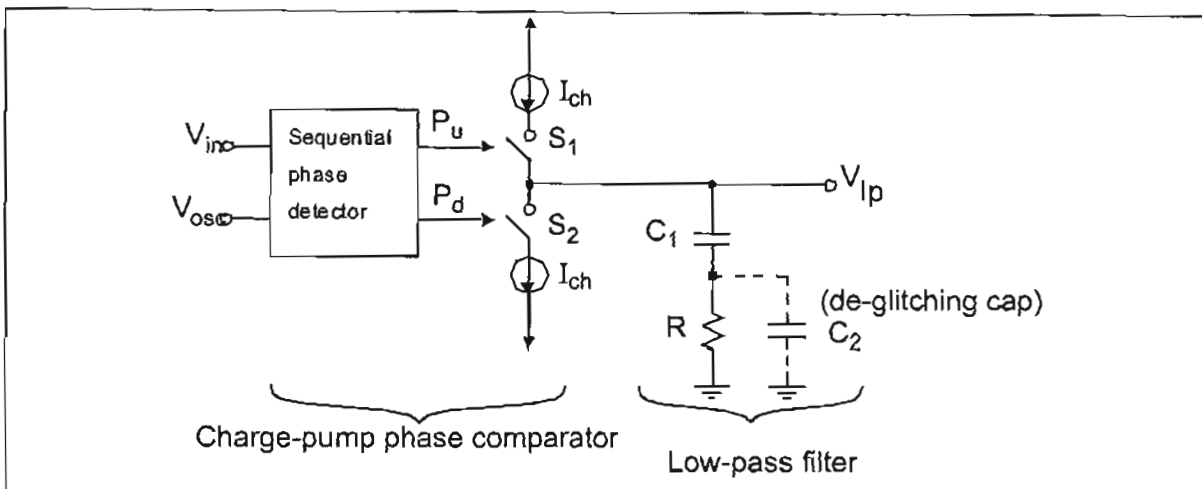**Problem 3** (Problem 1 has a weight of 26 % out of the total exam.)

Depicted below is a charge-pump phase comparator as well as some typical related waveforms.



**3 a)** (weight 10%)

Consider the information from the combination of the schematics and the waveforms and explain what is going on in the charge-pump phase comparator.

**3 b) ( weight 8 %)**

Assume that the loop have a time constant of 100 cycles, or  $2 \mu\text{s}$ , and that the free-running frequency of the oscillator is 50 MHz. Let  $K_{osc} = 2\pi \times 50 \text{ Mrad/s}$  and  $I_{ch} = 10 \mu\text{A}$ .  $C_2 = 0$ . A maximally flat group delay is desired. Design the components of the LP-filter.


**3 c) ( weight 8 %)**

Consider another case, wher the time,  $\Delta\phi_{in}$ , is  $0.1 \mu\text{s}$ ,  $I_{ch} = 1 \mu\text{A}$  and  $C_2 = 0$ . What is the maximum change in the voltage across the capacitor,  $C_1$ , during  $\Delta\phi_{in}$ , given that  $C_1 = 2 \text{ nF}$ ?

**Problem 4** (Problem 4 has a weight of 26 % out of the total exam.)

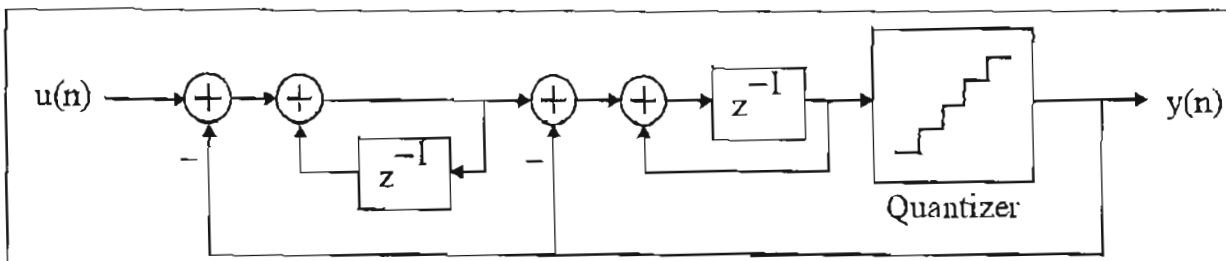**4 a) (weight 10 %)**

Below you find a description of a  $\Delta\Sigma$  modulator. Show how you can develop an expression for  $P_e$  (quantization noise power) for this topology, based on the formula below, ond relevant assumptions from "Johns & Martin".



$$P_e = \int_{f_0}^{f_0} S_e^2(f) |N_{TF}(f)|^2 df$$

**4 b) (weight 8 %)**

Show how you may develop an expression for  $\text{SNR}_{\text{max}}$ , based on a) and  $P_s = (\Delta^2 2^{2N}) / 8$ . Explain what normally happens to a  $\text{SNR}_{\text{max}}$  when the oversampling rate is doubled, in this case? Explain.

**4 c) (weight 8 %)**

Our mathematical expression for  $\text{SNR}_{\text{max}}$  for this oversampling converter does not provide an upper limit for the sampling rate ("OSR"). How would this be for a practical implementation in CMOS? Explain.

**Problem 5** (weight 10 %)

For a given power budget, performance may drop when migrating to newer technologies. This can complicate analog design. Could you please explain?

In the previous problem a part of an oversampling converter was shown. Could you say something about oversampling converters and how they are affected by technology scaling, when compared to Nyquist converters?

*Good luck!*