

UiO : **Department of Informatics**
University of Oslo

INF4420
Analog to Digital Converters

Jørgen Andreas Michaelsen
Spring 2013



1 / 34

UiO : **Department of Informatics**
University of Oslo

Outline

Overview of architectures for implementing analog
to digital conversion

Spring 2013

Analog to Digital Converters

2

2 / 34

Introduction

ADCs are used in numerous applications with differing requirements on speed, accuracy, and energy efficiency.


ADC architectures have different strengths and weaknesses with respect to these trade offs. It is therefore important to understand not only how each converter works, but also its limitations and key aspects for performance.

Numerous architectures

- Flash
- Interpolating
- Folding
- Interleaved
- Successive approximation
- Algorithmic
- Pipelined
- Two-step
- Integrating

Flash ADC

- The Kelvin divider is used to generate 2^N reference voltages
- Comparators compare the sample and held inputs to each derived reference voltage
- Thermometer output decoded to binary

 

Spring 2013

Analog to Digital Converters

5

5 / 34

Flash ADC considerations

- Fast: conversion is done in parallel
- Large number of comparators: power and area. Limits the practical number of bits.
- S&H output must drive all 2^N comparator inputs. Large capacitive load. Drives up power requirement for S&H. Must also be fast.
- Comparator input current results in errors in the derived reference voltages, "resistor-string bowing"

Spring 2013

Analog to Digital Converters

6

6 / 34

Flash ADC considerations

- Substrate and power supply noise: shielded (differential) clocks and separate analog supply to the comparator preamp. Bypass capacitors.
- Comparator errors such as metastability, noise, crosstalk, bandwidth, etc. cause “bubbles” in the thermometer code near the transition point. Thermometer decoder must take this into account.
- Comparator kickback noise.

Spring 2013

Analog to Digital Converters


7

7 / 34

Interpolating ADC

Similar to the flash ADC but comparator preamps are shared, and less derived reference voltages are needed. Less loading on the input.

Latches will see different delays. Can be compensated by adding resistance to latches close to the preamp.

 

Spring 2013


Analog to Digital Converters

8


8 / 34

Folding ADC

 Preprocess the input to compress the signal range and decide the MSBs. Often used with interpolating ADCs.



Difficult to implement the folding circuit.

 

Spring 2013

Analog to Digital Converters

9

9 / 34

Time-interleaved ADC

- Flash converters are fast (conversion in parallel)
- Still, there is a limit to how fast we can make the comparators
- Techniques considered so far have focused on how we can reduce hardware complexity (avoiding 2^N full comparators)
- We can make ADCs even faster by running multiple flash ADCs in parallel—time interleaved

Spring 2013

Analog to Digital Converters

10

10 / 34

Time-interleaved ADC

Example:

Monolithic
40 Gs/s
ADC in an
SiGe
process



http://www.lecroy.com/tm/Library/WhitePapers/PDF/DBI_Explained.pdf

Spring 2013

Analog to Digital Converters

11


11 / 34

Time-interleaved ADC

Technique to increase the sampling rate by interleaving.

Run N ADCs in parallel.
Requires fast S/H

Offset and gain mismatch
between channels and
clock misalignment

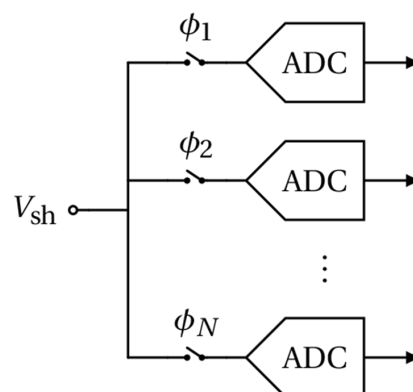

Spring 2013


Analog to Digital Converters

12

12 / 34

Time-interleaved ADC

Digital correction of gain and offset

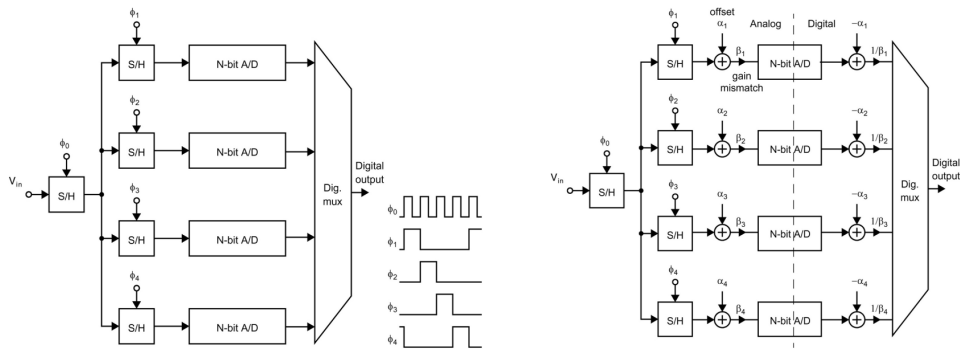

Spring 2013

Analog to Digital Converters

13

13 / 34

Two-step ADC



A system of two ADCs and one DAC. First ADC resolves the MSBs, M bits, and the second ADC resolves the LSBs, N bits. $2^N + 2^M$ comparators (if flash is used), rather than 2^{N+M} .

The MSB ADC must be accurate to $M + N$ bits.


Spring 2013

Analog to Digital Converters


14

14 / 34

Two-step ADC

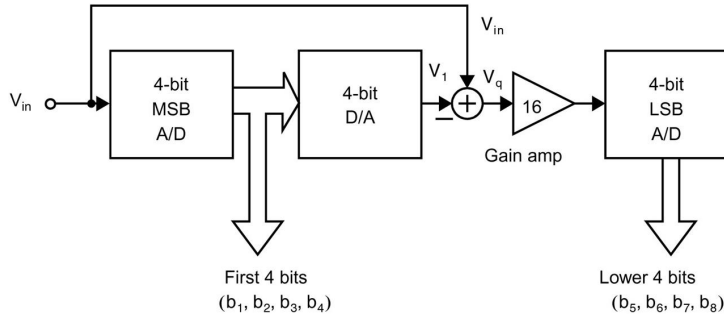

The residue is multiplied by 16 to scale it to a more practical range for the LSB ADC.

 

Spring 2013


Analog to Digital Converters

15

15 / 34

Two-step ADC error correction

Relax the accuracy requirement for the MSB ADC by overlapping the ranges of the ADCs.

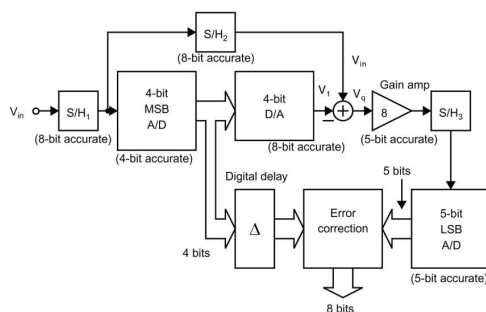

Spring 2013



Analog to Digital Converters

16

16 / 34

Pipelined ADC

Rather than using two ADC in sequence (two-step), we can use many.

  

Spring 2013


Analog to Digital Converters

17

17 / 34

Pipelined ADC

Outputs a sample every clock cycle but the *latency* is N (number of stages = number of bits assuming 1 bit per stage).

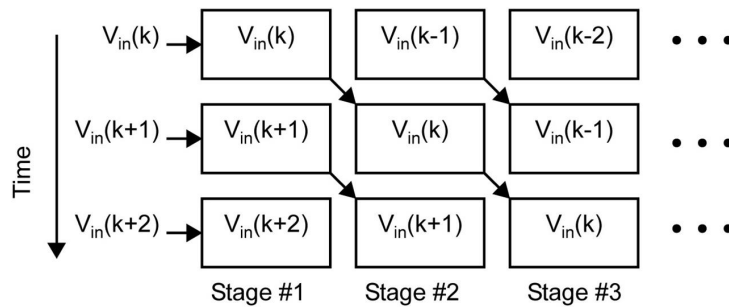


Spring 2013

Analog to Digital Converters

18


18 / 34

Pipelined ADC

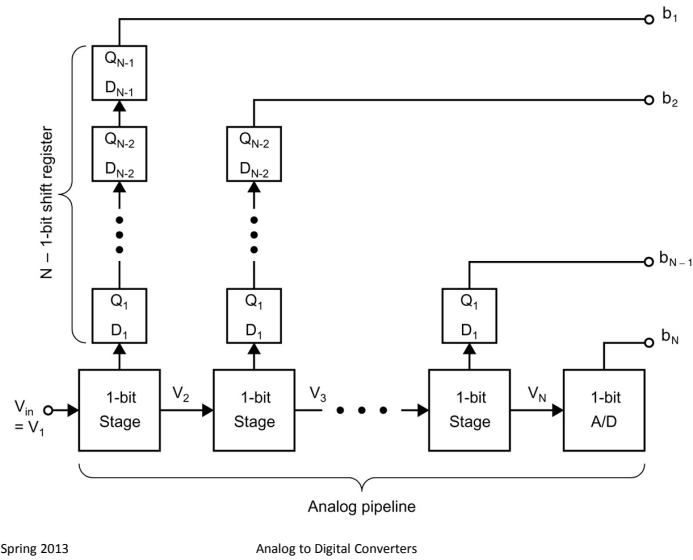

19 / 34

Pipelined ADC

 

Error free			Offset in second stage (30 mV)		
	b_i	residue		b_i	residue
$V_1 = V_{in}$	1	-20 mV	$V_1 = V_{in}$	1	-20 mV
V_2	0	460 mV	V_2	1	-540 mV
V_3	1	420 mV	V_3	0	-580 mV

Bipolar input, $V_{in} = 240 \text{ mV}$, $V_{ref} = 1 \text{ V}$, three stages (3 bit)
Quantized output 187.5 mV vs 312.5 mV (error is 52.5 mV vs 72.5 mV)

20 / 34

Pipelined ADC

The signal is gained up by each stage → First stage must be the most accurate. Accuracy requirement relaxed by $\times 2$ (input referred)

We can relax the offset accuracy requirements by adding redundancy, two comparators per stage, 1.5 bit, rather than one. Need more logic to decode the output value

Pipelined ADC


1.5 bit gives three possible output values from the DAC, $\left\{-\frac{V_{ref}}{4}, 0, \frac{V_{ref}}{4}\right\}$, rather than $\left\{-\frac{V_{ref}}{4}, \frac{V_{ref}}{4}\right\}$. The two LSBs are determined by a 2 bit ADC. The final equivalent quantized input voltage is

$$\widehat{V}_{in} = \frac{V_{ref}}{2} \left(\sum_{i=1}^{N-2} (b_{i,1} + b_{i,0} - 1) \cdot 2^{-i} + B_{N-1,1} \cdot 2^{N-2} + B_{N-1,0} \cdot 2^{N-1} \right)$$

Decoder must do this addition

Pipelined ADC

Random comparator offset, ε_0 and ε_1 is canceled if less than $V_{ref}/4$. Residue remains within $\pm V_{ref}/2$.

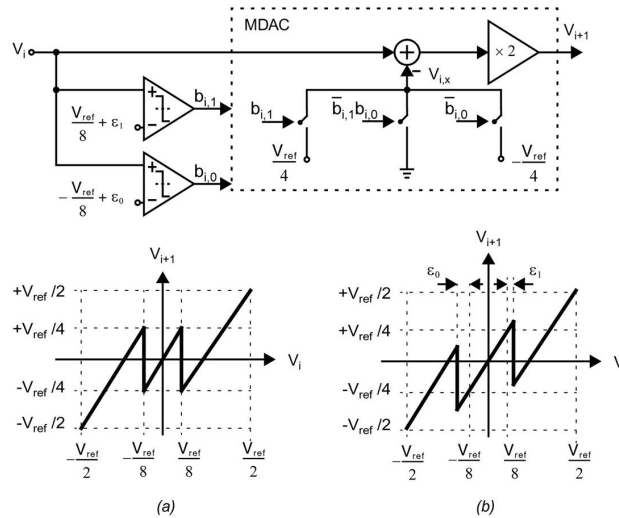

Spring 2013

Analog to Digital Converters

23

23 / 34

Pipelined ADC

Inaccuracy and noise in the DAC and gain circuit appear in the residue and is not canceled by the digital correction. Limits performance. Mismatch and noise in the first stage is most significant (more area, power).

Spring 2013

Analog to Digital Converters


24

24 / 34

Pipelined ADC

Generally, we can have k bit per stage. Two stages equivalent to a two-step ADC.

More bits per stage gives less latency

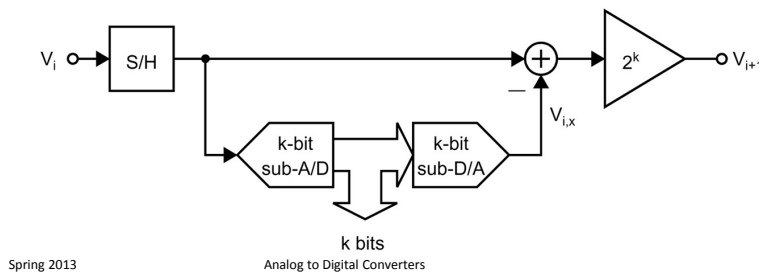

Spring 2013


Analog to Digital Converters

25

25 / 34

Algorithmic ADC

Instead of cascading multiple stages in hardware, like the pipelined ADC, the same stage can be reused. However, each conversion takes N clock cycles.

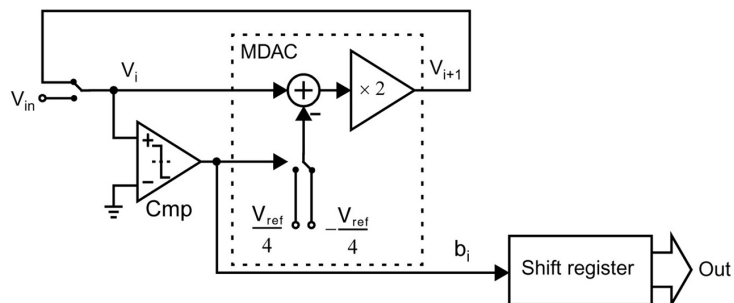

Spring 2013


Analog to Digital Converters

26

26 / 34

SAR ADC

The successive approximation register (SAR) tests each bit sequentially (MSB first, one clock period per bit), and decides whether to keep the bit or not based on the comparator's output.

 

Spring 2013


Analog to Digital Converters

27

27 / 34

SAR ADC

Loop through N bits
in N clock cycles.
Binary search for the
digital word (quantized
representation) that
is the closest match to
the input voltage.
MSB determined first.

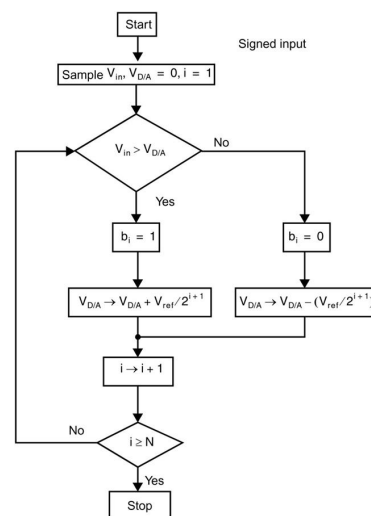

Spring 2013

Analog to Digital Converters

28


28 / 34

Charge redistribution SAR ADC

SAR ADCs are the most energy efficient ADCs (in terms of FoM).

Limited in resolution by capacitor matching (~ 10 bits).

 1. Sample mode
2. Hold mode
3. Bit cycling



- Inherent S/H function.
- Auto zero of the comparator is optional

Spring 2013

Analog to Digital Converters


29

29 / 34

Charge redistribution SAR ADC

No amplifiers needed (except for the comparator preamp). Saves power.

Comparator and charging of the capacitive array determines power consumption.

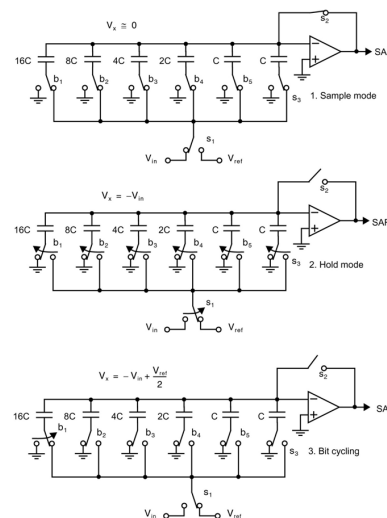

Spring 2013

Analog to Digital Converters

30


30 / 34

Charge redistribution SAR ADC speed

Speed limitation due to the RC time constant of the capacitor array and switches. $T > 0.69(N + 1)\tau_{eq}$

τ_{eq} estimated from zero value time constant.

Charging time, T , assuming better than $1/2$ LSB.

 

Spring 2013

Analog to Digital Converters

31

31 / 34

Charge redistribution SAR ADC

Error correction systems can be used to extend the resolution beyond the ~ 10 bit set by capacitor matching. Example in the textbook, fig. 17.11

We have considered SAR ADCs that determine one bit per clock cycle. To speed up, could consider converters that determine more than one bit per clock cycle.

Spring 2013


Analog to Digital Converters

32

32 / 34

Integrating ADC

High accuracy, but low speed.

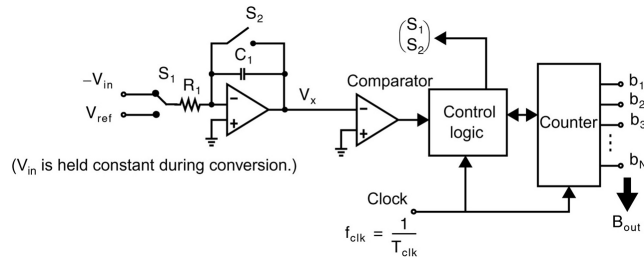

Phase I: Integrate V_{in} for a fixed amount of time

Phase II: Measure the time it takes to discharge the integrator to zero with a fixed voltage

Integrating ADC

Phase I lasts for $T_1 = 2^N \cdot T_{clk}$, counter value when phase II completes is the digital output.

Output word does not depend on RC .

