

INF1400- Uke 04

1. Regn ut følgende subtraksjon
 - a. $00001000 - 00000011$
 - b. $00001100 - 11110111$
 - c. $11100111 - 00010011$
 - d. $10001000 - 11100010$
2. Design a combinational circuit that adds one to a 4-bit binary number. For example, if the input of the circuit is 1101, the output is 1110. (HINT! The circuit can be designed using four half-adders)
3. A combinational circuit produces the binary sum of two 2-bit numbers, x_1x_0 and y_1y_0 . The outputs are C, S1, and S0. Provide a truth table of the combinational circuit.
4. Design a circuit for the above problem using two full-adders.
5. (VANSKELIG) Consider the 3-bit, 2-complement conversion below and implement it using full-adders

| A_2 | A_1 | A_0 | D_2 | D_1 | D_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |

6. Now implement the inverse operation, i.e. one that takes D_2, D_1, D_0 and produces the output (A_2, A_1, A_0) . (HINT! Remember how to perform subtraction using 2-complements)
7. Løs oppgaver i slutten av kapittel 4.