
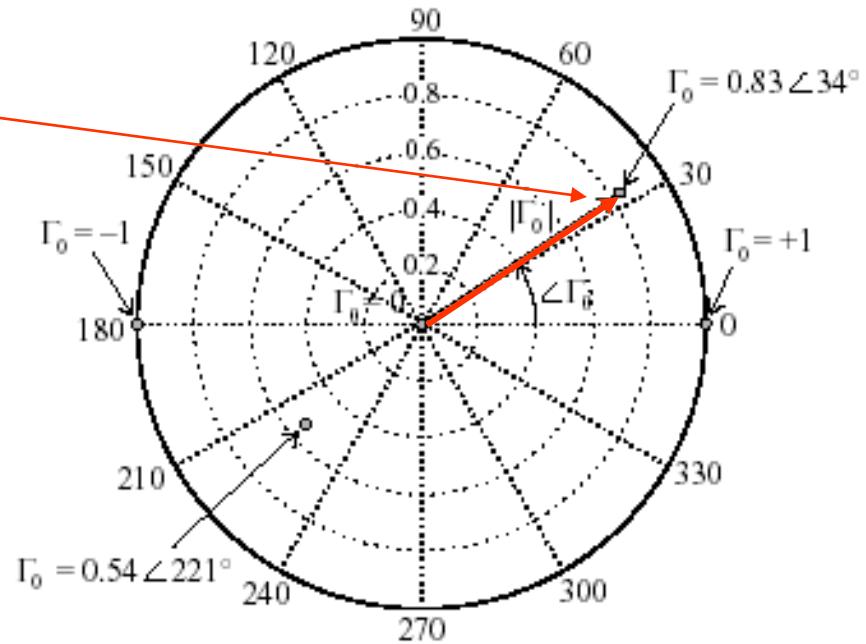



Ch. 3. The Smith Chart

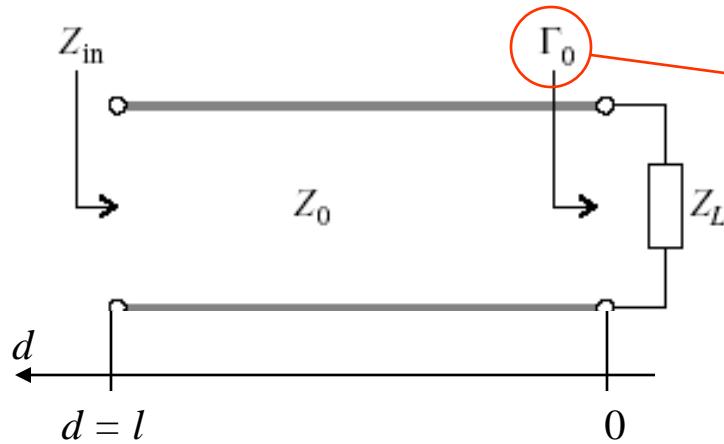

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_{0r} + j\Gamma_{0i} = |\Gamma_0| e^{j\theta_l}$$

Mapping of the reflection coefficient in the complex domain

Normalized impedance

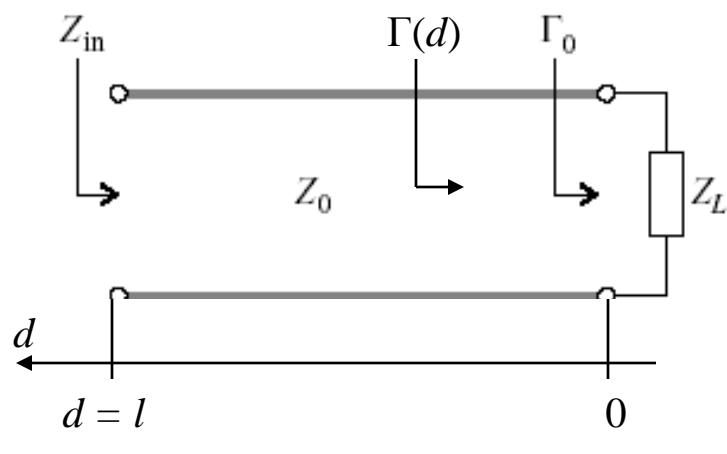

Generalized reflection coefficient:

$$\Gamma(d) = \Gamma_0 e^{-2j\beta d} = \Gamma_r + j\Gamma_i$$

Normalized impedance:

$$\frac{Z_{in}(d)}{Z_0} = z_{in} = r + jx = \frac{1 + \Gamma(d)}{1 - \Gamma(d)} = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i}$$

Real part:

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$\Rightarrow \left(\Gamma_r - \frac{r}{r+1} \right)^2 + \Gamma_i^2 = \left(\frac{1}{r+1} \right)^2$$

Imaginary part:

$$x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$\Rightarrow (\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x} \right)^2 = \left(\frac{1}{x} \right)^2$$

Representation of normalized resistance


$$\left(\Gamma_r - \frac{r}{r+1} \right)^2 + \Gamma_i^2 = \left(\frac{1}{r+1} \right)^2$$

Examples:

$$r = 0 \Rightarrow \Gamma_r^2 + \Gamma_i^2 = 1$$

$$r = 1 \Rightarrow \left(\Gamma_r - \frac{1}{2} \right)^2 + \Gamma_i^2 = \left(\frac{1}{2} \right)^2$$
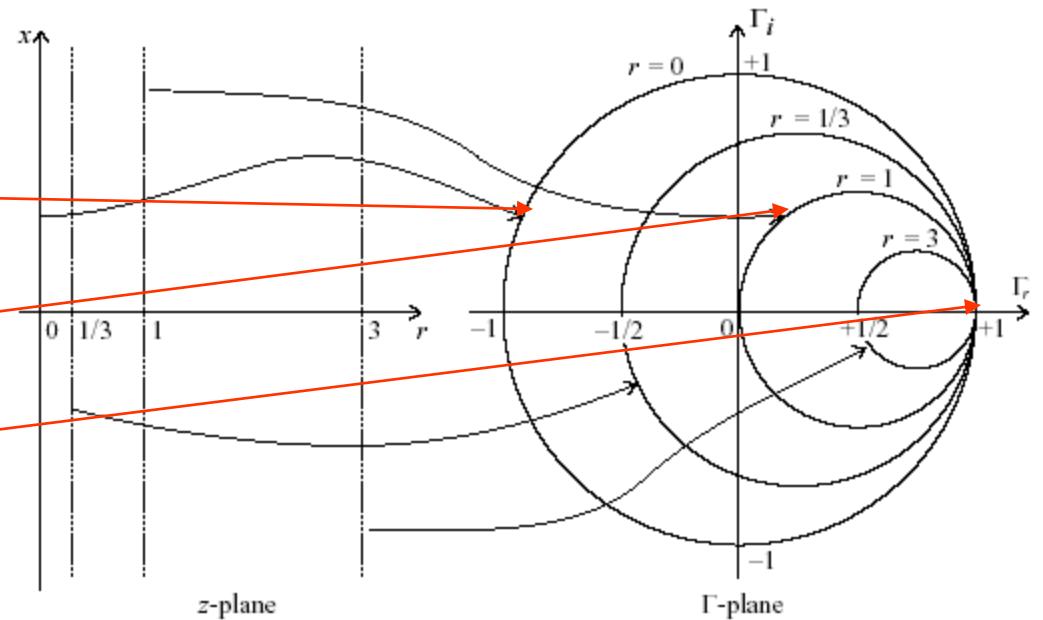
$$r = \infty \Rightarrow (\Gamma_r - 1)^2 + \Gamma_i^2 = 0$$



Representation of normalized reactance

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

Examples:


$$x = \infty \Rightarrow (\Gamma_r - 1)^2 + \Gamma_i^2 = 0$$

$$x = 1 \Rightarrow (\Gamma_r - 1)^2 + (\Gamma_i - 1)^2 = 1$$


$$x = 0 \Rightarrow \Gamma_i = 0$$

$$x = -1 \Rightarrow (\Gamma_r - 1)^2 + (\Gamma_i + 1)^2 = 1$$

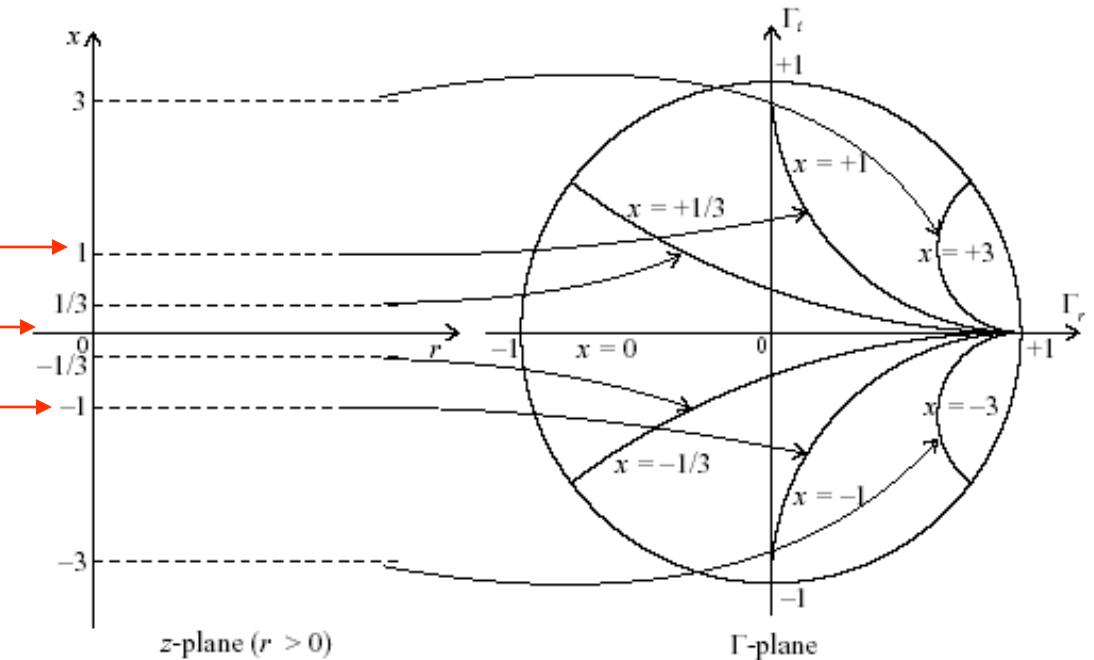
$$x = -\infty \Rightarrow (\Gamma_r - 1)^2 + \Gamma_i^2 = 0$$



Combined diagram: Smith Chart

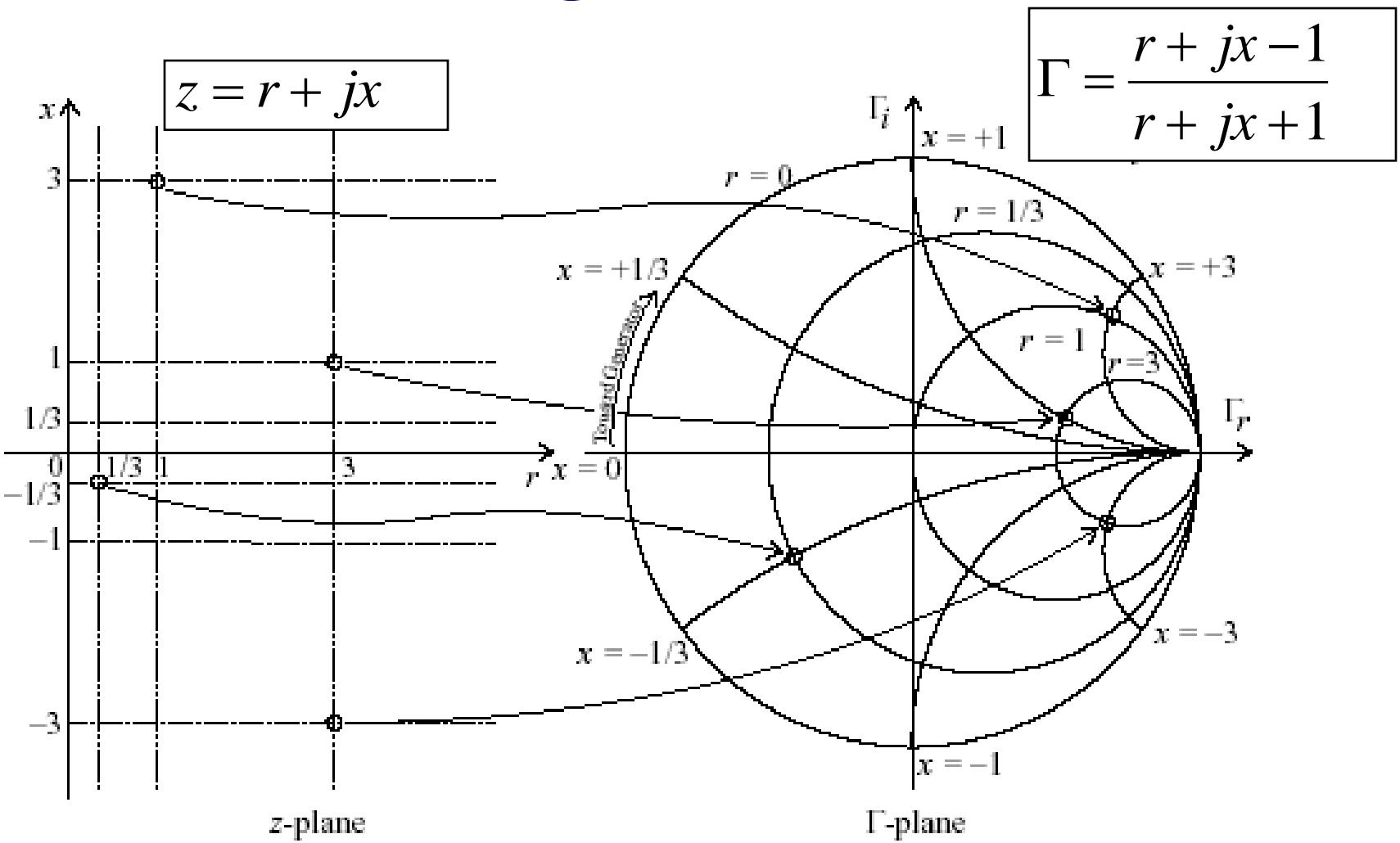

Repetition

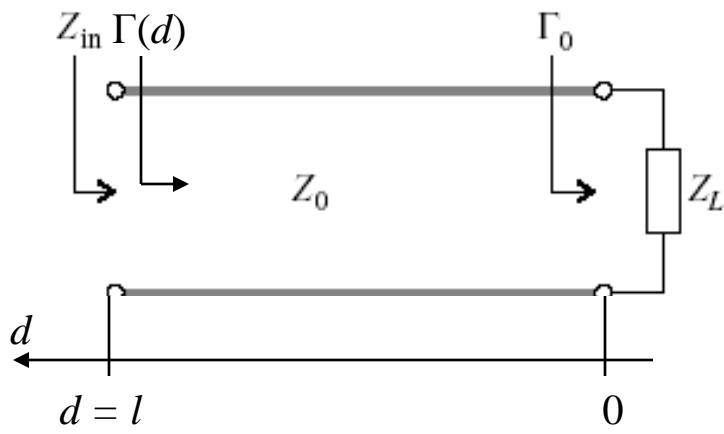

Reflection coefficient:

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_{0r} + j\Gamma_{0i} = |\Gamma_0| e^{j\theta_l}$$

Generalized reflection coefficient:

$$\Gamma(d) = \Gamma_0 e^{-2j\beta d} = \Gamma_r + j\Gamma_i$$


Normalized impedance: $\frac{Z_{in}(d)}{Z_0} = z_{in} = r + jx = \frac{1 + \Gamma(d)}{1 - \Gamma(d)} = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i}$

Normalized resistance: $r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$

Normalized reactance: $x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$

How to use the Smith Chart

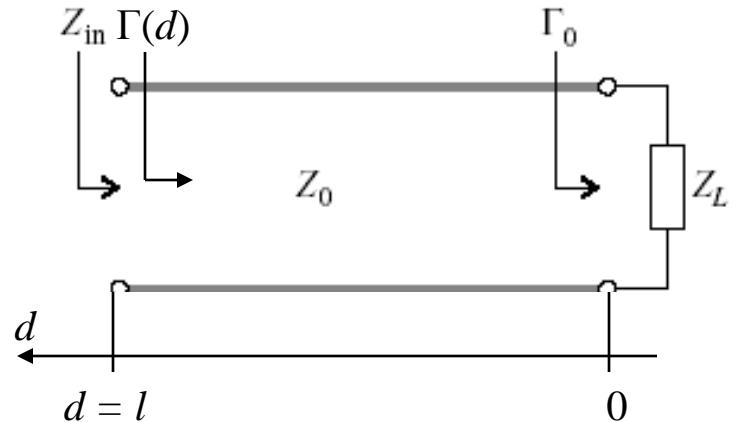*Example: determine
input impedance $Z_{in}(d)$*



- Normalize load impedance: $Z_L \rightarrow z_L$
- find reflection coefficient: $z_L \rightarrow \Gamma_0$
- rotate reflection coefficient: $\Gamma_0 \rightarrow \Gamma(d)$
- find normalized input impedance: $z_{in}(d)$
- de-normalize input impedance: $z_{in}(d) \rightarrow Z_{in}(d)$

Impedance transformation using Smith chart

1) Normalize load impedance:

$$Z_L \rightarrow z_L = Z_L/Z_0$$

2) Find reflection coefficient:

$$z_L \rightarrow \Gamma_0 = (z_L - 1)/(z_L + 1)$$

3) Rotate reflection coefficient:

$$\Gamma_0 \rightarrow \Gamma(d) = \Gamma_0 \exp(-j2\beta d)$$


4) Find normalized input impedance:

$$\Gamma(d) \rightarrow z_{in}(d) = (1 + \Gamma(d))/(1 - \Gamma(d))$$

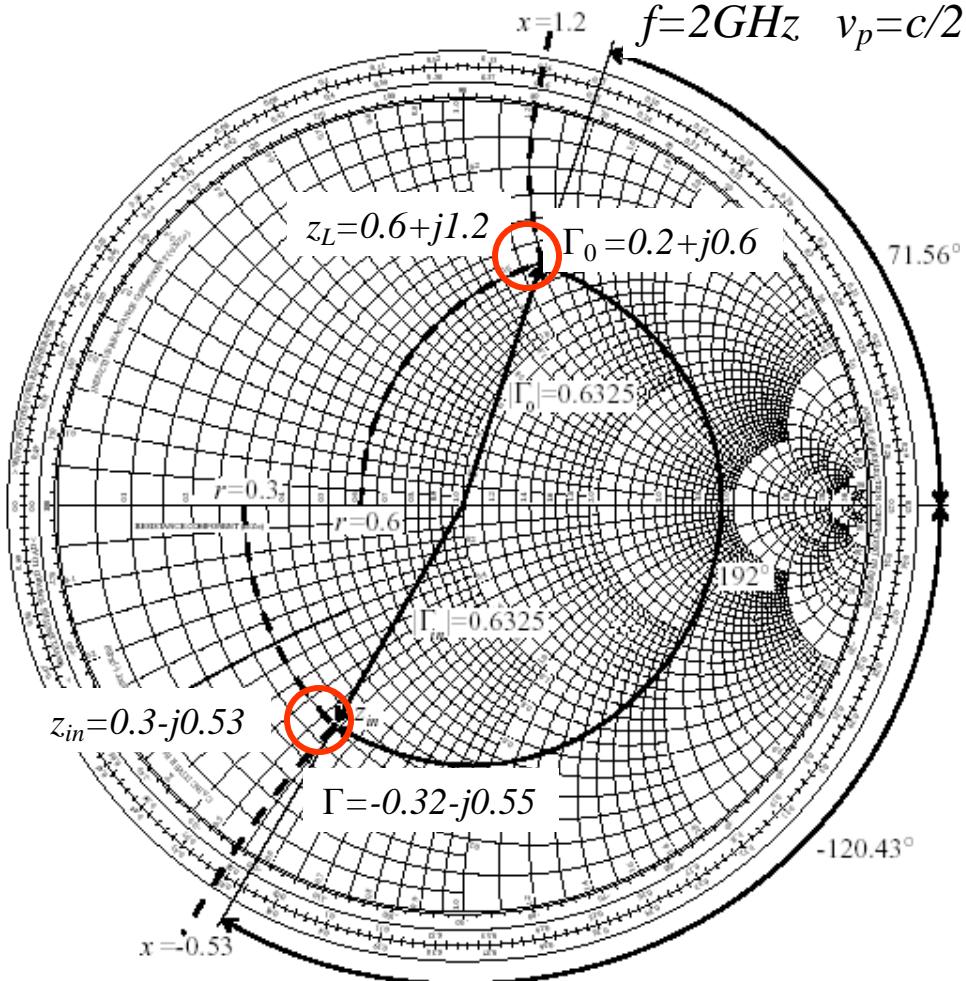5) De-normalize input impedance:

$$z_{in}(d) \rightarrow Z_{in}(d) = Z_0 z_{in}(d)$$

$$\begin{aligned} Z_L &= 30+j60 \Omega \\ Z_0 &= 50 \Omega \\ d &= l = 2 \text{ cm} \\ f &= 2 \text{ GHz} \quad v_p = c/2 \end{aligned}$$




Generalized standing wave ratio

$$\Gamma(d) = \Gamma_0 e^{-j2\beta d}$$

$$SWR(d) = \frac{1 + |\Gamma(d)|}{1 - |\Gamma(d)|}$$

$$\Rightarrow |\Gamma(d)| = \frac{SWR - 1}{SWR + 1}$$

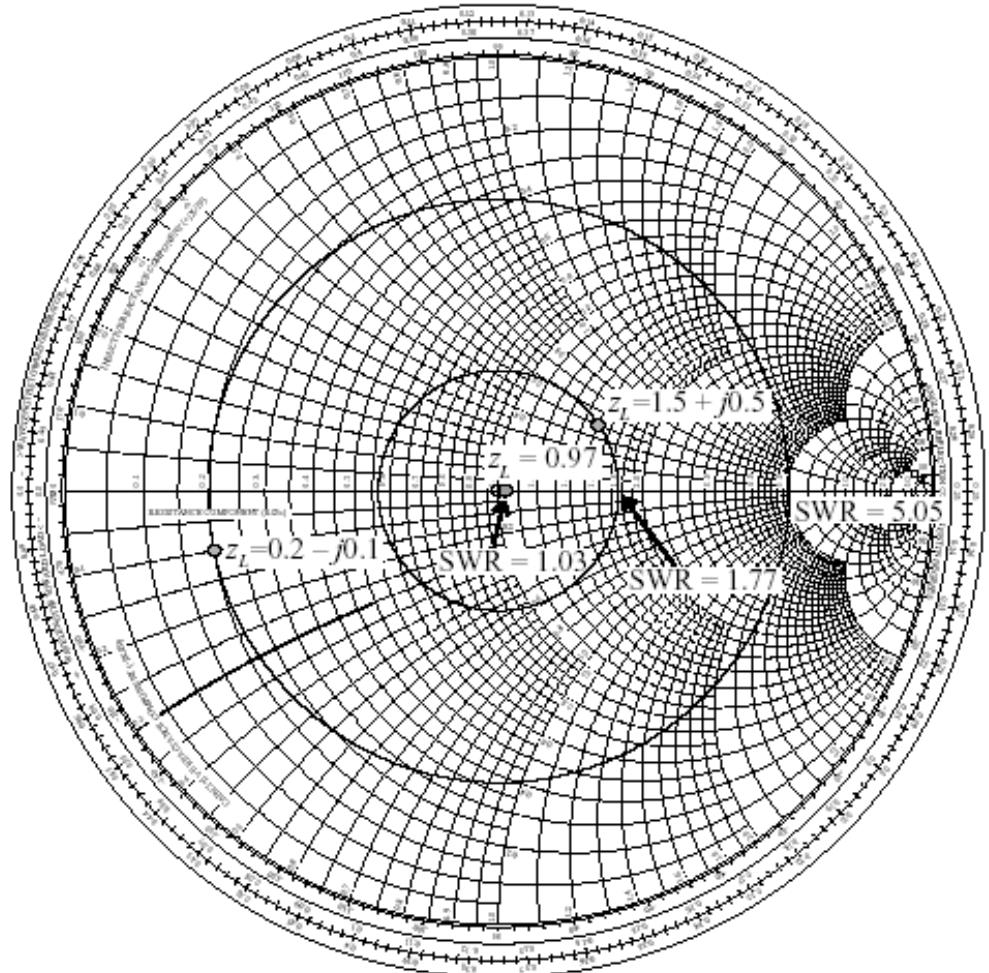Can determine SRW for a given $\Gamma(d)$ by drawing circle with center at $\Gamma = 0$ through $\Gamma(d)$ in the Smith chart.



Open circuit TL as a reactive element


$$z_{in} = \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \rightarrow -j \cot(\beta d)$$

Note: $Z_L = \infty$ corresponds to $r = 0$
 (outer circle of Smith chart)

Upper half-circle: **inductive**
 Lower half-circle: **capacitive**

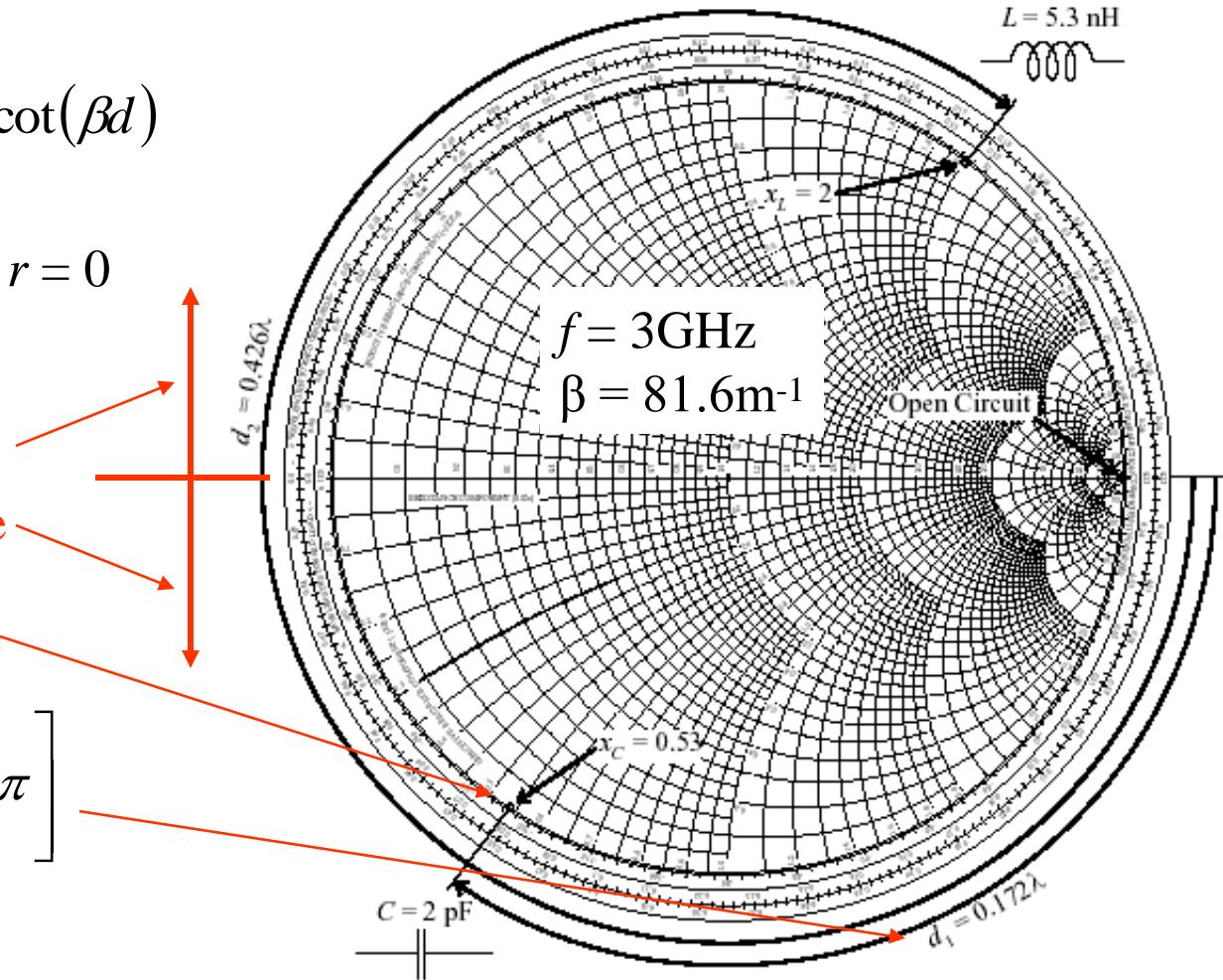Example: $z_{in} = jx = 1/j\omega CZ_0$

$$\Rightarrow d = \frac{1}{\beta} \left[\cot^{-1} \left(\frac{1}{\omega CZ_0} \right) + n\pi \right]$$



Short circuit TL as a reactive element


$$z_{in} = \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \rightarrow j \tan(\beta d)$$

Note: $Z_L = 0$ also corresponds to $r = 0$ (outer circle of Smith chart)

Upper half-circle: **inductive**
Lower half-circle: **capacitive**

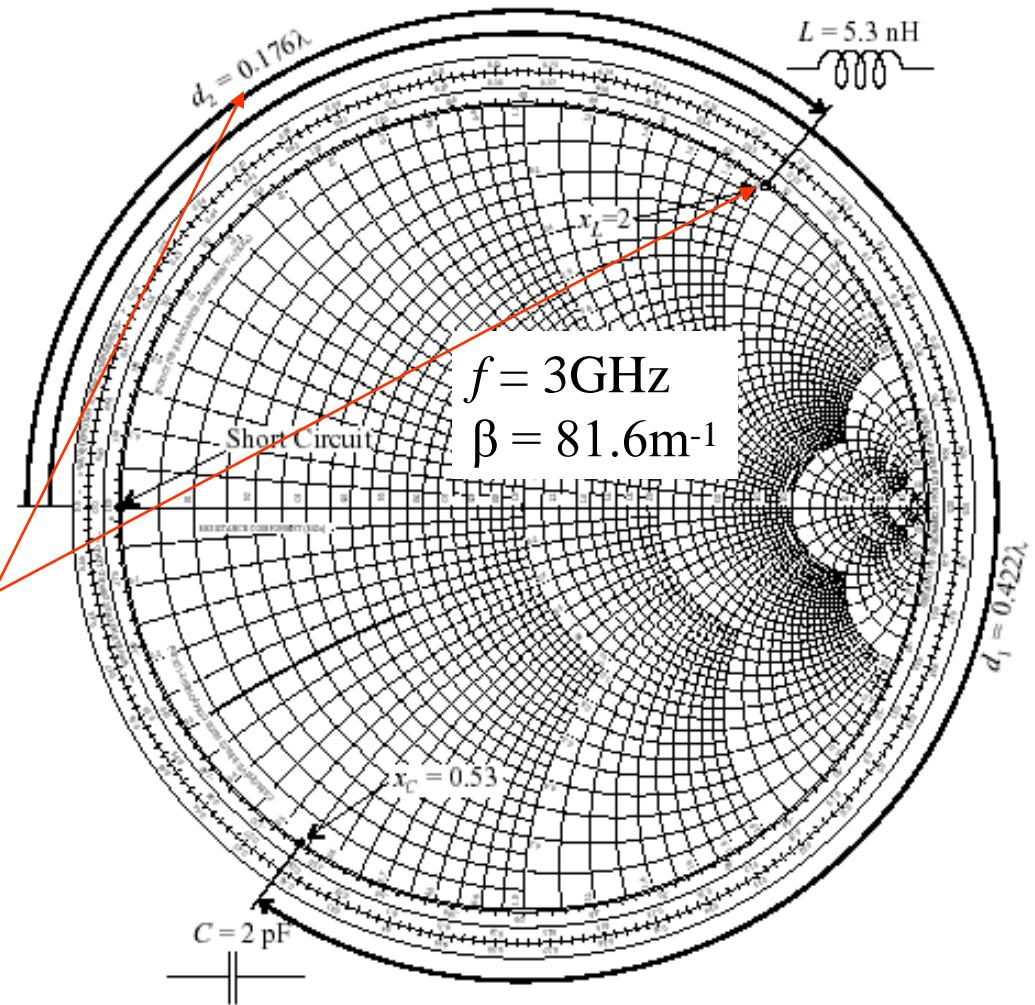Example: $z_{in} = jx = j\omega L/Z_0$

$$\Rightarrow d = \frac{1}{\beta} \left[\tan^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$




Admittance transformation

$$Y_{in} = \frac{1}{Z_{in}} = \frac{1}{Z_0} \frac{1-\Gamma(d)}{1+\Gamma(d)}$$


$$y_{in} = \frac{1}{z_{in}} = \frac{1-\Gamma(d)}{1+\Gamma(d)} = \frac{1+e^{-j\pi}\Gamma(d)}{1-e^{-j\pi}\Gamma(d)}$$

$e^{-j\pi}\Gamma(d)$ corresponds to 180° rotation of $\Gamma(d)$ in Smith chart.
This converts impedance to admittance

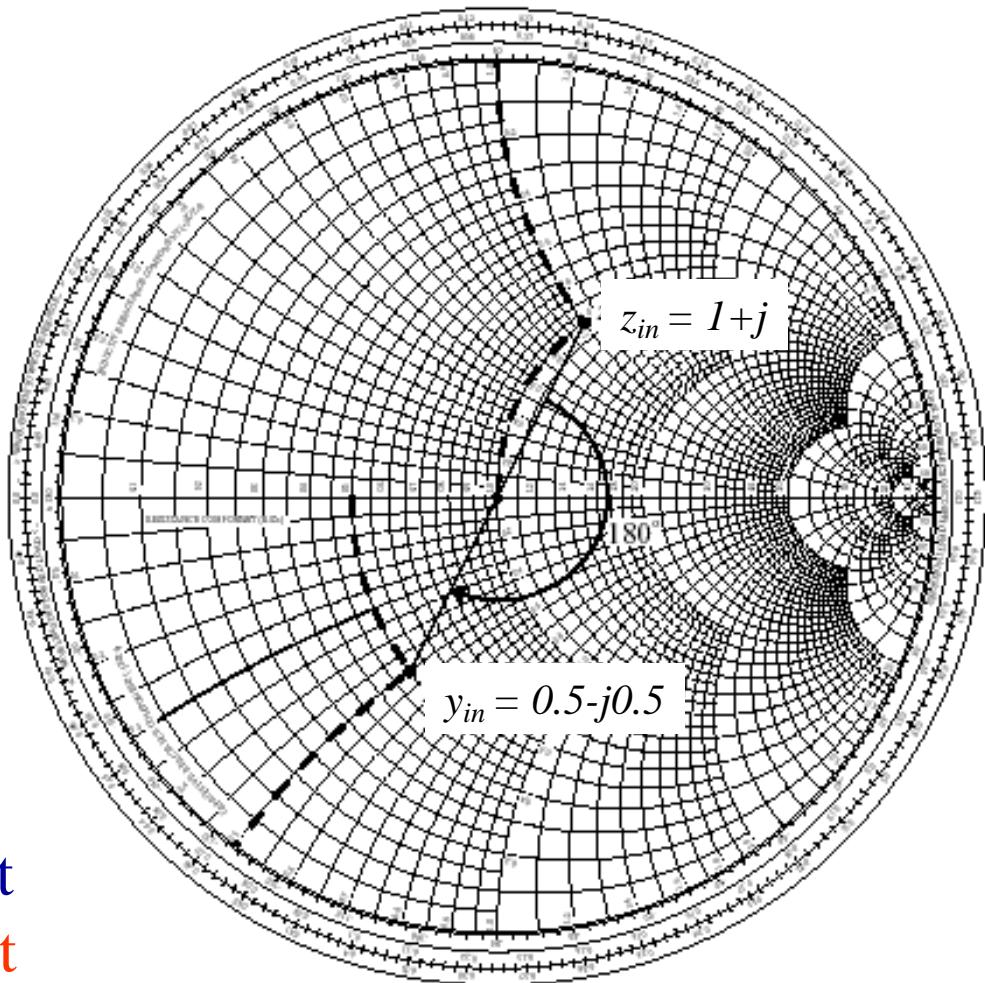
Alternatively: Rotate Smith chart by 180° : Admittance Smith chart



Admittance Smith chart

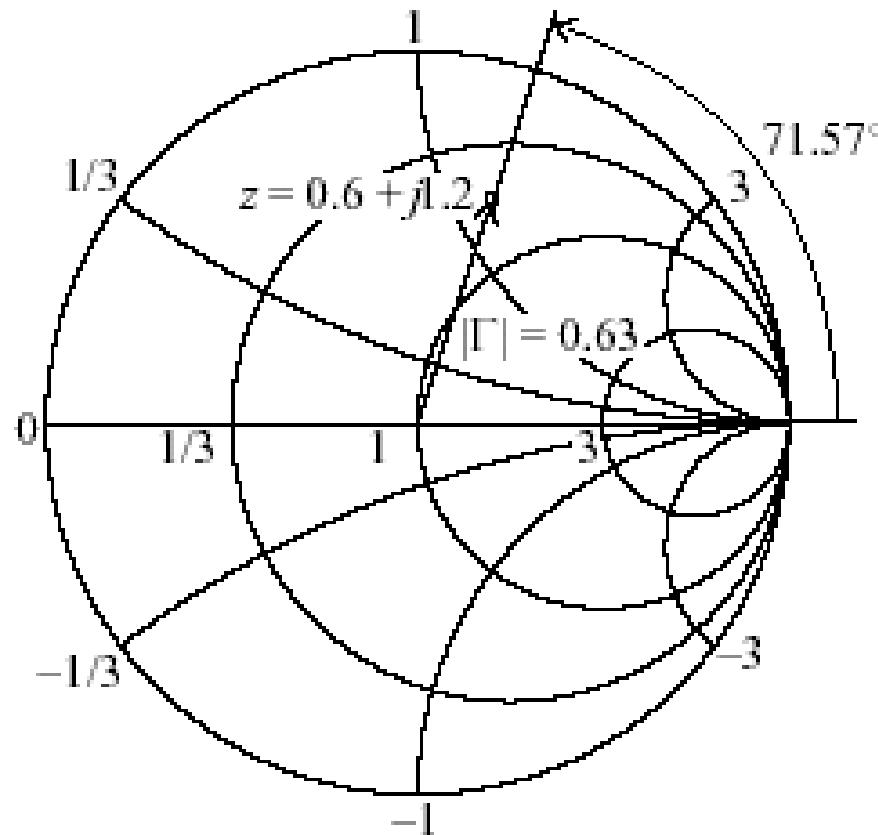

(a) Z -Smith Chart

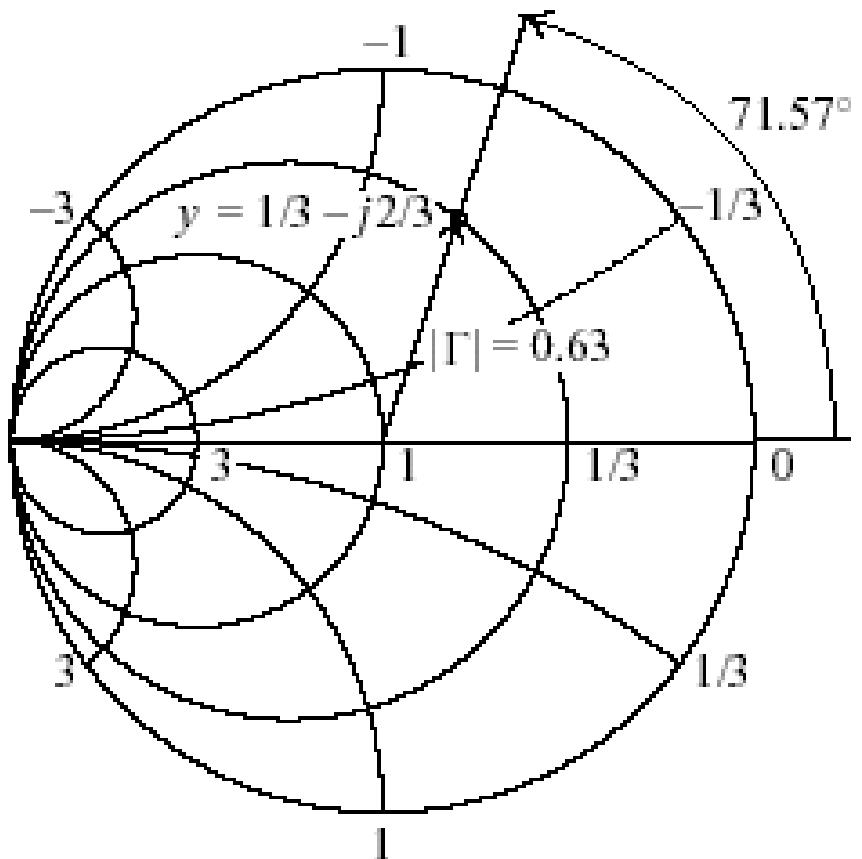


(b) Y -Smith Chart

ZY Smith chart

$$y_{in} = g + jb = \frac{1}{z_{in}} = \frac{1}{r + jx}$$

$$\Rightarrow g = \frac{r}{r^2 + x^2}, \quad b = \frac{-x}{r^2 + x^2}$$

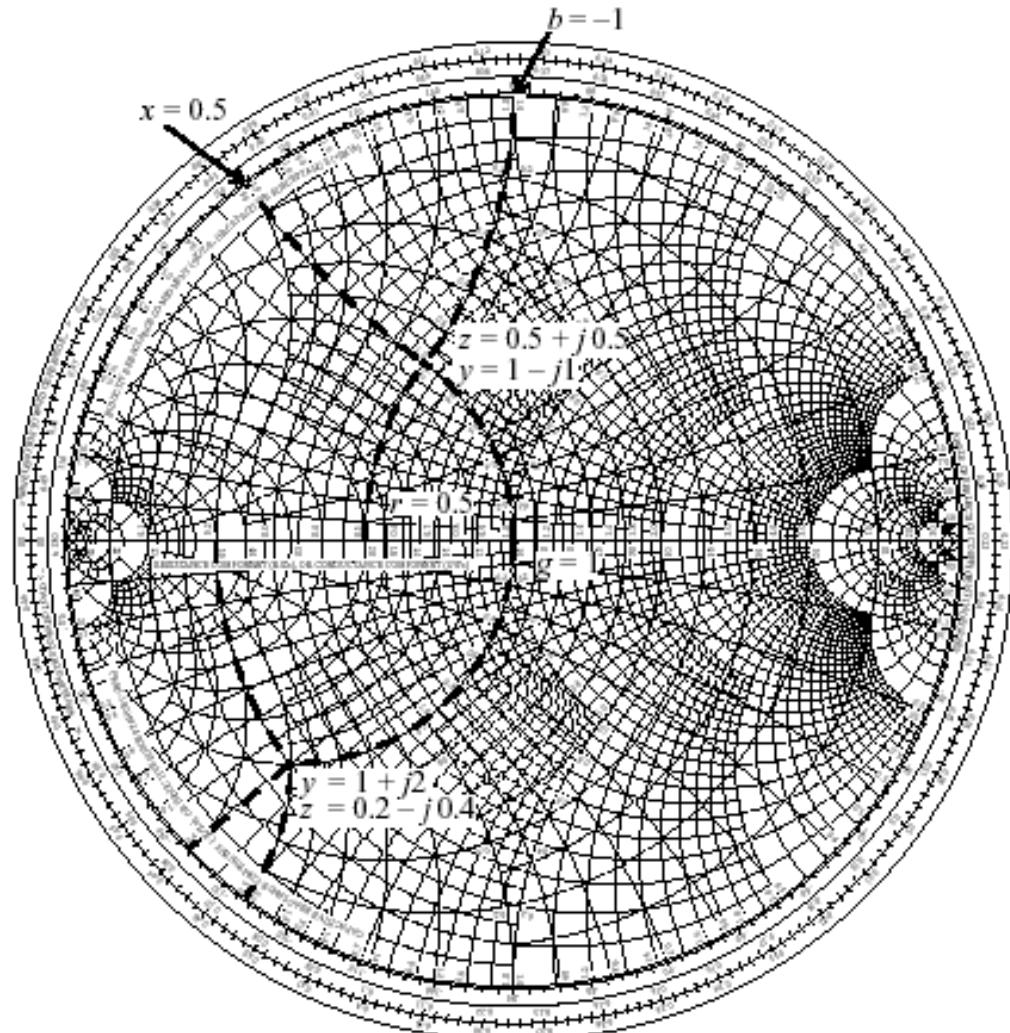Use original **Smith chart** to display **impedances** and **rotated chart** to display **admittances**.



Frequency dependence: parallel R and L


$$y_{in} = g + jb = \frac{Z_o}{R} - j \frac{Z_o}{\omega L}$$

Example:

$$Z_0 = 50 \Omega, L = 10 \text{ nH}$$

$$g = 0.3, 0.5, 0.7, 1$$
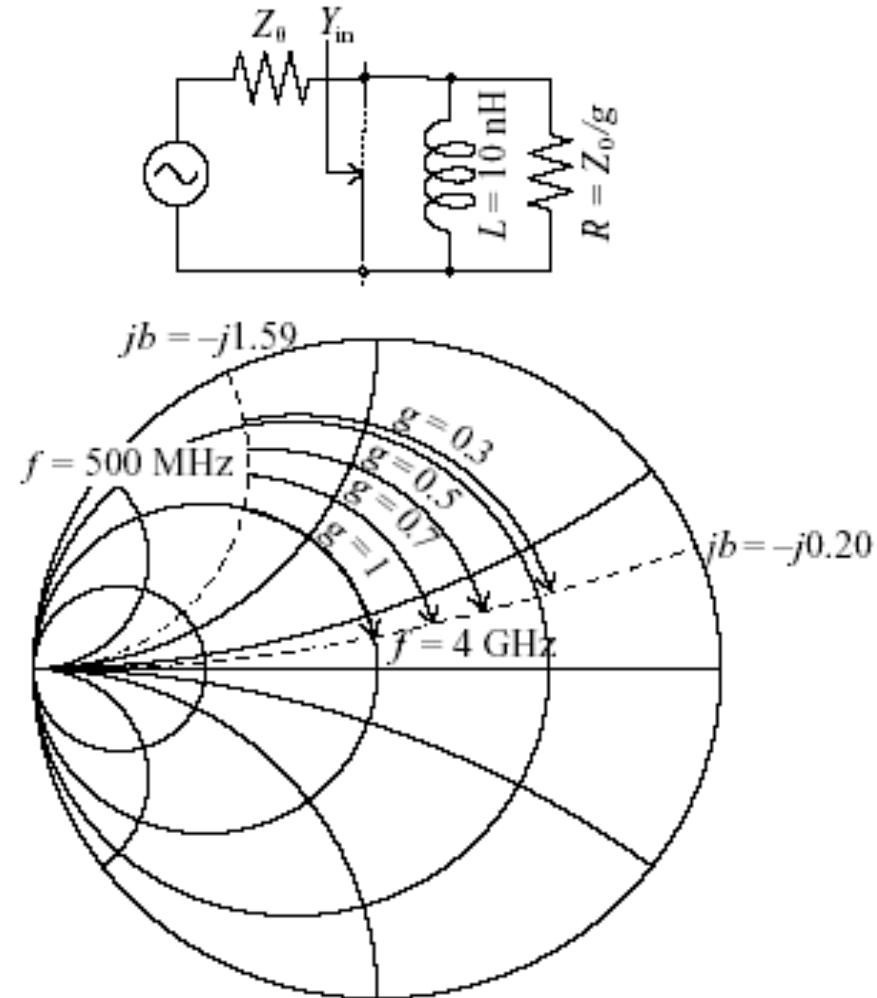
$$f = 500 \text{ MHz to } 4 \text{ GHz}$$



Frequency dependence: parallel R and C



$$y_{in} = g + jb = \frac{Z_o}{R} + jZ_o\omega C$$

Example:


$$Z_0 = 50 \Omega, C = 1 \text{ pF}$$

$$g = 0.3, 0.5, 0.7, 1$$
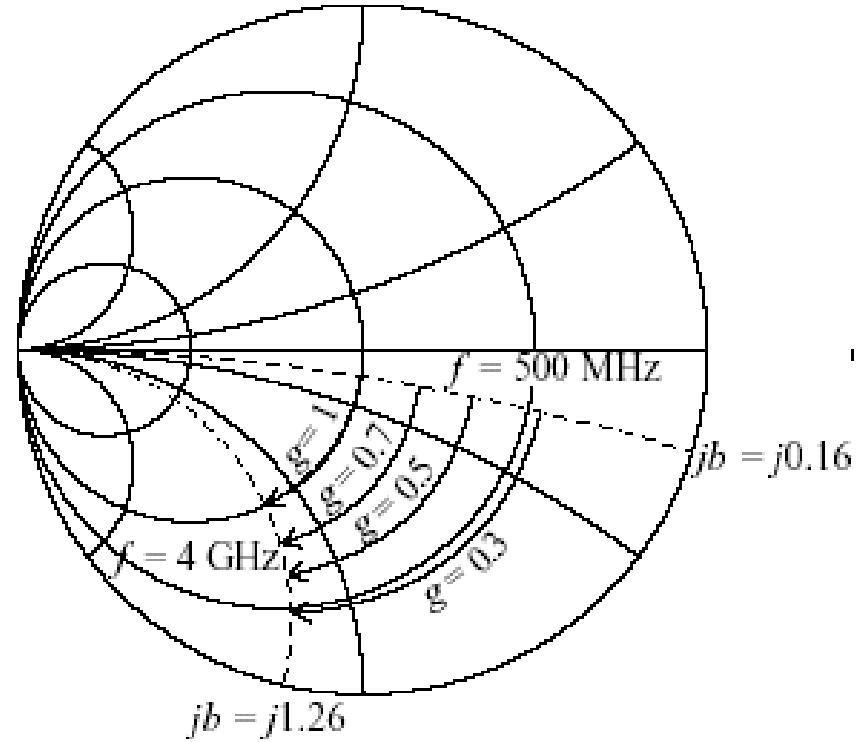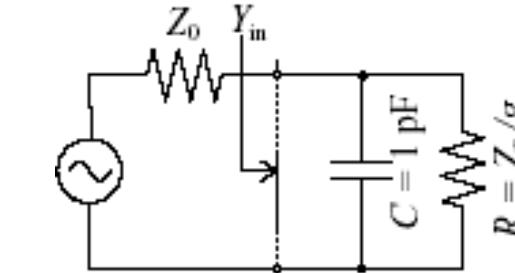
$$f = 500 \text{ MHz to } 4 \text{ GHz}$$






Frequency dependence: series connections

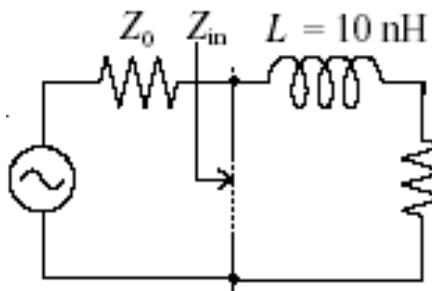


$$z_{in} = r + jx$$
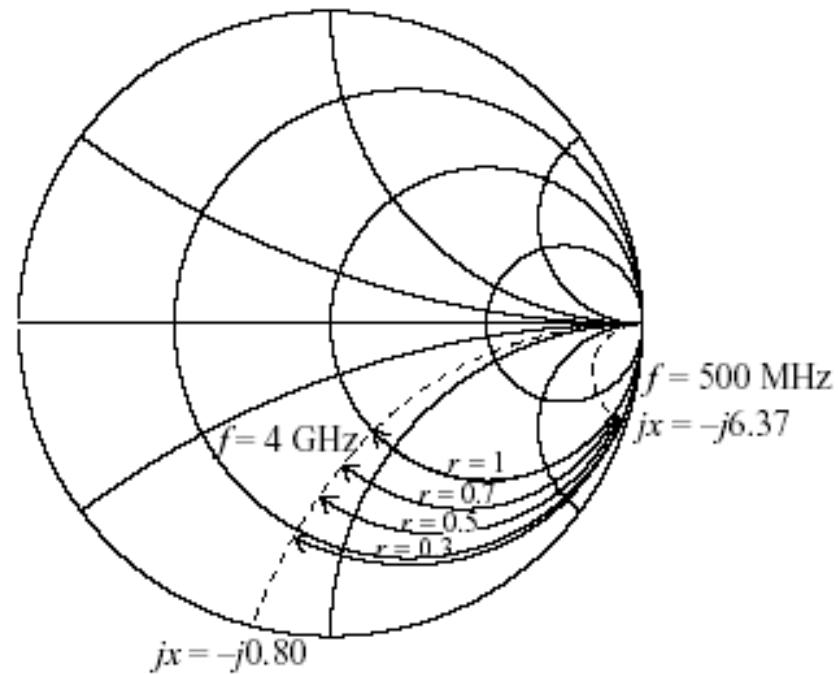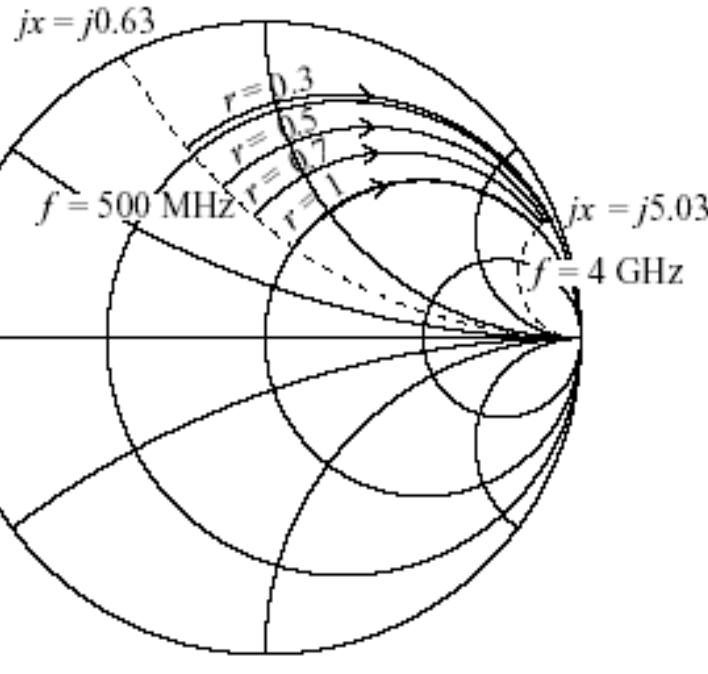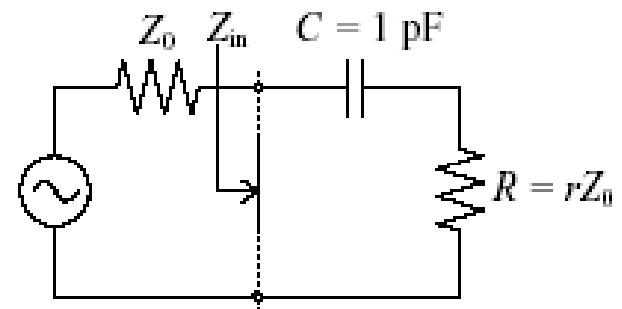
$$= \frac{R}{Z_o} + j \frac{\omega L}{Z_o} - j \frac{1}{Z_o \omega C}$$



Example: T-type network

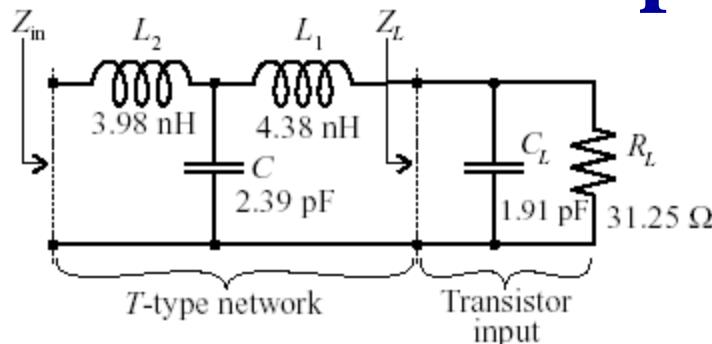

$$Z_0 = 50 \Omega \quad f = 2 \text{ GHz}$$

$$A: g_A = Z_0/R_L = 1.6$$

$$B: y_B = g_A + jZ_0\omega C_L = 1.6 + j1.2$$

$$\Rightarrow z_B = 0.4 - j0.3$$

$$C: z_C = z_B + j\omega L_1/Z_0 = 0.4 + j0.8$$


$$\Rightarrow y_C = 0.5 - j1.0$$

$$D: y_D = y_C + jZ_0\omega C = 0.5 + j0.5$$


$$\Rightarrow z_D = 1 - j1$$

$$E: z_E = z_D + j\omega L_2/Z_0 = 1$$
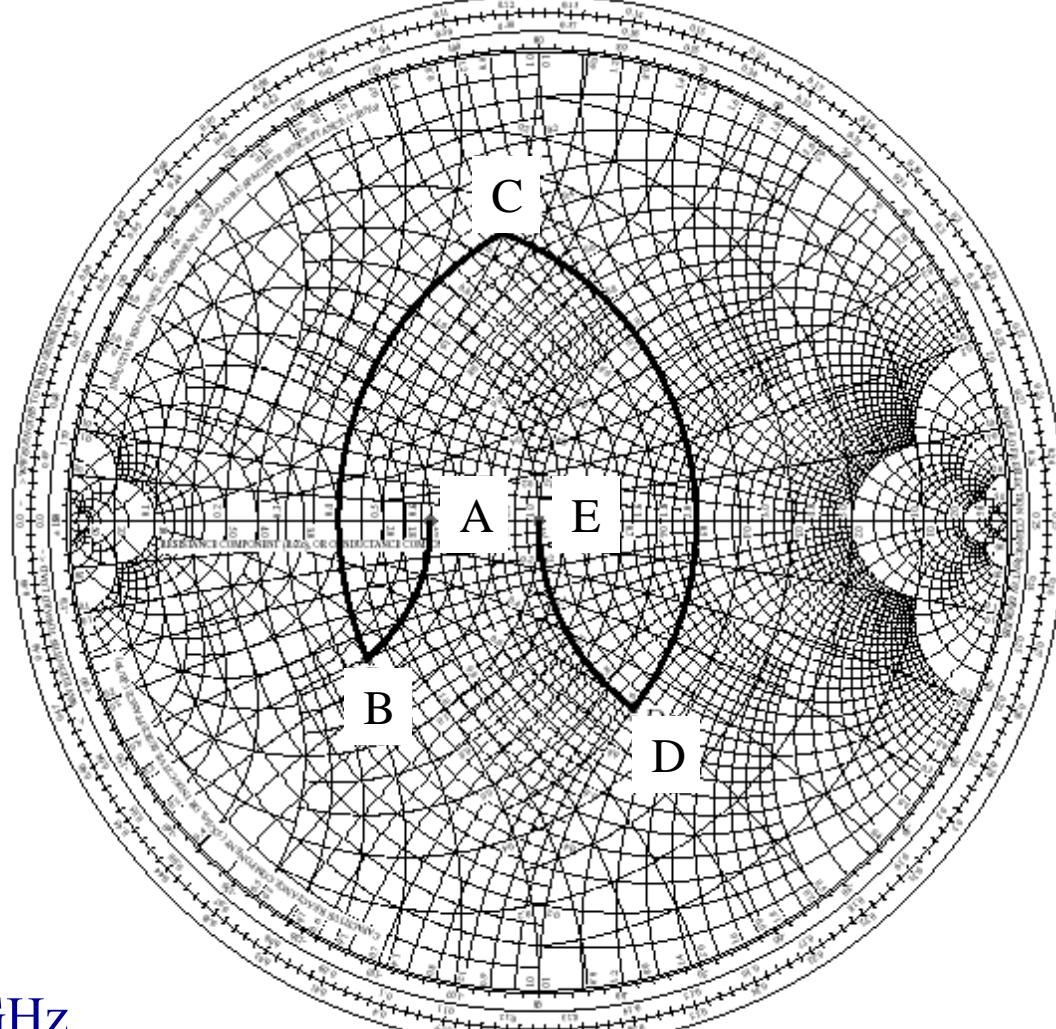
$$\Rightarrow Z_{in} = Z_0 = 50 \Omega : \text{ Match at 2 GHz}$$



Simulation of Z_{in} for T-network

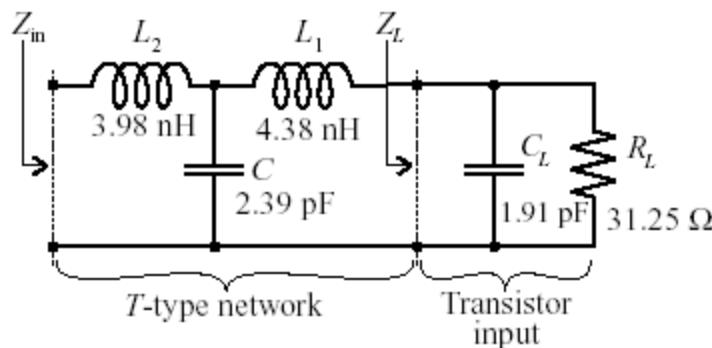

CAD simulation of Z_{in} for frequencies 0.5 – 4 GHz

Note that C behaves as a short at the highest frequencies and the network will be dominated by L_2 (purely inductive)

