

INF 5490 RF MEMS

L4: utfordringer ved RF kretsdesign

V2008, Oddvar Søråsen
Institutt for informatikk, UiO

Progresjon INF5490

- Bakgrunns-stoff
 - L1: Introduksjon. MEMS i RF
 - L2: Fremstilling
 - L3: Modellering, design og analyse (del 1, 2)
- Hovedtema i dagens forelesning:
Noen typiske trekk og utfordringer ved RF kretsdesign


Dagens forelesning

- Modellering: 3. Analyse ved Finite Element Methods
 - (fra "Modellering, design og analyse")
- RF kretsdesign
 - Elektromagnetiske bølger
 - "Skin depth"
 - Passive komponenter ved høye frekvenser
- Transmisjonslinje-teori
- To-port nettverk
 - S-parametre
- Filtre
- Q-faktor

3. Analyse ved Finite Element Methods

- Typiske trekk
 - Oppdeling av 3D-modell i små-elementer: "meshing"
 - Løse matematiske ligninger for interaksjonen mellom elementene
 - Mange iterasjoner utføres før stabil løsning oppnås
- + Mer realistiske resultater
 - Enkle matematiske modeller er approksimasjoner
 - Utilstrekkelige ved komplekse sammenhenger og strukturer
 - Jmfr. bøyning av bjelke: varierende ladningsfordeling \leftrightarrow kraft
- Bruk av FEM-simuleringer
 - CoventorWare
 - Eksempler fra modellering av bulk prosess \rightarrow

Finite Element Methods

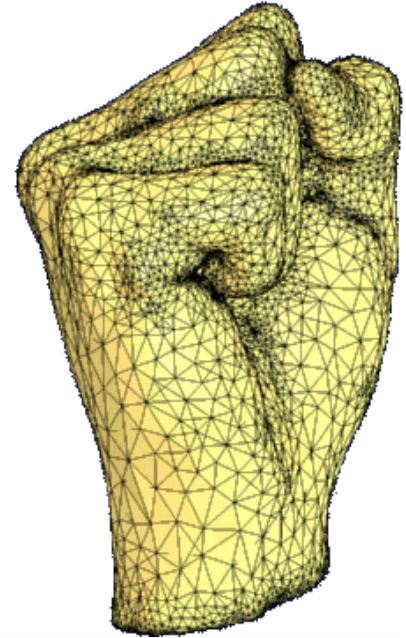

- Features
 - + good precision
 - + coupled electrostatic/ mech interaction
 - + can cope with irregular topologies
 - - insight into parameters influence is lost
 - - only small parts are practical
- Critical issues
 - proper system selection, building the 3D model
 - partitioning (meshing) , simulation parameters


3D model building: process specification



| Step | Action | Type | Layer Name | Material | Thic... | Color | Mask Name/ Polarity | Depth | Offset | Sidewall Angle | Comment |
|------|---------|------------------|------------|-------------|---------|----------|------------------------|--------|--------|-------------------|---------|
| 0 | Base | | Substrate | SILICON | 10.0 | blue | GND | | | | |
| 1 | Etch | Back, Substr... | | | | cyan | BETCH | - 10.0 | 0.0 | 0.0 | |
| 2 | Deposit | Stacked | Layer1 | SILICON | 0.01 | blue | | | | | |
| 3 | Deposit | Stacked | Layer2 | SILICON | 8.0 | blue | | | | | |
| 4 | Etch | Front, Last L... | | | | yellow | NOWEL | - 8.0 | 0.0 | 0.0 | |
| 5 | Deposit | Planar | Layer3 | SILICON | 0.0 | yellow | | | | | |
| 6 | Etch | Front, Partial | | | | white | BUCON | - 4.0 | 0.0 | 0.0 | |
| 7 | Etch | Front, Partial | | | | pink | BURES | - 1.0 | 0.0 | 0.0 | |
| 8 | Deposit | Planar | Layer4 | SILICON | 0.0 | white | | | | | |
| 9 | Etch | Front, Partial | | | | pink | BURES | - 1.0 | 0.0 | 0.0 | |
| 10 | Deposit | Planar | Layer5 | SILICON | 0.0 | pink | | | | | |
| 11 | Deposit | Stacked | Layer6 | SILICON | 3.0 | green | | | | | |
| 12 | Etch | Front, Last L... | | | | oran... | SUCON | - 3.0 | 0.0 | 0.0 | |
| 13 | Etch | Front, Partial | | | | mag... | SURES | - 1.0 | 0.0 | 0.0 | |
| 14 | Deposit | Planar | Layer7 | SILICON | 0.0 | oran... | | | | | |
| 15 | Etch | Front, Partial | | | | mag... | SURES | - 1.0 | 0.0 | 0.0 | |
| 16 | Deposit | Planar | Layer8 | SILICON | 0.0 | mag... | | | | | |
| 17 | Etch | Front, By Depth | | | | lemo... | NOSUR | - 1.0 | 0.0 | 0.0 | |
| 18 | Deposit | Planar | Layer9 | SILICON | 0.0 | gray | | | | | |
| 19 | Deposit | Stacked | Layer10 | THERM_OXIDE | 2.0 | tan | | | | | |
| 20 | Etch | Front, Last L... | | | | dlodg... | COHOL | - 2.0 | 0.0 | 0.0 | |
| 21 | Etch | Front, Last L... | | | | light... | NOBOA | - 2.0 | 0.0 | 0.0 | |
| 22 | Deposit | Conformal | Layer11 | ALUMINUM | 1.0 | red | | | | | |
| 23 | Etch | Front, Last L... | | | | red | MCOND | + 1.0 | 0.0 | 0.0 | |


- Specify a **process file** which matches an actual foundry process
 - simplifications
 - realistic: essential process features included
- → **pseudo layers**

MultiMEMS, typical features

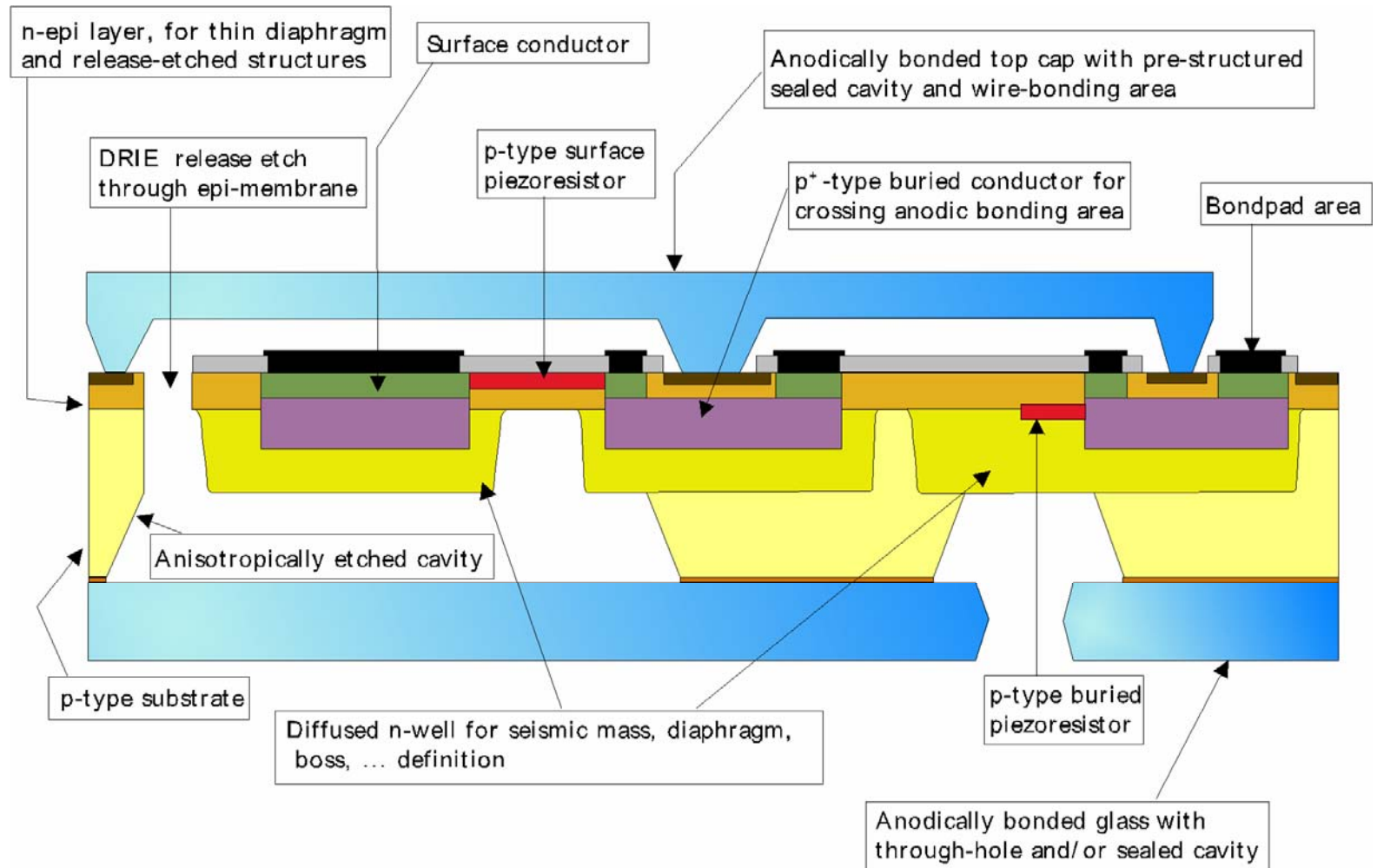

How to model the MultiMEMS bulk process in CoventorWare?

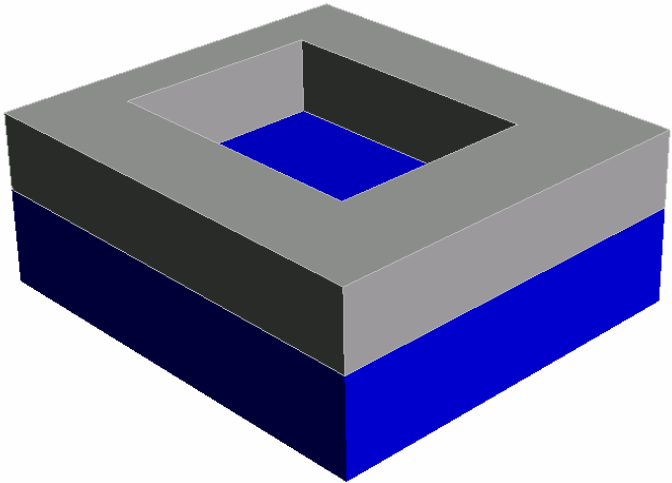- Problem:
 - the process is not based on “stacking layers”
- Create a **pseudo process!**
 - simplified, but matching
 - transfer to a procedure of **stacking layers**
 - some layers with zero spacing
 - slicing the bulk material into sub-layers **in contact**
 - make etchings and re-fillings




ProcessEditor: M:\Design_Files\testproject1\Devices\nlayers_c.proc

File Edit View Help

| Step | Action | Type | Layer Name | Material | Thic... | Color | Mask Name/ Polarity | Depth | Offset | Sidewall Angle | Comment |
|------|---------|------------------|------------|----------|---------|--------|------------------------|--------|--------|-------------------|---------|
| 0 | Base | | Substrate | SILICON | 10.0 | blue | GND | | | | |
| 1 | Etch | Back, Substr... | | | | cyan | BETCH | - 10.0 | 0.0 | 0.0 | |
| 2 | Deposit | Stacked | Layer1 | SILICON | 0.01 | blue | | | | | |
| 3 | Deposit | Stacked | Layer2 | SILICON | 8.0 | blue | | | | | |
| 4 | Etch | Front, Last L... | | | | yellow | NOWEL | - 8.0 | 0.0 | 0.0 | |

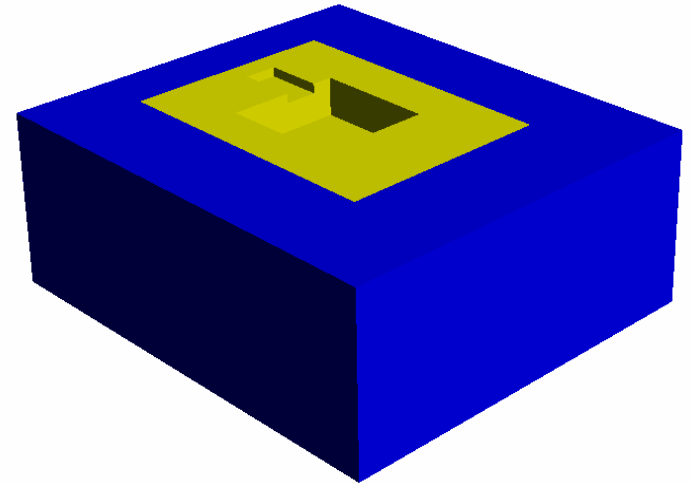Two slices of the base material stacked. **N-well** opening



ProcessEditor: M:\Design_Files\testproject1\Devices\layers_c.proc

File Edit View Help

↑ ↓ [Color icons] [ENABLE/DISABLE] [X] [?]

| Step | Action | Type | Layer Name | Material | Thic... | Color | Mask Name/ Polarity | Depth | Offset | Sidewall Angle | Comment |
|------|---------|------------------|------------|----------|---------|--------|------------------------|-------|--------|-------------------|---------|
| 0 | Base | | Substrate | SILICON | 10.0 | blue | GND | | | | |
| 1 | Etch | Back, Substr... | | | | cyan | BETCH - | 10.0 | 0.0 | 0.0 | |
| 2 | Deposit | Stacked | Layer1 | SILICON | 0.01 | blue | | | | | |
| 3 | Deposit | Stacked | Layer2 | SILICON | 8.0 | blue | | | | | |
| 4 | Etch | Front, Last L... | | | | yellow | NOWMEL - | 8.0 | 0.0 | 0.0 | |
| 5 | Deposit | Planar | Layer3 | SILICON | 0.0 | yellow | | | | | |
| 6 | Etch | Front, Partial | | | | white | BUCON - | 4.0 | 0.0 | 0.0 | |
| 7 | Etch | Front, Partial | | | | pink | BURES - | 1.0 | 0.0 | 0.0 | |


N-well in-filling. Etching holes for **buried conductor** implant and **buried resistor** implant

ProcessEditor: M:\Design_Files\testproject1\Devices\layers_c.proc


File Edit View Help

↑ ↓ [Color Swatches] [Enable/Disable] [Close] [Help]


| Step | Action | Type | Layer Name | Material | Thic... | Color | Mask Name/ Polarity | Depth | Offset | Sidewall Angle | Comment |
|------|---------|------------------|------------|----------|---------|---------|------------------------|-------|--------|-------------------|---------|
| 0 | Base | | Substrate | SILICON | 10.0 | blue | GND | | | | |
| 1 | Etch | Back, Substr... | | | | cyan | BETCH - | 10.0 | 0.0 | 0.0 | |
| 2 | Deposit | Stacked | Layer1 | SILICON | 0.01 | blue | | | | | |
| 3 | Deposit | Stacked | Layer2 | SILICON | 8.0 | blue | | | | | |
| 4 | Etch | Front, Last L... | | | | yellow | NOWEL - | 8.0 | 0.0 | 0.0 | |
| 5 | Deposit | Planar | Layer3 | SILICON | 0.0 | yellow | | | | | |
| 6 | Etch | Front, Partial | | | | white | BUCON - | 4.0 | 0.0 | 0.0 | |
| 7 | Etch | Front, Partial | | | | pink | BURES - | 1.0 | 0.0 | 0.0 | |
| 8 | Deposit | Planar | Layer4 | SILICON | 0.0 | white | | | | | |
| 9 | Etch | Front, Partial | | | | pink | BURES - | 1.0 | 0.0 | 0.0 | |
| 10 | Deposit | Planar | Layer5 | SILICON | 0.0 | pink | | | | | |
| 11 | Deposit | Stacked | Layer6 | SILICON | 3.0 | green | | | | | |
| 12 | Etch | Front, Last L... | | | | oran... | SUCON - | 3.0 | 0.0 | 0.0 | |
| 13 | Etch | Front, Partial | | | | mag... | SURES - | 1.0 | 0.0 | 0.0 | |
| 14 | Deposit | Planar | Layer7 | SILICON | 0.0 | oran... | | | | | |
| 15 | Etch | Front, Partial | | | | mag... | SURES - | 1.0 | 0.0 | 0.0 | |
| 16 | Deposit | Planar | Layer8 | SILICON | 0.0 | mag... | | | | | |
| 17 | Etch | Front, By Depth | | | | lemo... | NOSUR - | 1.0 | 0.0 | 0.0 | |

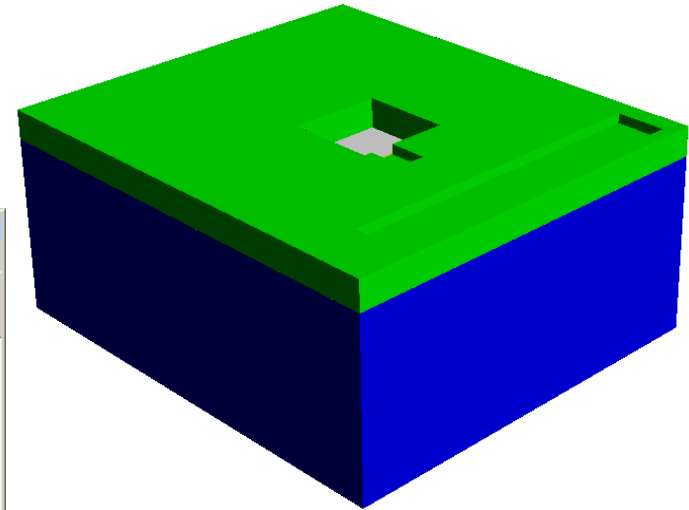

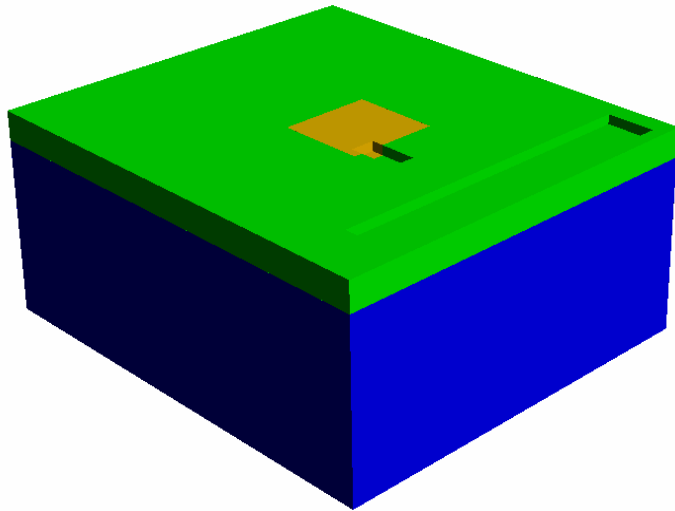Add **epi-layer**. Etch holes for **surface conductor** and **surface resistor**, -fill in.
Etch hole for n+ implant. (Implants are invisible)




Surface conductor is made visible


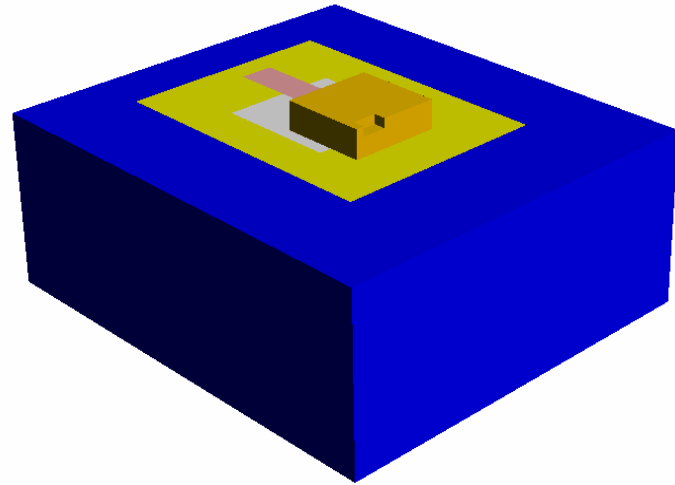


Epi-layer is invisible

3D model building: expansion

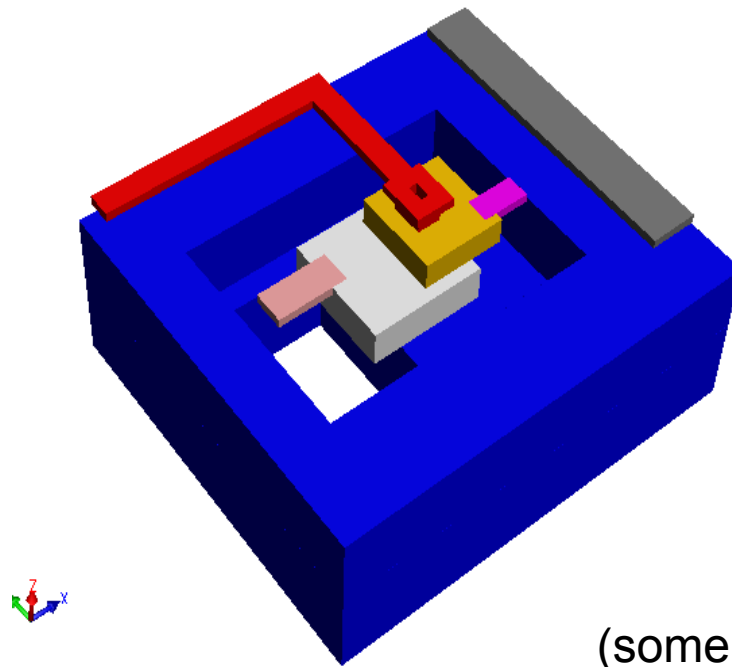

(some layers invisible)

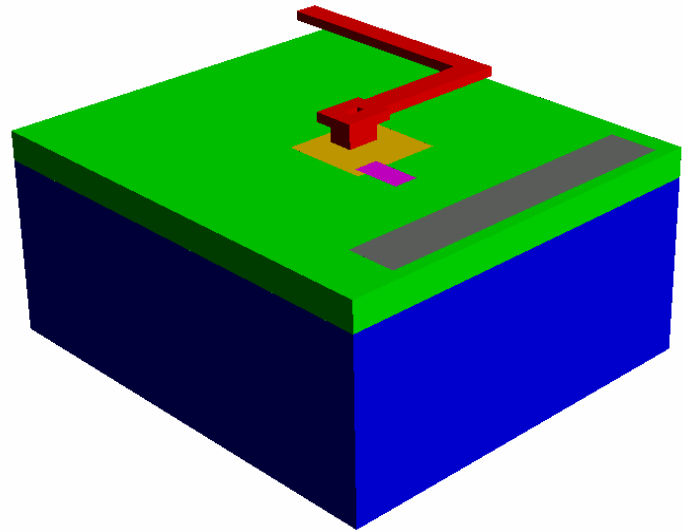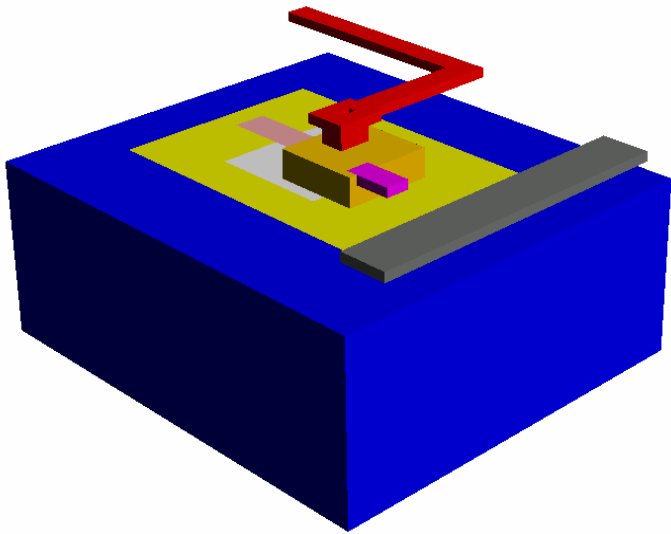


Complete structure with some layers made invisible

3D modeling procedure


- To introduce one diffusion:
 - etch base material
 - fill in implanted material
 - use “**deposit planar**” with **thickness = 0**
- To introduce multiple overlapping diffusions:
 - etch base material with all diffusion masks (the deepest first)
 - fill in the deepest implanted material
 - re-etch the remaining diffusion openings
 - fill in the next deepest implant etc.

Meshed model

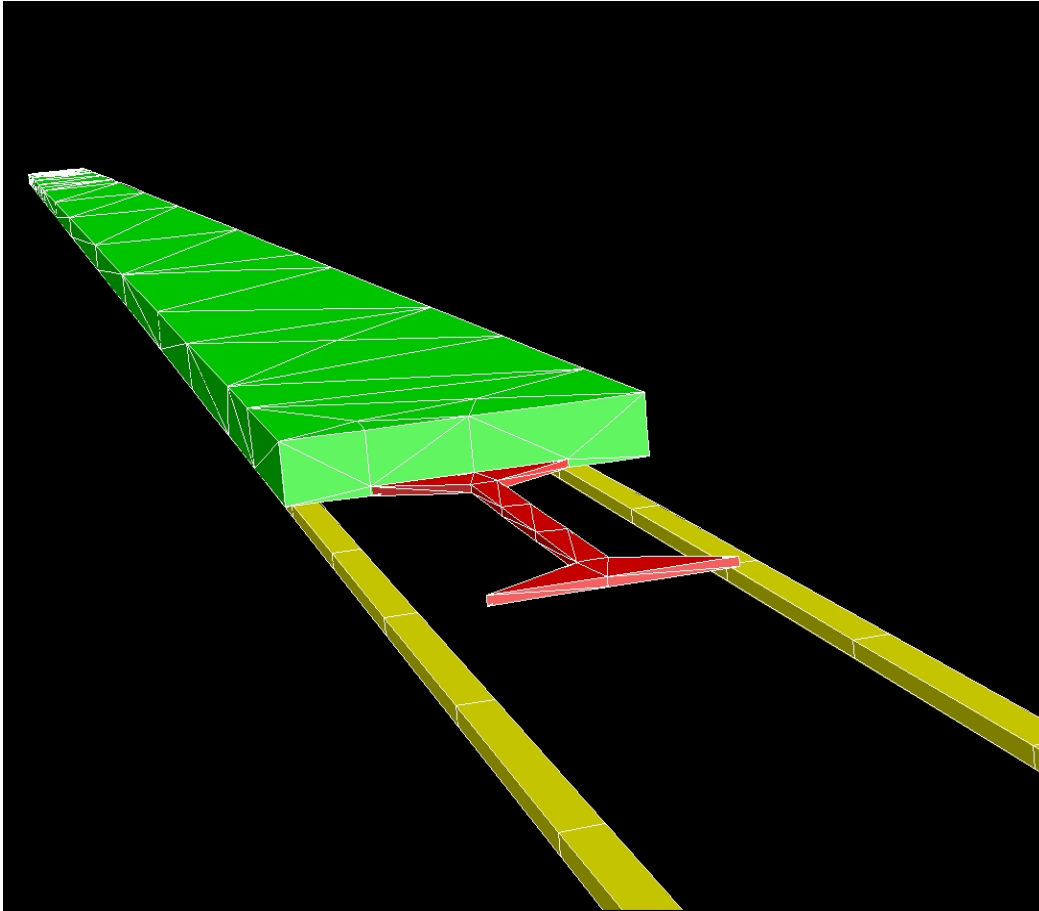


- Mirror meshed by tetrahedrons
 - 23 μm , 3 μm
- Electrodes meshed by Manhattan bricks
 - 5 μm
- Rather coarse dim due to pull-in analysis

Mirror deflection, snapshot

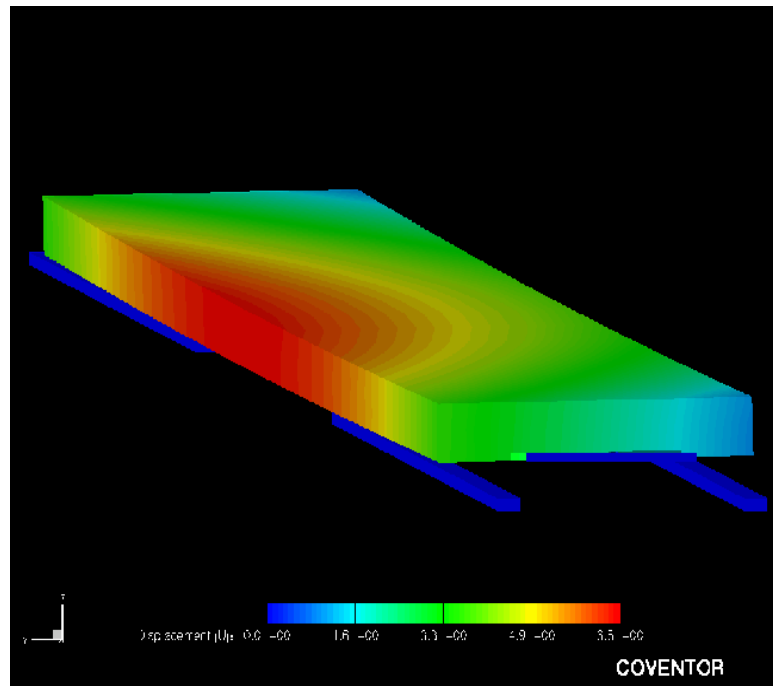

Simulation: pull-in

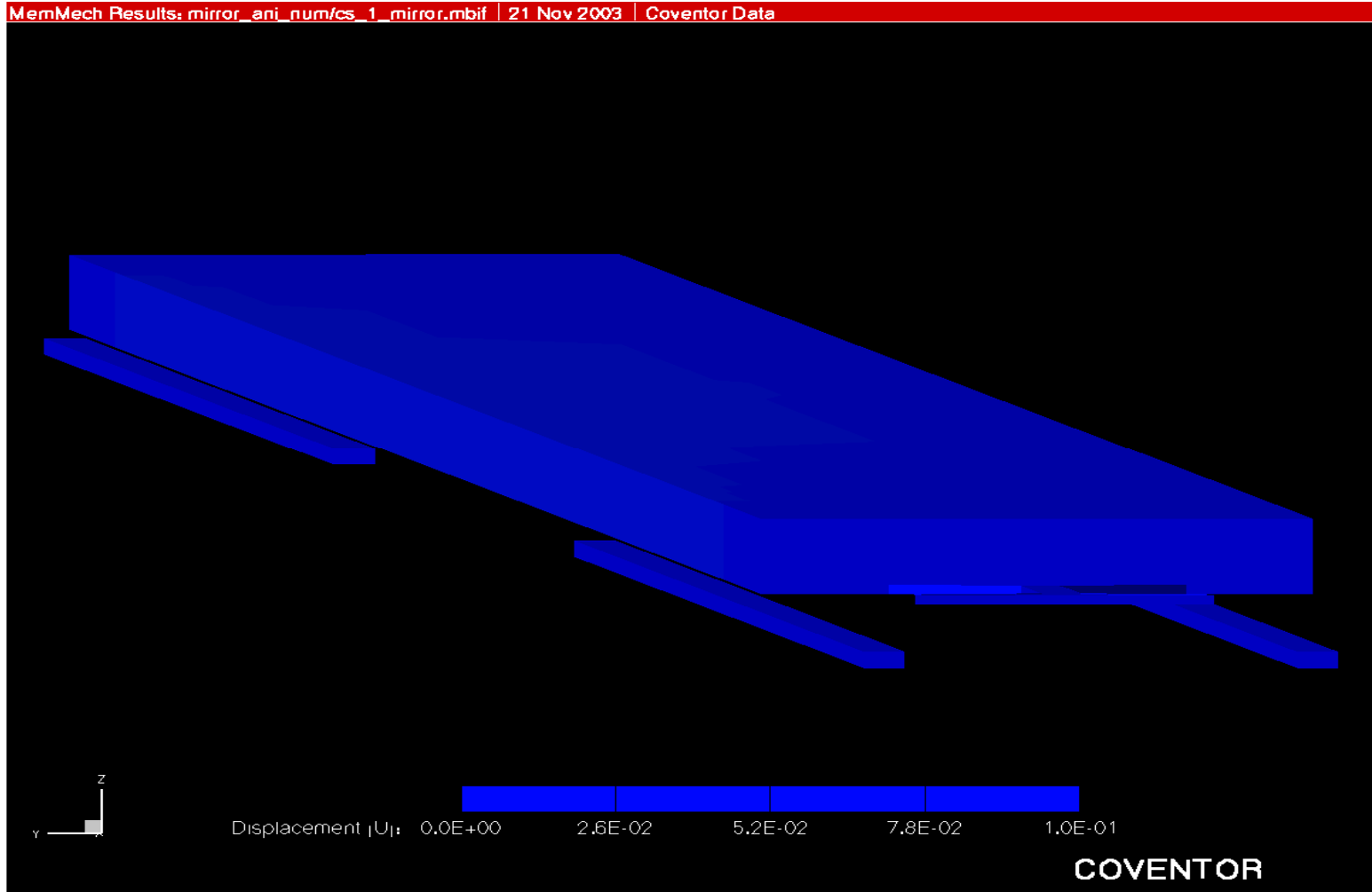

Dagens forelesning

- Modelling: 3. Analyse ved Finite Element Methods
- RF kretsdesign
 - → "Multidisciplin"
 - Elektromagnetiske bølger
 - "Skin depth"
 - Passive komponenter ved høye frekvenser
- Transmisjonslinje-teori
- To-port nettverk
 - S-parametre
- Filtre
- Q-faktor

RF- og mikrobølge-design er "multidisiplin"


- **Teoretisk** fundament
 - Elektromagnetisme
 - Signalbehandling
- **Teknologiske**, praktiske aspekter
 - Krets-teori
 - Kirchhoffs lover for strøm og spenning
- Noe av stoffet i dag overlapper INF5480
 - "RF-kretser, teori og design" (Tor Fjeldly)
 - Her: → **Sentrale punkter på en forelesning!**

RF kretsdesign

- Sentrale spørsmål
 - Hvordan oppfører kretser seg ved høye frekvenser?
 - Hvorfor endrer funksjonaliteten til komponentene seg?
 - Ved hvilke frekvenser blir vanlig kretsanalyse ugyldig?
 - Hva slags ny krets-teori trengs?
 - Hvordan kan denne teorien brukes i praksis?
 - → *Figurer og ligninger fra R. Ludwig et al: "RF Circuit Design"*

Elektromagnetiske bølger

- Elektrisk og magnetisk felt

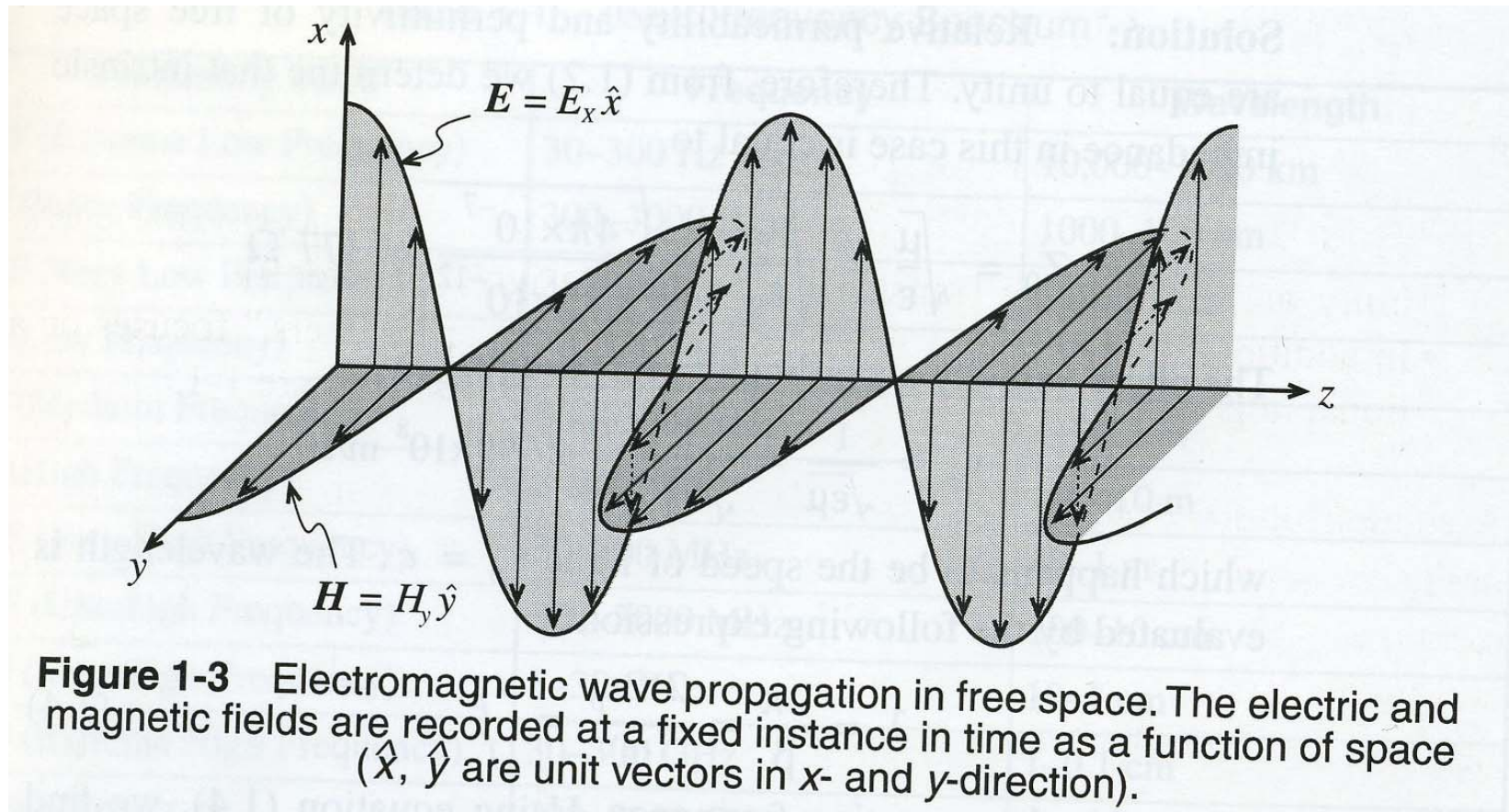

Sentrale bølgeparametre:

Elektrisk felt

$$E_x = E_{0x} \cos(\omega t - \beta z)$$

Magnetfelt

$$H_y = H_{0y} \cos(\omega t - \beta z)$$

Angular frekvens: ω

Propageringskonstant: β

Bølgen gjentar seg når: $\beta \cdot z = 2\pi$

Bølgelengde: $z = \lambda = \frac{2\pi}{\beta}$

Bølgen forplanter seg en avstand λ på en tid $T =$ perioden

Forplantningshastigheten:
(i vakuum: c)

$$v_p \cdot T = \lambda$$

$$v_p = \lambda \cdot \frac{1}{T} = \lambda \cdot f = \frac{2\pi}{\beta} \cdot \frac{\omega}{2\pi} = \frac{\omega}{\beta}$$

Sentrale bølgeparametre, forts.

Ved et gitt sted, dvs. $z = \text{konstant}$, gjentar bølgen seg etter perioden T :

$$\omega T = 2\pi \quad \text{og} \quad \omega = 2\pi / T = 2\pi f$$

der $f = \text{frekvensen}$

Frekvens og bølgelengde

- I vakuum: $\lambda * f = c$
 - Økende frekvens \rightarrow minkende bølgelengde
- Ved høye frekvenser (RF) er bølgelengden sammenlignbar med kretsdimensjonene
 - \rightarrow

Table 1-1 IEEE Frequency Spectrum

| Frequency Band | Frequency | Wavelength |
|------------------------------|------------------|-------------------|
| ELF (Extreme Low Frequency) | 30–300 Hz | 10,000–1000 km |
| VF (Voice Frequency) | 300–3000 Hz | 1000–100 km |
| VLF (Very Low Frequency) | 3–30 kHz | 100–10 km |
| LF (Low Frequency) | 30–300 kHz | 10–1 km |
| MF (Medium Frequency) | 300–3000 kHz | 1–0.1 km |
| HF (High Frequency) | 3–30 MHz | 100–10 m |
| VHF (Very High Frequency) | 30–300 MHz | 10–1 m |
| UHF (Ultrahigh Frequency) | 300–3000 MHz | 100–10 cm |
| SHF (Superhigh Frequency) | 3–30 GHz | 10–1 cm |
| EHF (Extreme High Frequency) | 30–300 GHz | 1–0.1 cm |
| Decimillimeter | 300–3000 GHz | 1–0.1 mm |
| P Band | 0.23–1 GHz | 130–30 cm |
| L Band | 1–2 GHz | 30–15 cm |
| S Band | 2–4 GHz | 15–7.5 cm |
| C Band | 4–8 GHz | 7.5–3.75 cm |
| X Band | 8–12.5 GHz | 3.75–2.4 cm |
| Ku Band | 12.5–18 GHz | 2.4–1.67 cm |
| K Band | 18–26.5 GHz | 1.67–1.13 cm |
| Ka Band | 26.5–40 GHz | 1.13–0.75 cm |
| Millimeter wave | 40–300 GHz | 7.5–1 mm |
| Submillimeter wave | 300–3000 GHz | 1–0.1 mm |

To sentrale lover

- **Faradays lov**
 - Varierende **magnetfelt** induserer **strøm**
- **Amperes lov**
 - **Strøm** som flyter setter opp **magnetfelt**

Faradays lov

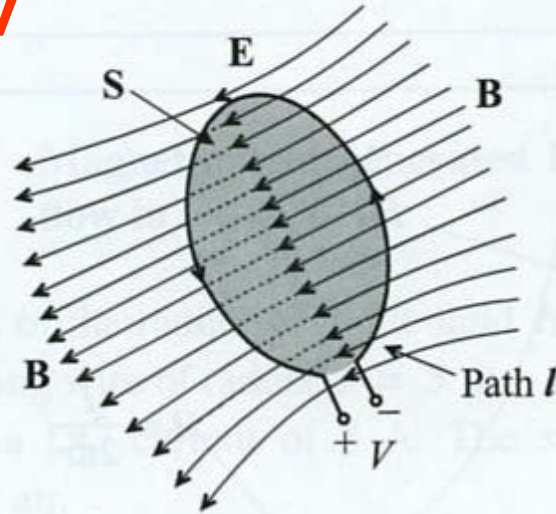


Figure 2-15 The time rate of change of the magnetic flux density induces a voltage.

$$\oint \bar{E} \cdot d\bar{l} = -\frac{d}{dt} \iint \bar{B} \cdot d\bar{S}$$


\bar{B} = magnetisk fluks – tetthet

$$\bar{B} = \mu \cdot \bar{H}$$

μ = permeabilitet = $\mu_0 \cdot \mu_r$

\bar{H} = magnetfelt

Amperes lov

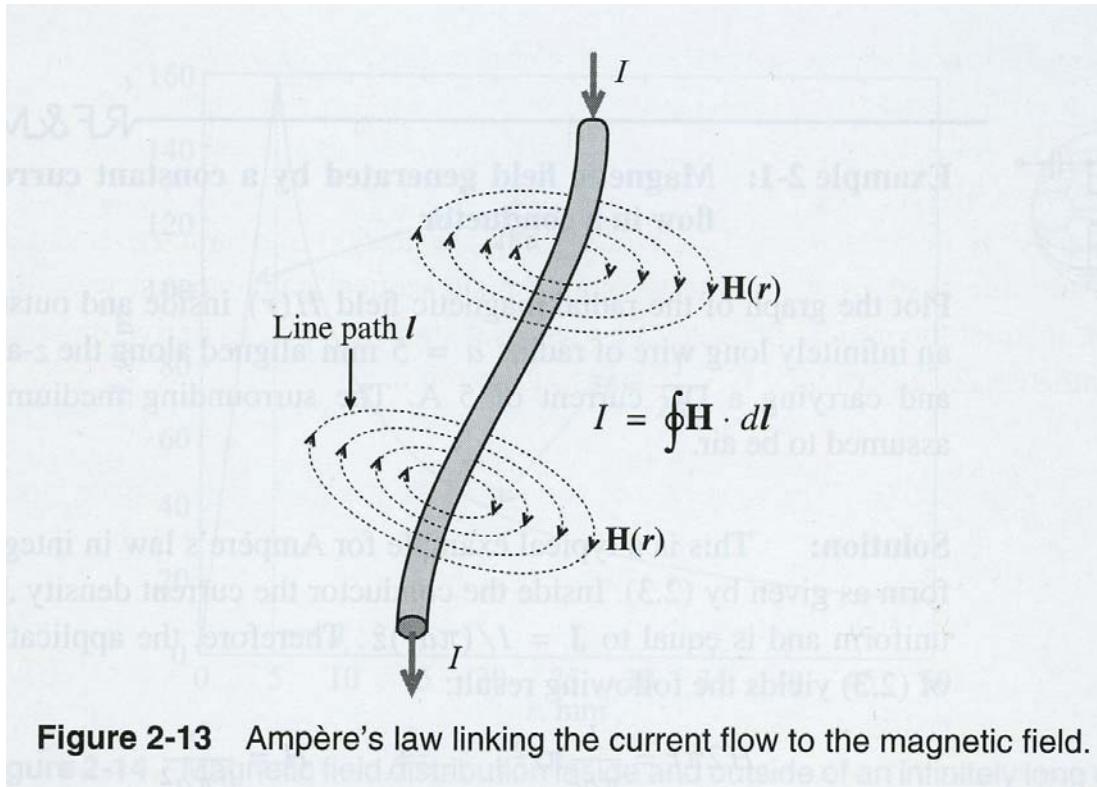

$$I = \oint \bar{H} \cdot d\bar{l} = \iint \bar{J} \cdot d\bar{S}$$

”Skin depth”

- Signaloverføring ved økende frekvens
 - **DC** signal:
 - Hele tverrsnittet leder strøm
 - **AC** signal (argumentasjons-rekkefølge):
 - Varierende strøm induserer et vekslende magnetfelt ([Amperes lov](#))
 - Magnetfeltet er sterkest når radius er liten
 - Størst tidsvariasjon av magnetfeltet når en nærmer seg sentrum
 - Varierende magnetfelt induserer et elektrisk felt ([Faradays lov](#))
 - Det induserte elektriske feltet (som motvirker det opprinnelige) øker i styrke mot midten av ledere

Skin depth, forts.

- Motstanden R øker mot sentrum av lederen
 - Strømmen flyter i **ytterkantene** ved økende frekvens
 - Formel: "skin-depth" →
 - Betegner reduksjon i strømtettheten til 1/e
- Hva betyr denne effekten i praksis? →

$$\delta = (\pi f \mu \sigma_{\text{cond}})^{-1/2}$$

"Skin-depth"

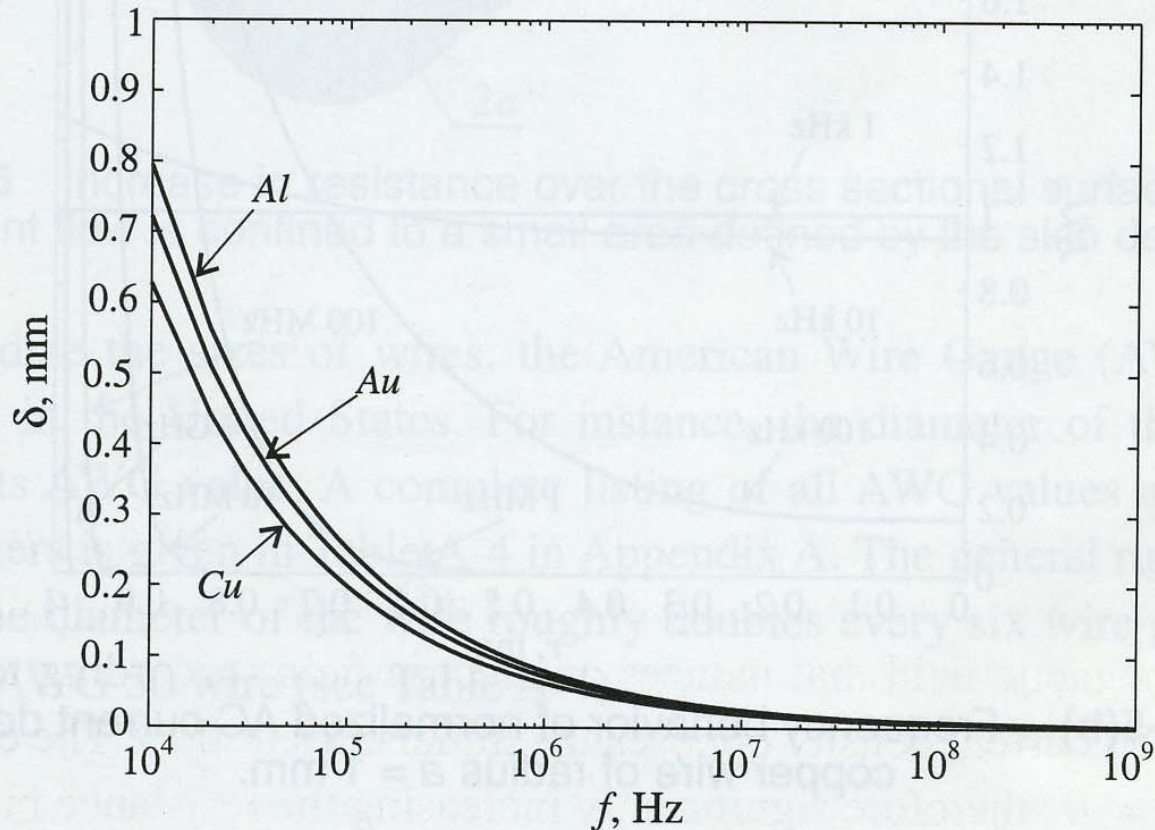


Figure 1-4 Skin depth behavior of copper $\sigma_{Cu} = 64.516 \times 10^6$ S/m, aluminum $\sigma_{Al} = 40.0 \times 10^6$ S/m, and gold $\sigma_{Au} = 48.544 \times 10^6$ S/m.

Strømtetthet ved ulike frekvenser

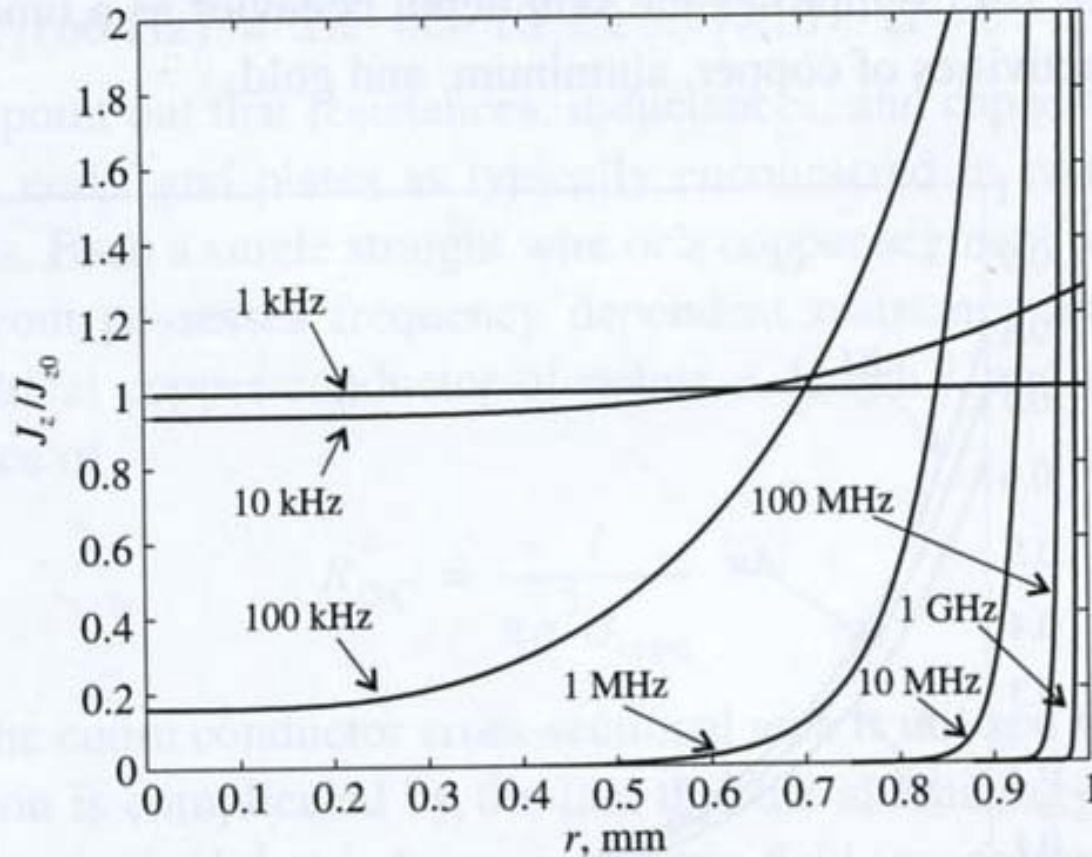


Figure 1-5(b) Frequency behavior of normalized AC current density for a copper wire of radius $a = 1$ mm.

Passive komponenter ved høye frekvenser

- Ekvivalentkrets for resistor


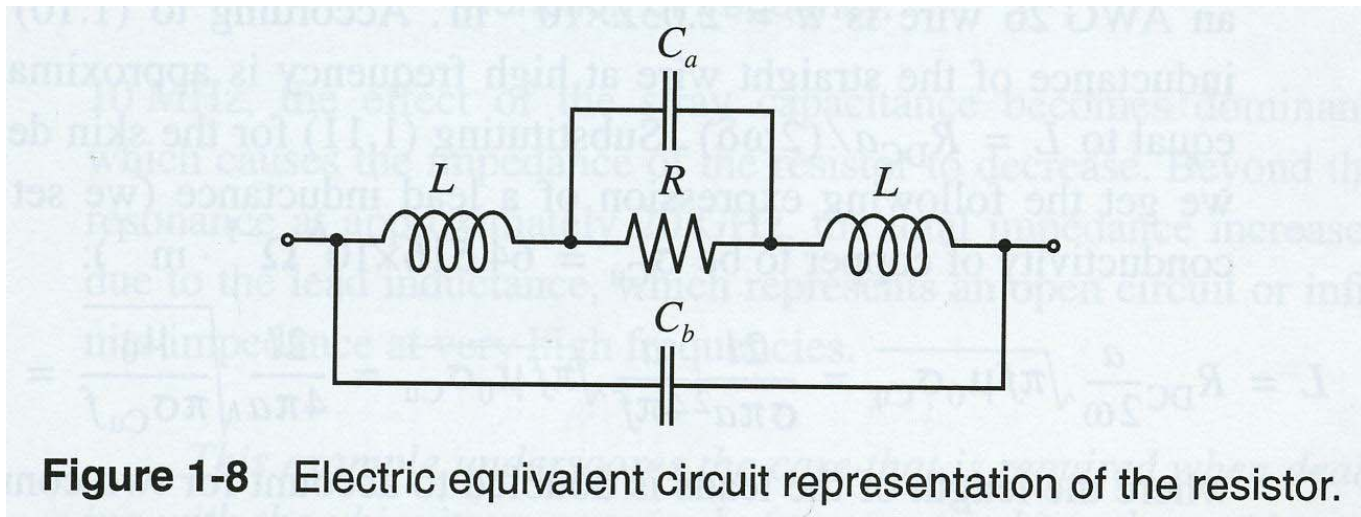


Figure 1-8 Electric equivalent circuit representation of the resistor.

Beregning av resistor-impedans

Forenklet modell:

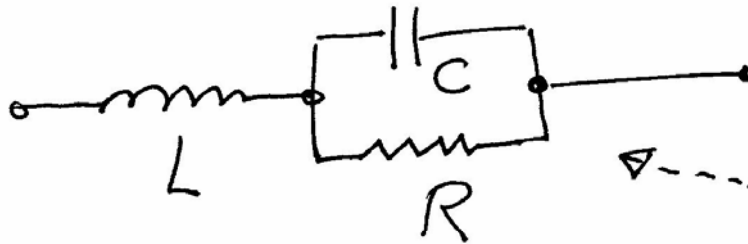


$$G = \frac{1}{R} + sC$$

$$z = sL + \frac{1}{\frac{1}{R} + sC} = sL + \frac{R}{1 + sRC}$$

$$z(j\omega) = j\omega L + \frac{R}{1 + j\omega RC}$$

Impedans som funksjon av f

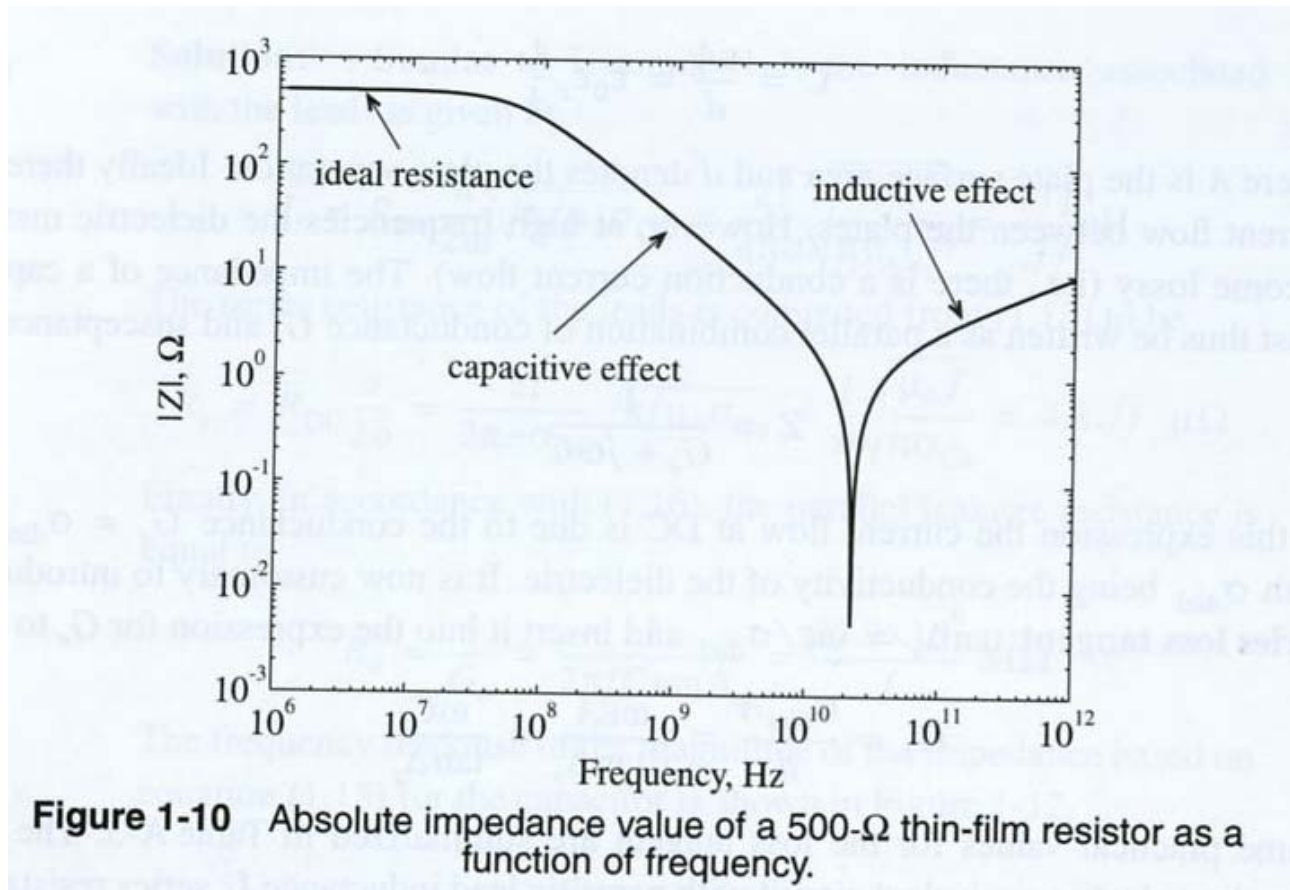

Drøfting :

$$z(j\omega) \rightarrow R, \text{ når } \omega \rightarrow 0$$

$$z(j\omega) \rightarrow j\omega L, \text{ når } \omega \rightarrow \infty$$

Resonans når leddene er motsatt like store

$$sL = -\frac{R}{1 + sRC}$$

$$LRCs^2 + Ls + R = 0$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$s = -\frac{1}{2RC} \pm j\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$$

Høyfrekvens kapasitans

- Ekvivalenteskjema

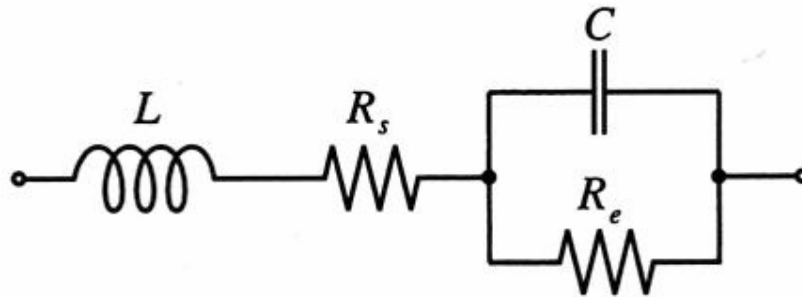


Figure 1-11 Electric equivalent circuit for a high-frequency capacitor.

Impedans som funksjon av f

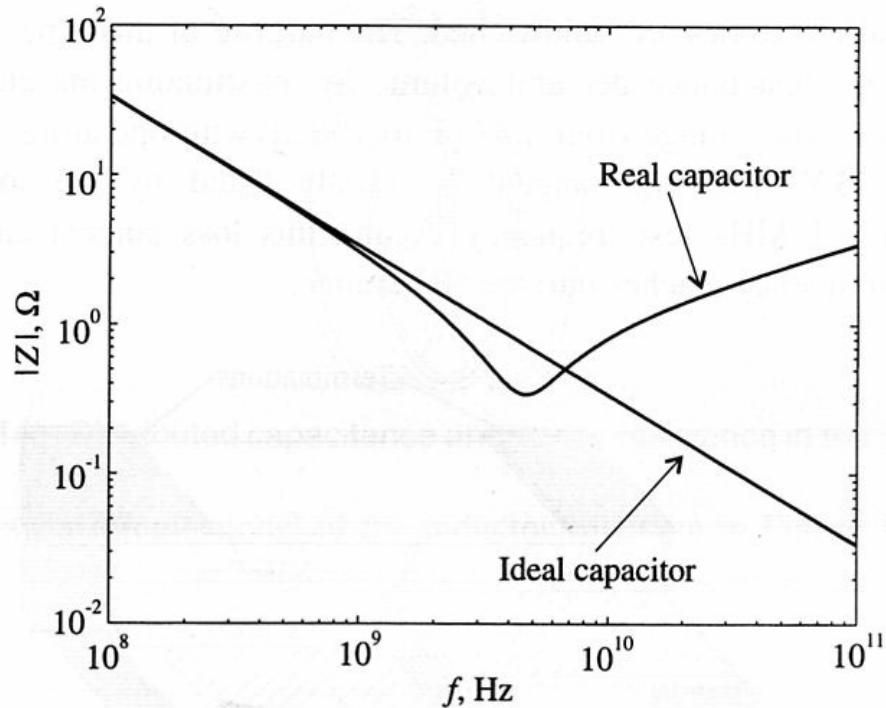


Figure 1-12 Absolute value of the capacitor impedance as a function of frequency.

Høyfrekvens induktans

- Ekvivalentskjema

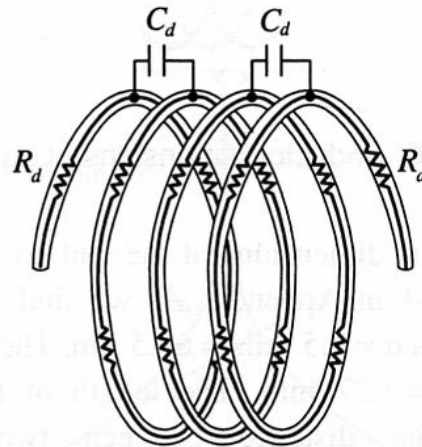


Figure 1-14 Distributed capacitance and series resistance in the inductor coil.

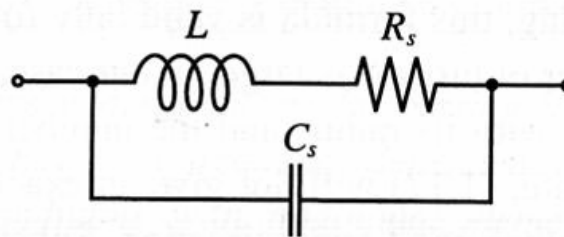


Figure 1-15 Equivalent circuit of the high-frequency inductor.

Impedans som funksjon av f

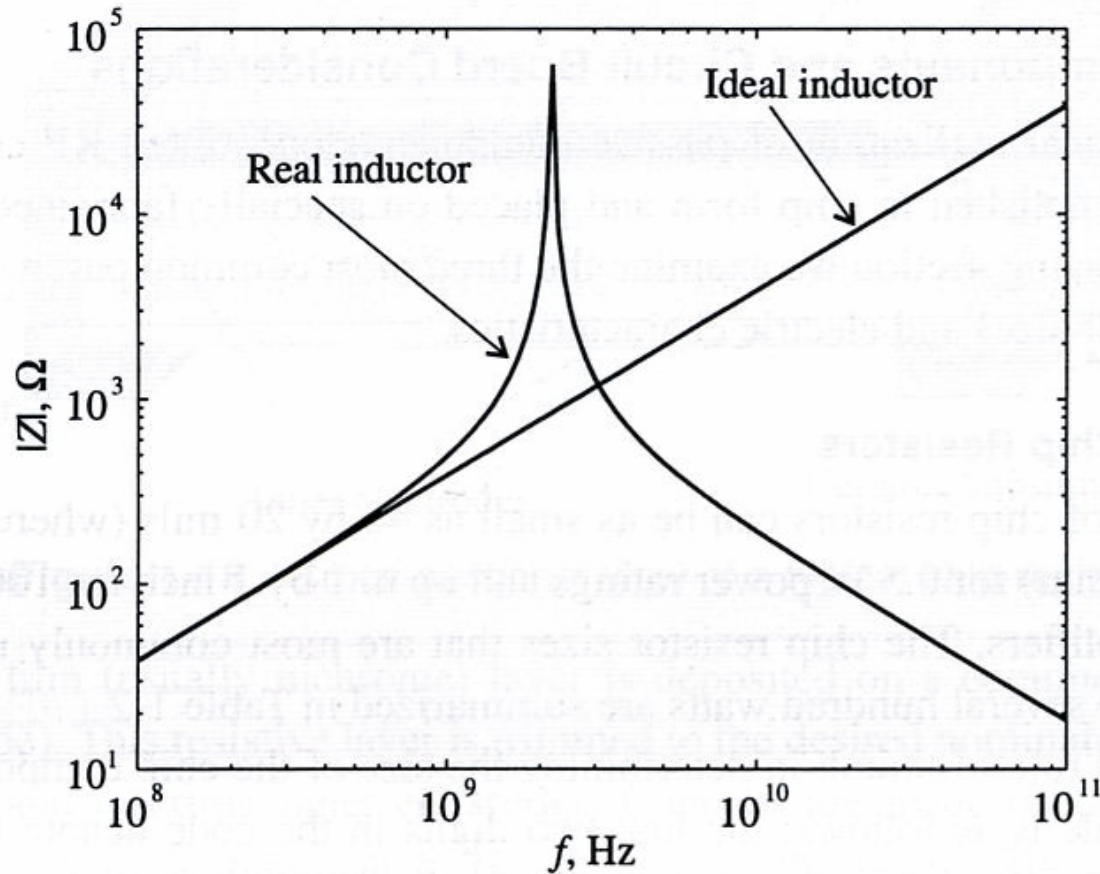


Figure 1-17 Frequency response of the impedance of an RFC.

Transmisjonslinje-teori

- Frekvens øker \rightarrow bølgelengde avtar (λ)
- Når λ blir sammenlignbar med komponentstørrelsen, vil en oppleve et **spenningsfall over komponenten!!**
 - Strøm og spenning har ikke en konstant verdi
- Spenning og strøm oppfører seg som **bølger** som utbrer seg i ledere og komponenter
 - De har derfor en verdi som avhenger av hvor en måler \rightarrow
 - Signalene må utbres ved **transmisjonslinjer**
 - Må ta hensyn til **refleksjoner, karakteristiske impedanser**

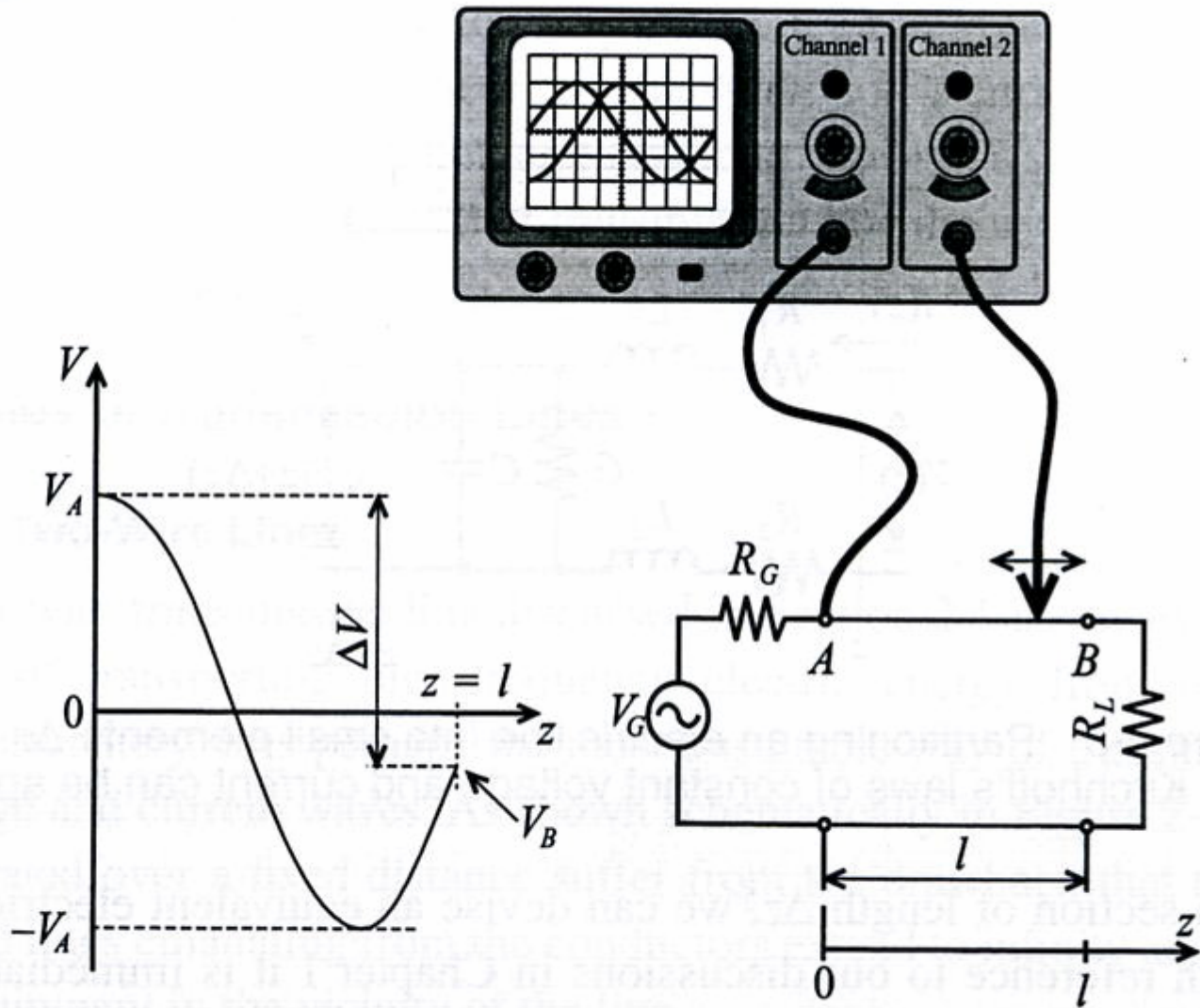


Figure 2-2 Amplitude measurements of 10 GHz voltage signal at the beginning (location A) and somewhere in between a wire connecting load to source.

Transmisjonslinje

- En leder kan modelleres som en transmisjonslinje

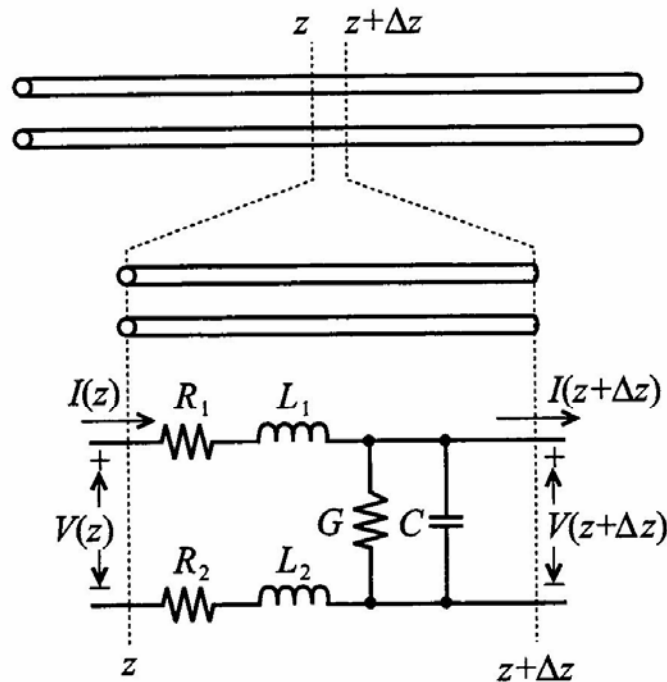


Figure 2-3 Partitioning an electric line into small elements Δz over which Kirchhoff's laws of constant voltage and current can be applied.

Kan deles opp i infinitesimale sub-enheter

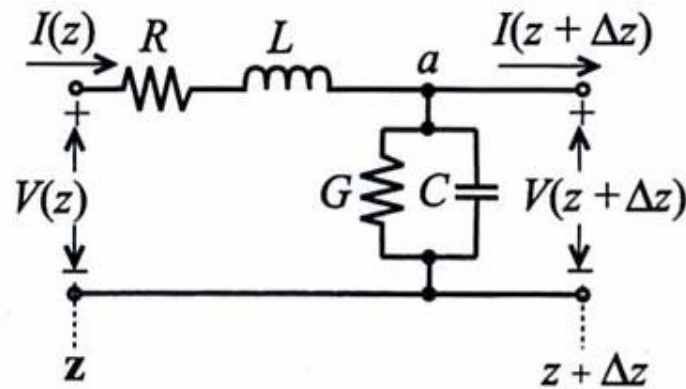


Figure 2-17 Segment of a transmission line with voltage loop and current node.

Benytte Kirchhoffs lover

- Gir 2 koblede 1.ordens diff-ligninger

$$(R + j\omega L)I(z)\Delta z + V(z + \Delta z) = V(z) \quad (2.26)$$

$$\lim_{\Delta z \rightarrow 0} \left(-\frac{V(z + \Delta z) - V(z)}{\Delta z} \right) = -\frac{dV(z)}{dz} = (R + j\omega L)I(z) \quad (2.27)$$

$$\boxed{-\frac{dV(z)}{dz} = (R + j\omega L)I(z)} \quad (2.28)$$

$$I(z) - V(z + \Delta z)(G + j\omega C)\Delta z = I(z + \Delta z) \quad (2.29)$$

$$\lim_{\Delta z \rightarrow 0} \frac{I(z + \Delta z) - I(z)}{\Delta z} = \frac{dI(z)}{dz} = -(G + j\omega C)V(z) \quad (2.30)$$

$$\frac{d^2 V(z)}{dz^2} - k^2 V(z) = 0 \quad (2.31)$$

$$k = k_r + jk_i = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (2.32)$$

$$\frac{d^2 I(z)}{dz^2} - k^2 I(z) = 0 \quad (2.33)$$

Løsning: 2 bølger

- Løsningen er bølger i **positiv** og **negativ** retning

$$V(z) = V^+ e^{-kz} + V^- e^{+kz} \quad (2.34)$$

$$I(z) = I^+ e^{-kz} + I^- e^{+kz} \quad (2.35)$$

$$I(z) = \frac{k}{(R + j\omega L)} (V^+ e^{-kz} - V^- e^{+kz}) \quad (2.36) \quad (\text{Jmfr.2.27})$$

Karakteristisk linje-impedans: $Z_0 = \frac{V^+}{I^+} = -\frac{V^-}{I^-}$

$$Z_0 = \frac{(R + j\omega L)}{k} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \quad (2.37)$$

Impedans ved **tapsfri** transmisjonslinje

$$Z_0 = \sqrt{L/C}$$

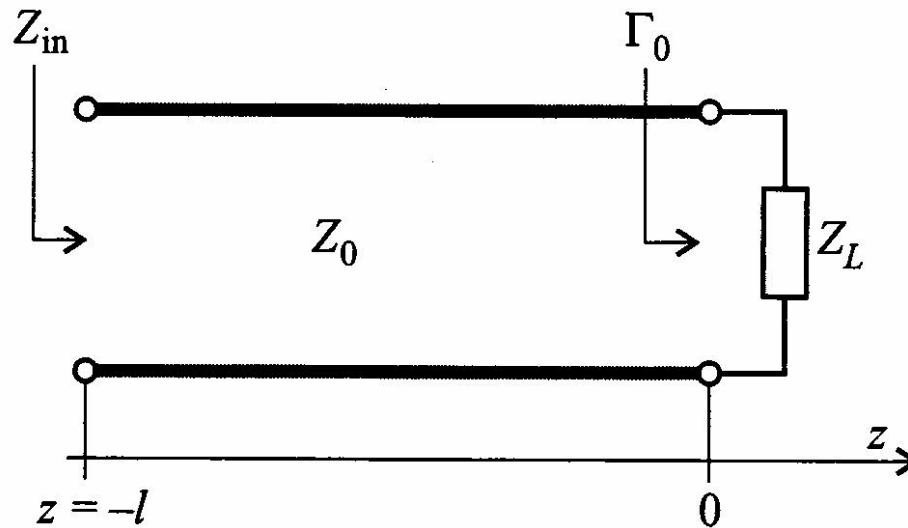


Figure 2-23 Terminated transmission line at location $z = 0$.

Refleksjon

- Hvordan hindre refleksjoner og sørge for god signalforplantning?
- Definisjon av **refleksjonskoeffisient** →

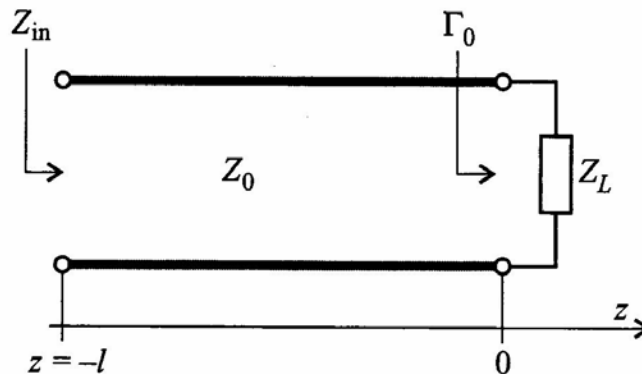


Figure 2-23 Terminated transmission line at location $z = 0$.

Refleksjonskoeffisient

$$\Gamma_0 = \frac{V^-}{V^+} \quad \leftarrow \text{definisjon av refleksjonskoeffisient i } z = 0$$

$$V(z) = V^+ (e^{-kz} + \Gamma_0 \cdot e^{+kz})$$

$$I(z) = \frac{V^+}{Z_0} (e^{-kz} - \Gamma_0 \cdot e^{+kz})$$

Impedans i $z = 0$:

$$Z(0) = \frac{V(0)}{I(0)} = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0} = Z_L \quad = \text{lastimpedansen}$$

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Ulike termineringer

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Åpen linje

→ refleksjon med lik polaritet

$$Z_L = \infty \Rightarrow \Gamma_0 = 1$$

Kortslutning

→ refleksjon med invers polaritet

$$Z_L = 0 \Rightarrow \Gamma_0 = -1$$

Ingen refleksjon når:

$$Z_0 = Z_L \Rightarrow \Gamma_0 = 0$$

→ "MATCHING"

Stående bølger

- Kortsluttet krets gir **stående bølger** ($Z_L = 0$)

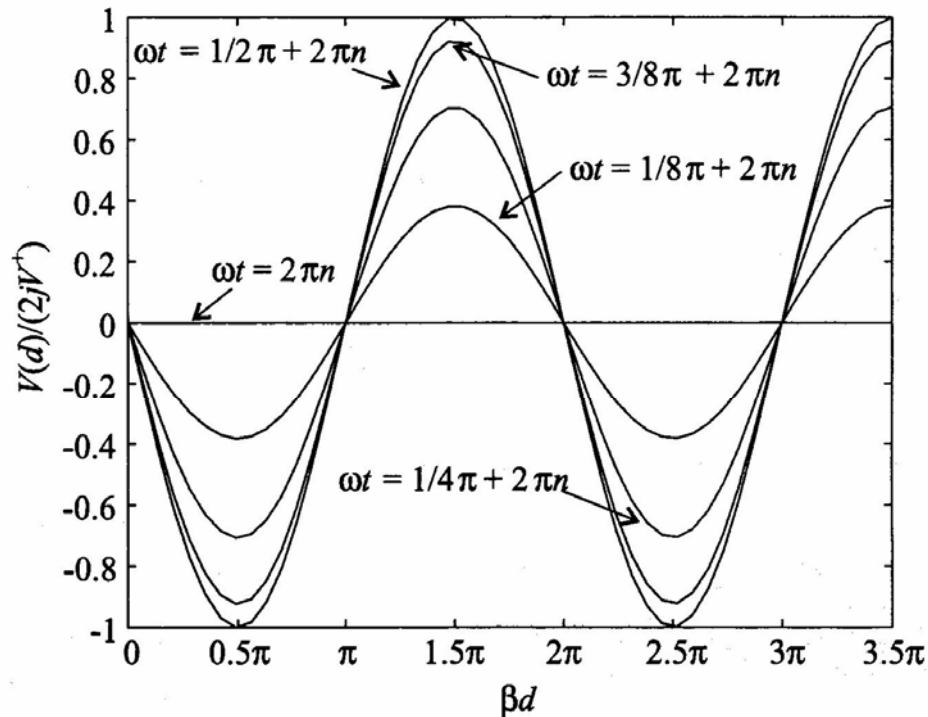


Figure 2-25 Standing wave pattern for various instances of time.

RF-kretser

- En høyfrekvens-krets kan betraktes som
 - en samling av et endelig antall **transmisjonslinje-seksjoner** forbundet med **diskrete aktive** og **passive** komponenter

To-port nettverk

- Fordelaktig med **to-port-beskrivelse**
 - Kretser kan deles opp i enkle bestanddeler
 - to-porter
 - Kan benyttes for å forenkle analysen av sammensatte nettverk
- Ulike typer to-porter
 - **Z, Y, h-matrix**
 - Hver har **ulike egenskaper ved sammenkobling**
 - $Z \rightarrow$ serie, $Y \rightarrow$ parallell, hybrid \rightarrow blanding
 - Figur \rightarrow

Multiport-nettverk

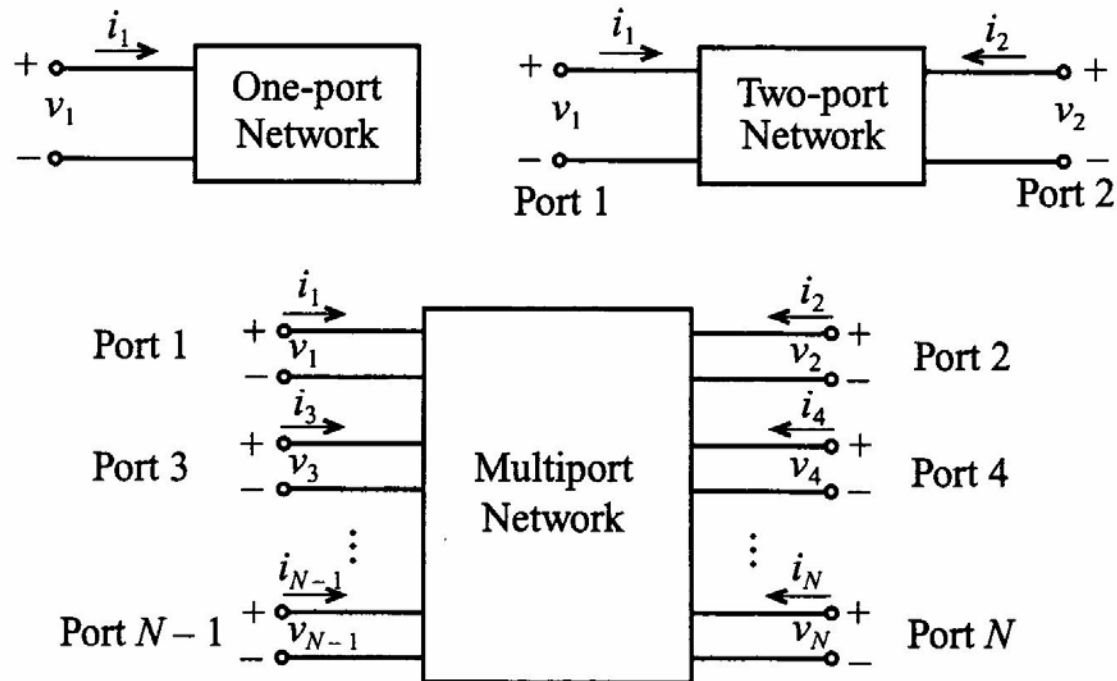


Figure 4-1 Basic voltage and current definitions for single- and multiport network.

Eks. Z-matrise

$$\begin{Bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{Bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & Z_{22} & \cdots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \cdots & Z_{NN} \end{bmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{Bmatrix} \quad (4.2)$$

$$\{\mathbf{V}\} = [\mathbf{Z}]\{\mathbf{I}\} \quad (4.3)$$

ABCD nettverk

$$\begin{Bmatrix} v_1 \\ i_1 \end{Bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{Bmatrix} v_2 \\ -i_2 \end{Bmatrix} \quad (4.10)$$

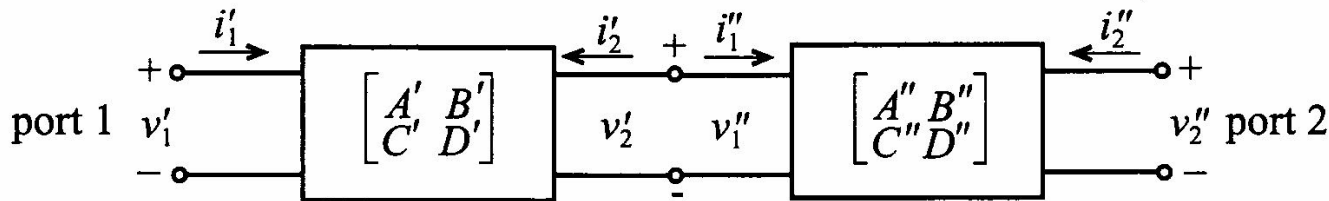








Figure 4-9 Cascading two networks.

$$\begin{aligned} \begin{Bmatrix} v_1 \\ i_1 \end{Bmatrix} &= \begin{Bmatrix} v_1' \\ i_1' \end{Bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{Bmatrix} v_2' \\ -i_2' \end{Bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{Bmatrix} v_1'' \\ i_1'' \end{Bmatrix} \\ &= \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix} \begin{Bmatrix} v_2'' \\ -i_2'' \end{Bmatrix} \end{aligned} \quad (4.21)$$

Velegnet for kaskadekobling

ABCD-parametre for "nyttige" 2-porter

Table 4-1 ABCD-Parameters of Some Useful Two-Port Circuits.
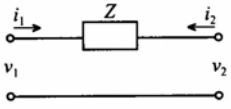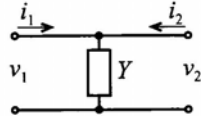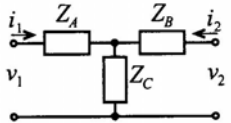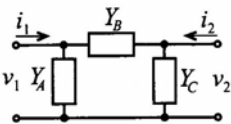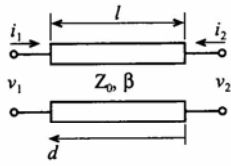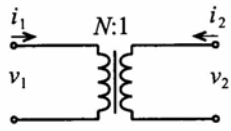
| Circuit | ABCD-Parameters | |
|---|--|--|
|  | $A = 1$ $C = 0$ | $B = Z$ $D = 1$ |
|  | $A = 1$ $C = Y$ | $B = 0$ $D = 1$ |
|  | $A = 1 + \frac{Z_A}{Z_C}$ $C = \frac{1}{Z_C}$ | $B = Z_A + Z_B + \frac{Z_A Z_B}{Z_C}$ $D = 1 + \frac{Z_B}{Z_C}$ |
|  | $A = 1 + \frac{Y_B}{Y_C}$ $C = Y_A + Y_B + \frac{Y_A Y_B}{Y_C}$ | $B = \frac{1}{Y_C}$ $D = 1 + \frac{Y_A}{Y_C}$ |
|  | $A = \cos \beta l$ $C = \frac{j \sin \beta l}{Z_0}$ | $B = j Z_0 \sin \beta l$ $D = \cos \beta l$ |
|  | $A = N$ $C = 0$ | $B = 0$ $D = \frac{1}{N}$ |

Konvertering mellom ulike 2-port realiseringer

Table 4-2 Conversion between Different Network Representations

| | [Z] | [Y] | [h] | [ABCD] |
|--------|--|--|--|---|
| [Z] | $\begin{matrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{matrix}$ | $\begin{matrix} \frac{Z_{22}}{\Delta Z} & \frac{Z_{12}}{-\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{matrix}$ | $\begin{matrix} \frac{\Delta Z}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ \frac{Z_{21}}{-Z_{22}} & \frac{1}{Z_{22}} \end{matrix}$ | $\begin{matrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta Z}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{matrix}$ |
| [Y] | $\begin{matrix} \frac{Y_{22}}{\Delta Y} & \frac{Y_{12}}{-\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{matrix}$ | $\begin{matrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{matrix}$ | $\begin{matrix} \frac{1}{Y_{11}} & \frac{Y_{12}}{-Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{matrix}$ | $\begin{matrix} \frac{Y_{22}}{Y_{21}} & \frac{1}{Y_{21}} \\ \frac{\Delta Y}{Y_{21}} & \frac{Y_{11}}{Y_{21}} \end{matrix}$ |
| [h] | $\begin{matrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{h_{21}}{-h_{22}} & \frac{1}{h_{22}} \end{matrix}$ | $\begin{matrix} \frac{1}{h_{11}} & \frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{matrix}$ | $\begin{matrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{matrix}$ | $\begin{matrix} \frac{\Delta h}{h_{21}} & \frac{h_{11}}{h_{21}} \\ \frac{h_{22}}{h_{21}} & \frac{1}{h_{21}} \end{matrix}$ |
| [ABCD] | $\begin{matrix} \frac{A}{C} & \frac{\Delta ABCD}{C} \\ \frac{1}{C} & \frac{D}{C} \end{matrix}$ | $\begin{matrix} \frac{D}{B} & \frac{\Delta ABCD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{matrix}$ | $\begin{matrix} \frac{B}{D} & \frac{\Delta ABCD}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{matrix}$ | $\begin{matrix} A & B \\ C & D \end{matrix}$ |

determinant

S-parametre

- 2-port benyttes for definisjon av S-parametre
- **”Power waves”** defineres som

$$a_n = \frac{1}{2\sqrt{Z_0}}(V_n + Z_0 I_n) \quad (4.36a)$$

$$b_n = \frac{1}{2\sqrt{Z_0}}(V_n - Z_0 I_n) \quad (4.36b)$$

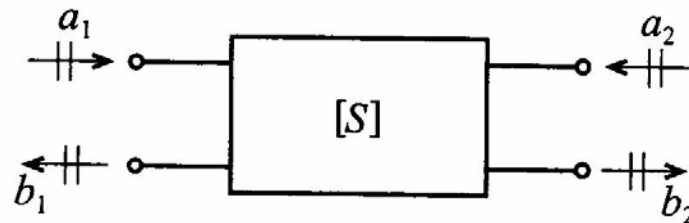


Figure 4-14 Convention used to define S-parameters for a two-port network.


Definisjon av S-parametrene

- Beregninger viser at effekten (power) blir:


$$P_n = \frac{1}{2} \operatorname{Re}\{V_n I_n^*\} = \frac{1}{2} (|a_n|^2 - |b_n|^2)$$

S-parametre
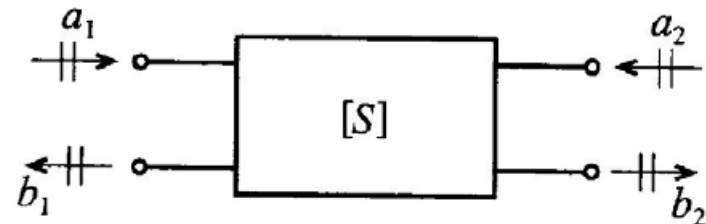
$$\begin{Bmatrix} b_1 \\ b_2 \end{Bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{Bmatrix} a_1 \\ a_2 \end{Bmatrix}$$



Hva hver enkelt S-parameter betyr

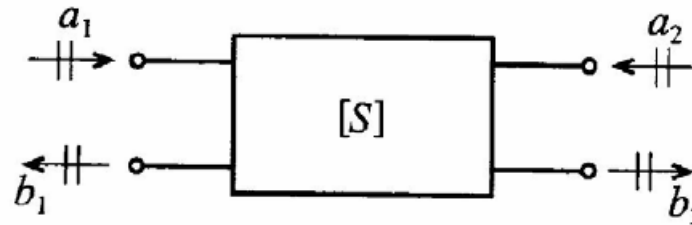

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \equiv \frac{\text{reflected power wave at port 1}}{\text{incident power wave at port 1}} \quad (4.42a)$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \equiv \frac{\text{transmitted power wave at port 2}}{\text{incident power wave at port 1}} \quad (4.42b)$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \equiv \frac{\text{reflected power wave at port 2}}{\text{incident power wave at port 2}} \quad (4.42c)$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \equiv \frac{\text{transmitted power wave at port 1}}{\text{incident power wave at port 2}} \quad (4.42d)$$

Måling av S-parametre

- S-parametrene måles når linjene er **terminert** med sin **karakteristiske impedans**

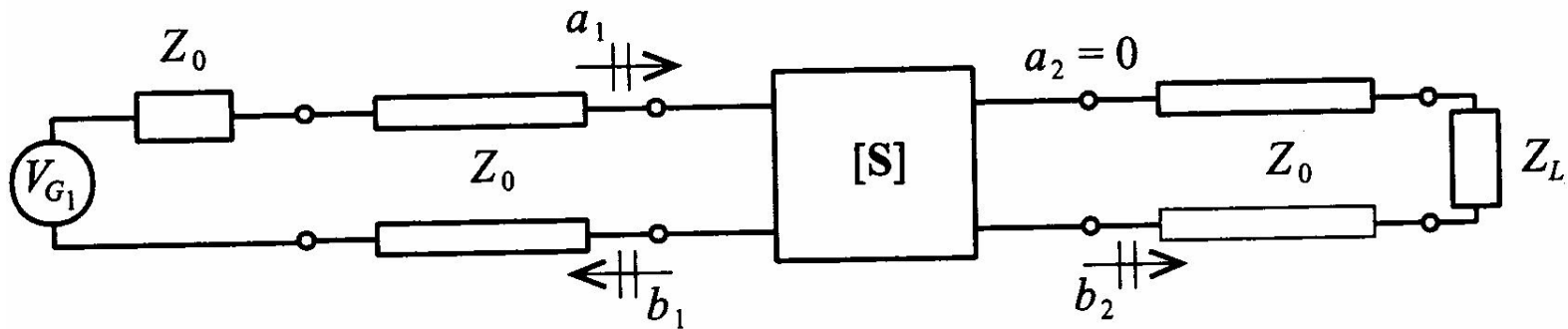


Figure 4-15 Measurement of S_{11} and S_{21} by matching the line impedance Z_0 at port 2 through a corresponding load impedance $Z_L = Z_0$.

Filtre

- Ulike filtertyper

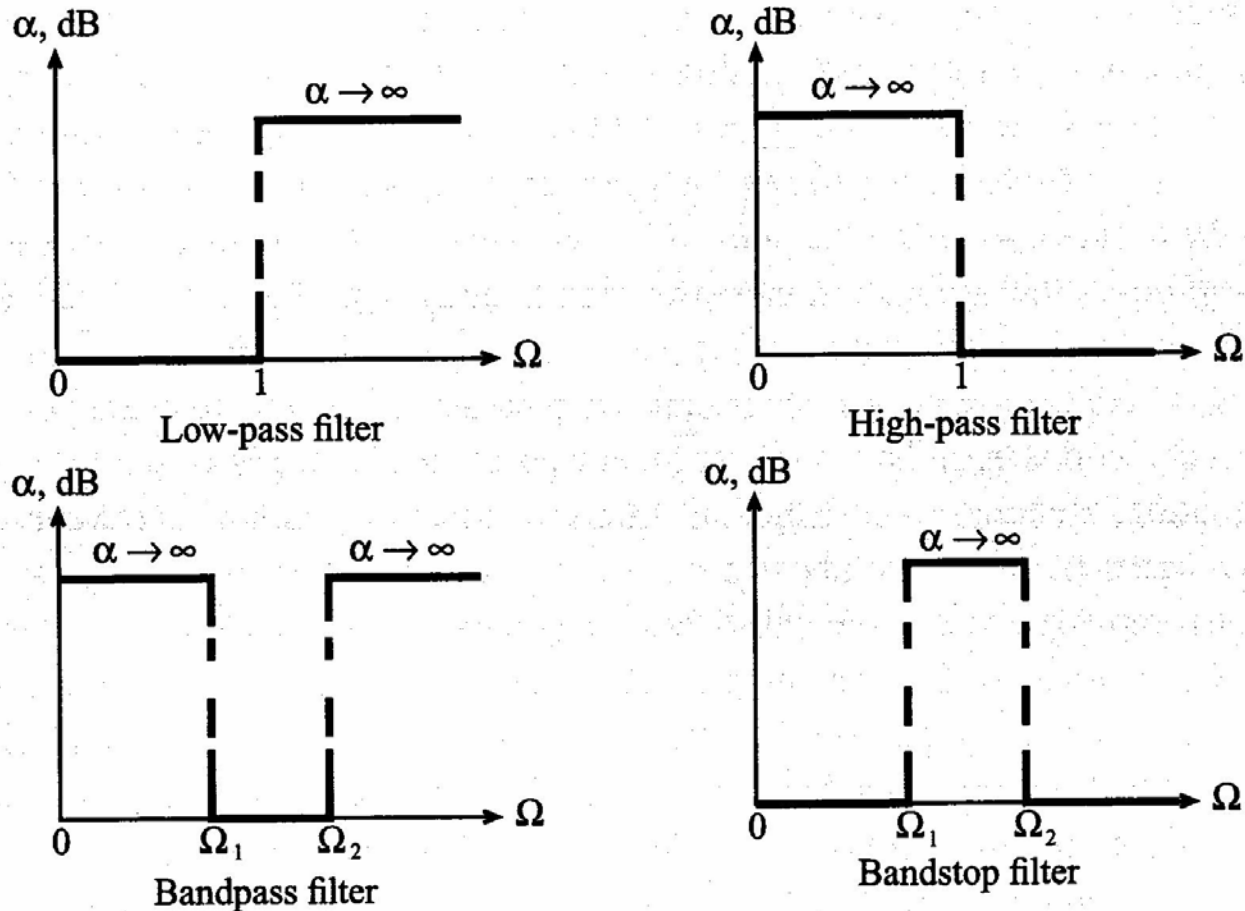


Figure 5-1 Four basic filter types.

Eks. på 3 ulike filtertyper

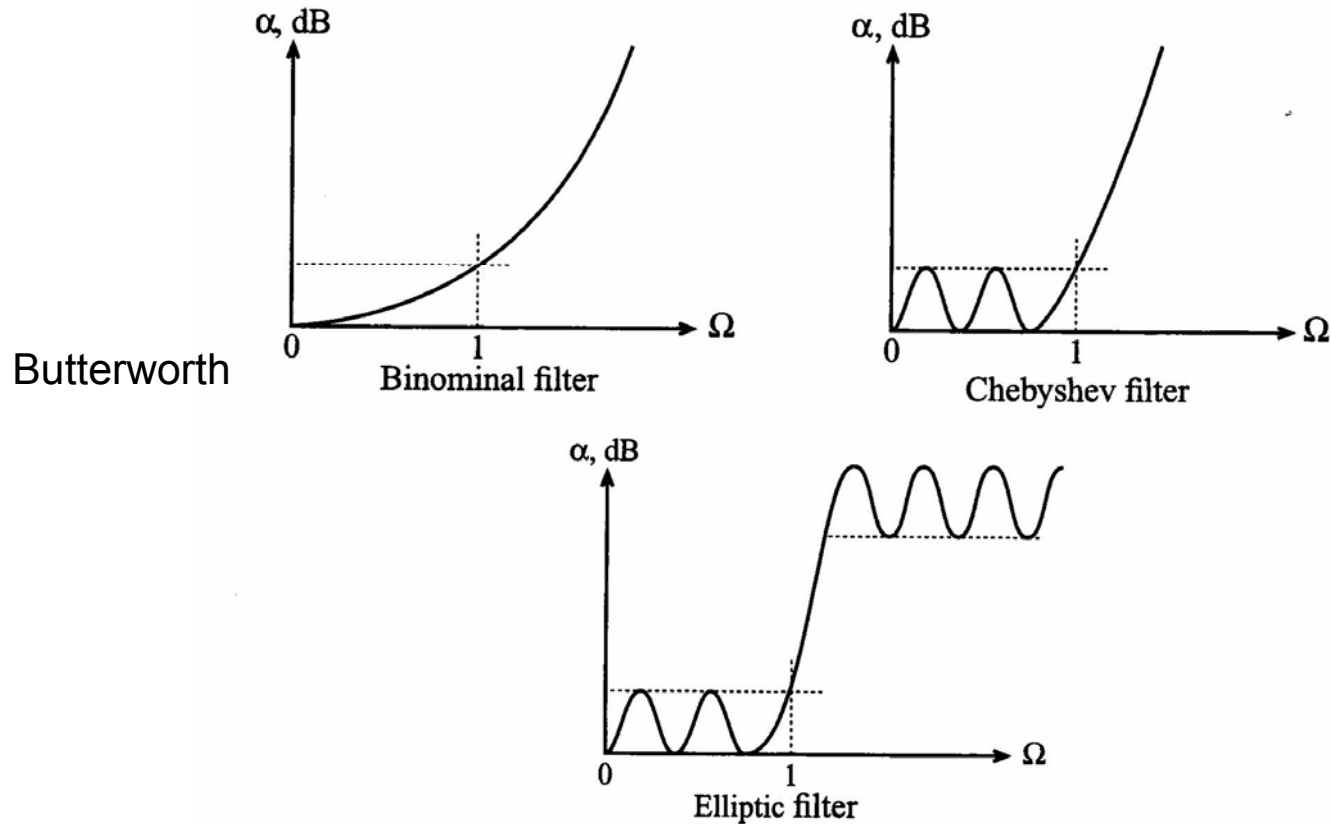


Figure 5-2 Actual attenuation profile for three types of low-pass filters.

Ulike betegnelser, begreper

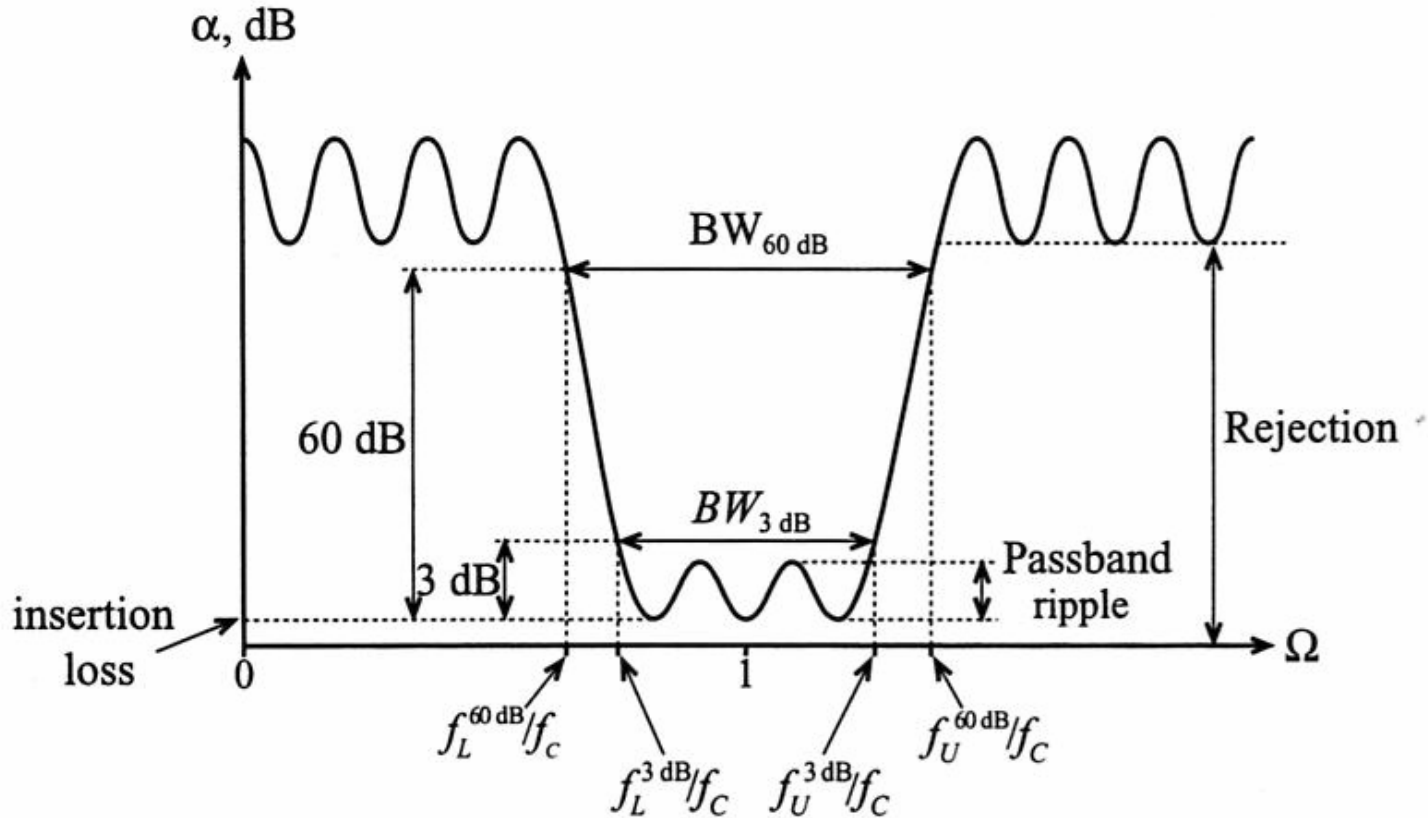


Figure 5-3 Generic attenuation profile for a bandpass filter.

Q-faktor

- Definisjon av **Q-faktor**

$$Q = \omega \left. \frac{\text{average stored energy}}{\text{energy loss per cycle}} \right|_{\omega = \omega_c} = \omega \left. \frac{\text{average stored energy}}{\text{power loss}} \right|_{\omega = \omega_c} = \omega \left. \frac{W_{\text{stored}}}{P_{\text{loss}}} \right|_{\omega = \omega_c} \quad (5.4)$$

- Det finnes ulike definisjoner av Q-faktor
 - Definisjonene er ekvivalente

$$Q_{LD} = \frac{f_c}{f_U^{3\text{dB}} - f_L^{3\text{dB}}} \equiv \frac{f_c}{BW^{3\text{dB}}}$$

Unloaded – loaded Q

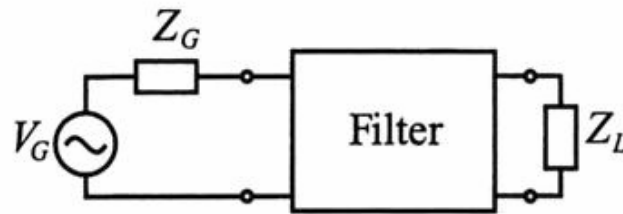


Figure 5-4 Filter as a two-port network connected to an RF source and load.

$$\frac{1}{Q_{LD}} = \frac{1}{\omega} \left(\frac{\text{power loss in filter}}{\text{average stored energy}} \right) \Bigg|_{\omega = \omega_r} + \frac{1}{\omega} \left(\frac{\text{power loss in load}}{\text{average stored energy}} \right) \Bigg|_{\omega = \omega_r} \quad (5.5)$$

$$\frac{1}{Q_{LD}} = \frac{1}{Q_F} + \frac{1}{Q_E}$$

Hva Q-faktoren betyr i praksis for stabilitet

Achieving High Oscillator Stability

Frequency-Selective Tank Element

$0^\circ - \Delta\theta$
 $0^\circ + \Delta\theta$

v_o

T_o

Low-Q

Q=10

(e.g. LC or ring oscillators)

$\Delta f = 400 \text{ kHz}$

$\Delta\theta = 40^\circ$

High-Q

Q=1000

(e.g. crystal oscillators)

$\Delta f = 4 \text{ kHz}$

$\Delta\theta = 40^\circ$

Amplitude [dB]

Phase [deg]

Freq. [MHz]

Freq. [MHz]

• High tank **Q** ⇒ high frequency stability

C. T.-C. Nguyen

Univ. of Michigan