

# INF 5490 RF MEMS

## **LN04: RF circuit design challenges**

Spring 2011, Oddvar Søråsen  
Department of Informatics, UoO

# Lecture overview INF5490

- Basic topics
  - LN01: Introduction. MEMS in RF
  - LN02: Fabrication
  - LN03: Modeling, design and analysis (part 1, 2 of 3)
- Main topic of today's lecture:
  - Modeling, 3: Analysis using **Finite Element Methods**
  - **Some characteristics and challenges of RF circuit design**

# References


- Supplementary literature ("cursory"):
- Finite Element Methods
  - <http://www.coventor.com/>
- RF circuit design
  - Reinhold Ludwig and Pavel Bretchko, " RF Circuit Design, Theory and Applications". Prentice Hall, 2000. ISBN 0-13-122475-1

# Methods for RF MEMS modeling

- 1. Simple mathematical modeling
- 2. Converting to electrical equivalents
- Why do we need Finite Element Methods analysis?
  - Simple mathematical models are **approximations**
  - Not accurate enough for complex structures
    - Ex. Beam deflection: non-uniform charge distribution  $\leftrightarrow$  force
- Tool for FEM-simulations
  - CoventorWare, CW
  - Used in Oblig1 and Oblig2
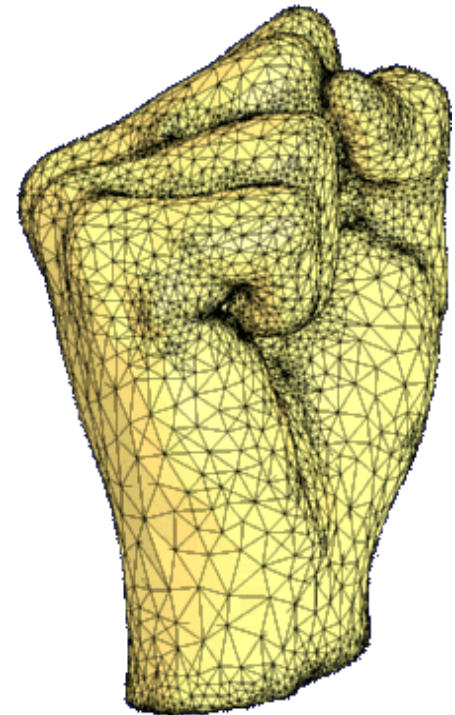
# 3. Finite Element Method analysis

- FEM characteristics
  - Build 3D model
  - **Mesh** the 3D model into smaller elements
  - Solve mathematical equations for interaction between elements
  - → Many iterations needed before a stable solution is obtained
- Features
  - + Good precision
  - + Coupled electrostatic/ mech. interaction
  - + Can cope with irregular topologies
  - - Insight into parameters influence is lost
  - - Only small parts are practical
- Critical issues
  - Proper system selection, building the 3D model
  - Partitioning (precision of meshing)
  - Simulation parameters



# Ex. 3D model building in CW: process specification




| Step | Action  | Type             | Layer Name | Material    | Thic... | Color    | Mask Name/<br>Polarity | Depth | Offset | Sidewall<br>Angle | Comment |
|------|---------|------------------|------------|-------------|---------|----------|------------------------|-------|--------|-------------------|---------|
| 0    | Base    |                  | Substrate  | SILICON     | 10.0    | blue     | GND                    |       |        |                   |         |
| 1    | Etch    | Back, Substr...  |            |             |         | cyan     | BETCH -                | 10.0  | 0.0    | 0.0               |         |
| 2    | Deposit | Stacked          | Layer1     | SILICON     | 0.01    | blue     |                        |       |        |                   |         |
| 3    | Deposit | Stacked          | Layer2     | SILICON     | 8.0     | blue     |                        |       |        |                   |         |
| 4    | Etch    | Front, Last L... |            |             |         | yellow   | NOWEL -                | 8.0   | 0.0    | 0.0               |         |
| 5    | Deposit | Planar           | Layer3     | SILICON     | 0.0     | yellow   |                        |       |        |                   |         |
| 6    | Etch    | Front, Partial   |            |             |         | white    | BUCON -                | 4.0   | 0.0    | 0.0               |         |
| 7    | Etch    | Front, Partial   |            |             |         | pink     | BURES -                | 1.0   | 0.0    | 0.0               |         |
| 8    | Deposit | Planar           | Layer4     | SILICON     | 0.0     | white    |                        |       |        |                   |         |
| 9    | Etch    | Front, Partial   |            |             |         | pink     | BURES -                | 1.0   | 0.0    | 0.0               |         |
| 10   | Deposit | Planar           | Layer5     | SILICON     | 0.0     | pink     |                        |       |        |                   |         |
| 11   | Deposit | Stacked          | Layer6     | SILICON     | 3.0     | green    |                        |       |        |                   |         |
| 12   | Etch    | Front, Last L... |            |             |         | oran...  | SUCON -                | 3.0   | 0.0    | 0.0               |         |
| 13   | Etch    | Front, Partial   |            |             |         | mag...   | SURES -                | 1.0   | 0.0    | 0.0               |         |
| 14   | Deposit | Planar           | Layer7     | SILICON     | 0.0     | oran...  |                        |       |        |                   |         |
| 15   | Etch    | Front, Partial   |            |             |         | mag...   | SURES -                | 1.0   | 0.0    | 0.0               |         |
| 16   | Deposit | Planar           | Layer8     | SILICON     | 0.0     | mag...   |                        |       |        |                   |         |
| 17   | Etch    | Front, By Depth  |            |             |         | lemo...  | NOSUR -                | 1.0   | 0.0    | 0.0               |         |
| 18   | Deposit | Planar           | Layer9     | SILICON     | 0.0     | gray     |                        |       |        |                   |         |
| 19   | Deposit | Stacked          | Layer10    | THERM_OXIDE | 2.0     | tan      |                        |       |        |                   |         |
| 20   | Etch    | Front, Last L... |            |             |         | dodg...  | COHOL -                | 2.0   | 0.0    | 0.0               |         |
| 21   | Etch    | Front, Last L... |            |             |         | light... | NOBOA -                | 2.0   | 0.0    | 0.0               |         |
| 22   | Deposit | Conformal        | Layer11    | ALUMINUM    | 1.0 ... | red      |                        |       |        |                   |         |
| 23   | Etch    | Front, Last L... |            |             |         | red      | MCOND +                | 1.0   | 0.0    | 0.0               |         |


- Specify a **process file** which matches an actual foundry process
  - simplifications
  - realistic: essential process features included
- → **pseudo layers**

# 3D model building: layout

Make accompanying  
**layout**

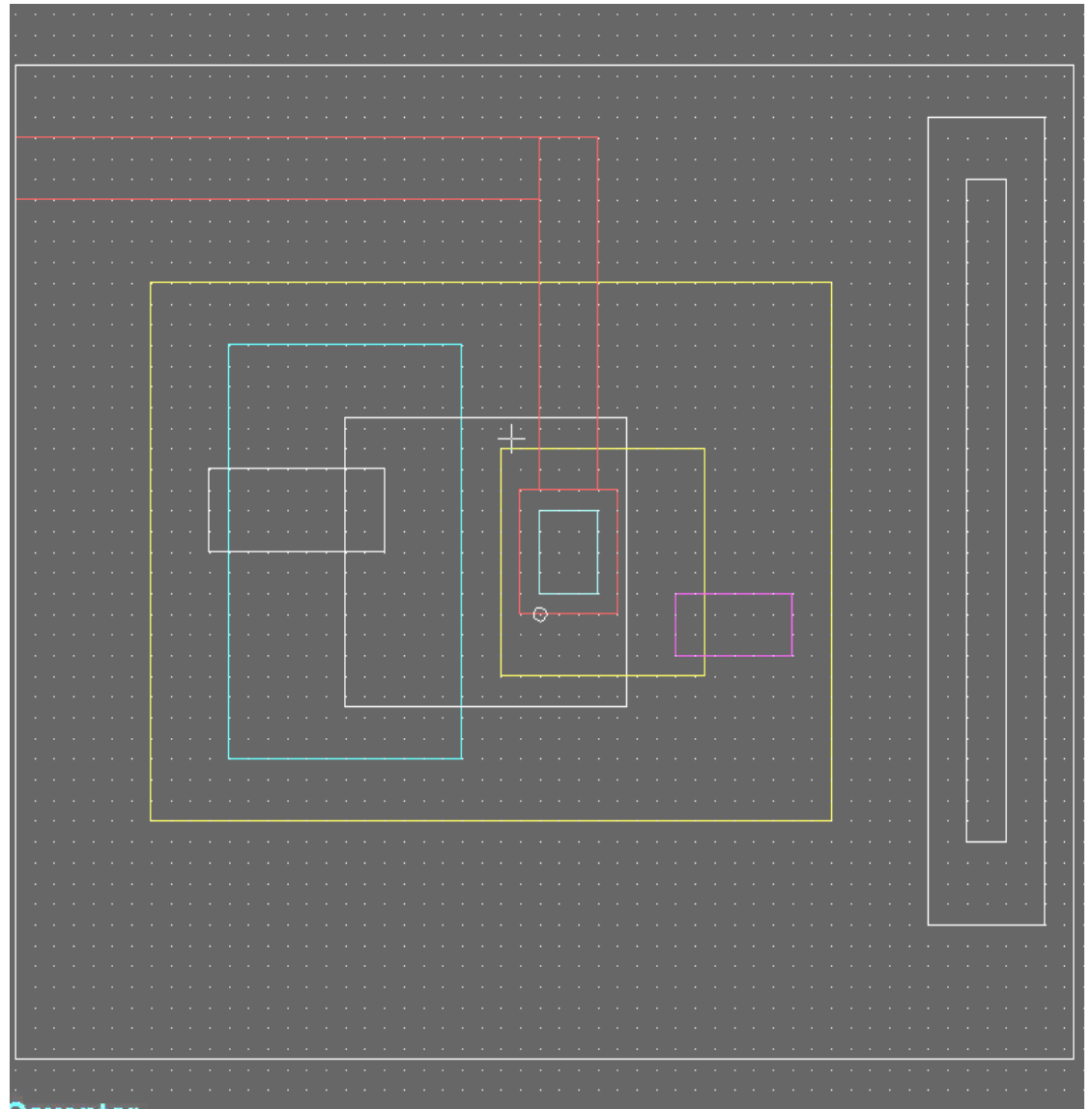


# MultiMEMS, typical features

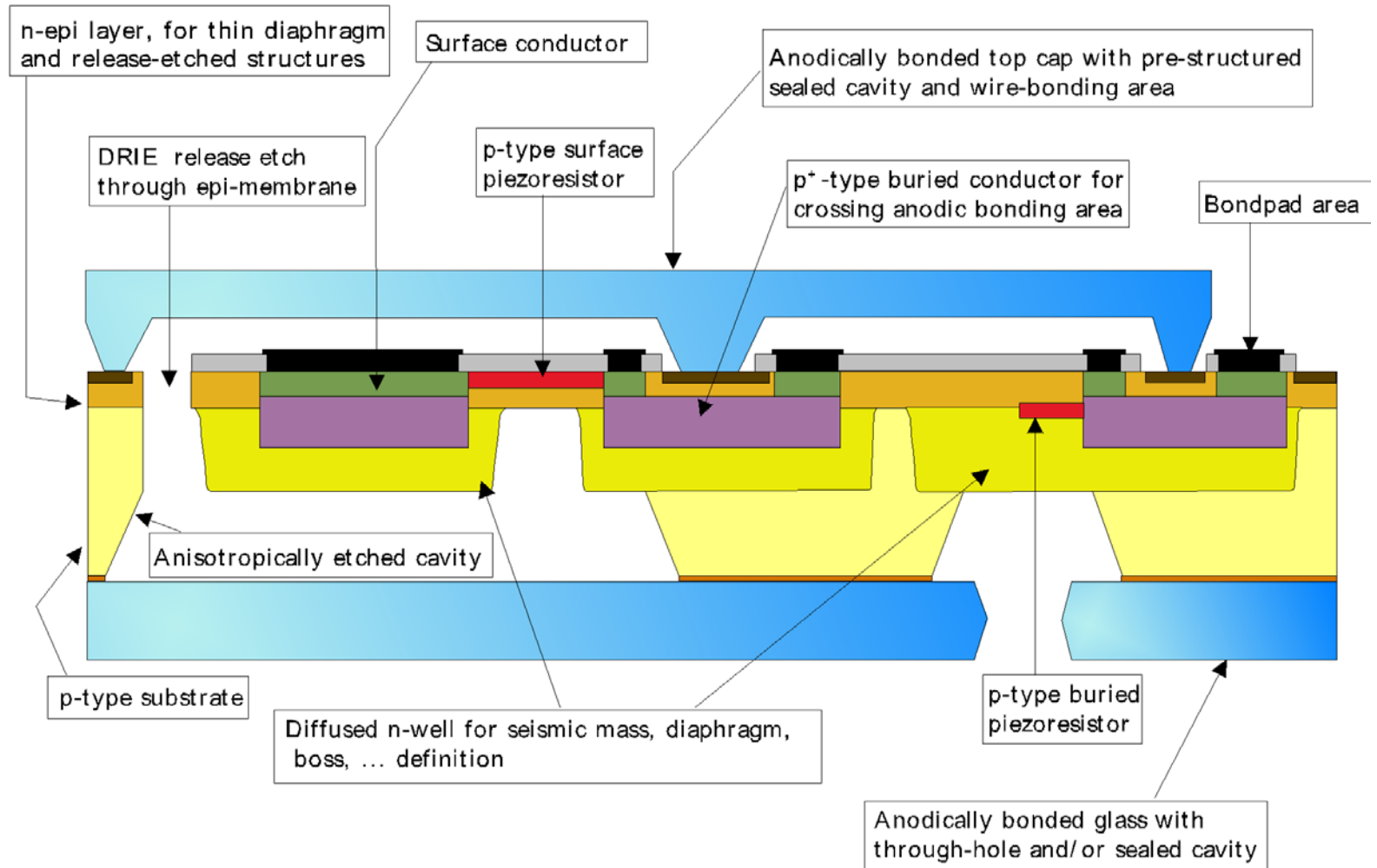



# How to model the MultiMEMS bulk process in CoventorWare?

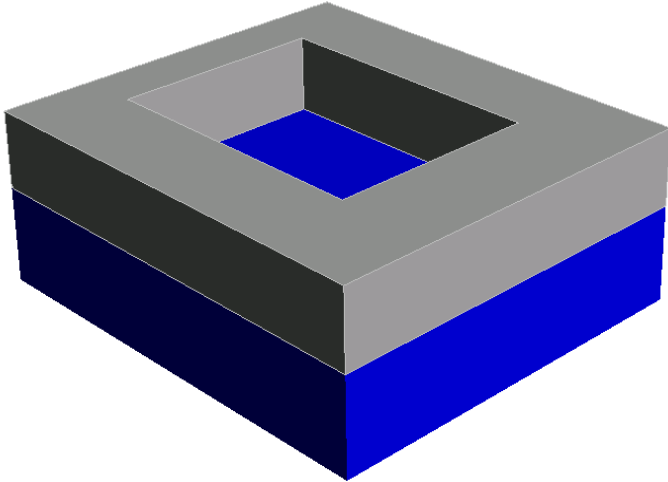- Problem:
  - The bulk process is not based on “stacking layers”
- Create a **pseudo process!**
  - Simplified, but matching
  - Transfer to a procedure of **stacking (pseudo) layers**
    - some layers with zero spacing
    - slicing the bulk material into sub-layers **in contact**
    - make etchings and re-fillings




ProcessEditor: M:\Design\_Files\testproject1\Devices\layers\_c.proc

File Edit View Help

| Step | Action  | Type             | Layer Name | Material | Thic... | Color  | Mask Name/<br>Polarity | Depth  | Offset | Sidewall<br>Angle | Comment |
|------|---------|------------------|------------|----------|---------|--------|------------------------|--------|--------|-------------------|---------|
| 0    | Base    |                  | Substrate  | SILICON  | 10.0    | blue   | GND                    |        |        |                   |         |
| 1    | Etch    | Back, Substr...  |            |          |         | cyan   | BETCH                  | - 10.0 | 0.0    | 0.0               |         |
| 2    | Deposit | Stacked          | Layer1     | SILICON  | 0.01    | blue   |                        |        |        |                   |         |
| 3    | Deposit | Stacked          | Layer2     | SILICON  | 8.0     | blue   |                        |        |        |                   |         |
| 4    | Etch    | Front, Last L... |            |          |         | yellow | NOWEL                  | - 8.0  | 0.0    | 0.0               |         |

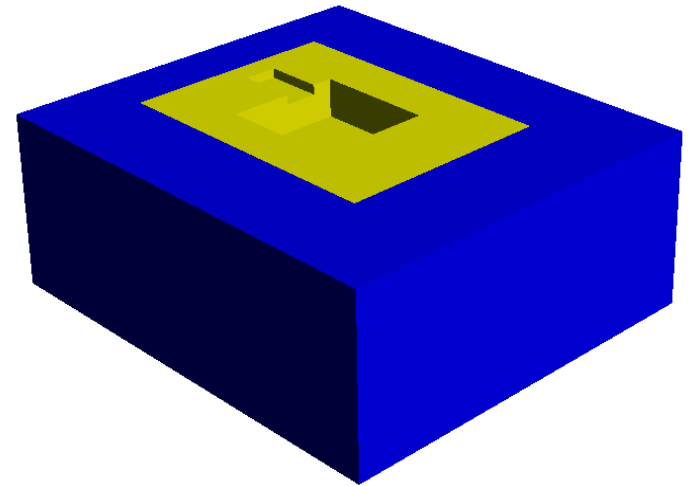Two slices of the base material stacked. **N-well** opening



ProcessEditor: M:\Design\_Files\testproject1\Devices\layers\_c.proc

File Edit View Help

↑ ↓ [Color icons] [ENABLE/DISABLE] [X] [?]

| Step | Action  | Type             | Layer Name | Material | Thic... | Color  | Mask Name/<br>Polarity | Depth | Offset | Sidewall<br>Angle | Comment |
|------|---------|------------------|------------|----------|---------|--------|------------------------|-------|--------|-------------------|---------|
| 0    | Base    |                  | Substrate  | SILICON  | 10.0    | blue   | GND                    |       |        |                   |         |
| 1    | Etch    | Back, Substr...  |            | SILICON  |         | cyan   | BETCH -                | 10.0  | 0.0    | 0.0               |         |
| 2    | Deposit | Stacked          | Layer1     | SILICON  | 0.01    | blue   |                        |       |        |                   |         |
| 3    | Deposit | Stacked          | Layer2     | SILICON  | 8.0     | blue   |                        |       |        |                   |         |
| 4    | Etch    | Front, Last L... |            |          |         | yellow | NOWEL -                | 8.0   | 0.0    | 0.0               |         |
| 5    | Deposit | Planar           | Layer3     | SILICON  | 0.0     | yellow |                        |       |        |                   |         |
| 6    | Etch    | Front, Partial   |            |          |         | white  | BUCON -                | 4.0   | 0.0    | 0.0               |         |
| 7    | Etch    | Front, Partial   |            |          |         | pink   | BURES -                | 1.0   | 0.0    | 0.0               |         |


**N-well** in-filling. Etching holes for **buried conductor** implant and **buried resistor** implant

ProcessEditor: M:\Design\_Files\testproject1\Devices\layers\_c.proc


File Edit View Help

↑ ↓ [Color Swatches] [ENABLE/DISABLE] [Close] [Help]


| Step | Action  | Type             | Layer Name | Material | Thic... | Color   | Mask Name/<br>Polarity | Depth | Offset | Sidewall<br>Angle | Comment |
|------|---------|------------------|------------|----------|---------|---------|------------------------|-------|--------|-------------------|---------|
| 0    | Base    |                  | Substrate  | SILICON  | 10.0    | blue    | GND                    |       |        |                   |         |
| 1    | Etch    | Back, Substr...  |            |          |         | cyan    | BETCH -                | 10.0  | 0.0    | 0.0               |         |
| 2    | Deposit | Stacked          | Layer1     | SILICON  | 0.01    | blue    |                        |       |        |                   |         |
| 3    | Deposit | Stacked          | Layer2     | SILICON  | 8.0     | blue    |                        |       |        |                   |         |
| 4    | Etch    | Front, Last L... |            |          |         | yellow  | NOWEL -                | 8.0   | 0.0    | 0.0               |         |
| 5    | Deposit | Planar           | Layer3     | SILICON  | 0.0     | yellow  |                        |       |        |                   |         |
| 6    | Etch    | Front, Partial   |            |          |         | white   | BUCON -                | 4.0   | 0.0    | 0.0               |         |
| 7    | Etch    | Front, Partial   |            |          |         | pink    | BURES -                | 1.0   | 0.0    | 0.0               |         |
| 8    | Deposit | Planar           | Layer4     | SILICON  | 0.0     | white   |                        |       |        |                   |         |
| 9    | Etch    | Front, Partial   |            |          |         | pink    | BURES -                | 1.0   | 0.0    | 0.0               |         |
| 10   | Deposit | Planar           | Layer5     | SILICON  | 0.0     | pink    |                        |       |        |                   |         |
| 11   | Deposit | Stacked          | Layer6     | SILICON  | 3.0     | green   |                        |       |        |                   |         |
| 12   | Etch    | Front, Last L... |            |          |         | oran... | SUCON -                | 3.0   | 0.0    | 0.0               |         |
| 13   | Etch    | Front, Partial   |            |          |         | mag...  | SURES -                | 1.0   | 0.0    | 0.0               |         |
| 14   | Deposit | Planar           | Layer7     | SILICON  | 0.0     | oran... |                        |       |        |                   |         |
| 15   | Etch    | Front, Partial   |            |          |         | mag...  | SURES -                | 1.0   | 0.0    | 0.0               |         |
| 16   | Deposit | Planar           | Layer8     | SILICON  | 0.0     | mag...  |                        |       |        |                   |         |
| 17   | Etch    | Front, By Depth  |            |          |         | lemo... | NOSUR -                | 1.0   | 0.0    | 0.0               |         |

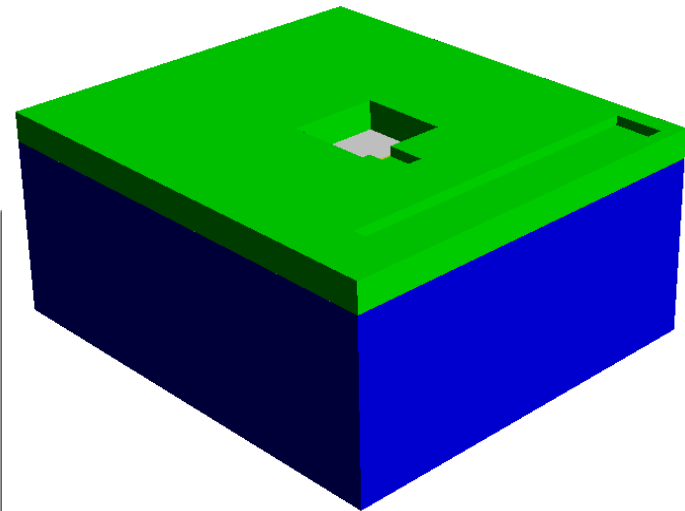

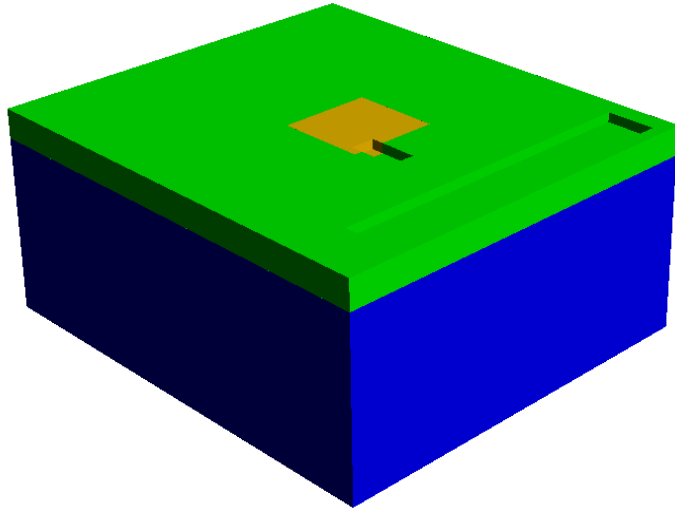Add **epi-layer**. Etch holes for **surface conductor** and **surface resistor**, -fill in.  
Etch hole for n+ implant. (Implants are invisible)




**Surface conductor** is made visible

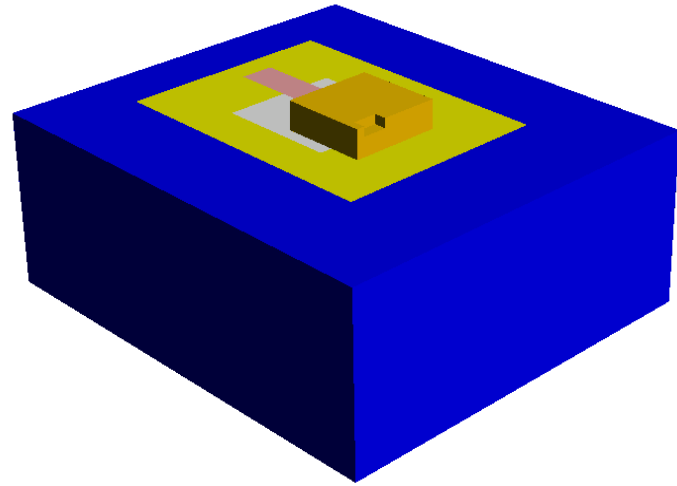


**Epi-layer** is invisible

# 3D model building: expansion

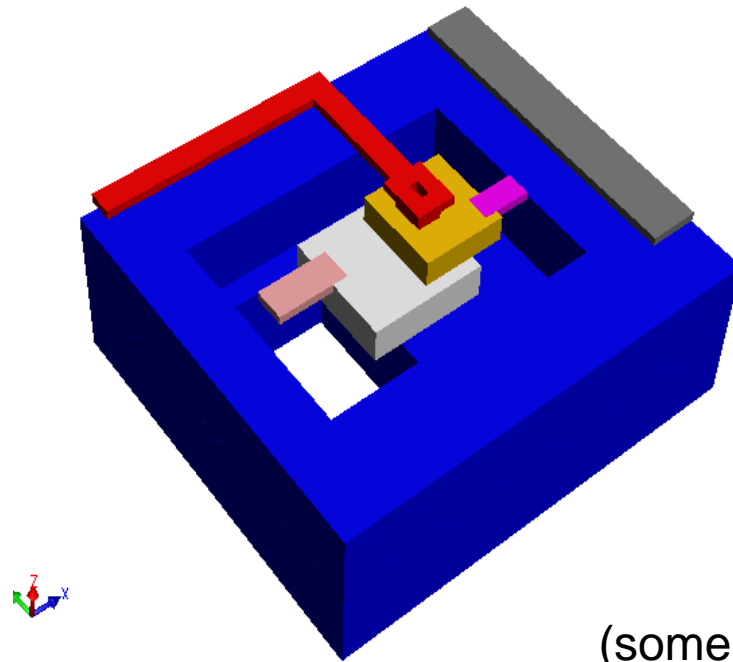

(some layers invisible)

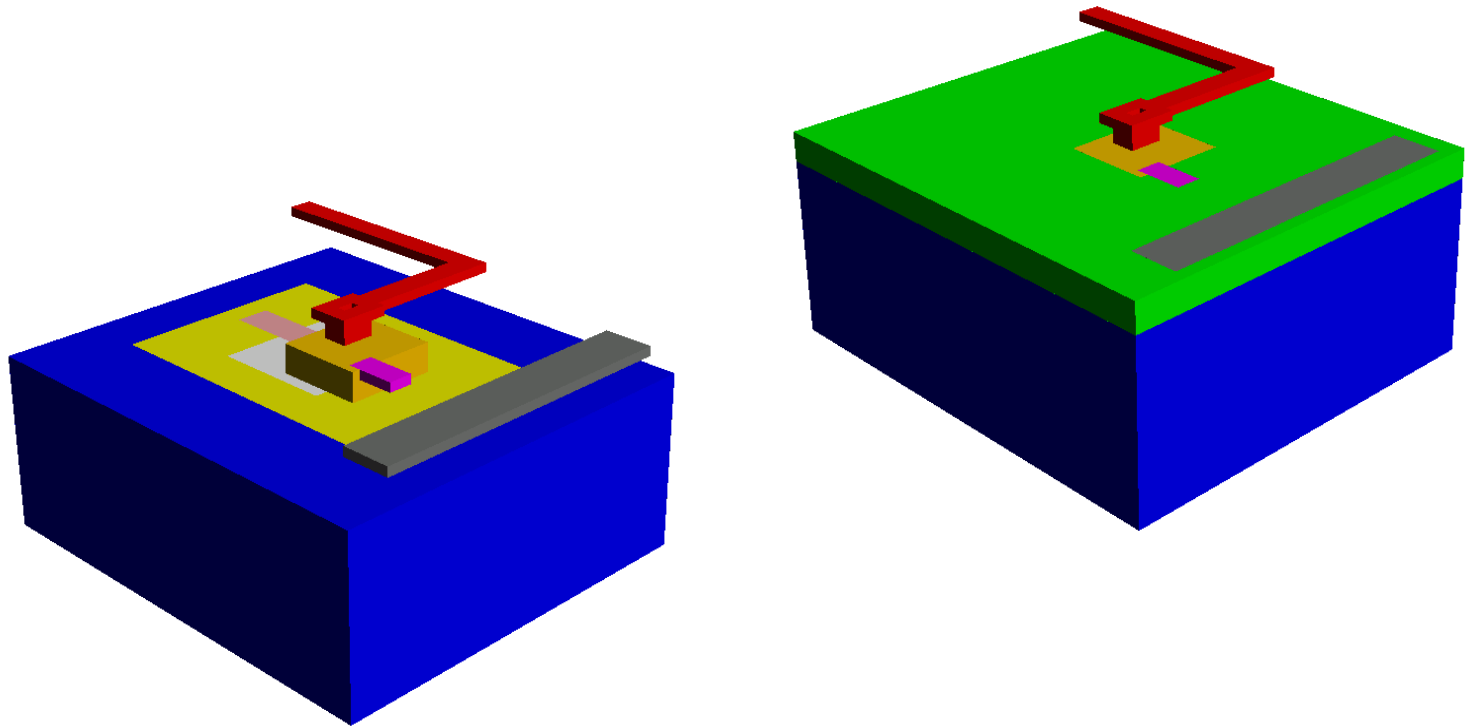


**Complete structure with some layers made invisible**

# 3D modeling procedure

- To introduce one diffusion:
  - Etch base material
  - Fill in implanted material
    - use “**deposit planar**” with **thickness = 0**
- To introduce multiple overlapping diffusions:
  - Etch base material with all (overlapping) diffusion masks (the deepest first)
  - Fill in the deepest implanted material
  - Re-etch the remaining diffusion openings
  - Fill in the next deepest implant etc.




# Meshed model

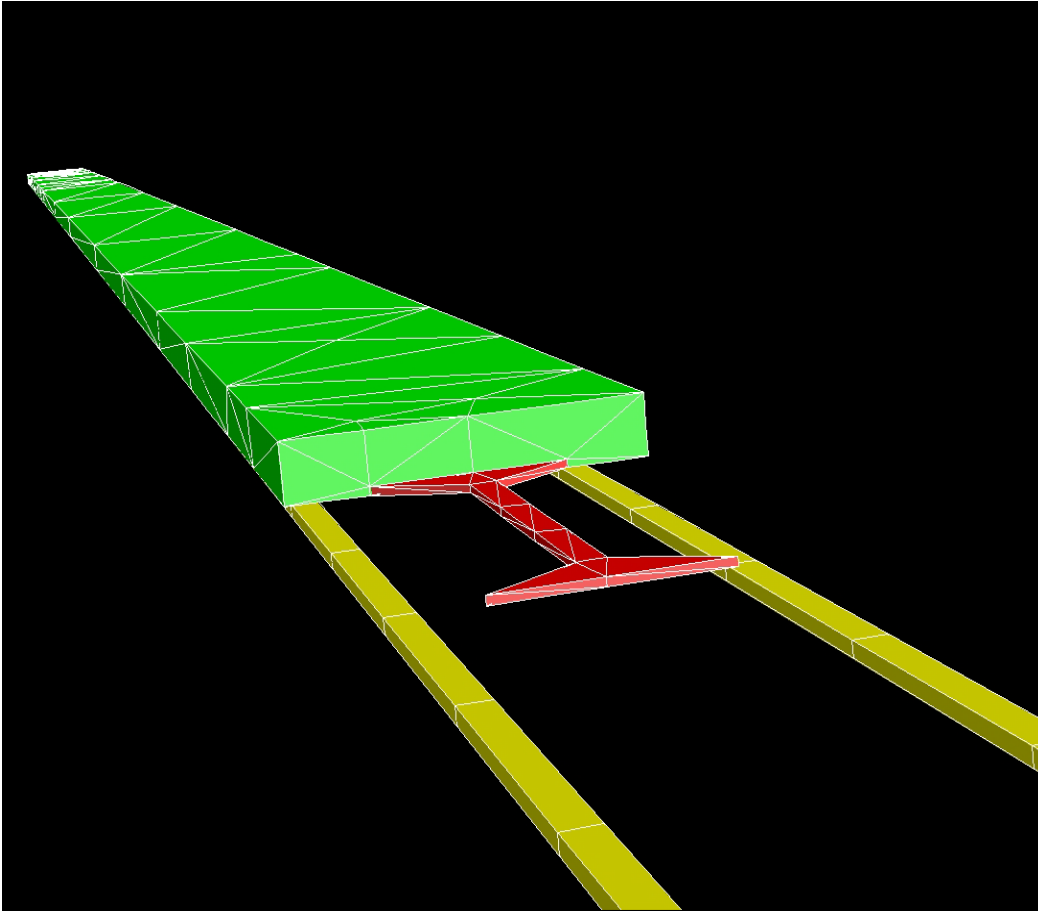


- Mirror meshed by tetrahedrons
  - 23  $\mu\text{m}$ , 3  $\mu\text{m}$
- Electrodes meshed by Manhattan bricks
  - 5  $\mu\text{m}$
- Rather coarse dimensions used due to time consuming **pull-in** analysis in CW

# Mirror deflection, snapshot

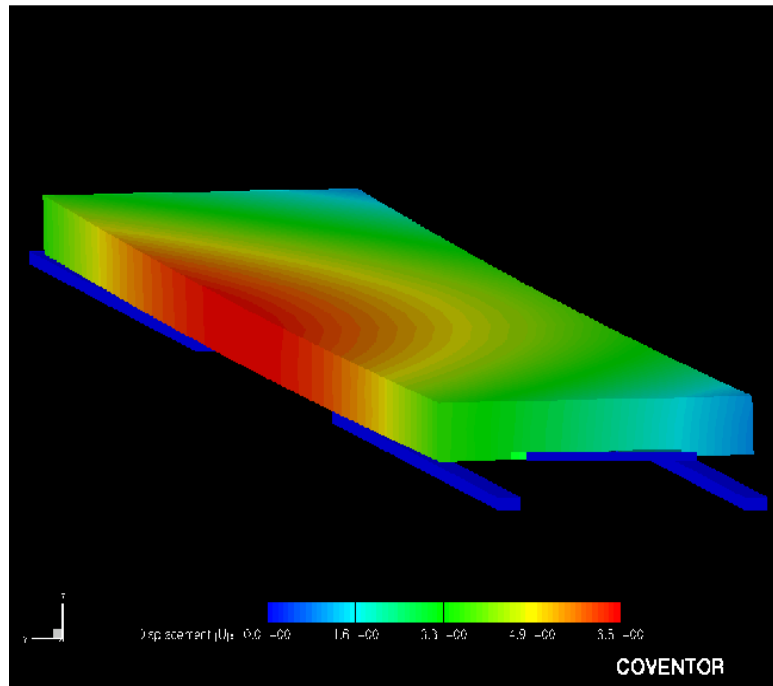

# Simulation: pull-in

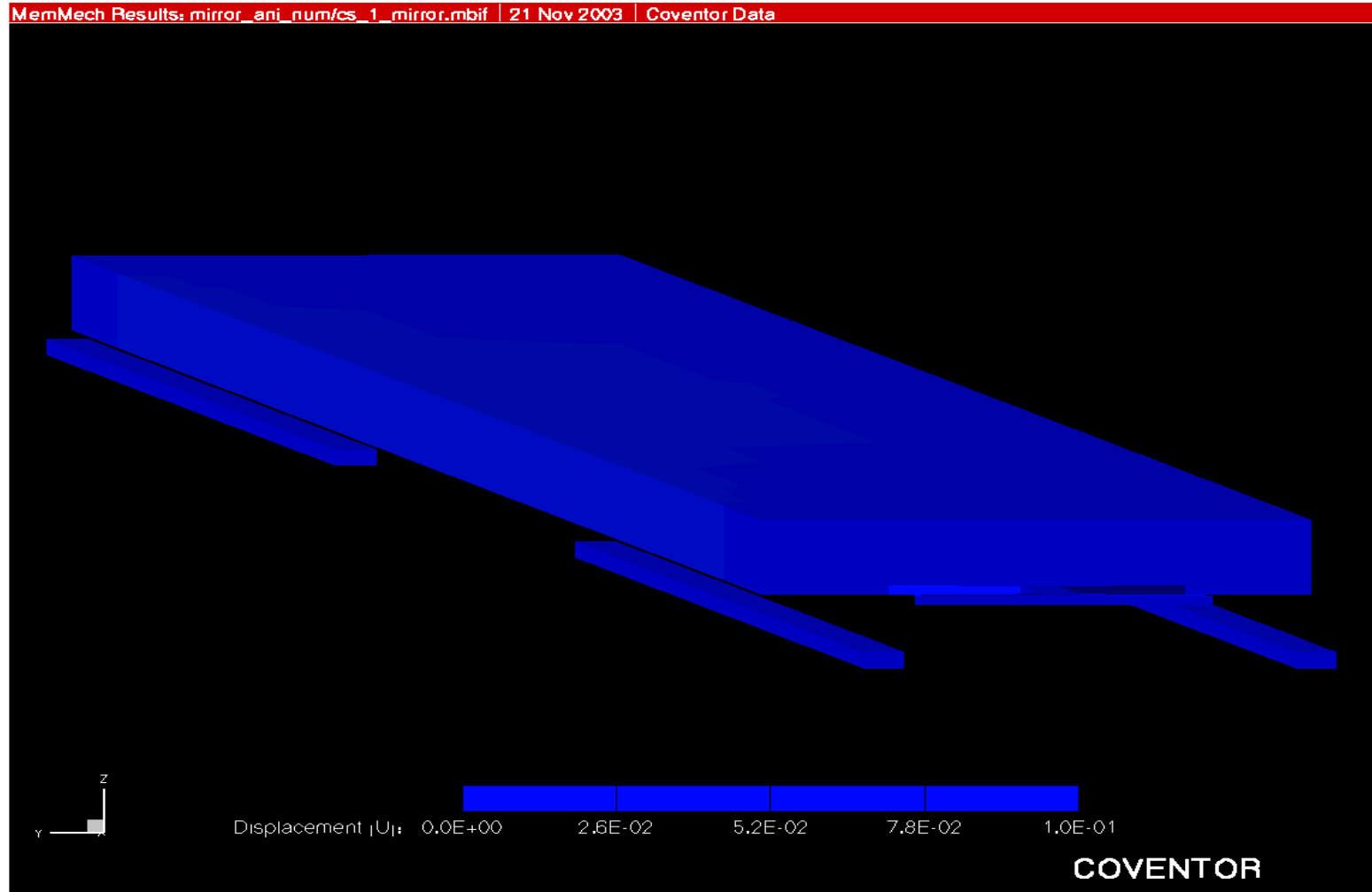

# Today's lecture

- Modeling: 3. Finite Element Method analysis
- **RF circuit design**
  - → "Multi disciplinary"
  - Electromagnetic waves
  - Skin depth
  - Passive components at high frequencies
  - Transmission line theory
  - Two-port networks
    - S-parameters
  - Filters
  - Q-factor

# RF- and microwave design is multi disciplinary


- **Theoretical** fundament
  - Electromagnetism, electromagnetic waves
  - Signal processing
- **Technology**, practical aspects
  - Circuit theory
  - Kirchhoff's laws for current and voltage
- Some topics of today's lecture is also covered in INF5480
  - "RF-circuits, theory and design" (Tor Fjeldly, fall semester)
- INF5490/9490:
  - → **Central issues covered in one lecture!**

# RF circuit design

- Some important questions
  - How do circuits behave at high frequencies?
  - Why do component functionality change?
  - At what frequencies is standard circuit analysis not valid?
  - What “new” circuit theory is needed?
  - How can this theory come into practical use?
    - → *Figures and equations from R. Ludwig et al: "RF Circuit Design"*

# Electromagnetic waves

- Electric and magnetic fields

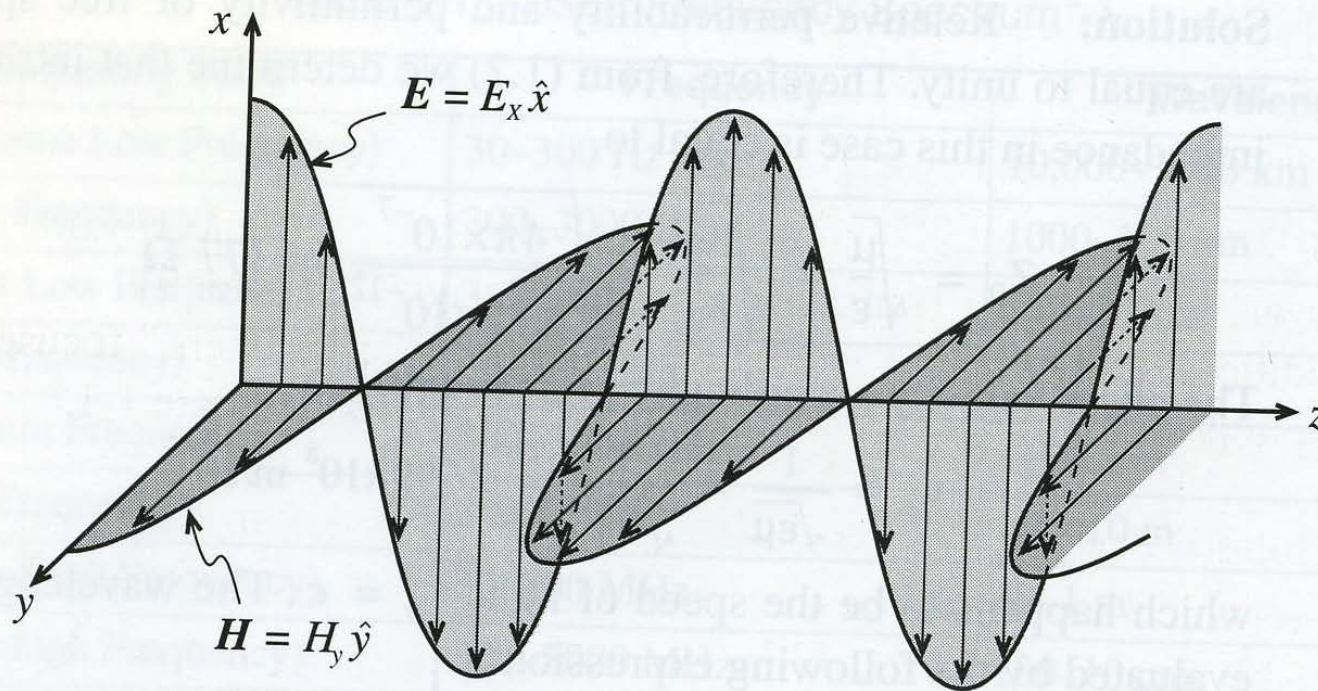

**Figure 1-3** Electromagnetic wave propagation in free space. The electric and magnetic fields are recorded at a fixed instance in time as a function of space ( $\hat{x}$ ,  $\hat{y}$  are unit vectors in x- and y-direction).

# Important wave parameters:

Electric field  $E_x = E_{0x} \cos(\omega t - \beta z)$

Magnetic field  $H_y = H_{0y} \cos(\omega t - \beta z)$

Angular frequency:  $\omega$       Propagation constant:  $\beta$

Wave is periodic, repeating when:  $\beta \cdot z = 2\pi$

**Wavelength:**  $z = \lambda = \frac{2\pi}{\beta}$

The wave propagates a distance  $\lambda$  during the time  $T =$  period

**Propagation velocity:**  
(in vacuum:  $c$ )

$$v_p \cdot T = \lambda$$
$$v_p = \lambda \cdot \frac{1}{T} = \lambda \cdot f = \frac{2\pi}{\beta} \cdot \frac{\omega}{2\pi} = \frac{\omega}{\beta}$$



## Important wave parameters, contd.

For a position  $z = \text{constant}$ , the wave repeats after a period  $T$ :

$$\omega T = 2\pi \quad \text{and} \quad \omega = 2\pi / T = 2\pi f$$

in which  $f = \text{frequency}$

# Frequency and wavelength

- In vacuum:  $\lambda * f = c$ 
  - Increasing frequency  $\rightarrow$  decreasing wavelength
- At high frequencies (RF) is the wavelength comparable to the circuit dimensions
  - $\rightarrow$

**Table 1-1 IEEE Frequency Spectrum**

| <b>Frequency Band</b>        | <b>Frequency</b> | <b>Wavelength</b> |
|------------------------------|------------------|-------------------|
| ELF (Extreme Low Frequency)  | 30–300 Hz        | 10,000–1000 km    |
| VF (Voice Frequency)         | 300–3000 Hz      | 1000–100 km       |
| VLF (Very Low Frequency)     | 3–30 kHz         | 100–10 km         |
| LF (Low Frequency)           | 30–300 kHz       | 10–1 km           |
| MF (Medium Frequency)        | 300–3000 kHz     | 1–0.1 km          |
| HF (High Frequency)          | 3–30 MHz         | 100–10 m          |
| VHF (Very High Frequency)    | 30–300 MHz       | 10–1 m            |
| UHF (Ultrahigh Frequency)    | 300–3000 MHz     | 100–10 cm         |
| SHF (Superhigh Frequency)    | 3–30 GHz         | 10–1 cm           |
| EHF (Extreme High Frequency) | 30–300 GHz       | 1–0.1 cm          |
| Decimillimeter               | 300–3000 GHz     | 1–0.1 mm          |
| P Band                       | 0.23–1 GHz       | 130–30 cm         |
| L Band                       | 1–2 GHz          | 30–15 cm          |
| S Band                       | 2–4 GHz          | 15–7.5 cm         |
| C Band                       | 4–8 GHz          | 7.5–3.75 cm       |
| X Band                       | 8–12.5 GHz       | 3.75–2.4 cm       |
| Ku Band                      | 12.5–18 GHz      | 2.4–1.67 cm       |
| K Band                       | 18–26.5 GHz      | 1.67–1.13 cm      |
| Ka Band                      | 26.5–40 GHz      | 1.13–0.75 cm      |
| Millimeter wave              | 40–300 GHz       | 7.5–1 mm          |
| Submillimeter wave           | 300–3000 GHz     | 1–0.1 mm          |

# Two important laws

- **Faradays law**
  - Varying **magnetic field** induces **current**
- **Amperes law**
  - **Current** is setting up a **magnetic field**

# Faradays law

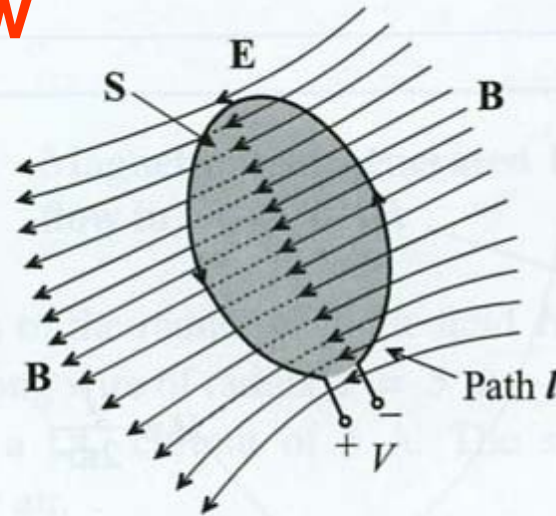


Figure 2-15 The time rate of change of the magnetic flux density induces a voltage.

$$\oint \bar{E} \cdot d\bar{l} = -\frac{d}{dt} \iint \bar{B} \cdot d\bar{S}$$


$\bar{B}$  = magnetic flux density

$$\bar{B} = \mu \cdot \bar{H}$$

$\mu$  = permeability =  $\mu_0 \cdot \mu_r$

$\bar{H}$  = magnetic field

# Amperes law

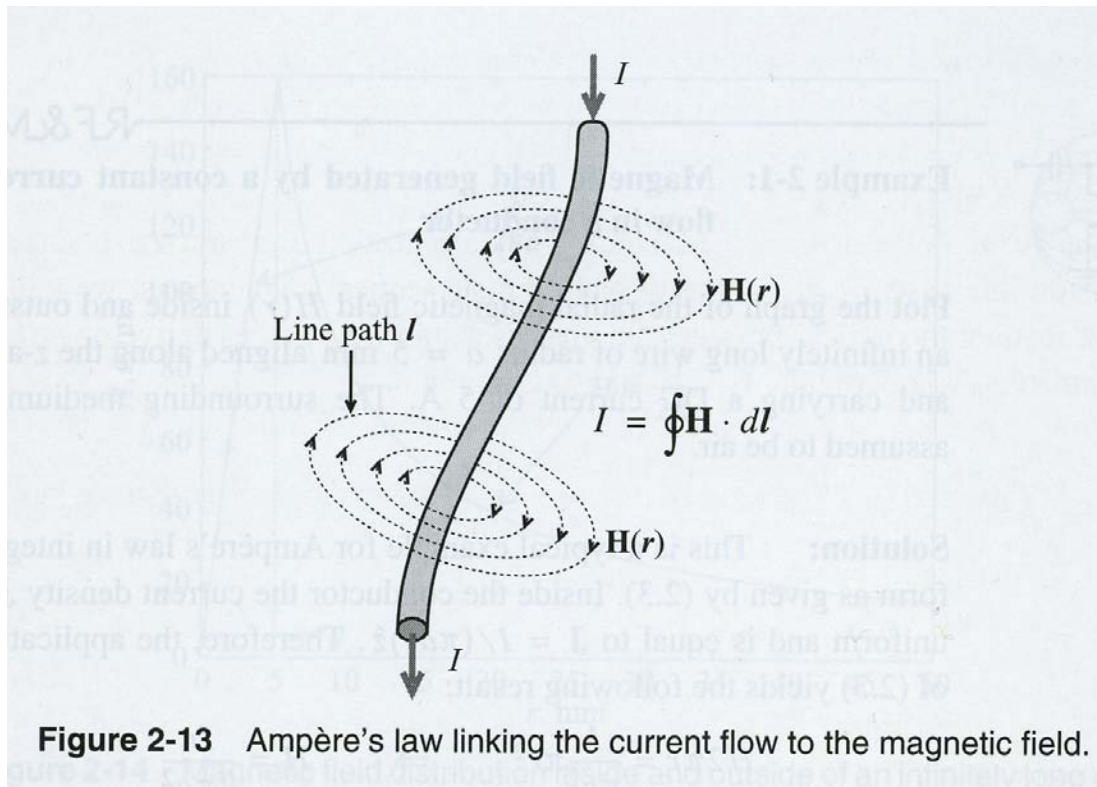


$$I = \oint \bar{H} \cdot d\bar{l} = \iint \bar{J} \cdot d\bar{S}$$

# ”Skin depth”

- Signal transmission at increasing frequency
  - **DC** signal:
    - Current is flowing in whole cross section
  - **AC** signal (sequence of arguments for the operation):
    - Varying current induces an alternating magnetic field (Amperes law)
    - Magnetic field strength higher for small radius
    - Increased time variation of magnetic field in centre
    - Varying magnetic field induces an electric field (Faradays law)
    - Induced electric field (opposing the original one) increases in strength towards the centre of the conductor

# Current density for various frequencies

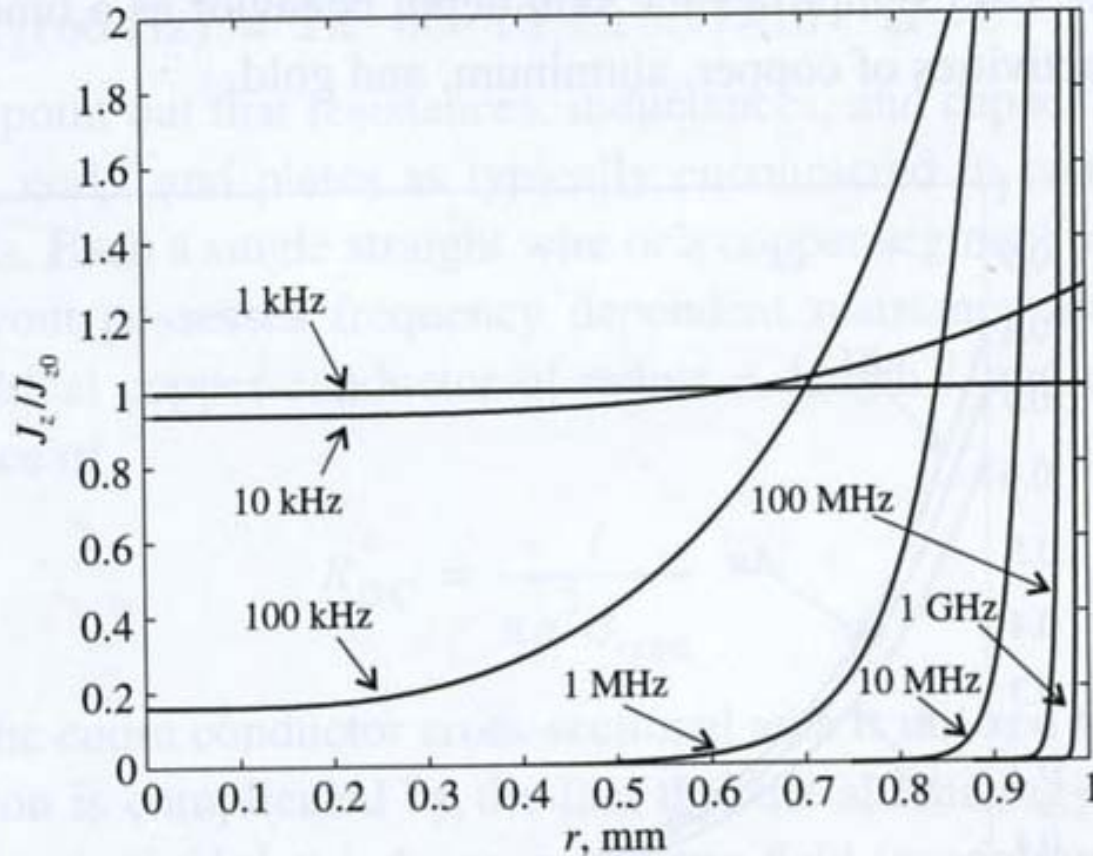


**Figure 1-5(b)** Frequency behavior of normalized AC current density for a copper wire of radius  $a = 1$  mm.



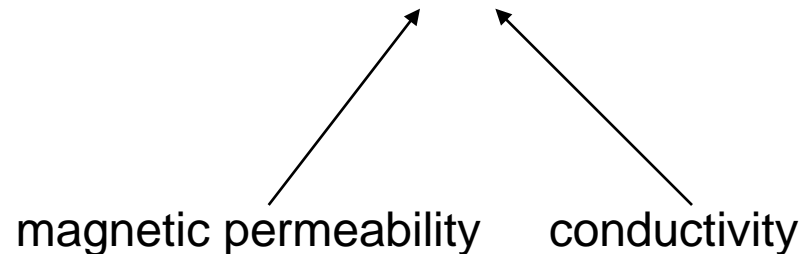
# Skin depth, contd.

- Resistance R increases towards centre of conductor
  - Current close to **surface** at increasing frequency
  - Formula: "skin-depth" →
    - Current density reduced by a factor 1/e
- What does this mean for practical designs? →

$$\delta = (\pi f \mu \sigma_{\text{cond}})^{-1/2}$$




# "Skin-depth"

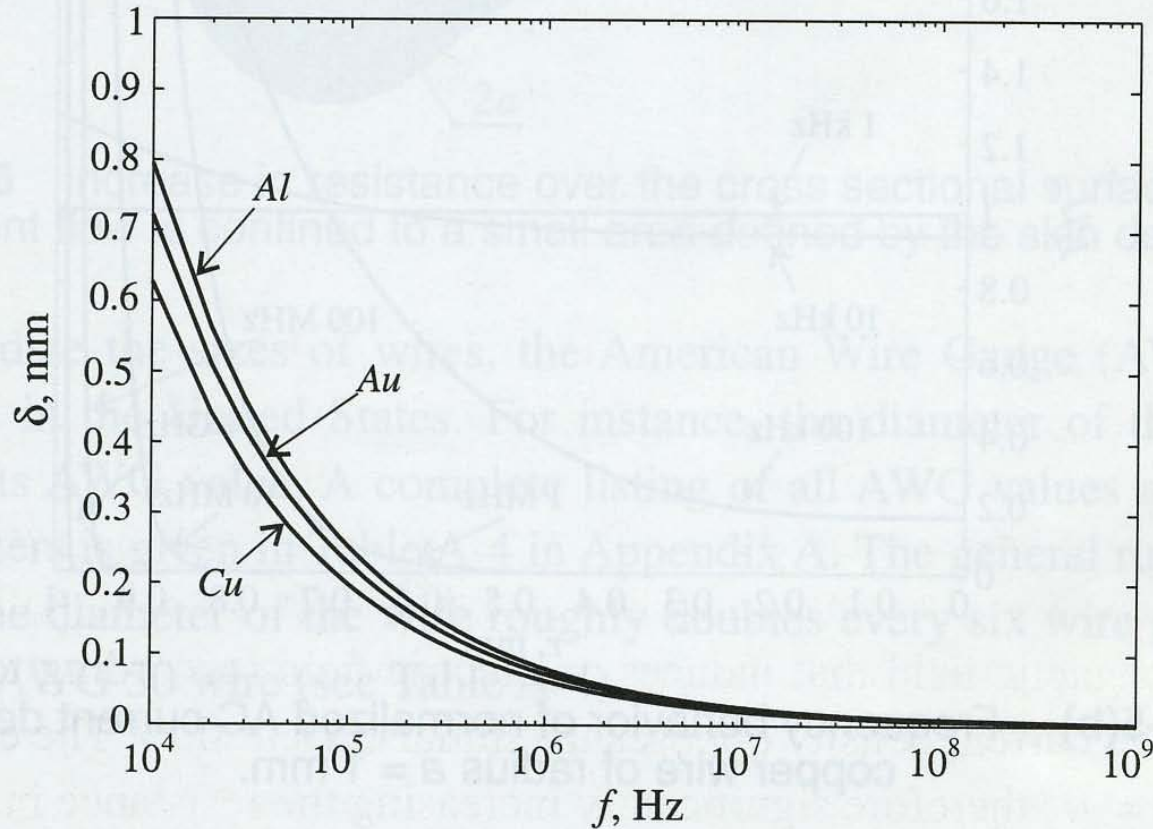

**Figure 1-4** Skin depth behavior of copper  $\sigma_{Cu} = 64.516 \times 10^6$  S/m, aluminum  $\sigma_{Al} = 40.0 \times 10^6$  S/m, and gold  $\sigma_{Au} = 48.544 \times 10^6$  S/m.

# Passive components at high frequencies


- Equivalent circuit diagram for resistor

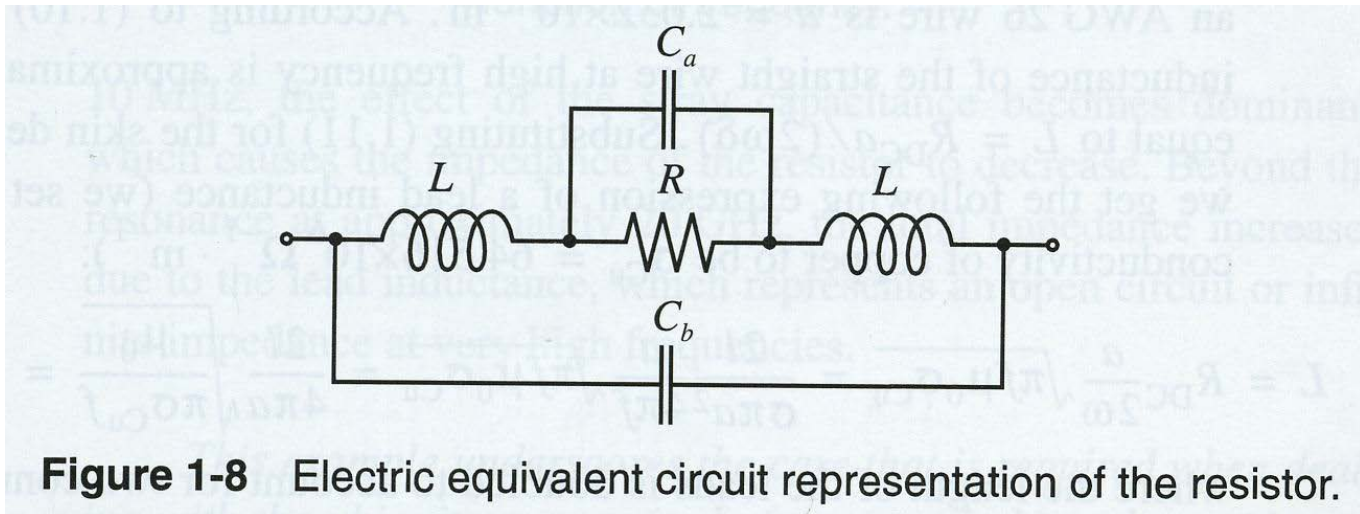

**Figure 1-8** Electric equivalent circuit representation of the resistor.

# Calculating resistor-impedance

Simplified model:

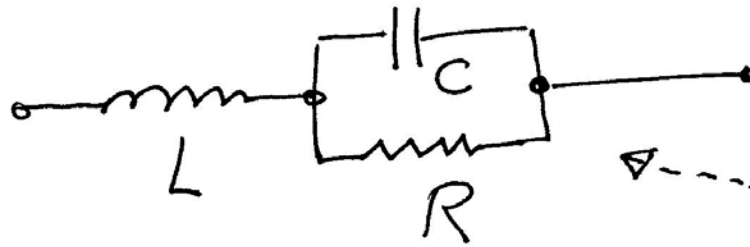


$$G = \frac{1}{R} + sC$$

$$z = sL + \frac{1}{\frac{1}{R} + sC} = sL + \frac{R}{1 + sRC}$$

$$z(j\omega) = j\omega L + \frac{R}{1 + j\omega RC}$$

# Impedance versus frequency

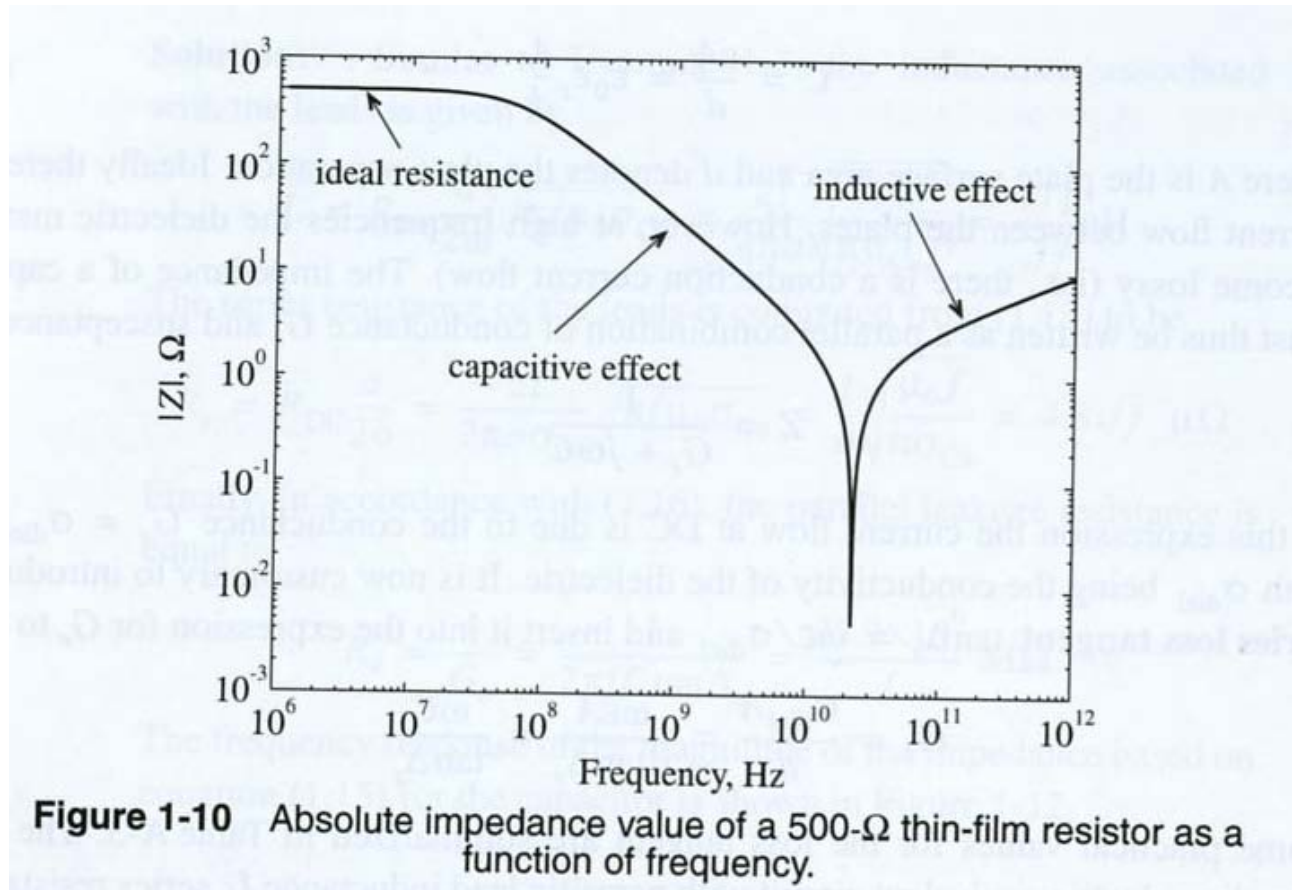

*Limits :*

$$z(j\omega) \rightarrow R, \text{ n\u00e5r } \omega \rightarrow 0$$

$$z(j\omega) \rightarrow j\omega L, \text{ n\u00e5r } \omega \rightarrow \infty$$

## Resonance when terms cancel

$$sL = -\frac{R}{1 + sRC}$$


$$LRCs^2 + Ls + R = 0$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$s = -\frac{1}{2RC} \pm j\sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$$


# High frequency capacitor

- Equivalent circuit

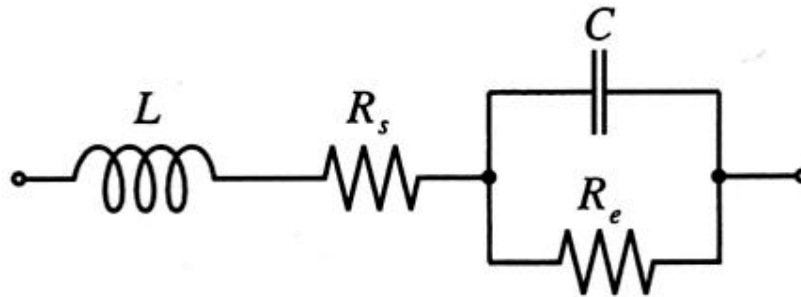

**Figure 1-11** Electric equivalent circuit for a high-frequency capacitor.

# Impedance versus frequency

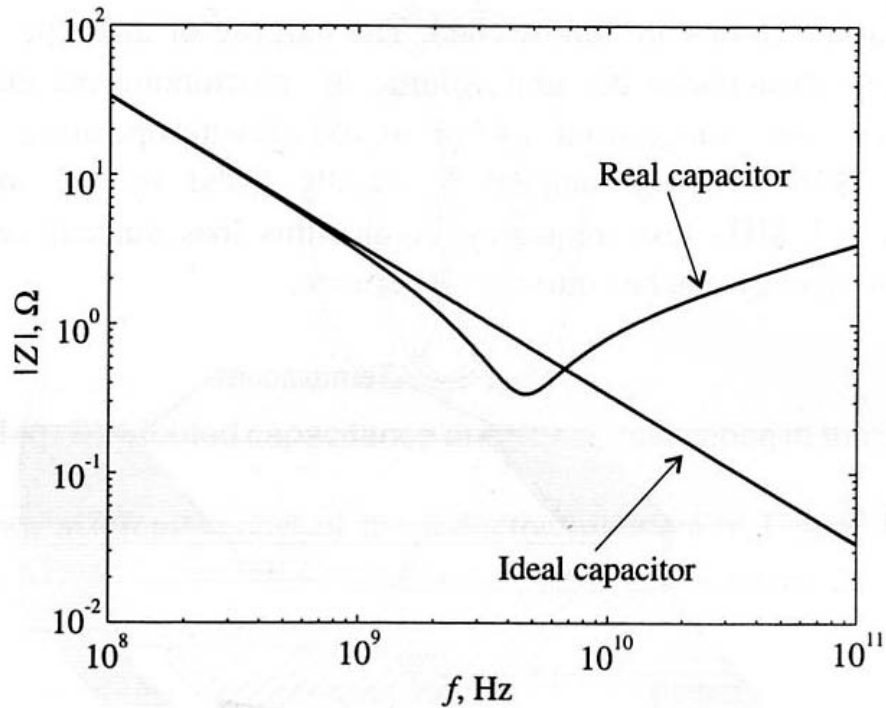


**Figure 1-12** Absolute value of the capacitor impedance as a function of frequency.




# High frequency inductor

- Equivalent circuit

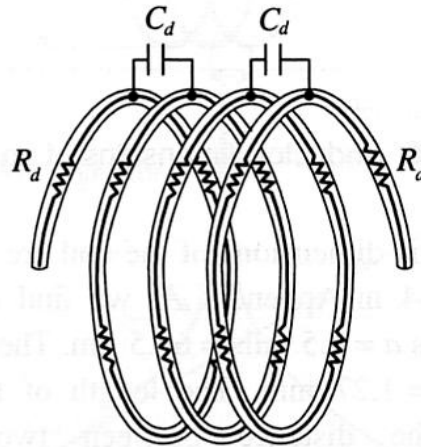


**Figure 1-14** Distributed capacitance and series resistance in the inductor coil.

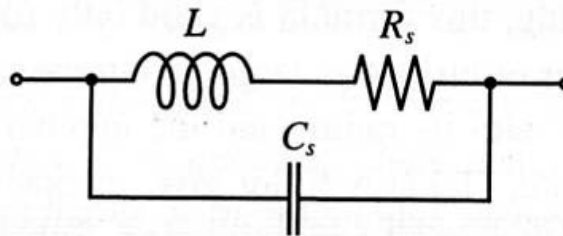

**Figure 1-15** Equivalent circuit of the high-frequency inductor.


# Impedance versus frequency

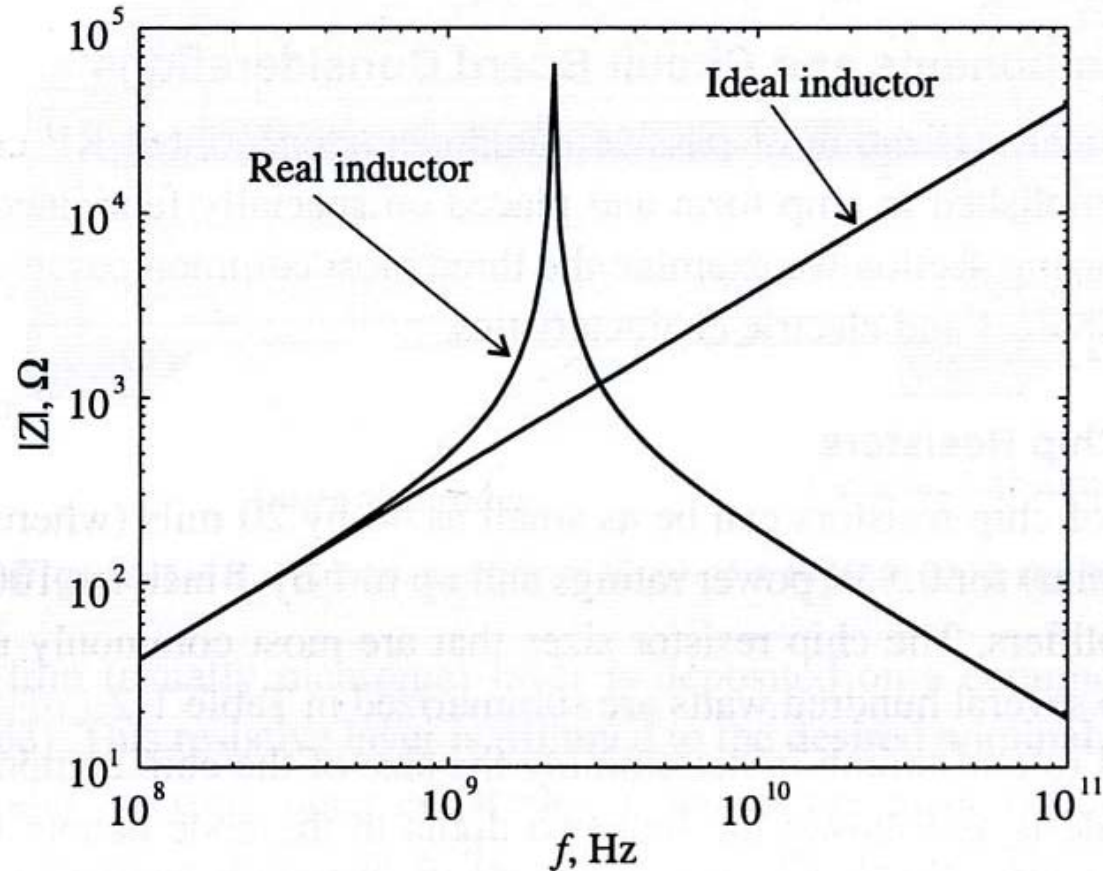

**Figure 1-17** Frequency response of the impedance of an RFC.

# Transmission line theory


- Frequency increases  $\rightarrow$  wavelength decreases ( $\lambda$ )
- When  $\lambda$  is comparable with component dimensions, there will be a **voltage drop over the component!!**
  - $\rightarrow$  Current and voltage are not constant
- Voltage and current are **waves** that propagate along conductors and components
  - Position dependent value  $\rightarrow$
  - Signal should propagate along **transmission lines**
  - **Reflections, characteristic impedances** must be controlled

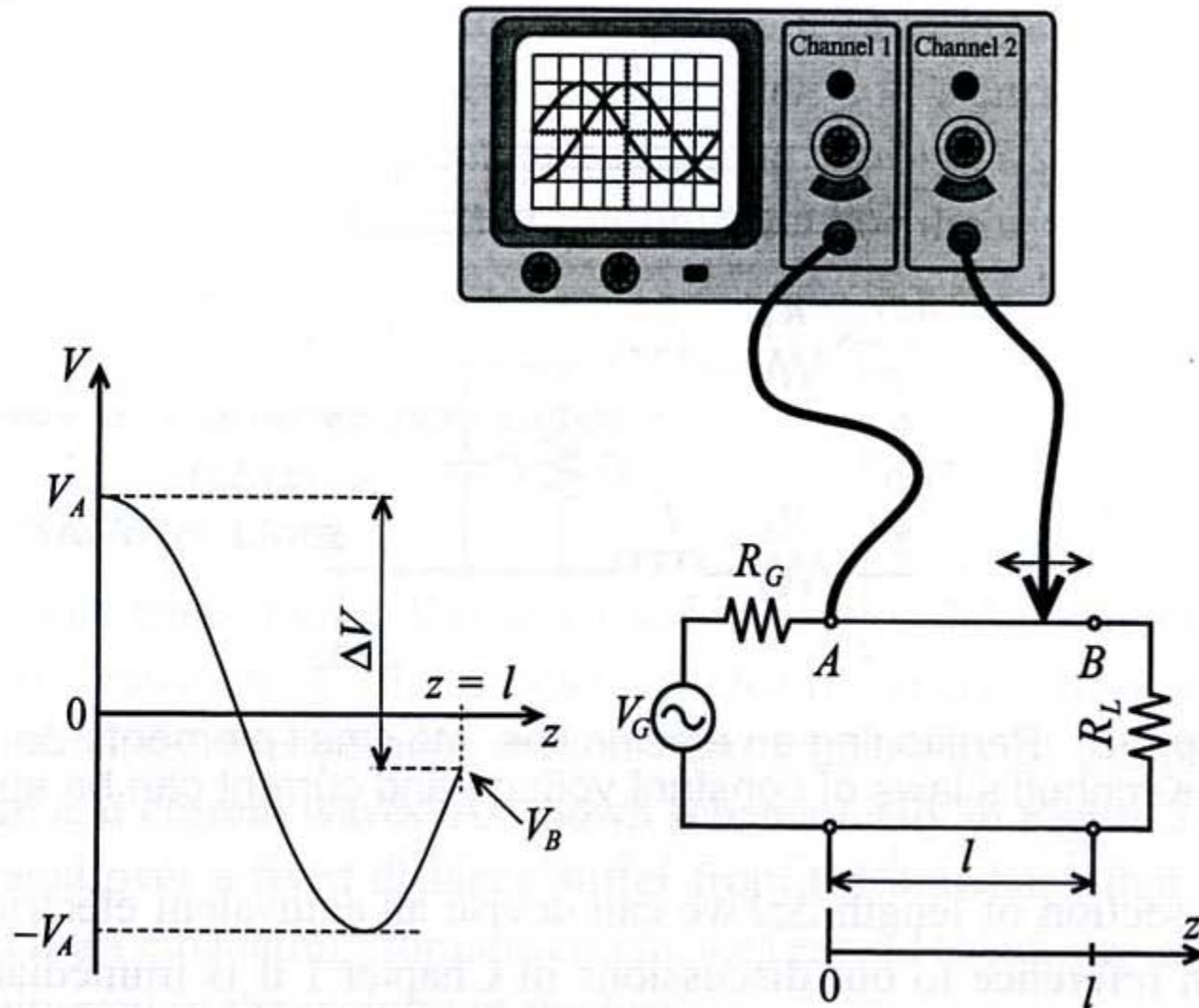

**Figure 2-2** Amplitude measurements of 10 GHz voltage signal at the beginning (location  $A$ ) and somewhere in between a wire connecting load to source.


# Transmission line

- A conductor has to be modeled as a transmission line

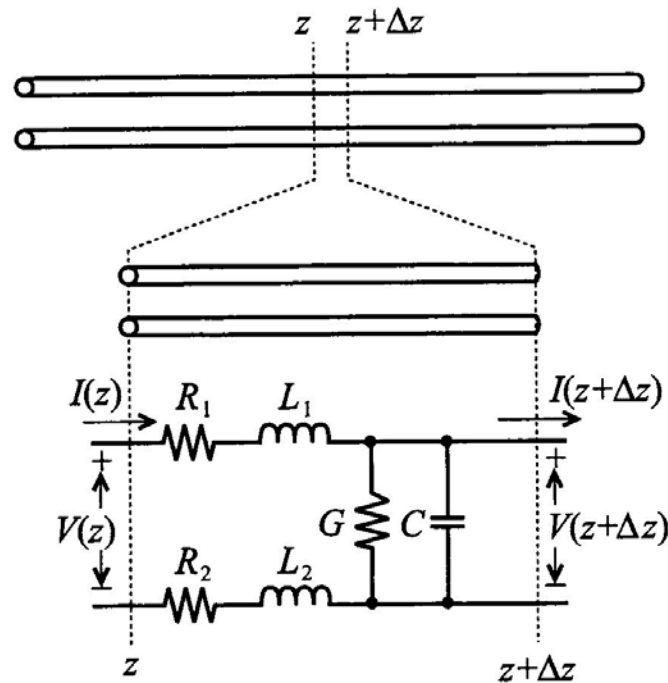

**Figure 2-3** Partitioning an electric line into small elements  $\Delta z$  over which Kirchhoff's laws of constant voltage and current can be applied.


The line is divided into infinitesimal sub-units

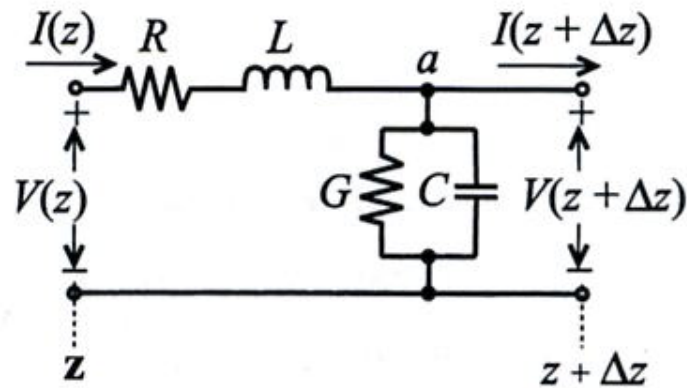

**Figure 2-17** Segment of a transmission line with voltage loop and current node.
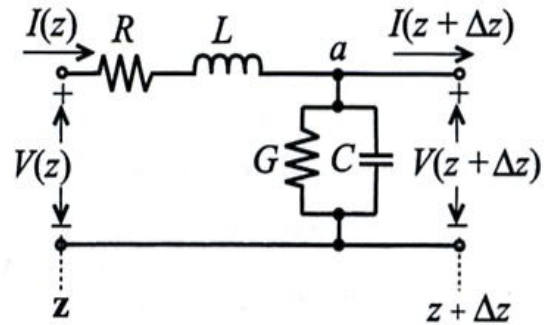
# Use Kirchhoff's laws

- Will give 2 coupled 1.order diff-equations



$$(R + j\omega L)I(z)\Delta z + V(z + \Delta z) = V(z) \quad (2.26)$$

$$\lim_{\Delta z \rightarrow 0} \left( -\frac{V(z + \Delta z) - V(z)}{\Delta z} \right) = -\frac{dV(z)}{dz} = (R + j\omega L)I(z) \quad (2.27)$$

$$\boxed{-\frac{dV(z)}{dz} = (R + j\omega L)I(z)} \quad (2.28)$$

$$I(z) - V(z + \Delta z)(G + j\omega C)\Delta z = I(z + \Delta z) \quad (2.29)$$

$$\lim_{\Delta z \rightarrow 0} \frac{I(z + \Delta z) - I(z)}{\Delta z} = \frac{dI(z)}{dz} = -(G + j\omega C)V(z) \quad (2.30)$$

$$\frac{d^2 V(z)}{dz^2} - k^2 V(z) = 0 \quad (2.31)$$

$$k = k_r + jk_i = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (2.32)$$

$$\frac{d^2 I(z)}{dz^2} - k^2 I(z) = 0 \quad (2.33)$$



# Solution: 2 waves

- The solution is waves in a **positive** and **negative** direction

$$V(z) = V^+ e^{-kz} + V^- e^{+kz} \quad (2.34)$$

$$I(z) = I^+ e^{-kz} + I^- e^{+kz} \quad (2.35)$$


$$I(z) = \frac{k}{(R + j\omega L)} (V^+ e^{-kz} - V^- e^{+kz}) \quad (2.36) \quad (\text{Jmfr.2.27})$$

**Characteristic line-impedance:**  $Z_0 = \frac{V^+}{I^+} = -\frac{V^-}{I^-}$

$$Z_0 = \frac{(R + j\omega L)}{k} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \quad (2.37)$$

# Impedance for **lossless** transmission line


$$Z_0 = \sqrt{L/C}$$

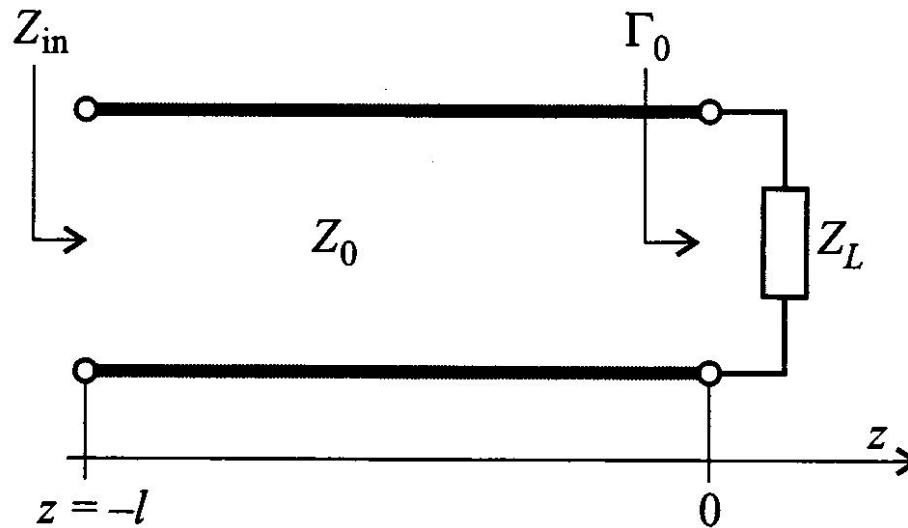

**Figure 2-23** Terminated transmission line at location  $z = 0$ .

# Reflection

- How to avoid reflections and have good signal propagation?
- Definition of **reflection coefficient** →

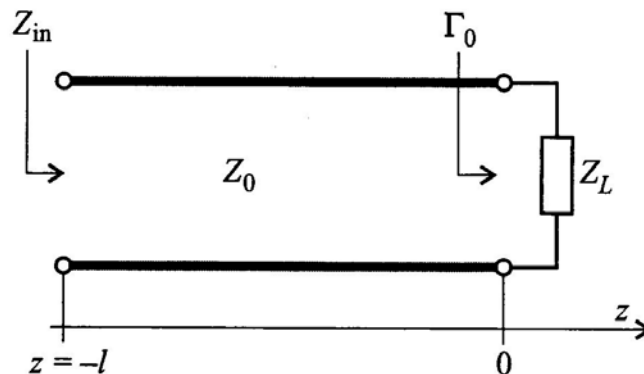

**Figure 2-23** Terminated transmission line at location  $z = 0$ .

# Reflection coefficient

$$\Gamma_0 = \frac{V^-}{V^+} \quad \leftarrow \text{definition of reflection coefficient for } z = 0$$

$$V(z) = V^+ (e^{-kz} + \Gamma_0 \cdot e^{+kz})$$

$$I(z) = \frac{V^+}{Z_0} (e^{-kz} - \Gamma_0 \cdot e^{+kz})$$

Impedance for  $z = 0$ :

$$Z(0) = \frac{V(0)}{I(0)} = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0} = Z_L \quad = \text{load impedance}$$

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

# Various terminations

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

## Open line

→ reflection with equal polarity

$$Z_L = \infty \Rightarrow \Gamma_0 = 1$$

## Short circuit

→ Reflection with inverse polarity

$$Z_L = 0 \Rightarrow \Gamma_0 = -1$$


No reflection when:

$$Z_0 = Z_L \Rightarrow \Gamma_0 = 0$$

→ **"MATCHING"**

# Standing waves

- Short circuiting gives **standing waves** ( $Z_L = 0$ )

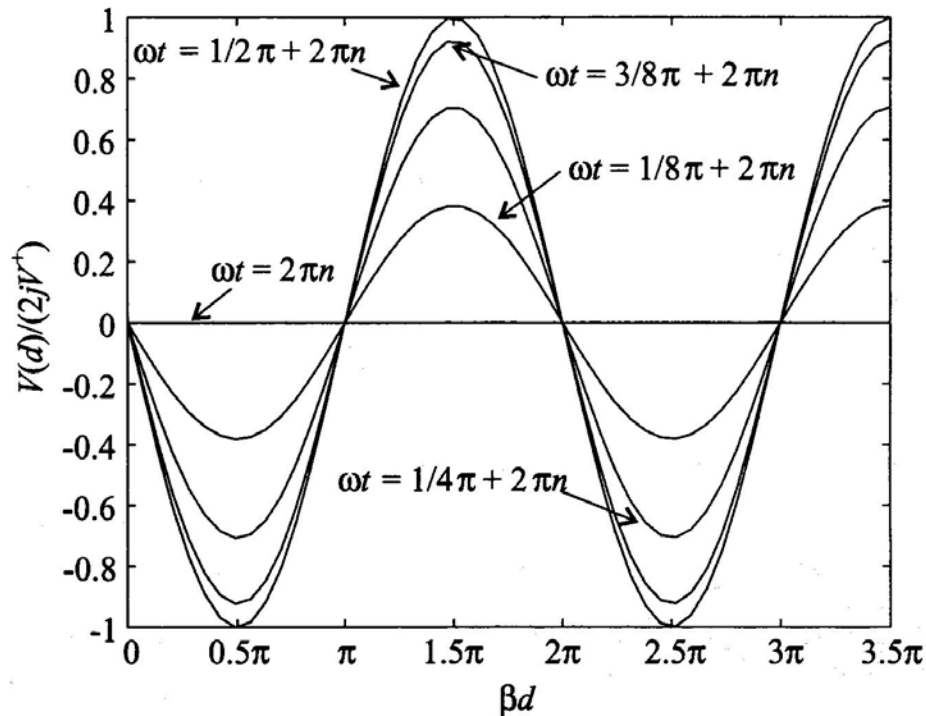

**Figure 2-25** Standing wave pattern for various instances of time.

# RF-circuits

- A high frequency circuit may be viewed as
  - a finite number of **transmission line sections** interconnected with **discrete active** and **passive** components

# Two-port network

- Circuits can be made up of simple parts:
  - **Two-ports**
- **Two-port-description** can be used to simplify analysis of complex networks
- Different types of two-ports
  - **Z, Y, h-matrix**
    - Each one is used in different situations and has **different properties when interconnected**
    - $Z \rightarrow$  series,  $Y \rightarrow$  parallel, hybrid
  - Figure  $\rightarrow$



# Two-ports at low frequencies

- **Open** and **shorts** are used for two-ports to determine **Z** (impedance) or **Y** (admittance) at low frequencies


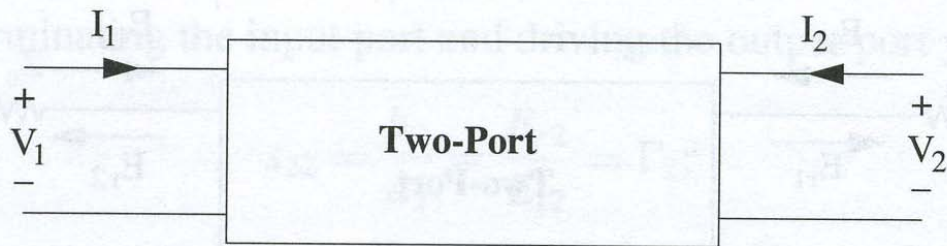


FIGURE 3.6. Port variable definitions

# Multiport-network

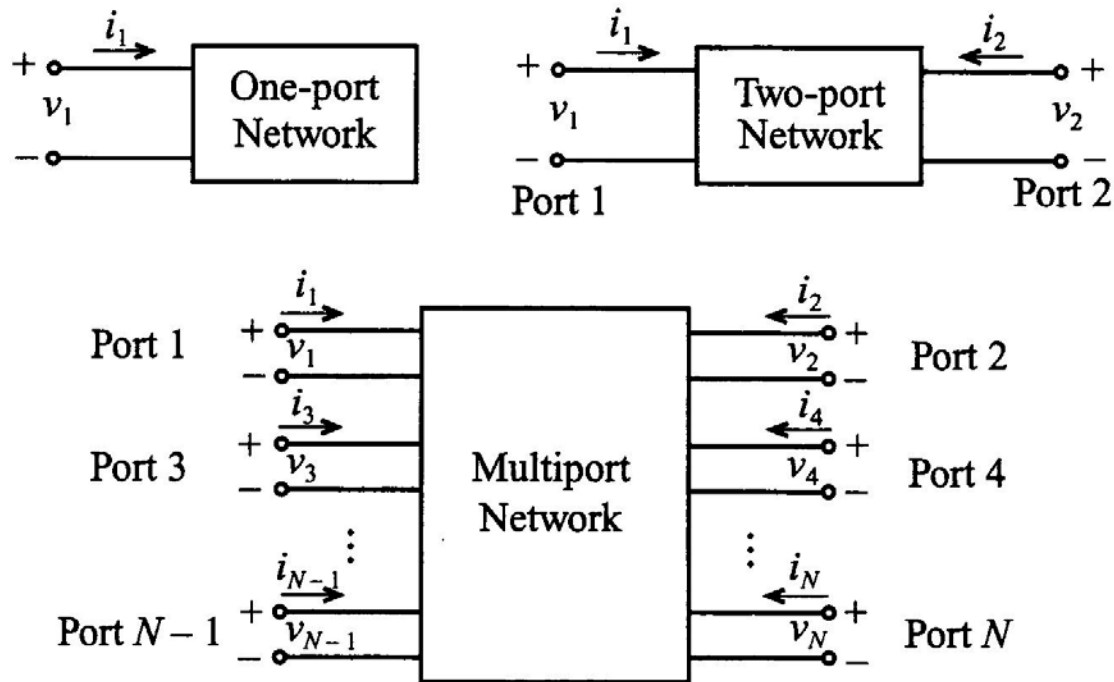

**Figure 4-1** Basic voltage and current definitions for single- and multiport network.


## Ex. Z-matrix

$$\begin{Bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{Bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & Z_{22} & \cdots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \cdots & Z_{NN} \end{bmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{Bmatrix} \quad (4.2)$$

$$\{\mathbf{V}\} = [\mathbf{Z}]\{\mathbf{I}\} \quad (4.3)$$

# ABCD network

$$\begin{Bmatrix} v_1 \\ i_1 \end{Bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{Bmatrix} v_2 \\ -i_2 \end{Bmatrix} \quad (4.10)$$

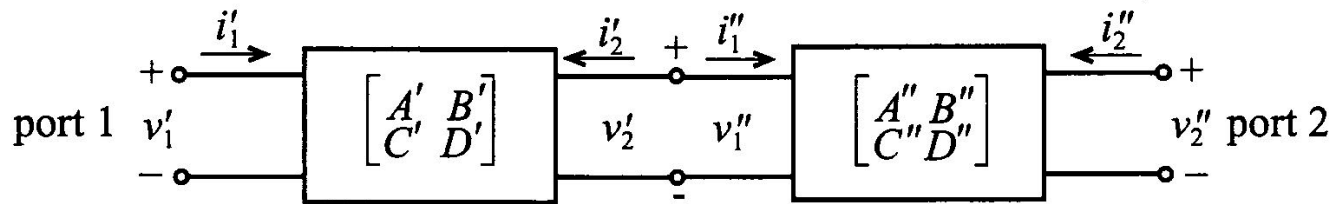







**Figure 4-9** Cascading two networks.

$$\begin{Bmatrix} v_1 \\ i_1 \end{Bmatrix} = \begin{Bmatrix} v_1' \\ i_1' \end{Bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{Bmatrix} v_2' \\ -i_2' \end{Bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{Bmatrix} v_1'' \\ i_1'' \end{Bmatrix} \quad (4.21)$$

$$= \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix} \begin{Bmatrix} v_2'' \\ -i_2'' \end{Bmatrix} \quad \text{Cascade coupling made easy}$$

# ABCD-parameters for "useful" 2-ports

Table 4-1 ABCD-Parameters of Some Useful Two-Port Circuits.
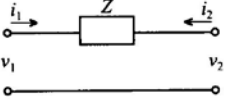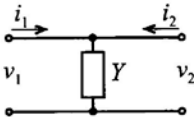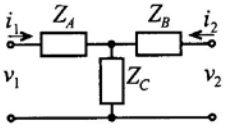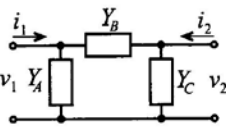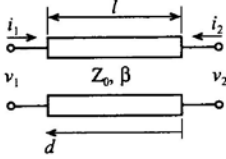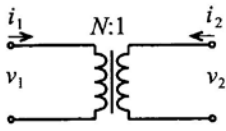
| Circuit   | ABCD-Parameters  |  |
|---|--|--|
|    | $A = 1$<br>$C = 0$   | $B = Z$<br>$D = 1$   |
|    | $A = 1$<br>$C = Y$   | $B = 0$<br>$D = 1$   |
|    | $A = 1 + \frac{Z_A}{Z_C}$<br>$C = \frac{1}{Z_C}$                   | $B = Z_A + Z_B + \frac{Z_A Z_B}{Z_C}$<br>$D = 1 + \frac{Z_B}{Z_C}$ |
|    | $A = 1 + \frac{Y_B}{Y_C}$<br>$C = Y_A + Y_B + \frac{Y_A Y_B}{Y_C}$ | $B = \frac{1}{Y_C}$<br>$D = 1 + \frac{Y_A}{Y_C}$                   |
|   | $A = \cos \beta l$<br>$C = \frac{j \sin \beta l}{Z_0}$             | $B = j Z_0 \sin \beta l$<br>$D = \cos \beta l$                     |
|  | $A = N$<br>$C = 0$   | $B = 0$<br>$D = \frac{1}{N}$                                       |

# Conversion between different 2-port types

**Table 4-2** Conversion between Different Network Representations

|        | [Z]  | [Y]  | [h]  | [ABCD]  |
|--------|--|--|--|---|
| [Z]    | $\begin{matrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{matrix}$   | $\begin{matrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{matrix}$ | $\begin{matrix} \frac{\Delta Z}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ \frac{Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{matrix}$  | $\begin{matrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta Z}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{matrix}$   |
| [Y]    | $\begin{matrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{matrix}$ | $\begin{matrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{matrix}$   | $\begin{matrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{matrix}$ | $\begin{matrix} \frac{Y_{22}}{Y_{21}} & -\frac{1}{Y_{21}} \\ -\frac{\Delta Y}{Y_{21}} & \frac{Y_{11}}{Y_{21}} \end{matrix}$ |
| [h]    | $\begin{matrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{matrix}$              | $\begin{matrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{matrix}$             | $\begin{matrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{matrix}$   | $\begin{matrix} \frac{\Delta h}{h_{21}} & -\frac{h_{11}}{h_{21}} \\ \frac{h_{22}}{h_{21}} & \frac{1}{h_{21}} \end{matrix}$  |
| [ABCD] | $\begin{matrix} \frac{A}{C} & \frac{\Delta ABCD}{C} \\ \frac{1}{C} & \frac{D}{C} \end{matrix}$   | $\begin{matrix} \frac{D}{B} & -\frac{\Delta ABCD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{matrix}$                                       | $\begin{matrix} \frac{B}{D} & \frac{\Delta ABCD}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{matrix}$                            | $\begin{matrix} A & B \\ C & D \end{matrix}$  |


determinant

# Two-ports at high frequencies

For high frequencies: Difficult to provide adequate shorts and opens due to **reflections**

Introduce: "scattering" parameters (**S-parameters**)

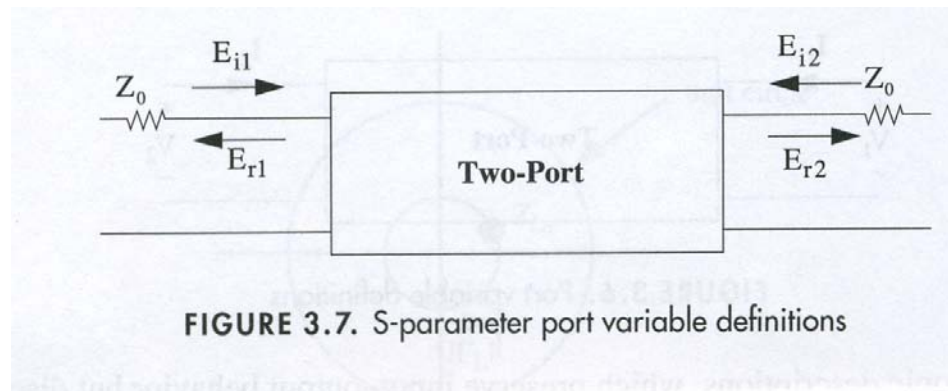Then: line terminated in its characteristic impedance  
→ gives no reflections!




# S-parameters

- 2-port used for definition of S-parameters
- **”Power waves”** defined as

$$a_n = \frac{1}{2\sqrt{Z_0}}(V_n + Z_0 I_n) \quad (4.36a)$$

$$b_n = \frac{1}{2\sqrt{Z_0}}(V_n - Z_0 I_n) \quad (4.36b)$$

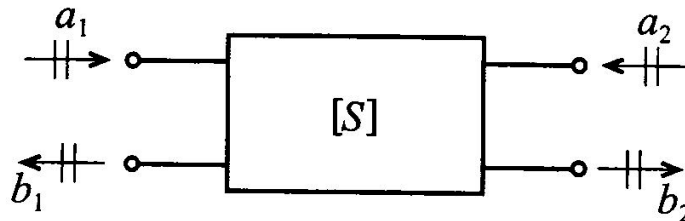

**Figure 4-14** Convention used to define S-parameters for a two-port network.



# Use incident and reflected voltage waves

- The solution is waves in a **positive** and **negative** direction

$$V(z) = V^+ e^{-kz} + V^- e^{+kz} \quad (2.34)$$

$$I(z) = I^+ e^{-kz} + I^- e^{+kz} \quad (2.35)$$

$$I(z) = \frac{k}{(R + j\omega L)} (V^+ e^{-kz} - V^- e^{+kz}) \quad (2.36) \quad (\text{Jmfr.2.27})$$

**Characteristic line-impedance:**  $Z_0 = \frac{V^+}{I^+} = -\frac{V^-}{I^-}$

$$Z_0 = \frac{(R + j\omega L)}{k} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} \quad (2.37)$$

$$\text{I. } V(z) = V^+ e^{-kz} + V^- e^{+kz}$$

$$\text{II. } I(z) = \frac{1}{Z_0} (V^+ e^{-kz} - V^- e^{+kz})$$

$$\text{I. } V^+ e^{-kz} = V(z) - V^- e^{+kz}$$

$$\text{II. } V^- e^{+kz} = V^+ e^{-kz} - Z_0 \cdot I(z)$$

$$\text{I. } V^+ e^{-kz} = \frac{1}{2} (V(z) + Z_0 I(z))$$

$$\text{II. } V^- e^{+kz} = \frac{1}{2} (V(z) - Z_0 I(z))$$

Define:

Incident power wave:  $a_n = \frac{1}{\sqrt{Z_0}} \cdot V_n^+ e^{-kz}$  Port  $n=1,2$

Reflected — " — " — :  $b_n = \frac{1}{\sqrt{Z_0}} \cdot V_n^- e^{+kz}$

$\frac{1}{\sqrt{Z_0}}$  = scaling factor

$$\text{I. } a_n = \frac{1}{2\sqrt{Z_0}} \cdot (V_n(z) + Z_0 I_n(z))$$

$$\text{II } b_n = \frac{1}{2\sqrt{Z_0}} \cdot (V_n(z) - Z_0 I_n(z))$$

$$\text{I+II. } a_n + b_n = \frac{1}{\sqrt{Z_0}} \cdot V_n(z)$$

$$a_n - b_n = \sqrt{Z_0} \cdot I_n(z)$$

Calculate the power of the wave:

$$P_n = \frac{1}{2} \operatorname{Re} \{ V_n \cdot I_n^* \}$$

$$\pm. \quad V_n = \sqrt{Z_0} (a_n + b_n)$$

$$\mp. \quad I_n = \frac{1}{\sqrt{Z_0}} (a_n - b_n)$$

$$\begin{aligned} \text{I.} \quad V_n &= \sqrt{Z_0} [(a_{nR} + ja_{ni}) + (b_{nR} + jb_{ni})] \\ &= \sqrt{Z_0} [(a_{nR} + b_{nR}) + j(a_{ni} + b_{ni})] \end{aligned}$$

$$\text{II} \quad I_n = \frac{1}{\sqrt{Z_0}} [(a_{nR} - b_{nR}) + j(a_{ni} - b_{ni})]$$

$$I_n^* = \dots \div \dots$$

$$V_n \cdot I_n^* = (a_{nR} + b_{nR}) \cdot (a_{nR} - b_{nR}) + j(\ ) + j(\ ) \\ + (a_{ni} + b_{ni}) \cdot (a_{ni} - b_{ni})$$

$$P_n = \frac{1}{2} \operatorname{Re}(V_n \cdot I_n^*) = \frac{1}{2} \left[ (a_{nR}^2 - b_{nR}^2) + (a_{ni}^2 - b_{ni}^2) \right] \\ = \frac{1}{2} \left[ (a_{nR}^2 + a_{ni}^2) - (b_{nR}^2 + b_{ni}^2) \right]$$

$$P_n = \frac{1}{2} \left( |a_n|^2 - |b_n|^2 \right) \quad n=1,2 \text{ (ports)}$$

Power of incident wave  $\nearrow$

Power of reflected wave  $\nwarrow$

$\uparrow$  = square of magnitude

Normalizing by  $\sqrt{Z_0}$  : convenient!


# Definition of S-parameters, cont.

- The power is:


$$P_n = \frac{1}{2} \operatorname{Re}\{V_n I_n^*\} = \frac{1}{2} (|a_n|^2 - |b_n|^2)$$
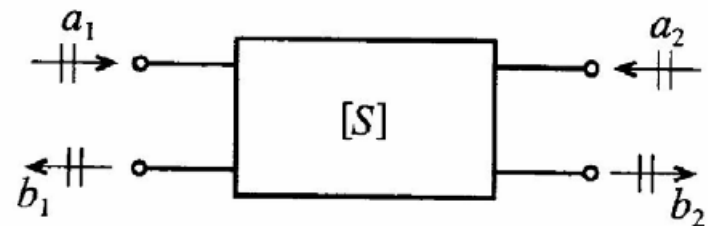
## S-parameters

$$\begin{Bmatrix} b_1 \\ b_2 \end{Bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{Bmatrix} a_1 \\ a_2 \end{Bmatrix}$$



# Interpretation of S-parameters

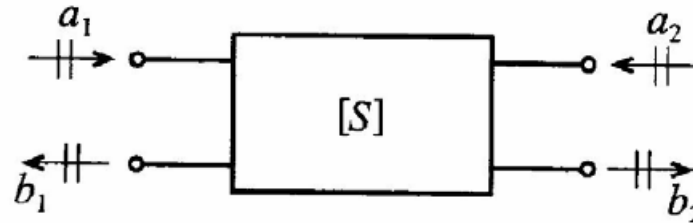

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \equiv \frac{\text{reflected power wave at port 1}}{\text{incident power wave at port 1}} \quad (4.42a)$$


$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \equiv \frac{\text{transmitted power wave at port 2}}{\text{incident power wave at port 1}} \quad (4.42b)$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \equiv \frac{\text{reflected power wave at port 2}}{\text{incident power wave at port 2}} \quad (4.42c)$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \equiv \frac{\text{transmitted power wave at port 1}}{\text{incident power wave at port 2}} \quad (4.42d)$$

# Measuring S-parameters

- S-parameters are measured when lines are terminated with their **characteristic impedances**

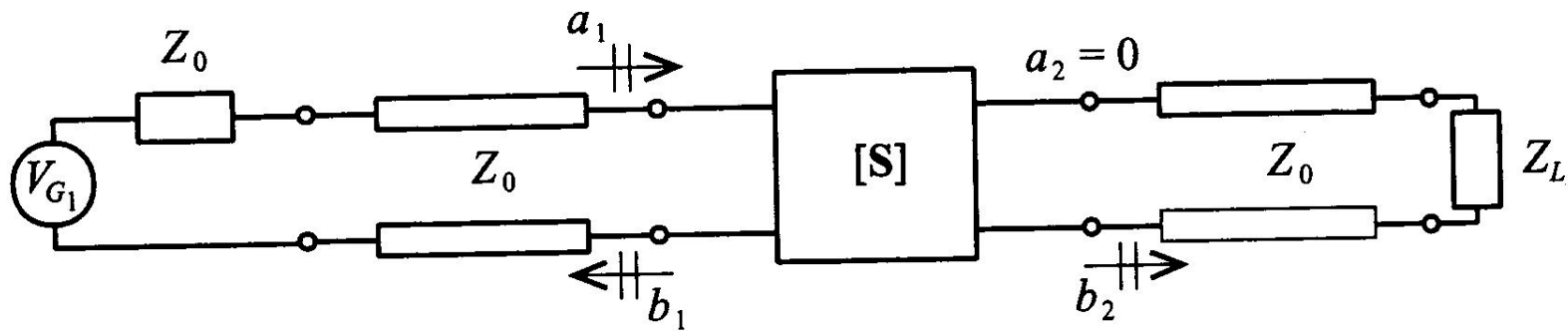

**Figure 4-15** Measurement of  $S_{11}$  and  $S_{21}$  by matching the line impedance  $Z_0$  at port 2 through a corresponding load impedance  $Z_L = Z_0$ .



# Filters

- Different filter types

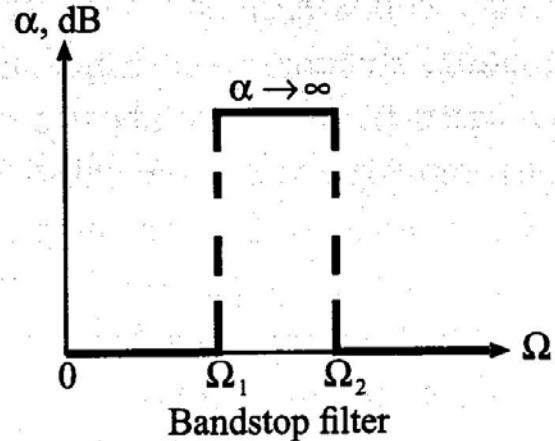
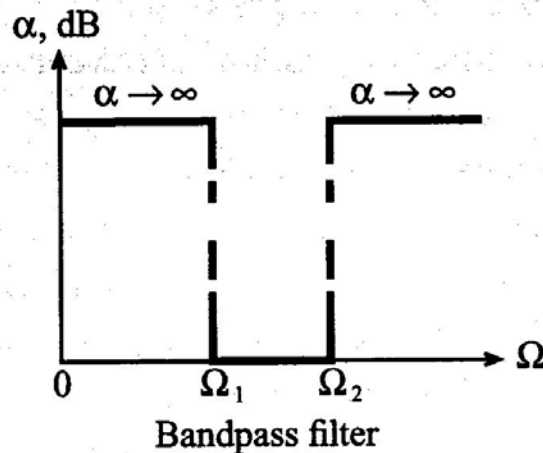
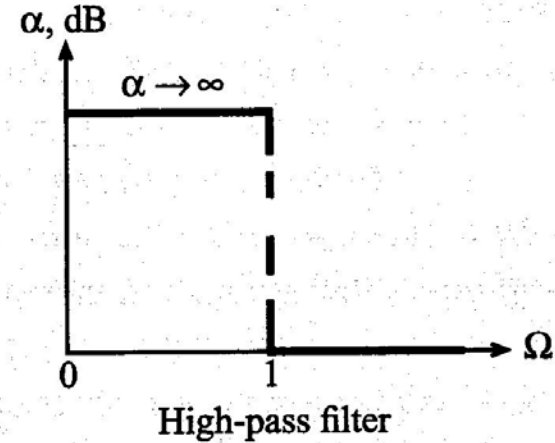
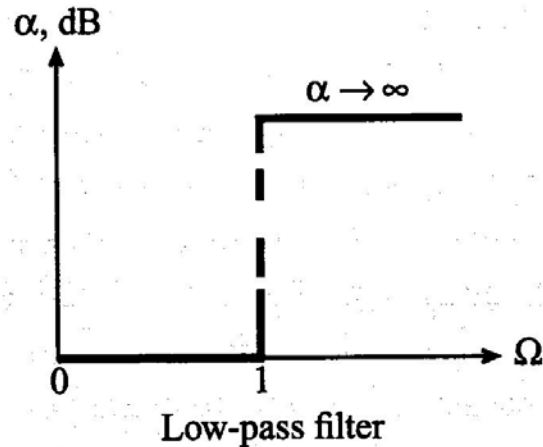


Figure 5-1 Four basic filter types.

# Ex. of 3 different filter types


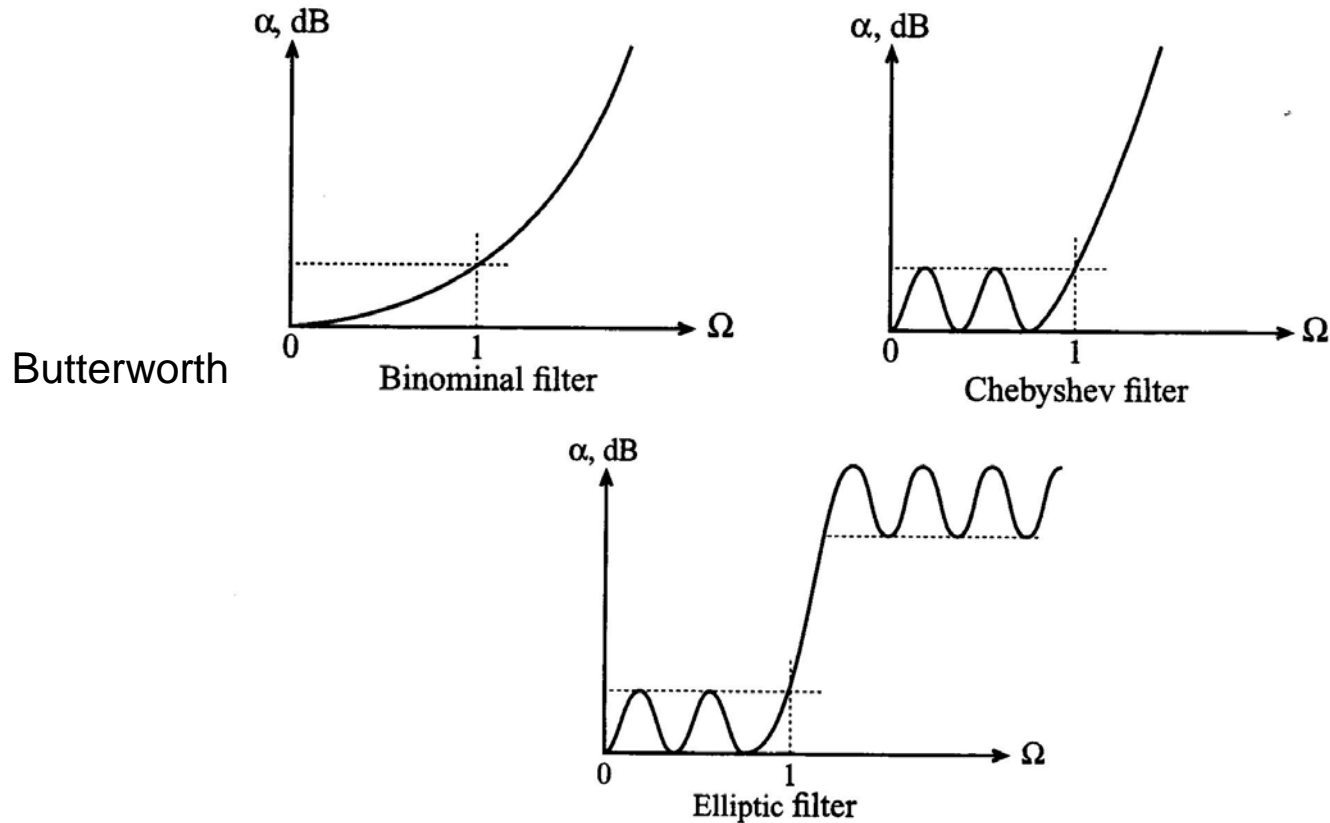


Figure 5-2 Actual attenuation profile for three types of low-pass filters.

# Filter parameters

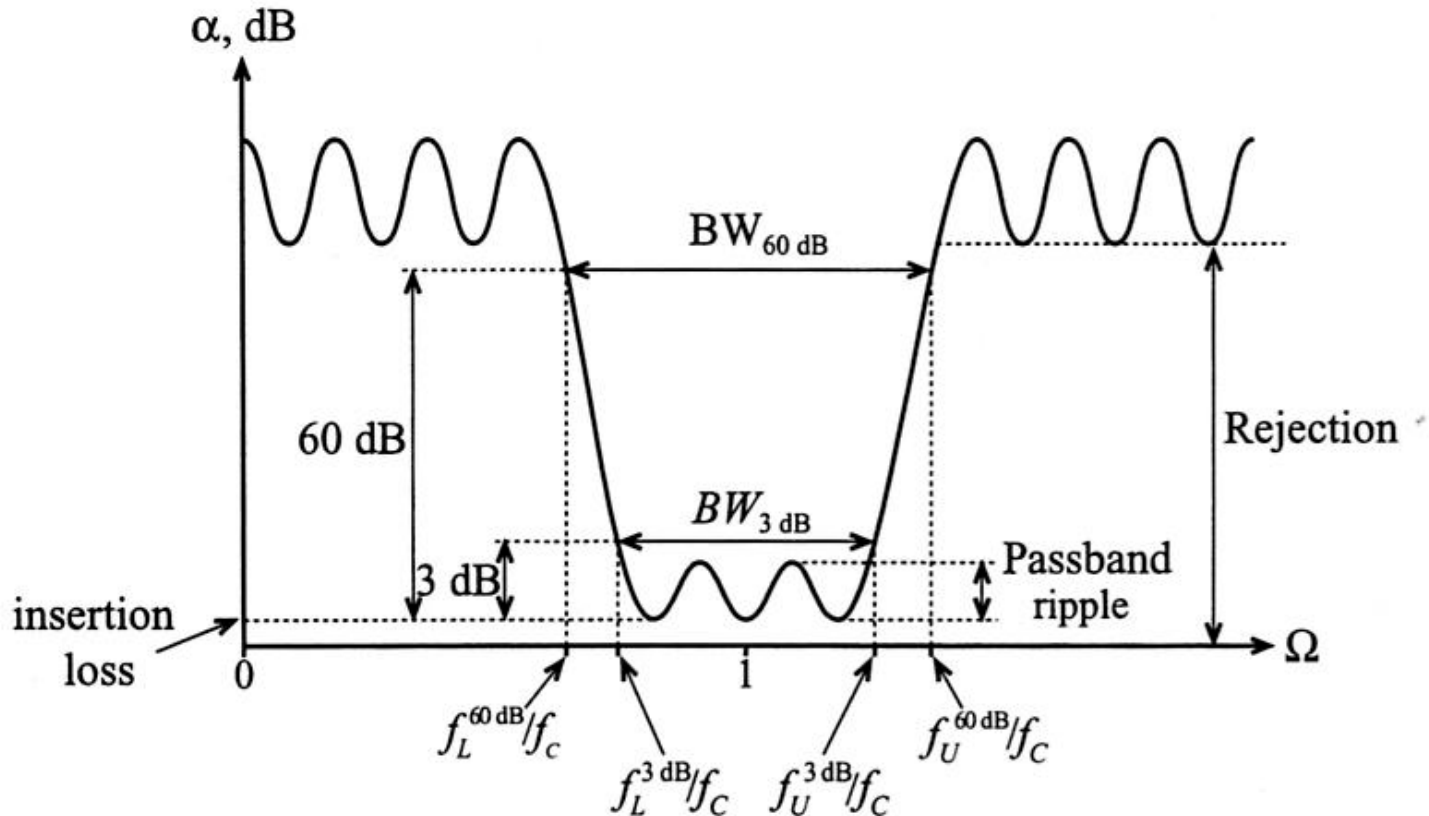

**Figure 5-3** Generic attenuation profile for a bandpass filter.

# Q-factor


- Definition of **Q-factor**

$$Q = \omega \frac{\text{average stored energy}}{\text{energy loss per cycle}} \Big|_{\omega = \omega_c} = \omega \frac{\text{average stored energy}}{\text{power loss}} \Big|_{\omega = \omega_c} = \omega \frac{W_{\text{stored}}}{P_{\text{loss}}} \Big|_{\omega = \omega_c} \quad (5.4)$$

- Different definitions of the Q-factor exist
  - The definitions are equivalent

$$Q_{LD} = \frac{f_c}{f_U^{3\text{dB}} - f_L^{3\text{dB}}} \equiv \frac{f_c}{BW^{3\text{dB}}}$$

# Unloaded – loaded Q

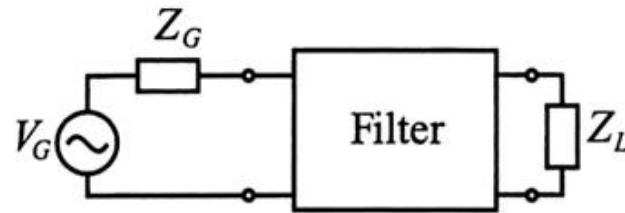

**Figure 5-4** Filter as a two-port network connected to an RF source and load.

$$\frac{1}{Q_{LD}} = \frac{1}{\omega} \left( \frac{\text{power loss in filter}}{\text{average stored energy}} \right) \Bigg|_{\omega = \omega_r} + \frac{1}{\omega} \left( \frac{\text{power loss in load}}{\text{average stored energy}} \right) \Bigg|_{\omega = \omega_r} \quad (5.5)$$

$$\frac{1}{Q_{LD}} = \frac{1}{Q_F} + \frac{1}{Q_E}$$

# Q-factor is important for frequency stability

